
ECE 481: Power Electronics

Prof. Daniel Costinett

Department of Electrical Engineering and Computer Science
University of Tennessee Knoxville
Fall 2013


ECE 481: Power Electronics

- Instructor: Prof. Daniel Costinett
 - Office: MK502
 - Telephone: (865) 974-3572
 - Email: dcostine@utk.edu
 - Please use **ECE481** in the subject line for all course-related e-mails.
 - Office Hours: T 12:30-2:00pm, F 10:00-11:30am
- TA: Zhuxian "Nicole" Xu
 - Email: z xu11@utk.edu
 - Office: MK517
 - Office Hours: MW 3:00-4:00pm

Course Materials

- Textbook:

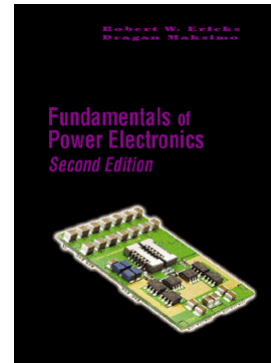- Erickson and Maksimovic, *Fundamentals of Power Electronics*, second edition, Kluwer Academic Publishers, ISBN 0-7923-7270-0
- Available through campus bookstore, online vendors, or UT libraries



- Course Website

- <http://web.eecs.utk.edu/courses/fall2013/ece481/>
- Includes lectures slides, handouts, supplemental notes, homework assignments, course announcements

Grading

- Homework

- Due at beginning of class on date listed on Lecture Schedule web page
- Homework counts for 40% of grade
- Collaboration is encouraged on all homework assignments


- Exams

- 2 Midterms: 25% of grade
- 1 Final: 35% of grade
- 1 week, take-home exams
- Absolutely *no collaboration* allowed on exams

Power Electronics Courses at UTK


Junior	Senior	Graduate	
ECE 325 Electric Energy System Components	ECE 481 Power Electronics	ECE 523 Power Electronics and Drives	ECE 623 Advanced Power Electronics and Drives
	ECE 482 Power Electronic Circuits	ECE 525 Alternative Energy Sources	ECE 625 Utility Applications of Power Electronics
			ECE 626 Solid State Power Semiconductors

1.1 Introduction to Power Processing

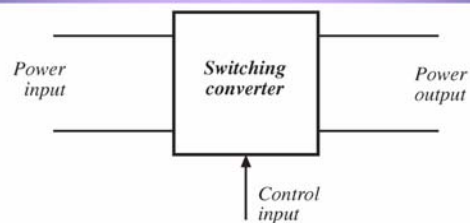

- Dc-dc conversion:* Change and control voltage magnitude
- Ac-dc rectification:* Possibly control dc voltage, ac current
- Dc-ac inversion:* Produce sinusoid of controllable magnitude and frequency
- Ac-ac cycloconversion:* Change and control voltage magnitude and frequency


Example Server Power Distribution

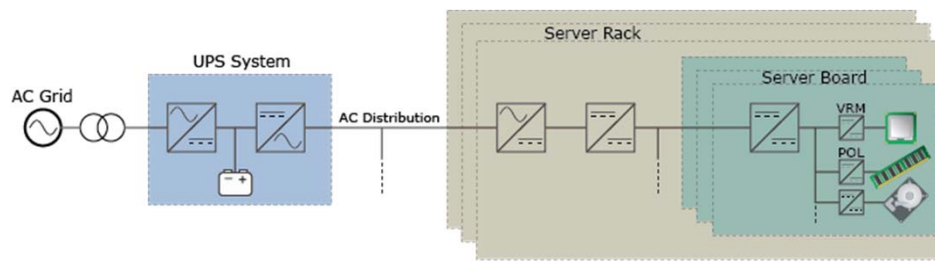


Example VRM Design




Variations in Load

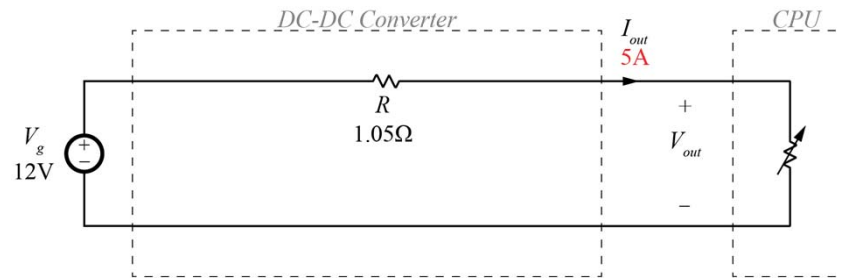

Control is invariably required

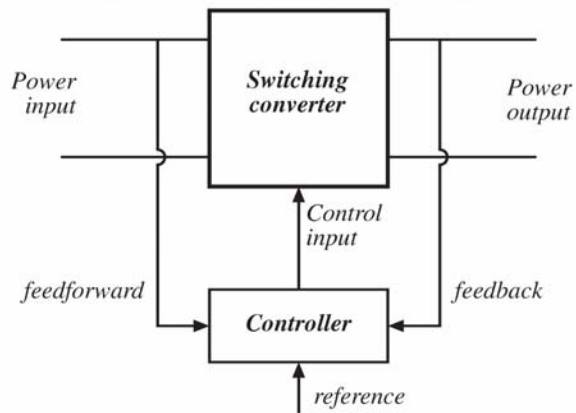

Linear Regulator

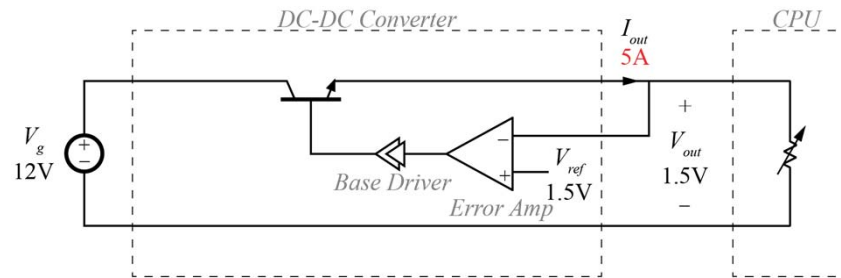


High efficiency is essential


$$\eta = \frac{P_{out}}{P_{in}}$$

$$P_{loss} = P_{in} - P_{out} = P_{out} \left(\frac{1}{\eta} - 1 \right)$$

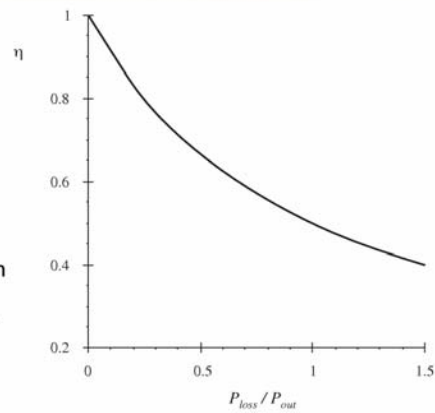
High efficiency leads to low
power loss within converter
Small size and reliable operation
is then feasible
Efficiency is a good measure of
converter performance



Example Server Power Distribution

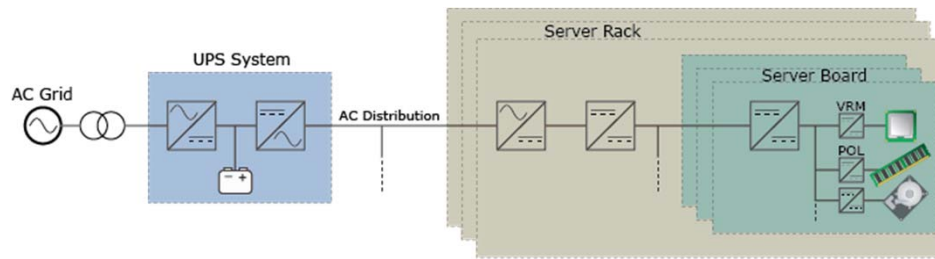


A high-efficiency converter

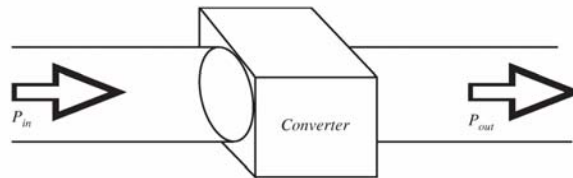

A goal of current converter technology is to construct converters of small size and weight, which process substantial power at high efficiency

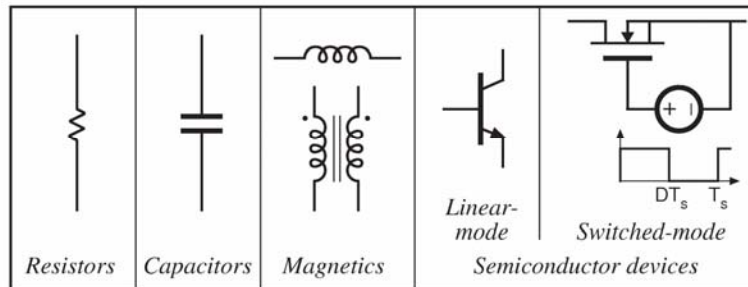Devices available to the circuit designer




Fundamentals of Power Electronics

7


Chapter 1: Introduction

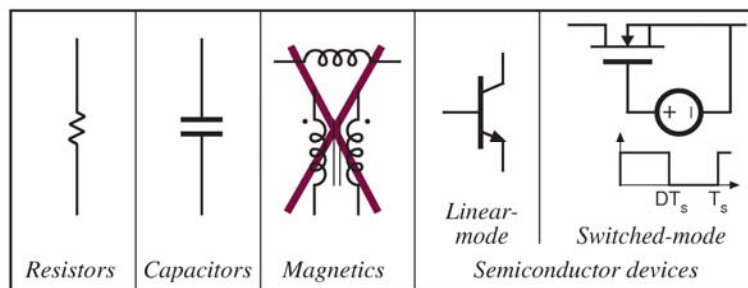Devices available to the circuit designer



Signal processing: avoid magnetics

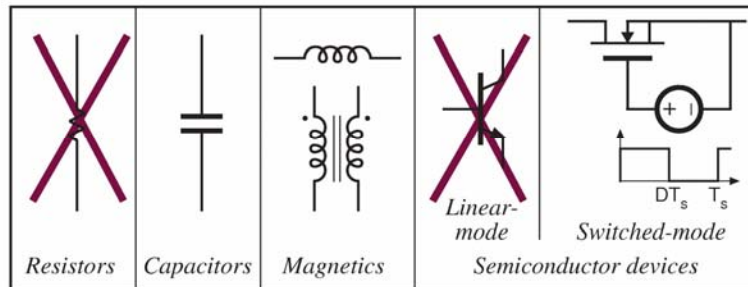Devices available to the circuit designer



Power processing: avoid lossy elements


Power loss in an ideal switch

Switch closed: $v(t) = 0$


Switch open: $i(t) = 0$

In either event: $p(t) = v(t) i(t) = 0$


Ideal switch consumes zero power

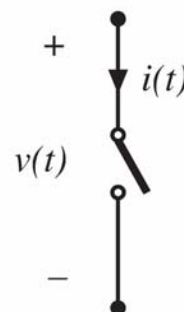

Use of a SPDT switch

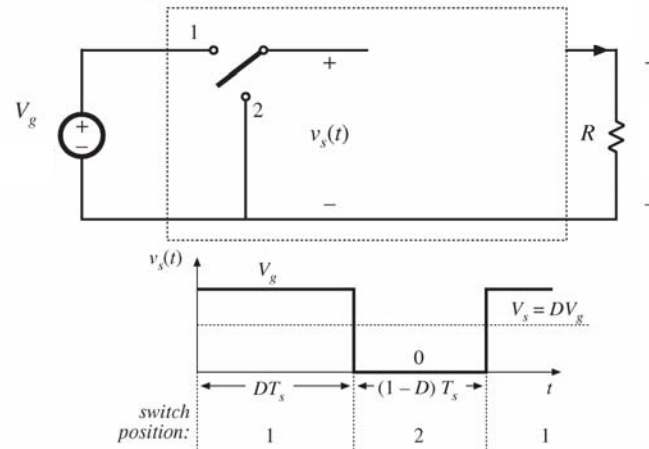

The switch changes the dc voltage level

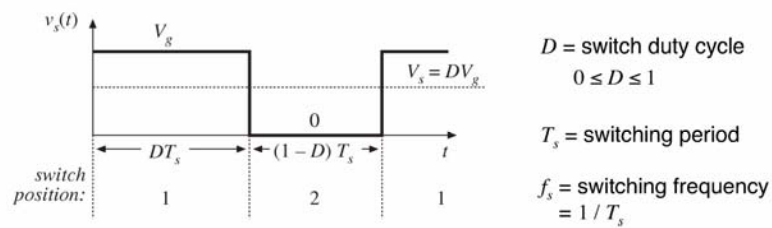


DC component of $v_s(t)$ = average value:

$$V_s = \frac{1}{T_s} \int_0^{T_s} v_s(t) dt = DV_g$$


Addition of low pass filter

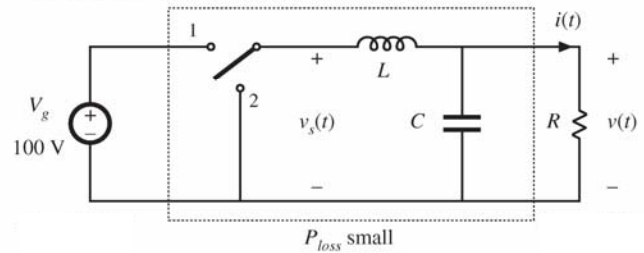Addition of (ideally lossless) L - C low-pass filter, for removal of switching harmonics:



- Choose filter cutoff frequency f_0 much smaller than switching frequency f_s
- This circuit is known as the “buck converter”

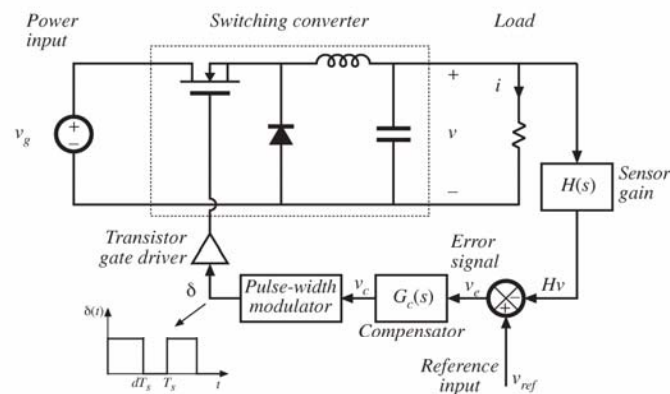Addition of control system for regulation of output voltage




1.2 Several applications of power electronics


Power levels encountered in high-efficiency converters

- less than 1 W in battery-operated portable equipment
- tens, hundreds, or thousands of watts in power supplies for computers or office equipment
- kW to MW in variable-speed motor drives
- 1000 MW in rectifiers and inverters for utility dc transmission lines


A laptop computer power supply system

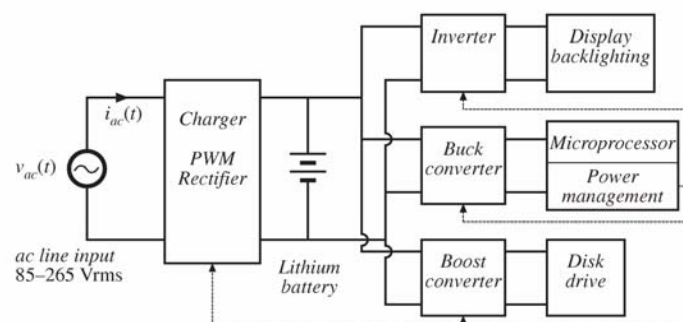

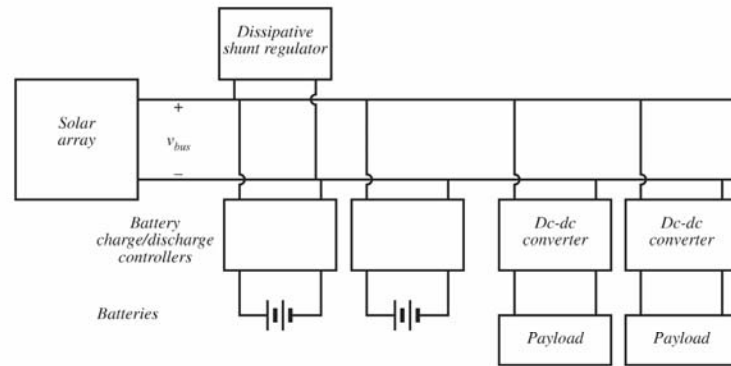
Power system of an earth-orbiting spacecraft



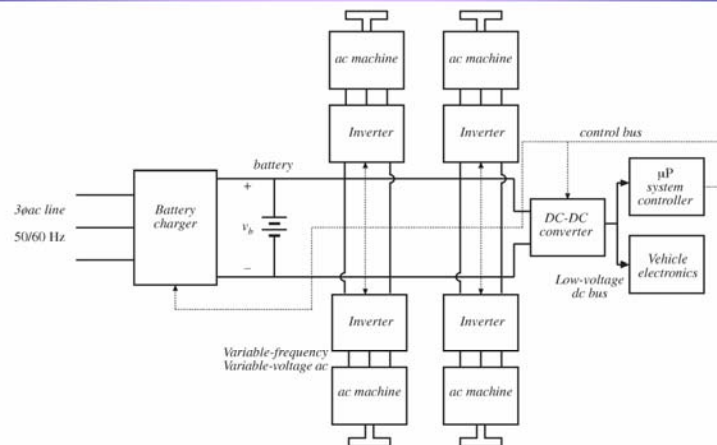
An electric vehicle power and drive system



Power management in mobile electronics

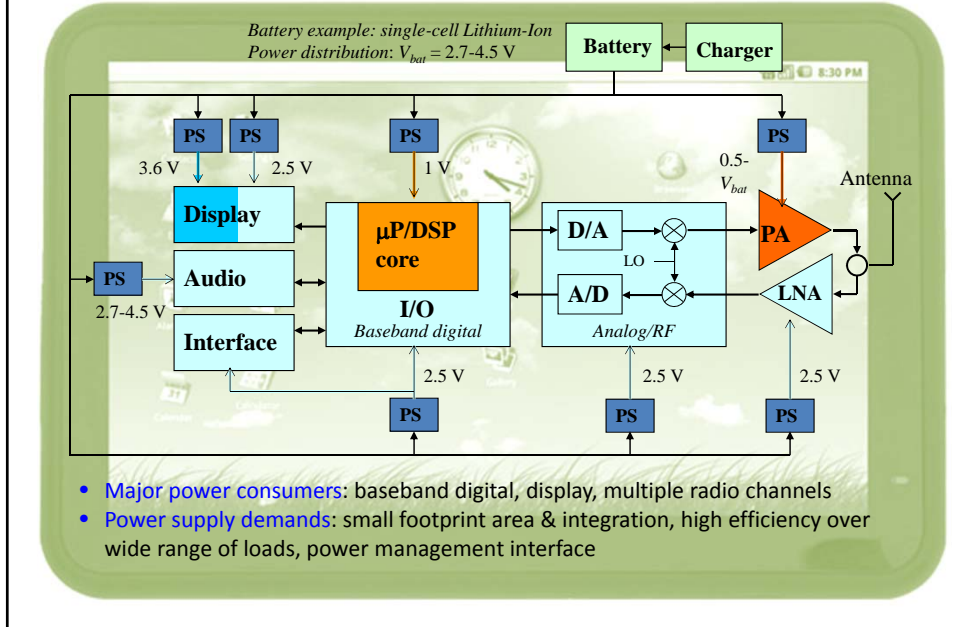

Future Applications: Hyperloop

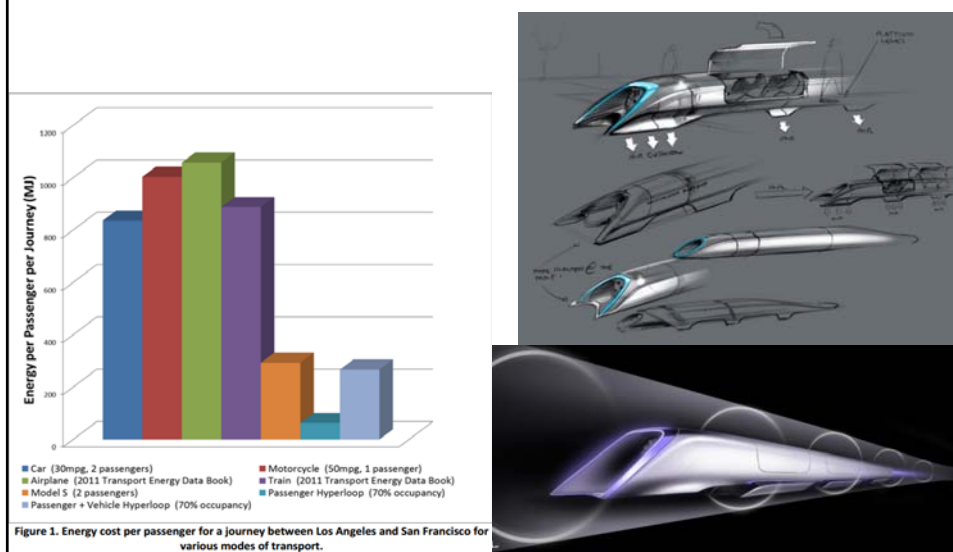

Proposed Power Conversion Architecture

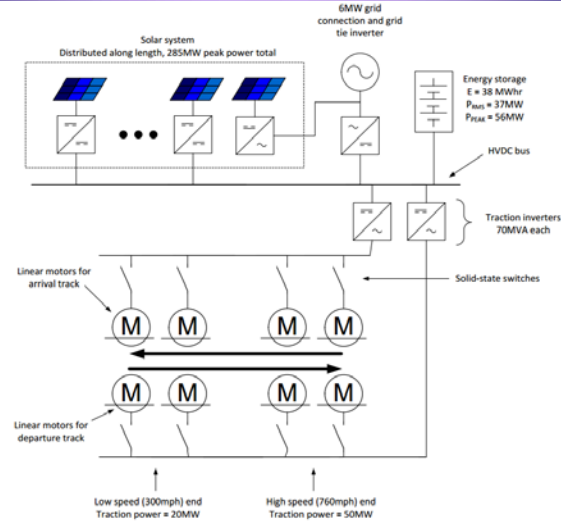


Figure 22. Linear accelerator concept for capsule acceleration and deceleration between 300 and 760 mph (480 and 1,220 kph).

1.3 Elements of power electronics

Power electronics incorporates concepts from the fields of


- analog circuits
- electronic devices
- control systems
- power systems
- magnetics
- electric machines
- numerical simulation

Part I. Converters in equilibrium

2. Principles of steady state converter analysis
3. Steady-state equivalent circuit modeling, losses, and efficiency
4. Switch realization
5. The discontinuous conduction mode
6. Converter circuits


Part I. Converters in equilibrium

Inductor waveforms

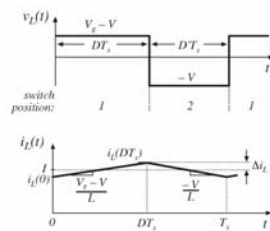


Discontinuous conduction mode
Transformer isolation

Averaged equivalent circuit

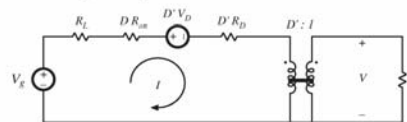


Predicted efficiency

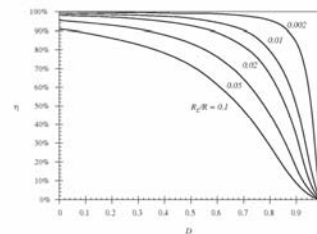


Switch realization: semiconductor devices

The IGBT

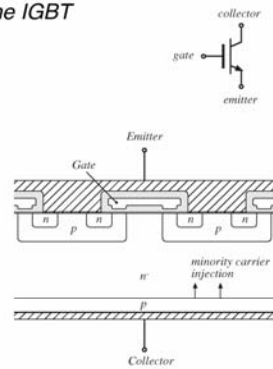

Fundamentals of Power Electronics

Switching loss

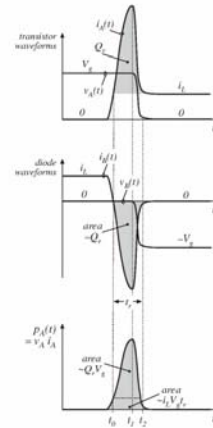

Chapter 1: Introduction

26

Part II. Converter dynamics and control

7. Ac modeling
8. Converter transfer functions
9. Controller design
10. Input filter design
11. Ac and dc equivalent circuit modeling of the discontinuous conduction mode
12. Current-programmed control


Fundamentals of Power Electronics

29


Chapter 1: Introduction

Part II. Converter dynamics and control


Closed-loop converter system

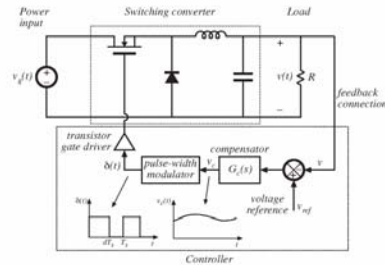

Averaging the waveforms

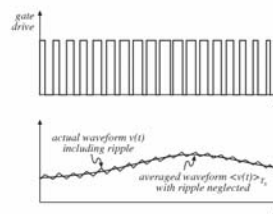

Small-signal averaged equivalent circuit

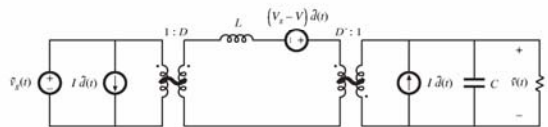


Part III. Magnetics


13. Basic magnetics theory
14. Inductor design
15. Transformer design

Part III. Magnetics

transformer design

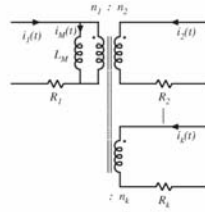

the proximity effect

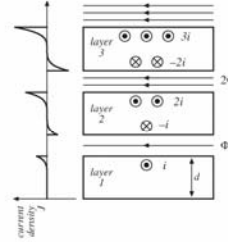

transformer size vs. switching frequency

