

Lecture 20: Feedback Loop Compensation

ECE 481: Power Electronics

Prof. Daniel Costinett


Department of Electrical Engineering and Computer Science

University of Tennessee Knoxville


Fall 2013

35-35-30

9.5.4. Design example


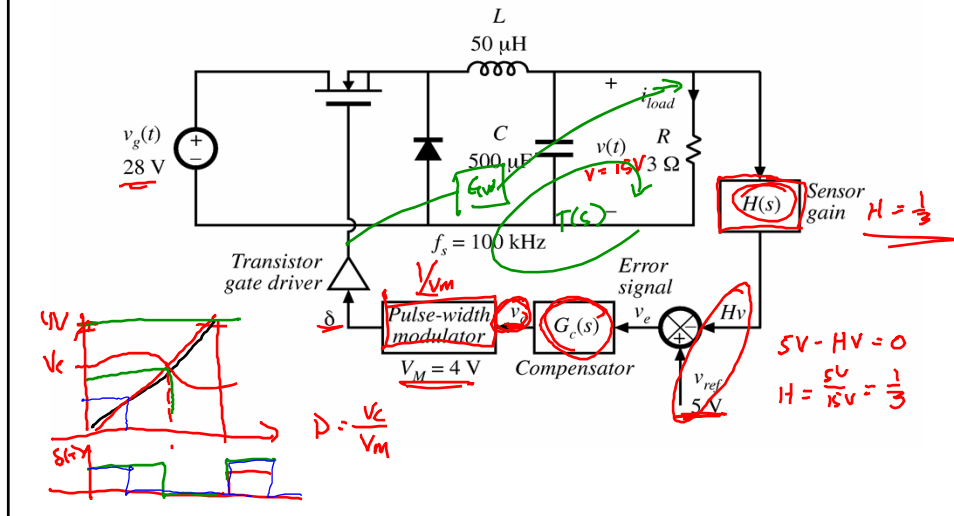


Quiescent operating point @ DC

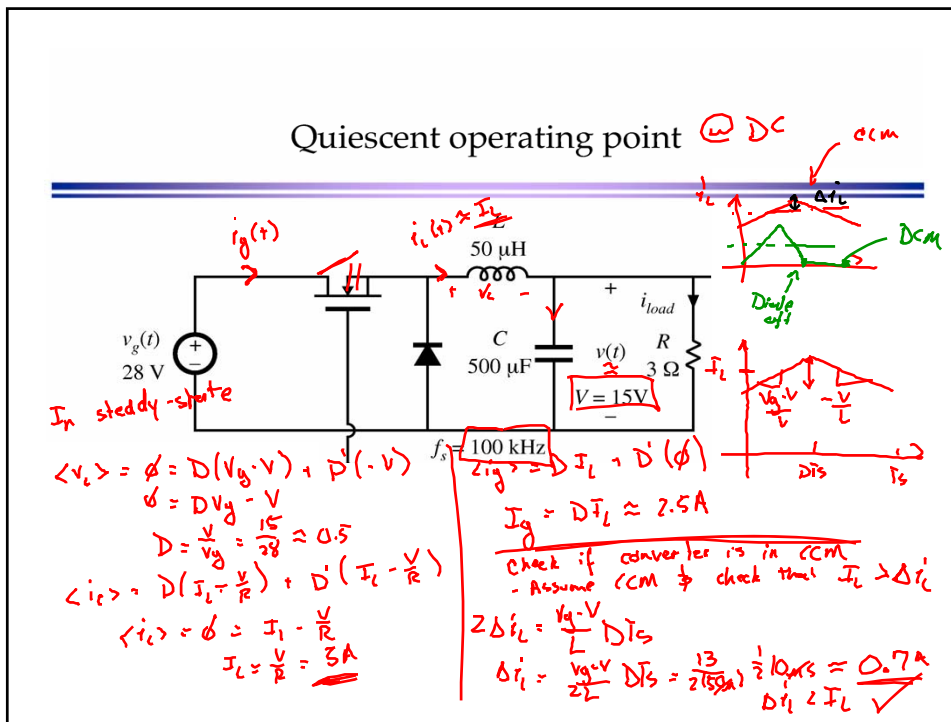


Quiescent operating point


Input voltage	$V_g = 28V$
Output	$V = 15V, I_{load} = 5A, R = 3\Omega$
Quiescent duty cycle	$D = 15/28 = 0.536$
Reference voltage	$V_{ref} = 5V$
Quiescent value of control voltage	$V_c = DV_M = 2.14V$
Gain $H(s)$	$H = V_{ref}/V = 5/15 = 1/3$

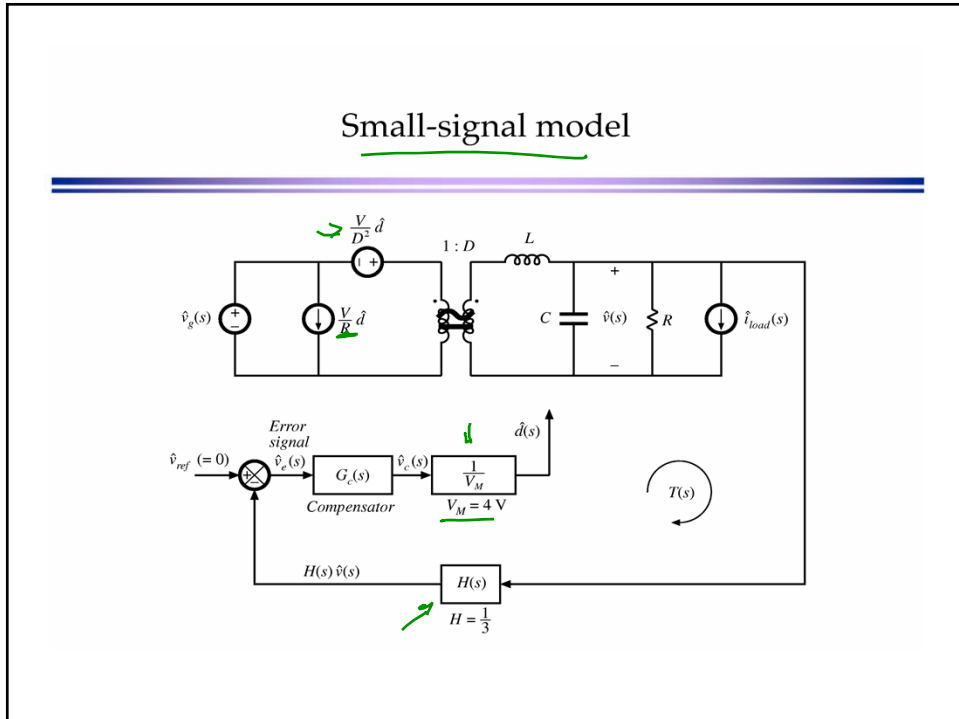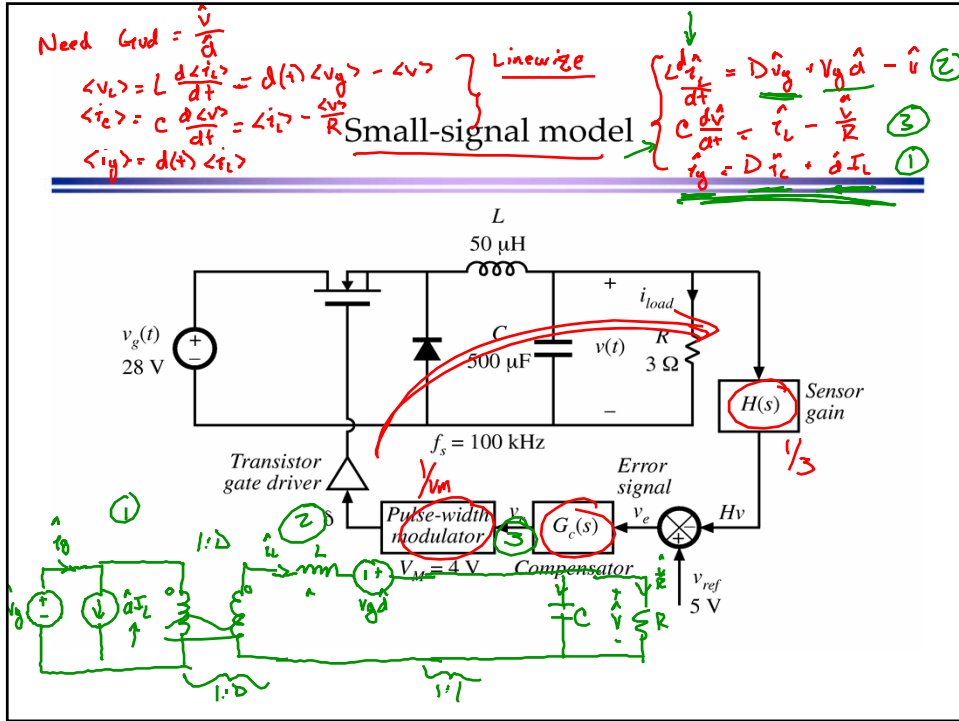


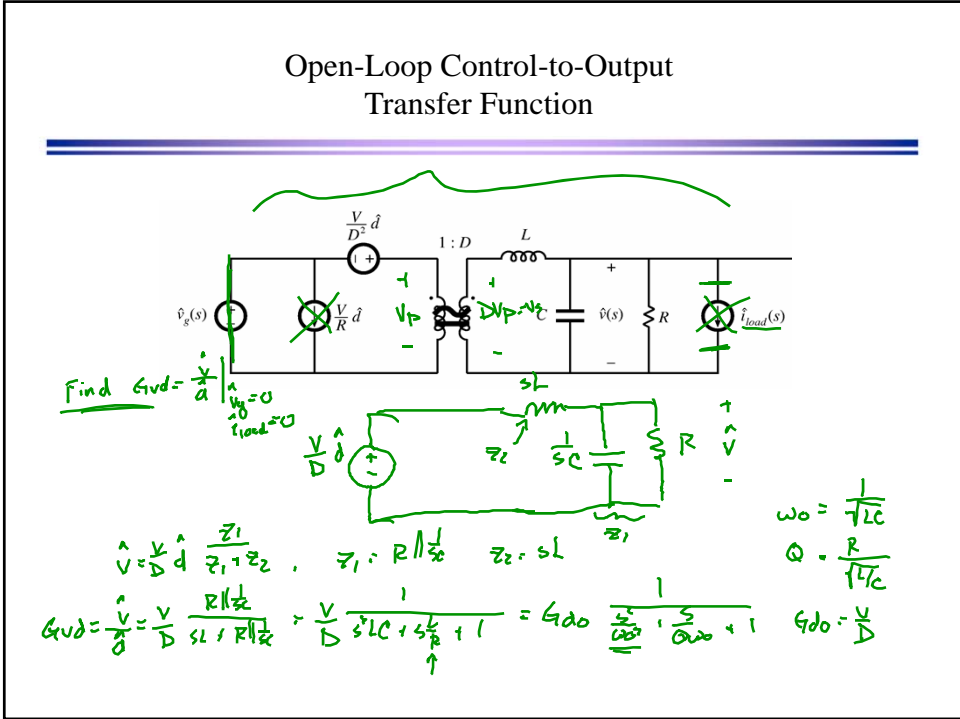Open-Loop Control-to-Output Transfer Function



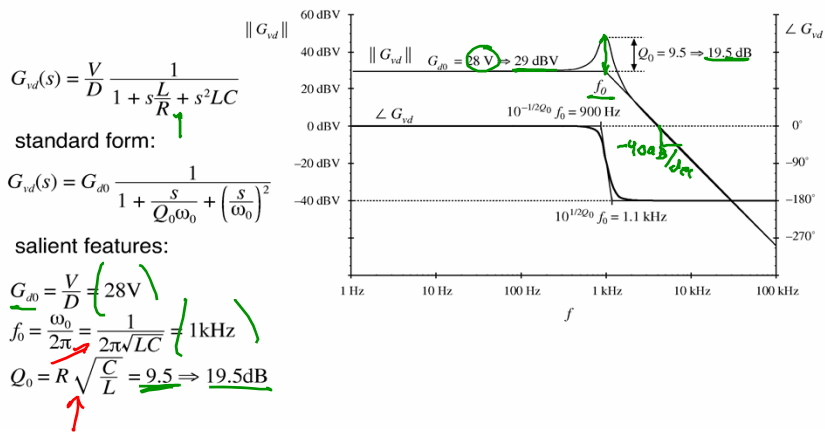Open-loop control-to-output transfer function $G_{vd}(s)$



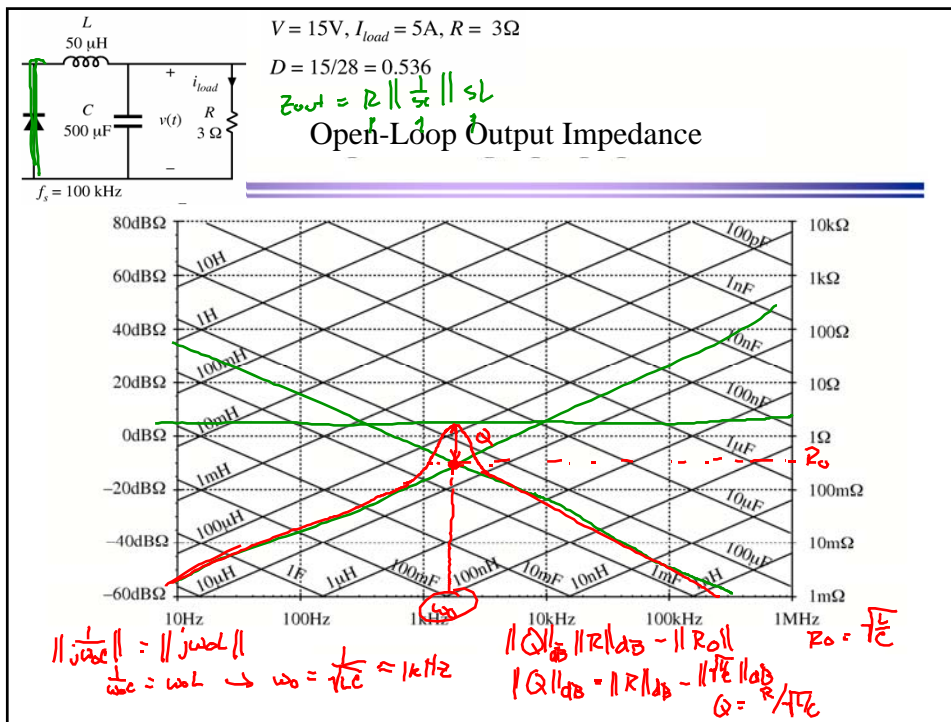

Open-loop line-to-output transfer function and output impedance

$G_{vg}(s) = D \frac{1}{1 + s\frac{L}{R} + s^2LC}$


— same poles as control-to-output transfer function
standard form:

$$G_{vg}(s) = G_{s0} \frac{1}{1 + \frac{s}{Q_0\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

Output impedance:


$$Z_{out}(s) = R \parallel \frac{1}{sC} \parallel sL = \frac{sL}{1 + s\frac{L}{R} + s^2LC}$$

System block diagram

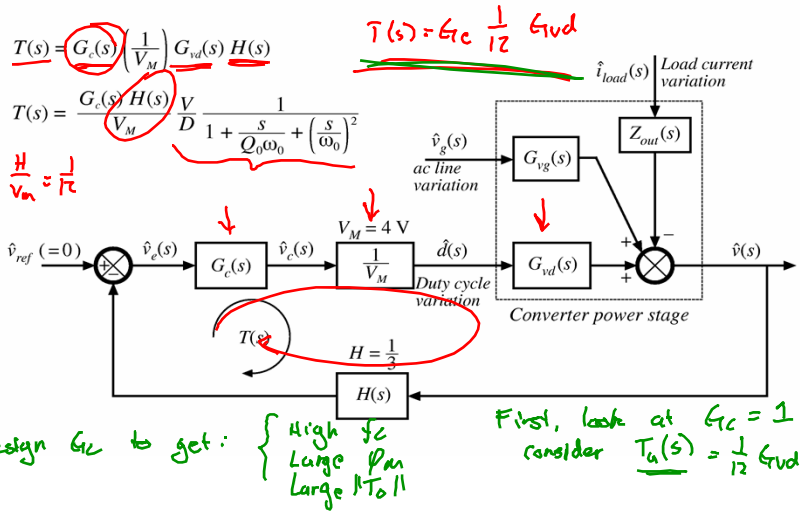


$V = \frac{1}{14} \frac{T}{1+T} V_{ref}$
 $= 3 \frac{2.33}{1+2.33} \approx 10V$ wanted $V = 15V$

Uncompensated loop gain (with $G_c = 1$)

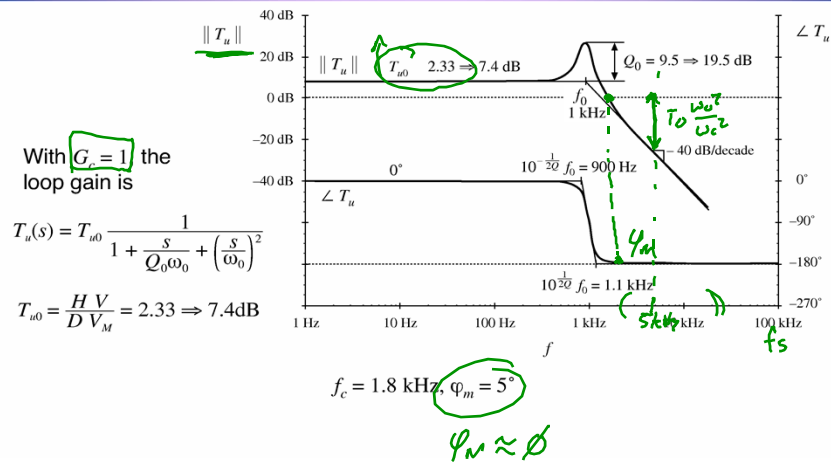

Q vs. φ_m

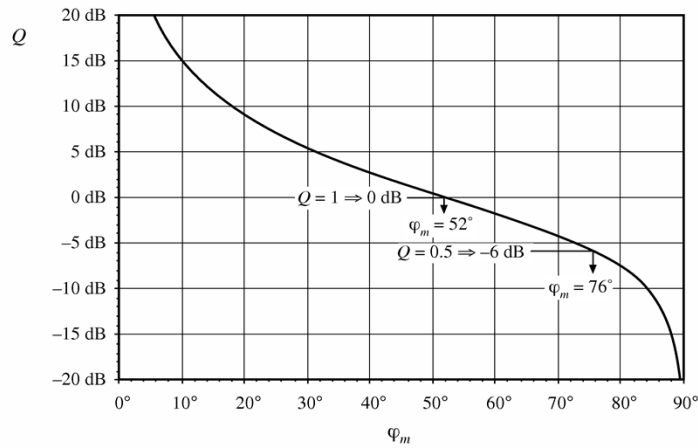

Lead compensator design


To optimally obtain a compensator phase lead of θ at frequency f_c , the pole and zero frequencies should be chosen as follows:

$$f_z = f_c \sqrt{\frac{1 - \sin(\theta)}{1 + \sin(\theta)}}$$

$$f_p = f_c \sqrt{\frac{1 + \sin(\theta)}{1 - \sin(\theta)}}$$

If it is desired that the magnitude of the compensator gain at f_c be unity, then G_{c0} should be chosen as

$$G_{c0} = \sqrt{\frac{f_c}{f_p}}$$

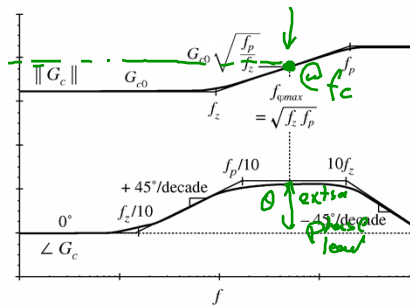

Lead compensator design

- Obtain a crossover frequency of 5 kHz, with phase margin of 52°

$\varphi_m \approx \phi$ T_u has phase of approximately -180° at 5 kHz, hence lead (PD) compensator is needed to increase phase margin.

- Lead compensator should have phase of $+52^\circ$ at 5 kHz $\theta = 52^\circ$
- T_u has magnitude of -20.6 dB at 5 kHz
- Lead compensator gain should have magnitude of $+20.6$ dB at 5 kHz
- Lead compensator pole and zero frequencies should be


$$f_z = (5\text{kHz}) \sqrt{\frac{1 - \sin(52^\circ)}{1 + \sin(52^\circ)}} = 1.7\text{kHz}$$

$$f_p = (5\text{kHz}) \sqrt{\frac{1 + \sin(52^\circ)}{1 - \sin(52^\circ)}} = 14.5\text{kHz}$$


- Compensator dc gain should be $G_{c0} = \left(\frac{f_c}{f_0}\right)^2 \frac{1}{T_{u0}} \sqrt{\frac{f_z}{f_p}} = 3.7 \Rightarrow 11.3\text{dB}$

Gain of T_u @ $f_{crossover}$ Gain of PD compensator


Lead compensator Bode plot

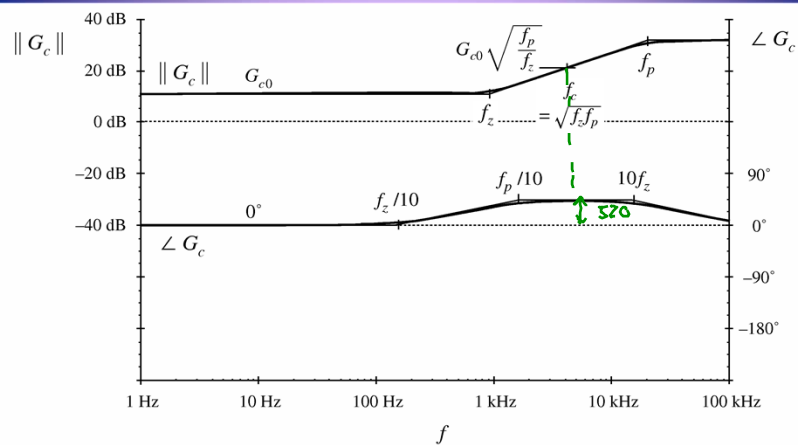


Loop gain, with lead compensator

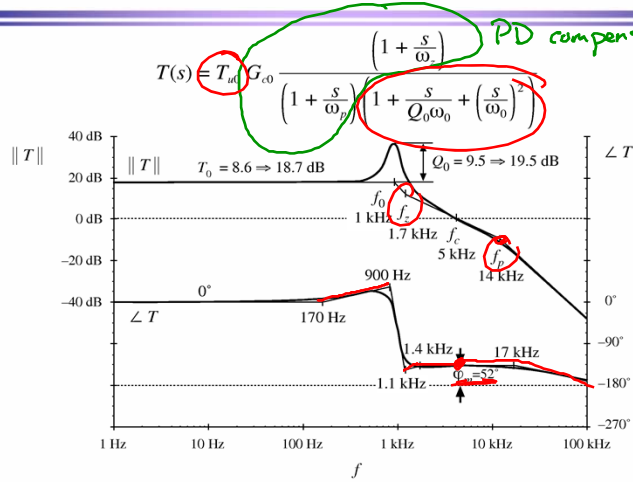


$1/(1+T)$, with lead compensator

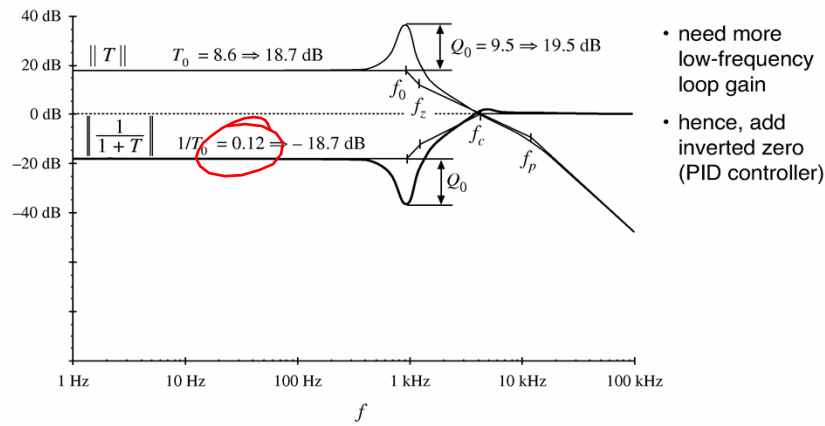

Improved compensator (PID)

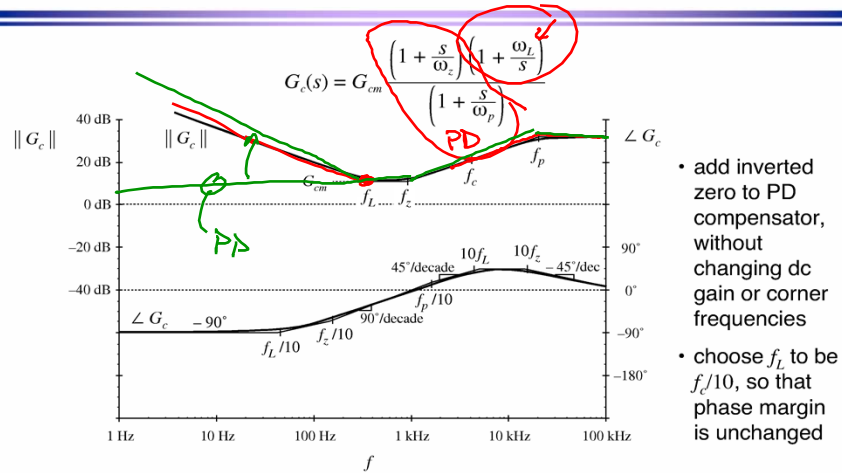

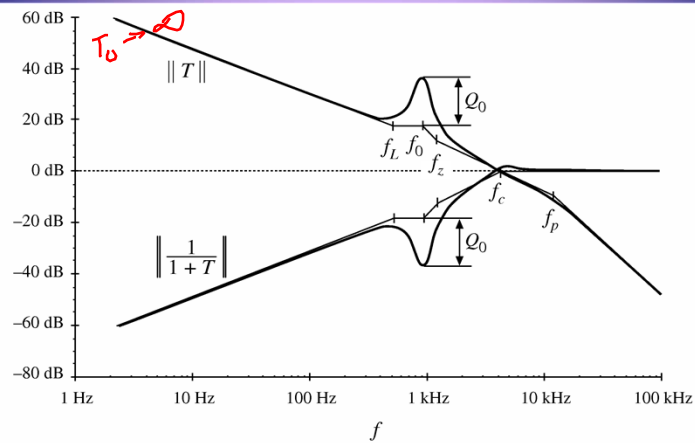$T(s)$ and $1/(1+T(s))$, with PID compensator



Line-to-output transfer function

