
Lecture 20: Feedback Loop Compensation

ECE 481: Power Electronics


Prof. Daniel Costinett

Department of Electrical Engineering and Computer Science

University of Tennessee Knoxville

Fall 2013


9.5.4. Design example


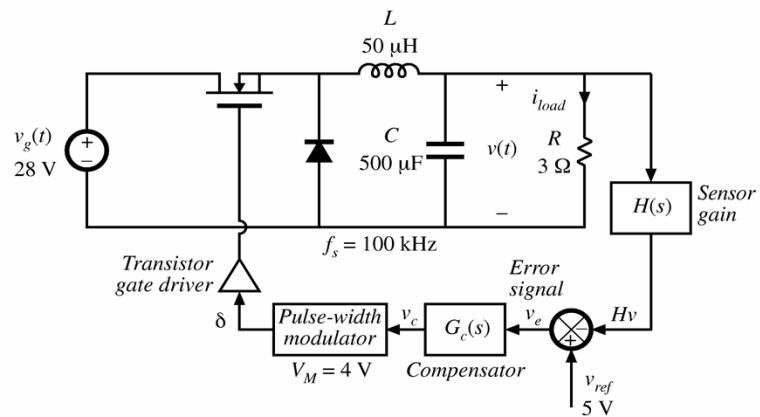


Quiescent operating point

Input voltage	$V_g = 28\text{V}$
Output	$V = 15\text{V}, I_{load} = 5\text{A}, R = 3\Omega$
Quiescent duty cycle	$D = 15/28 = 0.536$
Reference voltage	$V_{ref} = 5\text{V}$
Quiescent value of control voltage	$V_c = DV_M = 2.14\text{V}$
Gain $H(s)$	$H = V_{ref}/V = 5/15 = 1/3$

Small-signal model

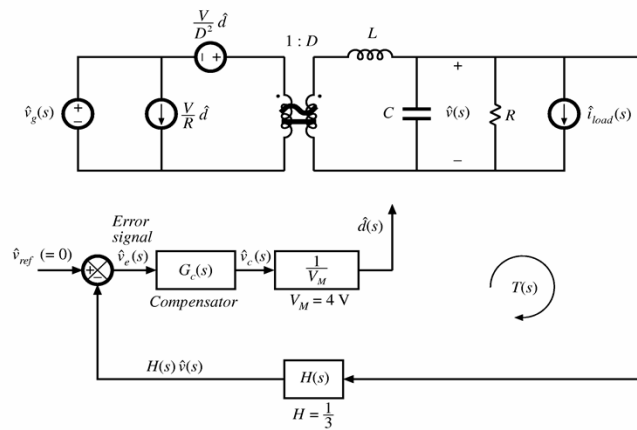

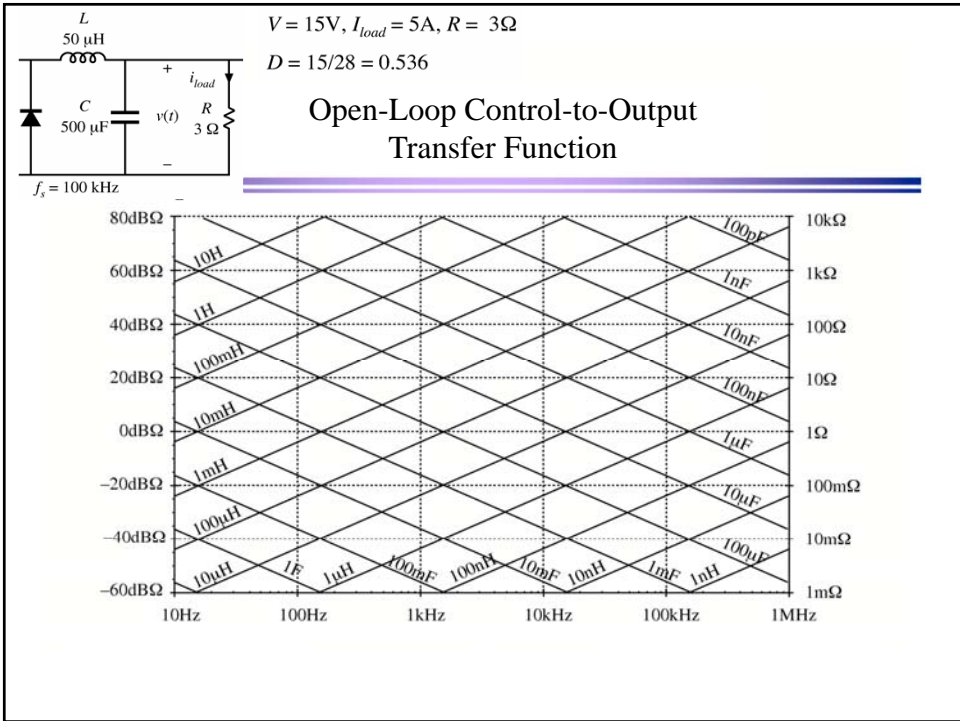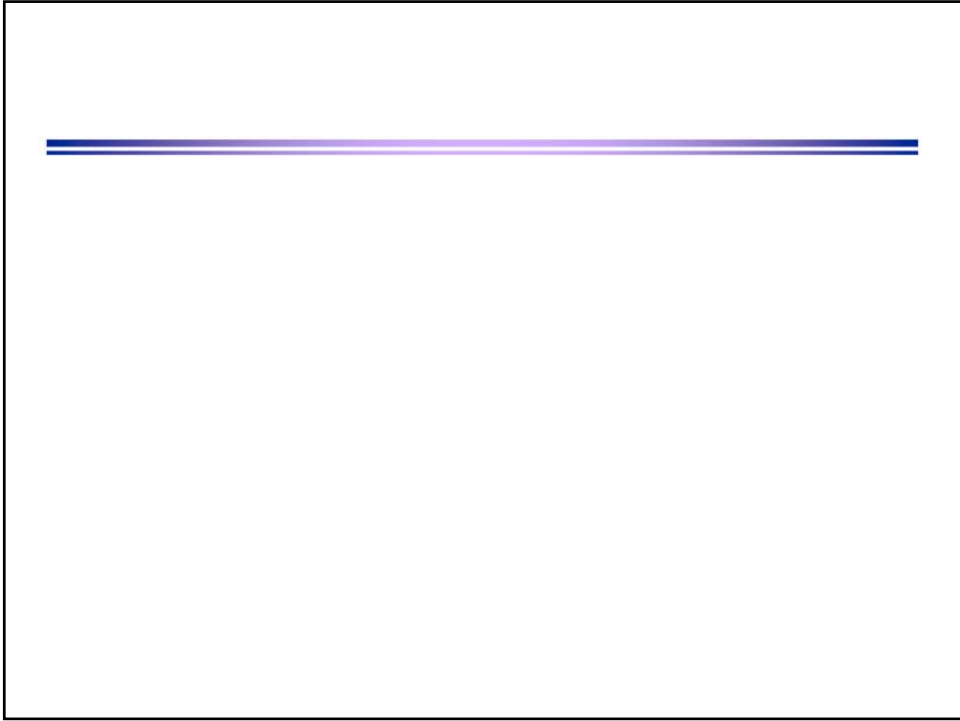

Open-loop control-to-output transfer function $G_{vd}(s)$

$$G_{vd}(s) = \frac{V}{D} \frac{1}{1 + s\frac{L}{R} + s^2LC}$$

standard form:


$$G_{vd}(s) = G_{d0} \frac{1}{1 + \frac{s}{Q_0\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$

salient features:

$$G_{d0} = \frac{V}{D} = 28\text{V}$$

$$f_0 = \frac{\omega_0}{2\pi} = \frac{1}{2\pi\sqrt{LC}} = 1\text{kHz}$$
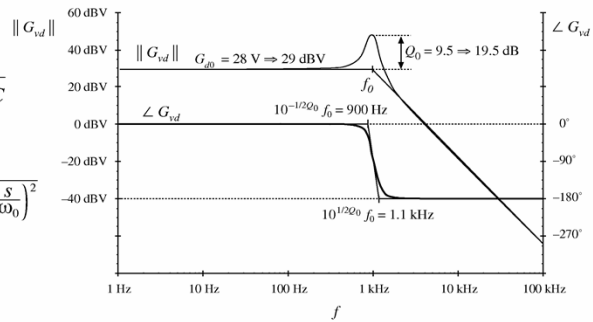
$$Q_0 = R\sqrt{\frac{C}{L}} = 9.5 \Rightarrow 19.5\text{dB}$$



Open-loop line-to-output transfer function and output impedance

$$G_{vg}(s) = D \frac{1}{1 + s\frac{L}{R} + s^2LC}$$

— same poles as control-to-output transfer function


standard form:

$$G_{vg}(s) = G_{g0} \frac{1}{1 + \frac{s}{Q_0\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$


Output impedance:

$$Z_{out}(s) = R \parallel \frac{1}{sC} \parallel sL = \frac{sL}{1 + s\frac{L}{R} + s^2LC}$$

System block diagram

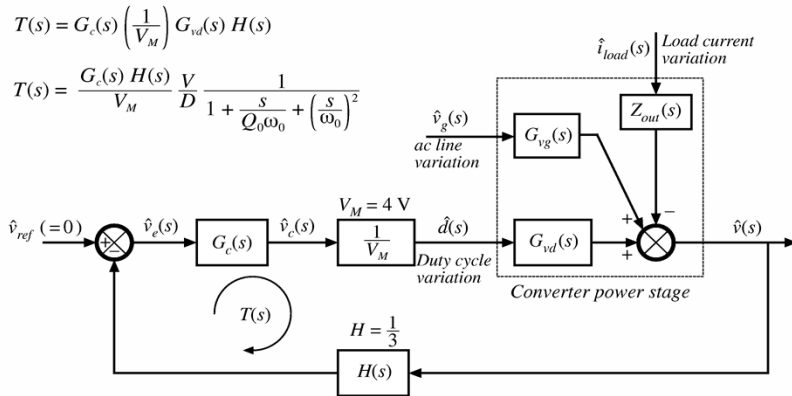

Uncompensated loop gain (with $G_c = 1$)

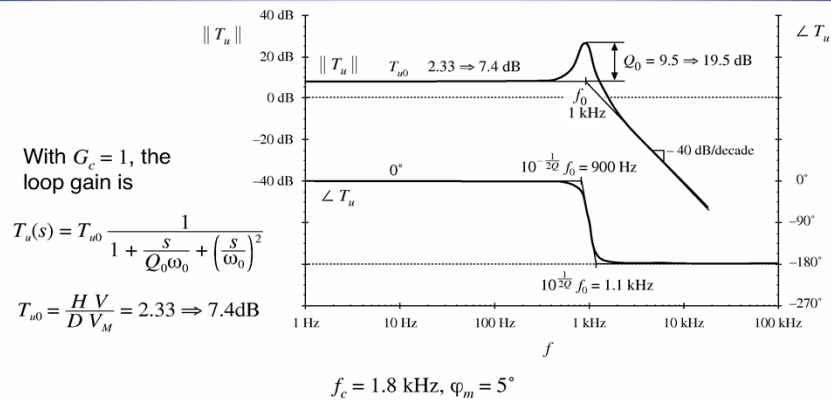

Lead compensator design


- Obtain a crossover frequency of 5 kHz, with phase margin of 52°
- T_u has phase of approximately -180° at 5 kHz, hence lead (PD) compensator is needed to increase phase margin.
- Lead compensator should have phase of $+52^\circ$ at 5 kHz
- T_u has magnitude of -20.6 dB at 5 kHz
- Lead compensator gain should have magnitude of $+20.6$ dB at 5 kHz
- Lead compensator pole and zero frequencies should be

$$f_z = (5\text{kHz}) \sqrt{\frac{1 - \sin(52^\circ)}{1 + \sin(52^\circ)}} = 1.7\text{kHz}$$


$$f_p = (5\text{kHz}) \sqrt{\frac{1 + \sin(52^\circ)}{1 - \sin(52^\circ)}} = 14.5\text{kHz}$$

- Compensator dc gain should be $G_{c0} = \left(\frac{f_c}{f_0}\right)^2 \frac{1}{T_{u0}} \sqrt{\frac{f_z}{f_p}} = 3.7 \Rightarrow 11.3\text{dB}$


Lead compensator Bode plot

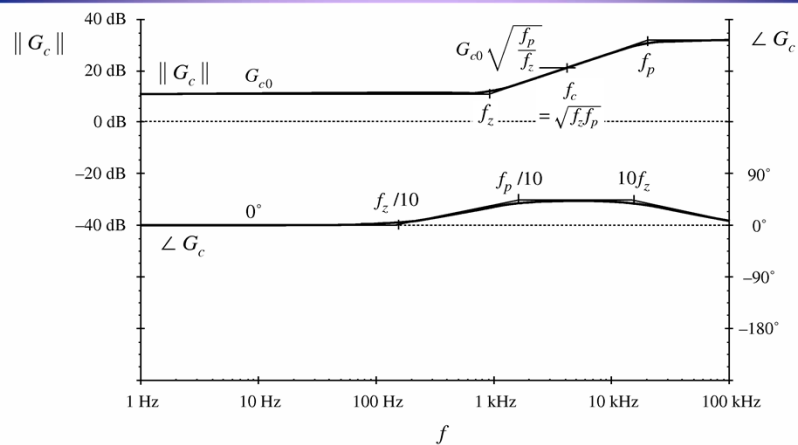


Loop gain, with lead compensator

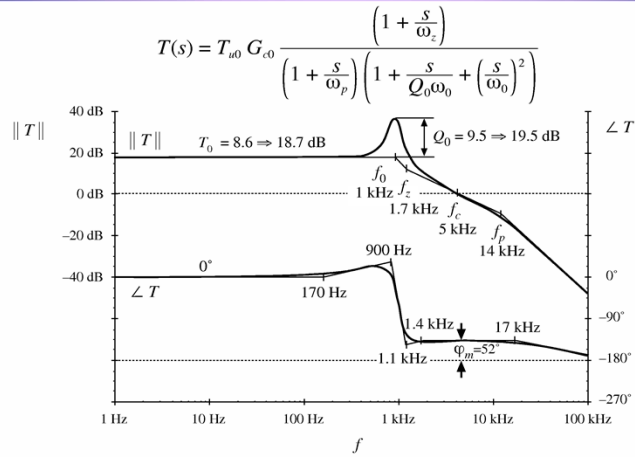

$1/(1+T)$, with lead compensator

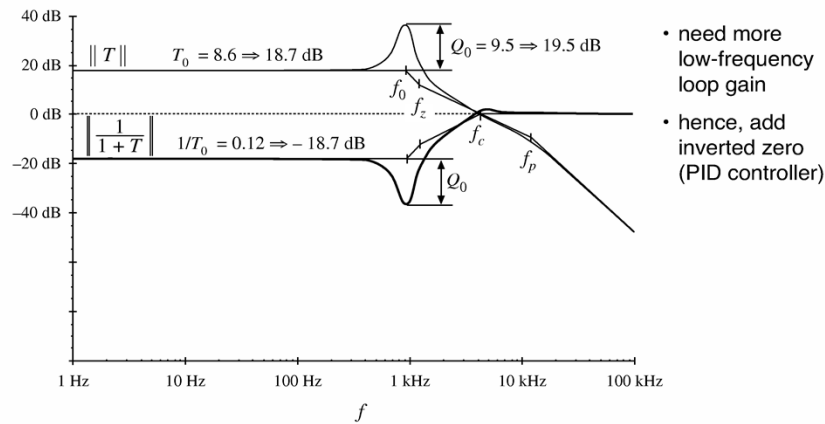


Improved compensator (PID)

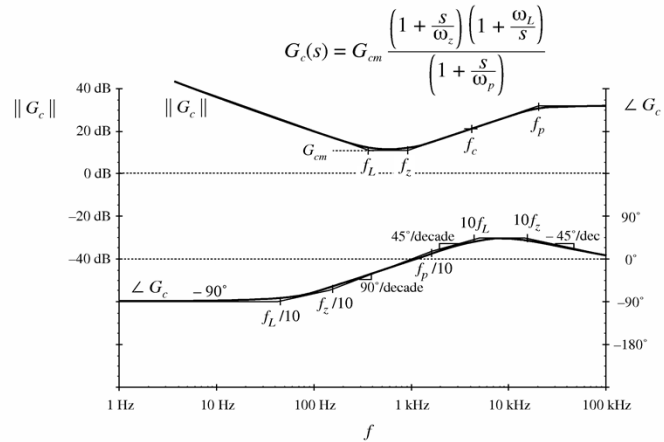


- add inverted zero to PD compensator, without changing dc gain or corner frequencies
- choose f_L to be $f_c/10$, so that phase margin is unchanged

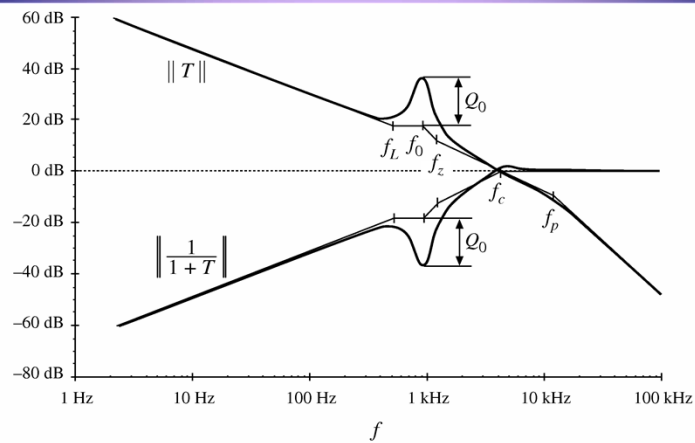
$T(s)$ and $1/(1+T(s))$, with PID compensator



Line-to-output transfer function

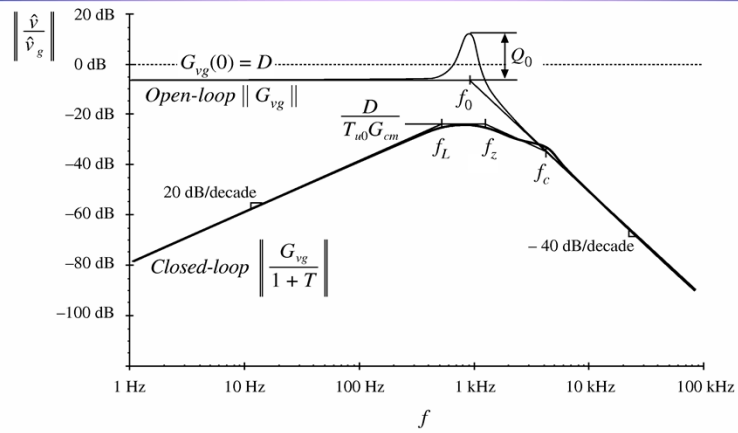

Another Compensator Design Example

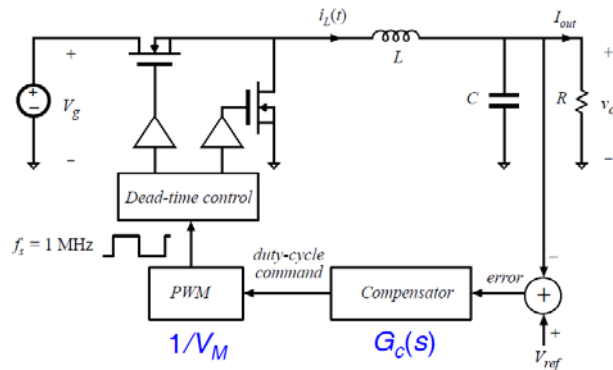


Point-of-Load Synchronous Buck Regulator

Power stage parameters

- Switching frequency: $f_s = 1\text{MHz}$
- $V_{ref} = 1.8\text{V}$
- $I_{out} = 0\text{ to }5\text{A}$
- $V_g = 5\text{V}$
- $L = 1\text{ }\mu\text{H}$
- $R_L = 30\text{ m}\Omega$
- $C = 200\text{ }\mu\text{F}$
- $R_{esr} = 0.8\text{ m}\Omega$
- $V_M = 1\text{V}$
- $H = 1$

Buck Averaged Small-Signal Model

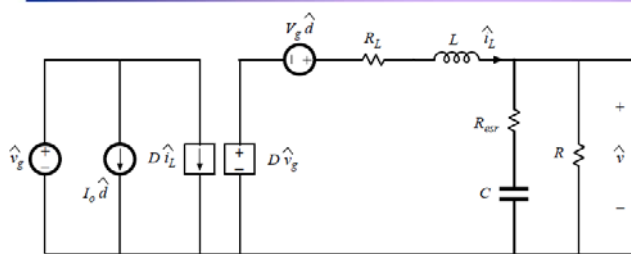

Pair of poles:

$$f_o = \frac{1}{2\pi\sqrt{CL}} = 11\text{ kHz}$$

$$Q_{loss} = \frac{\sqrt{L/C}}{R_{esr} + R_L} = 2.3 \rightarrow 7.2\text{ dB} \quad Q_{load} = \frac{R}{\sqrt{L/C}} > 5$$

$$Q = Q_{loss} \parallel Q_{load} = \frac{Q_{loss} Q_{load}}{Q_{loss} + Q_{load}} < 2.3 \rightarrow 7.2\text{ dB}$$

$$G_{vd}(s) = \frac{\hat{v}_o}{\hat{d}}$$

$$G_{vd}(s) = V_g \frac{1 + \frac{s}{\omega_{esr}}}{1 + \frac{1}{Q} \frac{s}{\omega_o} + \left(\frac{s}{\omega_o}\right)^2}$$


Low-frequency gain (including PWM gain):

$$G_{vdo} \frac{1}{V_M} = 5 \rightarrow 14\text{dB}$$

ESR zero:


$$f_{esr} = \frac{1}{2\pi CR_{esr}} = 1\text{ MHz}$$

Uncompensated loop gain T_u

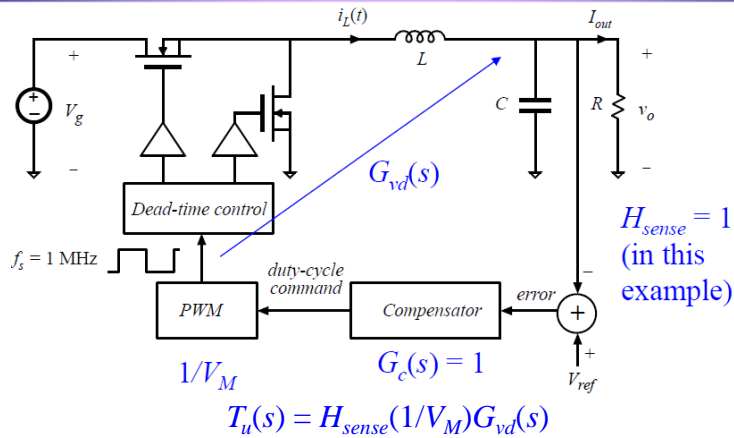


Plot magnitude and phase responses of $T_u(s)$ to plan how to design $G_c(s)$

Magnitude and phase Bode plots of T_u

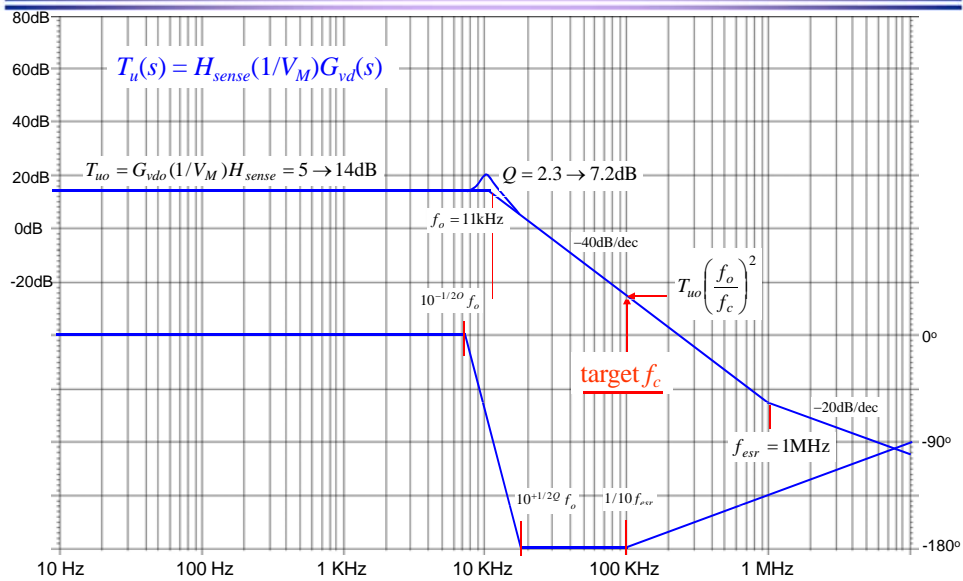

Magnitude and phase Bode plots of T_u

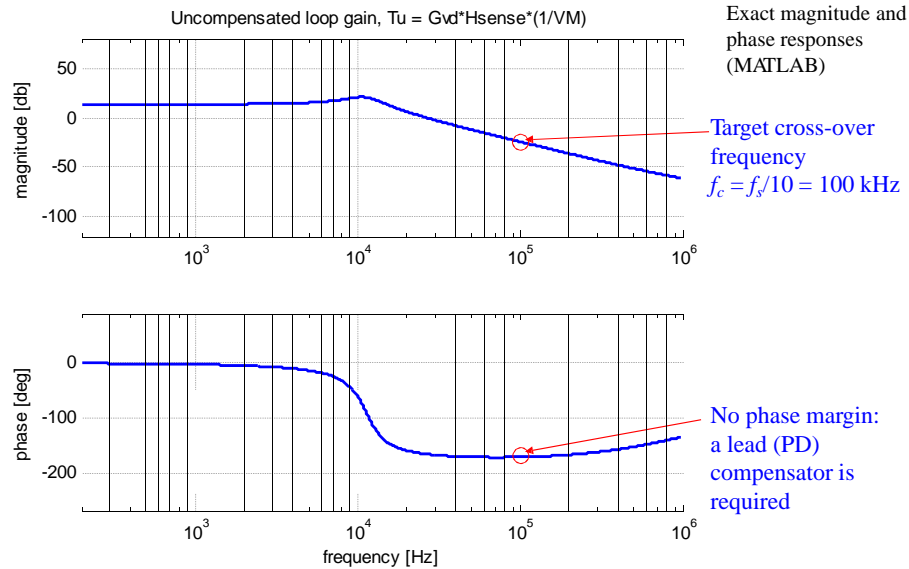

Lead (PD) compensator design

1. Choose: $f_c = 100 \text{ kHz}$
 $\theta = \varphi_m = 53^\circ$

2. Compute:

$$f_z = f_c \sqrt{\frac{1 - \sin(\theta)}{1 + \sin(\theta)}} = 33 \text{ kHz}$$


$$f_p = f_c \sqrt{\frac{1 + \sin(\theta)}{1 - \sin(\theta)}} = 300 \text{ kHz}$$

3. Find G_{co} to position the crossover frequency:

$$\underbrace{T_{uo} \left(\frac{f_o}{f_c} \right)^2}_{\text{Magnitude of } T_u \text{ at } f_c} \underbrace{G_{co} \sqrt{\frac{f_p}{f_z}}}_{\text{Magnitude of } G_c \text{ at } f_c} = 1$$

Magnitude of T_u at f_c Magnitude of G_c at f_c
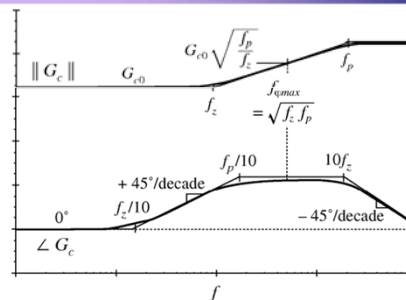
$$G_{co} = \frac{1}{T_{uo}} \left(\frac{f_c}{f_o} \right)^2 \sqrt{\frac{f_z}{f_p}} = 5.45 \rightarrow 15 \text{ dB}$$



Lead (PD) compensator summary

$$G_c(s) = G_{co} \underbrace{\left(1 + \frac{s}{\omega_z}\right)}_{\text{Lead compensator}} \underbrace{\frac{1}{\left(1 + \frac{s}{\omega_{p1}}\right)\left(1 + \frac{s}{\omega_{p2}}\right)}}_{\text{HF pole}}$$

$$G_{co} = 5.45 \rightarrow 15 \text{ dB}$$

$$f_z = 33 \text{ kHz}$$

$$f_{p1} = 300 \text{ kHz}$$


$$f_c = 100 \text{ kHz} \quad (=1/10 \text{ of } f_s)$$

High-frequency gain of the lead compensator: $G_{co}f_{p1}/f_z = 49$ (34 dB)

Added high-frequency pole: $f_{p2} = 1 \text{ MHz}$ ($=f_{esr} = f_s$ in this example)

Practical implementation would require an op-amp with a gain bandwidth product (GBW) of at least $49 * f_{p2} = 49 \text{ MHz}$


Loop gain with lead (PD) compensator

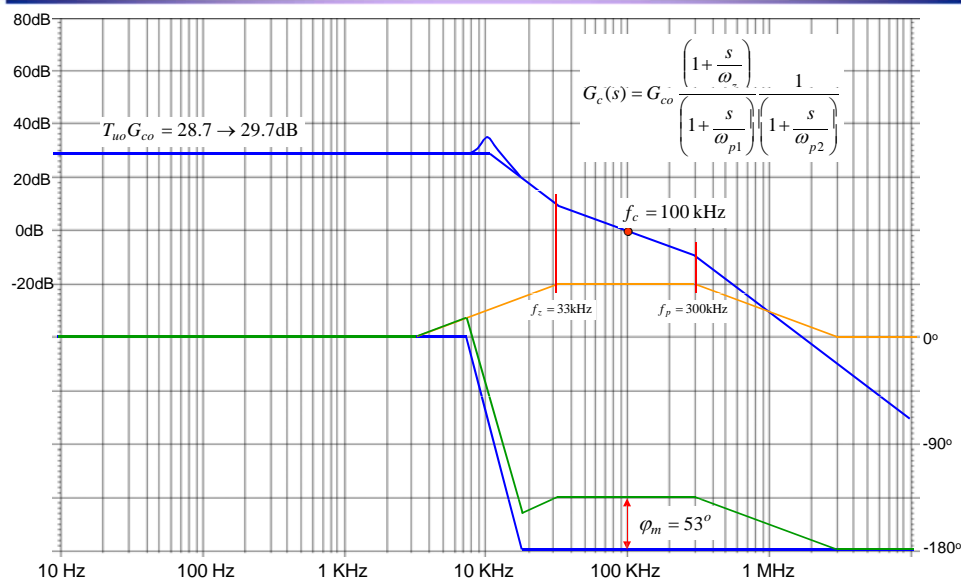

Add lag (PI) compensator

$$G_c(s) = G_{co} \left(1 + \frac{\omega_L}{s} \right)$$

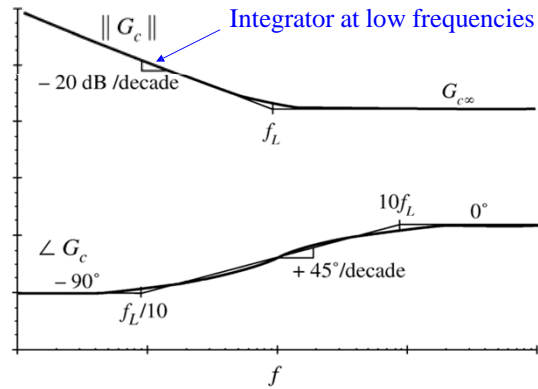
Improves low-frequency loop gain and regulation




Choose $10f_L < f_c$ so that phase margin stays approximately the same: $f_L = 8$ kHz

Keep the same cross-over frequency: $G_{co} = G_{co} = G_{cm} = 5.45 \rightarrow 15$ dB

Adding PI Compensator

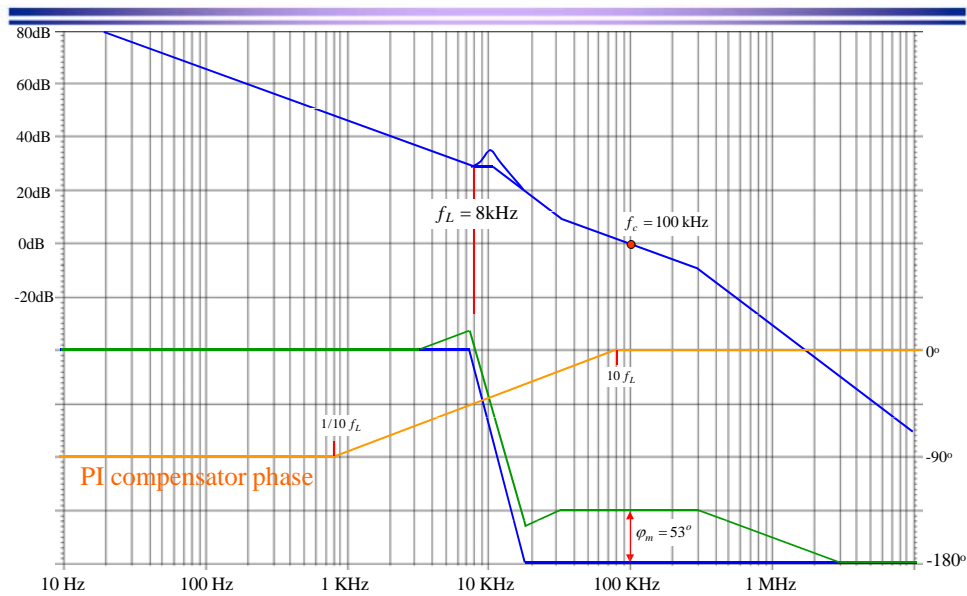


Complete analog PID compensator: summary

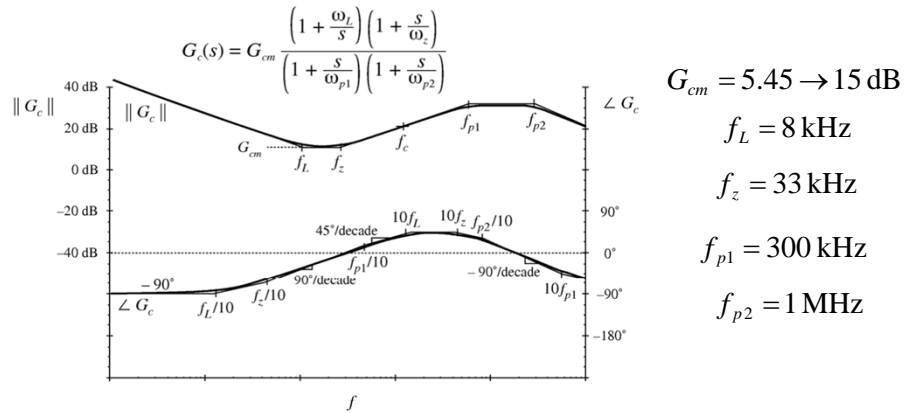


Crossover frequency: $f_c = 100 \text{ kHz}$ ($=1/10$ of f_s)

Phase margin: $\varphi_m = 53^\circ$


Magnitude and phase Bode plots of T

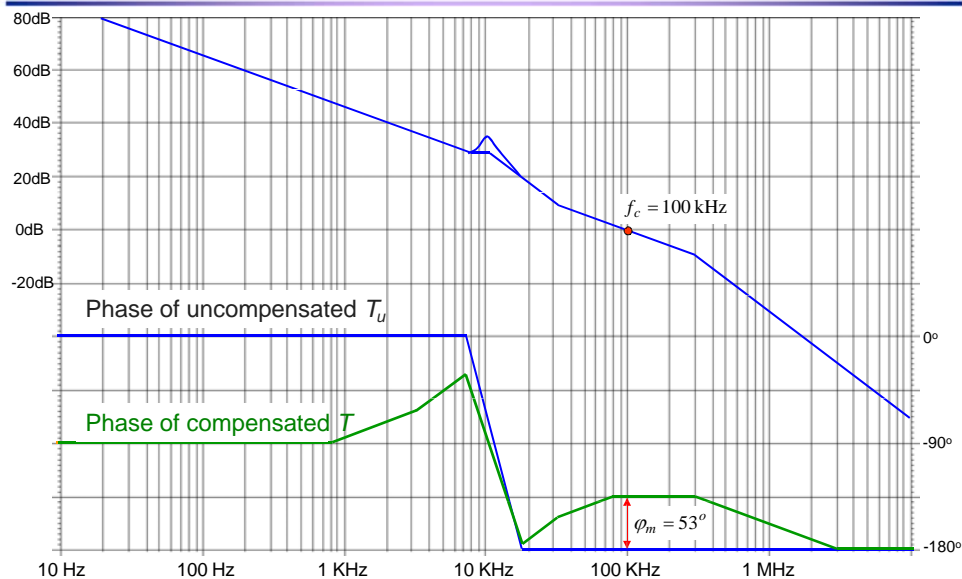

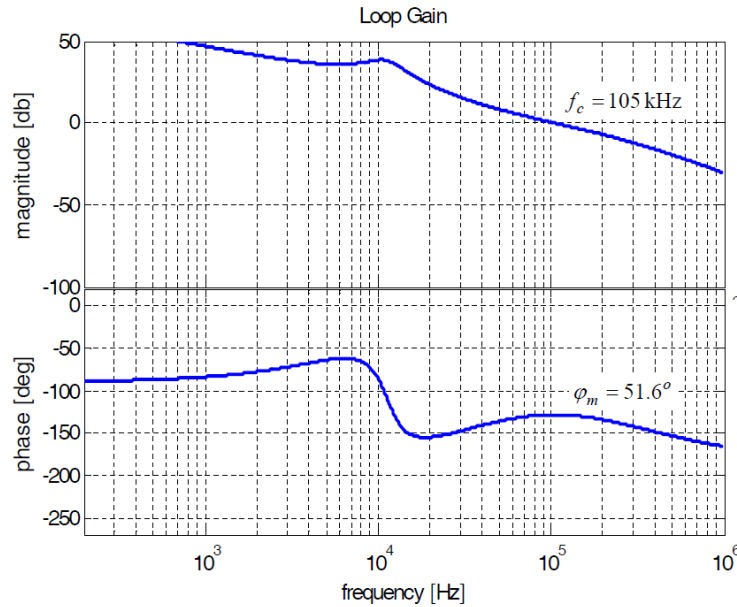Verification: exact loop gain magnitude and phase responses (MATLAB)



Analog PID compensator implementation

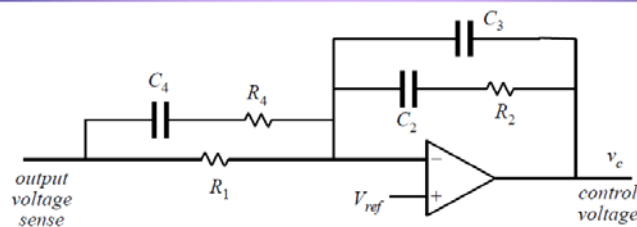

Design equations (approximate)

$$G_c(s) = G_{cm} \frac{\left(1 + \frac{\omega_L}{s}\right) \left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)}$$

$$G_{cm} = \frac{R_2}{R_1} \quad f_L = \frac{1}{2\pi R_2 C_2}$$

$$f_z = \frac{1}{2\pi(R_1 + R_4)C_4} \quad f_{p1} = \frac{1}{2\pi R_4 C_4}$$

$$f_{p2} = \frac{1}{2\pi R_2 C_3}$$

Verification of closed-loop responses

Closed-loop reference-to-output response

Closed-loop transfer function from \hat{v}_{ref} to $\hat{v}(s)$ is:


$$\left. \frac{\hat{v}(s)}{\hat{v}_{ref}(s)} \right|_{\substack{v_g=0 \\ i_{load}=0}} = \frac{1}{H(s)} \frac{T(s)}{1+T(s)}$$

Closed-loop output impedance


$$\left. \frac{\hat{v}(s)}{-\hat{i}_{load}(s)} \right|_{\substack{v_{ref}=0 \\ v_g=0}} = \frac{Z_{out}(s)}{1+T(s)}$$

and step-load transient response

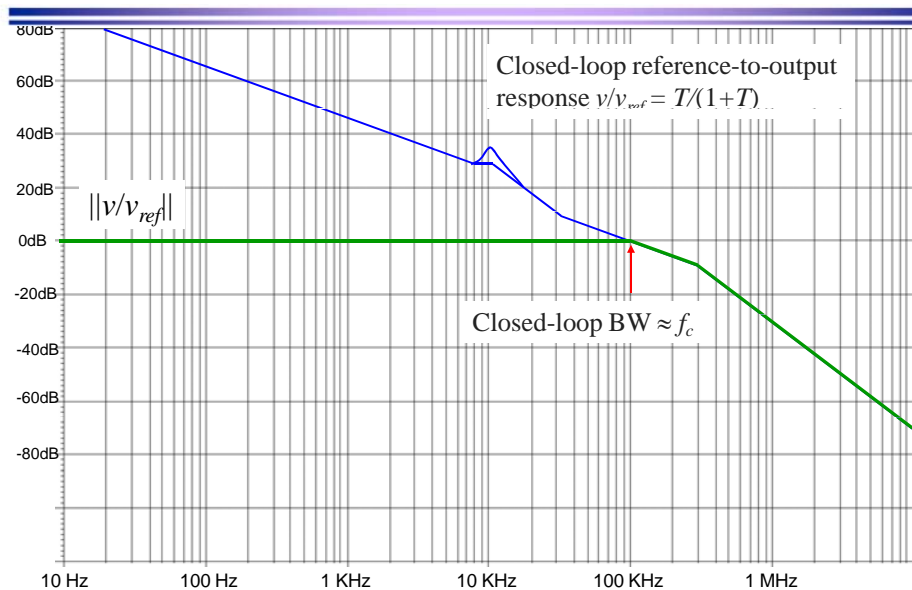
Construction of closed-loop $T/(1+T)$ response




Closed-loop reference-to-output response

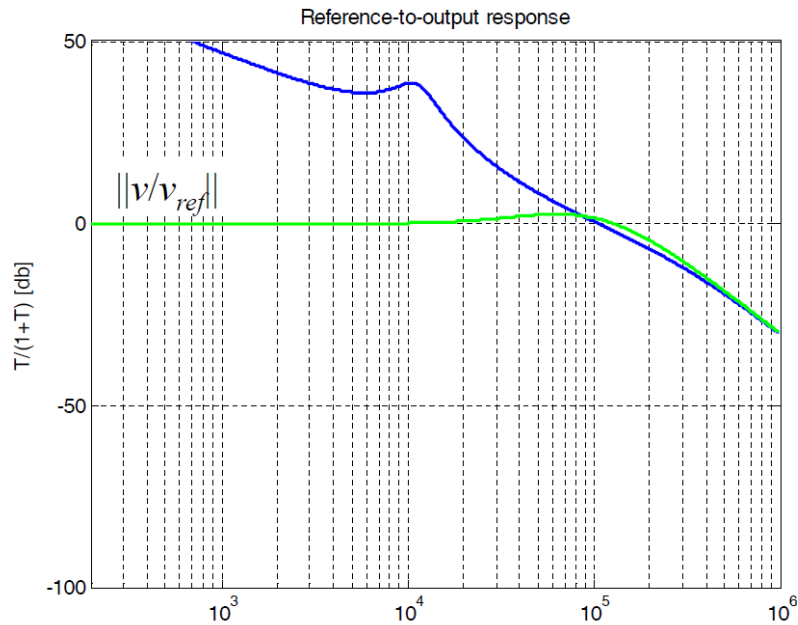

Small-signal step-reference response

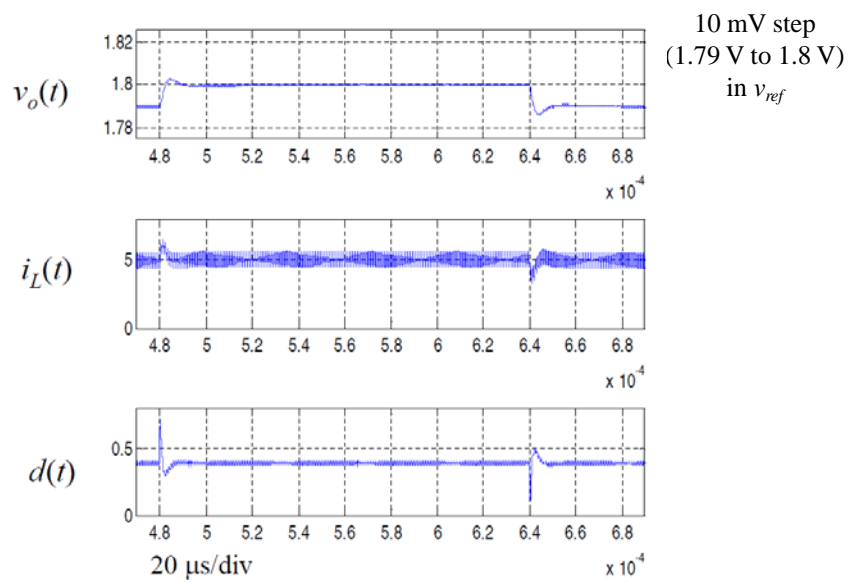


Small-signal step-reference response

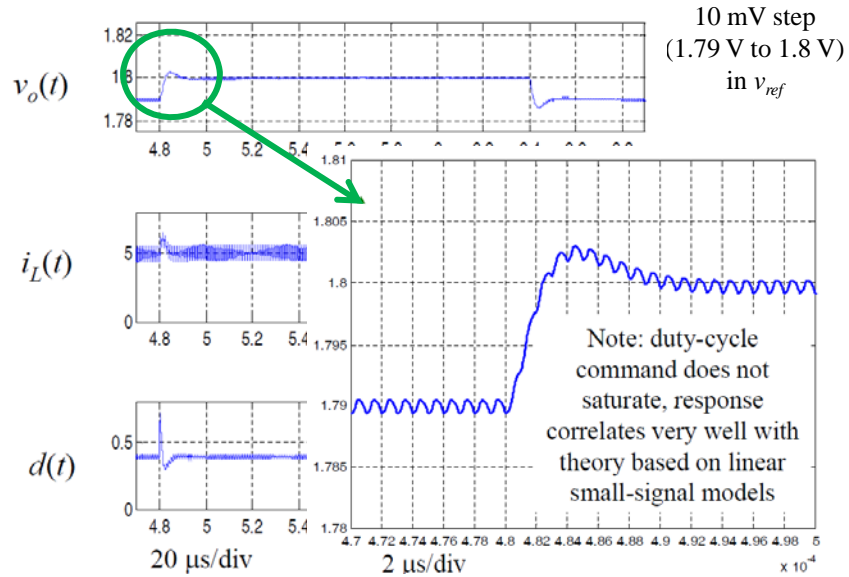

Output impedance

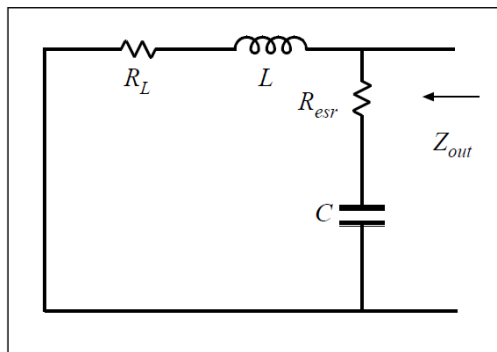
Synchronous buck open-loop output impedance




$$Z_{out}(s) = \left(R_{esr} + \frac{1}{sC} \right) \parallel (R_L + sL)$$

- $L = 1 \mu\text{H}$
- $R_L = 30 \text{ m}\Omega$
- $C = 200 \mu\text{F}$
- $R_{esr} = 0.8 \text{ m}\Omega$

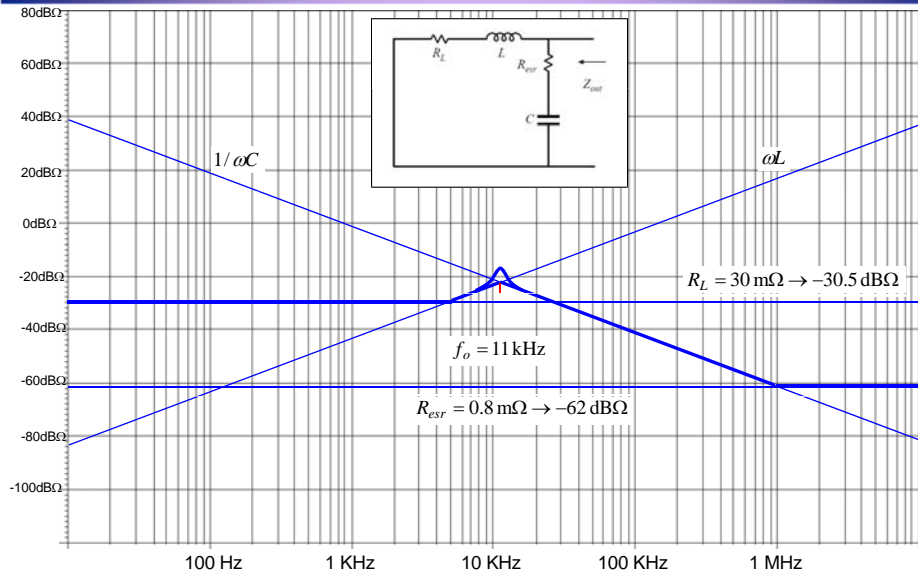
Open-loop output impedance: algebra on the graph




Construction of $1/(1+T)$

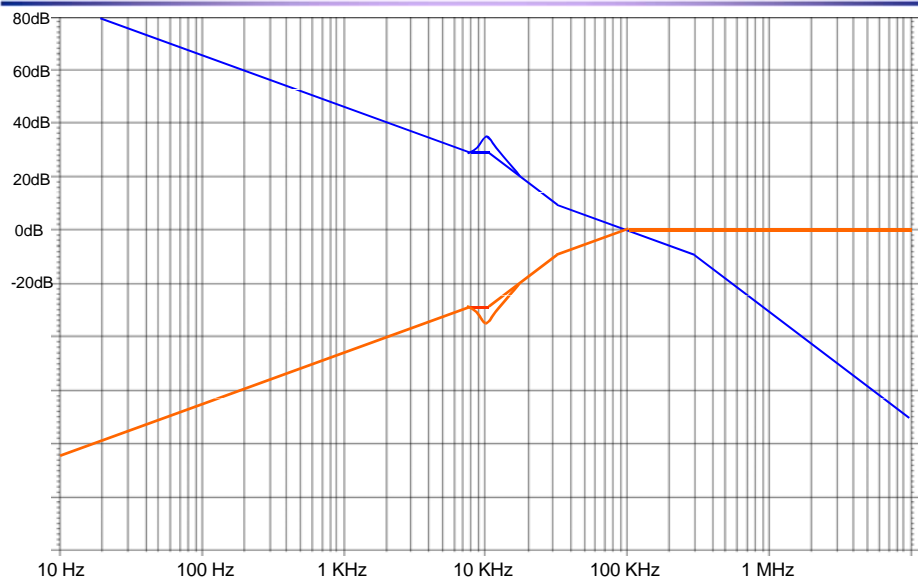

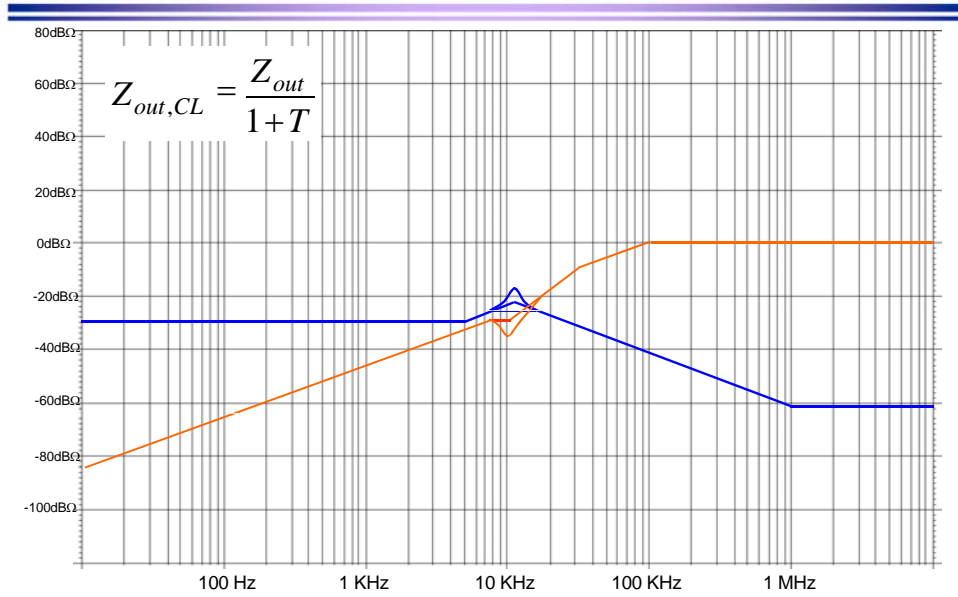
Construction of closed-loop output impedance



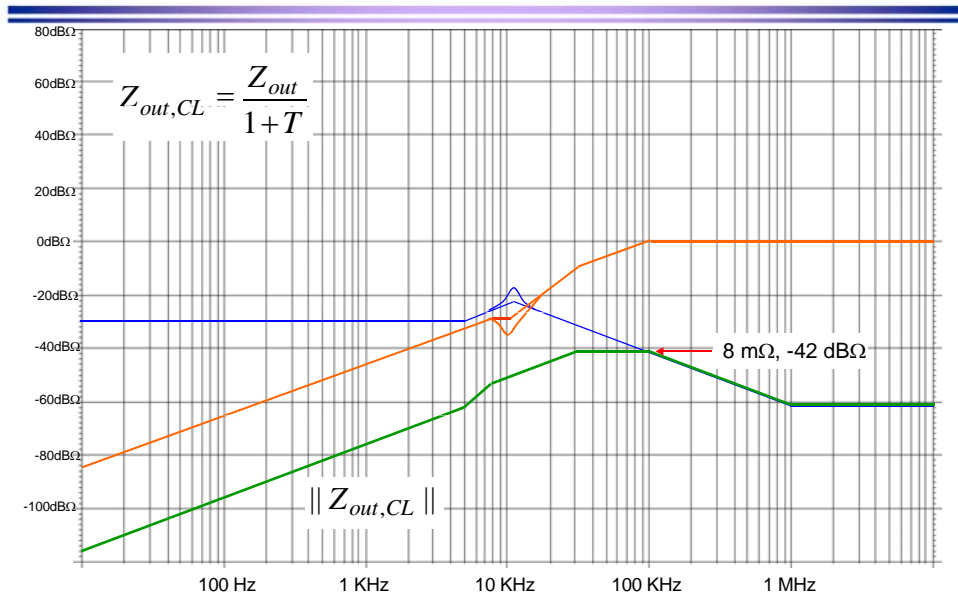
Closed-loop output impedance $Z_{out,CL}$



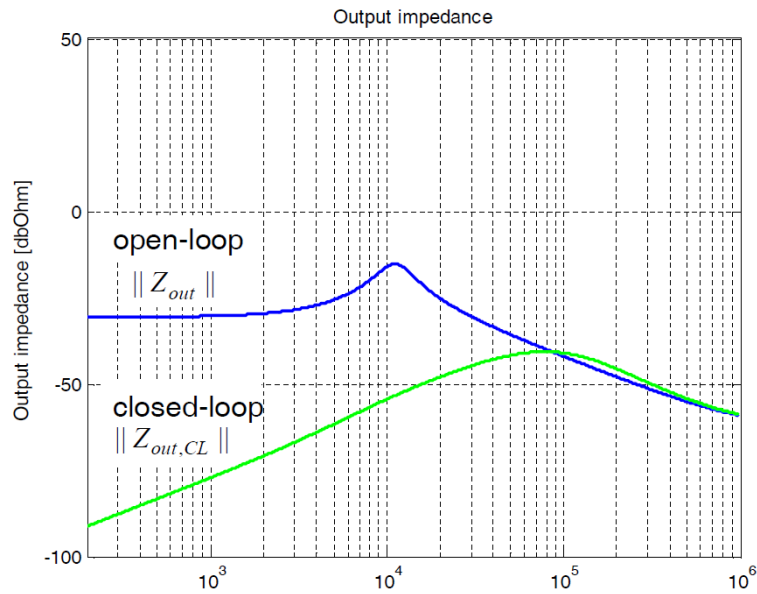Verification: closed-loop output impedance



Step-load transient responses

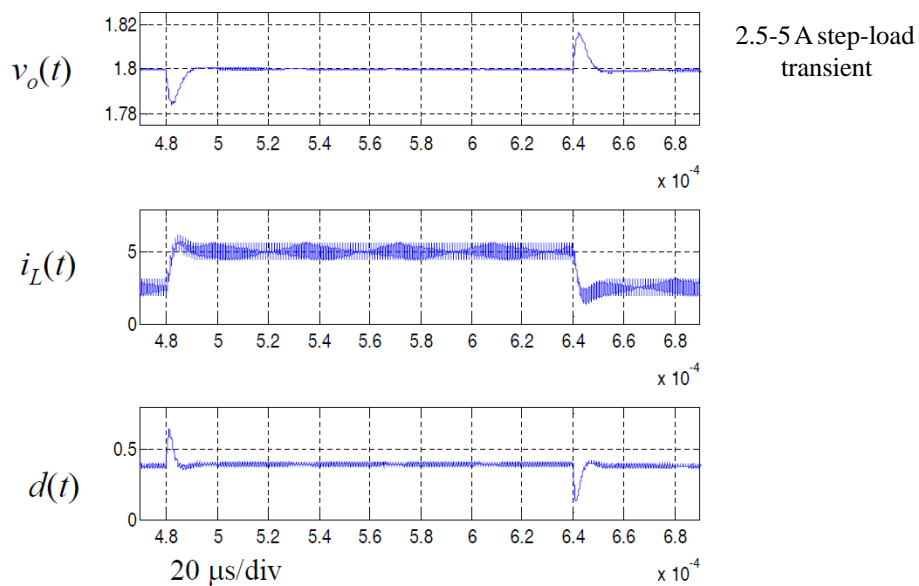

Step-load transient responses

