

Test  
Test

---

## Lecture 2: Volt-Second and Capacitor Charge Balance

ECE 481: Power Electronics

Prof. Daniel Costinett

Department of Electrical Engineering and Computer Science

University of Tennessee Knoxville

Fall 2013


### Chapter 2

## Principles of Steady-State Converter Analysis

---

- 2.1. Introduction
- 2.2. Inductor volt-second balance, capacitor charge balance, and the small ripple approximation
- 2.3. Boost converter example
- 2.4. Cuk converter example
- 2.5. Estimating the ripple in converters containing two-pole low-pass filters
- 2.6. Summary of key points


## A high-efficiency converter

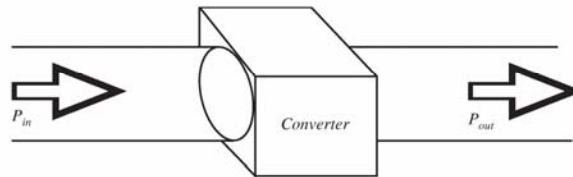

A goal of current converter technology is to construct converters of small size and weight, which process substantial power at high efficiency

*Cost, "performance"*

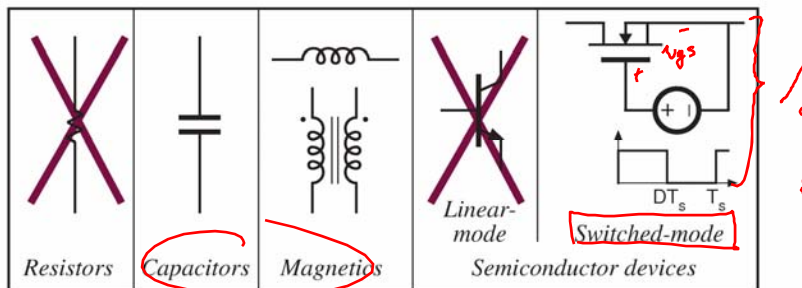
## Devices available to the circuit designer



Power processing: avoid lossy elements

## 2.1 Introduction Buck converter

SPDT switch changes dc component

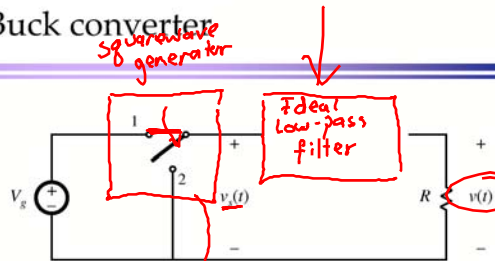


Switch output voltage waveform


Duty cycle  $D$ :  
 $0 \leq D \leq 1$

complement  $D'$ :  
 $D' = 1 - D$

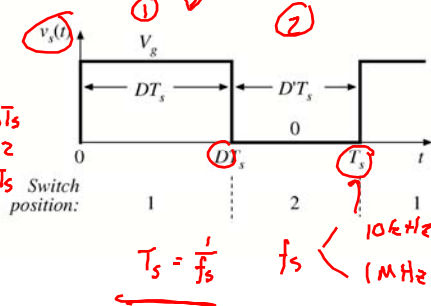switch in pos 1  
... in pos 2  
 $DT_s < 1/2 T_s$



## Dc component of switch output voltage

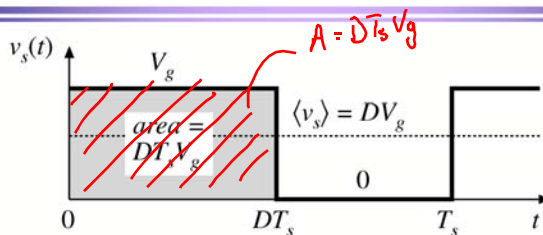

Fourier analysis: Dc component = average value

$$\langle v_s \rangle = \frac{1}{T_s} \int_0^{T_s} v_s(t) dt$$


$$\langle v_s \rangle = \frac{1}{T_s} (DT_s V_g) = DV_g$$

$$v(t) = \langle v_s \rangle$$


$$v(t) \approx V = DV_g$$

"Pulse Width Modulation" PWM

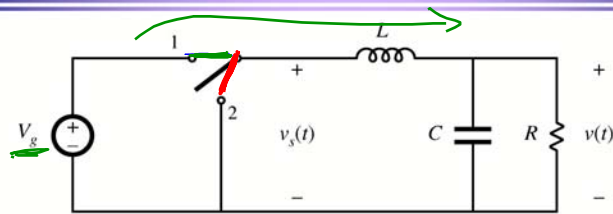
### Insertion of low-pass filter to remove switching harmonics and pass only dc component



$v = \langle v_s \rangle = DV_g$

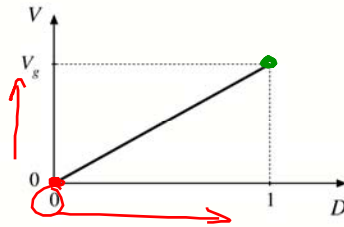


### Three basic dc-dc converters

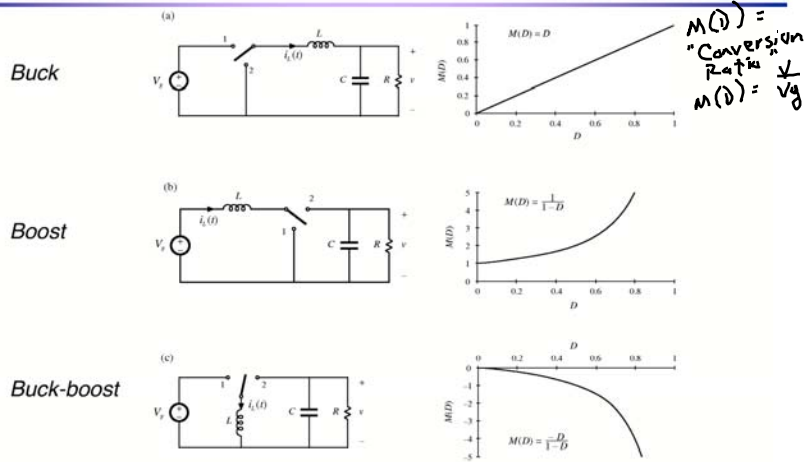


## Objectives of this chapter

- Develop techniques for easily determining output voltage of an arbitrary converter circuit
- Derive the principles of inductor volt-second balance and capacitor charge (amp-second) balance
- Introduce the key small ripple approximation
- Develop simple methods for selecting filter element values
- Illustrate via examples
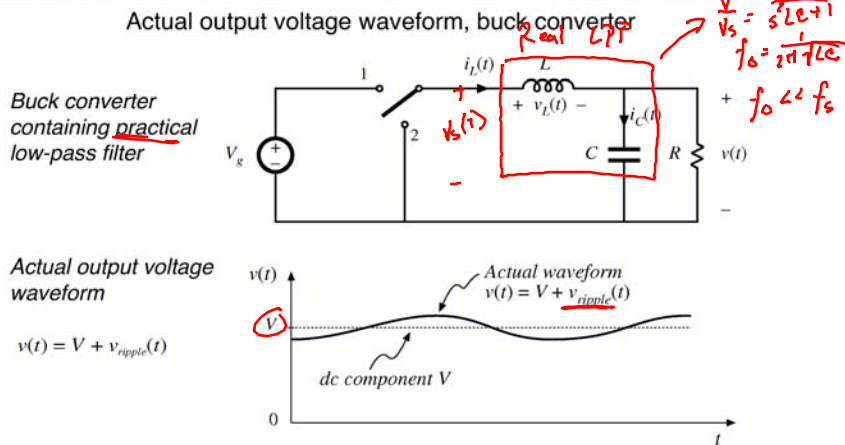
### 2.2. Inductor volt-second balance, capacitor charge balance, and the small ripple approximation



## The small ripple approximation

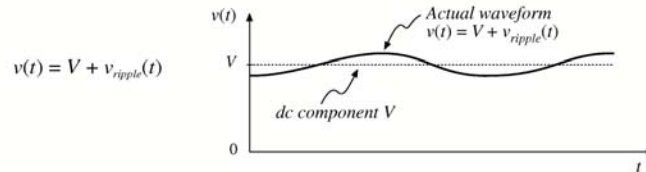


In a well-designed converter, the output voltage ripple is small. Hence, the waveforms can be easily determined by ignoring the ripple:

$$|v_{\text{ripple}}| \ll V$$

$$v(t) \approx V$$

$\|v_{\text{ripple}}\| \neq 0 \rightarrow$  neglect relative to  $V$
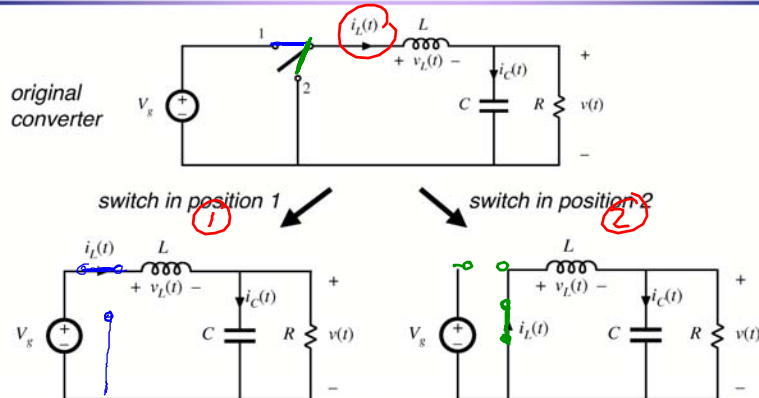
## Buck converter analysis: inductor current waveform



## Inductor voltage and current Subinterval 1: switch in position 1

$0 < t < DT_s$


Inductor voltage

$$V_{L1} = V_g - v(t)$$

Small ripple approximation:

$$v(t) \approx V$$


$$V_{L1} = V_g - V$$

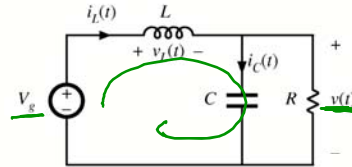

$$V_{L1} = L \frac{di_L}{dt}$$

Solve for the slope:
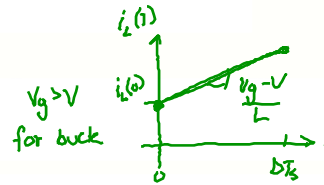
$$\frac{di_L}{dt} = \frac{V_g - V}{L} \rightarrow \frac{V_g - V}{L} > 0$$



## Inductor voltage and current Subinterval 2: switch in position 2

Inductor voltage



$$V_{L2} = 0 - v(t)$$

Small ripple approximation:



$$v(t) \approx V$$

$$V_{L2} = -V$$

$$\frac{di_L}{dt} = \frac{-V}{L} < 0$$

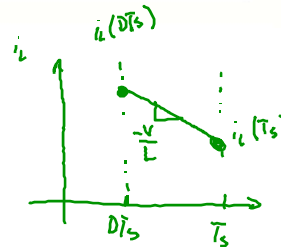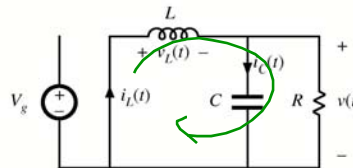


# Inductor Voltage and Current Waveforms

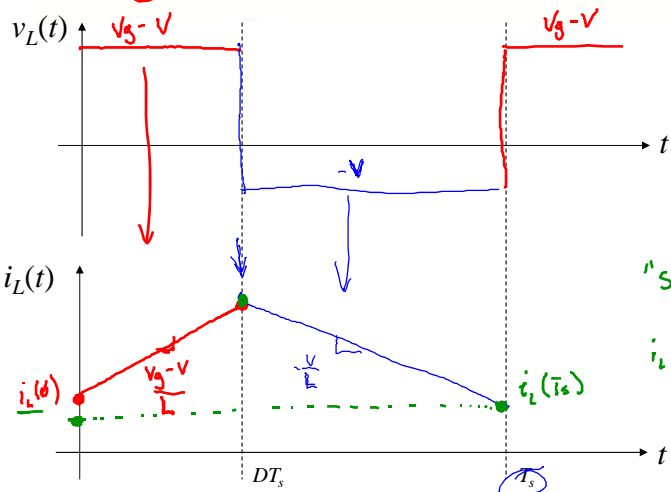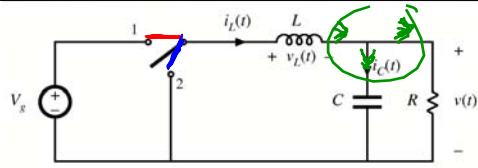
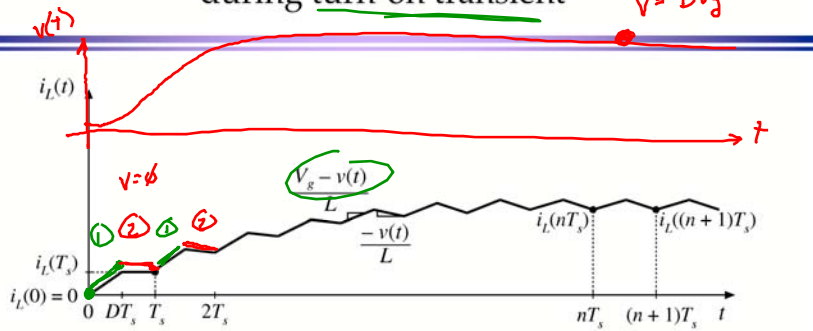
## "Buck" Converter

Inductor current waveform during turn-on transient




When the converter operates in equilibrium:

$$i_L((n+1)T_s) = i_L(nT_s)$$

"steady state"


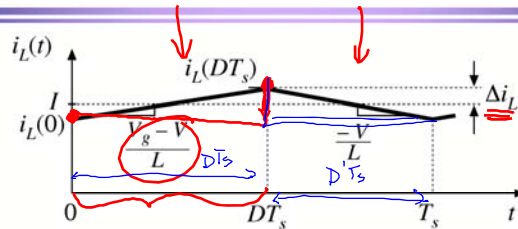
## Determination of inductor current ripple magnitude



$2\Delta i_L$  (change in  $i_L$ ) = (slope)(length of subinterval)

$$2\Delta i_L = \frac{V_g - V}{L} (DT_s)$$

$$-2\Delta i_L = \frac{-V}{L} (T_s - DT_s)$$

$$D' = 1 - D$$

$$\Delta i_L = \frac{V_g - V}{2L} DT_s$$

$$2\Delta i_L = \frac{V}{L} D' T_s$$

$$2\Delta i_L = \frac{DV_g}{L} (1-D) T_s$$

$$L = \frac{V_g - V}{2\Delta i_L} DT_s$$

$$L = \frac{V_g - DV_g}{2\Delta i_L} DT_s = \frac{V_g(1-D)}{2\Delta i_L} DT_s$$

## The principle of inductor volt-second balance: Derivation

Inductor defining relation:

$$v_L(t) = L \frac{di_L(t)}{dt}$$

Integrate over one complete switching period:

$$i_L(T_s) - i_L(0) = \frac{1}{L} \int_0^{T_s} v_L(t) dt$$

Steady state  
 $i_L(T_s) = i_L(0)$

In periodic steady state, the net change in inductor current is zero:

$$0 = \int_0^{T_s} v_L(t) dt$$


Hence, the total area (or volt-seconds) under the inductor voltage waveform is zero whenever the converter operates in steady state.

An equivalent form:

$$0 = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = \langle v_L \rangle$$

The average inductor voltage is zero in steady state.

## Buck Volt-Second Balance

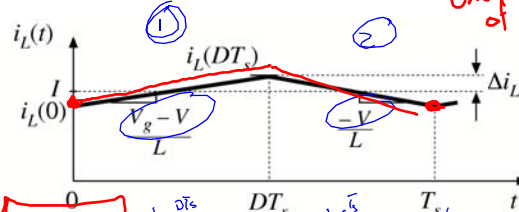

Assumption steady state

$$\langle v_L \rangle = \phi = \frac{1}{T_s} \int_0^{DT_s} v_L(t) dt + \frac{1}{T_s} \int_{DT_s}^{T_s} v_L(t) dt$$

$$\phi = \frac{1}{T_s} [(V_g - V)DT_s + -V(1-D)T_s]$$


$$\phi = \frac{1}{T_s} [V_g DT_s - VDT_s - VDT_s]$$

$$\phi = V_g D - V(D + D')$$

$$\phi = V_g D - V \rightarrow \boxed{V = DV_g}$$

Recall  $1-D = D'$
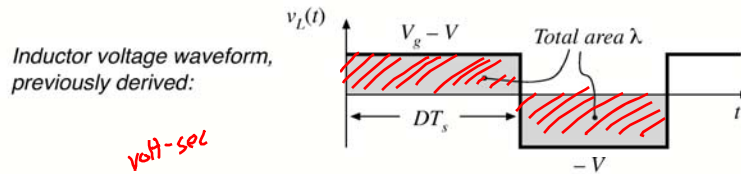
## Inductor volt-second balance: Buck converter example



Integral of voltage waveform is area of rectangles:

$$\lambda = \int_0^{T_s} v_L(t) dt = (V_g - V)(DT_s) + (-V)(D'T_s)$$

Average voltage is

$$\langle v_L \rangle = \frac{\lambda}{T_s} = D(V_g - V) + D'(-V)$$

Equate to zero and solve for V:

$$0 = DV_g - (D + D')V = DV_g - V \Rightarrow \boxed{V = DV_g} \quad \frac{V}{V_g} = D = M(D)$$

Conversion Ratio

## The principle of capacitor charge balance: Derivation

Capacitor defining relation:

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

Integrate over one complete switching period:

$$v_c(T_s) - v_c(0) = \frac{1}{C} \int_0^{T_s} i_c(t) dt$$

In periodic steady state, the net change in capacitor voltage is zero:

$$0 = \frac{1}{T_s} \int_0^{T_s} i_c(t) dt = \langle i_c \rangle$$

Hence, the total area (or charge) under the capacitor current waveform is zero whenever the converter operates in steady state. The average capacitor current is then zero.

## Buck Capacitor-Charge Balance

