
Lecture 2: Volt-Second and Capacitor Charge Balance

ECE 481: Power Electronics

Prof. Daniel Costinett

Department of Electrical Engineering and Computer Science

University of Tennessee Knoxville


Fall 2013

Chapter 2 Principles of Steady-State Converter Analysis

- 2.1. Introduction
- 2.2. Inductor volt-second balance, capacitor charge balance, and the small ripple approximation
- 2.3. Boost converter example
- 2.4. Cuk converter example
- 2.5. Estimating the ripple in converters containing two-pole low-pass filters
- 2.6. Summary of key points

2.1 Introduction Buck converter


SPDT switch changes dc component

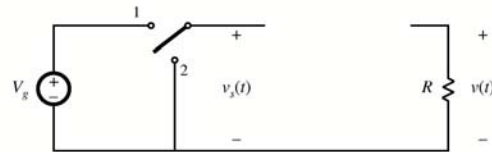


Switch output voltage waveform

Duty cycle D :
 $0 \leq D \leq 1$

complement D' :
 $D' = 1 - D$

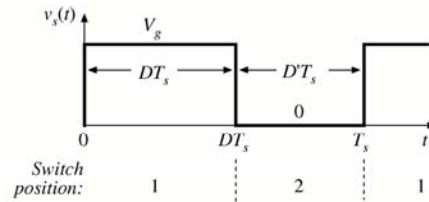

Dc component of switch output voltage

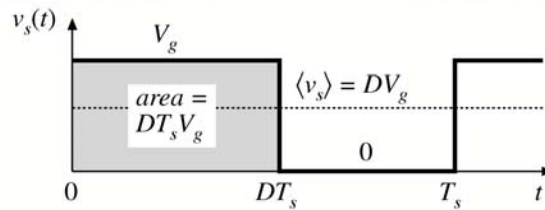


Fourier analysis: Dc component = average value


$$\langle v_s \rangle = \frac{1}{T_s} \int_0^{T_s} v_s(t) dt$$

$$\langle v_s \rangle = \frac{1}{T_s} (DT_s V_g) = DV_g$$

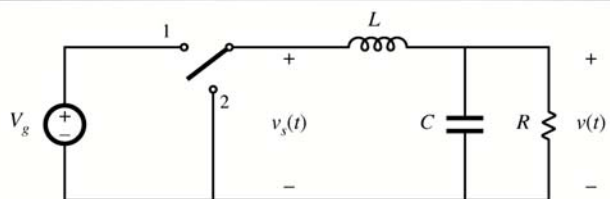
Insertion of low-pass filter to remove switching harmonics and pass only dc component



$$v \approx \langle v_s \rangle = DV_g$$

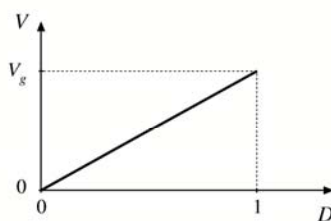

Three basic dc-dc converters

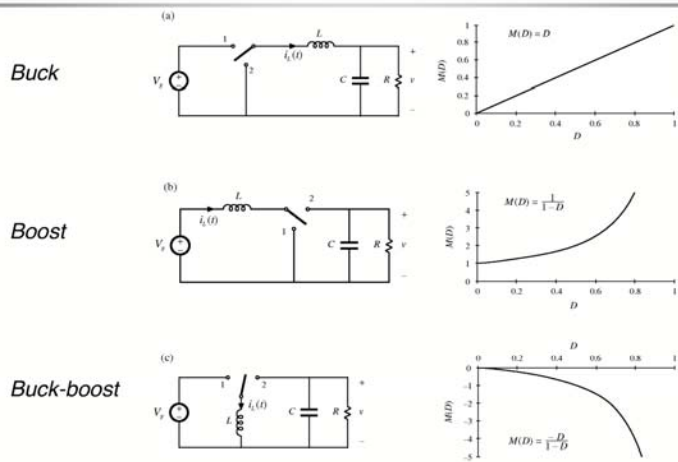


Objectives of this chapter

- Develop techniques for easily determining output voltage of an arbitrary converter circuit
- Derive the principles of *inductor volt-second balance* and *capacitor charge (amp-second) balance*
- Introduce the key *small ripple approximation*
- Develop simple methods for selecting filter element values
- Illustrate via examples

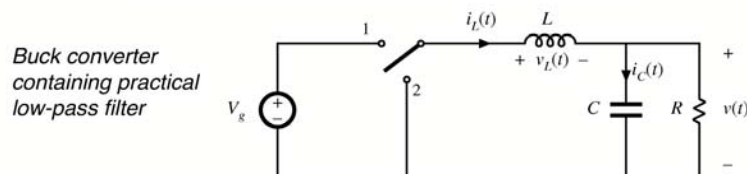
2.2. Inductor volt-second balance, capacitor charge balance, and the small ripple approximation

Actual output voltage waveform, buck converter




Actual output voltage waveform

$$v(t) = V + v_{\text{ripple}}(t)$$

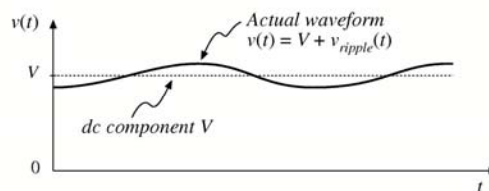

The small ripple approximation

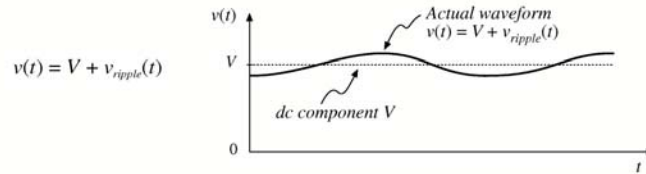


In a well-designed converter, the output voltage ripple is small. Hence, the waveforms can be easily determined by ignoring the ripple:

$$|v_{ripple}| \ll V$$

$$v(t) \approx V$$

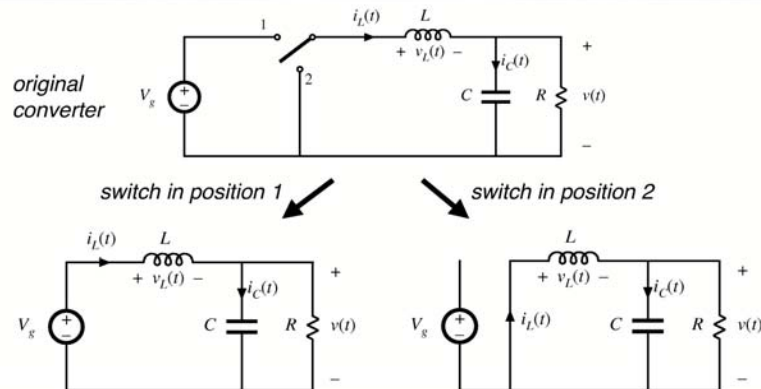
Buck converter analysis: inductor current waveform



Inductor voltage and current Subinterval 1: switch in position 1

Inductor voltage

Small ripple approximation:

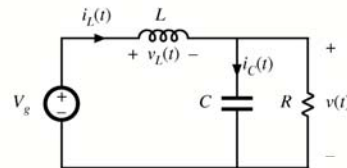


Solve for the slope:



Inductor voltage and current Subinterval 2: switch in position 2

Inductor voltage


Small ripple approximation:

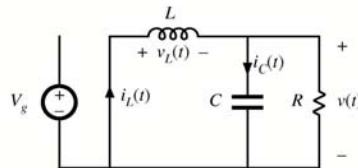

Inductor Voltage and Current Waveforms

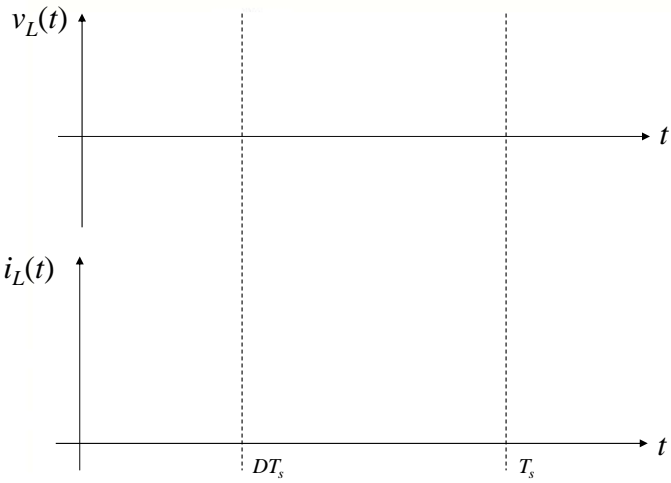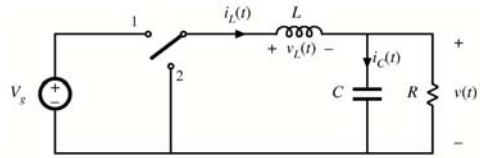

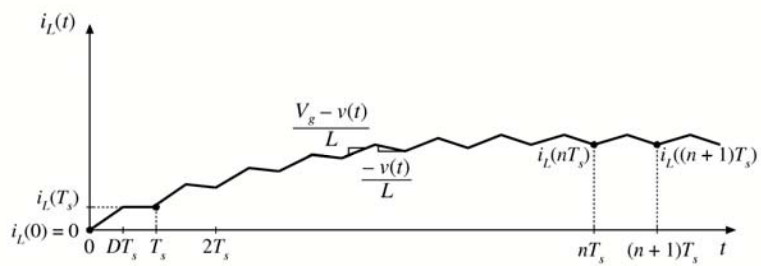
Inductor current waveform during turn-on transient



When the converter operates in equilibrium:

$$i_L((n+1)T_s) = i_L(nT_s)$$

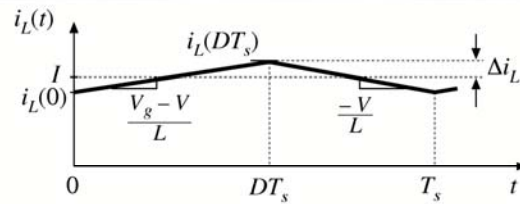Determination of inductor current ripple magnitude



(change in i_L) = (slope)(length of subinterval)

$$(2\Delta i_L) = \left(\frac{V_g - V}{L}\right)(DT_s)$$

$$\Rightarrow \Delta i_L = \frac{V_g - V}{2L} DT_s \quad L = \frac{V_g - V}{2\Delta i_L} DT_s$$

The principle of inductor volt-second balance: Derivation

Inductor defining relation:

$$v_L(t) = L \frac{di_L(t)}{dt}$$

Integrate over one complete switching period:

$$i_L(T_s) - i_L(0) = \frac{1}{L} \int_0^{T_s} v_L(t) dt$$

In periodic steady state, the net change in inductor current is zero:

$$0 = \int_0^{T_s} v_L(t) dt$$


Hence, the total area (or volt-seconds) under the inductor voltage waveform is zero whenever the converter operates in steady state.

An equivalent form:

$$0 = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = \langle v_L \rangle$$

The average inductor voltage is zero in steady state.

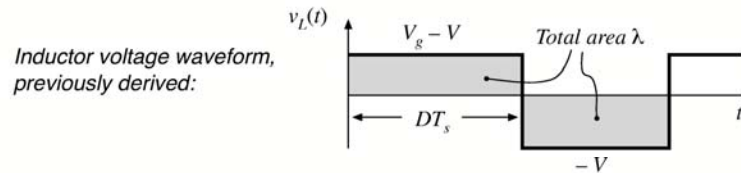Inductor volt-second balance: Buck converter example



Integral of voltage waveform is area of rectangles:

$$\lambda = \int_0^{T_s} v_L(t) dt = (V_g - V)(DT_s) + (-V)(D'T_s)$$

Average voltage is

$$\langle v_L \rangle = \frac{\lambda}{T_s} = D(V_g - V) + D'(-V)$$

Equate to zero and solve for V :

$$0 = DV_g - (D + D')V = DV_g - V \quad \Rightarrow \quad V = DV_g$$

The principle of capacitor charge balance: Derivation

Capacitor defining relation:

$$i_c(t) = C \frac{dv_c(t)}{dt}$$

Integrate over one complete switching period:

$$v_c(T_s) - v_c(0) = \frac{1}{C} \int_0^{T_s} i_c(t) dt$$


In periodic steady state, the net change in capacitor voltage is zero:

$$0 = \frac{1}{T_s} \int_0^{T_s} i_c(t) dt = \langle i_c \rangle$$


Hence, the total area (or charge) under the capacitor current waveform is zero whenever the converter operates in steady state. The average capacitor current is then zero.

2.3 Boost converter example

Boost converter
with ideal switch

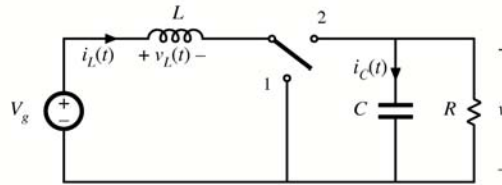

Realization using
power MOSFET
and diode

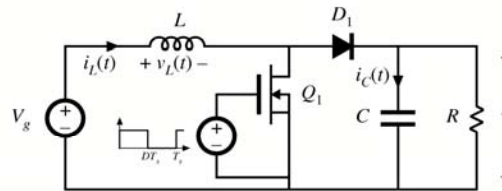

Boost converter analysis

