
Lecture 4: Steady-State Averaged Modeling

ECE 481: Power Electronics


Prof. Daniel Costinett

Department of Electrical Engineering and Computer Science
University of Tennessee Knoxville
Fall 2013

Chapter 3. Steady-State Equivalent Circuit Modeling, Losses, and Efficiency


- 3.1. The dc transformer model
- 3.2. Inclusion of inductor copper loss
- 3.3. Construction of equivalent circuit model
- 3.4. How to obtain the input port of the model
- 3.5. Example: inclusion of semiconductor conduction losses in the boost converter model
- 3.6. Summary of key points

Ideal Transformer Model

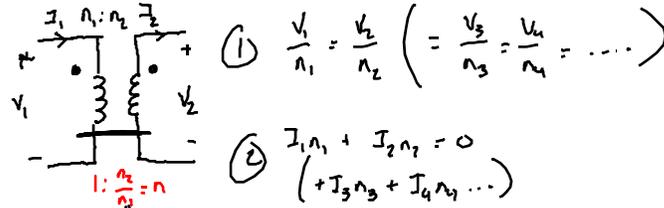

Dot Notation

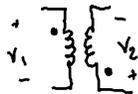- Pos. term of voltage
- Current "into" one dot comes "out" the other



① $V_2 = n V_1$

② $I_2 = \frac{1}{n} I_1$


$P_1 = V_1 I_1$

$P_2 = V_2 I_2$


$P_2 = n V_1 \frac{1}{n} I_1$

$P_2 = V_1 I_1 = P_1$


Simplifying Circuits With Ideal XF

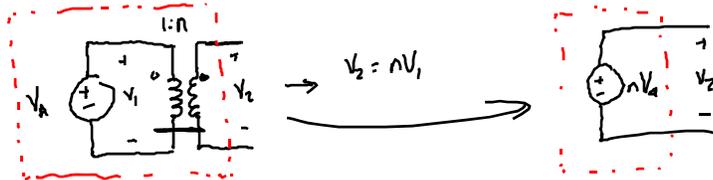

"Pushing" or "reflecting" through a XF

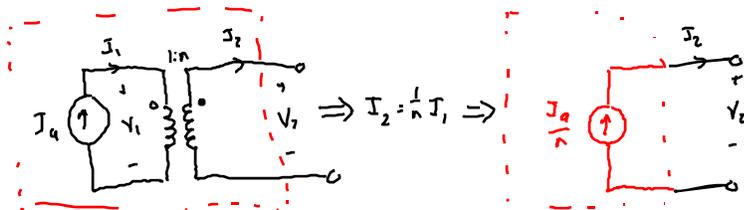

Simplifying Circuits With Ideal XF

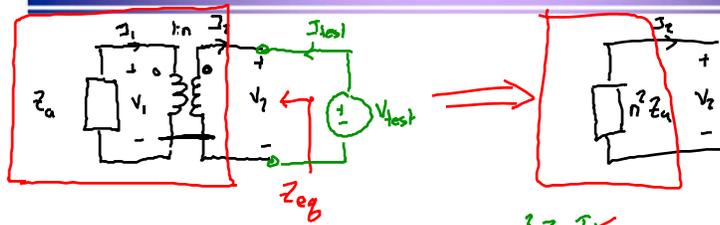

$$Z_{eq} = \frac{V_{test}}{I_{test}}$$

$$Z_{eq} = \frac{n^2 Z_a I_{test}}{I_{test}}$$

$$I_2 = -I_{test}$$

$$I_1 = n I_2 = -n I_{test}$$



$$V_1 = -I_1 Z_a = Z_a n I_{test}$$

$$V_2 = n V_1 = n^2 Z_a I_{test}$$

$$V_2 = V_{test}$$

$$Z_{eq} = n^2 Z_a$$

Simplifying Circuits With Ideal XF

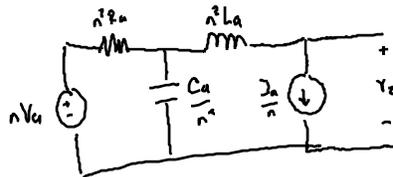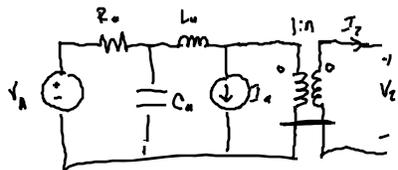

$$Z_c = \frac{1}{s C_a}$$

$$Z_c' = \frac{n^2}{s C_a} \Rightarrow \frac{C_a}{n^2}$$

3.1. The dc transformer model


Basic equations of an ideal dc-dc converter:

$$P_{in} = P_{out} \quad (\eta = 100\%)$$

$$V_g I_g = V I$$

$V = M(D) V_g$
 $I_g = M(D) I$

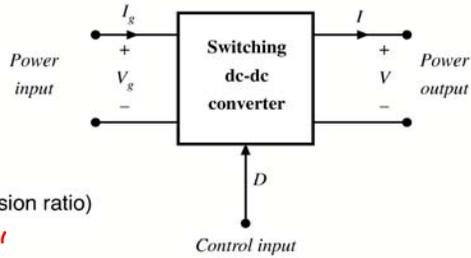
(ideal conversion ratio)
 $V_2 = n V_1$
 $I_2 = \frac{1}{n} I_1$
 $I_1 = n I_2$




These equations are valid in steady-state. During transients, energy storage within filter elements may cause $P_{in} \neq P_{out}$

Equivalent circuits corresponding to ideal dc-dc converter equations
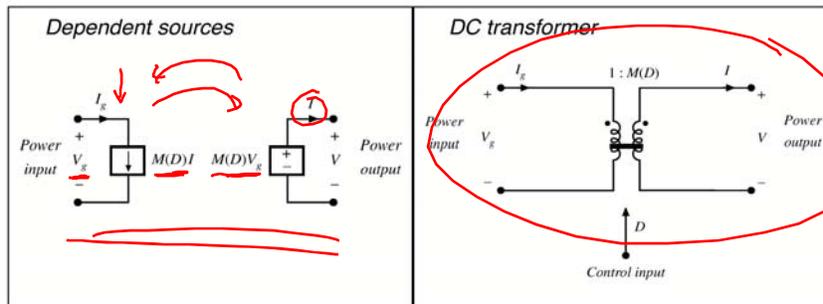
$$P_{in} = P_{out} \quad V_g I_g = V I \quad \boxed{V = M(D) V_g \quad I_g = M(D) I}$$



The DC transformer model

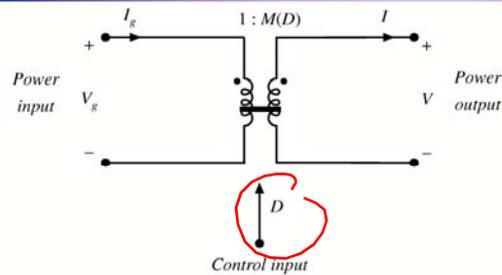


Models basic properties of ideal dc-dc converter:

- conversion of dc voltages and currents, ideally with 100% efficiency
- conversion ratio M = turns ratio controllable via duty cycle ratio


- Solid line denotes ideal transformer model, capable of passing dc voltages and currents

~~*~~ Time-invariant model (no switching) which can be solved to find dc components of converter waveforms


Example: use of the DC transformer model

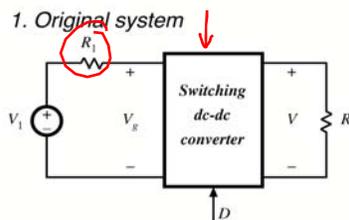

2. Insert dc transformer model

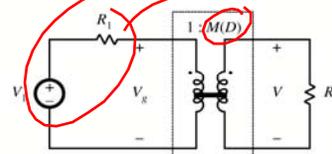

3. Push source through transformer

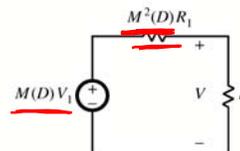

4. Solve circuit

$$V = M(D) V_1 \frac{R}{R + M^2(D) R_1}$$


3.2. Inclusion of inductor copper loss

Dc transformer model can be extended, to include converter nonidealities.

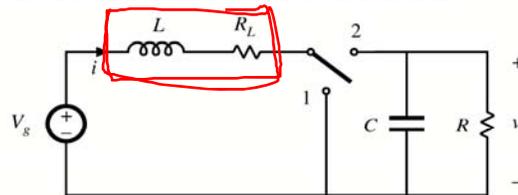
Example: inductor copper loss (resistance of winding):



Insert this inductor model into boost converter circuit:




Analysis of nonideal boost converter

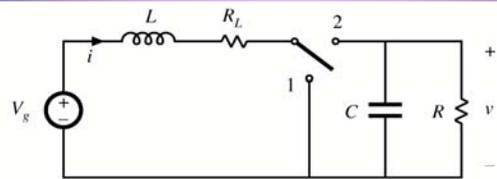


switch in position 1

switch in position 2

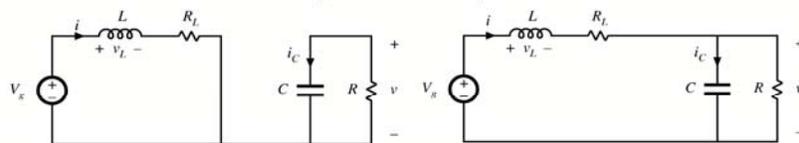

Nonideal Boost Converter

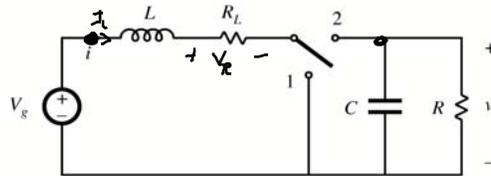

$$\langle v_L \rangle = \phi = V_g - I_L R_L - D'V$$


$$\langle i_C \rangle = \phi = D'I_L - \frac{V}{R}$$

Circuit equations, switch in position 1

Inductor current and capacitor voltage:

$$v_L(t) = V_g - i(t) R_L$$

$$i_C(t) = -v(t) / R$$

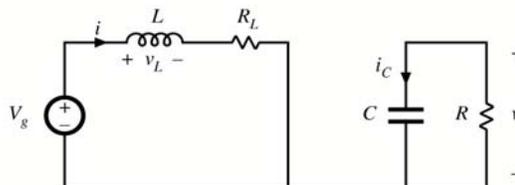


Small ripple approximation:

$$v_L(t) = V_g - I R_L$$

$$i_C(t) = -V / R$$

Circuit equations, switch in position 2

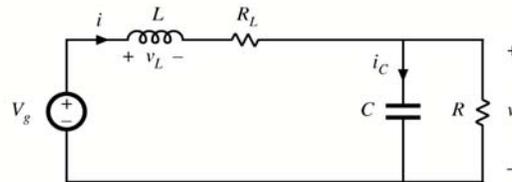

$$v_L(t) = V_g - i(t) R_L - v(t) = V_g - I R_L - V$$

$$i_C(t) = i(t) - v(t) / R = I - V / R$$

Inductor voltage and capacitor current waveforms

Average inductor voltage:

$$\langle v_L(t) \rangle = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt$$

$$= D(V_g - I R_L) + D'(V_g - I R_L - V)$$

Inductor volt-second balance:


$$0 = V_g - I R_L - D'V$$

Average capacitor current:

$$\langle i_C(t) \rangle = D(-V/R) + D'(I - V/R)$$

Capacitor charge balance:

$$0 = D'I - V/R$$

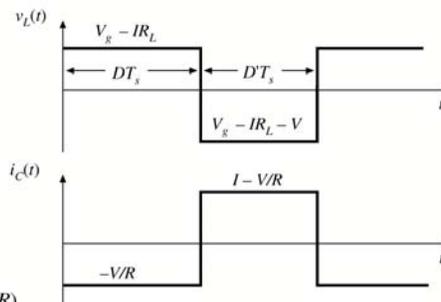

Solution for output voltage

We now have two equations and two unknowns:

$$0 = V_g - I R_L - D'V$$


$$0 = D'I - V/R$$

Eliminate I and solve for V :

$$M(D) = \frac{V}{V_g} = \frac{1}{D'} \frac{1}{(1 + R_L / D'^2 R)}$$

$$M = M_{ideal} \left(1 + \frac{R_L}{D'^2 R} \right)^{-1}$$

$$= ?$$

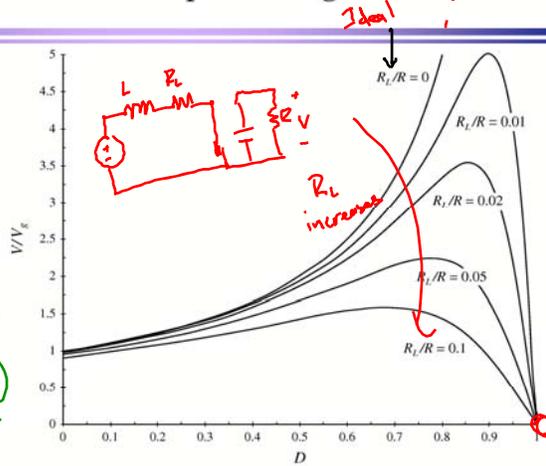


3.3. Construction of equivalent circuit model

Results of previous section (derived via inductor volt-sec balance and capacitor charge balance):

$$\textcircled{1} \langle v_L \rangle = 0 = V_g - I R_L - D'V \quad \rightarrow \text{KVL around } I_L \text{ loop}$$

$$\textcircled{2} \langle i_C \rangle = 0 = D'I - V/R \quad \rightarrow \text{KCL at node } V_C$$

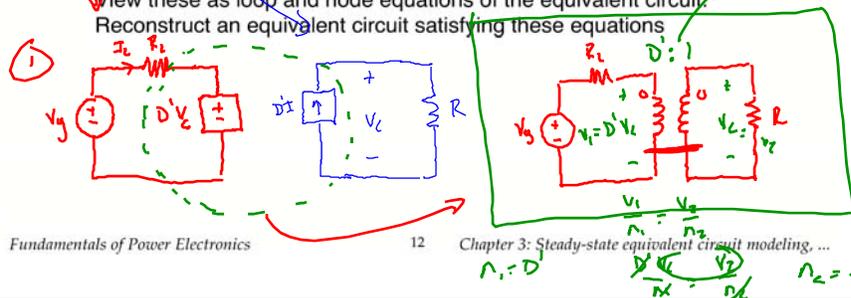
View these as loop and node equations of the equivalent circuit. Reconstruct an equivalent circuit satisfying these equations



Inductor voltage equation

$$\langle v_L \rangle = 0 = V_g - I R_L - D'V$$

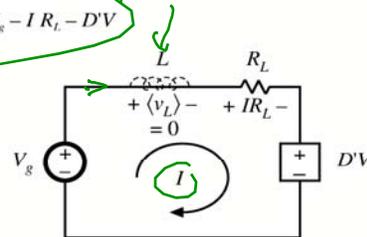- Derived via Kirchhoff's voltage law, to find the inductor voltage during each subinterval
- Average inductor voltage then set to zero
- This is a loop equation: the dc components of voltage around a loop containing the inductor sum to zero




- IR_L term: voltage across resistor of value R_L having current I
- $D'V$ term: for now, leave as dependent source

Capacitor current equation

$$\langle i_c \rangle = 0 = D'I - V/R$$

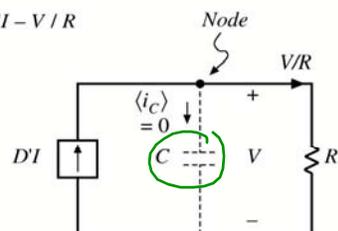
- Derived via Kirchhoff's current law, to find the capacitor current during each subinterval
- Average capacitor current then set to zero
- This is a node equation: the dc components of current flowing into a node connected to the capacitor sum to zero




- V/R term: current through load resistor of value R having voltage V
- $D'I$ term: for now, leave as dependent source

Complete equivalent circuit


The two circuits, drawn together:

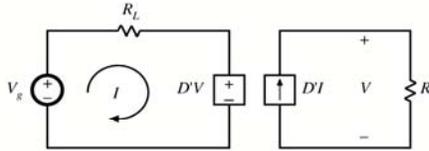

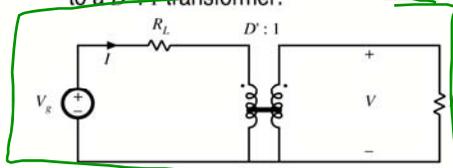The dependent sources are equivalent to a $D': 1$ transformer.




Dependent sources and transformers

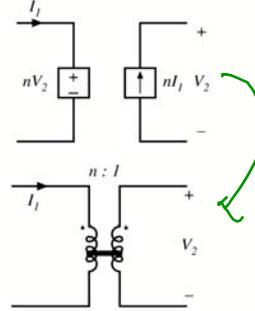


- sources have same coefficient
- reciprocal voltage/current dependence

Solution of equivalent circuit

Converter equivalent circuit

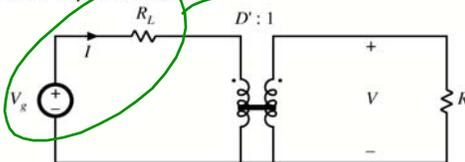

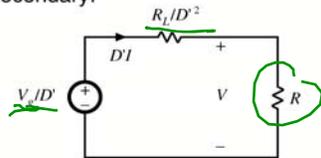Refer all elements to transformer secondary:




Solution for output voltage using voltage divider formula:

$$V = \frac{V_g}{D'} \frac{R}{R + \frac{R_L}{D'^2}} = \frac{V_g}{D'} \frac{1}{1 + \frac{R_L}{D'^2 R}}$$


$$M = \frac{1}{D'} \left(\frac{1}{1 + \frac{R_L}{D'^2 R}} \right) = M_{ideal} \eta$$

Solution for input (inductor) current

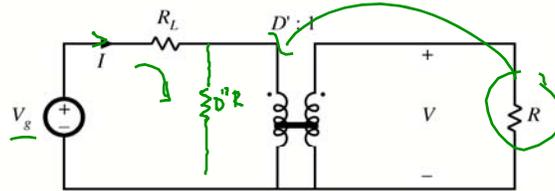

$$I = \frac{V_g}{D^2 R + R_L} = \frac{V_g}{D^2} \frac{1}{1 + \frac{R_L}{D^2 R}}$$

Solution for converter efficiency

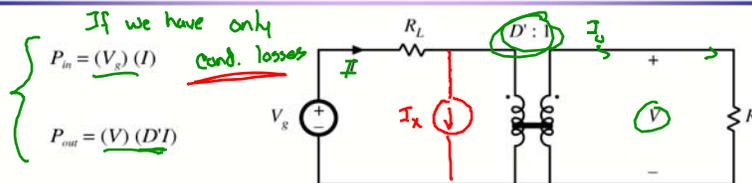

$$P_{in} = (V_g)(I)$$

cond. losses


$$P_{out} = (V)(D'I)$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{(V)(D'I)}{(V_g)(I)} = \frac{V}{V_g} D' = M \frac{1}{M_{ideal}}$$

$$\eta = \frac{1}{1 + \frac{R_L}{D^2 R}} \rightarrow M = M_{ideal} ?$$

Efficiency, for various values of R_L

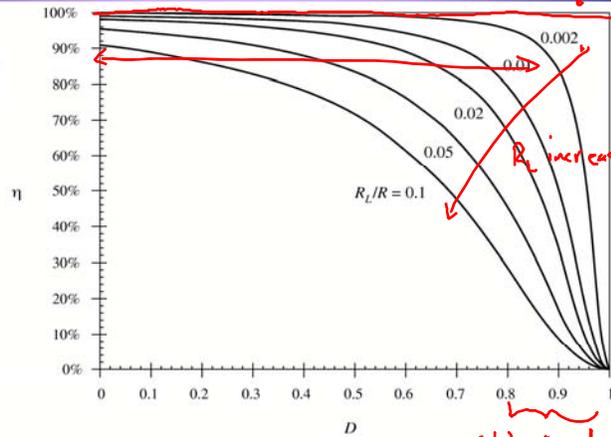
$$\eta = \frac{1}{1 + \frac{R_L}{D^2 R}}$$



3.4. How to obtain the input port of the model

Buck converter example — use procedure of previous section to derive equivalent circuit


- ① $i_g = i_L$
- ② $i_g = \phi$

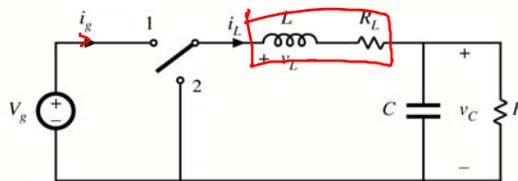

Average inductor voltage and capacitor current:

$$\langle v_L \rangle = 0 = DV_g - I_L R_L - V_C \quad \langle i_C \rangle = 0 = I_L - V_C / R$$

Construct equivalent circuit as usual

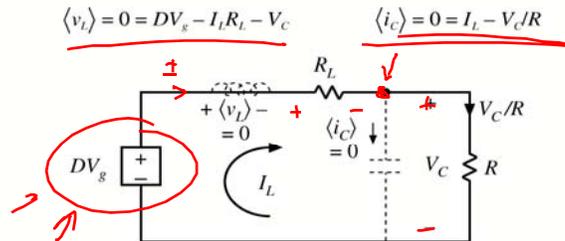


What happened to the transformer?

- Need another equation

Add 1 eq: Averaging of input part

Modeling the converter input port

Input current waveform $i_g(t)$:

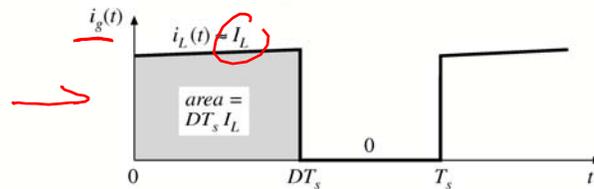


Dc component (average value) of $i_g(t)$ is

$$I_g = \frac{1}{T_s} \int_0^{T_s} i_g(t) dt = DI_L \rightarrow \boxed{I_g = DI_L}$$


Input port equivalent circuit
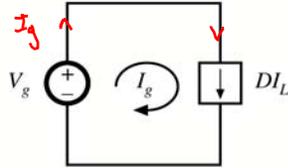
$$I_g = \frac{1}{T_s} \int_0^{T_s} i_g(t) dt = DI_L \quad I_g = DI_L$$




Complete equivalent circuit, buck converter

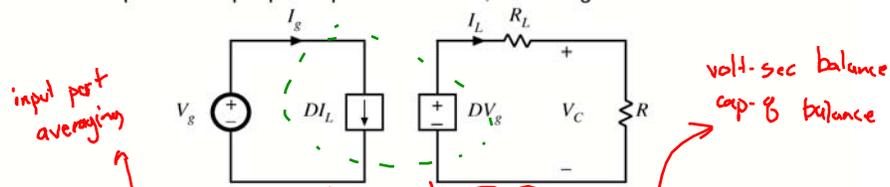Input and output port equivalent circuits, drawn together:




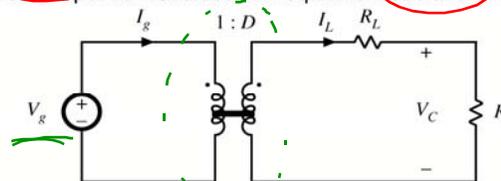Replace dependent sources with equivalent dc transformer:



3.5. Example: inclusion of semiconductor conduction losses in the boost converter model

Boost converter example

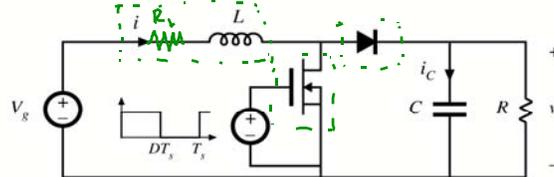

Models of on-state semiconductor devices:

MOSFET: on-resistance R_{on}

Diode: constant forward voltage V_D plus on-resistance R_D

Insert these models into subinterval circuits

Modeling of component conduction losses

