


# Lecture 5: Semiconductor Device Implementation

ECE 481: Power Electronics


Prof. Daniel Costinett

Department of Electrical Engineering and Computer Science  
 University of Tennessee Knoxville  
 Fall 2013

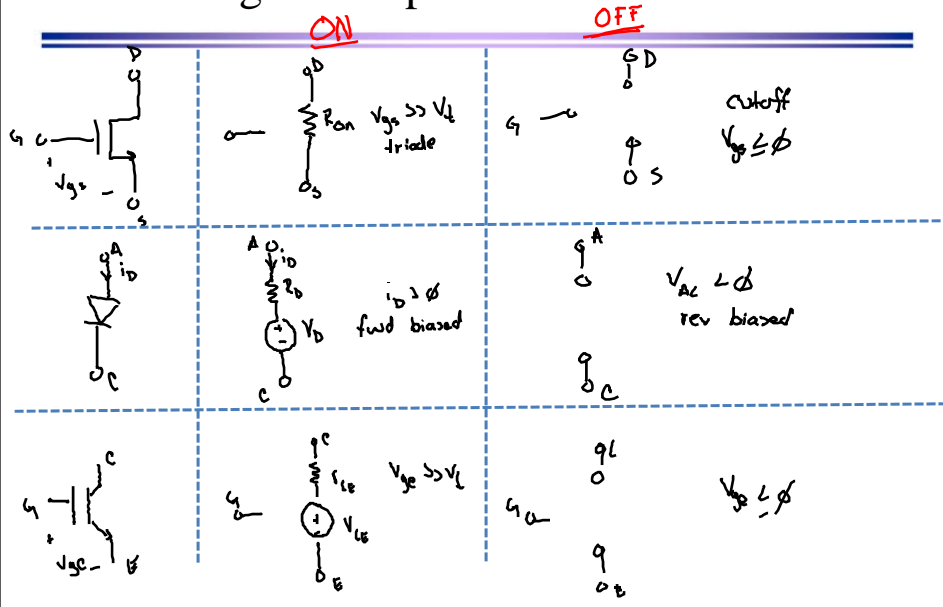
## Modeling of component conduction losses


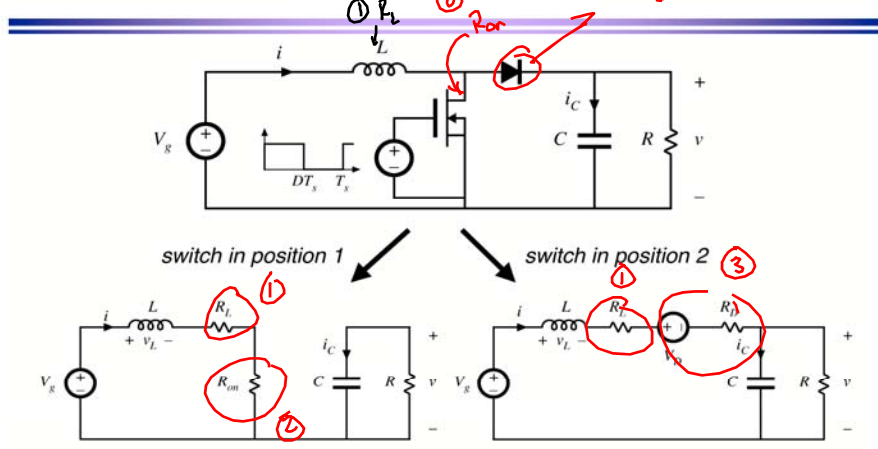
## Boost converter example: circuits during subintervals 1 and 2


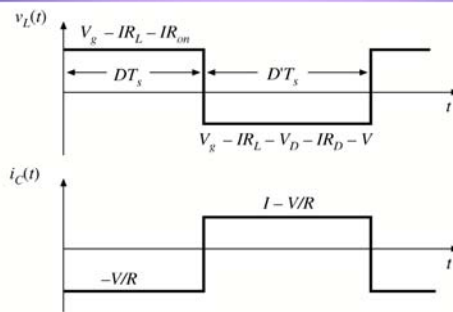
## Average inductor voltage and capacitor current




$$\langle v_L \rangle = D(V_g - IR_L - IR_{on}) + D'(V_g - IR_L - V_D - IR_D - V) = 0$$


$$\langle i_C \rangle = D(-V/R) + D'(I - V/R) = 0$$
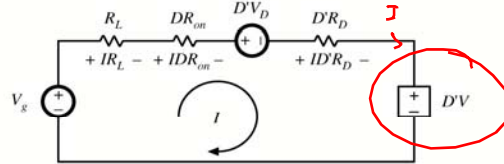
## Construction of equivalent circuits



$$V_g - IR_L - IDR_{on} - D'V_D - ID'R_D - D'V = 0$$



$$D'I - V/R = 0$$

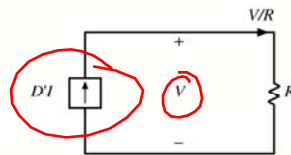


## Complete equivalent circuit

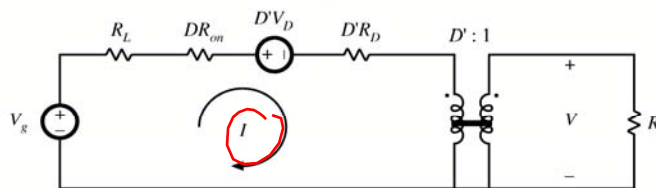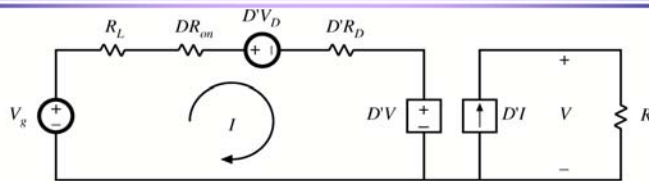

$$DV = \frac{D^2 R}{(1+R_2)} (V_g - DV_D)$$

### Solution for output voltage

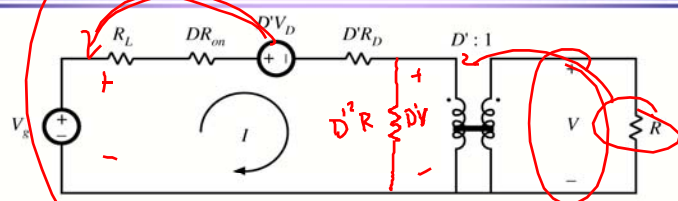

$$V = \left(\frac{1}{D'}\right) (V_g - DV_D) \left( \frac{D^2 R}{D^2 R + R_L + DR_{on} + D'R_D} \right)$$

$$\frac{V}{V_g} = \left(\frac{1}{D'}\right) \left(1 - \frac{DV_D}{V_g}\right) \left( \frac{1}{1 + \frac{R_L + DR_{on} + D'R_D}{D^2 R}} \right)$$


$$M = M_{ideal}$$

true if only cond. losses considered

### Solution for converter efficiency

$$P_{in} = (V_g)(I)$$

$$P_{out} = (V)(D'I)$$

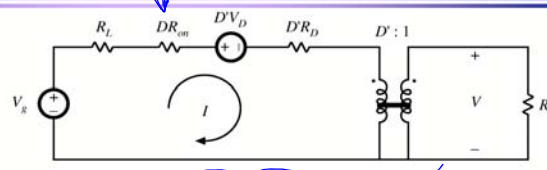

$$\eta = D' \frac{V}{V_g} = \frac{\left(1 - \frac{DV_D}{V_g}\right)}{\left(1 + \frac{R_L + DR_{on} + D'R_D}{D^2 R}\right)}$$

$$P_{mos} = I^2 (DR_{on}) \rightarrow \text{Avg current}$$

$$P_{msw(ac)} = I_{rms}^2 R_{on} \rightarrow \text{RMS current}$$

Conditions for high efficiency:

$$V_g D' \gg V_D$$


$$D^2 R \gg R_L + DR_{on} + D'R_D$$

$$\Delta i_L = \phi$$
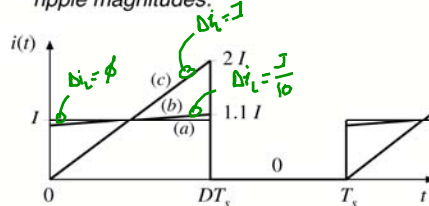
## Accuracy of the averaged equivalent circuit in prediction of losses

- Model uses average currents and voltages
- To correctly predict power loss in a resistor, use rms values
- Result is the same, provided ripple is small

MOSFET current waveforms, for various ripple magnitudes:



Inductor current ripple	MOSFET rms current	Average power loss in $R_{on}$
(a) $\Delta i = 0$	$I \sqrt{D}$	$D I^2 R_{on}$ → 0% error
(b) $\Delta i = 0.1 I$ 10%	$(1.00167) I \sqrt{D}$	$(1.0033) D I^2 R_{on}$ → 0.33% error
(c) $\Delta i = I$ 100%	$(1.155) I \sqrt{D}$	$(1.3333) D I^2 R_{on}$ → 33% error

## Summary of chapter 3

1. The dc transformer model represents the primary functions of any dc-dc converter: transformation of dc voltage and current levels, ideally with 100% efficiency, and control of the conversion ratio  $M$  via the duty cycle  $D$ . This model can be easily manipulated and solved using familiar techniques of conventional circuit analysis. *keeps ratio in XF*
2. The model can be refined to account for loss elements such as inductor winding resistance and semiconductor on-resistances and forward voltage drops. The refined model predicts the voltages, currents, and efficiency of practical nonideal converters.
3. In general, the dc equivalent circuit for a converter can be derived from the inductor volt-second balance and capacitor charge balance equations. Equivalent circuits are constructed whose loop and node equations coincide with the volt-second and charge balance equations. In converters having a pulsating input current, an additional equation is needed to model the converter input port; this equation may be obtained by averaging the converter input current.

# Chapter 4. Switch Realization

## 4.1. Switch applications

Single-, two-, and four-quadrant switches. Synchronous rectifiers

## 4.2. A brief survey of power semiconductor devices

Power diodes, MOSFETs, BJTs, IGBTs, and thyristors


## 4.3. Switching loss

Transistor switching with clamped inductive load. Diode recovered charge. Stray capacitances and inductances, and ringing. Efficiency vs. switching frequency.


## 4.4. Summary of key points
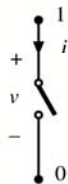
# SPST (single-pole single-throw) switches

SPST switch, with voltage and current polarities defined



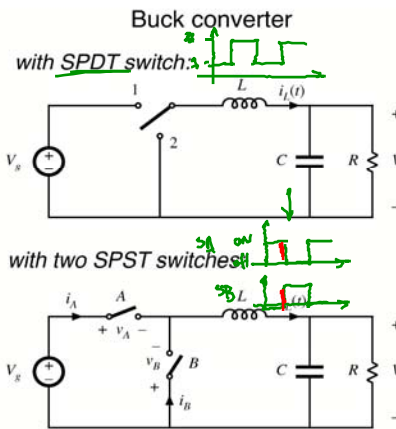All power semiconductor devices function as SPST switches.




"Cross-conduction"  
"Shoot-through I"


## Realization of SPDT switch using two SPST switches

- A nontrivial step: two SPST switches are not exactly equivalent to one SPDT switch
- It is possible for both SPST switches to be simultaneously ON or OFF
- Behavior of converter is then significantly modified  
— discontinuous conduction modes (chapter 5)
- Conducting state of SPST switch may depend on applied voltage or current — for example: diode

## Quadrants of SPST switch operation

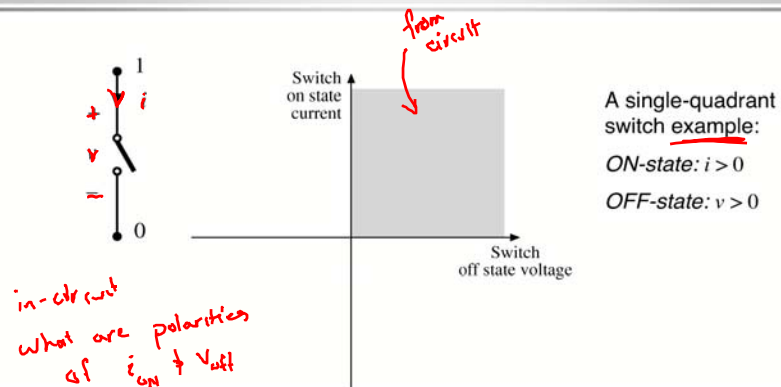

## Some basic switch applications

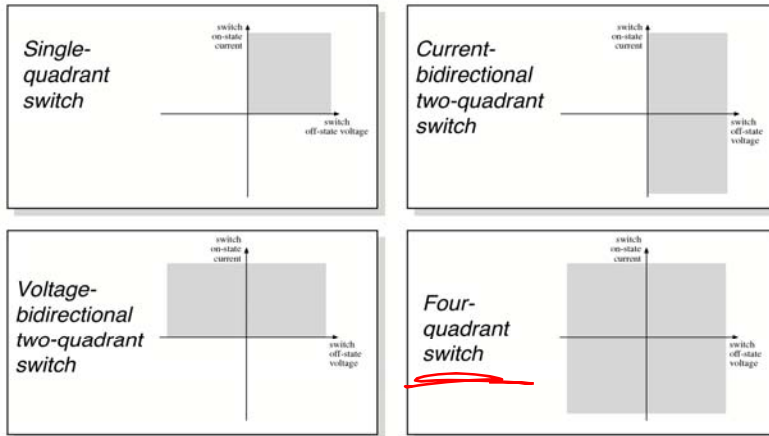


Fundamentals of Power Electronics

5

Chapter 4: Switch realization

### 4.1.1. Single-quadrant switches

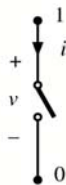

**Active switch:** Switch state is controlled exclusively by a third terminal (control terminal). *e.g. transistor*

**Passive switch:** Switch state is controlled by the applied current and/or voltage at terminals 1 and 2. *Diode*

**SCR:** A special case — turn-on transition is active, while turn-off transition is passive.

**Single-quadrant switch:** on-state  $i(t)$  and off-state  $v(t)$  are unipolar.


Fundamentals of Power Electronics

6


Chapter 4: Switch realization



## The diode

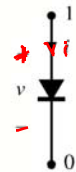



Symbol

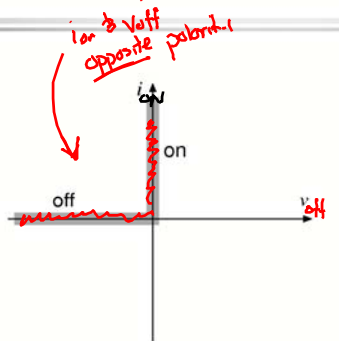


instantaneous  $i$ - $v$  characteristic

- A passive switch
- Single-quadrant switch:
- can conduct positive on-state current
- can block negative off-state voltage
- provided that the intended on-state and off-state operating points lie on the diode  $i$ - $v$  characteristic, then switch can be realized using a diode
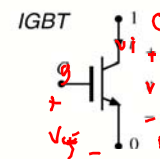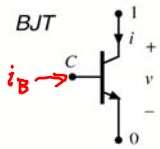
## The Bipolar Junction Transistor (BJT) and the Insulated Gate Bipolar Transistor (IGBT)




instantaneous  $i$ - $v$  characteristic

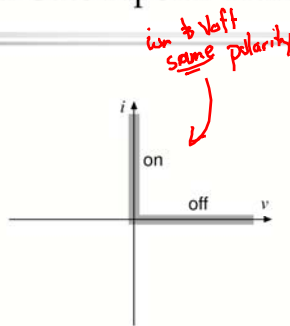

- An active switch, controlled by terminal C
- Single-quadrant switch:
- can conduct positive on-state current
- can block positive off-state voltage
- provided that the intended on-state and off-state operating points lie on the transistor  $i$ - $v$  characteristic, then switch can be realized using a BJT or IGBT
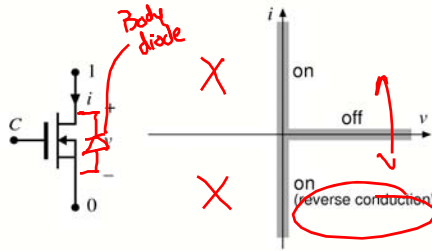
## The Metal-Oxide Semiconductor Field Effect Transistor (MOSFET)




Symbol      instantaneous  $i-v$  characteristic

- An active switch, controlled by terminal C
- Normally operated as single-quadrant switch:
- can conduct positive on-state current (can also conduct negative current in some circumstances)
- can block positive off-state voltage
- provided that the intended on-state and off-state operating points lie on the MOSFET  $i-v$  characteristic, then switch can be realized using a MOSFET


## Realization of switch using transistors and diodes

Buck converter example

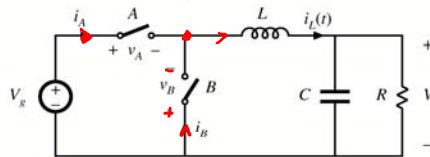


- ① A on B off  
 $i_A = i_L > 0$   
 $v_B = -V_g < 0$
- ② A off B on  
 $v_A = V_g > 0$   
 $i_B = i_L > 0$

SPST switch operating points

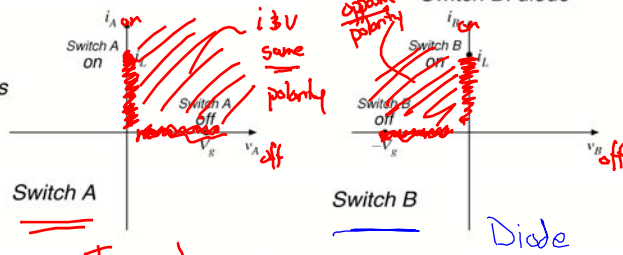


Transistor
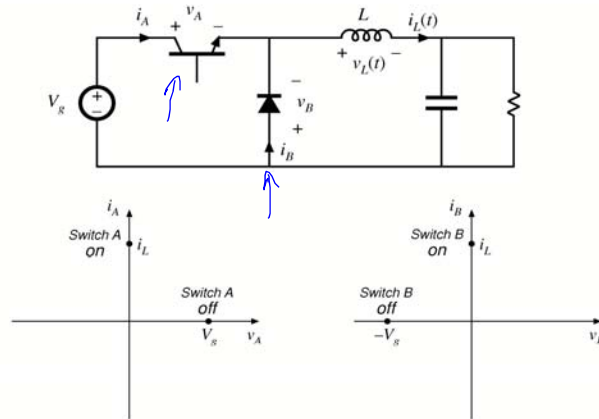
## Realization of buck converter using single-quadrant switches


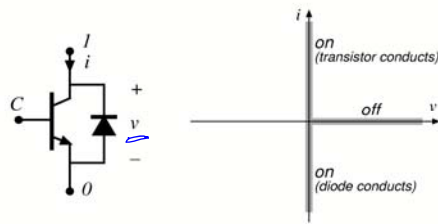
### 4.1.2. Current-bidirectional two-quadrant switches




BJT / anti-parallel diode realization


instantaneous  $i$ - $v$  characteristic

- Usually an active switch, controlled by terminal C
- Normally operated as two-quadrant switch:
- can conduct positive or negative on-state current
- can block positive off-state voltage
- provided that the intended on-state and off-state operating points lie on the composite  $i$ - $v$  characteristic, then switch can be realized as shown

## Two quadrant switches

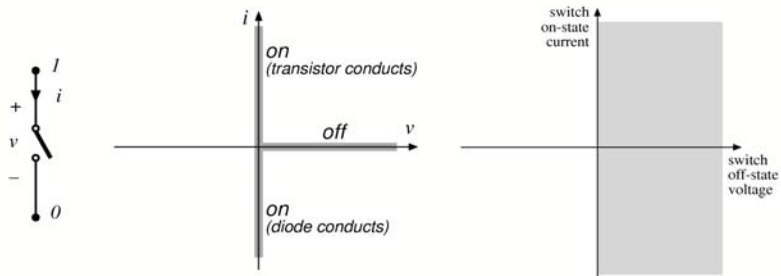


## MOSFET body diode

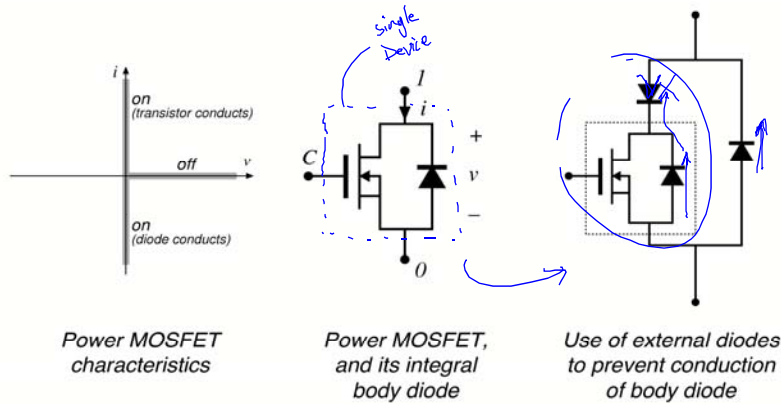


DC-AC

## A simple inverter

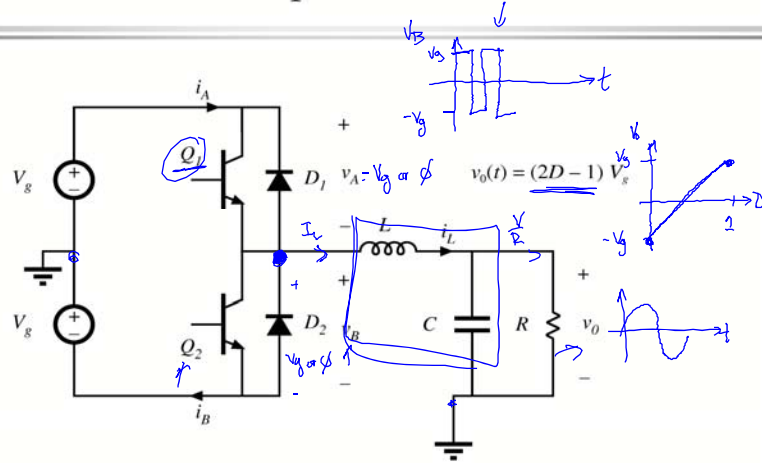

## Inverter: sinusoidal modulation of $D$

$$v_0(t) = (2D - 1)V_g$$

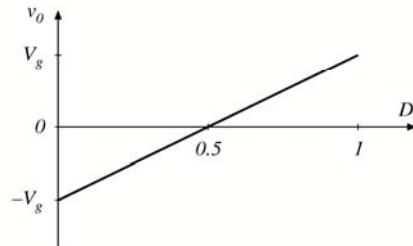

Sinusoidal modulation to produce ac output:


$$D(t) = 0.5 + D_m \sin(\omega t)$$

The resulting inductor current variation is also sinusoidal:

$$i_L(t) = \frac{v_0(t)}{R} = (2D - 1) \frac{V_g}{R}$$


Hence, current-bidirectional two-quadrant switches are required.
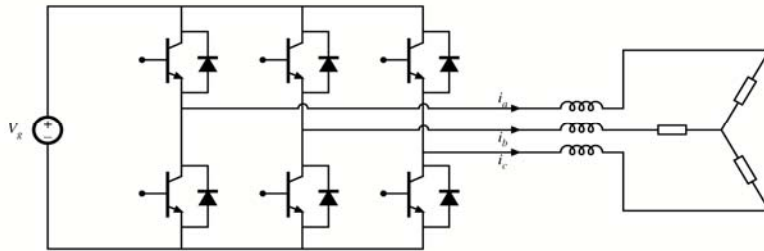
## The dc-3 $\phi$ ac voltage source inverter (VSI)




Switches must block dc input voltage, and conduct ac load current.
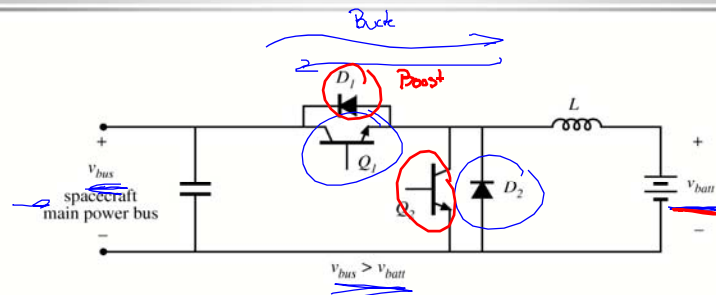
## Bidirectional battery charger/discharger




A dc-dc converter with bidirectional power flow.
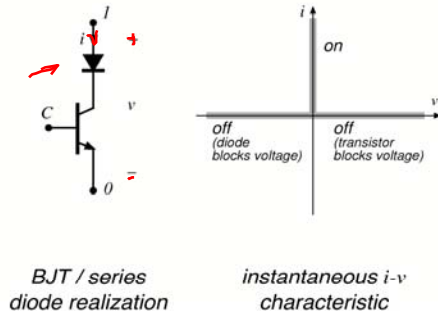
### 4.1.3. Voltage-bidirectional two-quadrant switches




- Usually an active switch, controlled by terminal C
- Normally operated as two-quadrant switch:
- can conduct positive on-state current
- can block positive or negative off-state voltage
- provided that the intended on-state and off-state operating points lie on the composite  $i-v$  characteristic, then switch can be realized as shown
- The SCR is such a device, without controlled turn-off

### Two-quadrant switches

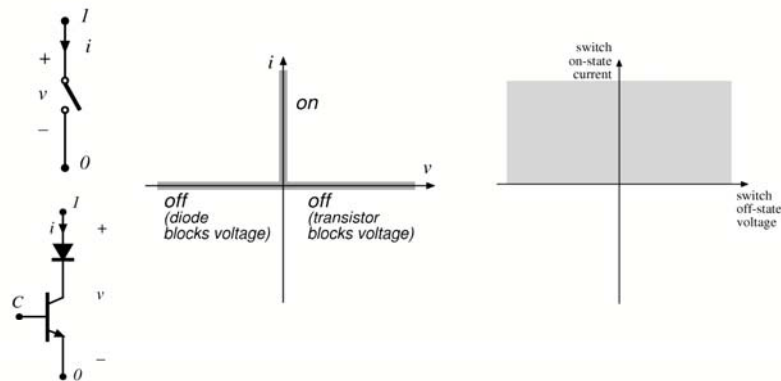


## A dc-3 $\phi$ ac buck-boost inverter

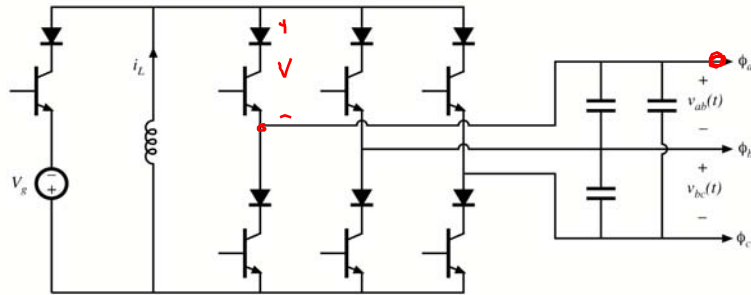

Requires voltage-bidirectional two-quadrant switches.

Another example: boost-type inverter, or current-source inverter (CSI).


### 4.1.4. Four-quadrant switches

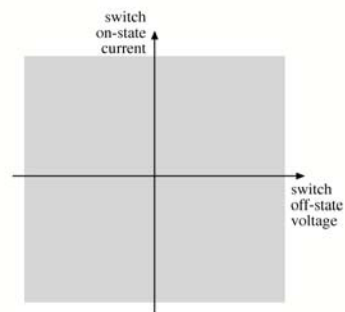


- Usually an active switch, controlled by terminal C
- can conduct positive or negative on-state current
- can block positive or negative off-state voltage


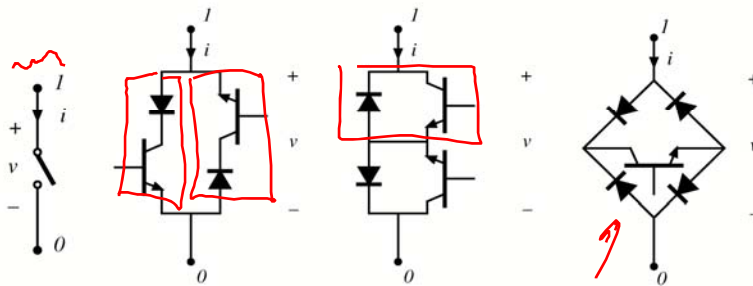
## Three ways to realize a four-quadrant switch



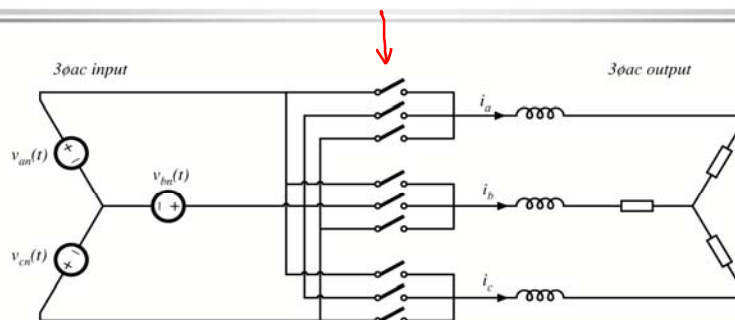
## A 3 $\phi$ ac-3 $\phi$ ac matrix converter




- All voltages and currents are ac; hence, four-quadrant switches are required.
- Requires nine four-quadrant switches
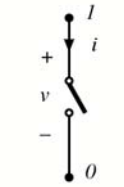
### 4.1.5. Synchronous rectifiers


Replacement of diode with a backwards-connected MOSFET, to obtain reduced conduction loss




ideal switch

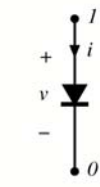

conventional diode rectifier

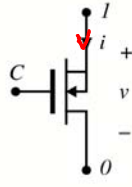


MOSFET as synchronous rectifier

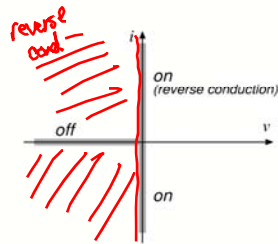

instantaneous i-v characteristic
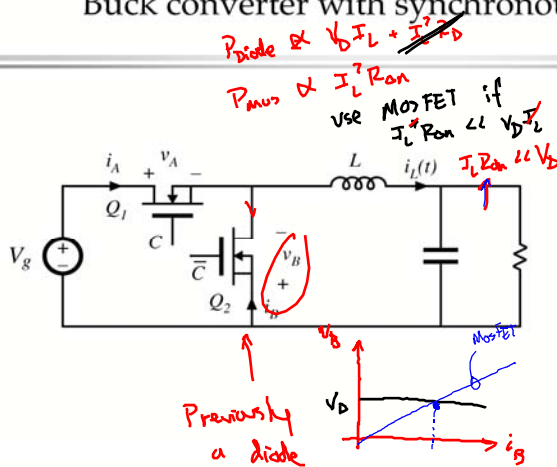
### Buck converter with synchronous rectifier



- MOSFET  $Q_2$  is controlled to turn on when diode would normally conduct
- Semiconductor conduction loss can be made arbitrarily small, by reduction of MOSFET on-resistances
- Useful in low-voltage high-current applications