
Lecture 7: MOSFET, IGBT, and Switching Loss

ECE 481: Power Electronics


Prof. Daniel Costinett

Department of Electrical Engineering and Computer Science
University of Tennessee Knoxville
Fall 2013

Announcements


- Homework #3 posted this afternoon
 - Plots in homeworks: label all salient features
 - Assignment clarity: Box answers, staple sheets, include course number
- Course E-mail list
- No office hours tomorrow
- No class next week
- Midterm Exam 1 handed out on 9/26

MOSFET On-State

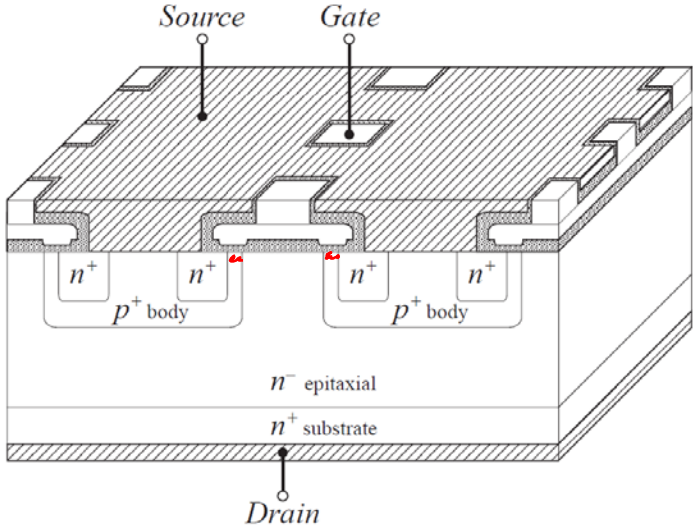


$$R_{on} = (R_s + R_{ch} + R_m + R_{epi} + R_{sub} + R_d)$$

↑ R_{ch} @ high V_{DS}

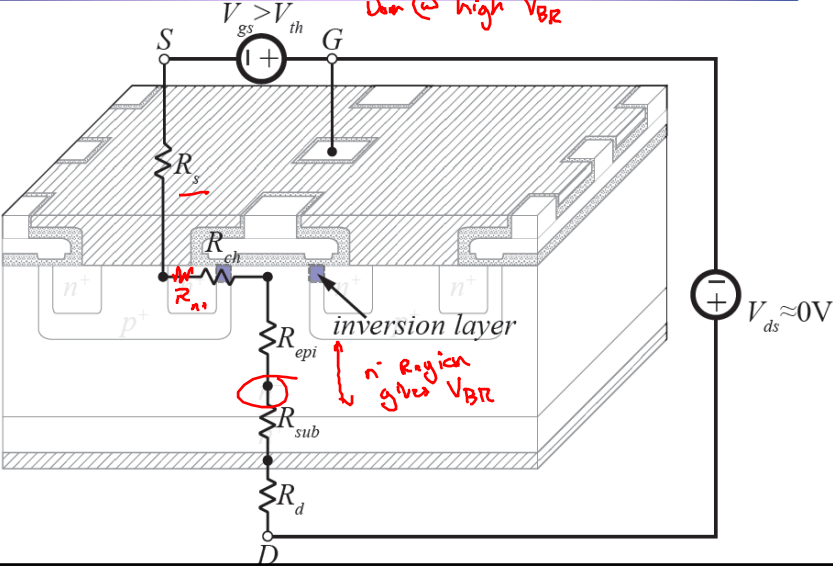

Typical MOSFET characteristics

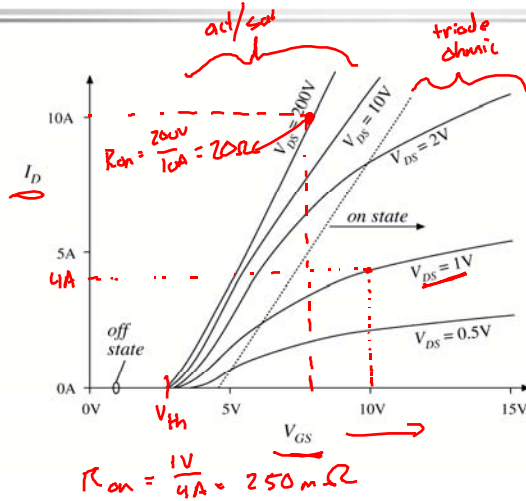

- Off state: $V_{GS} < V_{th}$
- On state: $V_{GS} \gg V_{th}$
- MOSFET can conduct peak currents well in excess of average current rating — characteristics are unchanged
- on-resistance has positive temperature coefficient, hence easy to parallel

MOSFET Datasheet



600V CoolMOS™ C6 Power Transistor

IPD60R2K0C6

1 Description

CoolMOS™ is a revolutionary technology for high voltage power MOSFETs, designed according to the superjunction (SJ) principle and pioneered by Infineon Technologies. CoolMOS™ C6 series combines the experience of the leading SJ MOSFET supplier with high class innovation. The resulting devices provide all benefits of a fast switching SJ MOSFET while not sacrificing ease of use. Extremely low switching and conduction losses make switching


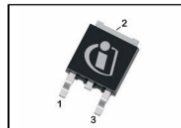
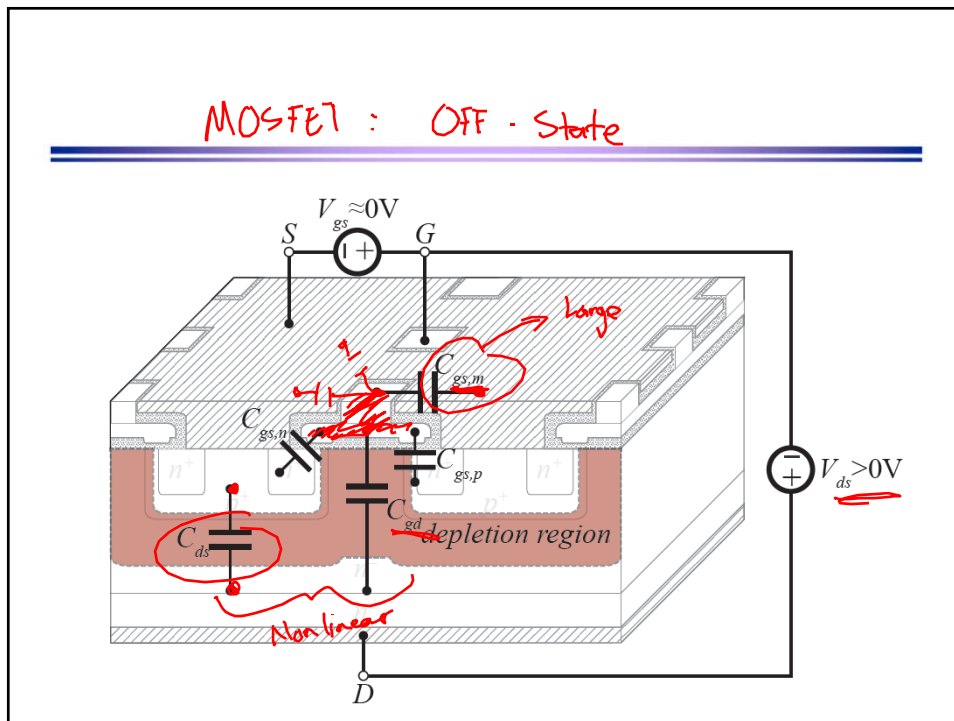




Table 1 Key Performance Parameters

Parameter	Value	Unit
$V_{DS} @ I_{T,max}$	650	V
$R_{DS(on),max}$	2.0	Ω
$Q_{g,typ}$	6.7	nC
$I_{D,pulse}$	6	A
$t_{oss} @ 400V$	0.76	μs
Body diode di/dr	500	A/ μs

Drain-source on-state resistance	$R_{DS(on)}$			Ω	$V_{GS}=10V, I_D=0.76A, T_J=25^\circ C$
		1.80	2.0		
		4.68			$V_{GS}=10V, I_D=0.76A, T_J=150^\circ C$

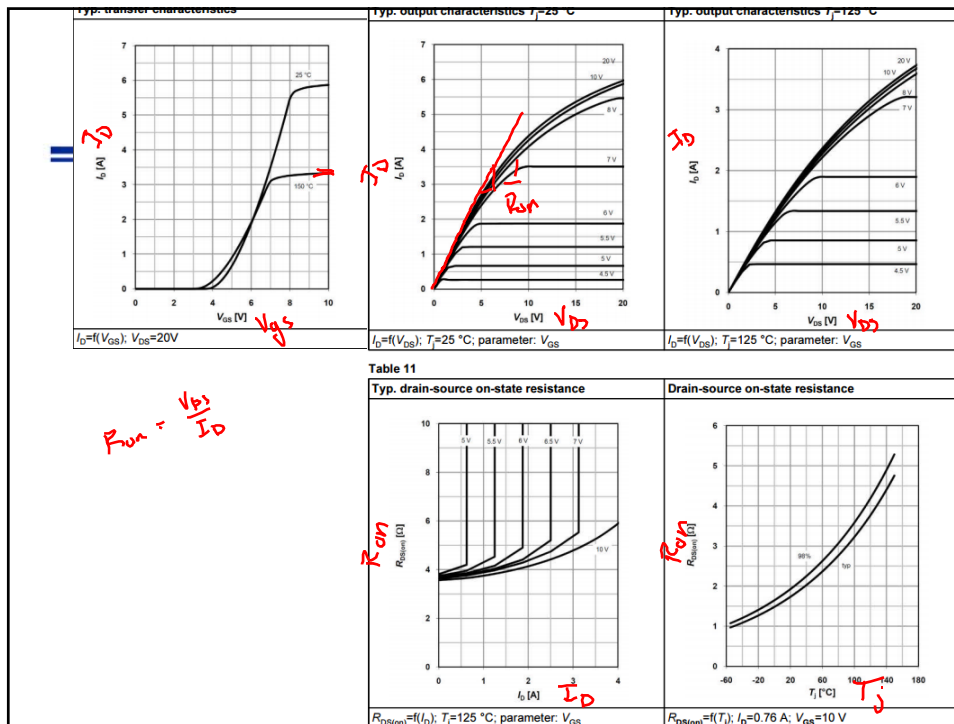

A simple MOSFET equivalent circuit

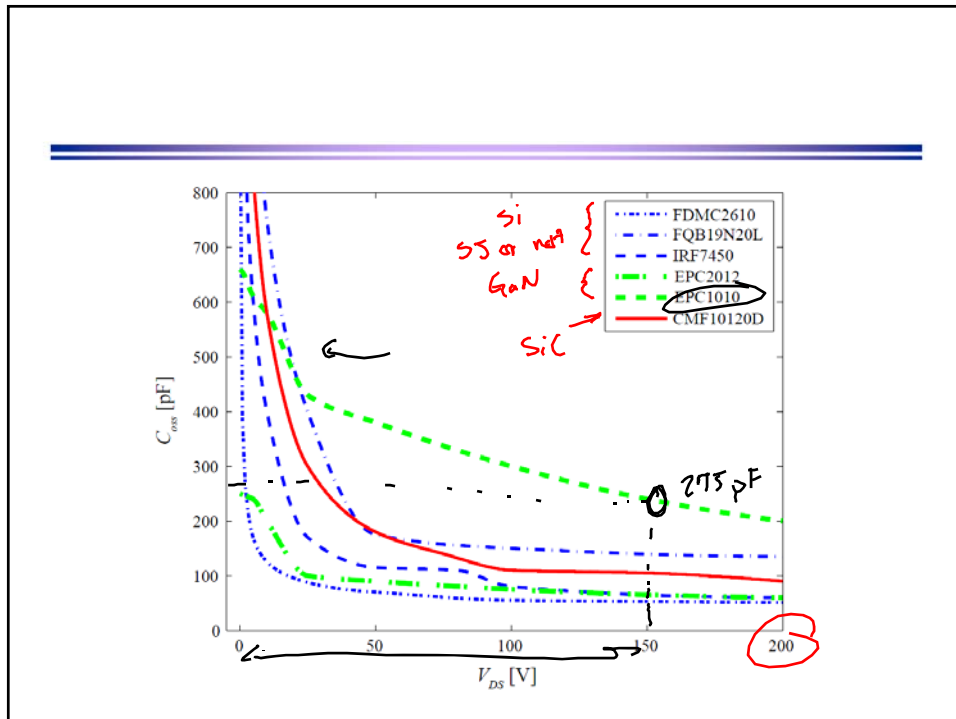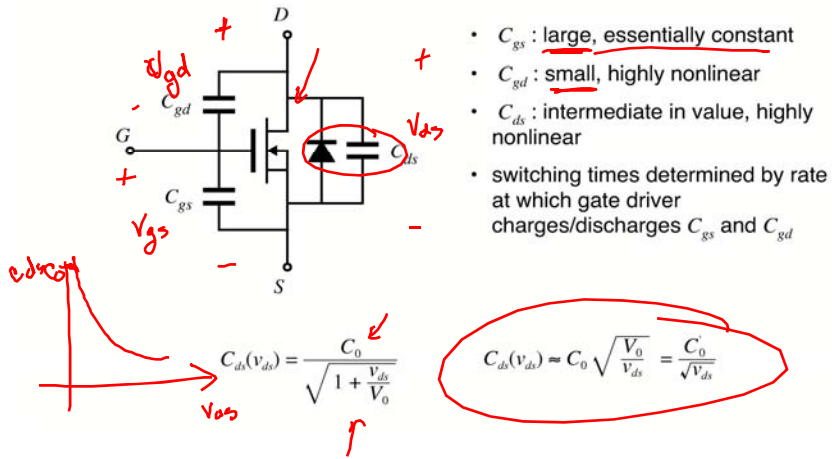

Switching loss caused by semiconductor output capacitances

Buck converter example

Before MOSFET turn-on
 $V_{ds} = V_g$
 $W_c = \frac{1}{2} C_{ds} V_g^2$

Energy lost during MOSFET turn-on transition
 (assuming linear capacitances):

$W_c = \frac{1}{2} (C_{ds} + C_j) V_g^2$

$E_j = \frac{1}{2} C_j V_g^2$
 $P_c = W_c f_s$

if you didn't believe

$i_c = c \frac{dv}{dt}$
 $P_R = i_c (V - V_c)$
 $E_x = \int_0^V c (V - V_c) \frac{dv}{dt} dt$
 $= \int_0^V c (V - V_c) dv$
 $= \int_0^V c V dv - \int_0^V c V_c dv$
 $= c V^2 - \frac{1}{2} c V^2 = \frac{1}{2} c V^2$

MOSFET nonlinear C_{ds}

Approximate dependence of incremental C_{ds} on v_{ds} :

$$C_{ds}(v_{ds}) \approx C_0 \sqrt{\frac{V_0}{v_{ds}}} = \frac{C_0}{\sqrt{v_{ds}}}$$

Energy stored in C_{ds} at $v_{ds} = V_{DS}$:

$$W_{C_{ds}} = \int_0^{V_{DS}} v_{ds} i_c dt = \int_0^{V_{DS}} v_{ds} C_{ds}(v_{ds}) dv_{ds}$$

$$W_{C_{ds}} = \int_0^{V_{DS}} C_0'(v_{ds}) \sqrt{v_{ds}} dv_{ds} = \frac{2}{3} C_{ds}(V_{DS}) V_{DS}^2$$

— same energy loss as linear capacitor having value $\frac{2}{3} C_{ds}(V_{DS})$

FOM \rightarrow $\downarrow R_{on}$ in C_{gs} or $\downarrow Q_g$ in C_{gs}

Characteristics of several commercial power MOSFETs


Part number	Rated max voltage	Rated avg current	R_{on}	Q_g (typical)
IRLHM620	20V	40A	0.0025 Ω	52nC
EPC2015	40V	33A	0.004 Ω	10.5nC
IRFZ48	60V	50A	0.018 Ω	110nC
IRF510	100V	5.6A	0.54 Ω	8.3nC
IRF540	100V	28A	0.077 Ω	72nC
APT10M25BNR	100V	75A	0.025 Ω	171nC
IRF740	400V	10A	0.55 Ω	63nC
MTM15N40E	400V	15A	0.3 Ω	110nC
APT5025BN	500V	23A	0.25 Ω	83nC
APT1001RBNR	1000V	11A	1.0 Ω	150nC
IPW60R099CP	600V	31A	0.1 Ω	60nC
IPW90R340C3	900V	15A	0.34 Ω	93nC
TPH3006PD	600V	17A	0.15 Ω	6nC
CMF20120	1200V	24A	0.098 Ω	49nC

GaN \rightarrow

superjunction

GaN \rightarrow

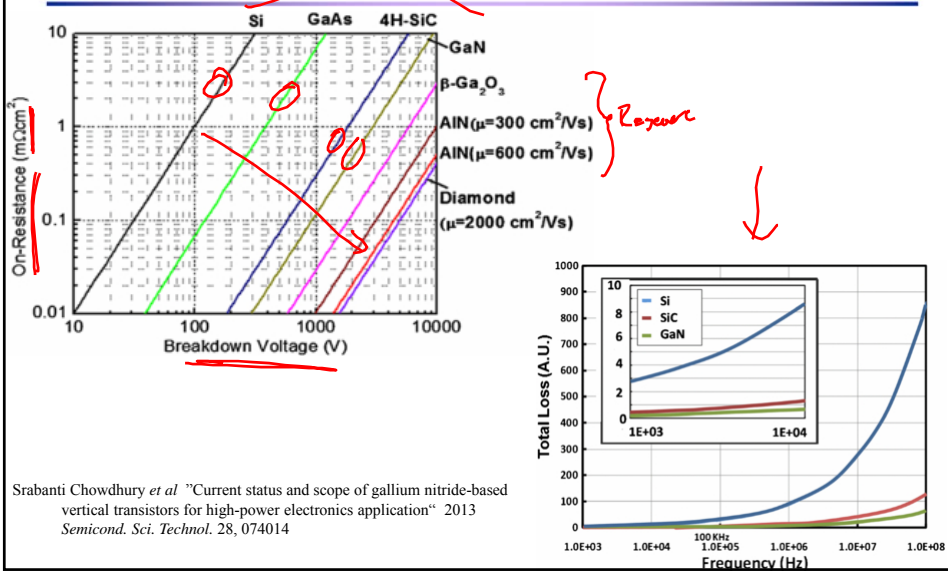Current Research in Wide Bandgap Materials




Srabanti Chowdhury *et al* "Current status and scope of gallium nitride-based vertical transistors for high-power electronics application" 2013 *Semicond. Sci. Technol.* 28, 074014

MOSFET: conclusions

- A majority-carrier device: fast switching speed
- Typical switching frequencies: tens and hundreds of kHz $\&$ above MHz
- On-resistance increases rapidly with rated blocking voltage
- Easy to drive
- The device of choice for blocking voltages less than 500V
- 1000V devices are available, but are useful only at low power levels (100W)
- Part number is selected on the basis of on-resistance rather than current rating

4.2.3. Bipolar Junction Transistor (BJT)

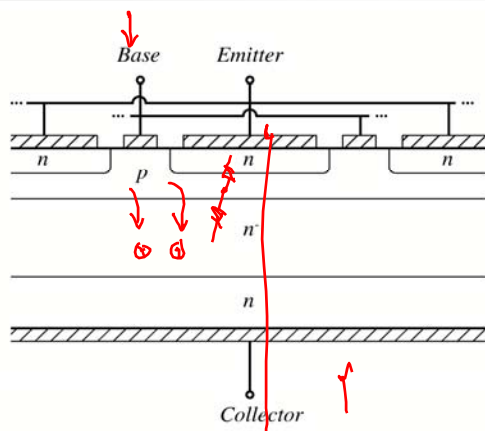


- Interdigitated base and emitter contacts
- Vertical current flow
- npn device is shown
- minority carrier device
- on-state: base-emitter and collector-base junctions are both forward-biased
- on-state: substantial minority charge in p and n^+ regions, conductivity modulation

Conclusions: BJT


- BJT has been replaced by MOSFET in low-voltage (<500V) applications
- BJT is being replaced by IGBT in applications at voltages above 500V
- A minority-carrier device: compared with MOSFET, the BJT exhibits slower switching, but lower on-resistance at high voltages

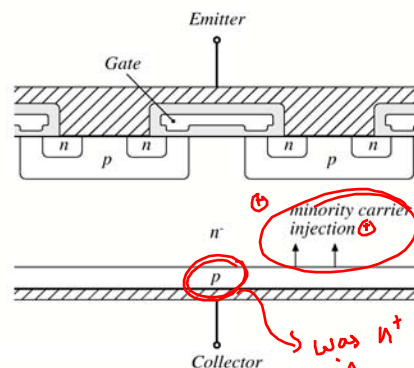4.2.4. The Insulated Gate Bipolar Transistor (IGBT)




- A four-layer device
- Similar in construction to MOSFET, except extra p region
- On-state: minority carriers are injected into n region, leading to conductivity modulation
- compared with MOSFET: slower switching times, lower on-resistance, useful at higher voltages (up to 1700V)


The IGBT

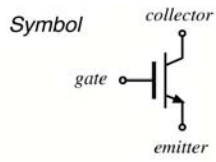



Equivalent circuit

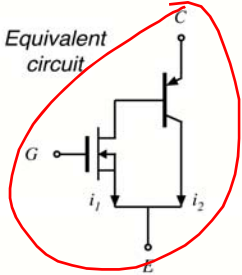


Location of equivalent devices

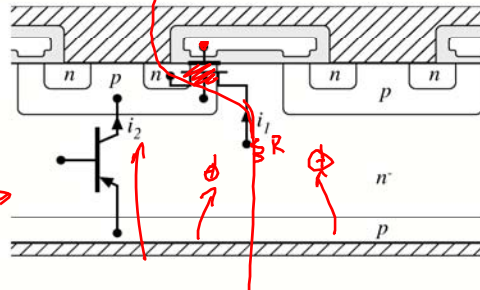

Current tailing in IGBTs

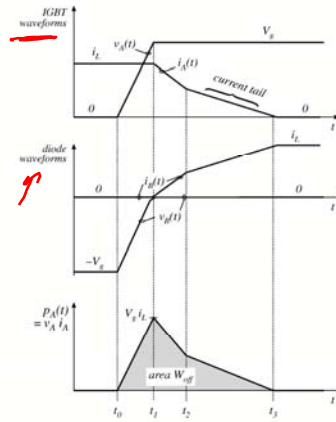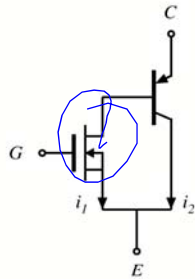

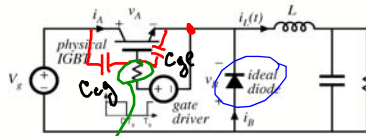
Switching loss due to current-tailing in IGBT



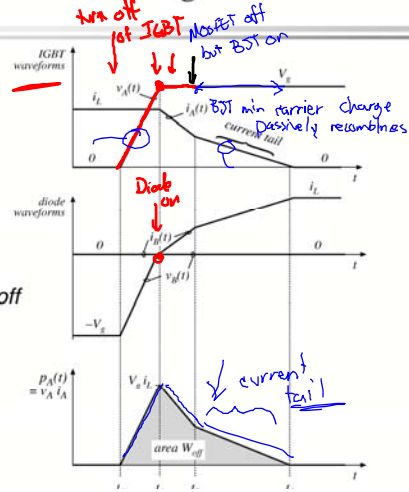Example: buck converter with IGBT

transistor turn-off transition

$$P_{sw} = \frac{1}{T_s} \int_{\text{switching transitions}} p_A(t) dt = (W_{on} + W_{off}) f_s$$



Characteristics of several commercial devices


Part number	Rated max voltage	Rated avg current	V_F (typical)	t_f (typical)
Single-chip devices				
HGTG32N60E2	600V	32A	2.4V	0.62 μ s
HGTG30N120D2	1200V	30A	3.2A	0.58 μ s
Multiple-chip power modules				
CM400HA-12E	600V	400A	2.7V	0.3 μ s
CM300HA-24E	1200V	300A	2.7V	0.3 μ s

Conclusions: IGBT

- Becoming the device of choice in 500 to 1700V+ applications, at power levels of 1-1000kW
- Positive temperature coefficient at high current —easy to parallel and construct modules
- Forward voltage drop: diode in series with on-resistance. 2-4V typical
- Easy to drive —similar to MOSFET
- Slower than MOSFET, but faster than Darlington, GTO, SCR
- Typical switching frequencies: 3-30kHz
- IGBT technology is rapidly advancing:
 - 3300 V devices: HVIGBTs
 - 150 kHz switching frequencies in 600 V devices


→ 4.2.5. Thyristors (SCR, GTO, MCT)

The SCR

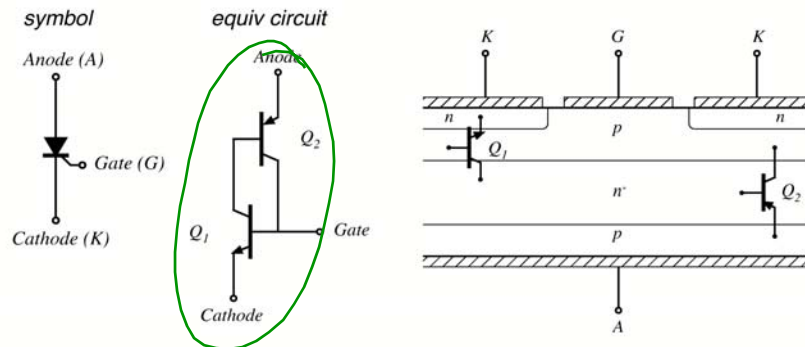

The Silicon Controlled Rectifier (SCR)

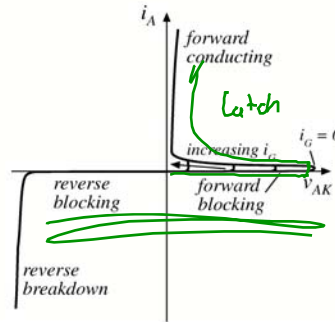- Positive feedback — a latching device
- A minority carrier device
- Double injection leads to very low on-resistance, hence low forward voltage drops attainable in very high voltage devices
- Simple construction, with large feature size
- Cannot be actively turned off
- A voltage-bidirectional two-quadrant switch
- 5000-6000V, 1000-2000A devices



Transistor Selection

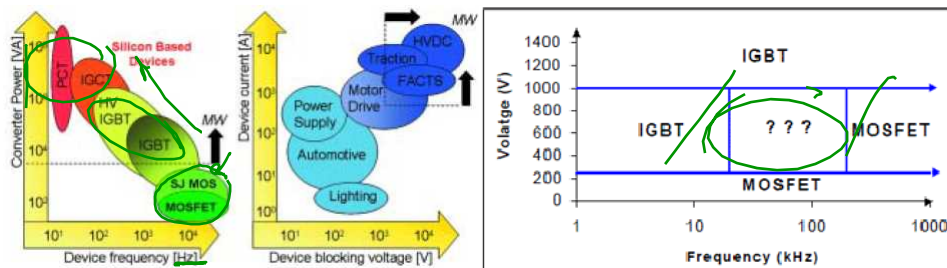


Figure 1: Power Semiconductor devices and applications

Transistor Selection


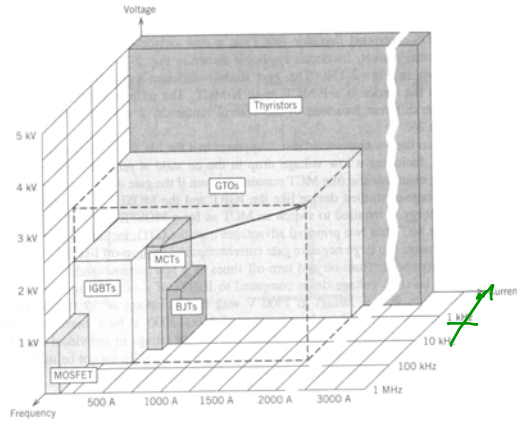


Figure 2-14 Summary of power semiconductor device capabilities. All devices except the MCT have a relatively mature technology, and only evolutionary improvements in the device capabilities are anticipated in the next few years. However, MCT technology is in a state of rapid expansion, and significant improvements in the device capabilities are possible, as indicated by the expansion arrow in the diagram.

Moham

Transistor Hybridization

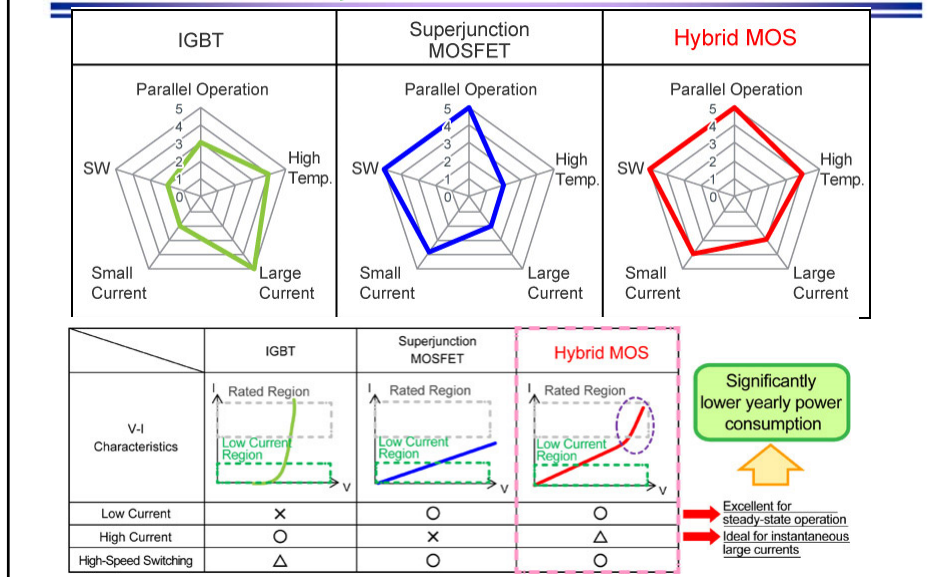

4.3. Switching loss

- Energy is lost during the semiconductor switching transitions, via several mechanisms:
 - ~~Transistor switching times~~ *Outdated*
 - Diode stored charge Q_r
 - Energy stored in device capacitances and parasitic inductances
- Semiconductor devices are *charge controlled*
- Time required to insert or remove the controlling charge determines switching times

Some other sources of this type of switching loss

- Schottky diode (*majority carrier*)
- Essentially no stored charge $Q_r = \emptyset$ but $C_j \rightarrow \emptyset$
 - Significant reverse-biased junction capacitance
- Transformer leakage inductance
- Effective inductances in series with windings
 - A significant loss when windings are not tightly coupled
- Interconnection and package inductances
- Diodes
 - Transistors
 - A significant loss in high current applications

4.3.4. Efficiency vs. switching frequency

Add up all of the energies lost during the switching transitions of one switching period:

$$W_{tot} = W_{on} + W_{off} + W_D + W_C + W_L + \dots$$

Average switching power loss is

$$P_{sw} = W_{tot} f_{sw}$$

Total converter loss can be expressed as

$$P_{loss} = P_{cond} + P_{fixed} + W_{tot} f_{sw}$$


where

P_{fixed} = fixed losses (independent of load and f_{sw})

P_{cond} = conduction losses

Efficiency vs. switching frequency
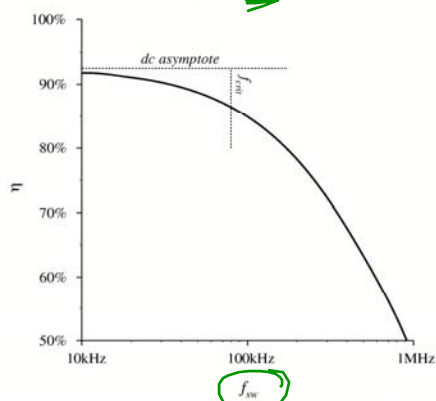
$$P_{loss} = P_{cond} + P_{fixed} + W_{tot} f_{sw}$$



Inclusion of Switching Loss in the Averaged Equivalent Circuit Model

The methods of Chapter 3 can be extended to include switching loss in the converter equivalent circuit model

- • Include switching transitions in the converter waveforms
- Model effects of diode reverse recovery, etc.

To obtain tractable results, the waveforms during the switching transitions must usually be approximated

Things that can substantially change the results:


- { • Ringing caused by parasitic tank circuits
- { • Snubber circuits

The Modeling Approach

Extension of Chapter 3 Methods


- Sketch the converter waveforms
 - Including the switching transitions (idealizing assumptions are made to lead to tractable results)
 - In particular, sketch inductor voltage, capacitor current, and input current waveforms
- The usual steady-state relationships:
 - $\langle v_L \rangle = 0, \langle i_C \rangle = 0, \langle i_g \rangle = I_g$
- Use the resulting equations to construct an equivalent circuit model, as usual

Buck Converter Example

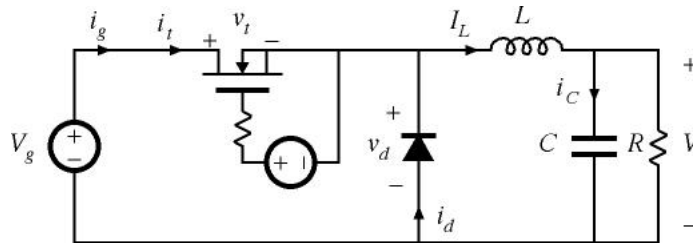

- Ideal MOSFET, p-n diode with reverse recovery
- Neglect semiconductor device capacitances, MOSFET switching times, etc.
- Neglect conduction losses
- Neglect ripple in inductor current and capacitor voltage


Assumed waveforms

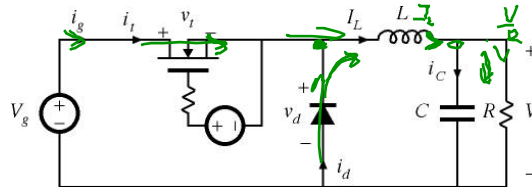


Diode recovered charge Q_r , reverse recovery time t_r

These waveforms assume that the diode voltage changes at the end of the reverse recovery transient

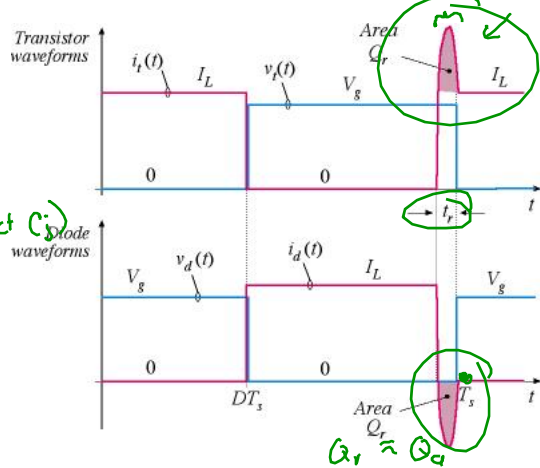- a "snappy" diode (Neglect C_j)
- Voltage of soft-recovery diodes changes sooner
- Leads to a pessimistic estimate of induced switching loss



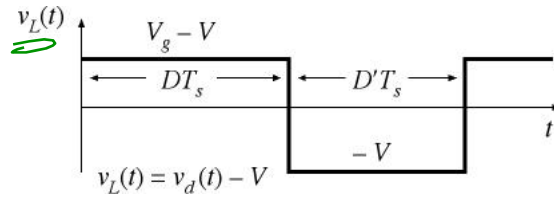
Inductor volt-second balance and capacitor charge balance



As usual: $\langle v_L \rangle = 0 = DV_g - V$

Also as usual: $\langle i_C \rangle = 0 = I_L - V/R$

Average input current

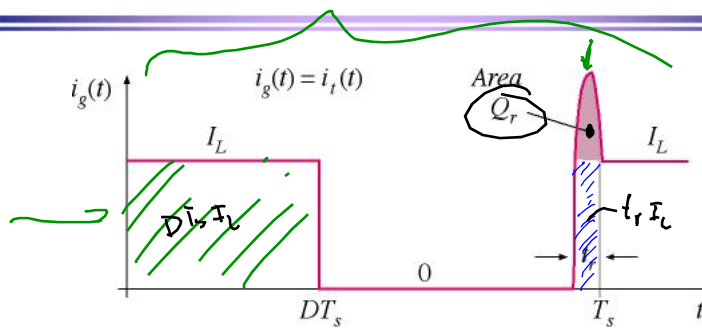


$$\begin{aligned} \langle i_g \rangle &= I_g = (\text{area under curve})/T_s \\ &= (DT_s I_L + t_r I_L + Q_r)/T_s \\ &= DI_L + t_r I_L/T_s + Q_r/T_s = \langle i_g \rangle \end{aligned}$$

Construction of Equivalent Circuit Model


From inductor volt-second balance: $\langle v_L \rangle = 0 = DV_g - V$

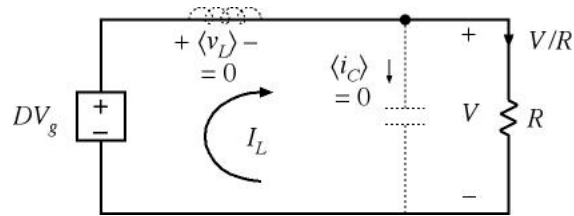From capacitor charge balance: $\langle i_C \rangle = 0 = I_L - V/R$




Input port of model
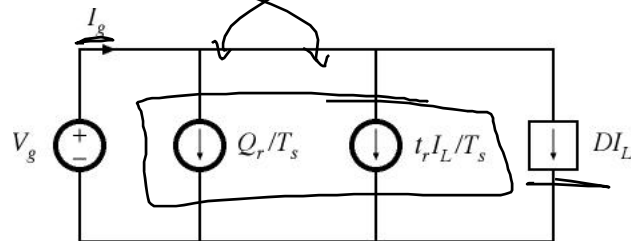
$$\langle i_g \rangle = I_g = DI_L + t_r I_L / T_s + Q_r / T_s$$



Combine for complete model

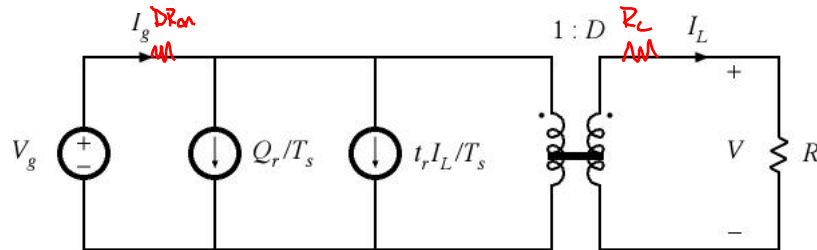


The two independent current sources consume power

$$V_g (t_r I_L / T_s + Q_r / T_s)$$

equal to the switching loss induced by diode reverse recovery

Solution of model

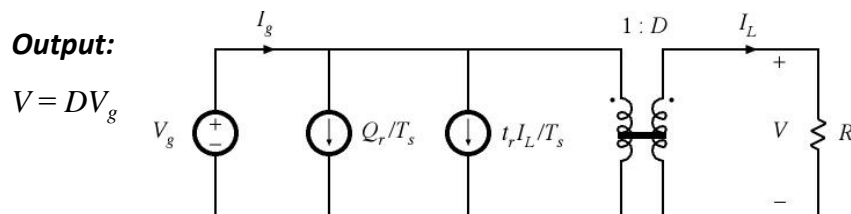

$$V = D V_g$$

Efficiency: $\eta = P_{out} / P_{in}$

$$P_{out} = V I_L \quad P_{in} = V_g (D I_L + t_r I_L / T_s + Q_r / T_s)$$

Combine and simplify:


$$\eta = 1 / [1 + f_s (t_r / D + Q_r R / D^2 V_g)] = \frac{1}{1 + f_s (\quad)}$$

Predicted Efficiency vs Duty Cycle


- Switching frequency 100 kHz
- Input voltage 24 V
- Load resistance 15 Ω
- Recovered charge 0.75 μCoul
- Reverse recovery time 75 nsec

• (no attempt is made here to model how the reverse recovery process varies with inductor current)

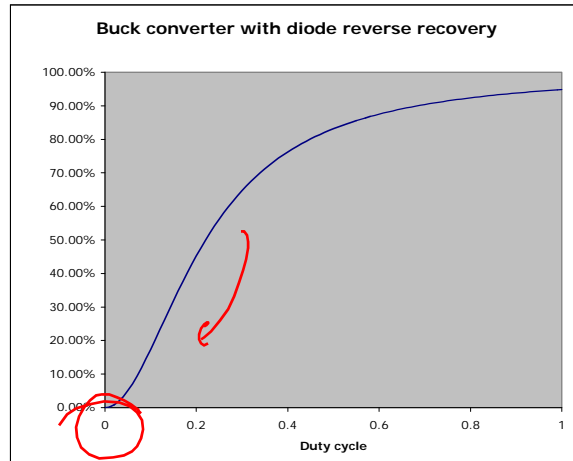- Substantial degradation of efficiency
- Poor efficiency at low duty cycle




Boost Converter Example

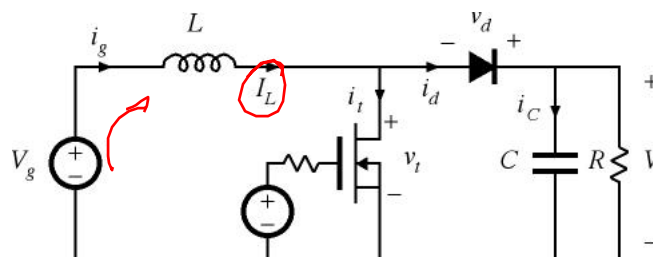


- Model same effects as in previous buck converter example:
- Ideal MOSFET, $p-n$ diode with reverse recovery
- Neglect semiconductor device capacitances, MOSFET switching times, etc.
- Neglect conduction losses
- Neglect ripple in inductor current and capacitor voltage


Boost converter

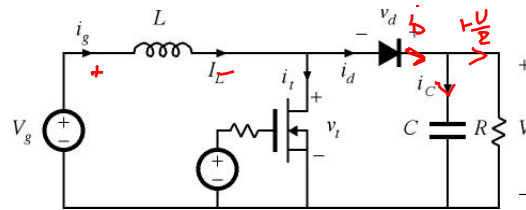

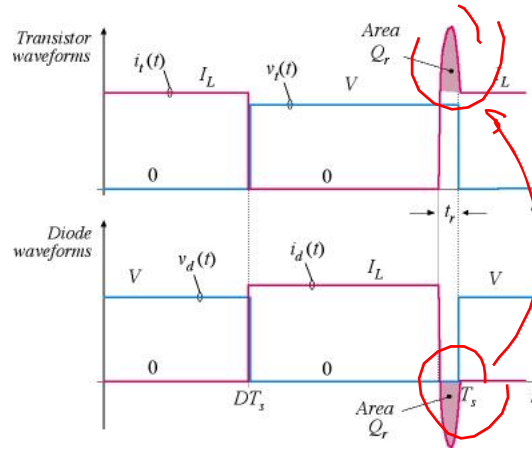Transistor and diode waveforms have same shapes as in buck example, but depend on different quantities




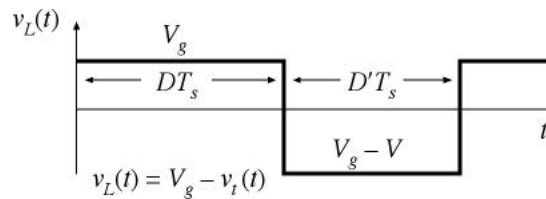
Inductor volt-second balance and average input current



As usual: $\langle v_L \rangle = 0 = V_g - D'V$

Also as usual: $\langle i_g \rangle = I_L$

Capacitor charge balance

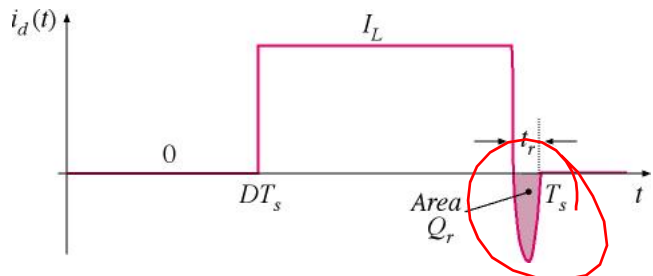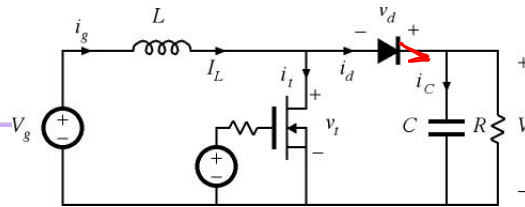


$$\langle i_C \rangle = \langle i_d \rangle - V/R = 0$$

$$= -V/R + I_L(D'T_s - t_r)/T_s - Q_r/T_s$$

$$\text{Collect terms: } V/R = \underbrace{I_L(D'T_s - t_r)/T_s - Q_r/T_s}$$

Construct model

The result is:

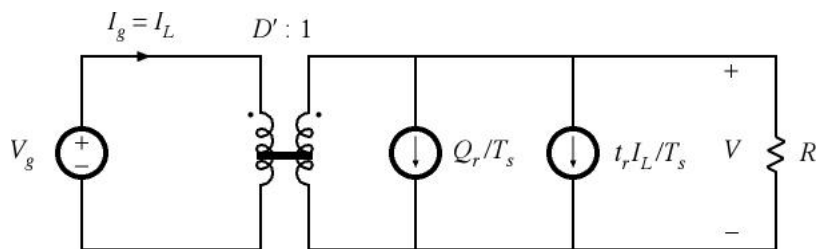


The two independent current sources consume power

$$V(t_r I_L/T_s + Q_r/T_s)$$

equal to the switching loss induced by diode reverse recovery

Predicted V/V_g vs duty cycle

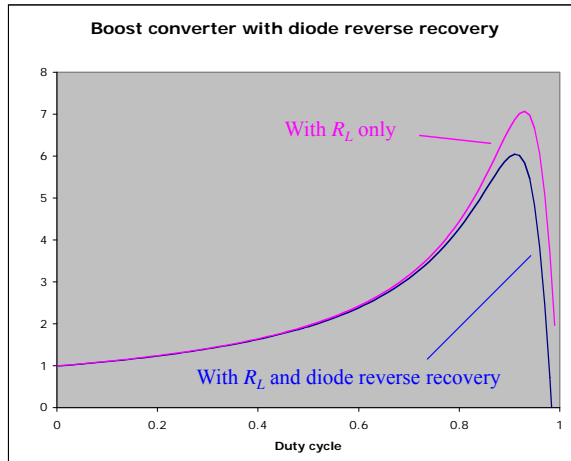- Switching frequency 100 kHz
- Input voltage 24 V
- Load resistance 60 Ω
- Recovered charge 5 μCoul
- Reverse recovery time 100 nsec
- Inductor resistance $R_L = 0.3 \Omega$
- (inductor resistance also inserted into averaged model here)



Summary

- The averaged modeling approach can be extended to include effects of switching loss
- Transistor and diode waveforms are constructed, including the switching transitions. The effects of the switching transitions on the inductor, capacitor, and input current waveforms can then be determined
- Inductor volt-second balance and capacitor charge balance are applied
- Converter input current is averaged
- Equivalent circuit corresponding to the the averaged equations is constructed