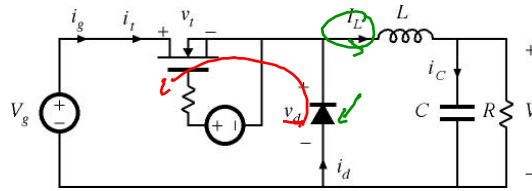

Lecture 8: Flyback Example

ECE 481: Power Electronics
Prof. Daniel Costinett
Department of Electrical Engineering and Computer Science
University of Tennessee Knoxville
Fall 2013

Announcements

- Homework #3 due today
- Midterm exam handed out on Thursday


Assumed waveforms




Diode recovered charge Q_r ,
reverse recovery time t_r

These waveforms assume that the diode voltage changes at the end of the reverse recovery transient

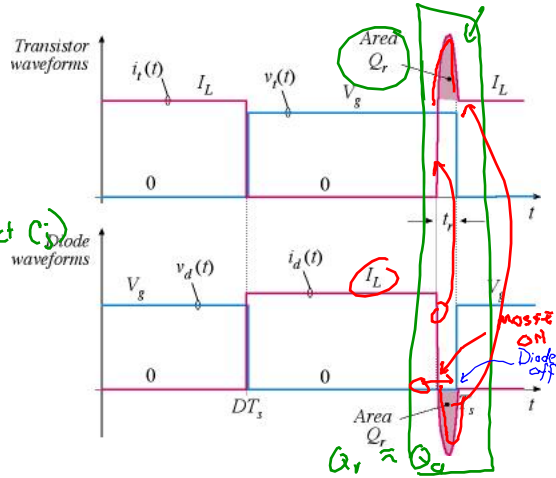- a "snappy" diode (Neglect C_j)
- Voltage of soft-recovery diodes changes sooner
- Leads to a pessimistic estimate of induced switching loss




Average input current

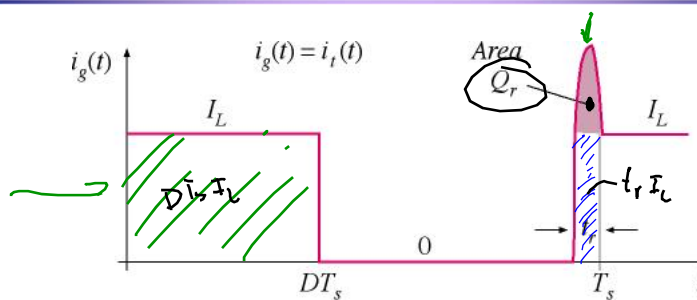

$$\begin{aligned} \langle i_g \rangle &= I_g = (\text{area under curve})/T_s \\ &= (DT_s I_L + t_r I_L + Q_r)/T_s \\ &= DI_L + t_r I_L/T_s + Q_r/T_s = \langle i_g \rangle \end{aligned}$$

Solution of model

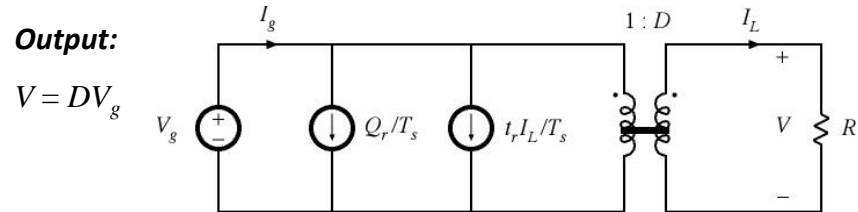


Efficiency: $\eta = P_{out} / P_{in}$

$$P_{out} = VI_L \quad P_{in} = V_g (DI_L + t_r I_L / T_s + Q_r / T_s)$$

Combine and simplify:


$$\eta = 1 / [1 + f_s (t_r / D + Q_r R / D^2 V_g)]$$

Boost Converter Example

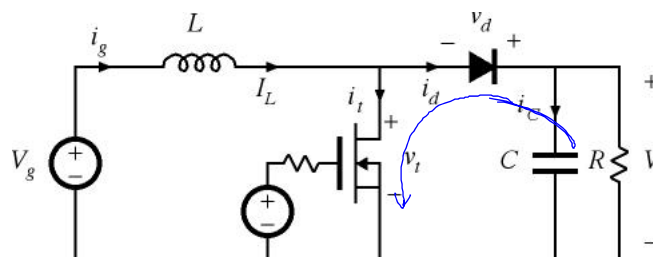


- Model same effects as in previous buck converter example:
- Ideal MOSFET, $p-n$ diode with reverse recovery
- Neglect semiconductor device capacitances, MOSFET switching times, etc.
- Neglect conduction losses
- Neglect ripple in inductor current and capacitor voltage

Boost converter

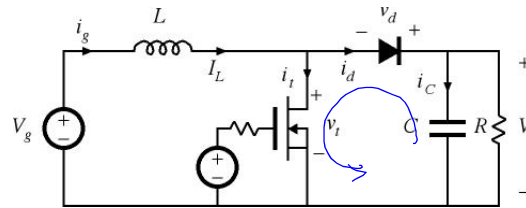


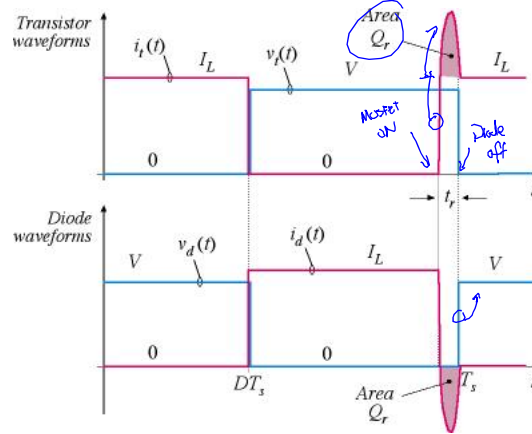Transistor and diode waveforms have same shapes as in buck example, but depend on different quantities



Construct model

The result is:

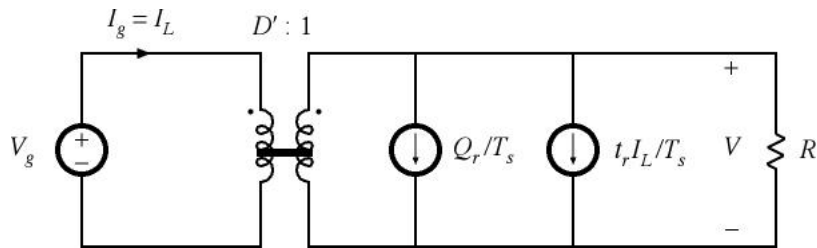

The two independent current sources consume power

$$V (t_r I_L / T_s + Q_r / T_s)$$

equal to the switching loss induced by diode reverse recovery

Summary

- The averaged modeling approach can be extended to include effects of switching loss
- Transistor and diode waveforms are constructed, including the switching transitions. The effects of the switching transitions on the inductor, capacitor, and input current waveforms can then be determined
- Inductor volt-second balance and capacitor charge balance are applied
- Converter input current is averaged
- Equivalent circuit corresponding to the the averaged equations is constructed

6.2. A short list of converters

An infinite number of converters are possible, which contain switches embedded in a network of inductors and capacitors



Two simple classes of converters are listed here:

- Single-input single-output converters containing a single inductor. The switching period is divided into two subintervals. This class contains eight converters.
- Single-input single-output converters containing two inductors. The switching period is divided into two subintervals. Several of the more interesting members of this class are listed.

Converters producing a unipolar output voltage



1. Buck

$$M(D) = D$$

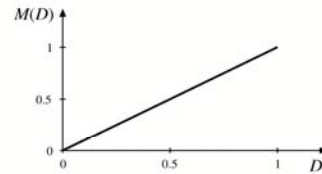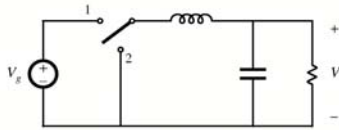

2. Boost



$$M(D) = \frac{1}{1-D}$$

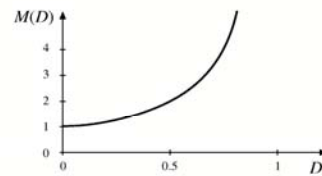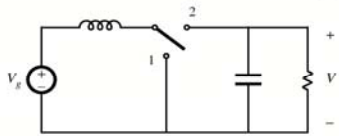

Converters producing a unipolar output voltage



3. Buck-boost

$$M(D) = -\frac{D}{1-D}$$

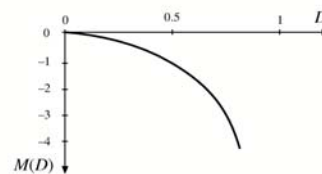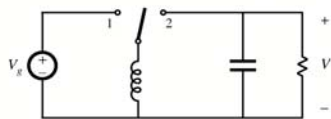

4. Noninverting buck-boost



$$M(D) = \frac{D}{1-D}$$

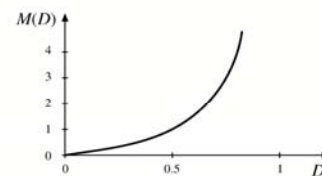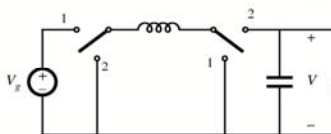

Converters producing a bipolar output voltage suitable as dc-ac inverters



5. Bridge

$$M(D) = 2D - 1$$

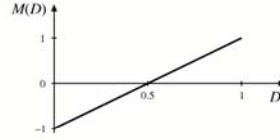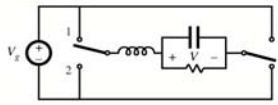

6. Watkins-Johnson



$$M(D) = \frac{2D-1}{D}$$

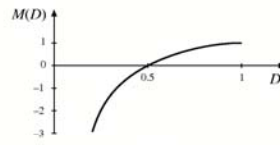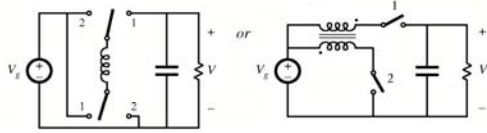

Converters producing a bipolar output voltage suitable as ac-dc rectifiers



7. Current-fed bridge

$$M(D) = \frac{1}{2D-1}$$

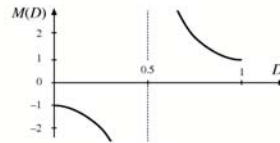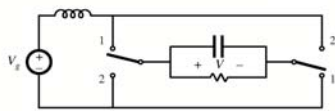

8. Inverse of Watkins-Johnson



$$M(D) = \frac{D}{2D-1}$$

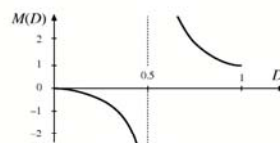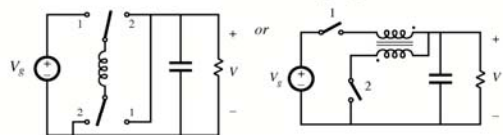

Several members of the class of two-inductor converters



1. *Ćuk*

$$M(D) = -\frac{D}{1-D}$$

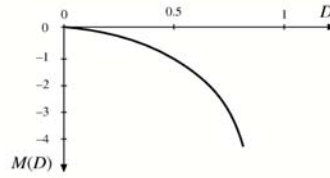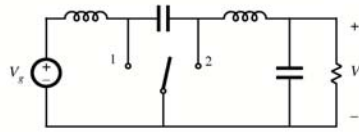

2. *SEPIC*



$$M(D) = \frac{D}{1-D}$$

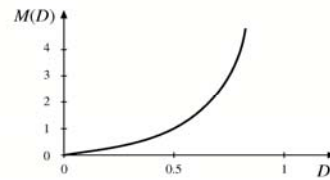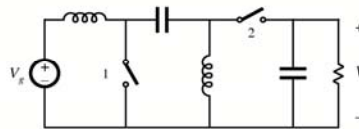

Several members of the class of two-inductor converters



3. *Inverse of SEPIC*

$$M(D) = \frac{D}{1-D}$$

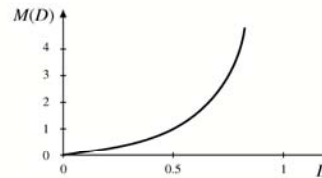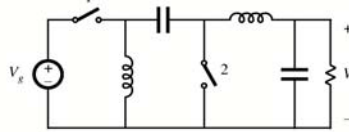

4. *Buck²*


$$M(D) = D^2$$

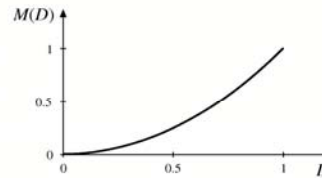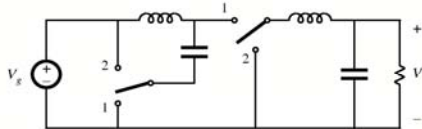

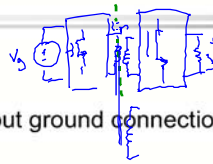
6.3. Transformer isolation

Objectives:

- Isolation of input and output ground connections, to meet safety requirements
- Reduction of transformer size by incorporating high frequency isolation transformer inside converter
- Minimization of current and voltage stresses when a large step-up or step-down conversion ratio is needed —use transformer turns ratio
- Obtain multiple output voltages via multiple transformer secondary windings and multiple converter secondary circuits




A simple transformer model

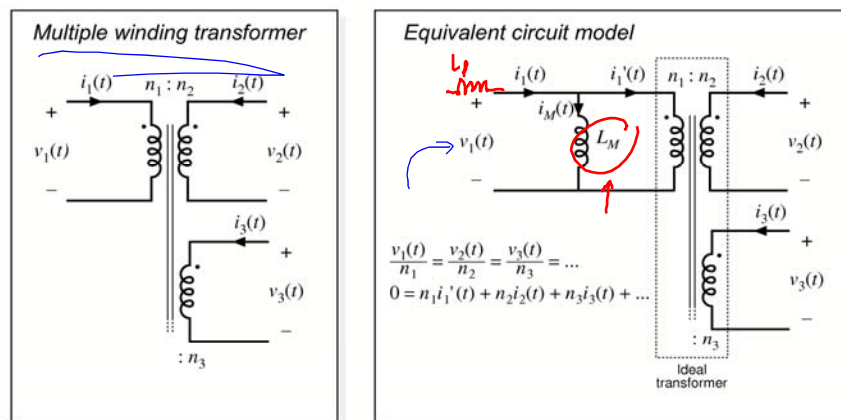

The magnetizing inductance L_M

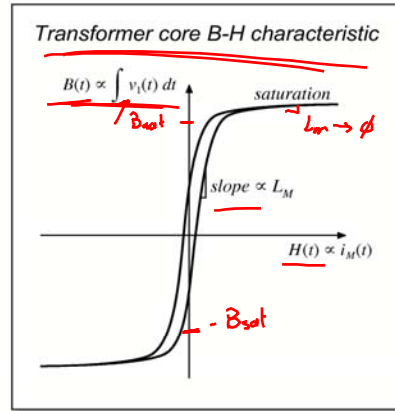- Models magnetization of transformer core material
- Appears effectively in parallel with windings
- If all secondary windings are disconnected, then primary winding behaves as an inductor, equal to the magnetizing inductance
- At dc: magnetizing inductance tends to short-circuit. Transformers cannot pass dc voltages
- Transformer saturates when magnetizing current i_M is too large



Volt-second balance in L_M

The magnetizing inductance is a real inductor, obeying


$$v_1(t) = L_M \frac{di_M(t)}{dt}$$

integrate:

$$i_M(t) - i_M(0) = \frac{1}{L_M} \int_0^t v_1(\tau) d\tau$$

Magnetizing current is determined by integral of the applied winding voltage. The magnetizing current and the winding currents are independent quantities. Volt-second balance applies: in steady-state, $i_M(T_s) = i_M(0)$, and hence
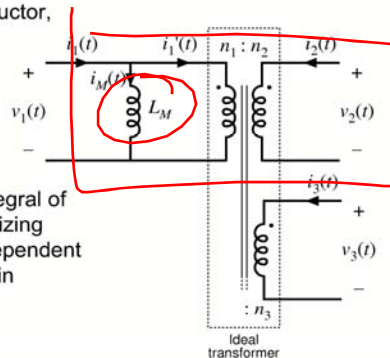
$$0 = \frac{1}{T_s} \int_0^{T_s} v_1(t) dt$$




Transformer reset


- "Transformer reset" is the mechanism by which magnetizing inductance volt-second balance is obtained
- The need to reset the transformer volt-seconds to zero by the end of each switching period adds considerable complexity to converters
- To understand operation of transformer-isolated converters:
 - replace transformer by equivalent circuit model containing magnetizing inductance
 - analyze converter as usual, treating magnetizing inductance as any other inductor
 - apply volt-second balance to all converter inductors, including magnetizing inductance

6.3.4. Flyback converter

buck-boost converter:

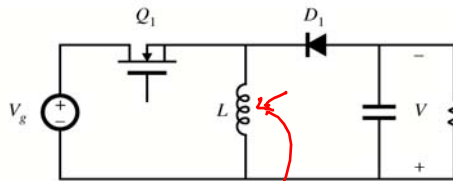


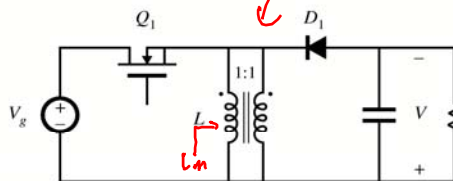construct inductor winding using two parallel wires:




Derivation of flyback converter, cont.

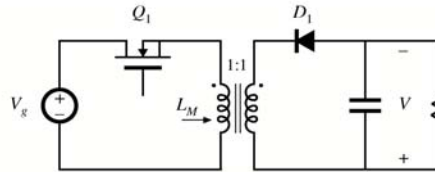
Isolate inductor windings: the flyback converter



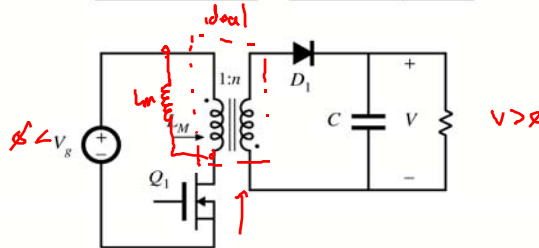Flyback converter having a 1:n turns ratio and positive output:




The "flyback transformer"

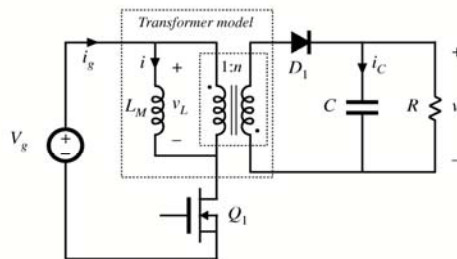


- A two-winding inductor
- Symbol is same as transformer, but function differs significantly from ideal transformer
- Energy is stored in magnetizing inductance
- Magnetizing inductance is relatively small

- Current does not simultaneously flow in primary and secondary windings
- Instantaneous winding voltages follow turns ratio
- Instantaneous (and rms) winding currents do not follow turns ratio
- Model as (small) magnetizing inductance in parallel with ideal transformer


Flyback Converter Example

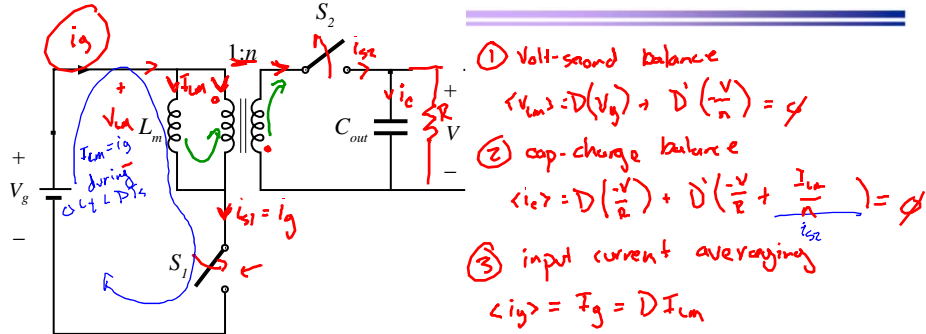

Equivalent Circuit Model

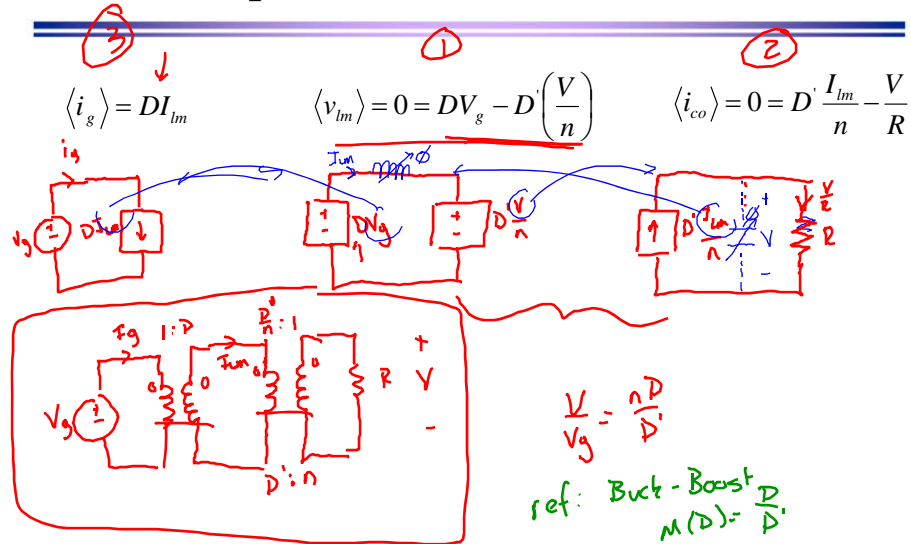

Subinterval 1

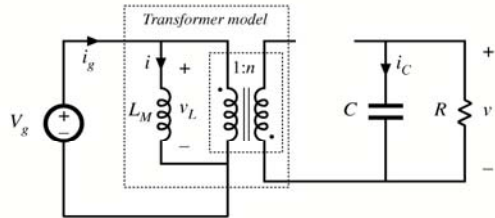


$$\begin{aligned} v_L &= V_g \\ i_C &= -\frac{v}{R} \\ i_g &= i \end{aligned}$$

CCM: small ripple approximation leads to

$$\begin{aligned} v_L &= V_g \\ i_C &= -\frac{V}{R} \\ i_g &= I \end{aligned}$$

Q_1 on, D_1 off

Subinterval 2

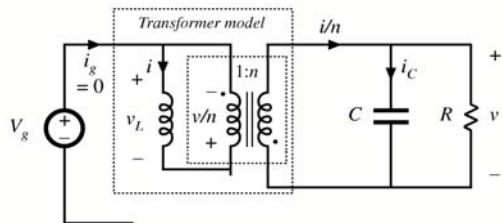


$$\begin{aligned} v_L &= -\frac{v}{n} \\ i_C &= \frac{i}{n} - \frac{v}{R} \\ i_g &= 0 \end{aligned}$$

CCM: small ripple approximation leads to

$$\begin{aligned} v_L &= -\frac{V}{n} \\ i_C &= \frac{I}{n} - \frac{V}{R} \\ i_g &= 0 \end{aligned}$$

Q_1 off, D_1 on

CCM Flyback waveforms and solution

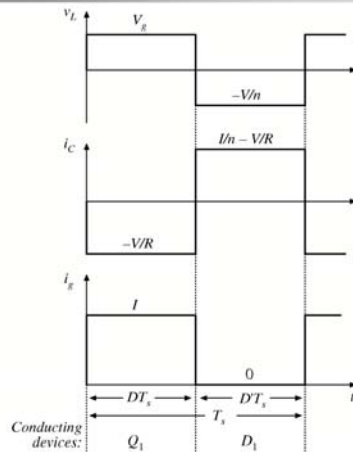

Volt-second balance:

$$\langle v_L \rangle = D(V_g) + D'(-\frac{V}{n}) = 0$$

Conversion ratio is

$$M(D) = \frac{V}{V_g} = n \frac{D}{D'}$$

Charge balance:

$$\langle i_C \rangle = D(-\frac{V}{R}) + D'(\frac{I}{n} - \frac{V}{R}) = 0$$

Dc component of magnetizing current is

$$I = \frac{nV}{D'R}$$

Dc component of source current is

$$I_g = \langle i_g \rangle = D(I) + D'(0)$$

Equivalent circuit model: CCM Flyback

$$\langle v_L \rangle = D(V_g) + D'(-\frac{V}{n}) = 0$$



$$\langle i_C \rangle = D(-\frac{V}{R}) + D'(\frac{I}{n} - \frac{V}{R}) = 0$$

$$I_g = \langle i_g \rangle = D(I) + D'(0)$$


Handwritten notes:

$$V = \frac{Dn}{D'} V_g > \phi$$

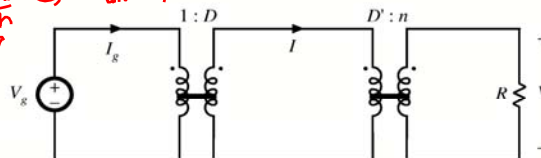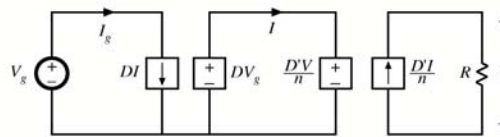
$$\frac{V}{R} = D' \frac{I}{n} \rightarrow I_{Lm} > \phi$$




Large Step Conversion Ratio

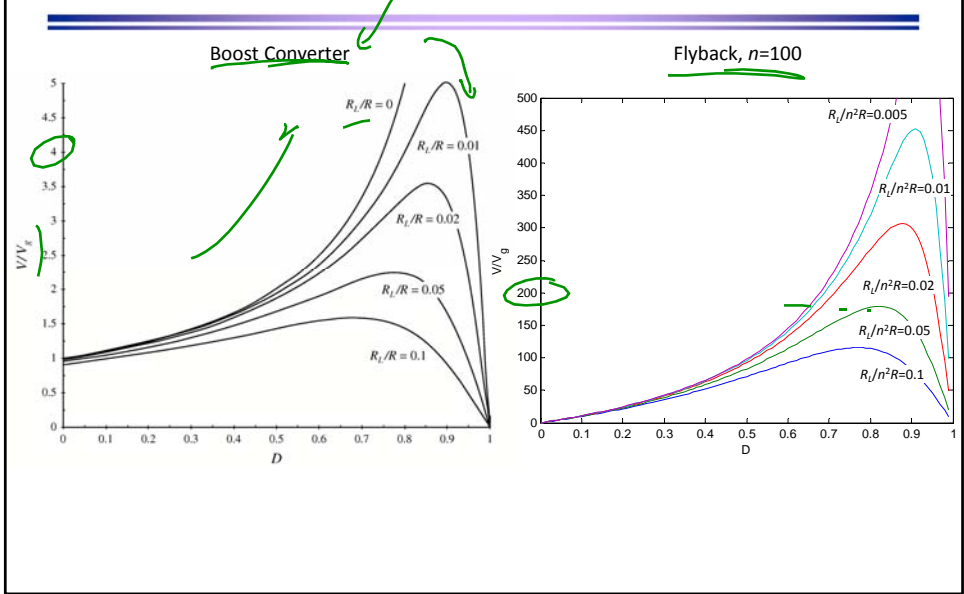


Flyback Semiconductor Waveforms

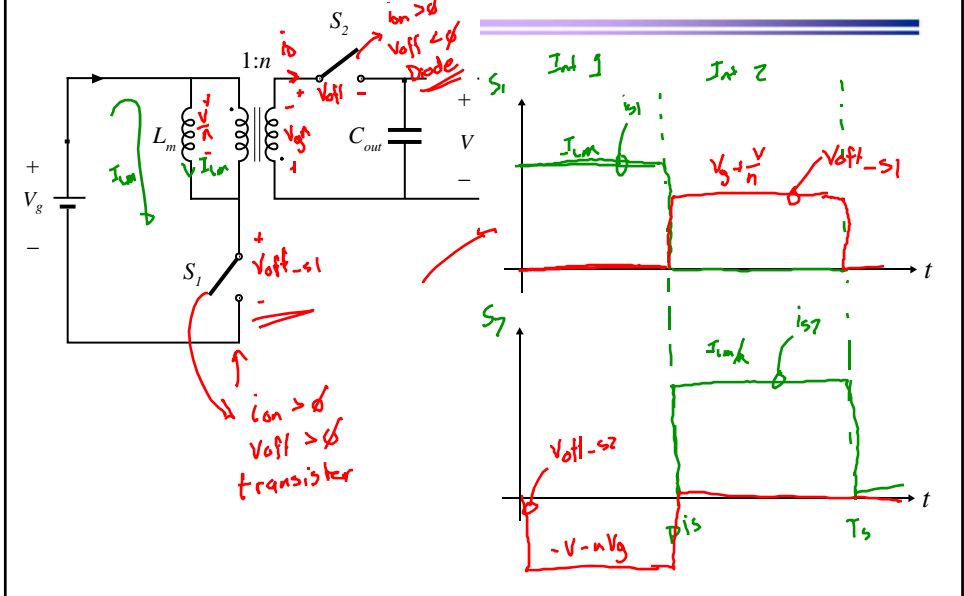


Flyback Switch Implementation

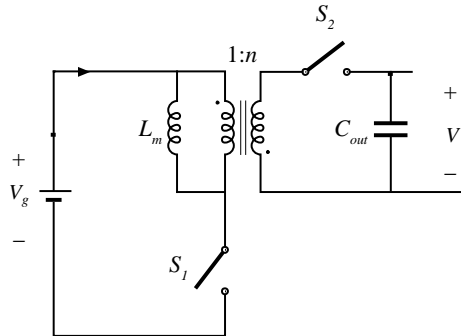


Flyback Semiconductor Waveforms

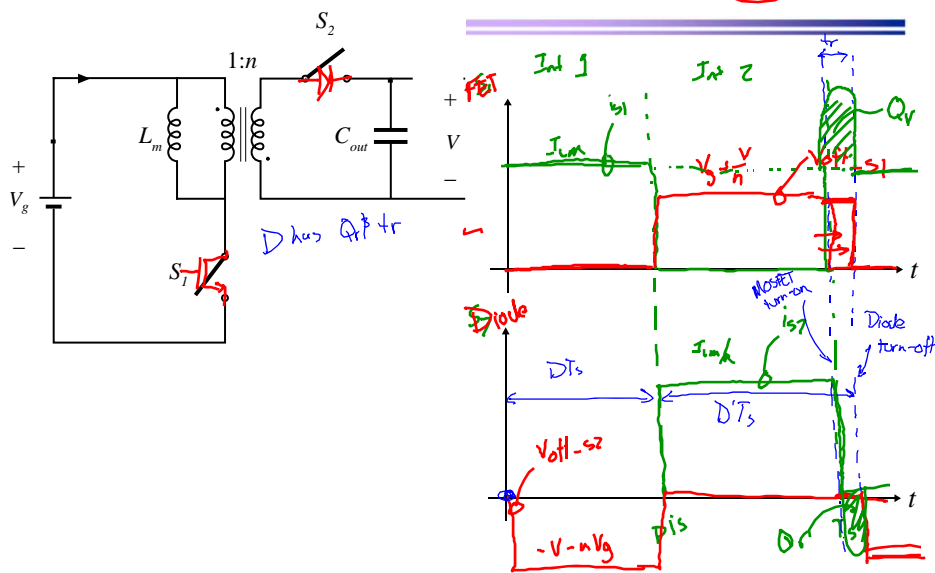

Flyback Reverse Recovery

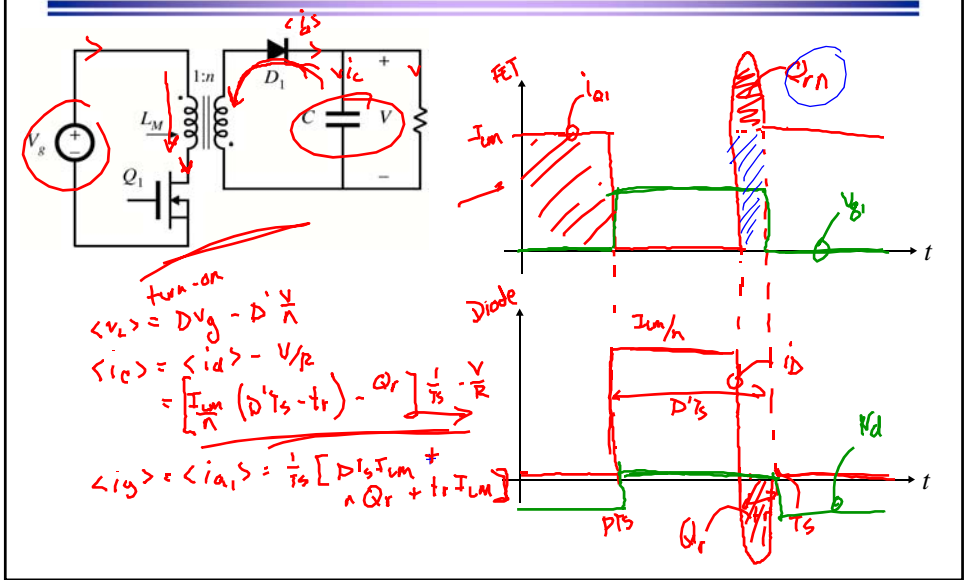

Flyback Reverse Recovery

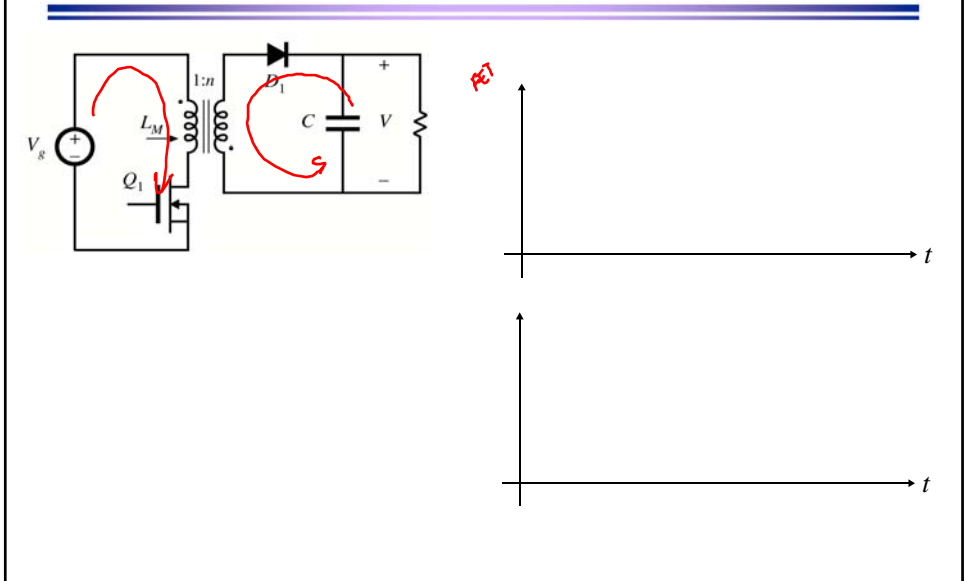

Flyback Reverse Recovery

$$\langle i_g \rangle = DI_{lm} + \frac{t_r}{T_s} I_{lm} + \frac{Q_r}{T_s}$$

$$\langle i_{co} \rangle = 0 = D' \frac{I_{lm}}{n} - \frac{V}{R} - \frac{t_r}{nT_s} I_{lm} - \frac{Q_r}{nT_s}$$

$$\langle v_{lm} \rangle = 0 = DV_g - D' \left(\frac{V}{n} \right)$$

