
Lecture 9: Isolated Converters

ECE 481: Power Electronics

Prof. Daniel Costinett

Department of Electrical Engineering and Computer Science

University of Tennessee Knoxville

Fall 2013

Announcements

- Midterm exam begins at the end of class today
 - Turn in Thursday, 10/3
 - You may use extra sheets

Midterm Exam #1

Fall 2013
ECE 481: Power Electronics



Instructions: This is a one-week take-home exam. It is an open-book, open-note, but *absolutely no collaboration is allowed*. You may not use internet resources other than the course website and contained materials. Show all work, partial credit will be given. When you have completed the exam, sign the University of Tennessee Knoxville Honor Statement below:

As a student of the University, I pledge that I have neither knowingly given nor received any inappropriate assistance in this academic work, thus affirming my own personal commitment to honor and integrity

Signature: _____

This exam is due at the beginning of class, 11:10am, Thursday October 3rd. The exam contains three problems.

Flyback Reverse Recovery

  

Discussion: Flyback converter

- Widely used in low power and/or high voltage applications
- Low parts count
- Multiple outputs are easily obtained, with minimum additional parts
- Cross regulation is inferior to buck-derived isolated converters
- Often operated in discontinuous conduction mode
- DCM analysis: DCM buck-boost with turns ratio

6.4. Converter evaluation and design

For a given application, which converter topology is best?

There is no ultimate converter, perfectly suited for all possible applications

Trade studies

- Rough designs of several converter topologies to meet the given specifications
- An unbiased quantitative comparison of worst-case transistor currents and voltages, transformer size, etc.

Comparison via switch stress, switch utilization, and semiconductor cost

Spreadsheet design

6.4.1. Switch stress and switch utilization

- Largest single cost in a converter is usually the cost of the active semiconductor devices
- Conduction and switching losses associated with the active semiconductor devices often dominate the other sources of loss

This suggests evaluating candidate converter approaches by comparing the voltage and current stresses imposed on the active semiconductor devices.

Minimization of total switch stresses leads to reduced loss, and to minimization of the total silicon area required to realize the power devices of the converter.

Total active switch stress S

In a converter having k active semiconductor devices, the total active switch stress S is defined as

$$S = \sum_{j=1}^k V_j I_j$$

where

V_j is the peak voltage applied to switch j ,

I_j is the rms current applied to switch j (peak current is also sometimes used).

In a good design, the total active switch stress is minimized.

Active switch utilization U

It is desired to minimize the total active switch stress, while maximizing the output power P_{load} .

The active switch utilization U is defined as

$$U = \frac{P_{load}}{S}$$

The active switch utilization is the converter output power obtained per unit of active switch stress. It is a converter figure-of-merit, which measures how well a converter utilizes its semiconductor devices.

Active switch utilization is less than 1 in transformer-isolated converters, and is a quantity to be maximized.

Converters having low switch utilizations require extra active silicon area, and operate with relatively low efficiency.

Active switch utilization is a function of converter operating point.

CCM flyback example: Determination of S

During subinterval 2, the transistor blocks voltage $V_{Q1,pk}$ equal to V_g plus the reflected load voltage:



$$V_{Q1,pk} = V_g + \frac{V}{n} = \frac{V_g}{D}$$

Transistor current coincides with $i_g(t)$. RMS value is

$$I_{Q1,rms} = I \sqrt{D} = \frac{P_{load}}{V_g \sqrt{D}}$$

Switch stress S is
  
$$S = V_{Q1,pk} I_{Q1,rms} = \left(V_g + \frac{V}{n} \right) (I \sqrt{D})$$



CCM flyback example: Determination of U

Express load power P_{load} in terms of V and I :


$$P_{load} = D' V \frac{I}{n}$$

Previously-derived expression for S :

$$S = V_{Q1,pk} I_{Q1,rms} = \left(V_g + \frac{V}{n} \right) (I \sqrt{D})$$

Hence switch utilization U is

$$U = \frac{P_{load}}{S} = D' \sqrt{D}$$

 

Flyback example: switch utilization $U(D)$


For given V , V_g , P_{load} , the designer can arbitrarily choose D . The turns ratio n must then be chosen according to

$$n = \frac{V}{V_g} \frac{D'}{D}$$

Single operating point design: choose $D = 1/3$.

small D leads to large transistor current

 large D leads to large transistor voltage



Comparison of switch utilizations of some common converters

Table 6.1. Active switch utilizations of some common dc-dc converters, single operating point.

Converter	$U(D)$	max $U(D)$	max $U(D)$ occurs at $D =$
Buck	\sqrt{D}	1	1
Boost	$\frac{D'}{\sqrt{D}}$	∞	0
Buck-boost, flyback, nonisolated SEPIC, isolated SEPIC, nonisolated Cuk, isolated Cuk	$D\sqrt{D}$	$\frac{2}{3\sqrt{3}} = 0.385$	$\frac{1}{3}$
Forward, $n_1 = n_2$	$\frac{1}{2}\sqrt{D}$	$\frac{1}{2\sqrt{2}} = 0.353$	$\frac{1}{2}$
Other isolated buck-derived converters (full-bridge, half-bridge, push-pull)	$\frac{\sqrt{D}}{2\sqrt{2}}$	$\frac{1}{2\sqrt{2}} = 0.353$	1
Isolated boost-derived converters (full bridge, push-pull)	$\frac{D'}{2\sqrt{1+D}}$	$\frac{1}{2}$	0

Active semiconductor cost vs. switch utilization

$$\left(\begin{array}{c} \text{semiconductor cost} \\ \text{per kW output power} \end{array} \right) = \frac{\left(\begin{array}{c} \text{semiconductor device cost} \\ \text{per rated kVA} \end{array} \right)}{\left(\begin{array}{c} \text{voltage} \\ \text{derating} \\ \text{factor} \end{array} \right) \left(\begin{array}{c} \text{current} \\ \text{derating} \\ \text{factor} \end{array} \right) \left(\begin{array}{c} \text{converter} \\ \text{switch} \\ \text{utilization} \end{array} \right)}$$


(semiconductor device cost per rated kVA) = cost of device, divided by product of rated blocking voltage and rms current, in \$/kVA. Typical values are less than \$1/kVA

(voltage derating factor) and (current derating factor) are required to obtain reliable operation. Typical derating factors are 0.5 - 0.75


Typical cost of active semiconductor devices in an isolated dc-dc converter: \$1 - \$10 per kW of output power.

6.3.1. Full-bridge and half-bridge isolated buck converters


Full-bridge isolated buck converter

 

 Full-bridge, with transformer equivalent circuit



Full-bridge: waveforms

 

- During first switching period: transistors Q_1 and Q_4 conduct for time DT_s , applying volt-seconds $V_g DT_s$ to primary winding
- During next switching period: transistors Q_2 and Q_3 conduct for time DT_s , applying volt-seconds $-V_g DT_s$ to primary winding
- Transformer volt-second balance is obtained over two switching periods
- Effect of nonidealities?

Effect of nonidealities on transformer volt-second balance

Volt-seconds applied to primary winding during first switching period:

$$(V_g - (Q_1 \text{ and } Q_4 \text{ forward voltage drops}))(Q_1 \text{ and } Q_4 \text{ conduction time})$$

Volt-seconds applied to primary winding during next switching period:

$$-(V_g - (Q_2 \text{ and } Q_3 \text{ forward voltage drops}))(Q_2 \text{ and } Q_3 \text{ conduction time})$$


These volt-seconds never add to *exactly* zero.

Net volt-seconds are applied to primary winding

Magnetizing current slowly increases in magnitude


Saturation can be prevented by placing a capacitor in series with primary, or by use of current programmed mode (Chapter 12)

Operation of secondary-side diodes

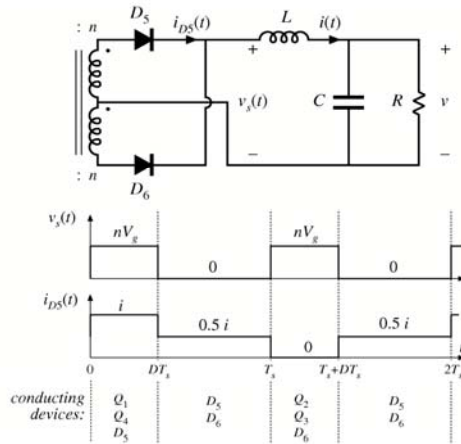

- During second (D') subinterval, both secondary-side diodes conduct
- Output filter inductor current divides approximately equally between diodes
- Secondary amp-turns add to approximately zero
- Essentially no net magnetization of transformer core by secondary winding currents

 Volt-second balance on output filter inductor




$$V = \langle v_s \rangle$$

$$V = nDV_g$$

$$M(D) = nD$$


buck converter with turns ratio

Half-bridge isolated buck converter

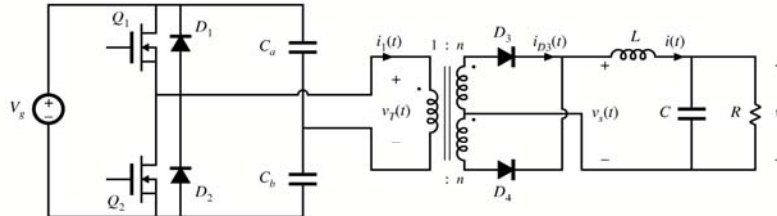


- Replace transistors Q_3 and Q_4 with large capacitors
- Voltage at capacitor centerpoint is $0.5V_g$
- $v_s(t)$ is reduced by a factor of two
- $M = 0.5 nD$

6.3.3. Push-pull isolated buck converter

 


$$V = nDV_g \quad 0 \leq D \leq 1$$

Waveforms: push-pull

 


- Used with low-voltage inputs
- Secondary-side circuit identical to full bridge
- As in full bridge, transformer volt-second balance is obtained over two switching periods
- Effect of nonidealities on transformer volt-second balance?
- Current programmed control can be used to mitigate transformer saturation problems. Duty cycle control not recommended.

6.3.2. Forward converter

 


- Buck-derived transformer-isolated converter
- Single-transistor and two-transistor versions
- Maximum duty cycle is limited
- Transformer is reset while transistor is off

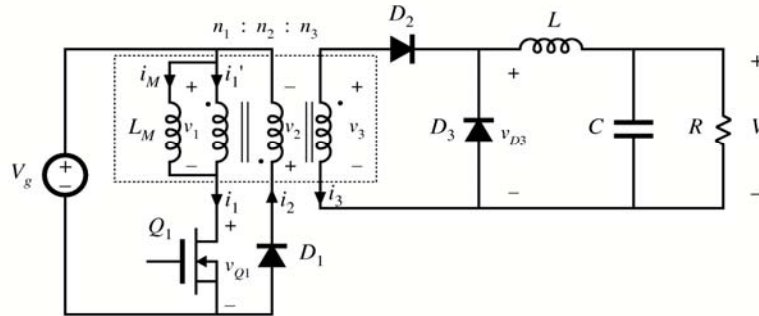Forward converter with transformer equivalent circuit




Forward converter: waveforms

 


- Magnetizing current, in conjunction with diode D_1 , operates in discontinuous conduction mode
- Output filter inductor, in conjunction with diode D_3 , may operate in either CCM or DCM


Subinterval 1: transistor conducts

 


Subinterval 2: transformer reset

 

Subinterval 3

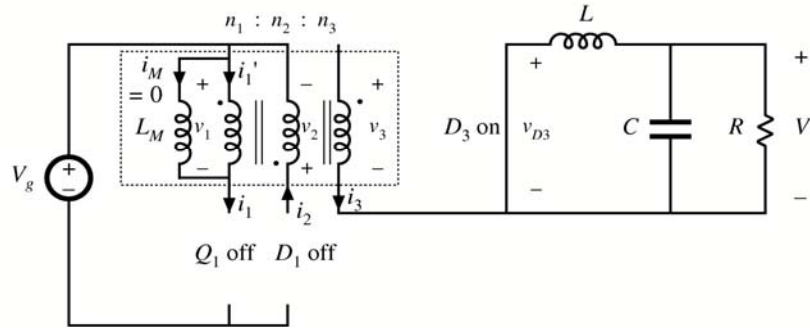

 Magnetizing inductance volt-second balance



Transformer reset

From magnetizing current volt-second balance:

$$\langle v_1 \rangle = D(V_g) + D_2(-V_g n_1/n_2) + D_3(0) = 0$$

Solve for D_2 :

$$D_2 = \frac{n_2}{n_1} D$$

D_3 cannot be negative. But $D_3 = 1 - D - D_2$. Hence

$$D_3 = 1 - D - D_2 \geq 0$$



$$D_3 = 1 - D \left(1 + \frac{n_2}{n_1} \right) \geq 0$$

Solve for D


$$D \leq \frac{1}{1 + \frac{n_2}{n_1}} \quad \text{for } n_1 = n_2: \quad D \leq \frac{1}{2}$$

What happens when $D > 0.5$

  magnetizing current waveforms, for $n_1 = n_2$



Conversion ratio $M(D)$

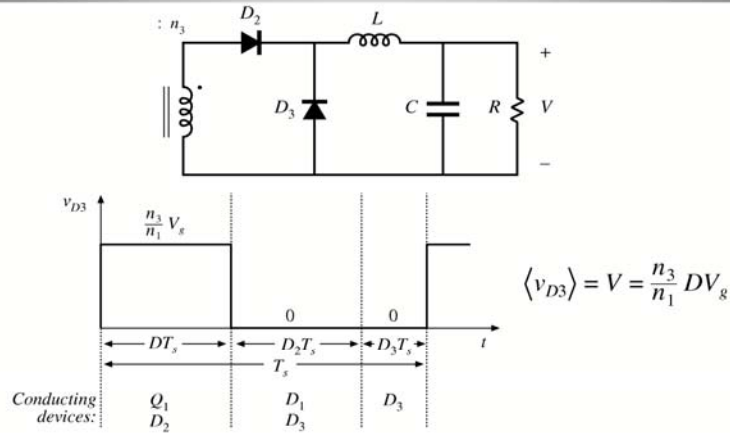

Maximum duty cycle vs. transistor voltage stress

Maximum duty cycle limited to

$$D \leq \frac{1}{1 + \frac{n_2}{n_1}}$$


which can be increased by increasing the turns ratio n_2/n_1 . But this increases the peak transistor voltage:

$$\max(v_{Q1}) = V_g \left(1 + \frac{n_1}{n_2} \right)$$

For $n_1 = n_2$

$$D \leq \frac{1}{2} \quad \text{and} \quad \max(v_{Q1}) = 2V_g$$

The two-transistor forward converter

 

$$V = nDV_g$$

$$D \leq \frac{1}{2}$$

$$\max(v_{Q1}) = \max(v_{Q2}) = V_g$$

Chapter 5. The Discontinuous Conduction Mode

- 5.1. Origin of the discontinuous conduction mode, and mode boundary
- 5.2. Analysis of the conversion ratio $M(D, K)$
- 5.3. Boost converter example
- 5.4. Summary of results and key points