
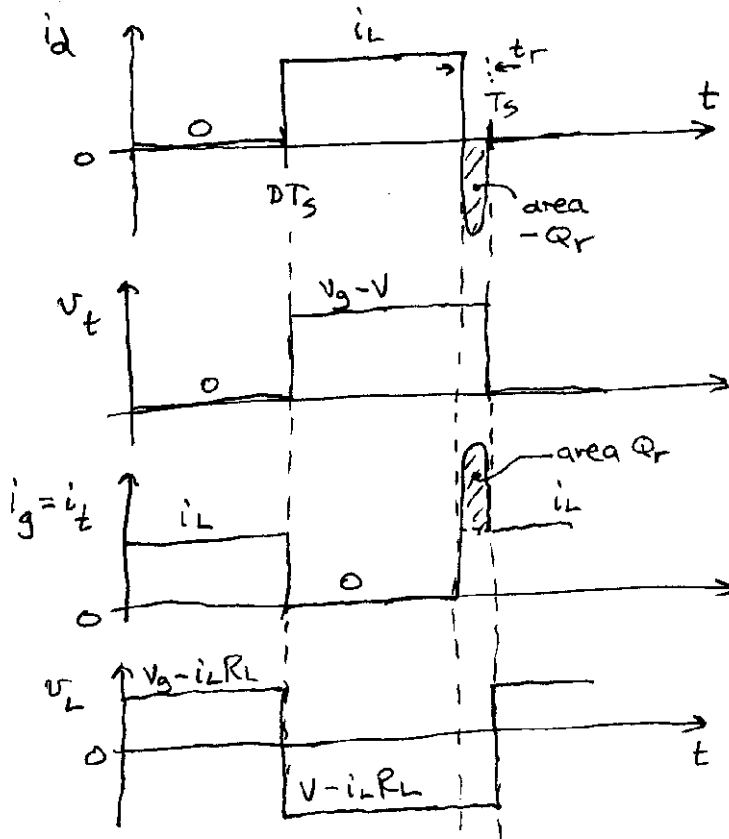


# Additional Problems on Switching Loss

Introduction to Power Electronics  
Fall 2004

- 1 A certain buck-boost converter is implemented with a MOSFET and a  $p-n$  diode. The MOSFET can be modeled as ideal, but the diode exhibits a substantial reverse-recovery process, with reverse recovery time  $t_r$  and recovered charge  $Q_r$ . In addition, the inductor has winding resistance  $R_L$ .  
Derive an equivalent circuit that models the dc components of the converter waveforms and that accounts for the loss elements described above.

Solution

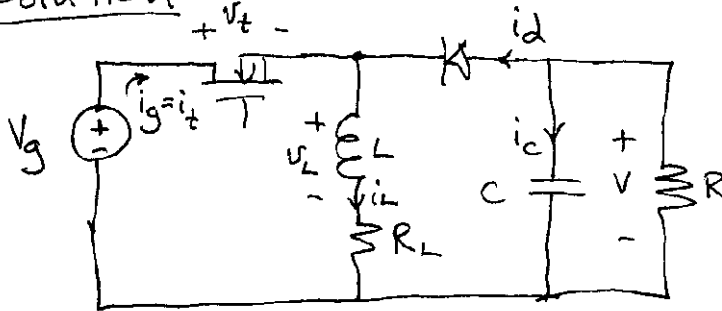


Small ripple approximation:  
 $i_L(t) \approx I_L$   
 $v(t) \approx V$

## Volt-second balance

$$\langle v_L \rangle = 0 = D(V_g - I_L R_L) + D'(V - I_L R_L)$$

$$\text{with } D' = 1 - D$$
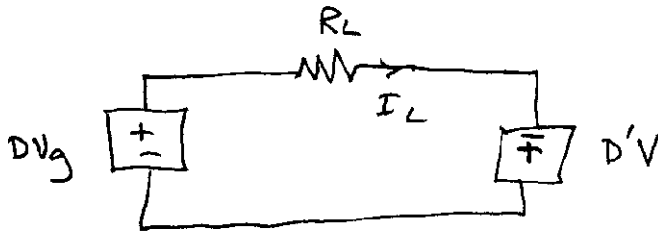
$$\text{so } \langle v_L \rangle = 0 = D V_g - I_L R_L + D' V$$




## charge balance

$$i_c + i_d + \frac{V}{R} = 0 \quad \text{with } \langle i_c \rangle = 0$$

$$\text{so } \langle i_c \rangle = - \langle i_d \rangle - \frac{V}{R} = 0$$

$$\text{and } \langle i_d \rangle = \left[ -Q_r + I_L \cdot (D'T_s - t_r) \right] \frac{1}{T_s}$$

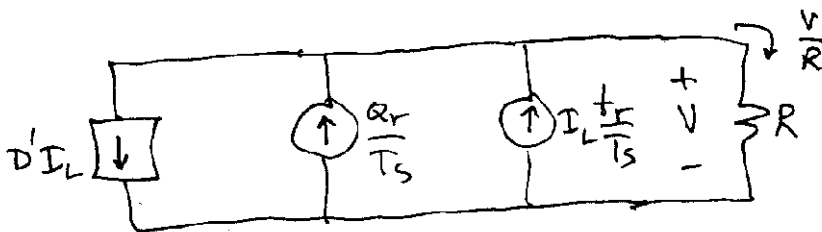
$$\text{so } \langle i_c \rangle = 0 = \frac{Q_r}{T_s} - D'I_L + I_L \frac{t_r}{T_s} - \frac{V}{R}$$




average input current

$$I_g = \langle i_g \rangle = \langle i_t \rangle = \frac{1}{T_s} \left[ I_L D T_s + Q_r + t_r I_L \right]$$

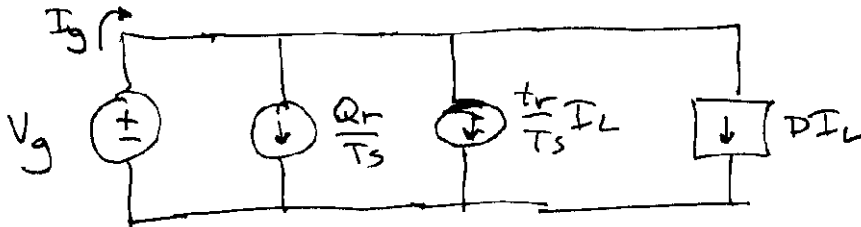
$$= D I_L + \frac{Q_r}{T_s} + \frac{t_r}{T_s} I_L$$



Combine circuits

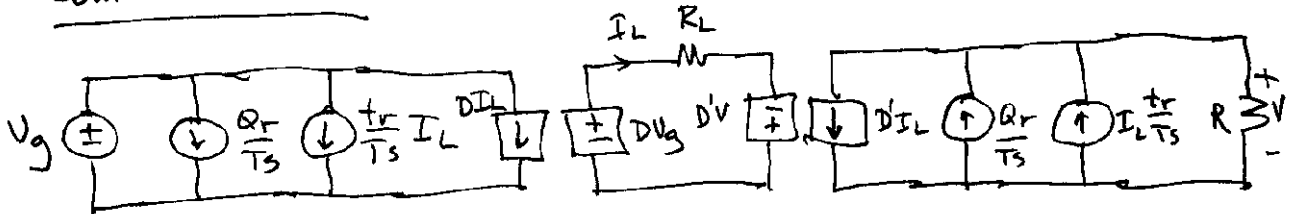

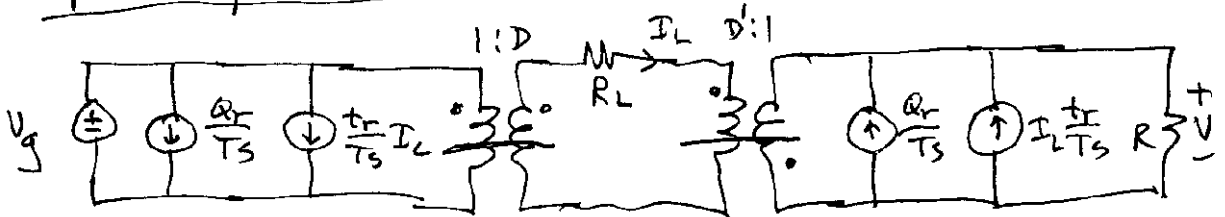Replace dependant sources with transformers



Note that V is negative