

## Announcements

**Systems Skill Series**

# Soldering Workshop

*Come sharpen your soldering skills  
with Systems and IEEE East TN*

**Wednesday, September 16, 2015**

**4:30PM**

**MK 336**


**Refreshments Provided**



THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE




## MOSFET Cross Section

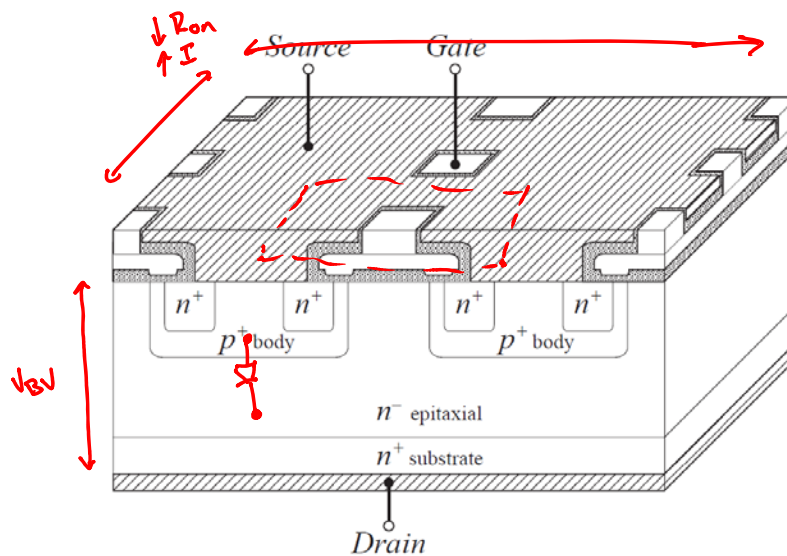

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE




## Power MOSFET in Ohmic Region

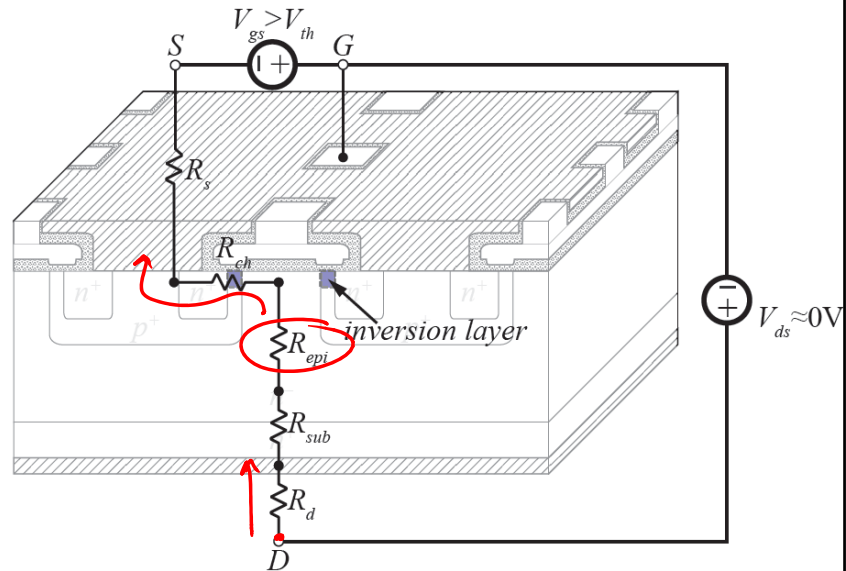


THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE

## MOSFET Static Characteristics

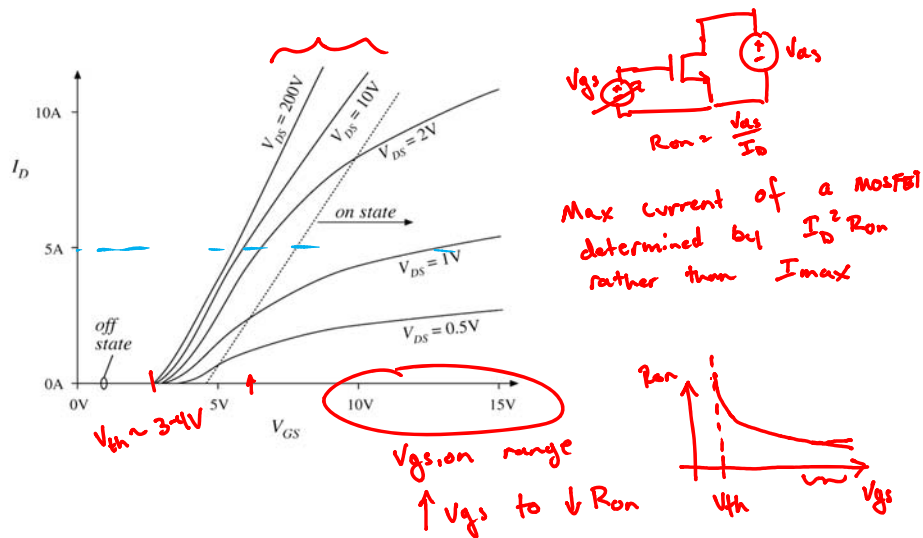


THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE

## MOSFET Depletion capacitance

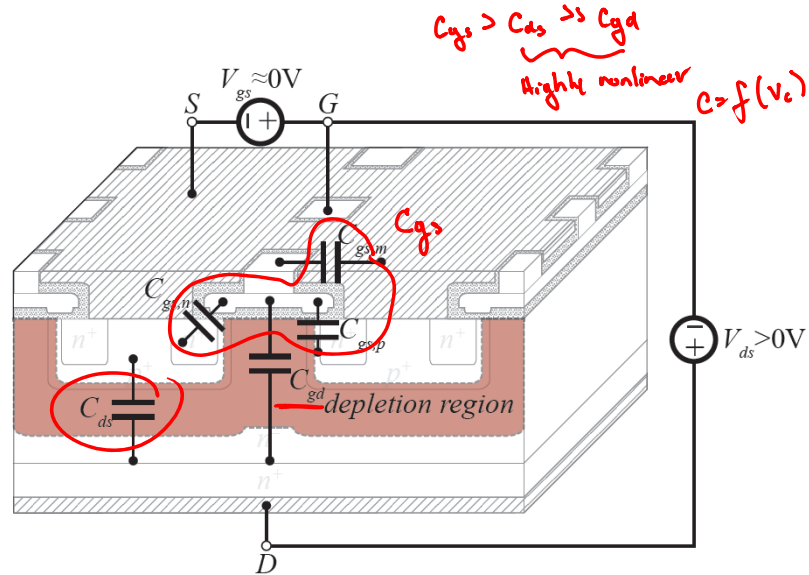

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE


## MOSFET Equivalent Circuit

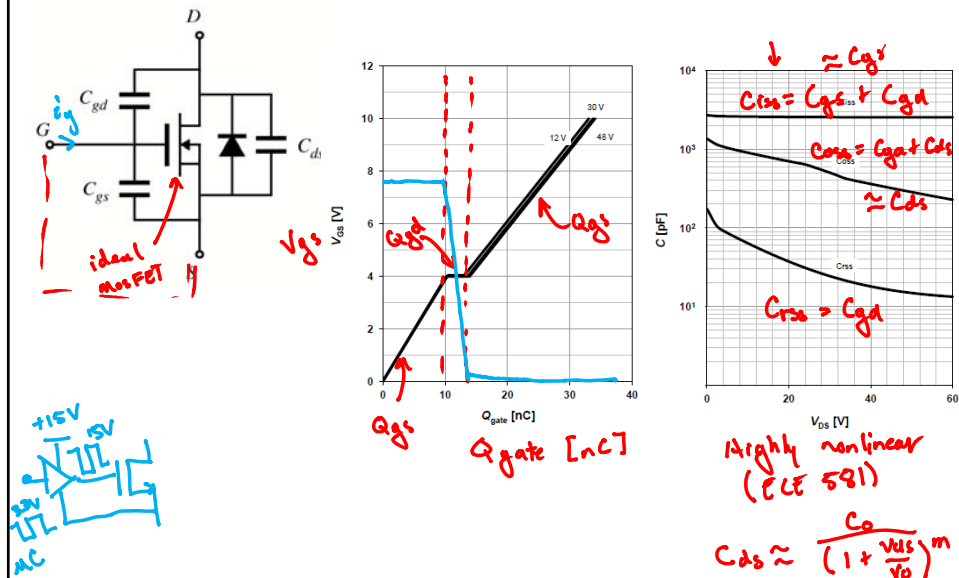


THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE
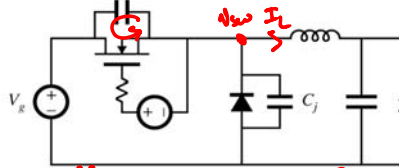
## Switching Losses: Output Capacitance

Assume  $C_{ds}$  &  $C_j$  are linear  
+  $V_{ds} -$




① MOSFET Turn-off

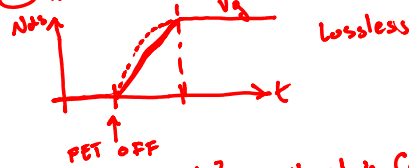

$$E_{ds} = \frac{1}{2} C_{ds} V_g^2 \rightarrow \text{stored in } C_{ds}$$

$$E_j = -\frac{1}{2} C_j V_g^2 \rightarrow \text{supplied by } C_j$$

② MOSFET Turn-on

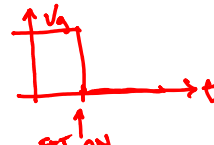


$$E_{ds} = \frac{1}{2} C_{ds} V_g^2 \rightarrow \text{Now lost in MOSFET}$$

$$E_j = \frac{1}{2} C_j V_g^2 \rightarrow \text{Also lost in MOSFET}$$

$$P_{sw,e} = (E_{ds} + E_j) f_s$$

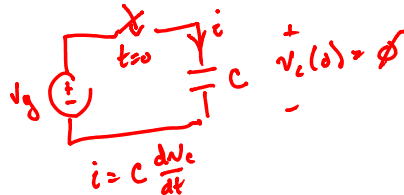THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE



$$i = C \frac{dv_c}{dt}$$

$$P_{sw} = \int_0^\infty i (V_g - v_c) dt$$

$$P_{sw} = \int_0^\infty C (V_g - v_c) \frac{dv_c}{dt} dt$$

$$= \int_0^{V_g} C (V_g - v_c) dv_c$$

$$= \int_0^{V_g} C V_g dv_c - \int_0^{V_g} C v_c dv_c$$

$$= C V_g^2 - C \frac{V_g^2}{2} = \frac{1}{2} C V_g^2$$

$$C V_g \int_0^{V_g} 1 dv_c - C \int_0^{V_g} v_c dv_c$$

Power losses due  
to capacitive switching  
even in an ideal  
switch!

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE



### Averaged Equivalent Circuit Model – Switching Loss


- The methods of Chapter 3 can be extended to include switching loss in the converter equivalent circuit model
  - Include switching transitions in the converter waveforms
  - Model effects of ~~diode reverse recovery~~, etc.
- To obtain tractable results, the waveforms during the switching transitions must usually be approximated
- Things that can substantially change the results:
  - Ringing caused by parasitic tank circuits
  - Snubber circuits

### The Modeling Approach

- Sketch the converter waveforms
  - Including the switching transitions (idealizing assumptions are made to lead to tractable results)
  - In particular, sketch inductor voltage, capacitor current, and input current waveforms
- The usual steady-state relationships:
  - $\langle v_L \rangle = 0, \langle i_C \rangle = 0, \langle i_g \rangle = I_g$
- Use the resulting equations to construct an equivalent circuit model, as usual

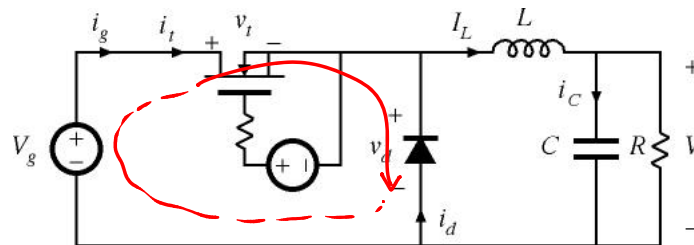
## Buck Converter Example

- Ideal MOSFET,  $p$ - $n$  diode with reverse recovery
- Neglect semiconductor device capacitances, MOSFET switching times, etc.
- Neglect conduction losses
- Neglect ripple in inductor current and capacitor voltage



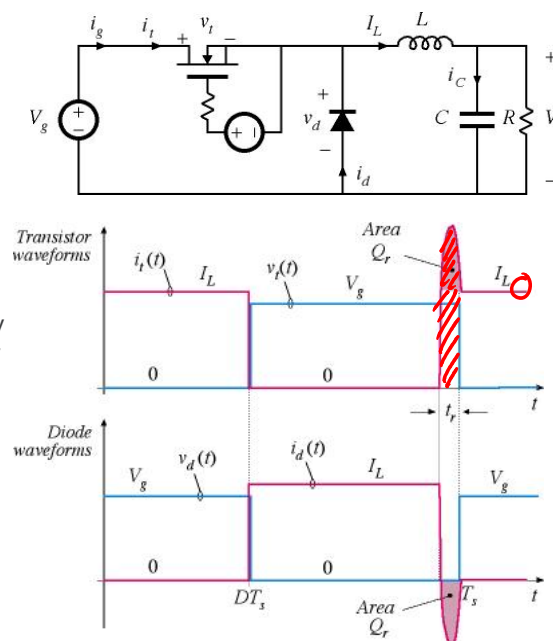
## Assumed waveforms

- Diode recovered charge  $Q_r$ , reverse recovery time  $t_r$
- These waveforms assume that the diode voltage changes at the end of the reverse recovery transient
  - a “snappy” diode
  - Voltage of soft-recovery diodes changes sooner
  - Leads to a pessimistic estimate of induced switching loss



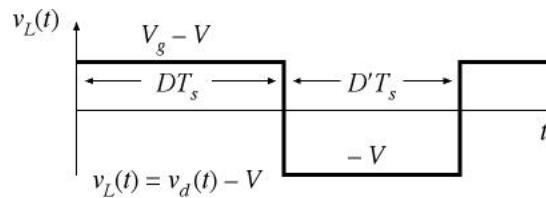
## Inductor volt-second & Cap-Charge balance



As usual:  $\langle v_L \rangle = 0 = DV_g - V$  ✓

Also as usual:  $\langle i_C \rangle = 0 = I_L - V/R$  ✓

## Average input current

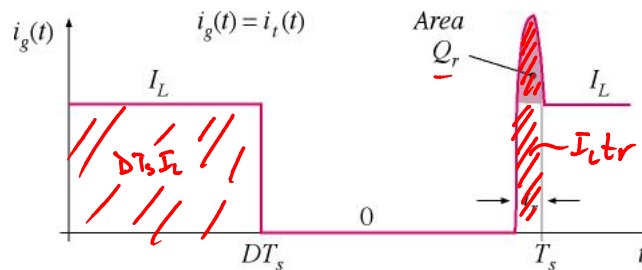


$$\begin{aligned}\langle i_g \rangle &= I_g = (\text{area under curve})/T_s \\ &= (DT_s I_L + t_r I_L + Q_r)/T_s \\ &= DI_L + t_r I_L/T_s + Q_r/T_s\end{aligned}$$
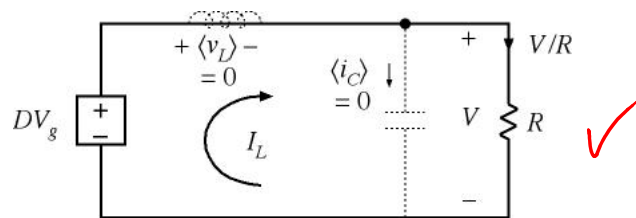
## Construction of Equivalent Circuit Model


From inductor volt-second balance:  $\langle v_L \rangle = 0 = DV_g - V$

From capacitor charge balance:  $\langle i_C \rangle = 0 = I_L - V/R$



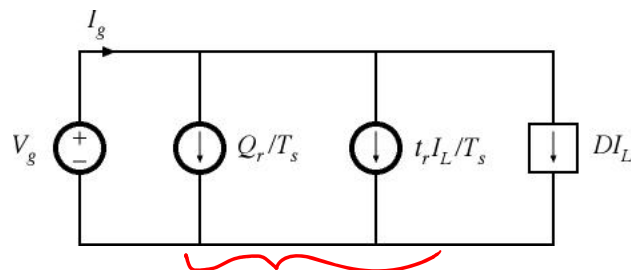
## Input port of model

$$\langle i_g \rangle = I_g = DI_L + t_r I_L / T_s + Q_r / T_s$$





## Combine for complete model

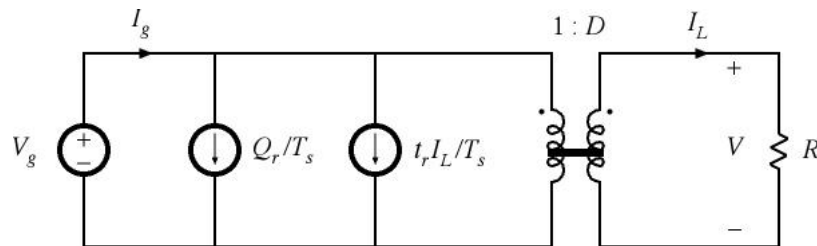

The two independent current sources consume power


$$V_g (t_r I_L / T_s + Q_r / T_s)$$

equal to the switching loss induced by diode reverse recovery

## Solution of model

**Output:**

$$V = DV_g$$

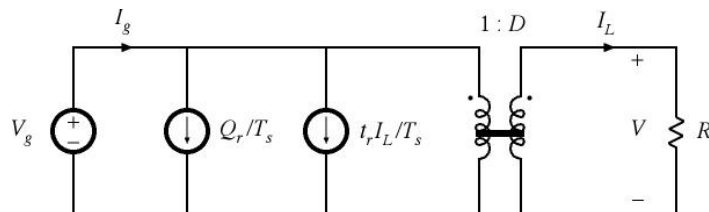

**Efficiency:**  $\eta = P_{out} / P_{in}$


$$P_{out} = VI_L \quad P_{in} = V_g (DI_L + t_r I_L / T_s + Q_r / T_s)$$

Combine and simplify:

$$\eta = 1 / [1 + f_s (t_r / D + Q_r R / D^2 V_g)]$$

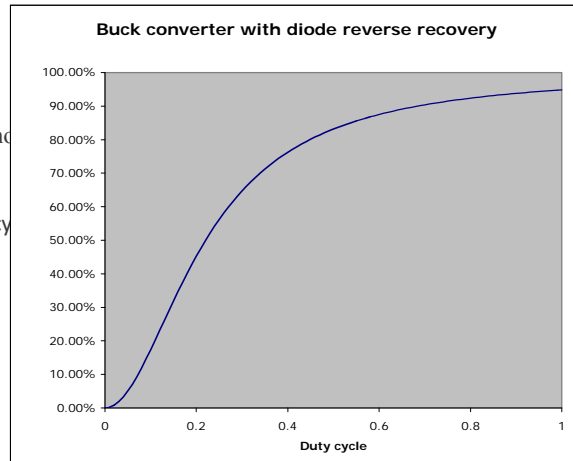
## Predicted Efficiency vs Duty Cycle

- Switching frequency 100 kHz
- Input voltage 24 V
- Load resistance 15  $\Omega$
- Recovered charge 0.75  $\mu\text{Coul}$
- Reverse recovery time 75 nsec
- (no attempt is made here to model h  
inductor current)
- Substantial degradation of efficiency
- Poor efficiency at low duty cycle



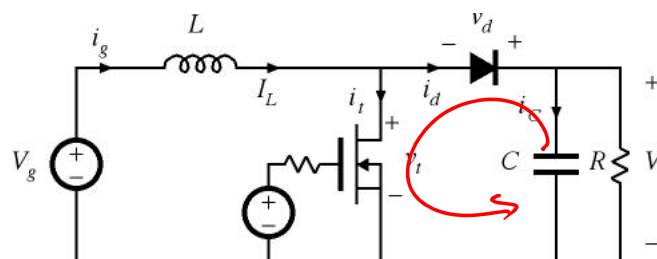
## Boost Converter Example

- Model same effects as in previous buck converter example:
- Ideal MOSFET,  $p-n$  diode with reverse recovery
- Neglect semiconductor device capacitances, MOSFET switching times, etc.
- Neglect conduction losses
- Neglect ripple in inductor current and capacitor voltage




## Boost converter

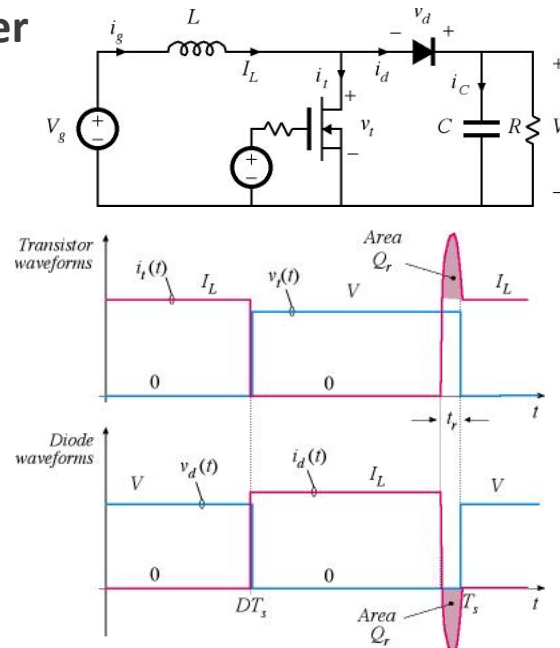

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE


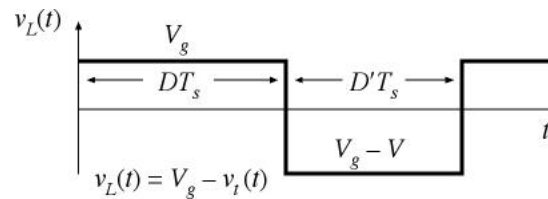
## Inductor volt-second balance and average input current




As usual:  $\langle v_L \rangle = 0 = V_g - D'V$

Also as usual:  $\langle i_g \rangle = I_L$

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE



## Capacitor charge balance

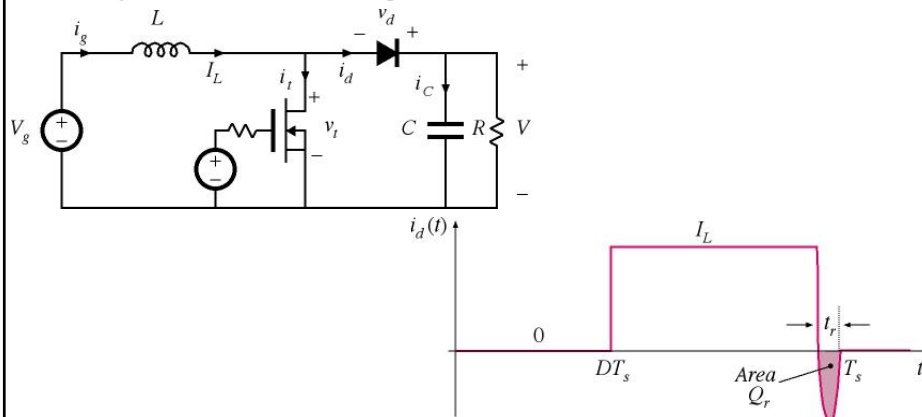


$$\langle i_C \rangle = \langle i_d \rangle - V/R = 0$$

$$= -V/R + I_L(D'T_s - t_r)/T_s - Q_r/T_s$$

$$\text{Collect terms: } V/R = I_L(D'T_s - t_r)/T_s - Q_r/T_s$$

## Construct model

The result is:

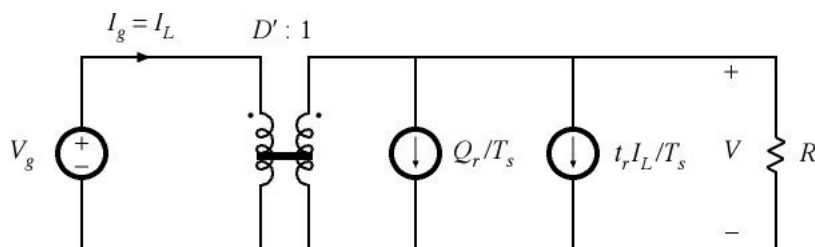

The two independent current sources consume power

$$V(t_r I_L/T_s + Q_r/T_s)$$

equal to the switching loss induced by diode reverse recovery

## Predicted $M$ vs duty cycle

- Switching frequency 100 kHz
- Input voltage 24 V
- Load resistance 60  $\Omega$
- Recovered charge 5  $\mu\text{Coul}$
- Reverse recovery time 100 nsec
- Inductor resistance  $R_L = 0.3 \Omega$
- (inductor resistance also inserted into averaged model here)

