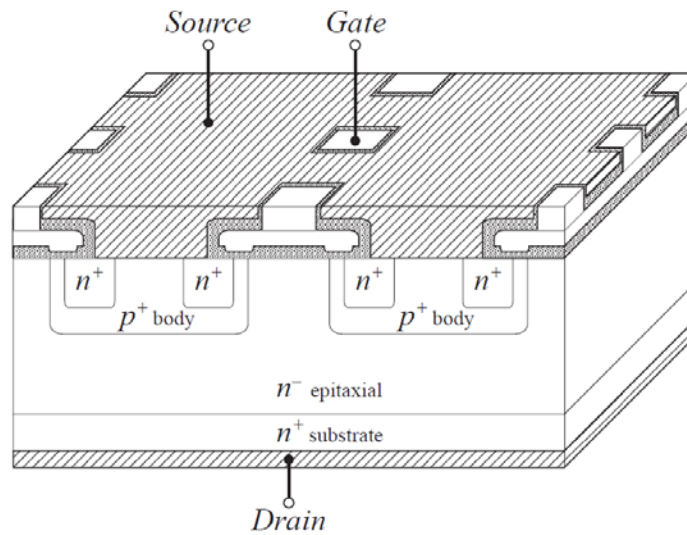



MOSFET Cross Section



THE UNIVERSITY OF
TENNESSEE
KNOXVILLE




Power MOSFET in Ohmic Region

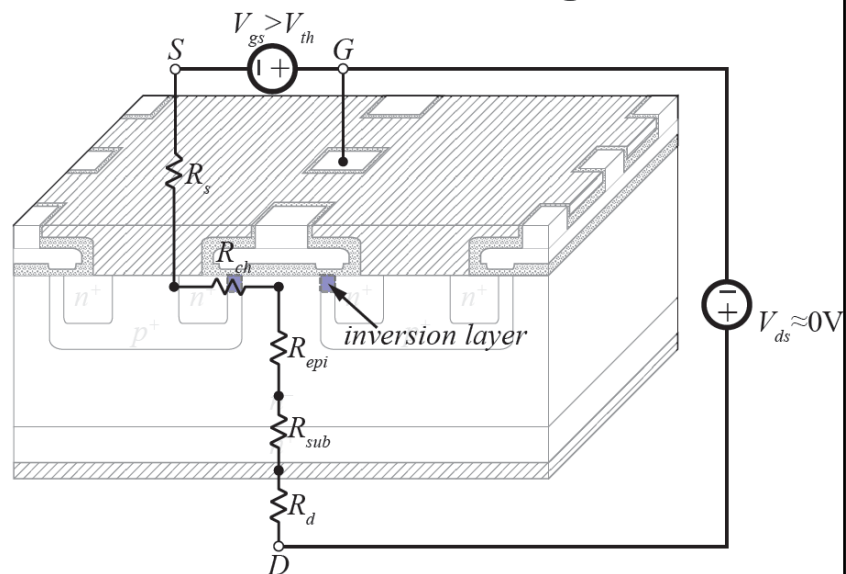


THE UNIVERSITY OF
TENNESSEE
KNOXVILLE




MOSFET Static Characteristics

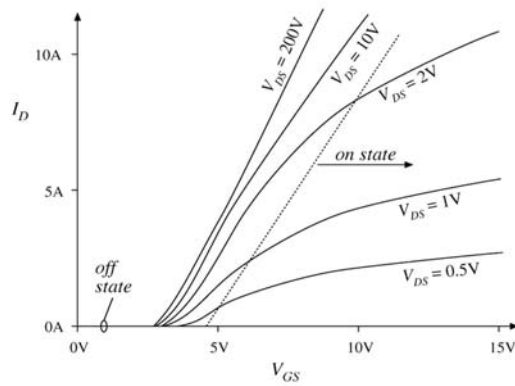

MOSFET Depletion capacitance

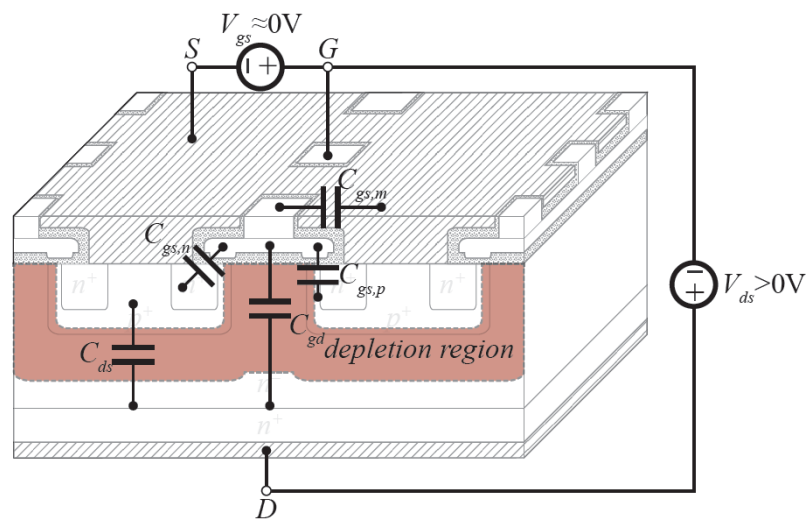


MOSFET Equivalent Circuit

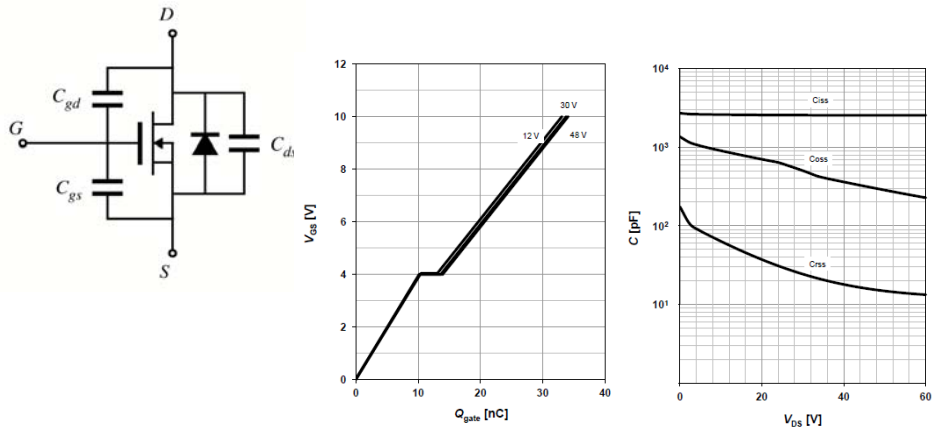

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE




Switching Losses: Output Capacitance

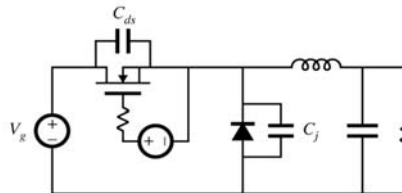

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE



Wide Bandgap Materials

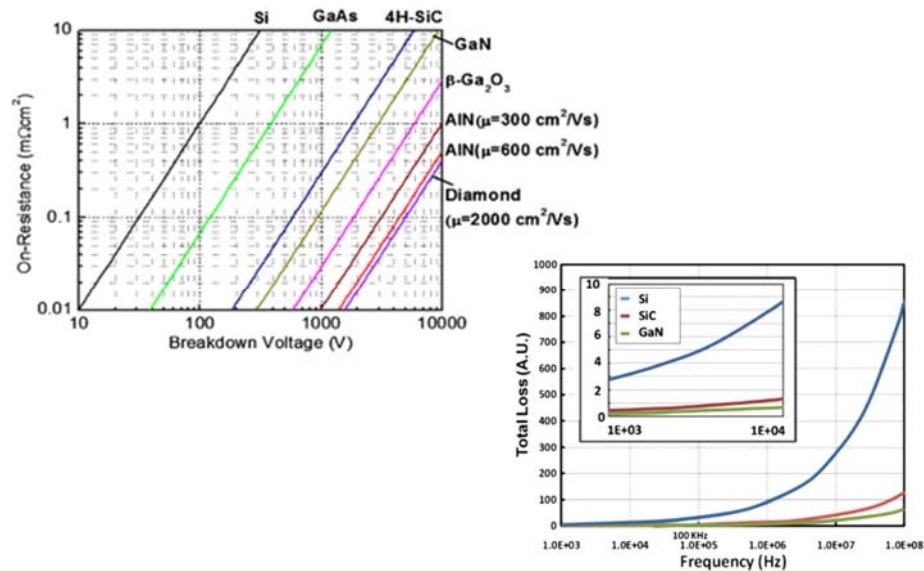


Srabanti Chowdhury *et al* "Current status and scope of gallium nitride-based vertical transistors for high-power electronics application" 2013 *Semicond. Sci. Technol.* 28, 074014



Power MOSFET: Conclusions

- A majority-carrier device: fast switching speed
- Typical switching frequencies: tens and hundreds of kHz
- On-resistance increases rapidly with rated blocking voltage
- Easy to drive
- The device of choice for blocking voltages less than 500V
- 1000V devices are available, but are useful only at low power levels (100W)
- Part number is selected on the basis of on-resistance rather than current rating

Bipolar Junction Transistor

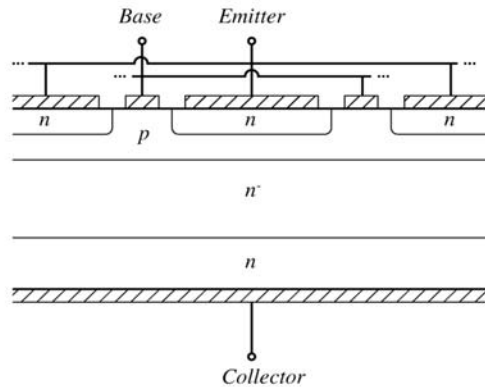


- Interdigitated base and emitter contacts
- Vertical current flow
- npn device is shown
- minority carrier device
- on-state: base-emitter and collector-base junctions are both forward-biased
- on-state: substantial minority charge in p and n^+ regions, conductivity modulation

BJT: Conclusions



- BJT has been replaced by MOSFET in low-voltage (<500V) applications
- BJT is being replaced by IGBT in applications at voltages above 500V
- A minority-carrier device: compared with MOSFET, the BJT exhibits slower switching, but lower on-resistance at high voltages

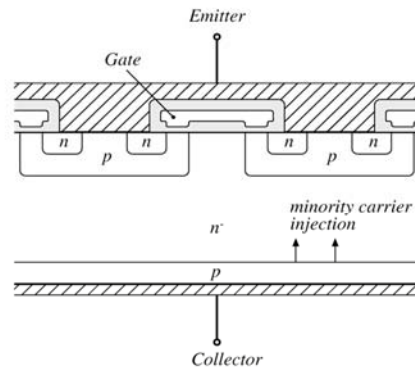Insulated Gate Bipolar Junction Transistor




- A four-layer device
- Similar in construction to MOSFET, except extra p region
- On-state: minority carriers are injected into n^- region, leading to conductivity modulation
- compared with MOSFET: slower switching times, lower on-resistance, useful at higher voltages (up to 1700V)



The IGBT

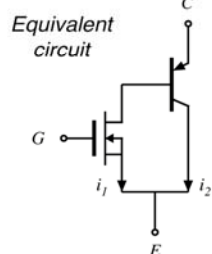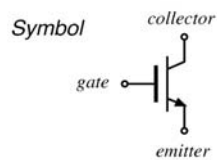

Location of equivalent devices

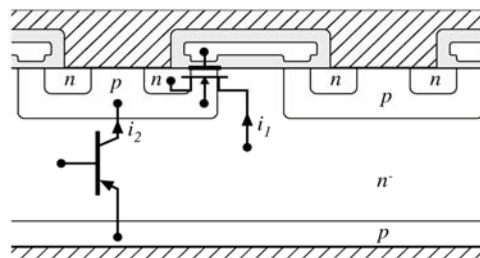

IGBT: Current Tailing

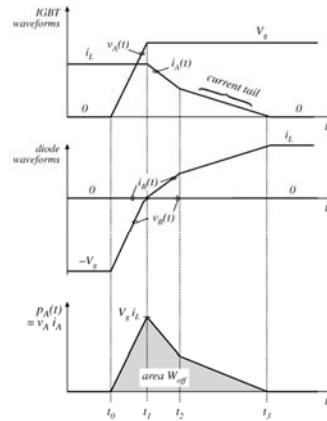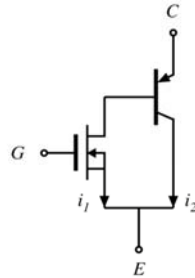

Fundamentals of Power Electronics

66

Chapter 4: Switch realization

Conclusions: IGBT

- Becoming the device of choice in 500 to 1700V+ applications, at power levels of 1-1000kW
- Positive temperature coefficient at high current —easy to parallel and construct modules
- Forward voltage drop: diode in series with on-resistance. 2-4V typical
- Easy to drive —similar to MOSFET
- Slower than MOSFET, but faster than Darlington, GTO, SCR
- Typical switching frequencies: 3-30kHz
- IGBT technology is rapidly advancing:
 - 3300 V devices: HVIGBTs
 - 150 kHz switching frequencies in 600 V devices

Fundamentals of Power Electronics

69

Chapter 4: Switch realization

Averaged Equivalent Circuit Model – Switching Loss


- The methods of Chapter 3 can be extended to include switching loss in the converter equivalent circuit model
 - Include switching transitions in the converter waveforms
 - Model effects of diode reverse recovery, etc.
- To obtain tractable results, the waveforms during the switching transitions must usually be approximated
- Things that can substantially change the results:
 - Ringing caused by parasitic tank circuits
 - Snubber circuits

The Modeling Approach

- Sketch the converter waveforms
 - Including the switching transitions (idealizing assumptions are made to lead to tractable results)
 - In particular, sketch inductor voltage, capacitor current, and input current waveforms
- The usual steady-state relationships:
 - $\langle v_L \rangle = 0, \langle i_C \rangle = 0, \langle i_g \rangle = I_g$
- Use the resulting equations to construct an equivalent circuit model, as usual


Buck Converter Example

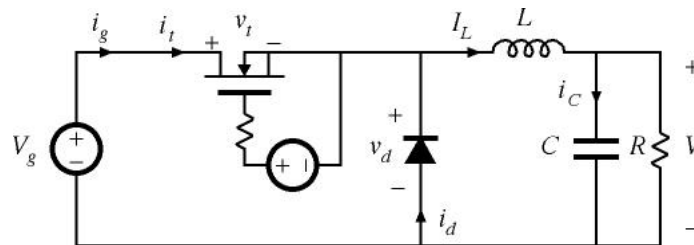- Ideal MOSFET, p - n diode with reverse recovery
- Neglect semiconductor device capacitances, MOSFET switching times, etc.
- Neglect conduction losses
- Neglect ripple in inductor current and capacitor voltage




Assumed waveforms

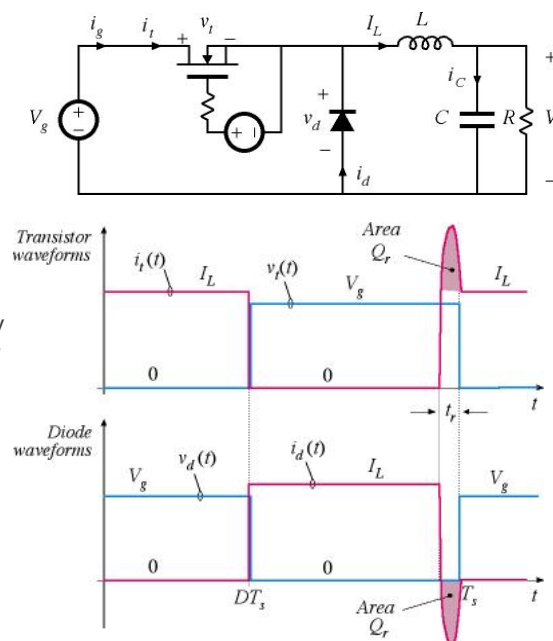- Diode recovered charge Q_r , reverse recovery time t_r
- These waveforms assume that the diode voltage changes at the end of the reverse recovery transient
 - a “snappy” diode
 - Voltage of soft-recovery diodes changes sooner
 - Leads to a pessimistic estimate of induced switching loss



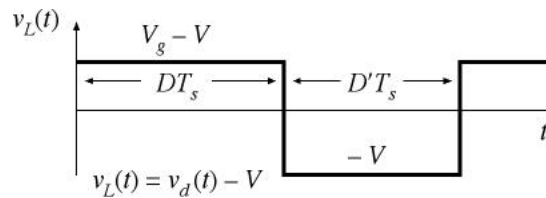
Inductor volt-second & Cap-Charge balance



As usual: $\langle v_L \rangle = 0 = DV_g - V$

Also as usual: $\langle i_C \rangle = 0 = I_L - V/R$

Average input current

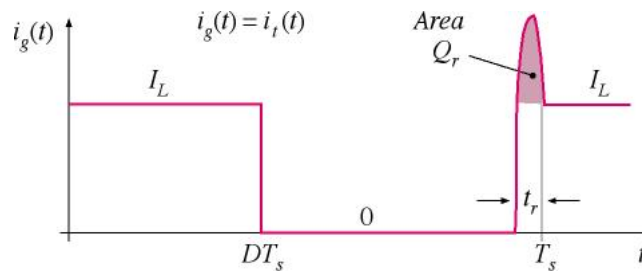


$$\begin{aligned} \langle i_g \rangle &= I_g = (\text{area under curve})/T_s \\ &= (DT_s I_L + t_r I_L + Q_r)/T_s \\ &= DI_L + t_r I_L/T_s + Q_r/T_s \end{aligned}$$

Construction of Equivalent Circuit Model


From inductor volt-second balance: $\langle v_L \rangle = 0 = DV_g - V$

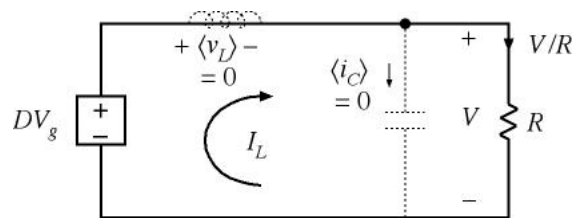From capacitor charge balance: $\langle i_C \rangle = 0 = I_L - V/R$




Input port of model
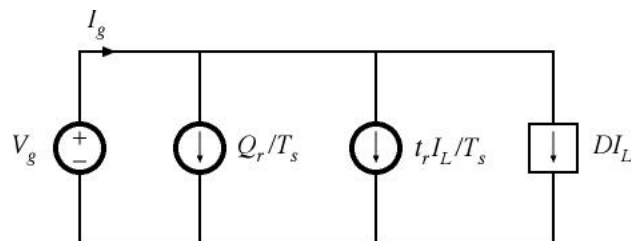
$$\langle i_g \rangle = I_g = DI_L + t_r I_L / T_s + Q_r / T_s$$



Combine for complete model

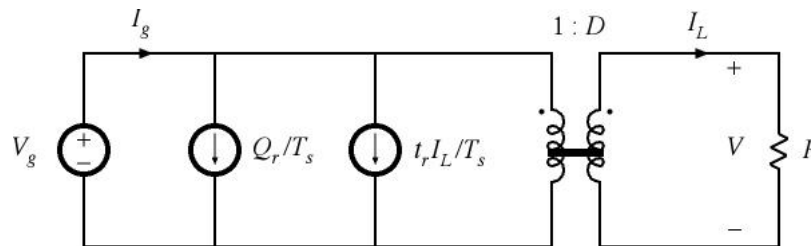

The two independent current sources consume power


$$V_g (t_r I_L / T_s + Q_r / T_s)$$

equal to the switching loss induced by diode reverse recovery

Solution of model

Output:

$$V = DV_g$$

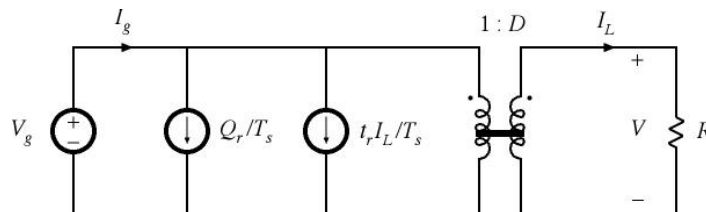

Efficiency: $\eta = P_{out} / P_{in}$


$$P_{out} = VI_L \quad P_{in} = V_g (DI_L + t_r I_L / T_s + Q_r / T_s)$$

Combine and simplify:

$$\eta = 1 / [1 + f_s (t_r / D + Q_r R / D^2 V_g)]$$


Predicted Efficiency vs Duty Cycle

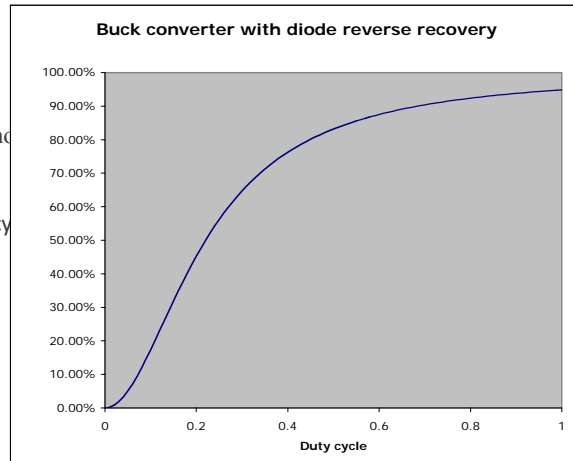- Switching frequency 100 kHz
- Input voltage 24 V
- Load resistance 15 Ω
- Recovered charge 0.75 μCoul
- Reverse recovery time 75 nsec
- (no attempt is made here to model h
inductor current)
- Substantial degradation of efficiency
- Poor efficiency at low duty cycle




Boost Converter Example

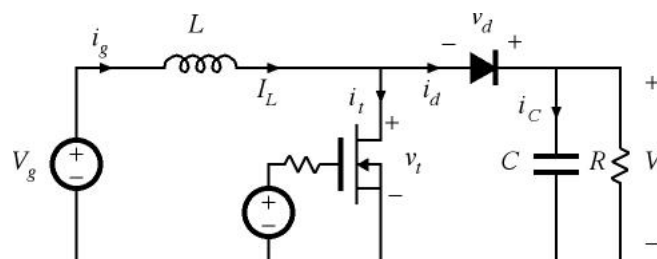- Model same effects as in previous buck converter example:
- Ideal MOSFET, $p-n$ diode with reverse recovery
- Neglect semiconductor device capacitances, MOSFET switching times, etc.
- Neglect conduction losses
- Neglect ripple in inductor current and capacitor voltage




Boost converter

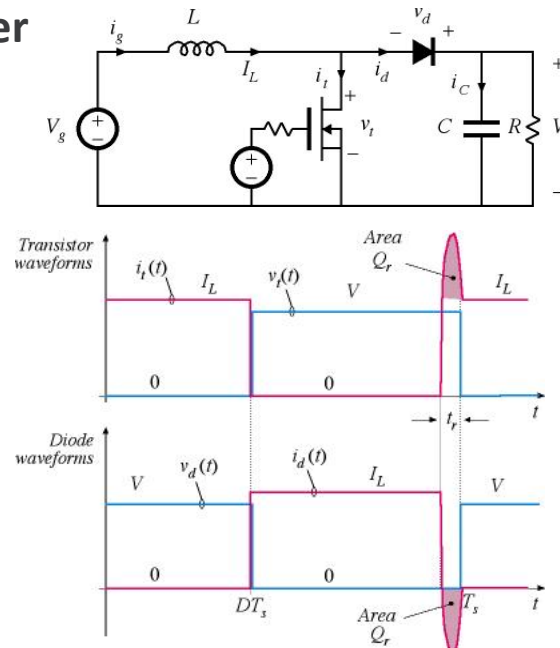

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE



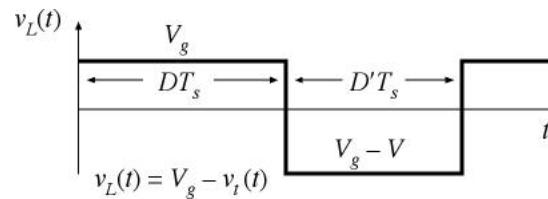Inductor volt-second balance and average input current




As usual: $\langle v_L \rangle = 0 = V_g - D'V$

Also as usual: $\langle i_g \rangle = I_L$

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE



Capacitor charge balance

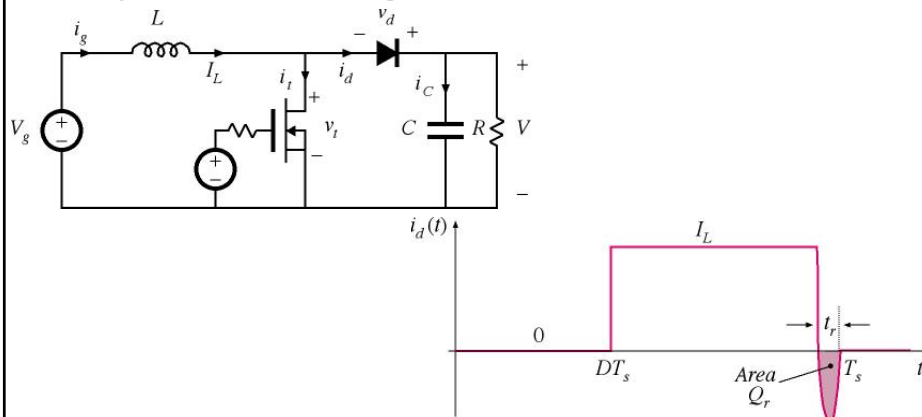


$$\langle i_C \rangle = \langle i_d \rangle - V/R = 0$$

$$= -V/R + I_L(D'T_s - t_r)/T_s - Q_r/T_s$$

$$\text{Collect terms: } V/R = I_L(D'T_s - t_r)/T_s - Q_r/T_s$$

Construct model

The result is:

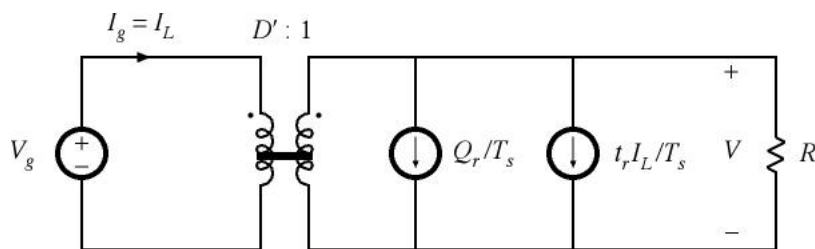

The two independent current sources consume power

$$V(t_r I_L/T_s + Q_r/T_s)$$

equal to the switching loss induced by diode reverse recovery

Predicted M vs duty cycle

- Switching frequency 100 kHz
- Input voltage 24 V
- Load resistance 60 Ω
- Recovered charge 5 μCoul
- Reverse recovery time 100 nsec
- Inductor resistance $R_L = 0.3 \Omega$
- (inductor resistance also inserted into averaged model here)

