
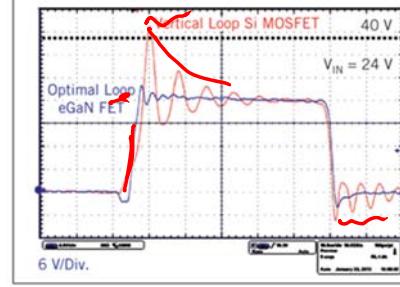


Experimental Switching Waveforms

Ct. more detailed switching model

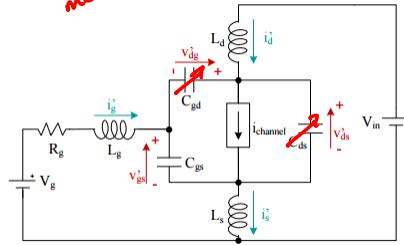

Approaches to reduce ringing:

- (1) Select new device
- (2) Improve layout

D Reusch, "eGaN® FET-Silicon Power Shoot-Out Vol. 13, Part 2: Optimal PCB Layout"
M Rodriguez et al, "Analysis of the switching process of power MOSFETs using a new analytical losses model"

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

The Double Pulse Test

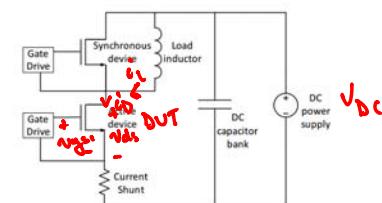


Fig. 7. Double pulse test circuit schematic.

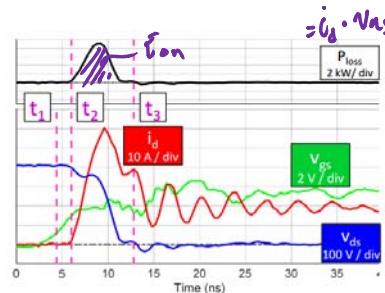
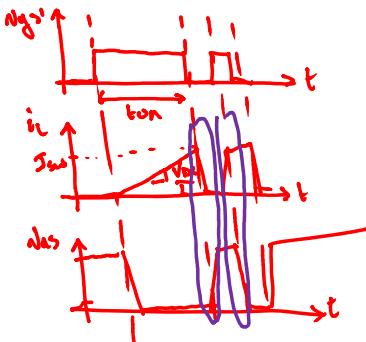


Fig. 11. Turn-on waveform at 400 V, 10 A, 25 °C.

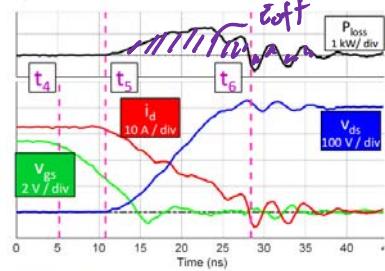


Fig. 12. Turn-off waveform at 400 V, 10 A, 25 °C.

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

The Double Pulse Test

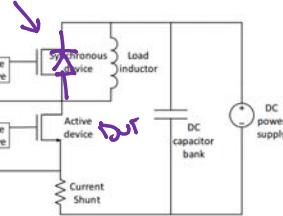
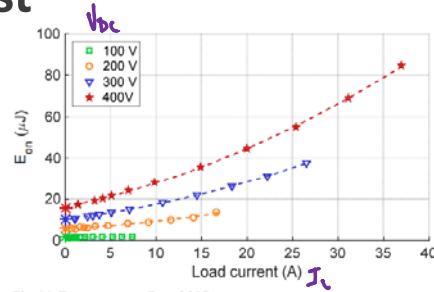
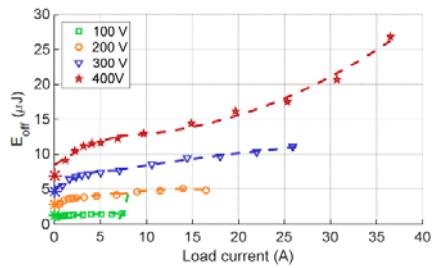


Fig. 7. Double pulse test circuit schematic.

- Purely empirical approach
- occasionally provided in a datasheet
- $E_{on} \rightarrow E_{off}$ vary significantly w/ layout & Gate Drive circuit


Fig. 16. Turn-on energy E_{on} at 25 °C.THE UNIVERSITY OF
TENNESSEE
KNOXVILLE 

Converter Efficiency Vs. f_s



$$P_{loss} = P_{cond} + P_{sw} + P_{fixed} \quad \text{e.g. controller power}$$

$f(f_s)$

- | | |
|--|---|
| <ul style="list-style-type: none"> • Less P_{sw} • lower EMI/ noise at HF | <ul style="list-style-type: none"> • Less ripple • smaller passives • faster control |
|--|---|
- f_s
- oltz
- 60Hz 1kHz 60Hz 100kHz 1MHz
- High power line-commutated rectifier
- High power IGBT-based e.g. EV traction drives
- General power supplies


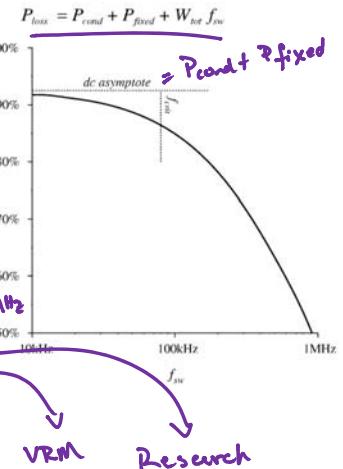
THE UNIVERSITY OF
TENNESSEE
KNOXVILLE 

Die Size Selection

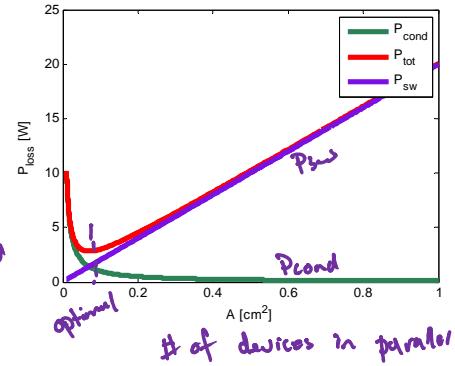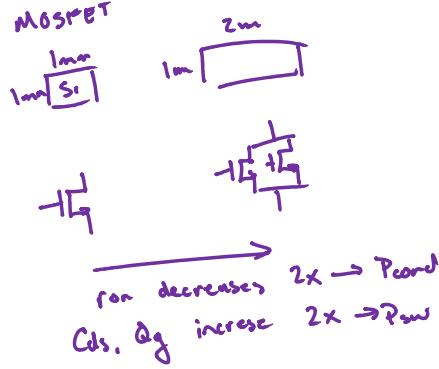

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Converter Optimization

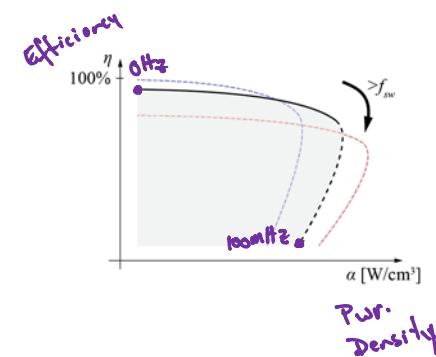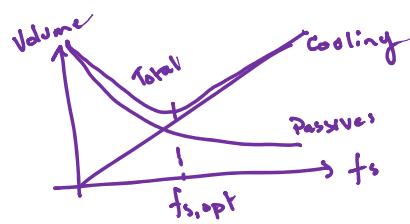

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

