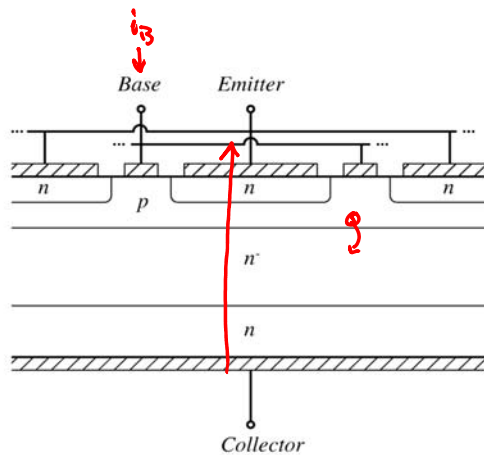


## Announcements

- Next week: ECCE Conference Mon.-Thurs.
  - Recorded lectures to be posted on the website
  - Generally available via e-mail for questions
  - Homework as normal
  - [http://2015.ecceconferences.org/wp-content/uploads/2015/09/ECCE2015program\\_webSep131.pdf](http://2015.ecceconferences.org/wp-content/uploads/2015/09/ECCE2015program_webSep131.pdf)

## Bipolar Junction Transistor




- Interdigitated base and emitter contacts
- Vertical current flow
- npn device is shown
- minority carrier device
- on-state: base-emitter and collector-base junctions are both forward-biased
- on-state: substantial minority charge in  $p$  and  $n$  regions, conductivity modulation

## BJT: Conclusions



- BJT has been replaced by MOSFET in low-voltage (<500V) applications
- BJT is being replaced by IGBT in applications at voltages above 500V
- A minority-carrier device: compared with MOSFET, the BJT exhibits slower switching, but lower on-resistance at high voltages
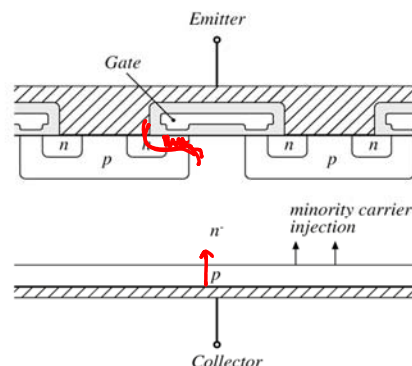
## Insulated Gate Bipolar Junction Transistor




- A four-layer device
- Similar in construction to MOSFET, except extra  $p$  region
- On-state: minority carriers are injected into  $n^-$  region, leading to conductivity modulation
- compared with MOSFET: slower switching times, lower on-resistance, useful at higher voltages (up to 1700V)

# The IGBT

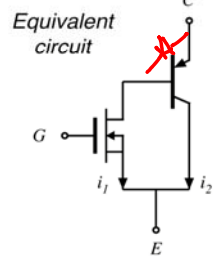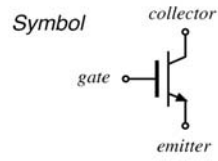

Location of equivalent devices


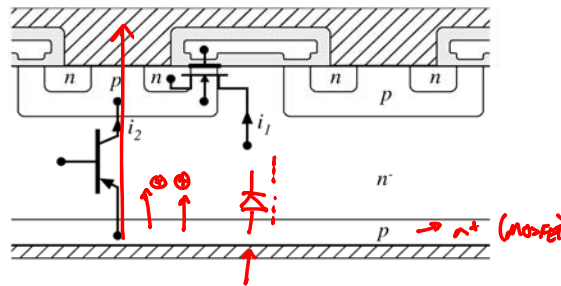


Fundamentals of Power Electronics

65

Chapter 4: Switch realization

## IGBT: Current Tailing

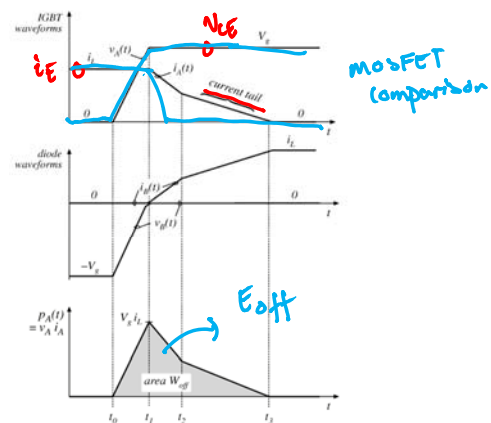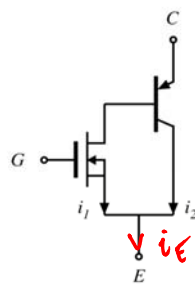

Fundamentals of Power Electronics

66

Chapter 4: Switch realization

## Conclusions: IGBT

- Becoming the device of choice in ~~500~~ <sup>Recent competition from WBG FETs</sup> to 1700V+ applications, at power levels of 1-1000kW
- Positive temperature coefficient at high current —easy to parallel and construct modules
- Forward voltage drop: diode in series with on-resistance. 2-4V typical
- • Easy to drive —similar to MOSFET
- Slower than MOSFET, but faster than Darlington, GTO, SCR
- Typical switching frequencies: 3-30kHz
- IGBT technology is rapidly advancing:
  - ~~3300~~ <sup>6500V</sup> V devices: HVIGBTs
  - 150 kHz switching frequencies in 600 V devices



## Chapter 5: Discontinuous Conduction Mode

- 5.1. Origin of the discontinuous conduction mode, and mode boundary
- 5.2. Analysis of the conversion ratio  $M(D, K)$
- 5.3. Boost converter example
- 5.4. Summary of results and key points

## DCM Introduction

- Occurs because switching ripple in inductor current or capacitor voltage causes polarity of applied switch current or voltage to reverse, such that the current- or voltage-unidirectional assumptions made in realizing the switch are violated.
- Commonly occurs in dc-dc converters and rectifiers, having single-quadrant switches. May also occur in converters having two-quadrant switches.
- Typical example: dc-dc converter operating at light load (small load current). Sometimes, dc-dc converters and rectifiers are purposely designed to operate in DCM at all loads.
- Properties of converters change radically when DCM is entered:
  - $M$  becomes load-dependent
  - Output impedance is increased
  - Dynamics are altered
  - Control of output voltage may be lost when load is removed


Fundamentals of Power Electronics

2

Chapter 5: Discontinuous conduction mode



## Buck Converter Example

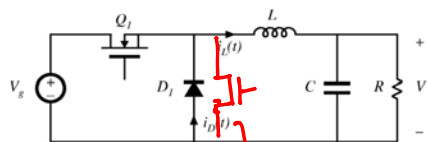



$V = \Delta V_g$   
 $I_L = \frac{V}{R}$   
 $2 \Delta i_L = \frac{V_g - V}{L} DT_s$

ex  
 $V_g = 12$     $V = 3$     $L = 100 \mu\text{H}$   
 $T_s = 50 \mu\text{s}$

first,  $R = 1 \Omega$

Now  $R \rightarrow 10 \Omega$


synchronous implementation (No DCM)

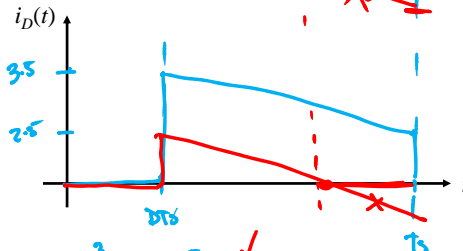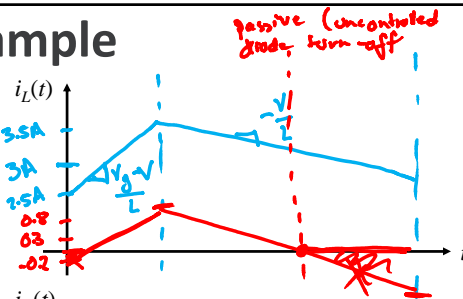

$D = \frac{3}{12} = 0.25$  ✓  
 $I_L = \frac{3V}{10\Omega} = 0.3A$  →  $0.3A \neq 3A$  (DCM)  
 $\Delta i_L = 0.56A$  ✓



## Buck Converter: Low Load

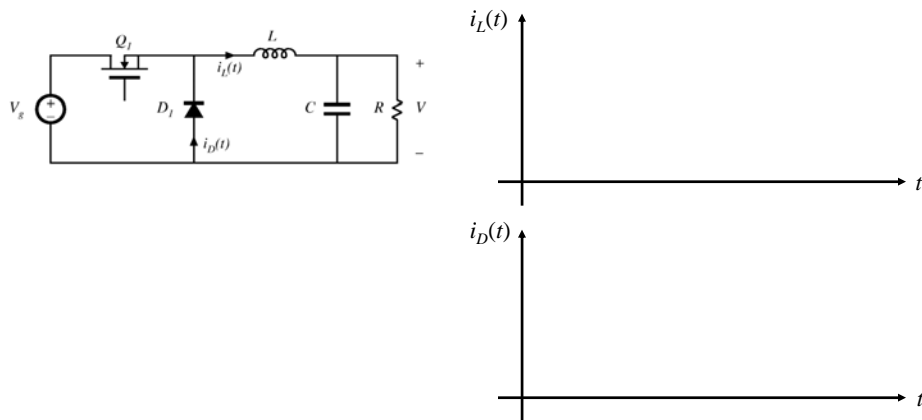

## DCM/CCM Modes of Operation

Continuous Conduction Mode: (CCM)

- what we've seen so far
- one switch is always on in each 'pair' that implements an SPDT switch

Discontinuous Conduction Mode (DCM):

- some element's ripple causes passive turn off of a switch

- e.g.  $\Delta i_L > I_L$   
calculated for CCM

Critical Conduction Mode (CRM) or Boundary Cond. Mode (BCM)

- e.g.  $\Delta i_L = I_L$

**$K_{crit}$  and  $R_{crit}$**  ( $v=Vg$ )

Buck converter:

$$I_L = \frac{V}{R} > \frac{Vg}{R}$$

$$\Delta i_L = \frac{Vg - V}{2L} DT_s \approx \frac{Vg}{2L} DT_s$$

is in CCM when  $I_L > \Delta i_L$   
go into DCM when  $I_L < \Delta i_L$

for CCM:

$$\frac{Vg}{R} > \frac{Vg}{2L} DT_s$$

$$K = \left\lfloor \frac{2L}{RT_s} > D' \right\rfloor = K_{crit}(D)$$

$$K > K_{crit}(D) \quad \text{for CCM}$$

## DCM Mode Boundary: Summary

$$\begin{array}{ll} K > K_{crit}(D) & \text{or} \quad R < R_{crit}(D) \quad \text{for CCM} \\ K < K_{crit}(D) & \text{or} \quad R > R_{crit}(D) \quad \text{for DCM} \end{array}$$

Table 5.1. CCM-DCM mode boundaries for the buck, boost, and buck-boost converters

Converter	$K_{crit}(D)$	$\max_{0 \leq D \leq 1} (K_{crit})$	$R_{crit}(D)$	$\min_{0 \leq D \leq 1} (R_{crit})$
Buck	$(1-D)$	1	$\frac{2L}{(1-D)T_s}$	$2 \frac{L}{T_s}$
Boost	$D(1-D)^2$	$\frac{4}{27}$	$\frac{2L}{D(1-D)^2 T_s}$	$\frac{27}{2} \frac{L}{T_s}$
Buck-boost	$(1-D)^2$	1	$\frac{2L}{(1-D)^2 T_s}$	$2 \frac{L}{T_s}$