

## Lecture 14: Discontinuous Conduction Mode Examples

ECE 481: Power Electronics

Prof. Daniel Costinett


Department of Electrical Engineering and Computer Science

University of Tennessee Knoxville



THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE

### Buck Converter Example

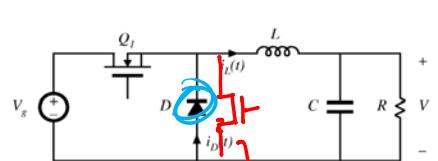


$$\begin{aligned} V_o &= D V_s \\ \rightarrow I_L &= \frac{V_o}{R} \\ \rightarrow 2 \Delta i_L &= \frac{V_s - V_o}{L} D T_s \end{aligned}$$

$$\begin{aligned} \cancel{C/T} \quad V_s &= 12 \quad V_o = 3 \quad L = 100 \mu H \\ T_s &> 50 \mu s \end{aligned}$$

first,  $R = 1 \Omega$

Now  $R \rightarrow 10 \Omega$

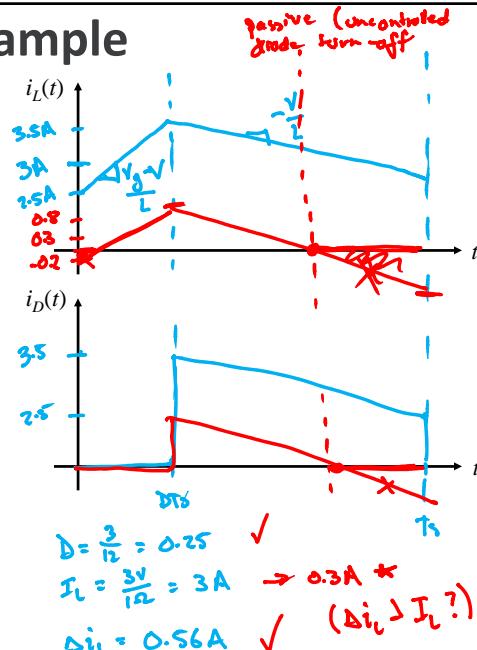

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE

$K_{crit}$  and  $R_{crit}$  ( $V=0Vg$ )

$$I_L = \frac{V}{R} > \frac{DV}{R} \quad D_iL = \frac{V_0 - V}{2L} D T_s = \frac{D'}{2L} D T_s$$

Buck converter:

In CCM when  $I_L > D_iL \leftarrow$  converter parameters  
 Go into DCM when  $I_L < D_iL$        $\cdot L \}$   $D_iL$   
 $\cdot T_s \}$   
 $\cdot R \rightarrow I_L$

for CCM:

$$\frac{\Delta K}{R} > \frac{V(D)}{2L} D T_s \quad \frac{2L}{D T_s} > R$$

$$K = \left| \frac{2L}{R T_s} > D' \right| = k_{crit}(D)$$

$n > k_{crit}(D)$  for CCM


THE UNIVERSITY OF TENNESSEE KNOXVILLE 

## DCM Mode Boundary: Summary

$$\begin{array}{ll} \text{fixed} & \text{fixed} \\ \downarrow & \downarrow \\ K > K_{crit}(D) & \text{or} \quad R < R_{crit}(D) \quad \text{for CCM} \\ K < K_{crit}(D) & \text{or} \quad R > R_{crit}(D) \quad \text{for DCM} \\ \text{when as a function of } D, \text{ does } \text{year occur?} \end{array}$$

Table 5.1 CCM-DCM mode boundaries for the buck, boost, and buck-boost converters

Converter	$K_{crit}(D)$	$\max_{0 \leq D \leq 1} (K_{crit})$	$R_{crit}(D)$	$\min_{0 \leq D \leq 1} (R_{crit})$
Buck	$\rightarrow (1-D)$	1	$\frac{2L}{(1-D)T_s}$	$2 \frac{L}{T_s}$
Boost	$D(1-D)^2$	$\frac{4}{27}$	$\frac{2L}{D(1-D)^2 T_s}$	$\frac{27}{2} \frac{L}{T_s}$
Buck-boost	$(1-D)^2$	1	$\frac{2L}{(1-D)^2 T_s}$	$2 \frac{L}{T_s}$

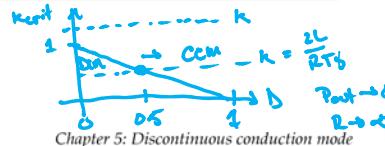

## Finding the Conversion Ratio M(D,K)

$$\frac{v}{v_g} = M$$

Analysis techniques for the discontinuous conduction mode:

Inductor volt-second balance ✓

$$\langle v_L \rangle = \frac{1}{T_s} \int_0^{T_s} v_L(t) dt = 0$$

Capacitor charge balance ✓

$$\rightarrow \langle i_C \rangle = \frac{1}{T_s} \int_0^{T_s} i_C(t) dt = 0$$

Only assumption was steady-state operation

$$i_L(T_s) = i_L(0)$$

$$v_L(T_s) = v_L(0)$$


Small ripple approximation sometimes applies:

$$\rightarrow v(t) \approx V \text{ because } \Delta v \ll V$$

$$\rightarrow i(t) \approx I \text{ is a poor approximation when } \Delta i > I$$

Converter steady-state equations obtained via charge balance on each capacitor and volt-second balance on each inductor. Use care in applying small ripple approximation.

## Buck Converter in DCM

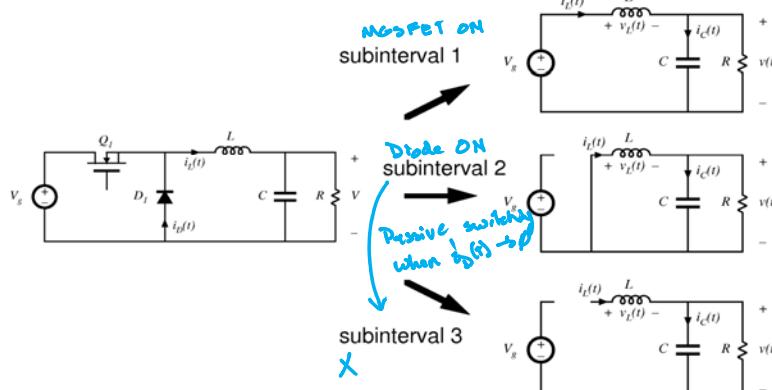

## Subinterval Analysis

$$v_L = v_g - v(t) \approx v_g - V \quad \text{SRA still applies}$$

$$\textcircled{1} \quad i_C = i_L(t) - \frac{v(t)}{R} \approx i_L(t) - \frac{V}{R}$$

↑ SRA no longer applies




$$v_L = 0 - v(t) \approx -V$$

$$\textcircled{2} \quad i_C = i_L(t) - \frac{v(t)}{R} \approx i_L(t) - \frac{V}{R}$$

$$v_L = \phi$$

$$\textcircled{3} \quad i_C = i_L(t) - \frac{v(t)}{R} = i_L(t) - \frac{V}{R}$$

↓ has gone to zero

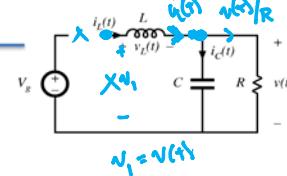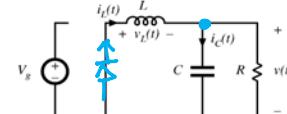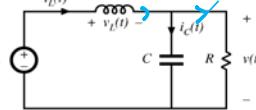

THE UNIVERSITY OF  
TENNESSEE KNOXVILLE

## Waveforms in DCM

$$\langle v_L \rangle = \phi = D_1(v_g - V) + D_2(-V) + D_3(\phi)$$

$$\phi = D_1 v_g - V(D_1 + D_2)$$


$$\boxed{\frac{V}{v_g} = \frac{D_1}{D_1 + D_2}}$$

$$\langle i_C \rangle = \phi = \frac{1}{T_S} \int_0^{T_S} i_L(t) - \frac{V}{R} dt$$

$$\langle i_C \rangle = \phi = \frac{1}{T_S} \int_0^{T_S} i_L(t) dt \quad \text{constant } -\frac{V}{R}$$

$$\frac{V}{R} = \langle i_L \rangle$$
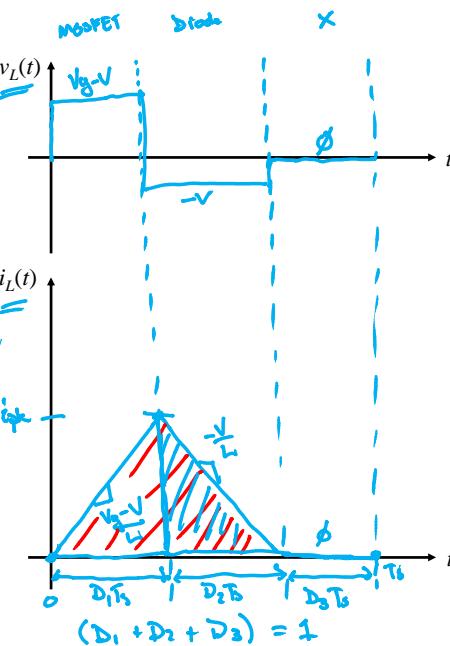
$$\frac{V}{R} = \frac{1}{T_S} \left[ \frac{1}{2} D_1 T_S i_{ph} + \frac{1}{2} D_2 T_S i_{pk} \right]$$



THE UNIVERSITY OF  
TENNESSEE KNOXVILLE

$$i_{pl} = \frac{V_g - V}{L} D_1 T_s$$

$$\frac{V}{R} = \frac{1}{2} [ \frac{1}{2} D_1 T_s i_{pl} + \frac{1}{2} D_2 T_s / i_{pl} ]$$

$$\boxed{\frac{V}{R} = \frac{1}{2} (D_1 + D_2) \frac{(V_g - V)}{L} D_1 T_s}$$



## Solving $M(D, K)$

Two equations and two unknowns ( $V$  and  $D_2$ ):

$$\left\{ \begin{array}{l} V = V_g \frac{D_1}{D_1 + D_2} \\ \text{(from inductor volt-second balance)} \end{array} \right.$$

$$\frac{V}{R} = \frac{D_1 T_s}{2L} (D_1 + D_2) (V_g - V) \quad \text{(from capacitor charge balance)}$$

Eliminate  $D_1$ , solve for  $V$ :

$$M(D_1, K) \quad \frac{V}{V_g} = \frac{2}{1 + \sqrt{1 + 4K^2}}$$


$$\text{where } K = 2L / R T_s$$

$$\text{valid for } K < K_{crit}$$

*Controlled duty cycle*



## Buck Converter $M(D, K)$

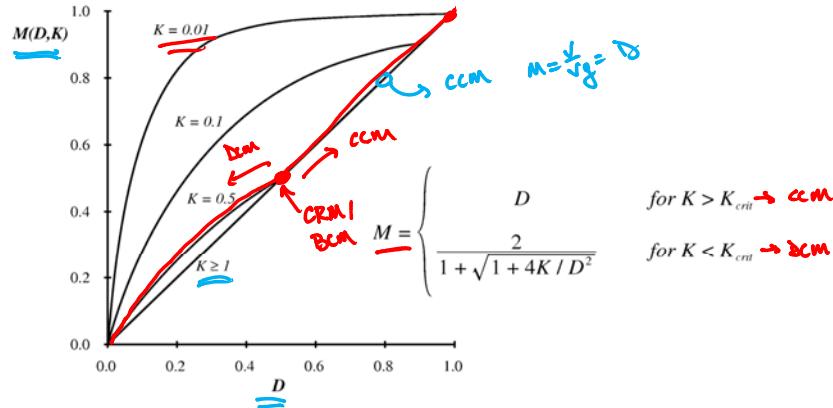


Fundamentals of Power Electronics

19

Chapter 5: Discontinuous conduction mode

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE 

## Boost Converter in DCM

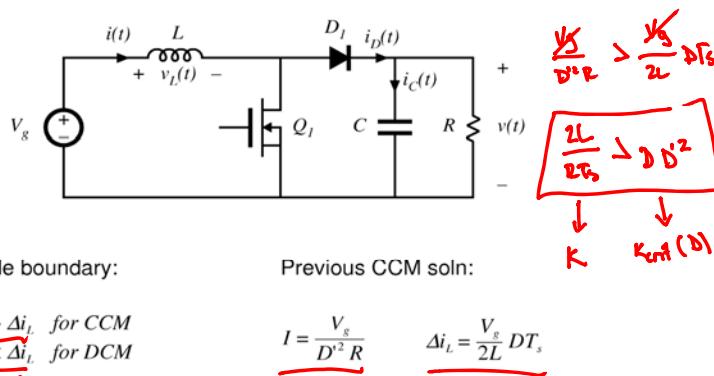

Mode boundary:

$$\begin{array}{ll} I > \Delta i_L & \text{for CCM} \\ I < \Delta i_L & \text{for DCM} \end{array}$$

Previous CCM soln:

$$I = \frac{V_g}{D^2 R} \quad \Delta i_L = \frac{V_g}{2L} D T_s$$

Fundamentals of Power Electronics

20

Chapter 5: Discontinuous conduction mode


THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE

## Boost DCM Boundary


$$\frac{V_g}{D^2 R} > \frac{DT_s V_g}{2L} \quad \text{for CCM}$$

$$\frac{2L}{RT_s} > DD'^2 \quad \text{for CCM}$$

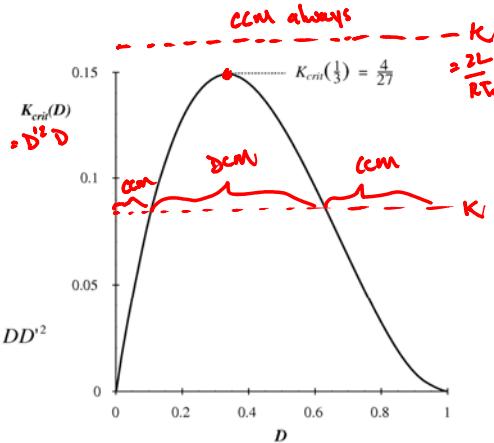where  $K = \frac{2L}{RT_s}$  and  $K_{crit}(D) = DD'^2$




## Boost Converter Subintervals

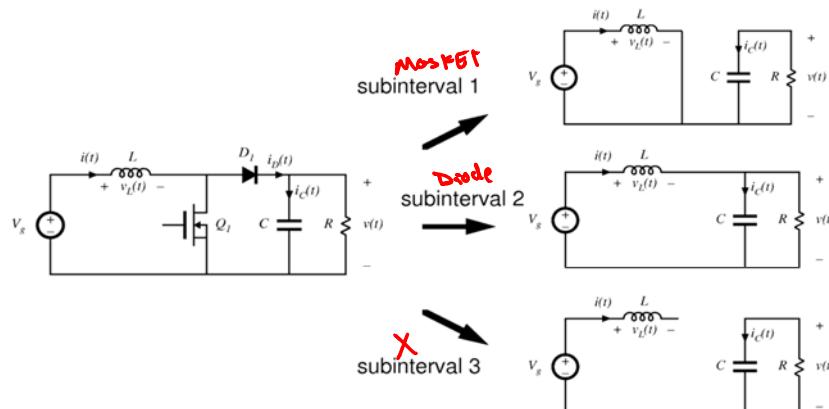
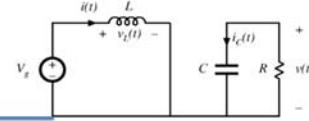
## Boost Conversion Ratio


$$v_L = V_g$$

$$\textcircled{1} \quad i_c = -\frac{v(t)}{R} \approx -\frac{V}{R}$$




$$v_L = V_g - v(t) \approx V_g - V$$
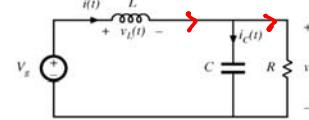
$$\textcircled{2} \quad i_c = i_L(t) - \frac{v(t)}{R} \approx i_L(t) - \frac{V}{R}$$



$$v_L = \phi$$
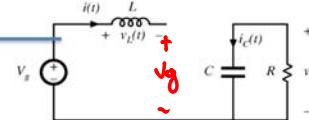
$$\textcircled{3} \quad i_c = -\frac{v(t)}{R} \approx -\frac{V}{R}$$



THE UNIVERSITY OF  
TENNESSEE   
KNOXVILLE


## Boost Waveforms in DCM

$$\langle v_c \rangle = \phi = D_1 V_g + D_2 (V_g - V) + D_3 \phi$$

$$\phi = V_g(D_1 + D_2) + D_2(-V)$$

$$\boxed{\frac{V}{V_g} = \frac{D_1 + D_2}{D_2}}$$
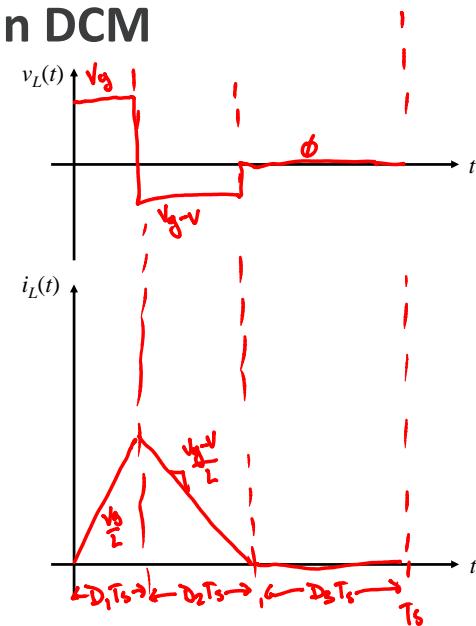
$$\begin{aligned} \langle i_c \rangle &= -\frac{V}{R} + \frac{1}{T_s} \int_{D_1 T_s}^{(D_1+D_2) T_s} i_c(t) dt \\ &= -\frac{V}{R} + \langle i_D(t) \rangle \end{aligned}$$



THE UNIVERSITY OF  
TENNESSEE   
KNOXVILLE

## Boost Cap-Charge Balance


$$\phi = \langle i_c \rangle = \langle i_d \rangle - \left\langle \frac{v(t)}{R} \right\rangle$$

$$\langle i_c \rangle = \phi = \frac{V}{R} + \left[ \frac{1}{2} D_2 T_s i_{pk} \right] \frac{1}{T_s}$$

$$i_{pk} = \frac{V_g}{L} D_1 T_s$$

$$\langle i_c \rangle = \phi = \frac{V}{R} + \frac{1}{T_s} \left[ \frac{1}{2} D_2 T_s \frac{V_g}{L} D_1 T_s \right]$$

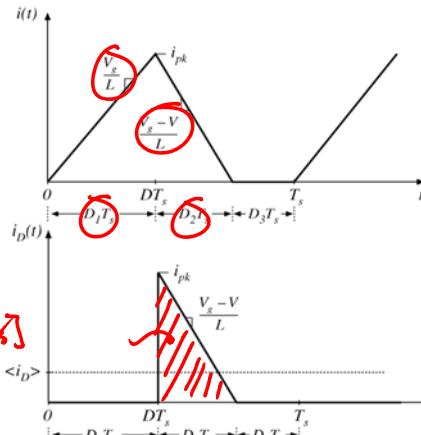$\frac{V}{R} = \frac{D_1 D_2 V_g T_s}{2L}$



THE UNIVERSITY OF  
TENNESSEE

## Boost DCM Conversion Ratio

$$\rightarrow V^2 - VV_g - \frac{V_g^2 D_1^2}{K} = 0$$

Use quadratic formula:

$$\rightarrow \frac{V}{V_g} = \frac{1 + \sqrt{1 + 4D_1^2 / K}}{2}$$

Note that one root leads to positive  $V$ , while other leads to negative  $V$ . Select positive root:


$$\frac{V}{V_g} = M(D_1, K) = \frac{1 + \sqrt{1 + 4D_1^2 / K}}{2}$$

where  $K = 2L / RT_s$   
 valid for  $K < K_{crit}(D)$

Transistor duty cycle  $D$  = interval 1 duty cycle  $D_1$

THE UNIVERSITY OF  
TENNESSEE

## Boost Conversation Ratio

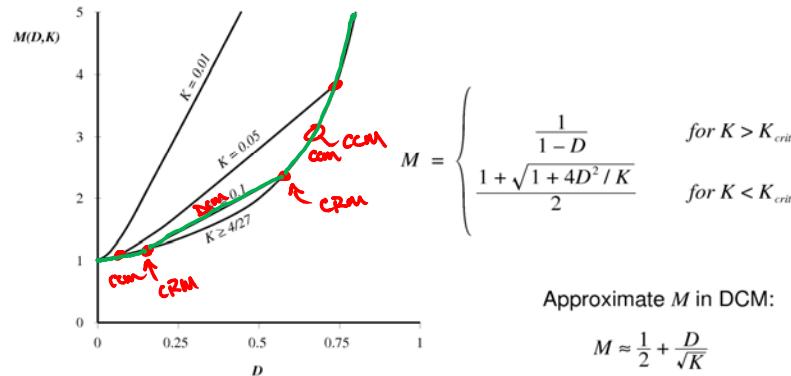

Fundamentals of Power Electronics

33

Chapter 5: Discontinuous conduction mode



## Summary of DCM Characteristics

Table 5.2 Summary of CCM-DCM characteristics for the buck, boost, and buck-boost converters

Converter	$K_{crit}(D)$	$DCM\ M(D, K)$	$DCM\ D_2(D, K)$	$CCM\ M(D)$
Buck	$(1 - D)$	$\frac{2}{1 + \sqrt{1 + 4K/D^2}}$	$\frac{K}{D} M(D, K)$	$D$
Boost	$D(1 - D)^2$	$\frac{1 + \sqrt{1 + 4D^2/K}}{2}$	$\frac{K}{D} M(D, K)$	$\frac{1}{1 - D}$
Buck-boost	$(1 - D)^2$	$-\frac{D}{\sqrt{K}}$	$\sqrt{K}$	$-\frac{D}{1 - D}$

with  $K = 2L / RT_{v_s}$ ,  $DCM$  occurs for  $K < K_{crit}$ .

$D_1 \rightarrow$  control

$D_2 \rightarrow$  from table

$$D_3 = 1 - D_1 - D_2$$


Fundamentals of Power Electronics

34

Chapter 5: Discontinuous conduction mode



## Summary of DCM Characteristics

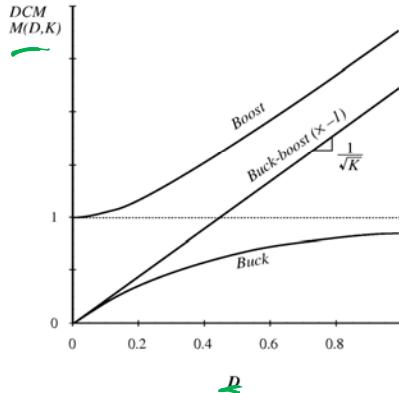

- DCM buck and boost characteristics are asymptotic to  $M = 1$  and to the DCM buck-boost characteristic
- DCM buck-boost characteristic is linear
- CCM and DCM characteristics intersect at mode boundary. Actual  $M$  follows characteristic having larger magnitude
- DCM boost characteristic is nearly linear

Fundamentals of Power Electronics

35

Chapter 5: Discontinuous conduction mode



## Chapter 5 Summary

1. The discontinuous conduction mode occurs in converters containing current- or voltage-unidirectional switches, when the inductor current or capacitor voltage ripple is large enough to cause the switch current or voltage to reverse polarity.
2. Conditions for operation in the discontinuous conduction mode can be found by determining when the inductor current or capacitor voltage ripples and dc components cause the switch on-state current or off-state voltage to reverse polarity.
3. The dc conversion ratio  $M$  of converters operating in the discontinuous conduction mode can be found by application of the principles of inductor volt-second and capacitor charge balance.
4. Extra care is required when applying the small-ripple approximation. Some waveforms, such as the output voltage, should have small ripple which can be neglected. Other waveforms, such as one or more inductor currents, may have large ripple that cannot be ignored.
5. The characteristics of a converter changes significantly when the converter enters DCM. The output voltage becomes load-dependent, resulting in an increase in the converter output impedance.

