
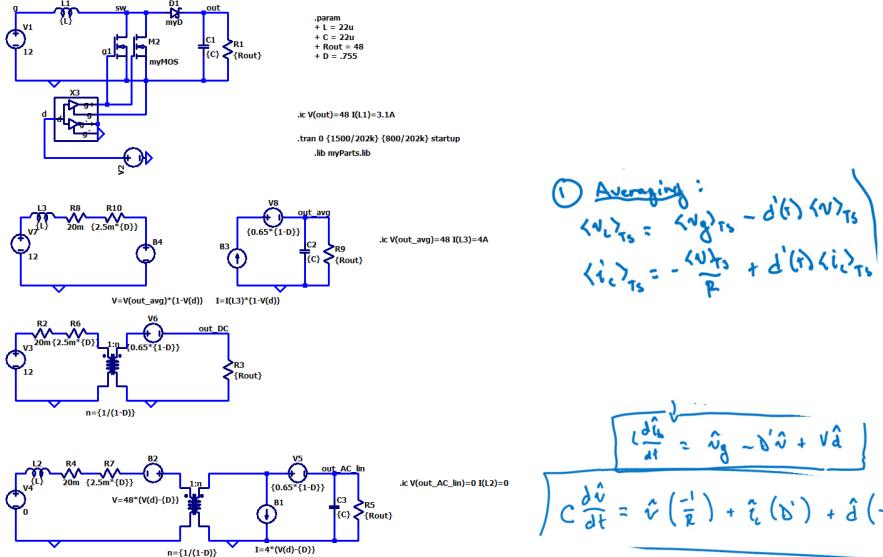


Model Simulation

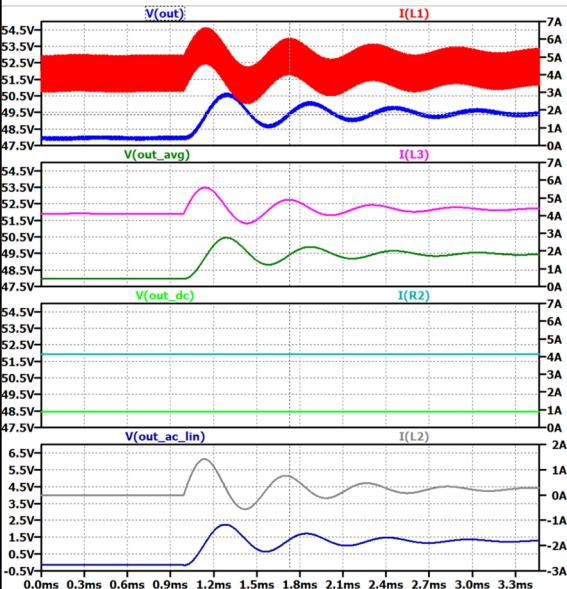


THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Model Comparison



THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

7.2.9: Nonideal Flyback Modeling

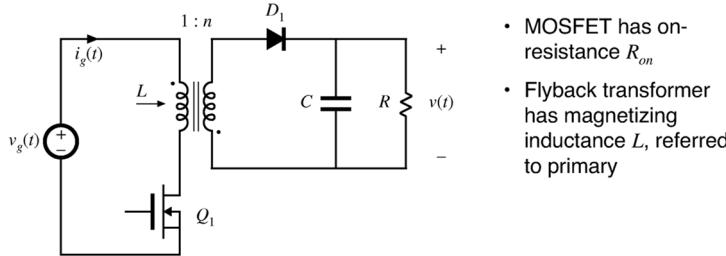

- MOSFET has on-resistance R_{on}
- Flyback transformer has magnetizing inductance L , referred to primary


Fundamentals of Power Electronics

47

Chapter 7: AC equivalent circuit modeling



Inductor Waveforms

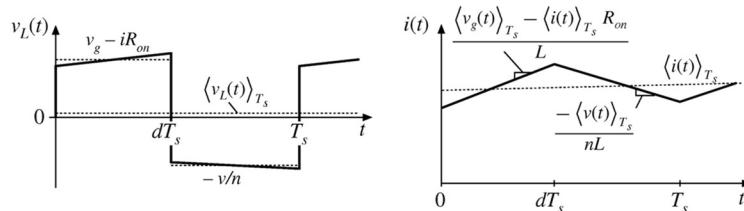

Average inductor voltage:

$$\langle v_L(t) \rangle_{T_s} = d(t) \left(\langle v_g(t) \rangle_{T_s} - \langle i(t) \rangle_{T_s} R_{on} \right) + d'(t) \left(\frac{-\langle v(t) \rangle_{T_s}}{n} \right)$$

Hence, we can write:

$$L \frac{d \langle i(t) \rangle_{T_s}}{dt} = d(t) \langle v_g(t) \rangle_{T_s} - d(t) \langle i(t) \rangle_{T_s} R_{on} - d'(t) \frac{\langle v(t) \rangle_{T_s}}{n}$$


Fundamentals of Power Electronics

51

Chapter 7: AC equivalent circuit modeling



Capacitor Waveforms

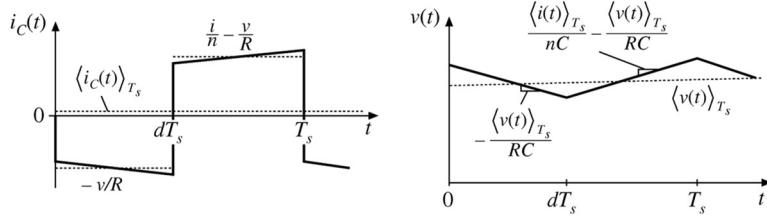


Average capacitor current:

$$\langle i_C(t) \rangle_{T_s} = d(t) \left(\frac{-\langle v(t) \rangle_{T_s}}{R} \right) + d'(t) \left(\frac{\langle i(t) \rangle_{T_s} - \langle v(t) \rangle_{T_s}}{n} \right)$$

Hence, we can write:

$$C \frac{d\langle v(t) \rangle_{T_s}}{dt} = d'(t) \frac{\langle i(t) \rangle_{T_s} - \langle v(t) \rangle_{T_s}}{n}$$

Input Current Waveform

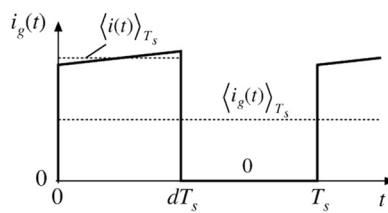

Average input current:

$$\langle i_g(t) \rangle_{T_s} = d(t) \langle i(t) \rangle_{T_s}$$

Flyback Linearization




Flyback Equivalent Circuit Model




Flyback AC Model

Combine circuits:

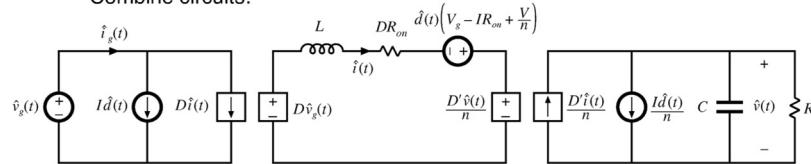

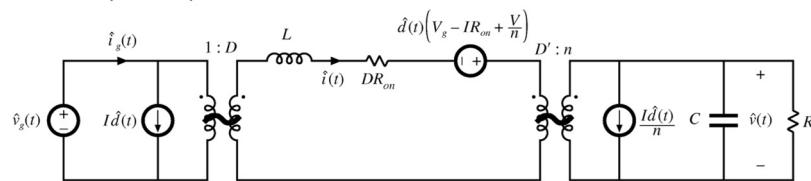Replace dependent sources with ideal transformers:





Remainder of Chapter 7

- 7.1 Introduction
- 7.2 The basic AC modeling approach
- 7.3 State-space averaging
- 7.4 Circuit averaging and averaged switch modeling
- 7.5 The canonical circuit model
- 7.6 Modeling the pulse-width modulator
- 7.7 Summary of key points

