

Lecture 2: Volt-Second and Capacitor Charge Balance

ECE 481: Power Electronics

Prof. Daniel Costinett

Department of Electrical Engineering and Computer Science

University of Tennessee Knoxville

Fall 2015



THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Announcements


- HW #1 due Friday (8/29)

Part I: Converters in Equilibrium


2. Principles of steady state converter analysis
3. Steady-state equivalent circuit modeling, losses, and efficiency
4. Switch realization
5. The discontinuous conduction mode
6. Converter circuits

Part I: Converters in Equilibrium


Inductor waveforms

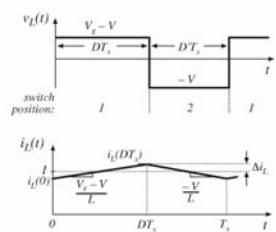

Averaged equivalent circuit

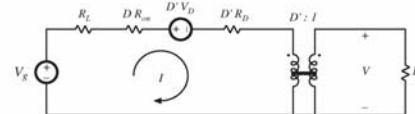



Predicted efficiency

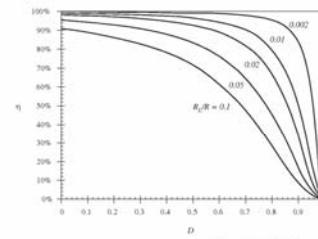

Discontinuous conduction mode

Transformer isolation

Switch Realization: Semiconductor Devices

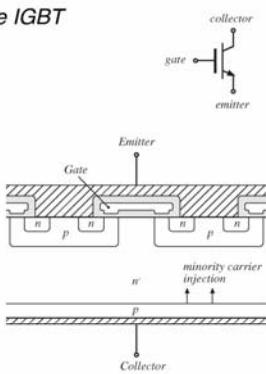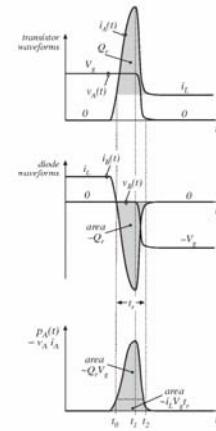The IGBT*Switching loss**Fundamentals of Power Electronics*

26

Chapter 1: Introduction

Part II: Converter Dynamics and Control

7. Ac modeling
8. Converter transfer functions
9. Controller design
10. Input filter design
11. Ac and dc equivalent circuit modeling of the discontinuous conduction mode
12. Current-programmed control


Fundamentals of Power Electronics

29


Chapter 1: Introduction

Part II: Converter Dynamics and Control

Closed-loop converter system

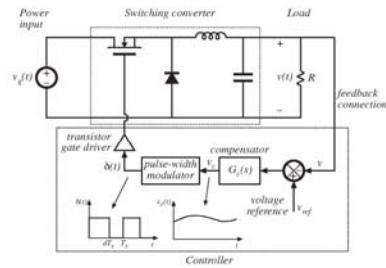

Averaging the waveforms

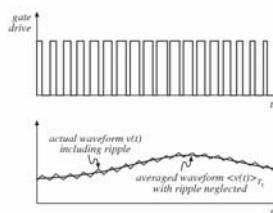

Small-signal averaged equivalent circuit



Fundamentals of Power Electronics

28

Chapter 1: Introduction

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Part III: Magnetics

13. Basic magnetics theory
14. Inductor design
15. Transformer design

Fundamentals of Power Electronics


31

Chapter 1: Introduction


THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Part III: Magnetics


transformer design

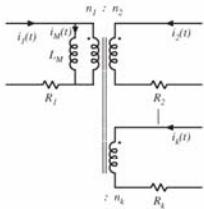

the proximity effect

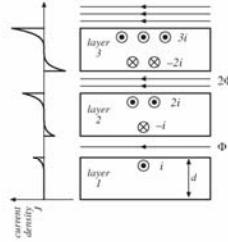

transformer size vs. switching frequency

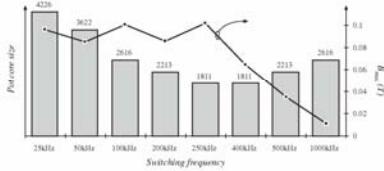

Fundamentals of Power Electronics

30

Chapter 1: Introduction


THE UNIVERSITY OF
TENNESSEE 
KNOXVILLE

Chapter 2: Converters in Equilibrium



THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Buck Converter Review

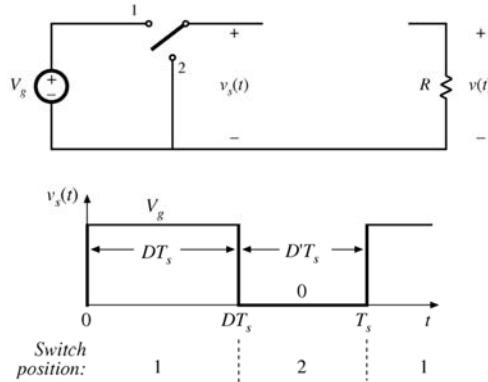







Fundamentals of Power Electronics

2

Chapter 2: Principles of steady-state converter analysis



Three Basic DC-DC PWM Converters

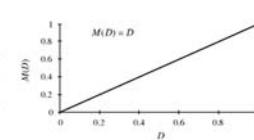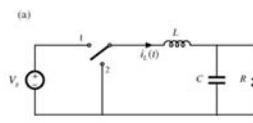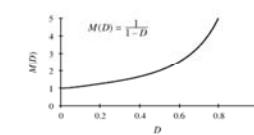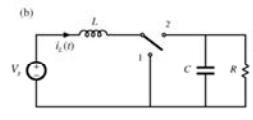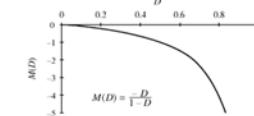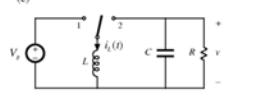Buck*Boost**Buck-boost*

Fundamentals of Power Electronics

Chapter 2: Principles of steady-state converter analysis




Chapter 2: Goals

- Develop techniques for easily determining output voltage of an arbitrary converter circuit
- Derive the principles of *inductor volt-second balance* and *capacitor charge (amp-second) balance*
- Introduce the key *small ripple approximation*
- Develop simple methods for selecting filter element values
- Illustrate via examples


Buck Output Voltage Ripple

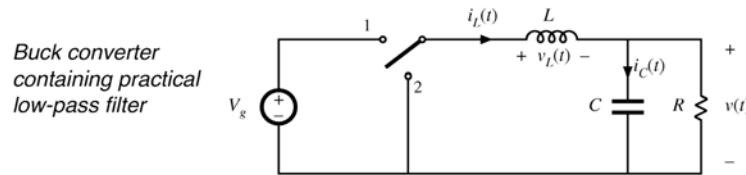Actual output voltage waveform, buck converter




Actual output voltage waveform

$$v(t) = V + v_{\text{ripple}}(t)$$

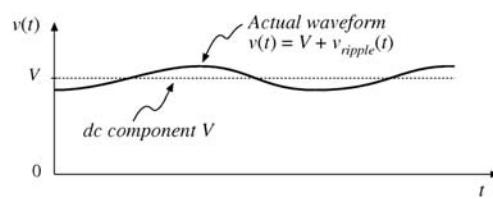

The Small Ripple Approximation

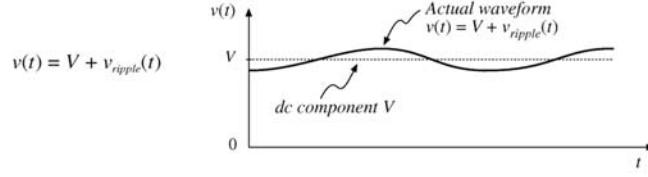

In a well-designed converter, the output voltage ripple is small. Hence, the waveforms can be easily determined by ignoring the ripple:

$$\|v_{\text{ripple}}\| \ll V$$


$$v(t) \approx V$$

Fundamentals of Power Electronics

Chapter 2: Principles of steady-state converter analysis



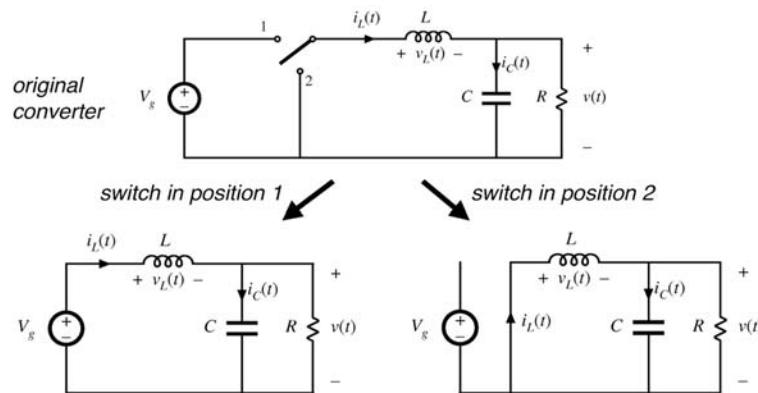Buck Switching Intervals: Inductor Current




Fundamentals of Power Electronics

Chapter 2: Principles of steady-state converter analysis




Subinterval 1

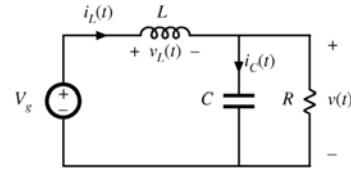


THE UNIVERSITY OF
TENNESSEE 
KNOXVILLE

Subinterval 2

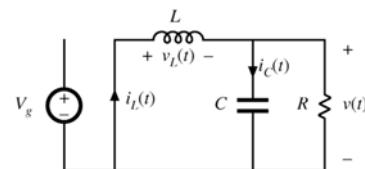


THE UNIVERSITY OF
TENNESSEE 
KNOXVILLE


Current Waveform

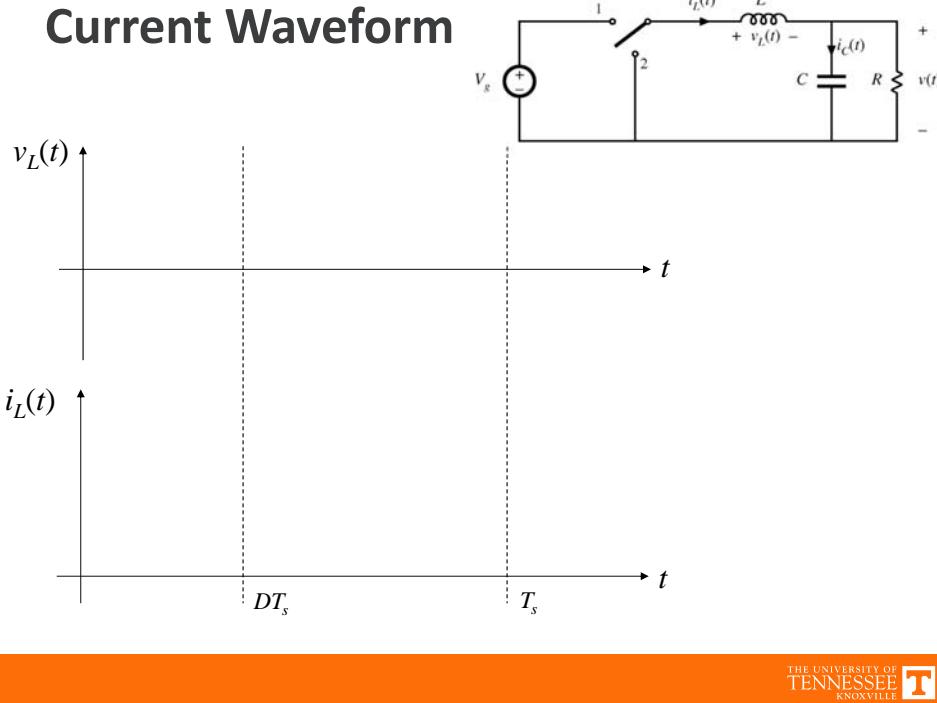

Transient vs. Steady-State Operation

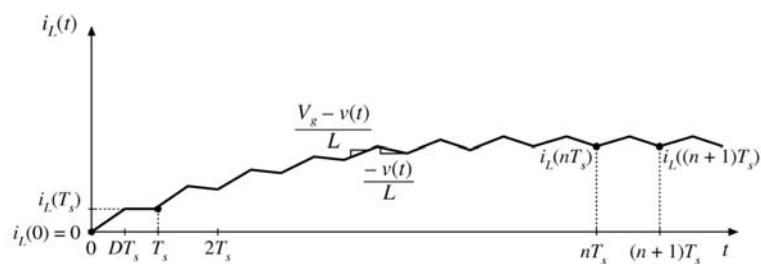

Volt-Second Balance

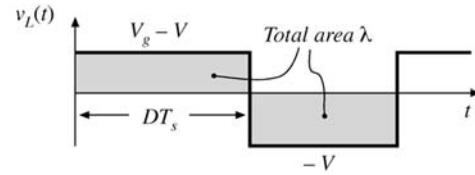


Fundamentals of Power Electronics

Chapter 2: Principles of steady-state converter analysis



Current Ripple Magnitude

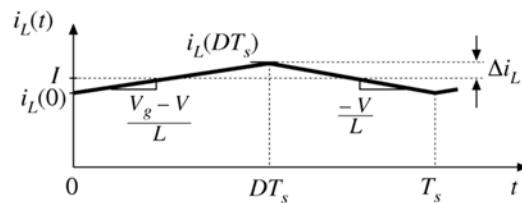


$$(change \text{ in } i_L) = (slope)(length \text{ of } subinterval)$$

Fundamentals of Power Electronics

Chapter 2: Principles of steady-state converter analysis



Capacitor Charge Balance

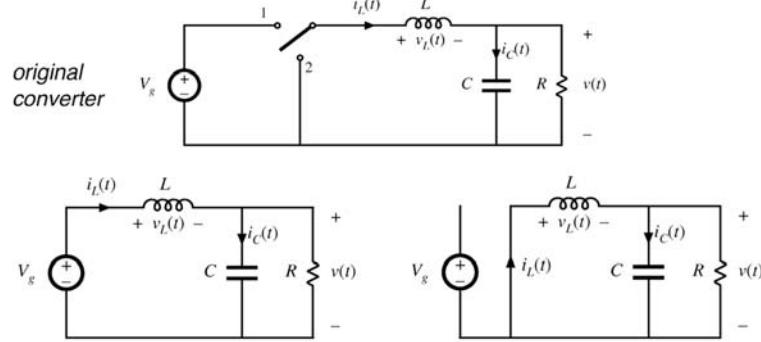

Fundamentals of Power Electronics

Chapter 2: Principles of steady-state converter analysis

