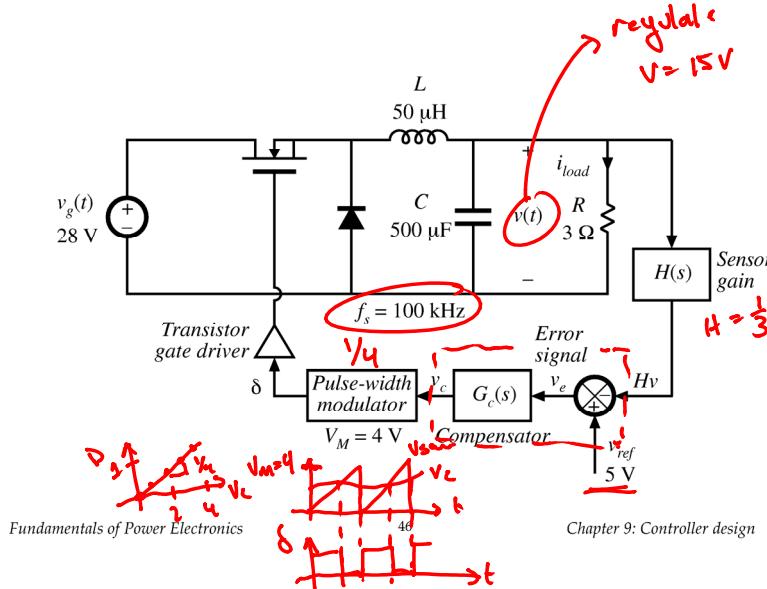


Example Design of Buck Compensator



THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

DC (Quiescent) Operating Point

Input voltage	$V_g = 28 \text{ V}$
Output	$V = 15 \text{ V}, I_{load} = 5 \text{ A}, R = 3 \Omega$
Quiescent duty cycle	$D = 15/28 = 0.536$
Reference voltage	$V_{ref} = 5 \text{ V}$
Quiescent value of control voltage	$V_c = DV_M = 2.14 \text{ V}$
Gain $H(s)$	$H = V_{ref}/V = 5/15 = 1/3$


Fundamentals of Power Electronics

47

Chapter 9: Controller design

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

AC Power Stage Model

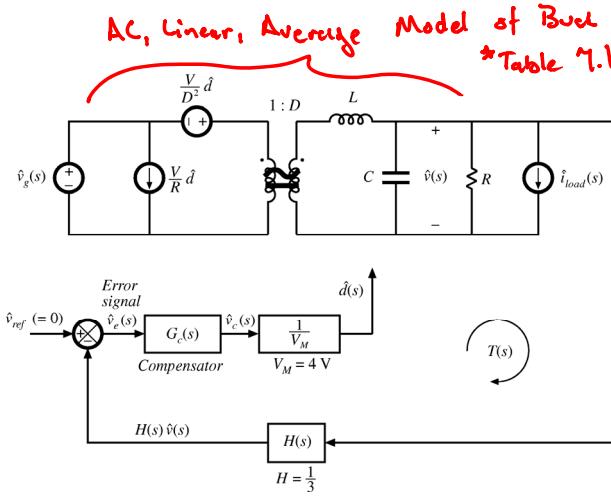


Fundamentals of Power Electronics

48

Chapter 9: Controller design

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

System Block Diagram

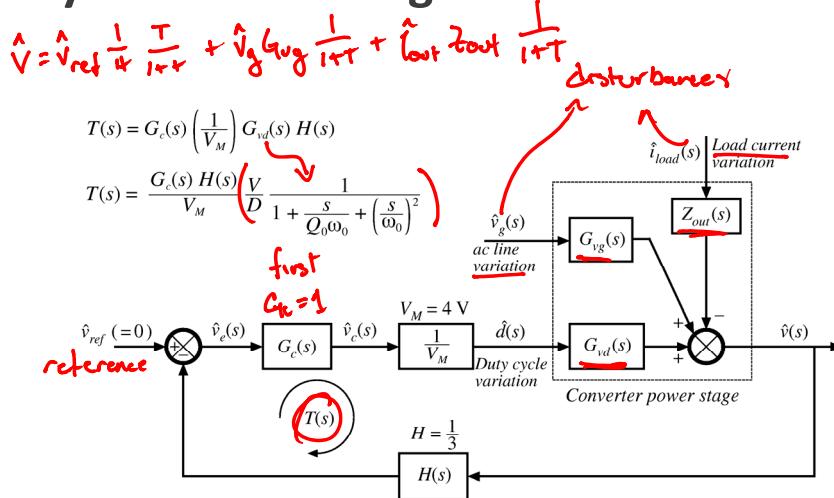

Fundamentals of Power Electronics

51

Chapter 9: Controller design

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE


Plotting Uncompensated Loop Gain (P component)

- (1) φ_m too small \rightarrow Risk instability, Bad transient ringing
- (2) LF gain too low \rightarrow steady-state error (integral component)
- (3) $f_c \approx \omega_0$ \rightarrow higher f_c will speed up transient response

With $G_c = 1$, the (P component) loop gain is

$$T_u(s) = T_{u0} \frac{1}{1 + \frac{s}{Q_0 \omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$
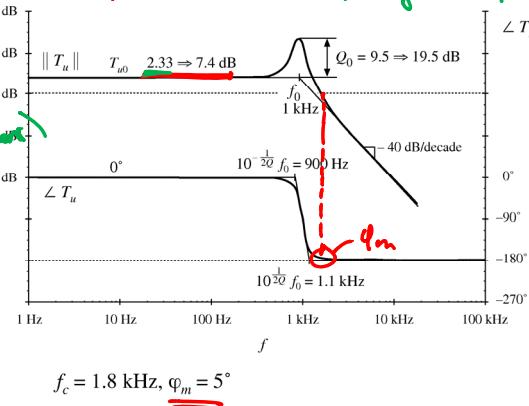
$$T_{u0} = \frac{H V}{D V_M} = 2.33 \Rightarrow 7.4 \text{ dB}$$




Fundamentals of Power Electronics

52

Chapter 9: Controller design


THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

LTSpice Simulation – AC, Uncompensated

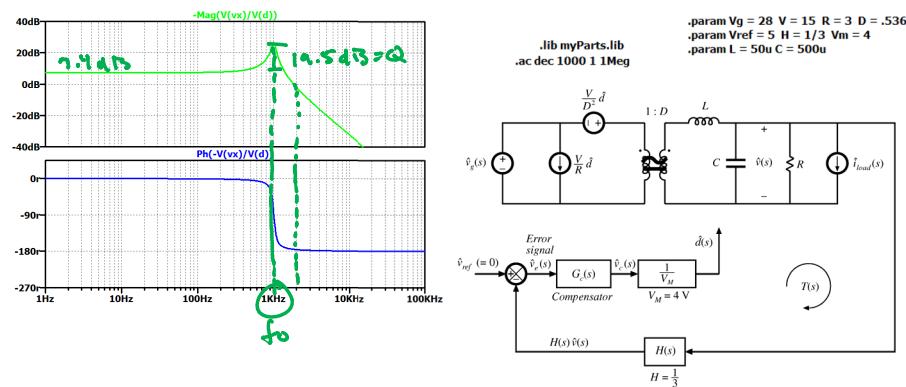


THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Transient Simulation, Uncompensated

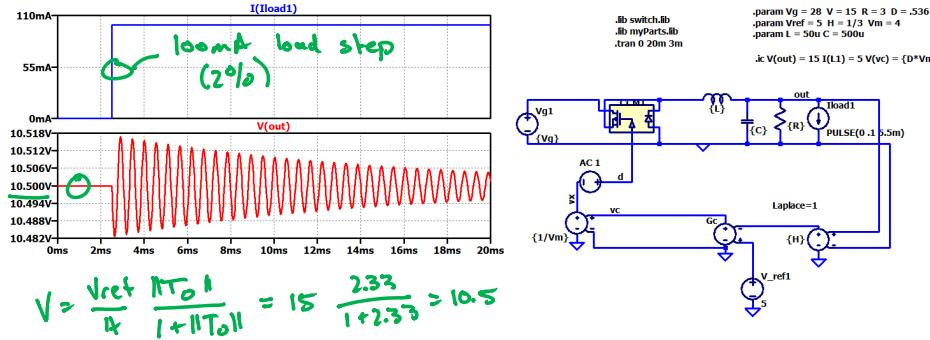


THE UNIVERSITY OF
TENNESSEE KNOXVILLE

Ringing Frequency

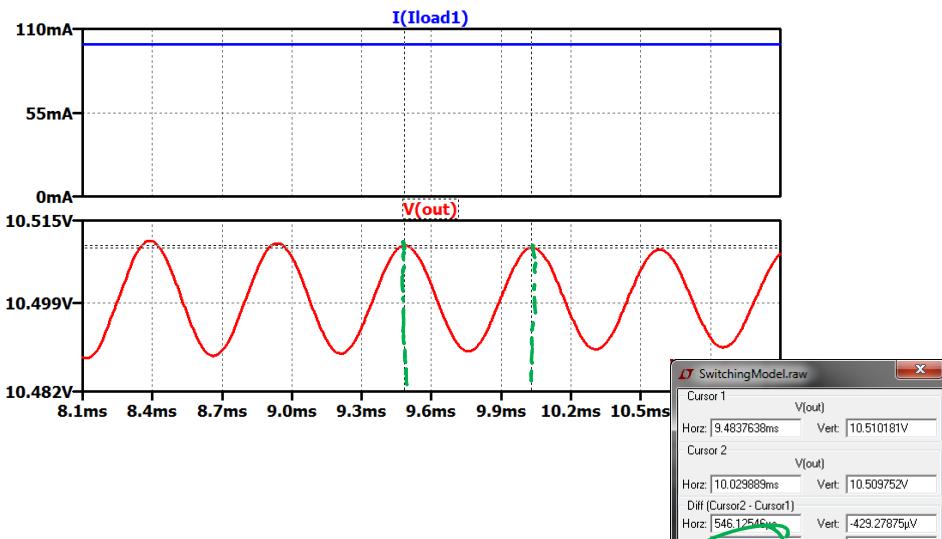

THE UNIVERSITY OF
TENNESSEE KNOXVILLE

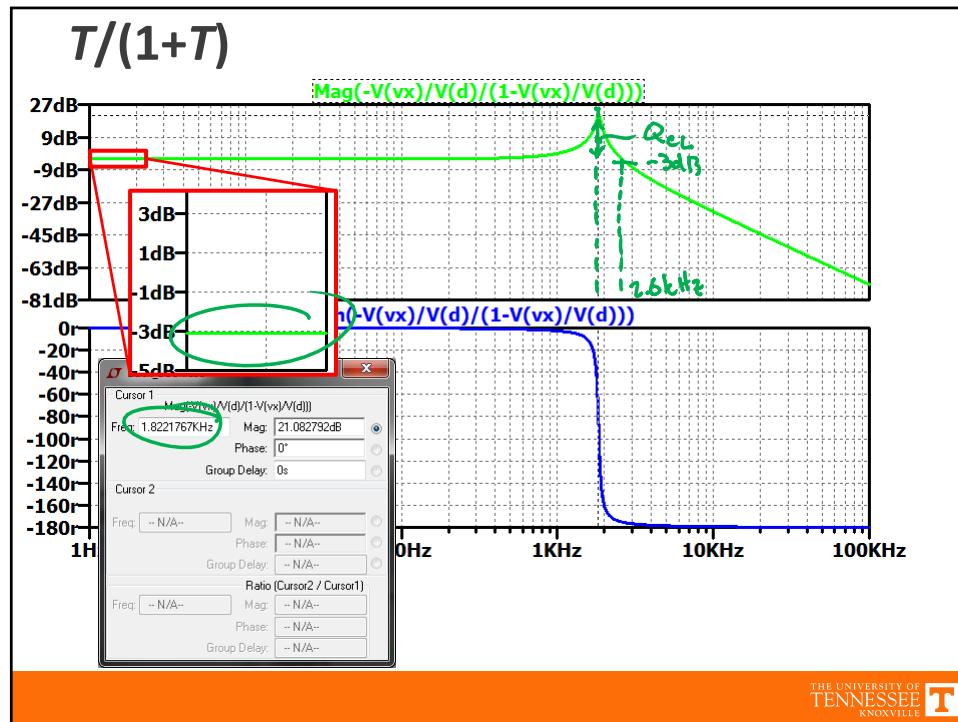


Summary: Uncompensated Behavior

- Significant steady-state error
 - Need to increase low-frequency gain
- Barely stable; significant ringing
 - Need to increase ϕ_m
- Speed: ok
 - $f_c = 1.8 \text{ kHz}$
 - $(BW)_{CL} = 2.6 \text{ kHz}$
 - OK for $f_s \approx 10 \text{ kHz}$ or above

Compensator Design


- As an example, try to
 - ✓ – Increase f_c to 10 kHz = $\frac{f_s}{10}$
 - Increase ϕ_m to 76° ($Q=0.5$)
 - ✓ – Increase $\|T_0\|$ to ∞
- Note: Book Chooses $f_c = 5$ kHz and $\phi_m = 52^\circ$ ($Q=0.5$)

THE UNIVERSITY OF
TENNESSEE 
KNOXVILLE

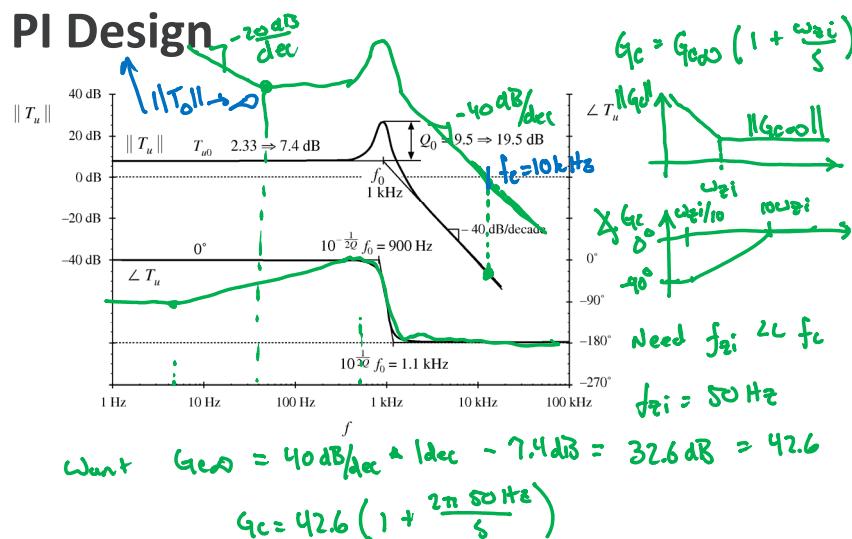

THE UNIVERSITY OF
TENNESSEE 
KNOXVILLE

PI Simulation

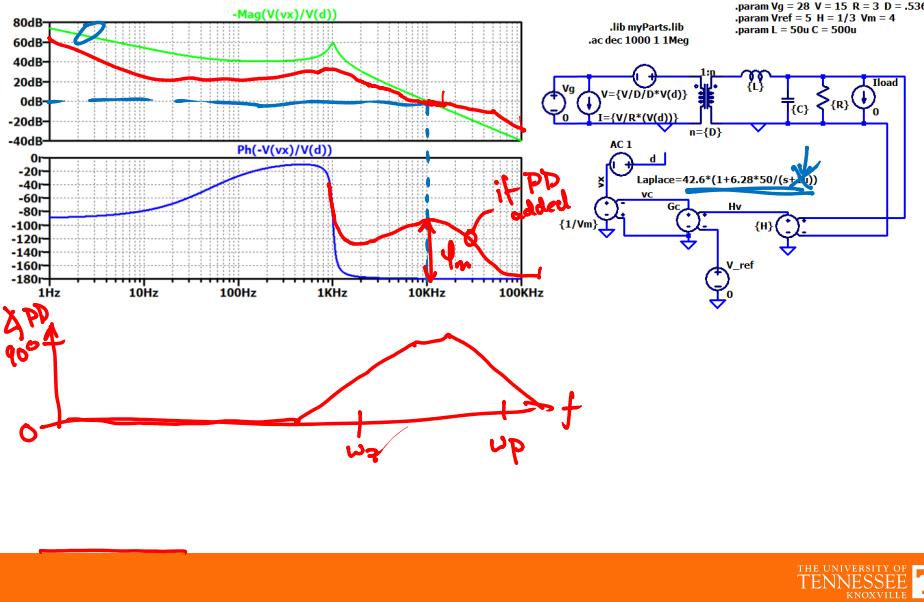

THE UNIVERSITY OF
TENNESSEE KNOXVILLE

PD Design

$$f_z = f_c \sqrt{\frac{1 - \sin(\theta)}{1 + \sin(\theta)}} \quad \begin{cases} \theta = 76^\circ \\ f_c = 10\text{kHz} \end{cases}$$

$$f_p = f_c \sqrt{\frac{1 + \sin(\theta)}{1 - \sin(\theta)}}$$

$$G_{C,PD} = G_{C0} \frac{(1 + \frac{s}{\omega_p})}{(1 + \frac{s}{\omega_z})}$$



$$G_{c0} = \sqrt{\frac{f_z}{f_p}}$$

$$\omega_z = 1.236\text{Hz}$$

$$\omega_p = 81\text{kHz}$$

$$G_{C0} = 0.12$$

THE UNIVERSITY OF
TENNESSEE KNOXVILLE

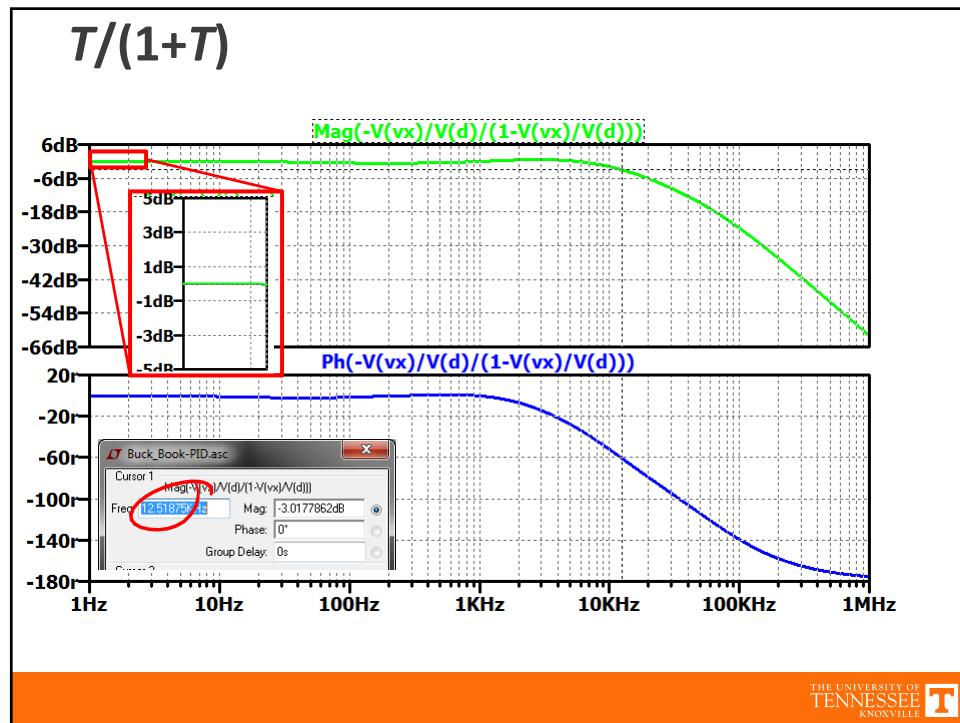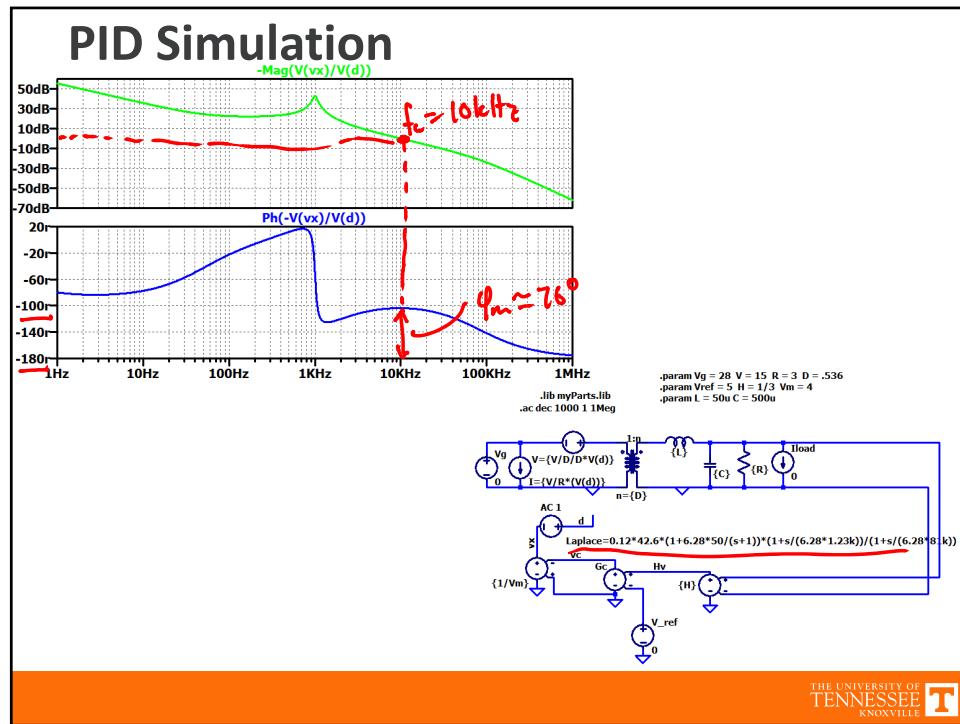

Transient Simulation

