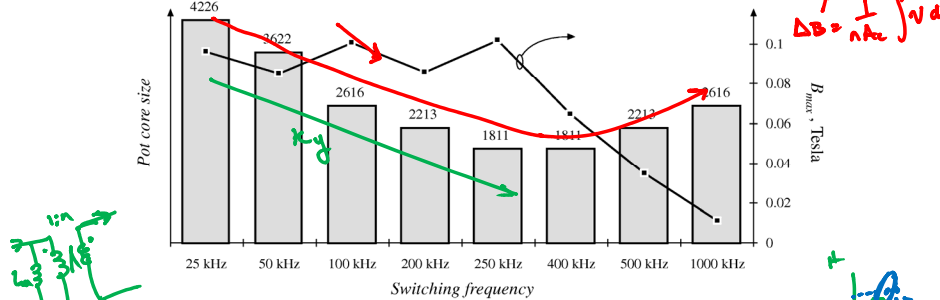


## Switching Frequency Vs. XF Size

kgfc method to design XF w/ constant  $P_{tot}$  ↓  
 $P_{fc} = A_c l_m K_m (AB)^2 f \alpha$   
 $\Delta B = \frac{1}{n A_c} \int v dt$



- As switching frequency is increased from 25 kHz to 250 kHz, core size is dramatically reduced

- As switching frequency is increased from 400 kHz to 1 MHz, core size increases

Fundamentals of Power Electronics

24

Chapter 15: Transformer design

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE




## FURTHER TOPICS IN POWER ELECTRONICS

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE




## Practical Issues in PE: Parasitics

Use loop analysis

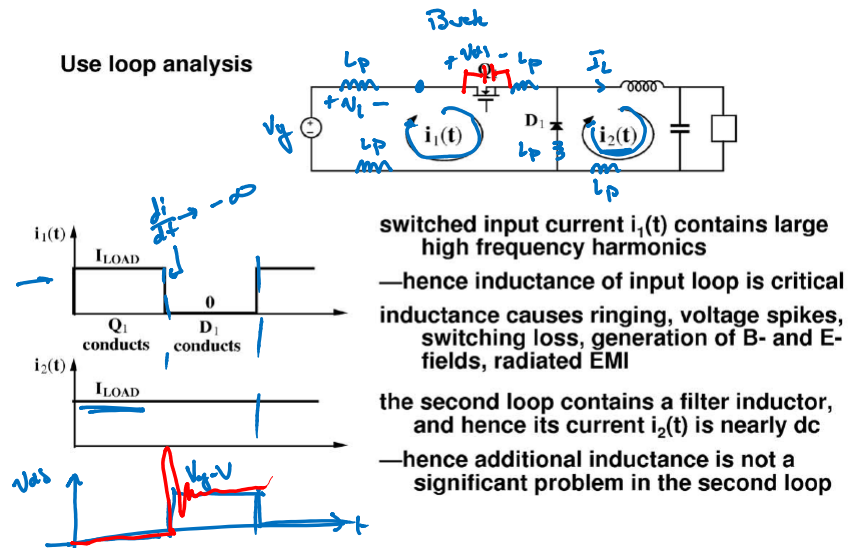

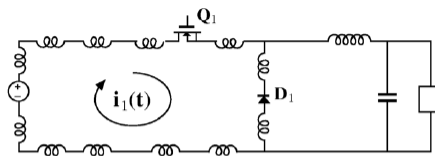
## Decoupling



Parasitic inductances of input loop explicitly shown:



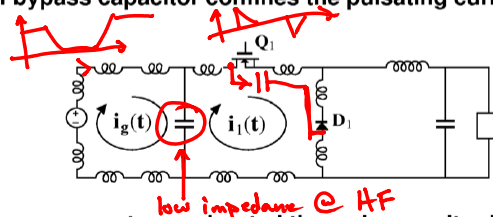Addition of bypass capacitor confines the pulsating current to a smaller loop:




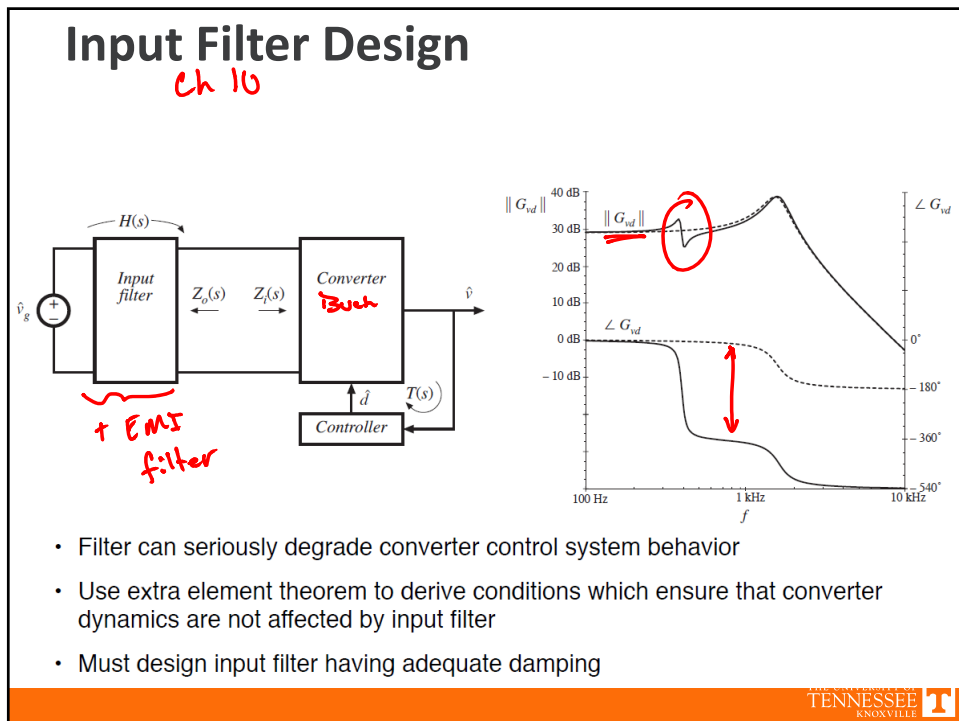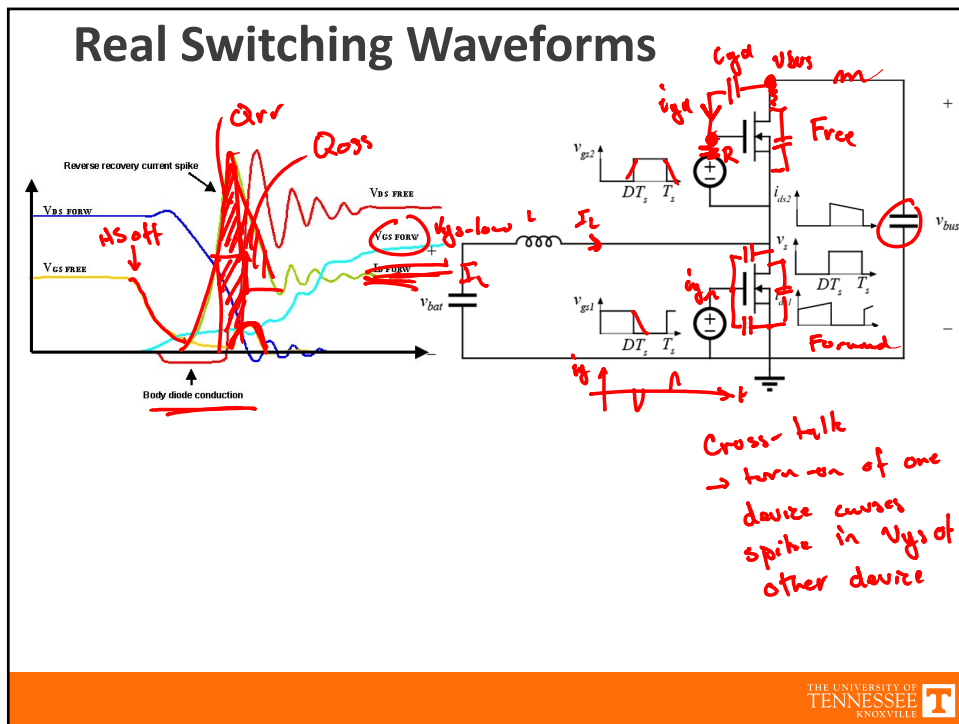high frequency currents are shunted through capacitor instead of input source



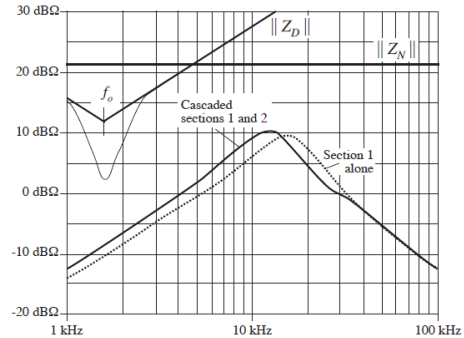
## Damped Input Filters


Design criteria derived via Extra Element theorem:




Two-section damped input filter design:

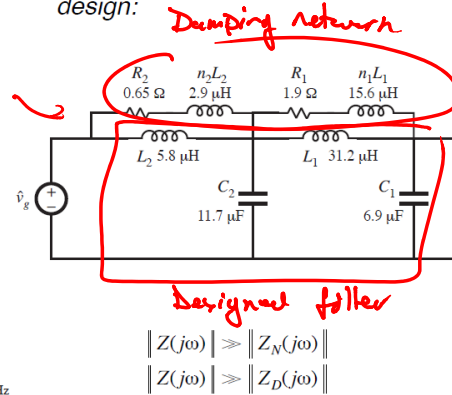

## Current Programmed Control

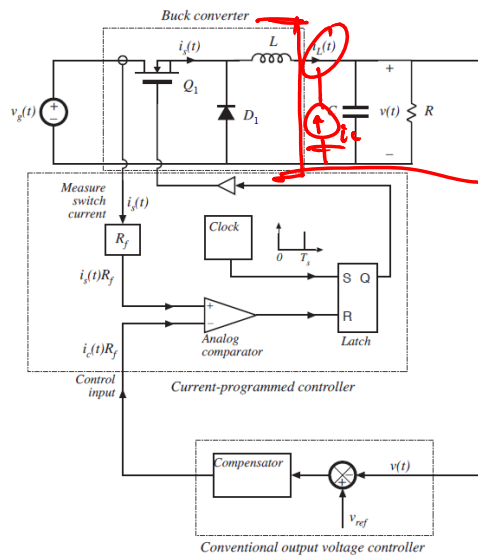


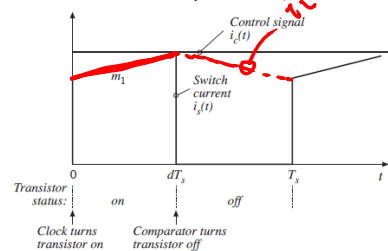- Chapter 12
- A very popular method for controlling PWM converters
- Transistor turns off when its current  $i_s(t)$  is equal to the control input  $i_c(t)$
- Simpler dynamics, more robust compensator



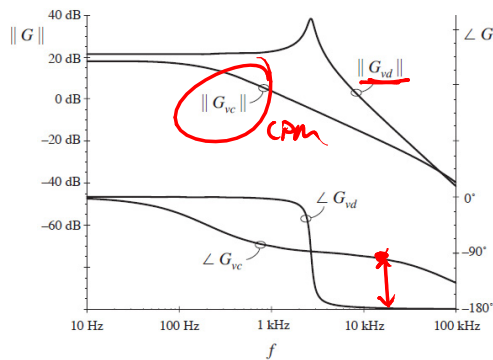
## Buck Converter With CPM


Comparison of control-to-output transfer functions



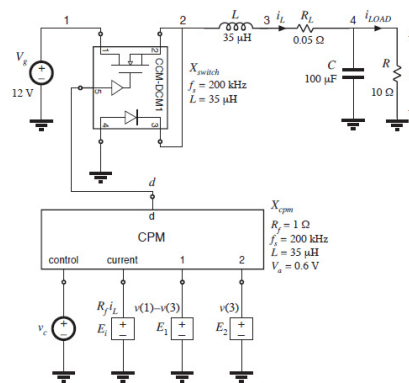Averaged switch model used in PSPICE simulations




## Digital Control of SMPS

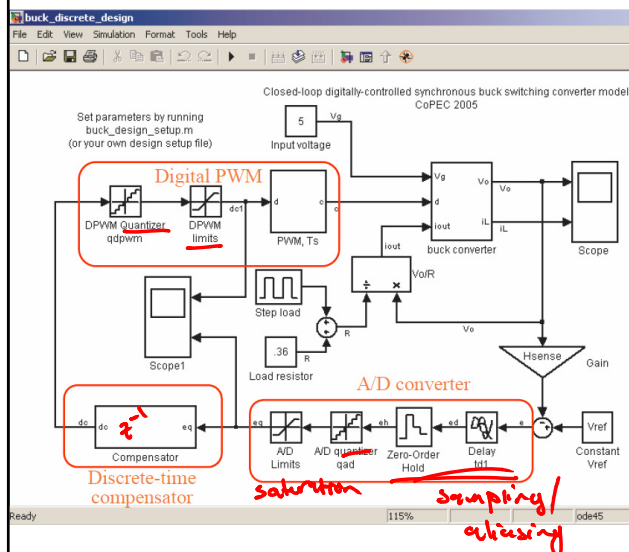


- Digital Control can improve noise immunity, element variation, size/cost
- Advanced tuning algorithms can be included to change compensator dynamically or over lifetime
- Can model power stage without averaging assumptions
- Need to include sampling, delay, saturation, and quantization effects
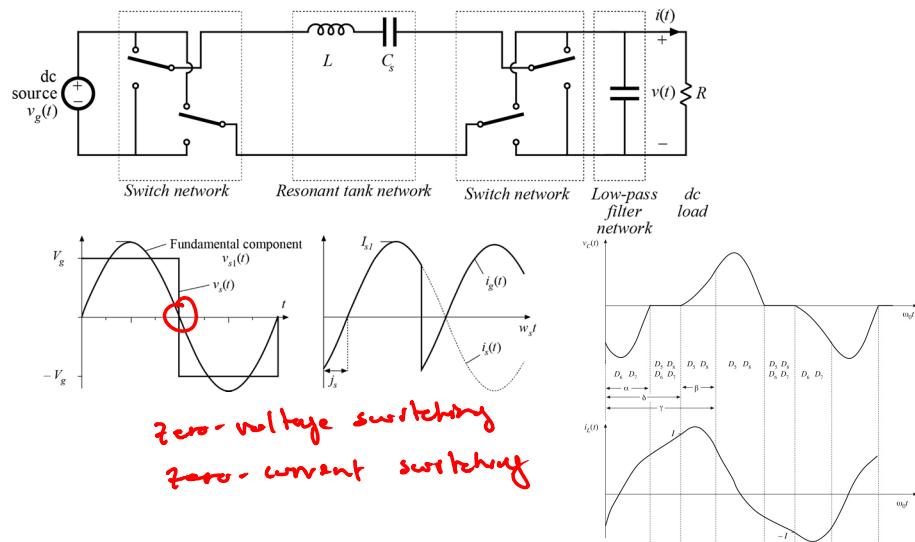
## Resonant and Soft-Switching Topologies



THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE
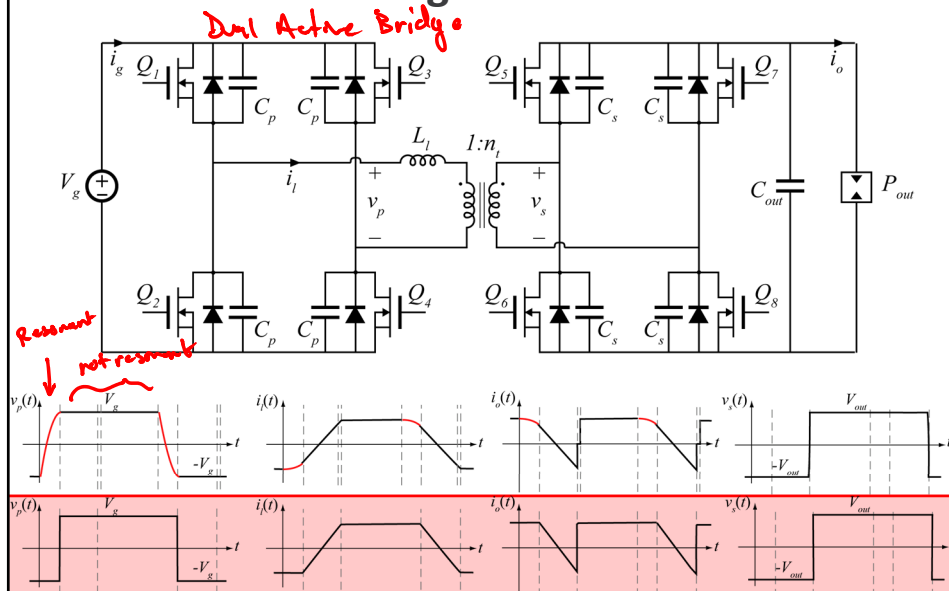
## Converters with Significant ZVS Interval



THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE

Power Electronics Courses at UTK			
Junior	Senior	Graduate	
ECE 325 Electric Energy System Components ✓	ECE 481 Power Electronics ✓	ECE 523 Power Electronics and Drives	ECE 623 Advanced Power Electronics and Drives
	ECE 482 Power Electronic Circuits <i>Practical construction</i>	ECE 525 Alternative Energy Sources	ECE 625 Utility Applications of Power Electronics
		ECE 581 High Frequency Power Electronics <i>Resonant soft-sw</i>	ECE 626 Solid State Power Semiconductors
		ECE 692 Power Electronics Technologies I	ECE 692 Power Electronics Technologies II
		+ 4 more <i>Wish</i>	

## APPLICATION OF ECE481 THEORY

## Example: Low-Power AC Adapters



Apple "Ultracompact USB Power Adapter"

### Goals:

- Produce regulated DC Voltage from universal input (85 to 276 Vrms, 47-63 Hz)
- Maintain high power factor / Low EMI
- High efficiency to allow small size
- *Low Cost!*

### Design Constraints:

- Single converter needs power stage which can operate over wide input voltage range
- For  $V_{dc} = +5\text{ V}$  (USB output) need very large step-down capability ( $M = 0.018$ )
- Isolation may be necessary for safety


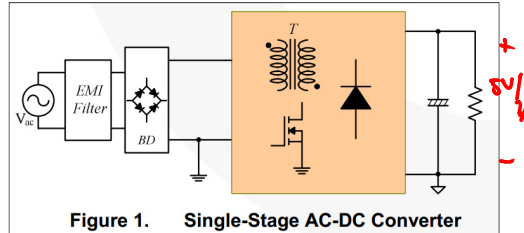
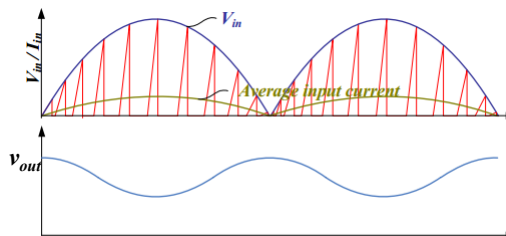


Figure 1. Single-Stage AC-DC Converter

Fairchild Semi, "Design Guideline of Single-Stage Flyback AC-DC Converter Using FAN7530 for LED Lighting"
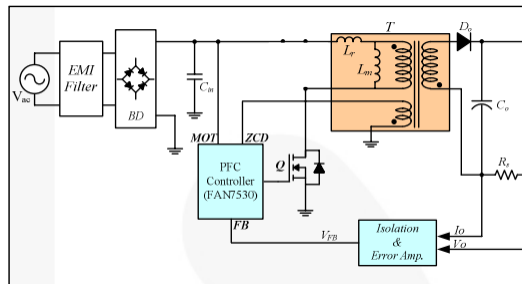
## Flyback Implementation



- Flyback selected as a simple, low part-count topology
- Used almost exclusively in Ac-to-LVDC applications at power levels less than ~100W
- DCM may be used for reduced diode RR and increased  $f_s$
- Pulsating input current requires filtering
- If unity power factor is obtained, significant output ripple results



Fairchild Semi, "Design Guideline of Single-Stage Flyback AC-DC Converter Using FAN7530 for LED Lighting"




## Practical Issue: Ringing in Flyback

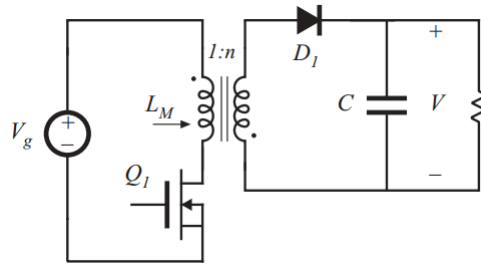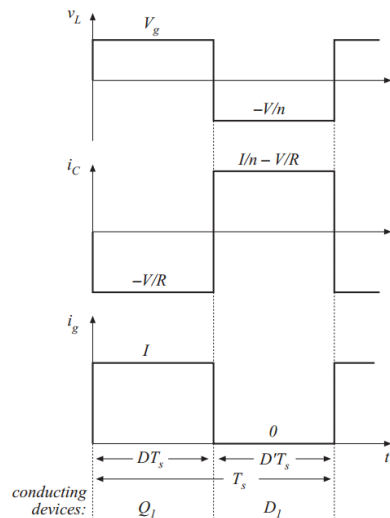

- Practical transformer implementation has nonzero leakage inductance
- When MOSFET switches off, it interrupts leakage current
- Inductor energy dumped into MOSFET output capacitance
- Lossy, high EMI, Potentially can over-voltage MOSFET  $Q_1$
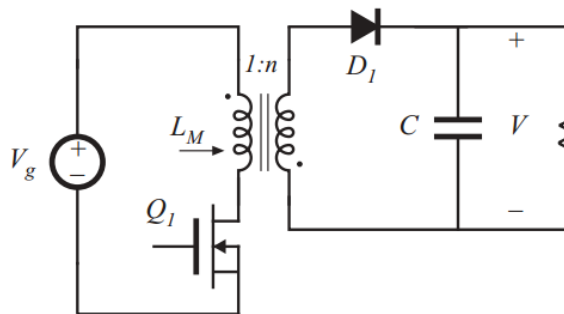
## Snubber Design

- Goal is to provide a path for leakage current to circulate



## Snubber Design

- Goal is to provide a path for leakage current to circulate

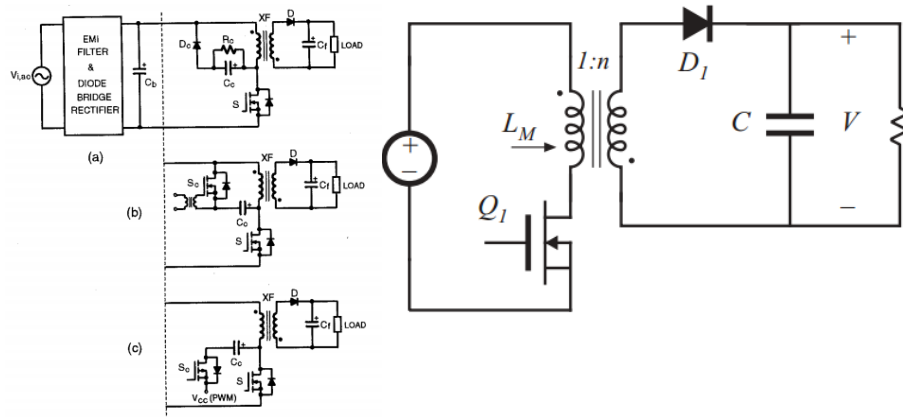



Fig. 1 Simplified circuit diagram of (a) RCD-clamp, (b) NMOS active-clamp, and (c) PMOS active-clamp flyback adapter/charger

L Huber and M Jovanovic, "Evaluation of Flyback Topologies for Notebook AC/DC Adapter/Charger Applications"

## Apple Power Adapter Implementation


Example:

- 5 Watt AC-to-5V adapter

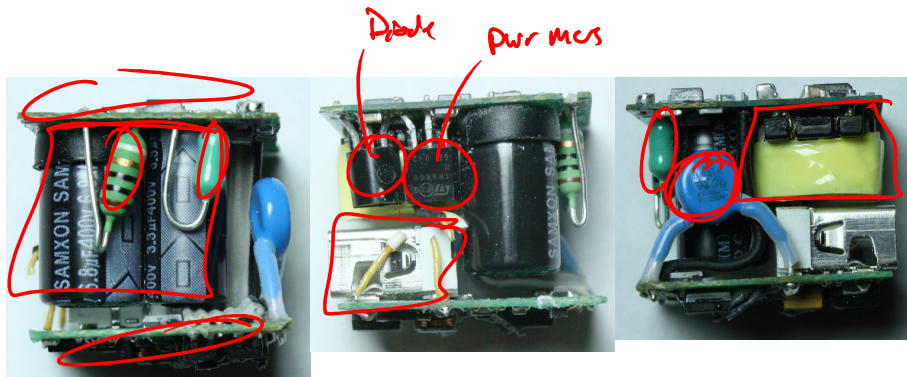

K Shirriff, "Apple iPhone charger teardown: quality in a tiny expensive package"



## Apple Circuit Primary

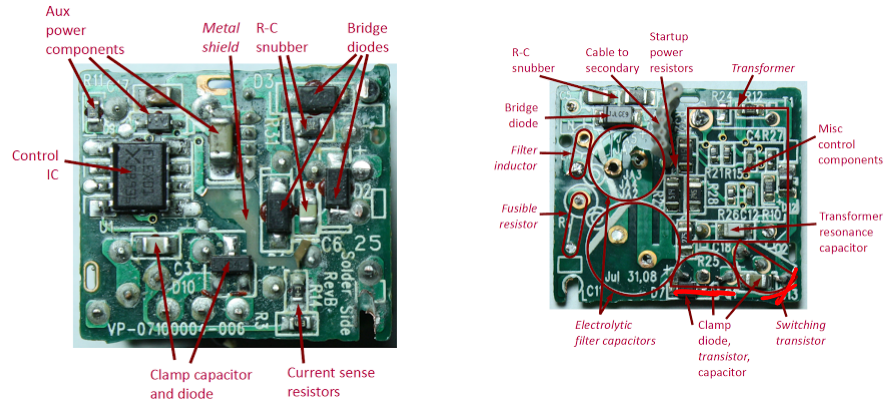

THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE




## Apple Circuit Secondary

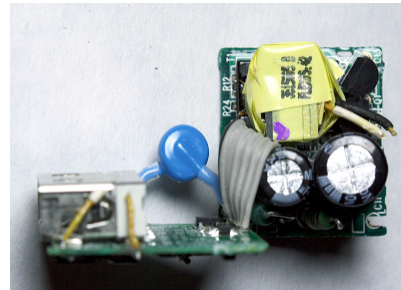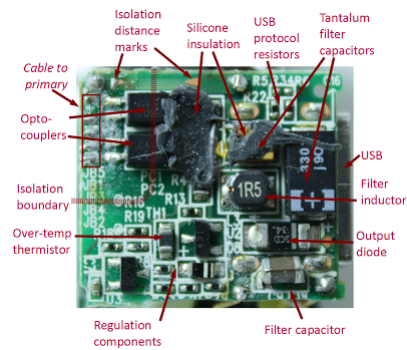


THE UNIVERSITY OF  
TENNESSEE  
KNOXVILLE



## Apple Adapter Schematic

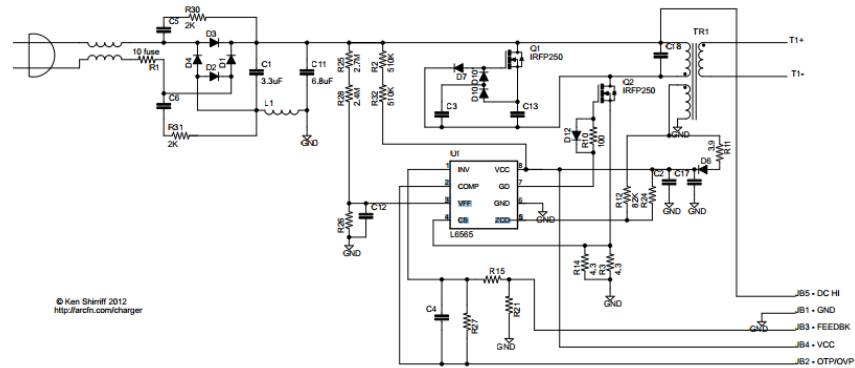

## Example Waveforms

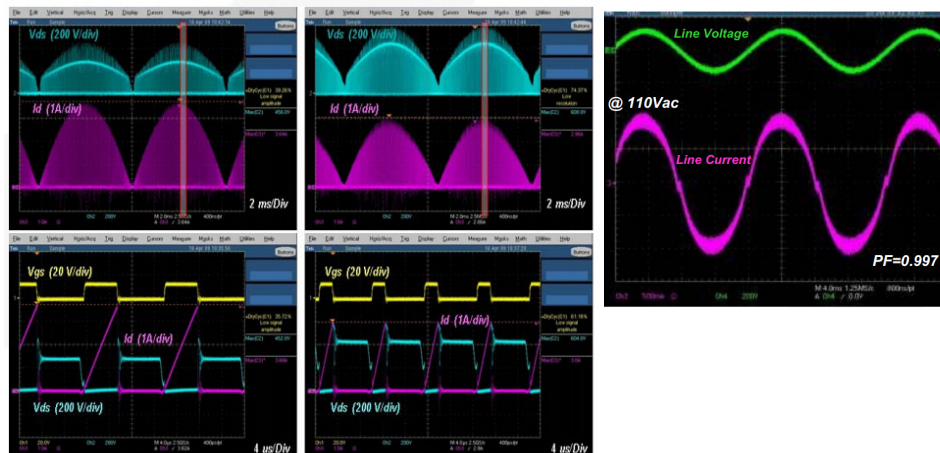

(a) at 110  $V_{ac}$  Input (b) at 220  $V_{ac}$  Input  
Figure 12. Switching Voltage and Current

L Huber and M Jovanovic, "Evaluation of Flyback Topologies for Notebook AC/DC Adapter/Charger Applications"