


Lecture 4: Cuk Converter Example; Ripple in second-order filters

ECE 481: Power Electronics
Prof. Daniel Costinett
Department of Electrical Engineering and Computer Science
University of Tennessee Knoxville
Fall 2015





THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Cuk Converter

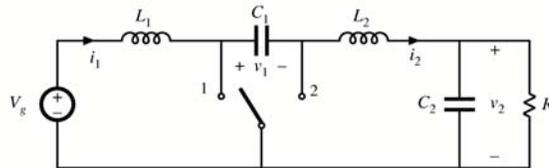


Cuk Equivalent Circuits

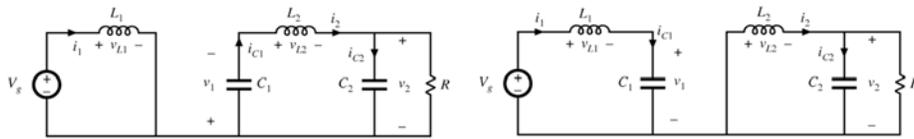

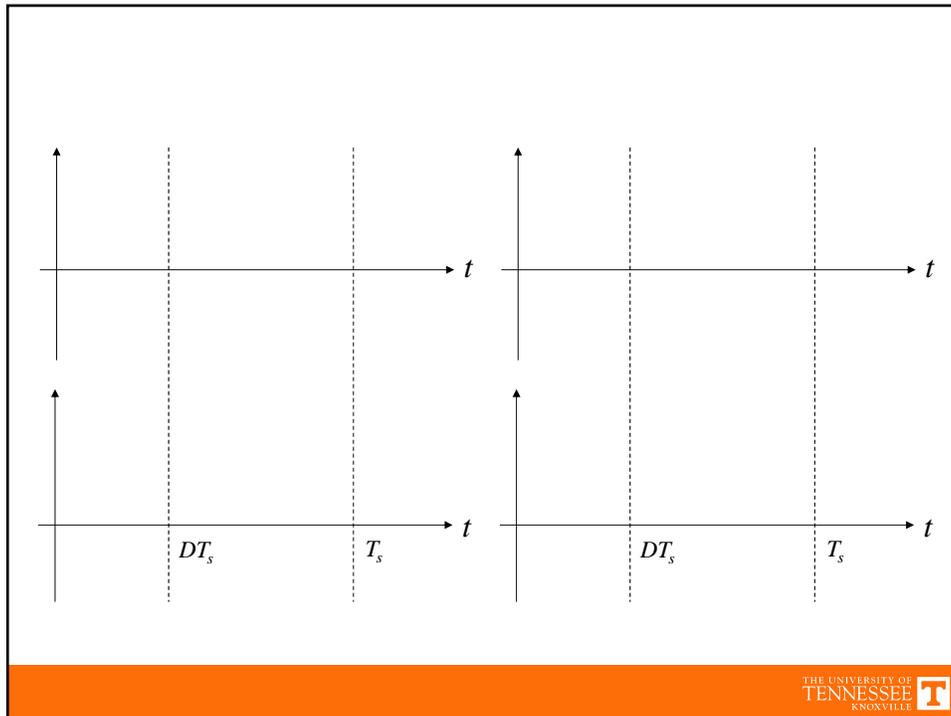

Ripple in Second Order Filters

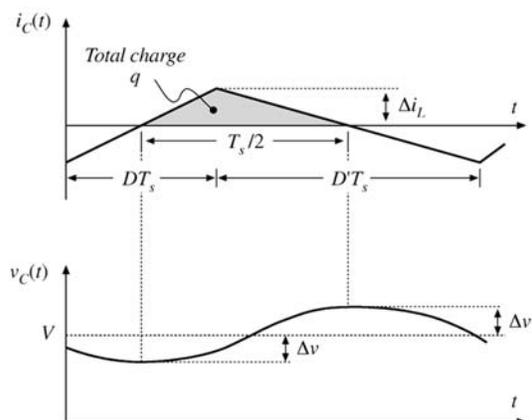

Steady-State Equivalent Circuit Modeling

- 3.1. The dc transformer model
- 3.2. Inclusion of inductor copper loss
- 3.3. Construction of equivalent circuit model
- 3.4. How to obtain the input port of the model
- 3.5. Example: inclusion of semiconductor conduction losses in the boost converter model
- 3.6. Summary of key points

Ideal Transformer Model

Simplifying Circuits with Ideal XF

Simplifying Circuits with Ideal XF

Simplifying Circuits with Ideal XF



The DC Transformer Model

