

Steady-State Equivalent Circuit Modeling

- 3.1. The dc transformer model
- 3.2. Inclusion of inductor copper loss
- 3.3. Construction of equivalent circuit model
- 3.4. How to obtain the input port of the model
- 3.5. Example: inclusion of semiconductor conduction losses in the boost converter model
- 3.6. Summary of key points


Ideal Transformer Model

Simplifying Circuits with Ideal XF

Simplifying Circuits with Ideal XF


Simplifying Circuits with Ideal XF

The DC Transformer Model

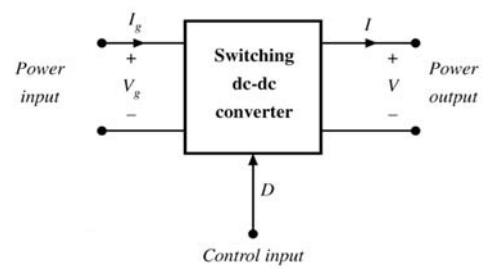

DC-DC Converter Equivalent Circuit
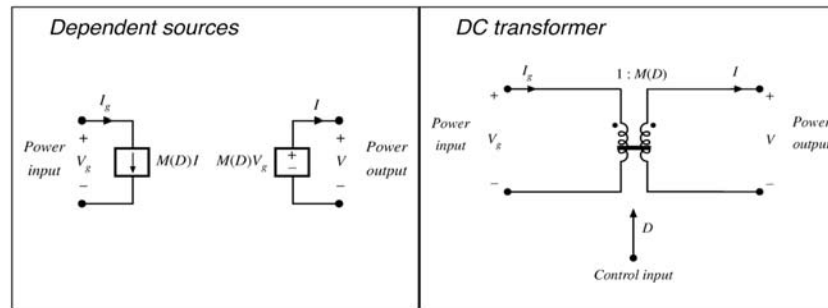
$$P_{in} = P_{out} \quad V_g I_g = V I \quad V = M(D) V_g \quad I_g = M(D) I$$



Fundamentals of Power Electronics

Chapter 2: Principles of steady-state converter analysis




Inclusion of Copper Loss

Dc transformer model can be extended, to include converter nonidealities.

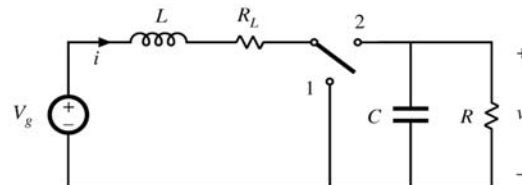
Example: inductor copper loss (resistance of winding):




Insert this inductor model into boost converter circuit:



Nonideal Boost Converter

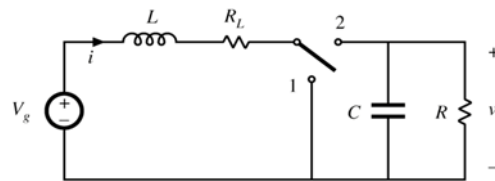

Nonideal Boost Output Voltage

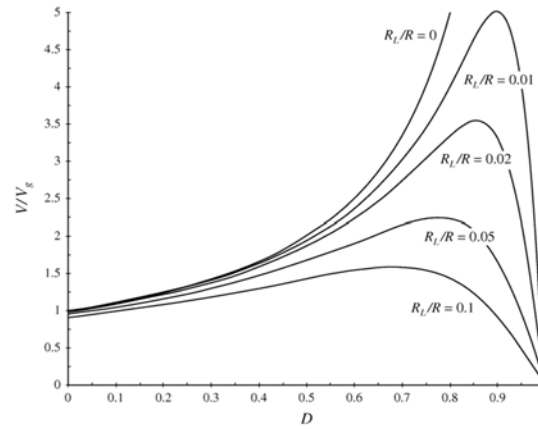

Construction of Equivalent Circuit Model



Buck Converter: Input Port Model

