

Implementing with SPST Switches

Step ①: Implement all switches w/ SPST


Non-trivial step

Now possible to have


~~X~~ A on & B on \rightarrow (shoot-through LARAS loss)
 OK A off & B off \rightarrow (dead time)
 \hookrightarrow used in discontinuous conduction mode (DCM) \rightarrow chapter 5

Buck converter

with SPDT switch:

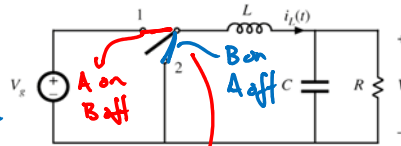

with two SPST switches:

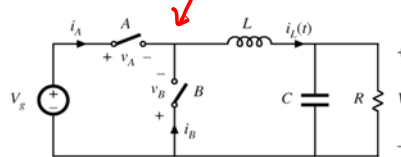


THE UNIVERSITY OF
TENNESSEE
KNOXVILLE



SPST Operating Quadrants

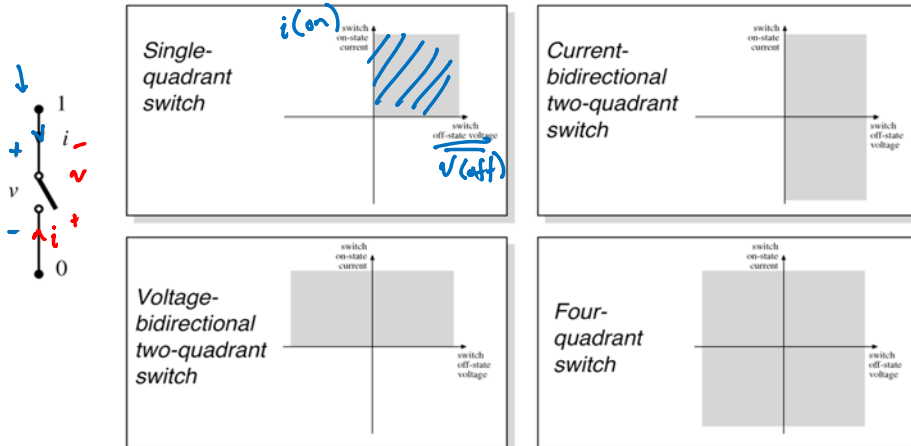step 2: Determine polarities of $v_{(off)}$ $i_{(on)}$ in the circuit




\rightarrow use ch. 2/3 techniques
 $v_{off}, i_{on} = f(V_g, R, D)$

know $V_g > 0$
 $R > 0$
 $0 < D < 1$

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE




The Diode

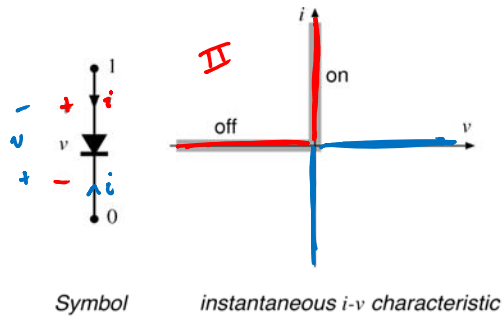

- A passive switch
- Single-quadrant switch:
- can conduct positive on-state current
- can block negative off-state voltage
- provided that the intended on-state and off-state operating points lie on the diode $i-v$ characteristic, then switch can be realized using a diode

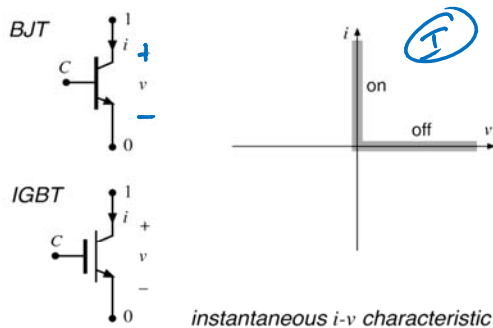
(Insulated Gate) Bipolar Junction Transistor



- An active switch, controlled by terminal C
- Single-quadrant switch:
- can conduct positive on-state current
- can block positive off-state voltage
- provided that the intended on-state and off-state operating points lie on the transistor $i-v$ characteristic, then switch can be realized using a BJT or IGBT

MOSFET

Body shorted to source

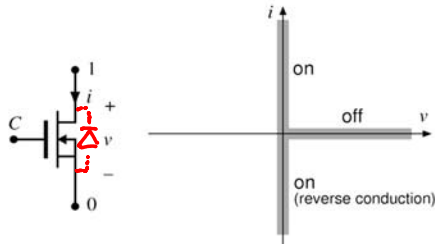

Symbol instantaneous i - v characteristic

- An active switch, controlled by terminal C
- Normally operated as single-quadrant switch:
- can conduct positive on-state current (can also conduct negative current in some circumstances)
- can block positive off-state voltage
- provided that the intended on-state and off-state operating points lie on the MOSFET i - v characteristic, then switch can be realized using a MOSFET

Fundamentals of Power Electronics


9

Chapter 4: Switch realization

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE




Buck Converter: Switch Realization

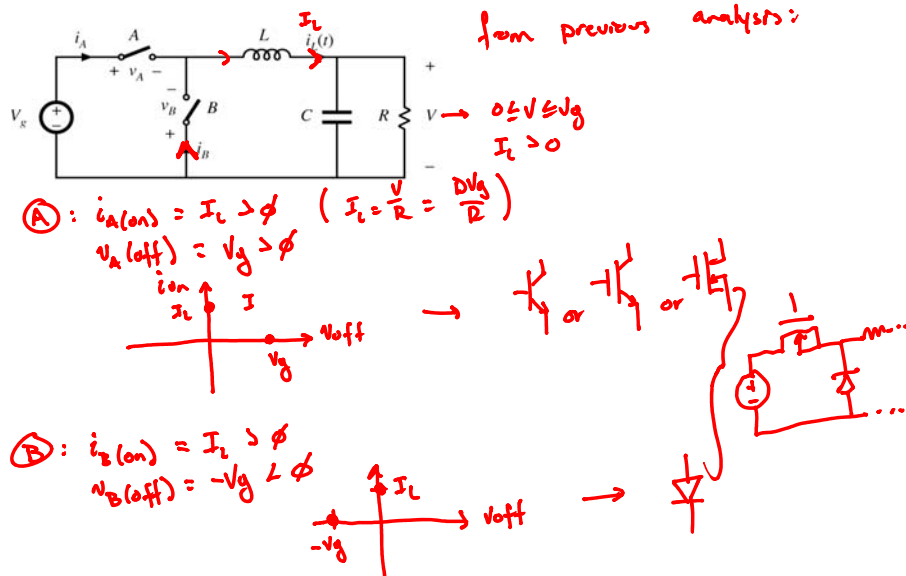

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE



Current Bidirectional Two-Quadrant

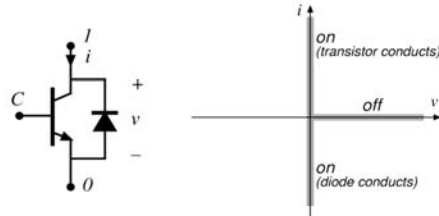


BJT / anti-parallel
diode realization


instantaneous i-v
characteristic

- Usually an active switch, controlled by terminal C
- Normally operated as two-quadrant switch:
- can conduct positive or negative on-state current
- can block positive off-state voltage
- provided that the intended on-state and off-state operating points lie on the composite i-v characteristic, then switch can be realized as shown


MOSFET Body Diode

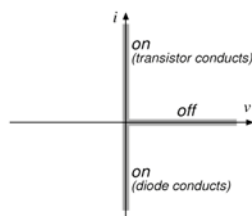

Power MOSFET
characteristics

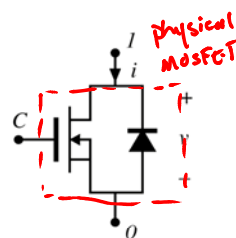


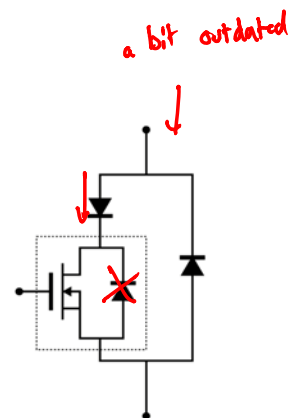Power MOSFET,
and its integral
body diode



Use of external diodes
to prevent conduction
of body diode

Voltage-bidirectional Two-Quadrant

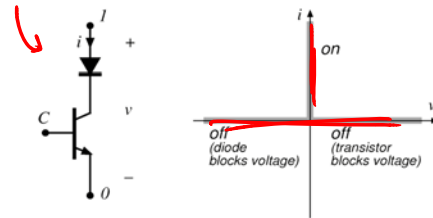

BJT / series
diode realization

instantaneous $i-v$
characteristic


- Usually an active switch, controlled by terminal C
- Normally operated as two-quadrant switch:
- can conduct positive on-state current
- can block positive or negative off-state voltage
- provided that the intended on-state and off-state operating points lie on the composite $i-v$ characteristic, then switch can be realized as shown
- The SCR is such a device, without controlled turn-off

Fundamentals of Power Electronics

19

Chapter 4: Switch realization

Four-Quadrant Switches

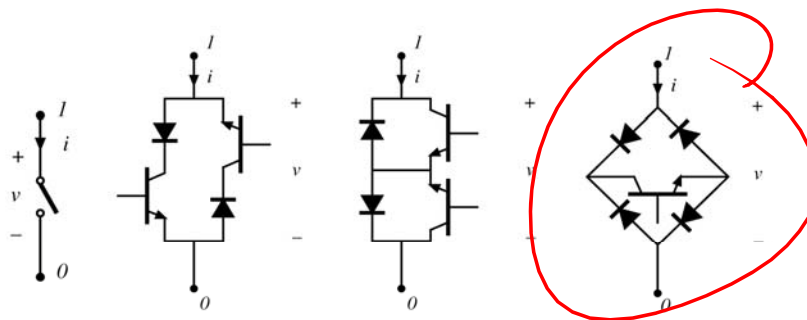


Fundamentals of Power Electronics


23

Chapter 4: Switch realization

Synchronous Rectifiers

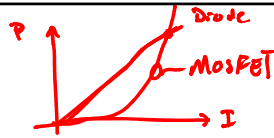

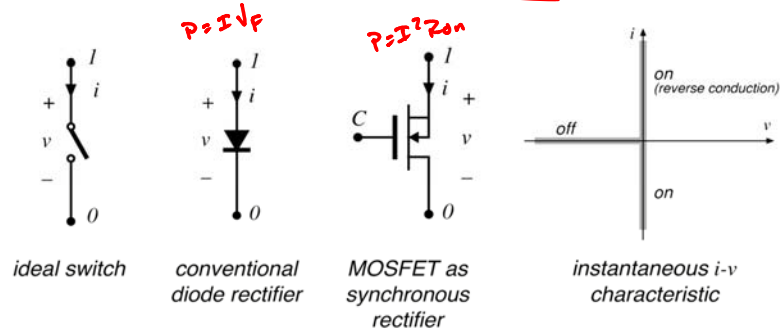Replacement of diode with a backwards-connected MOSFET, to obtain reduced conduction loss



Fundamentals of Power Electronics

25

Chapter 4: Switch realization

4.2: Survey of Power Semiconductor Devices

- Power diodes
- Power MOSFETs
- Bipolar Junction Transistors (BJTs)
- Insulated Gate Bipolar Transistors (IGBTs)
- Thyristors (SCR, GTO, MCT)
- On resistance vs. breakdown voltage vs. switching times
- Minority carrier and majority carrier devices

Fundamentals of Power Electronics

27

Chapter 4: Switch realization

Switching Nonidealities

