

Part II: Converter Dynamics and Control

7. AC equivalent circuit modeling
- 8. Converter transfer functions
- 9. Controller design
- ~~10.~~ Input filter design
- ~~11.~~ AC and DC equivalent circuit modeling of the discontinuous conduction mode
- ~~12.~~ Current programmed control — ECE 482

Chapter 7: AC Equivalent Circuit Modeling

7.1 Introduction

7.2 The basic AC modeling approach

waveform averaging

7.3 State-space averaging

Mention
only

7.4 Circuit averaging and averaged switch modeling

7.5 The canonical circuit model

7.6 Modeling the pulse-width modulator

7.7 Summary of key points

7.1: Introduction



Objective: maintain $v(t)$ equal to an accurate, constant value V .

There are disturbances:

- in $v_g(t)$
- in R

There are uncertainties:

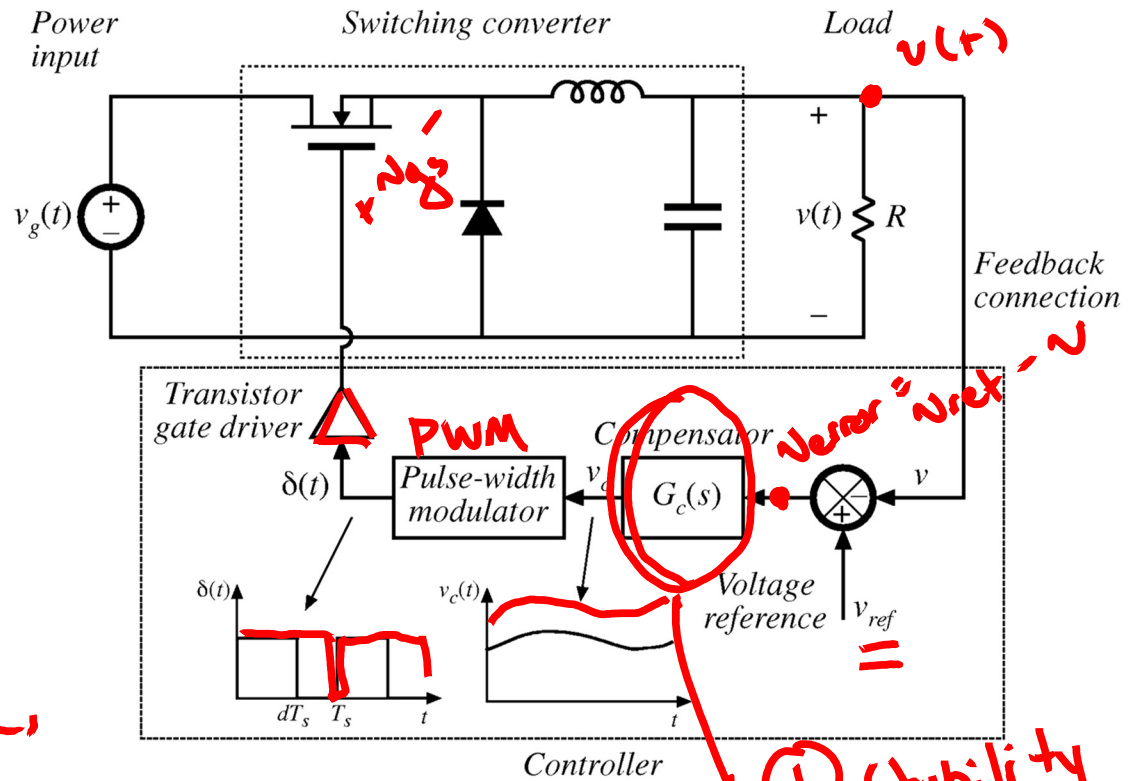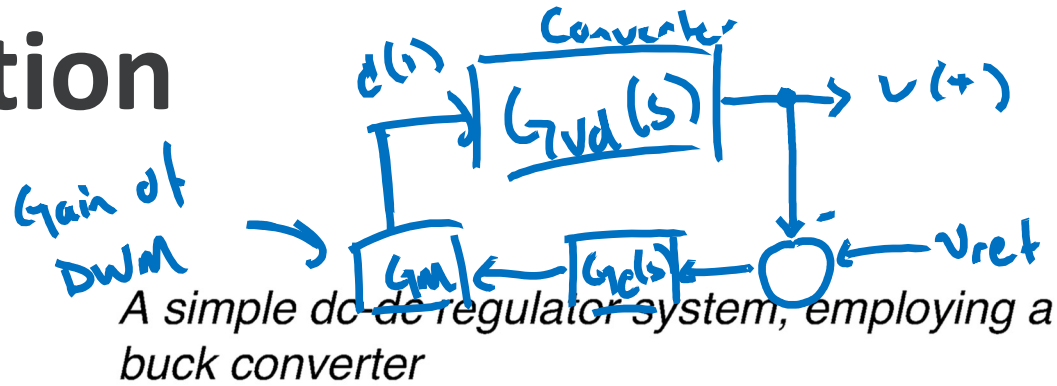- in element values
- in V_g
- in R
- loss mechanism



① Stability
② "well-behaved"

Control Objectives and Inputs

V_{out} control

- power supplies (DC)
- Off-grid inverter (AC)

I_{out} control



- grid-tied inverter (e.g. PV)

V_{in} control:

- PV MPP control

I_{in} control:

- Grid-tied rectifier

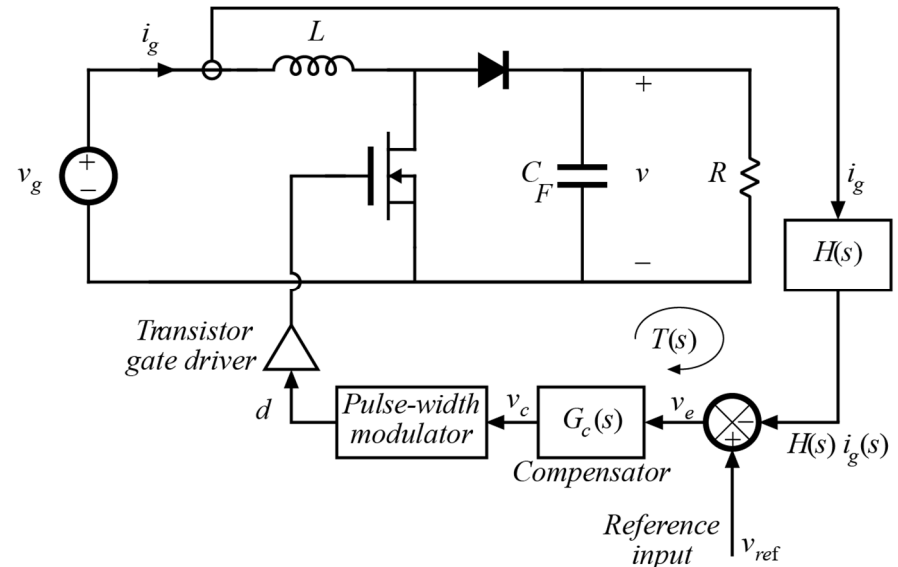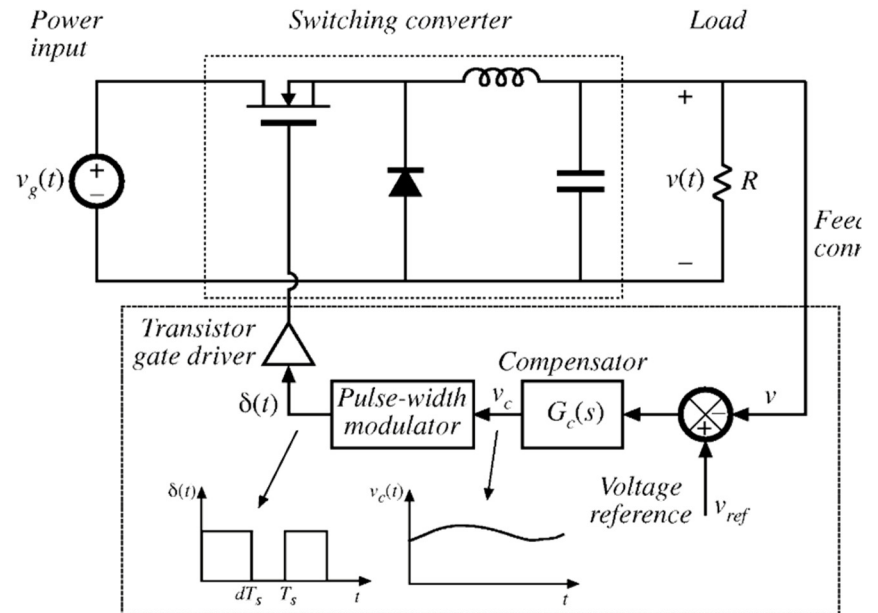

Objectives of Part II

Develop tools for modeling, analysis, and design of converter control systems

Need dynamic models of converters:

How do ac variations in $v_g(t)$, R , or $d(t)$ affect the output voltage $v(t)$?

What are the small-signal transfer functions of the converter?

- Extend the steady-state converter models of Chapters 2 and 3, to include CCM converter dynamics (Chapter 7)
- Construct converter small-signal transfer functions (Chapter 8)
- Design converter control systems (Chapter 9)
- ✗ Design input EMI filters that do not disrupt control system operation (Chapter 10)
- ✗ Model converters operating in DCM (Chapter 11)
- ✗ Current-programmed control of converters (Chapter 12)

$G_{vd}(s) = \frac{V_{or}(s)}{d(s)}$
↓
Linear, time-invariant (LTI)


PWM Spectrum

$$f_s = 450 \text{ kHz}$$



$$G_{vd}(s) = \frac{v}{d}$$

Inverter Output


$$D = 0.5$$

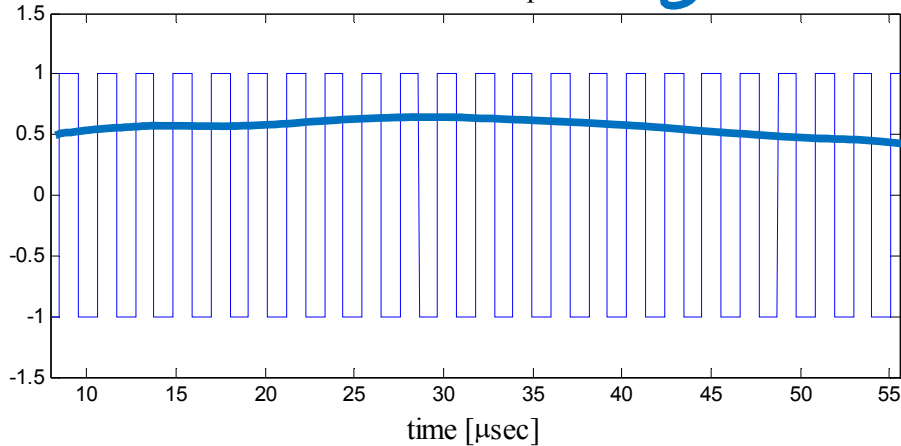

$d(t)$

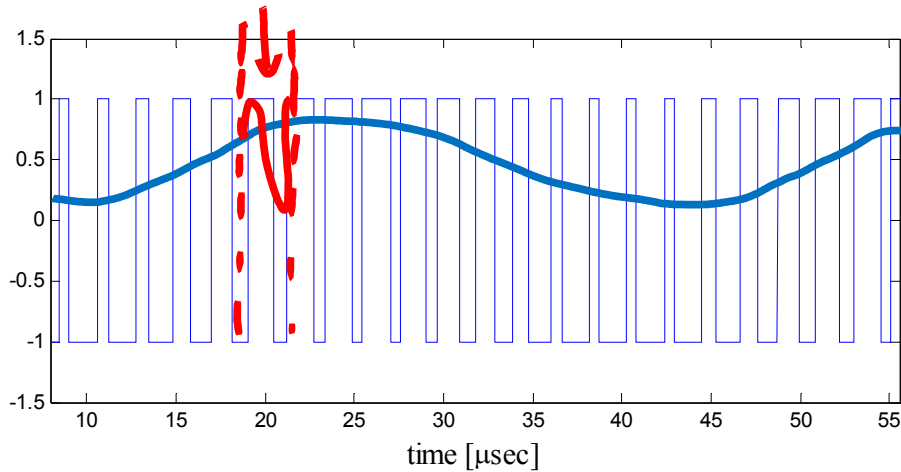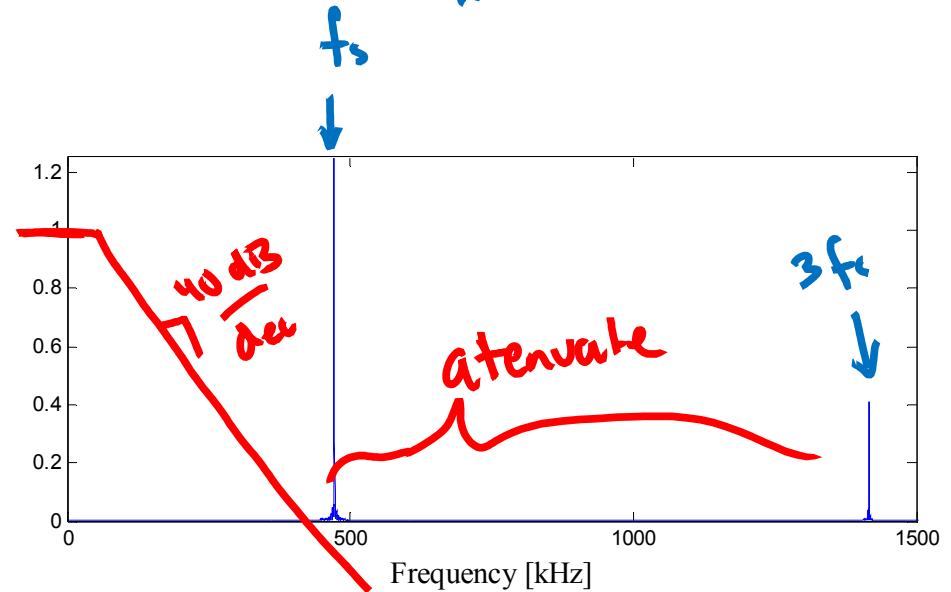

$d(t)$

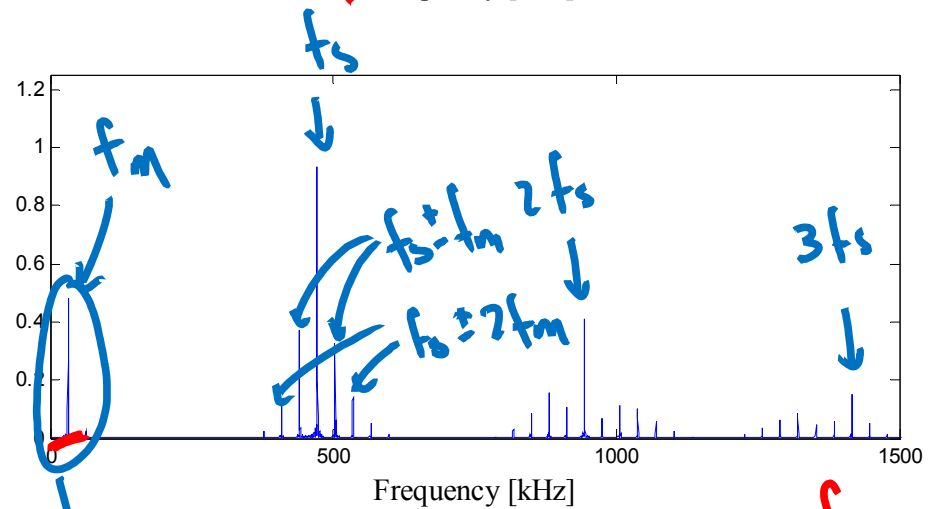

$$d(t) = 0.5 + D_m \cos(2\pi f_m t)$$

$$f_m = 50 \text{ kHz}$$

what we want to control

$$\underline{\underline{f_m \ll f_s}}$$

Neglecting The Switching Ripple


Suppose the duty cycle is modulated sinusoidally:

$$d(t) = \underline{D} + \underline{D}_m \cos \omega_m t$$


where D and D_m are constants, $|D_m| \ll D$, and the modulation frequency ω_m is much smaller than the converter switching frequency $\omega_s = 2\pi f_s$.

$$\omega_m \ll \omega_s$$

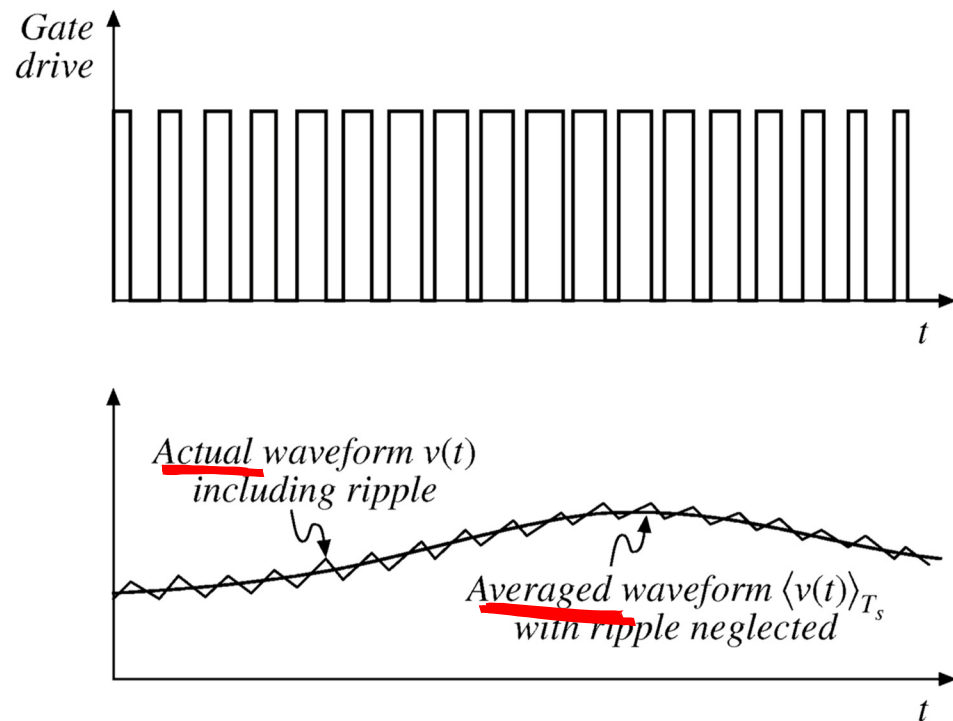The resulting variations in transistor gate drive signal and converter output voltage:



Output Voltage Spectrum

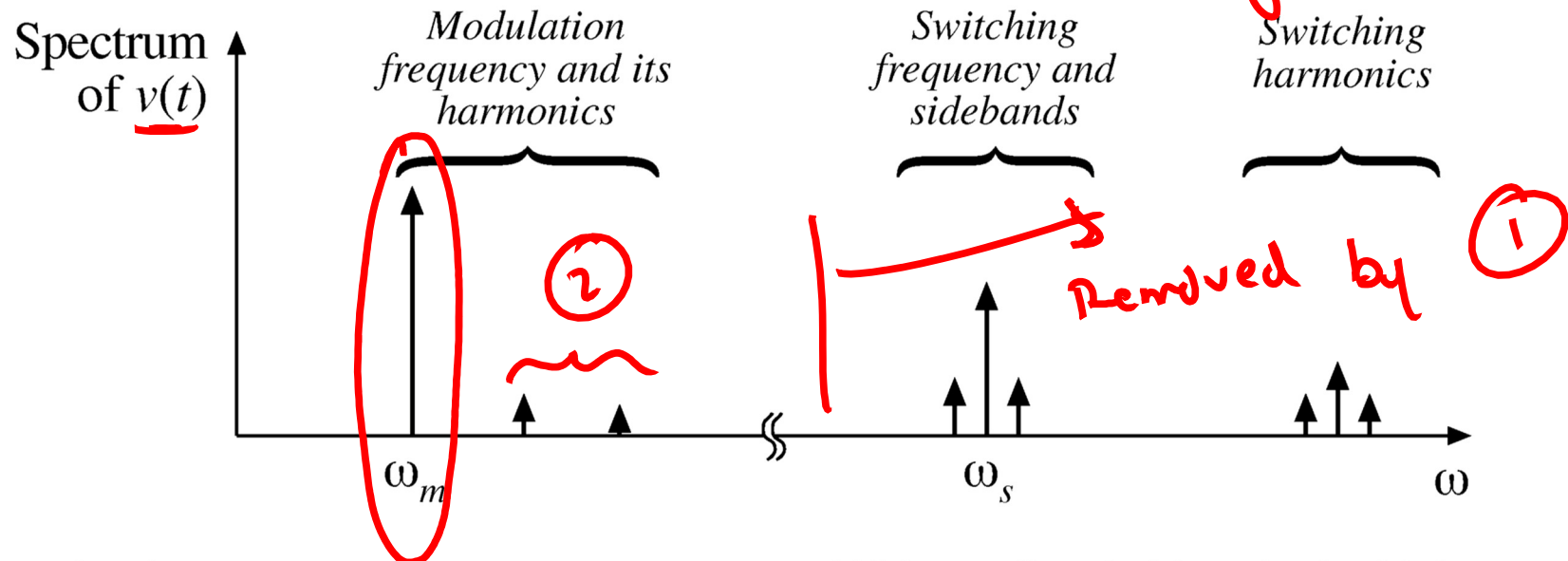

Contains frequency components at:

- Modulation frequency and its harmonics
- Switching frequency and its harmonics
- Sidebands of switching frequency

With small switching ripple, high-frequency components (switching harmonics and sidebands) are small.

If ripple is neglected, then only low-frequency components (modulation frequency and harmonics) remain.

Objectives of AC Modeling

@ $f_m \ll f_s$

- Predict how low-frequency variations in duty cycle induce low-frequency variations in the converter voltages and currents
- Ignore the switching ripple
- Ignore complicated switching harmonics and sidebands

Approach:

- Remove switching harmonics by averaging all waveforms over one switching period

Low-frequency Averaging

$\langle \cdot \rangle_{T_s} \rightarrow$ average over T_s

Average over one switching period to remove switching ripple:

$$L \frac{d\langle i_L(t) \rangle_{T_s}}{dt} = \langle v_L(t) \rangle_{T_s}$$

$$C \frac{d\langle v_C(t) \rangle_{T_s}}{dt} = \langle i_C(t) \rangle_{T_s}$$

where

$$\langle x(t) \rangle_{T_s} = \frac{1}{T_s} \int_t^{t+T_s} x(\tau) d\tau$$

Note that, in steady-state,

$$\langle v_L(t) \rangle_{T_s} = 0$$



$$\langle i_C(t) \rangle_{T_s} = 0$$

} not in transient conditions

by inductor volt-second balance and capacitor charge balance.

$L \nabla C$ will disappear from avg models / circuits

Averaging in Steady-State

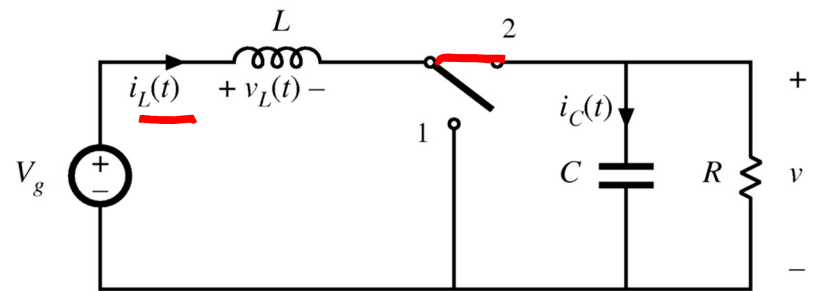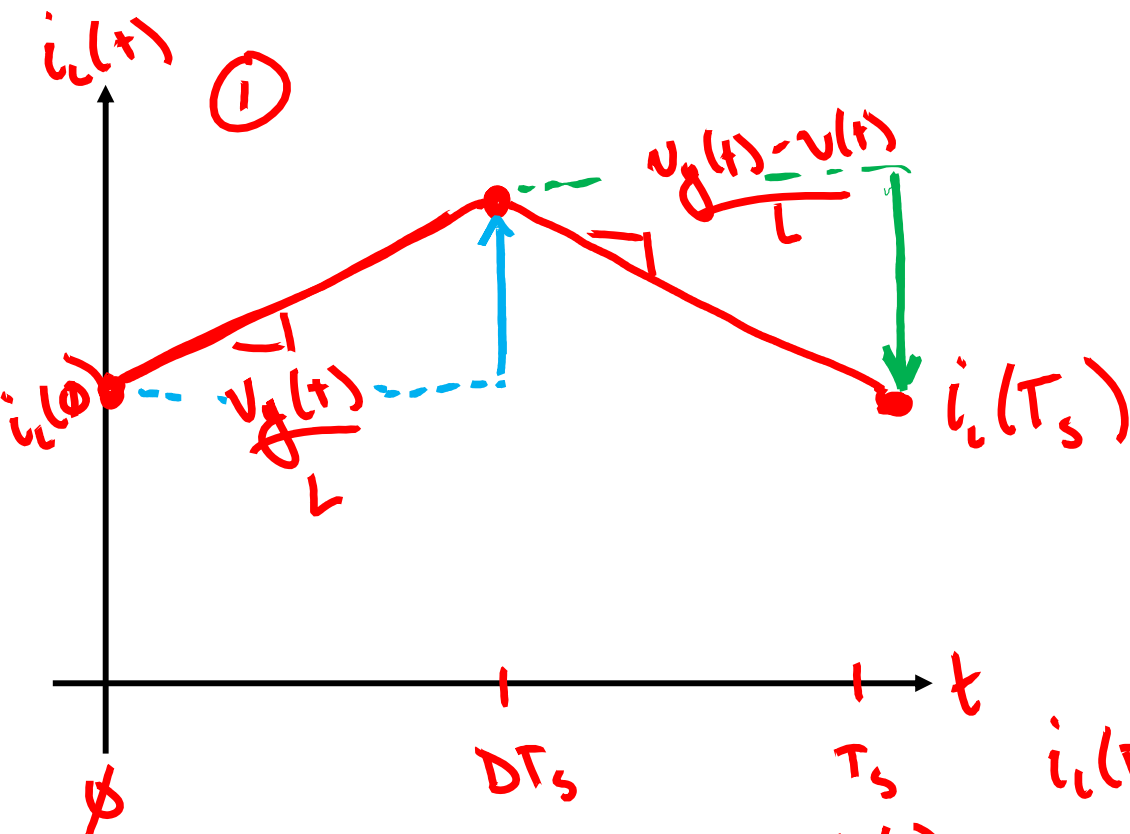

In steady-state:

$$\underline{i_L(0) = i_L(T_s)}$$

$$i_L(T_s) = i_L(0) + \uparrow + \downarrow$$

$$i_L(T_s) = i_L(0) + \frac{v_g(t)}{L} DT_s + \frac{v_g(t) - v(t)}{L} D'T_s$$

$$\frac{L}{T_s} [i_L(T_s) - i_L(0)] = (D + D') v_g(t) - D' v(t)$$

small ripple

Volts-second balance

$$L \frac{di}{dt} = \frac{L}{T_s} [i_L(T_s) - i_L(0)] = v_g - D'v = \langle v_L \rangle_{T_s}$$