
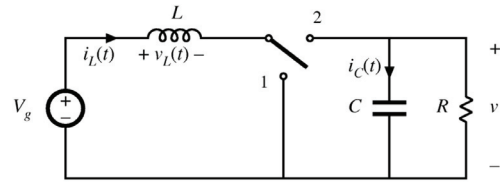


Averaging in Transient Operation

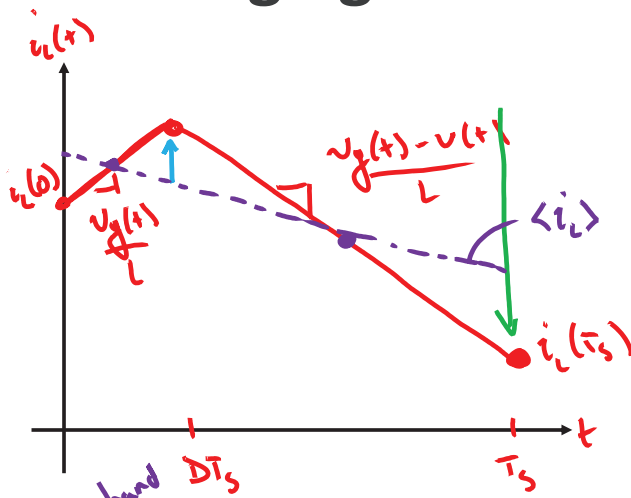

$$i_L(T_s) = i_L(0) + \frac{v_g(t)}{L} DT_s + \frac{v_g(t) - v(t)}{L} D' T_s$$

Small Ripple \rightarrow Averaging over T_s


short-hand $\langle x \rangle_{T_s}$

$$\frac{L}{T_s} [i_L(T_s) - i_L(0)] = D \langle v_g(t) \rangle_{T_s} + D' (\langle v_g(t) \rangle_{T_s} - \langle v(t) \rangle_{T_s})$$

$$\langle v_L \rangle = \frac{L}{T_s} [i_L(T_s) - i_L(0)] = \langle v_g \rangle - D' \langle v \rangle$$

$$\langle v_L \rangle = L \frac{d\langle i_L \rangle}{dt} = \langle v_g \rangle - d' \langle v \rangle$$


Averaging: Correct Prediction

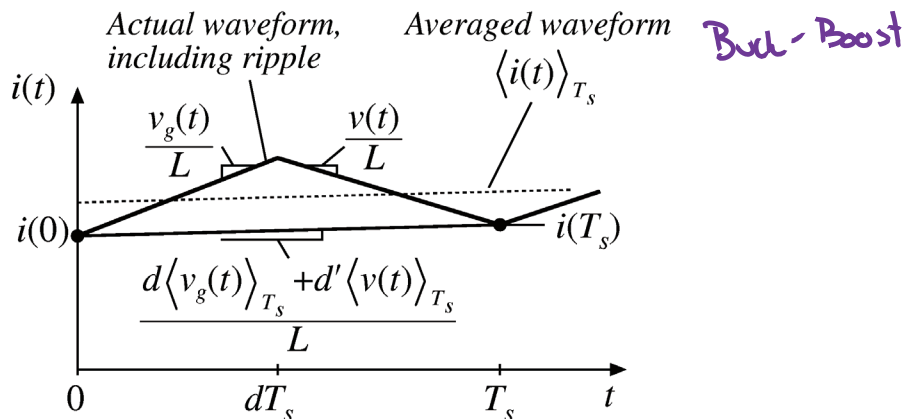

The net change in inductor current over one switching period is exactly equal to the period T_s multiplied by the average slope $\langle v_L \rangle_{T_s} / L$.

Averaging: Discussion

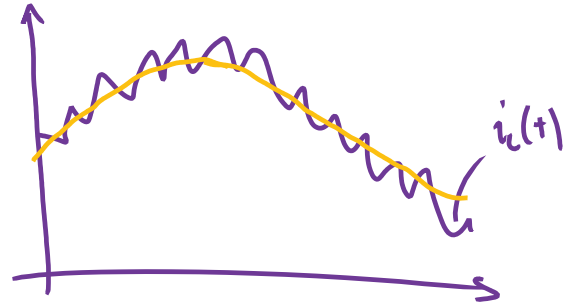Averaging will yield a correct prediction of averaged behaviors




Limitations:

- (1) Ripple \ll average value
- (2) $\omega_m \ll \omega_s$
- (3) circuit may still be nonlinear

Small Signal Modeling: Linearization

$$\langle v_c \rangle = L \frac{d\langle i_c \rangle}{dt} = \langle v_g \rangle - \underbrace{d'(+)\langle v \rangle}_{\text{Nonlinear, product of two time-varying signals}}$$

- want to linearize

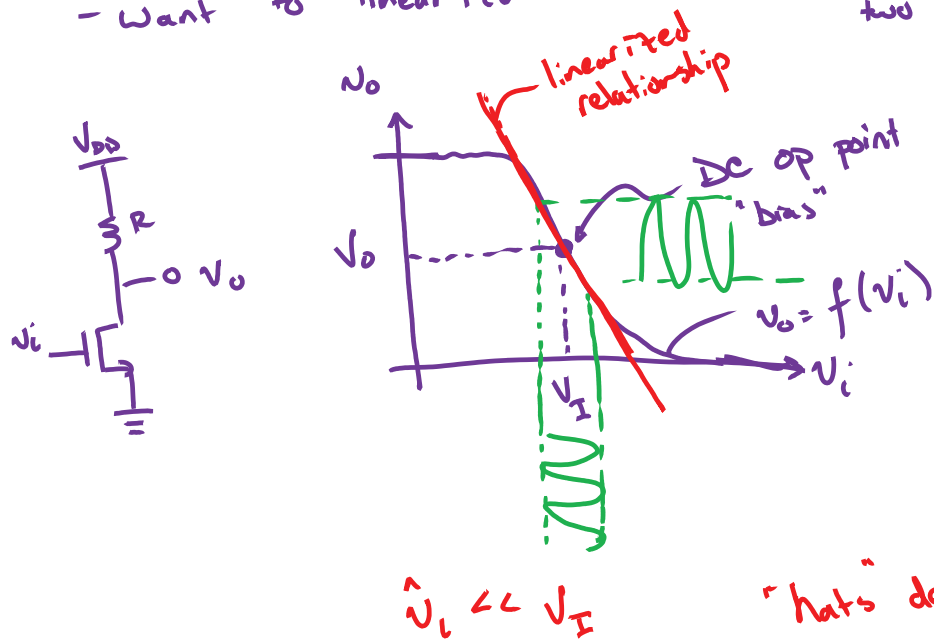

Small signal linearization
 if $v_o = f(v_i)$

$$v_o \approx f(V_I) + \hat{v}_i \left. \frac{df}{dv} \right|_{V_I}$$

$$\updownarrow$$

$$v_o$$

"hats" denote small-signal variables

(1) Perturb and Linearize

$$L \frac{d\langle i_c \rangle}{dt} = \langle v_g \rangle - d'(t) \langle v \rangle$$

$$\hat{x} \ll X$$

① Replace all $\langle x \rangle \rightarrow X + \hat{x}$
 ↑ DC op point ↖ AC small signal

② Eliminate all 2nd order or higher terms (nonlinear)

$$L \frac{d}{dt} (I_L + \hat{i}_c) = (V_g + \hat{v}_g) - (1 - D - \hat{d})(V + \hat{v})$$

$$L \frac{dI_L}{dt} + L \frac{d\hat{i}_c}{dt} = V_g + \hat{v}_g - V - \hat{v} + DV + D\hat{v} + \hat{d}V + \hat{d}\hat{v}$$

Neglect 2nd order terms

$$\text{DC} \begin{cases} L \frac{dI_L}{dt} = V_g - D'V \\ \text{AC} \begin{cases} L \frac{d\hat{i}_c}{dt} = \hat{v}_g - D'\hat{v} + \hat{d}V \end{cases} \end{cases}$$

(2) 1st order Taylor Series Expansion

Recall Taylor Series:

$$f(x_1, x_2, \dots) \approx f(x_1, x_2, \dots) + \hat{x}_1 \left. \frac{\partial f}{\partial x_1} \right|_{DC} + \hat{x}_2 \left. \frac{\partial f}{\partial x_2} \right|_{DC} + \text{2nd order \& higher terms}$$

$$L \frac{d\langle i_c \rangle}{dt} = \underbrace{\langle v_g \rangle}_{f(v_g, d, v)} - d'(t) \langle v \rangle =$$

$$\text{AC: } L \frac{d\hat{i}_c}{dt} = \hat{v}_g \left(\frac{\partial f}{\partial v_g} \right) + \hat{v} \left(-\frac{\partial f}{\partial v} \right) + \hat{d} \left(\frac{\partial f}{\partial d} \right)$$