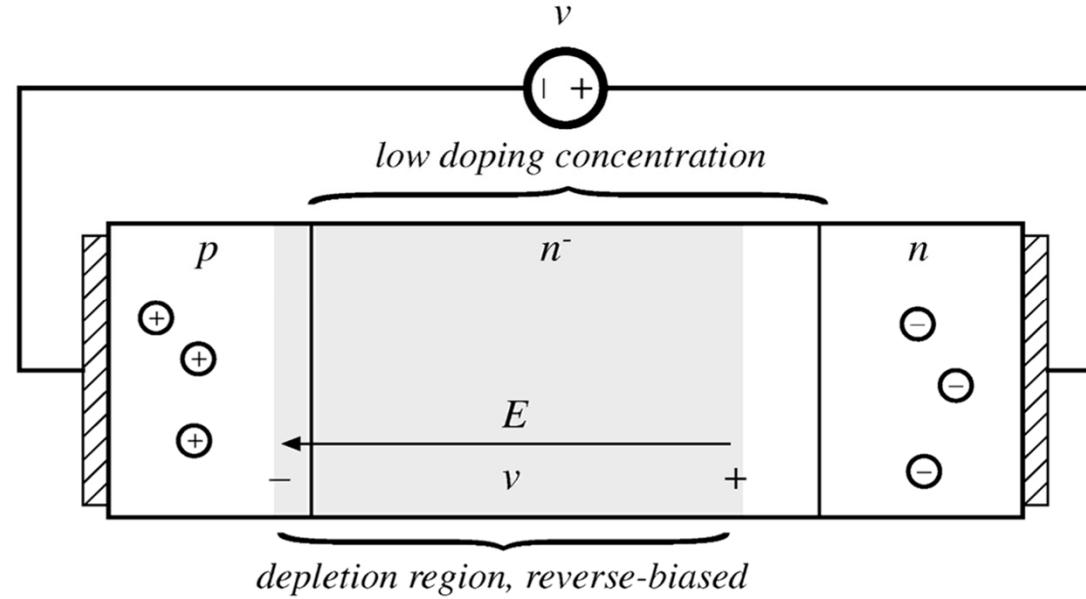


# Reverse Biased Diode



# Diode Stored Charge

The diode equation:

$$q(t) = Q_0 \left( e^{\lambda v(t)} - 1 \right)$$

Charge control equation:

$$\frac{dq(t)}{dt} = i(t) - \frac{q(t)}{\tau_L}$$

With:

$$\lambda = 1/(26 \text{ mV}) \text{ at } 300 \text{ K}$$


$\tau_L$  = minority carrier lifetime

(above equations don't include current that charges depletion region capacitance)

Fundamentals of Power Electronics

33


Chapter 4: Switch realization

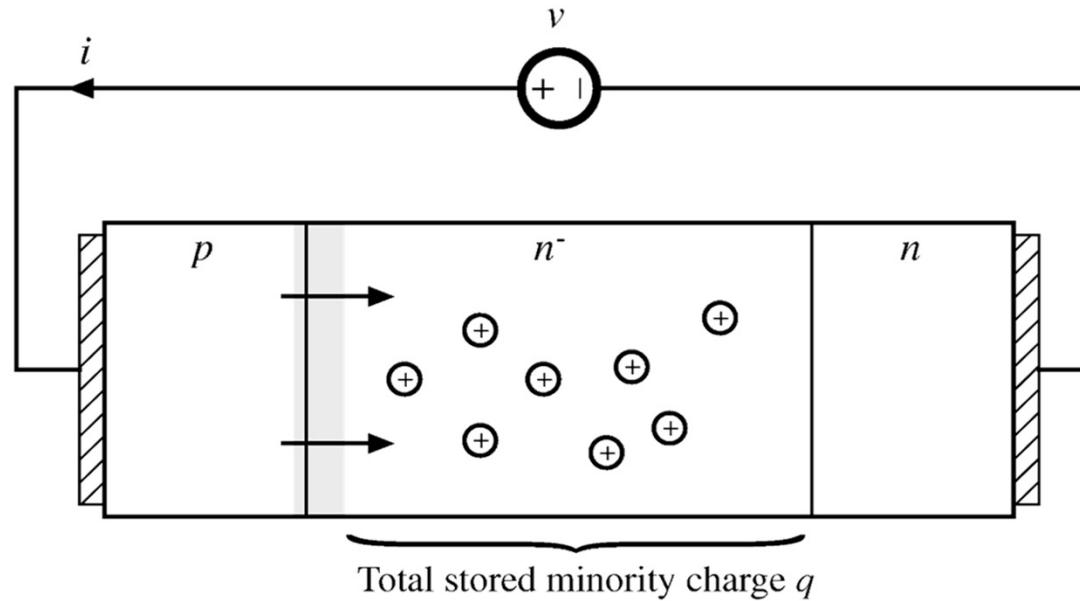


In equilibrium:  $dq/dt = 0$ , and hence

$$i(t) = \frac{q(t)}{\tau_L} = \frac{Q_0}{\tau_L} \left( e^{\lambda v(t)} - 1 \right) = I_0 \left( e^{\lambda v(t)} - 1 \right)$$



# Diode Turn-On

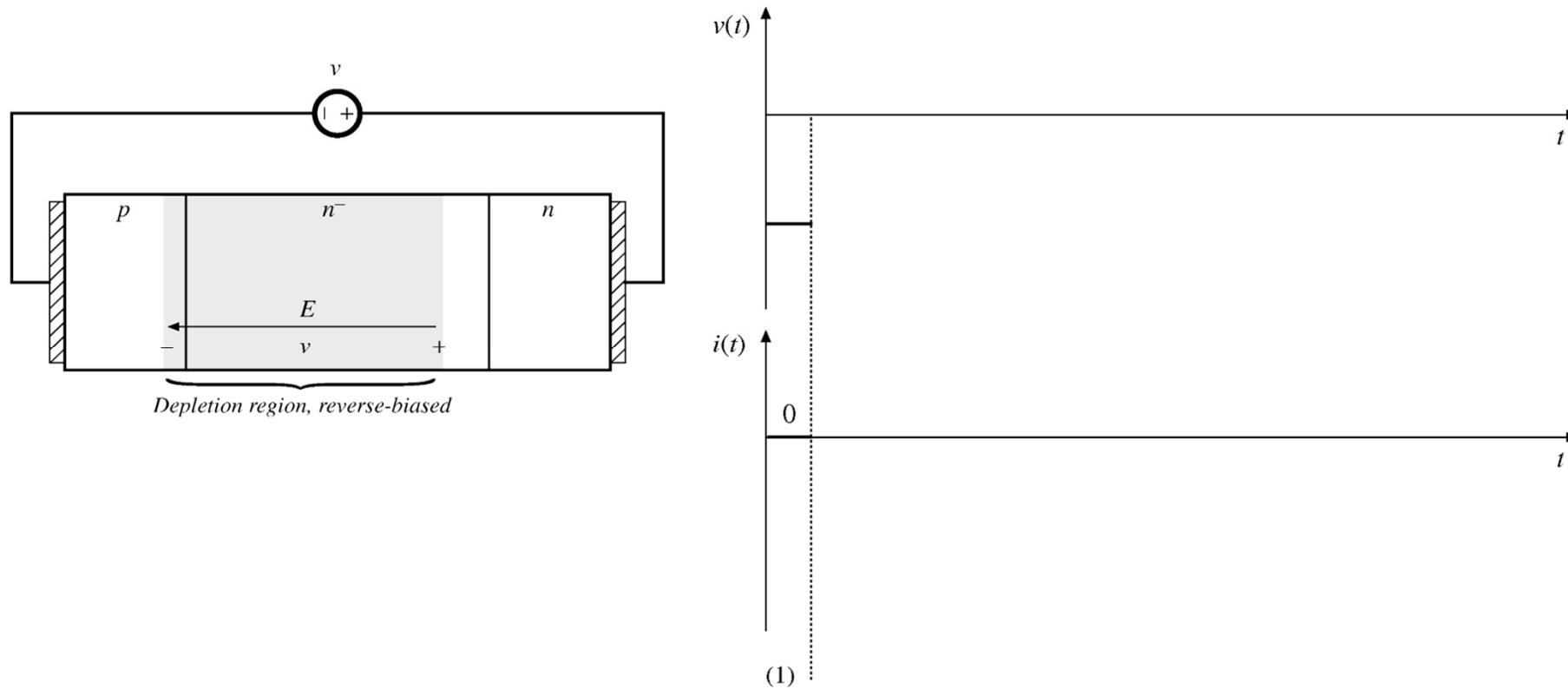

# Diode Turn-Off

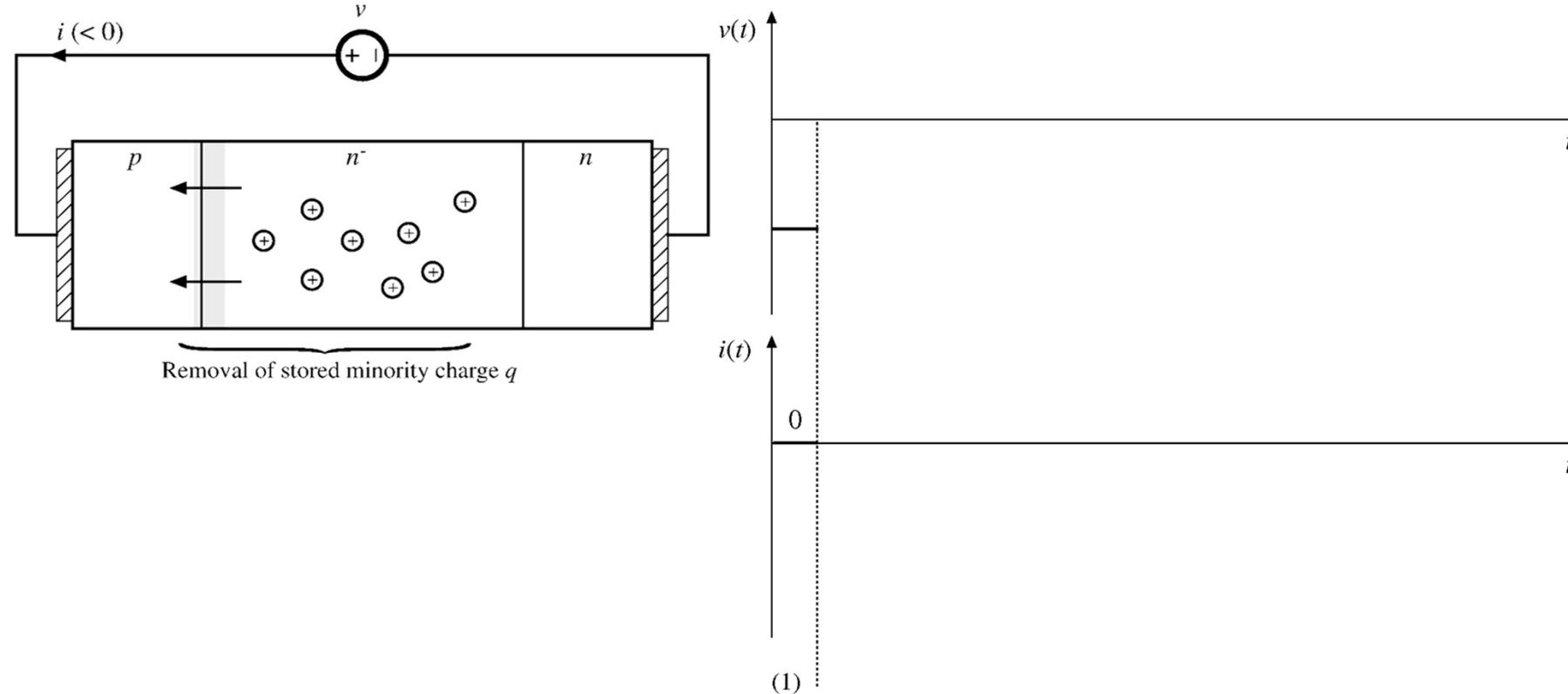

# Diode Reverse Recovery

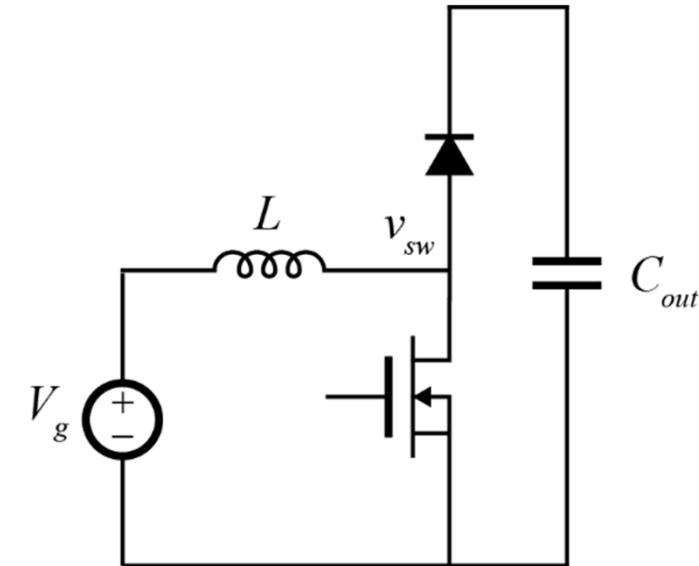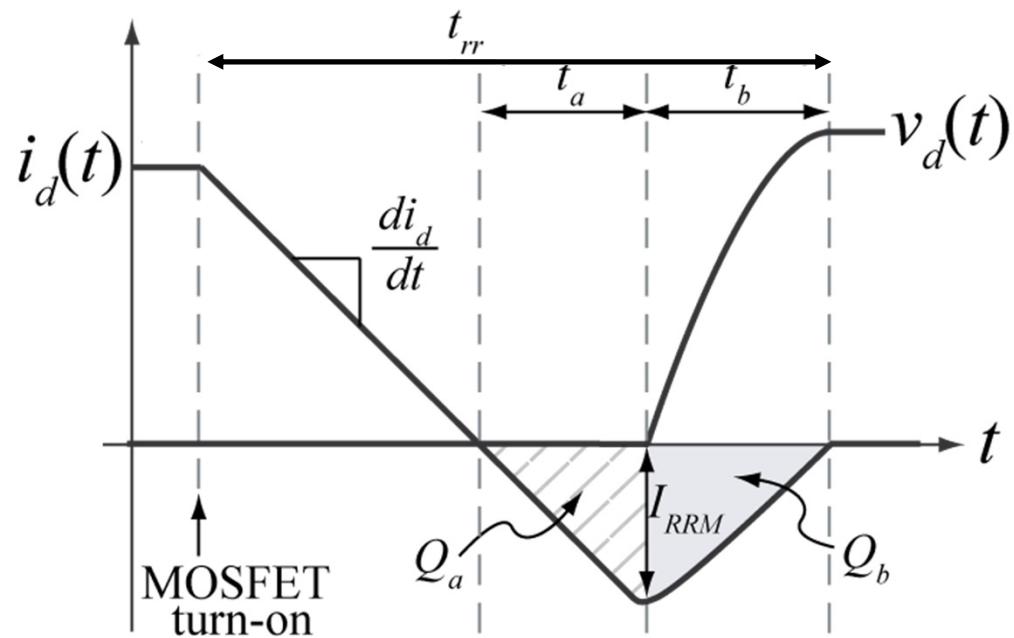

# Datasheet RR Characteristics

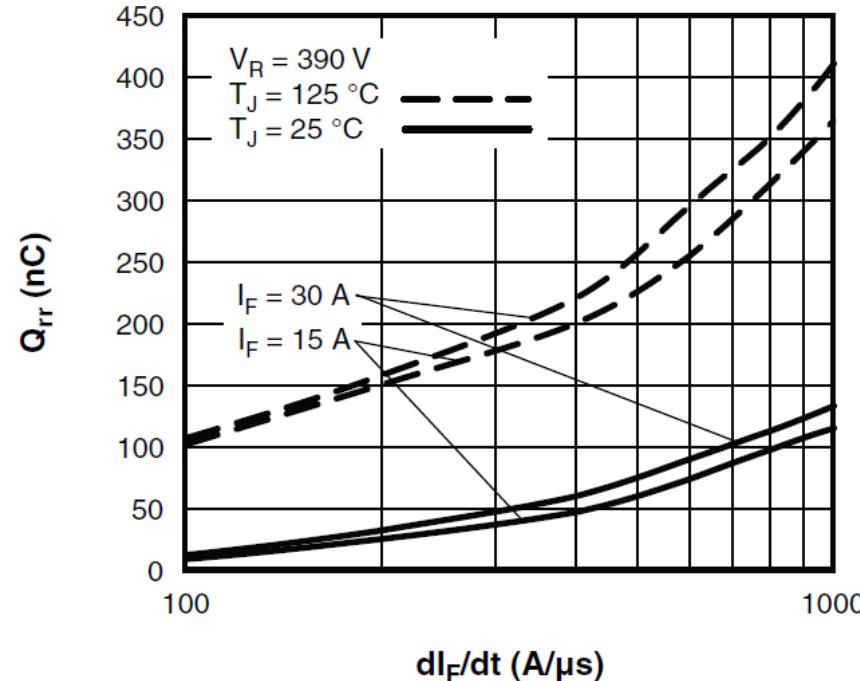


Fig. 10 - Typical Stored Charge vs.  $di_F/dt$


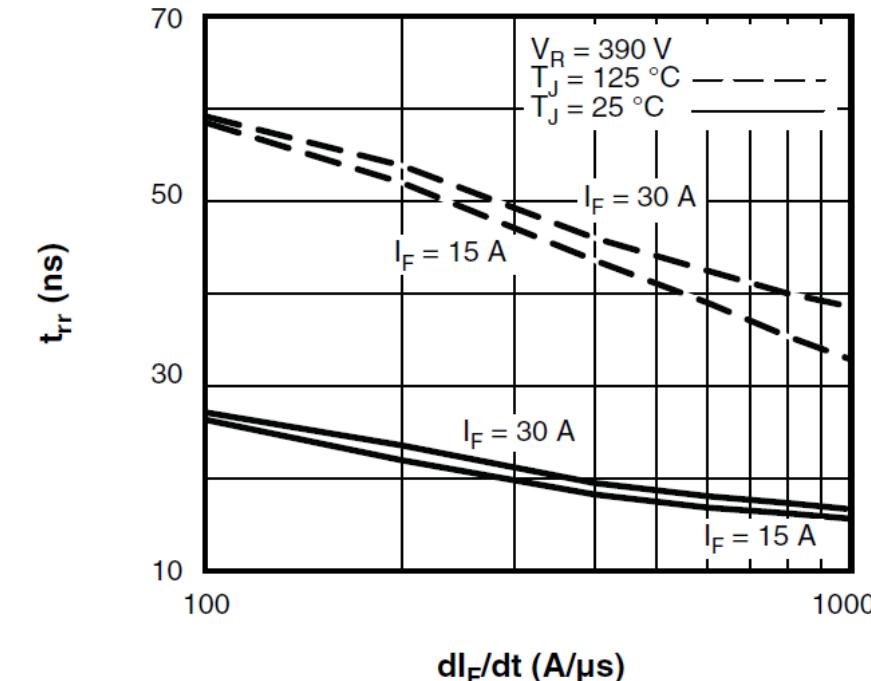


Fig. 9 - Typical Reverse Recovery Time vs.  $di_F/dt$
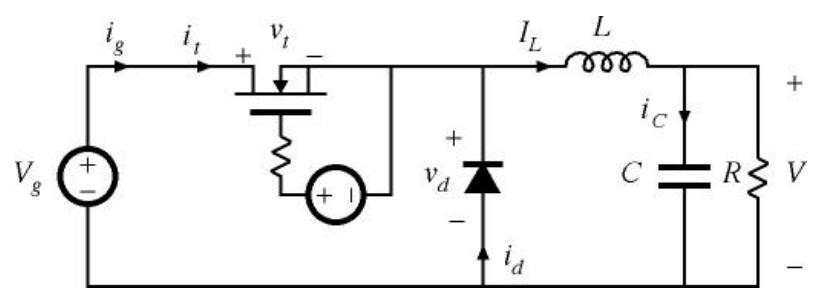
# Buck Converter Example

- All elements ideal except for reverse recovery ( $Q_r$  and  $t_r$ ) of diode



# Buck Average Model with RR