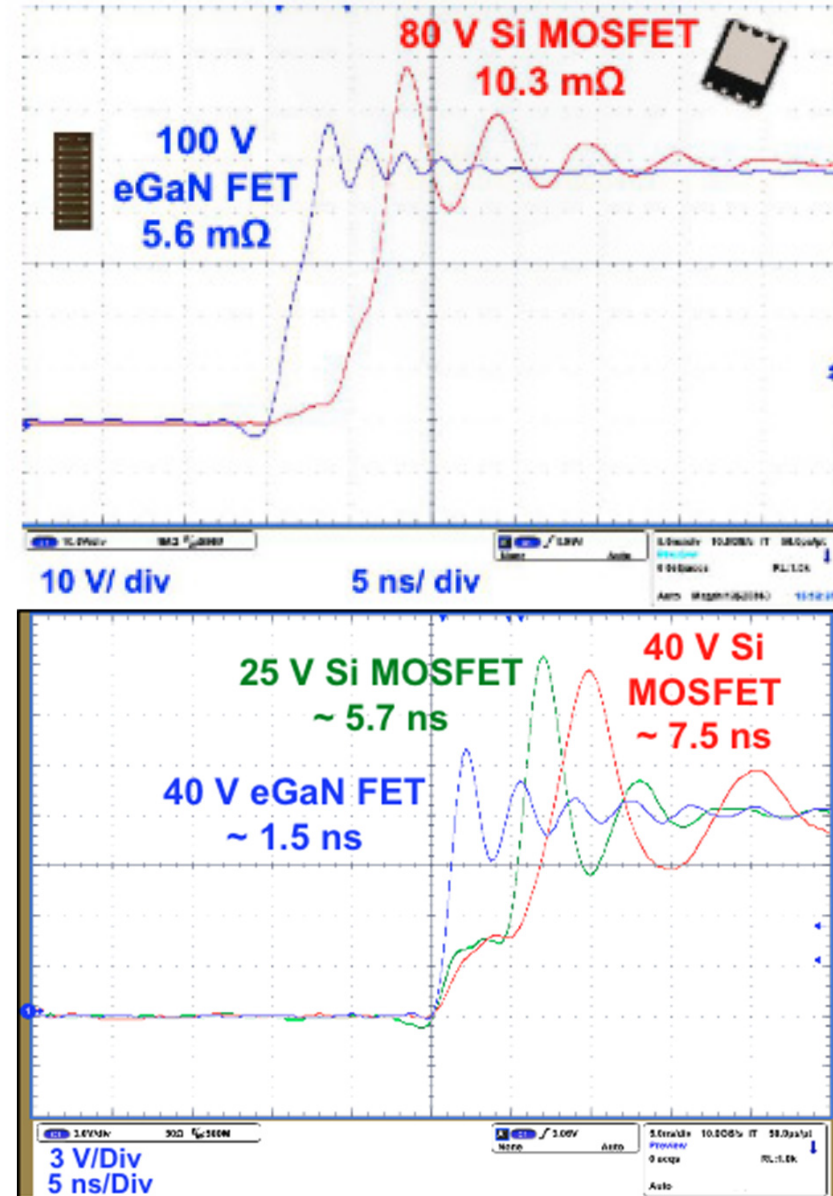






# Designing with GaN

- Because of high electric breakdown field and high electron velocity, GaN devices with comparable  $R_{on}$  can be significantly smaller and switch must faster.
- Need **very** good layout to prevent ringing from causing overvoltage and device failure.




# GaN Design Issues

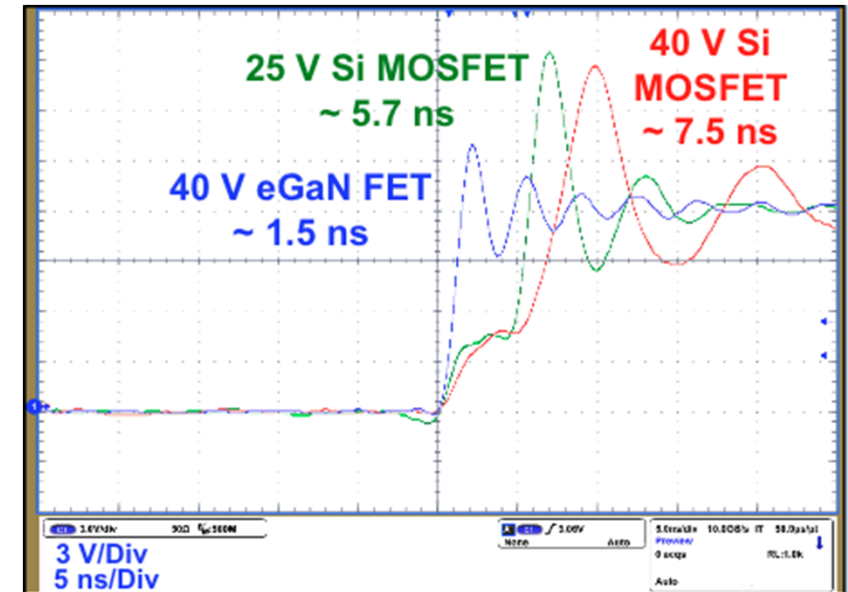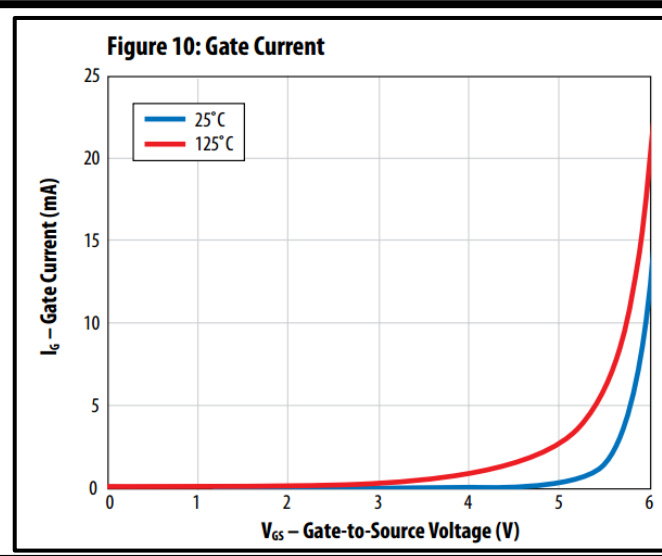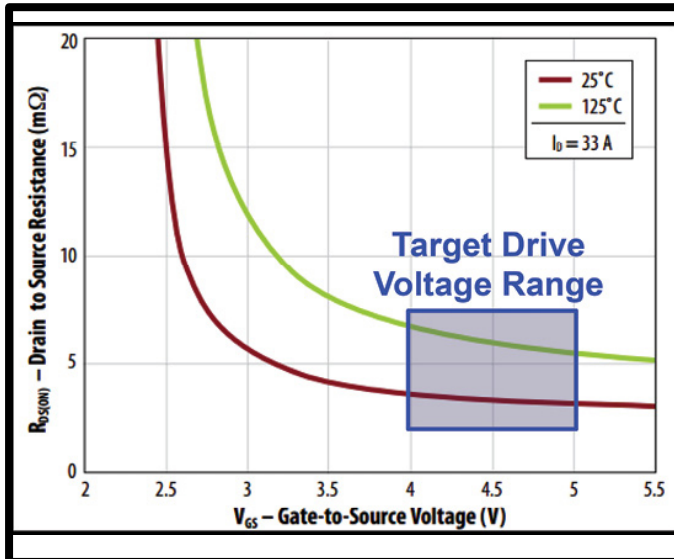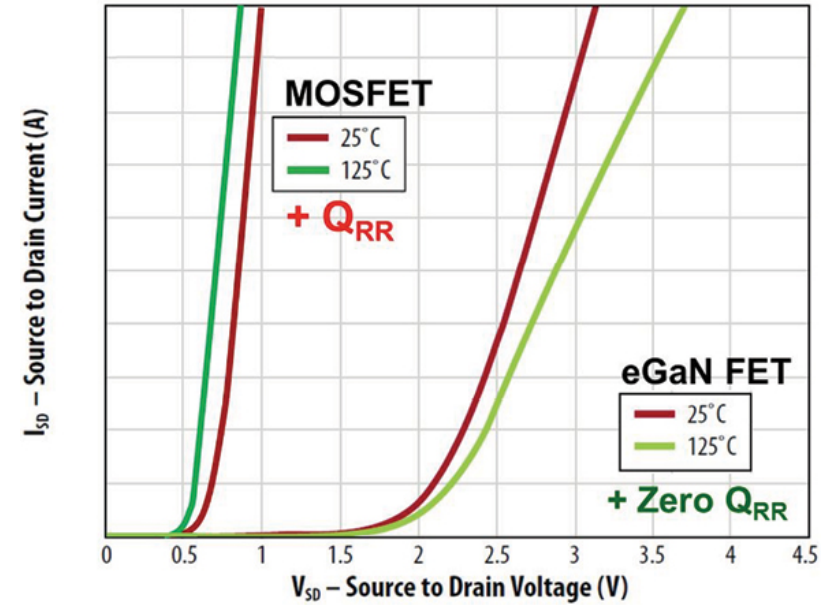1. Reverse conduction mechanism
2. Sensitivity to parasitics
3. Gate robustness
4. Small size -> Thermal limitations



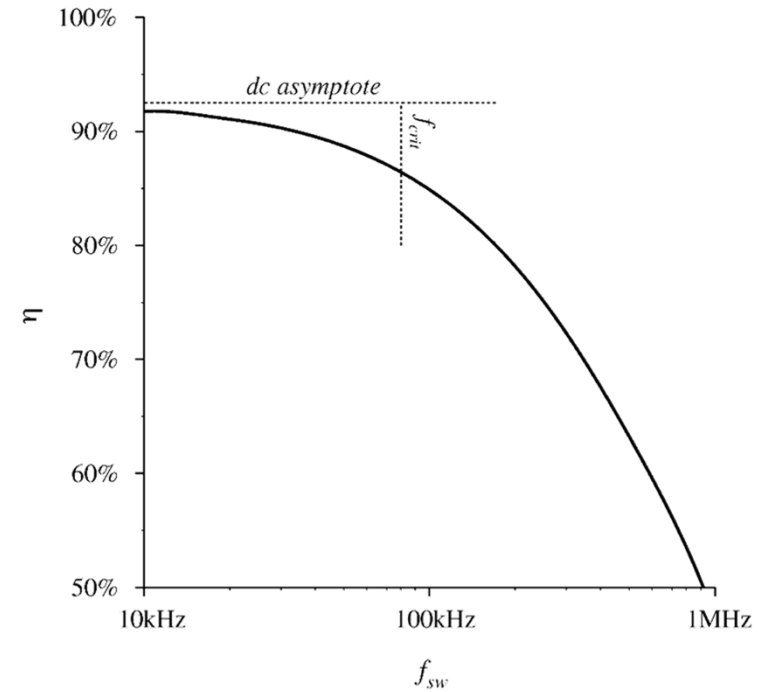
# Converter Efficiency Vs. $f_s$


$$P_{loss} = P_{cond} + P_{fixed} + W_{tot} f_{sw}$$



# Converter Optimization


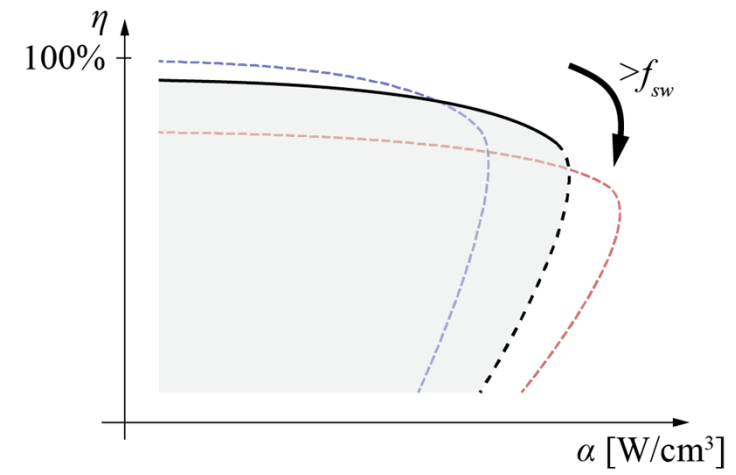


# Insulated Gate Bipolar Transistor

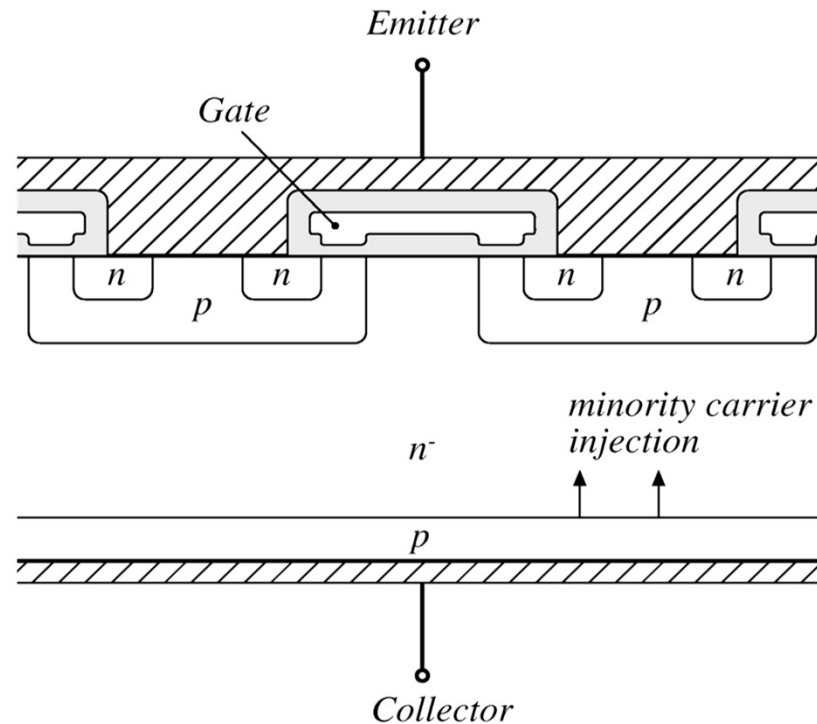


- A four-layer device
- Similar in construction to MOSFET, except extra  $p$  region
- On-state: minority carriers are injected into  $n$  region, leading to conductivity modulation
- compared with MOSFET: slower switching times, lower on-resistance, useful at higher voltages (up to 1700V)

# The IGBT

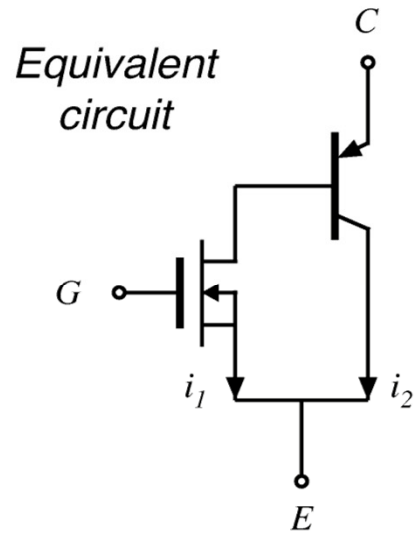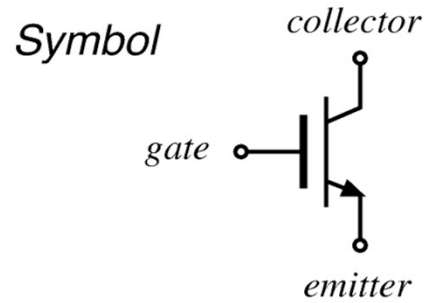

Fundamentals of Power Electronics



Location of equivalent devices

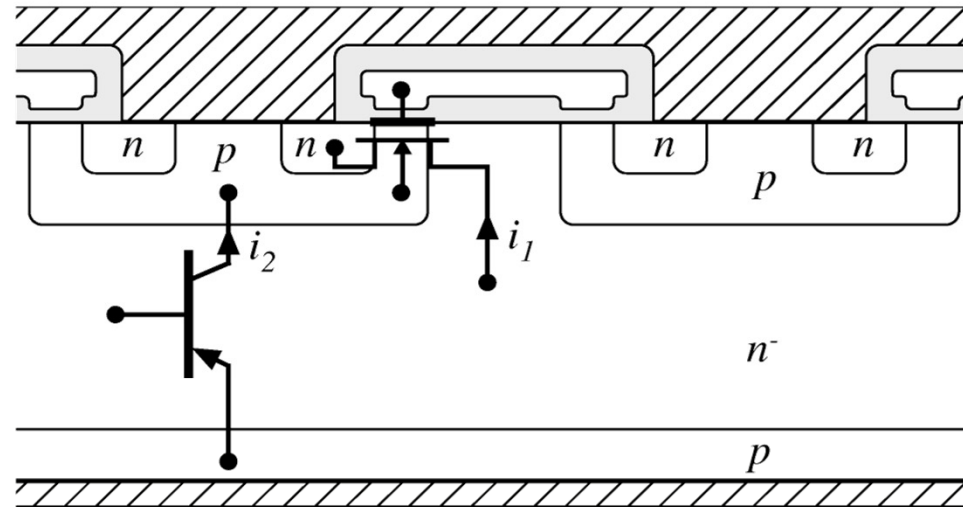

65

Chapter 4: Switch realization

# IGBT: Current Tailing

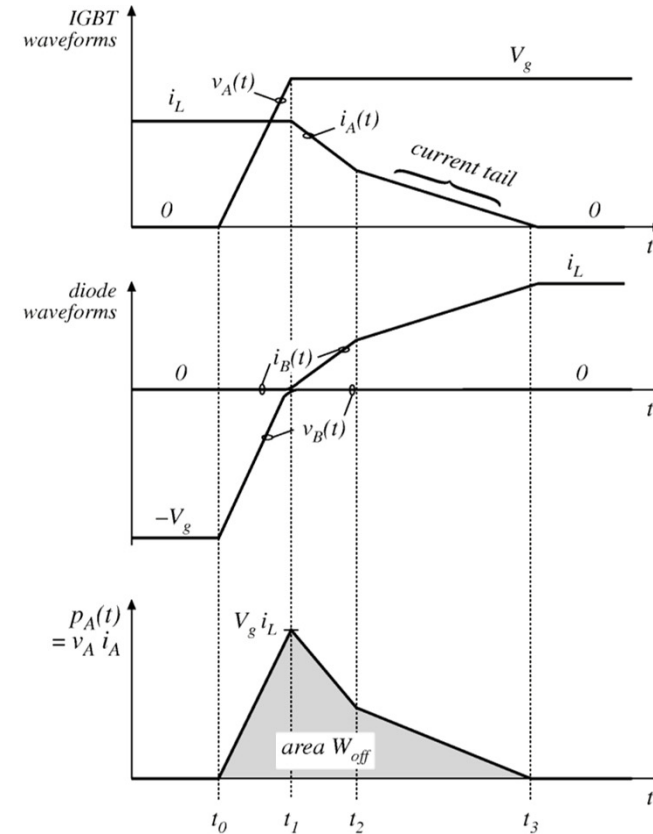
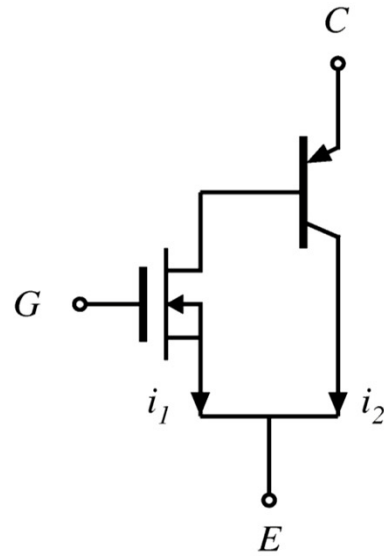


Chapter 5

# THE DISCONTINUOUS CONDUCTION MODE



# Buck Converter Example

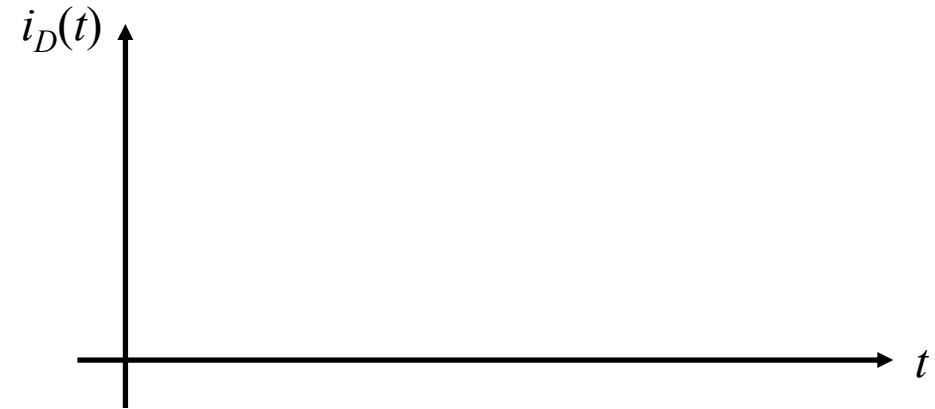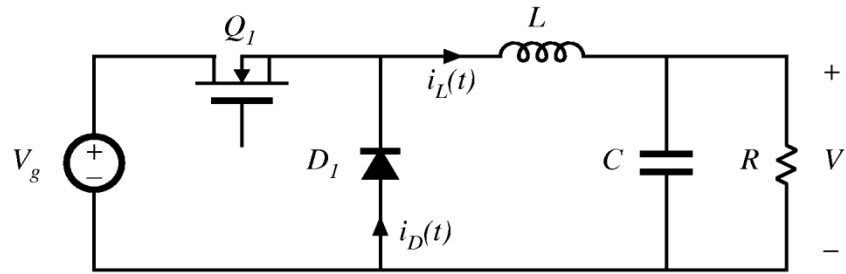

# DCM/CCM Modes of Operation