

DCM/CCM Modes of Operation

CCM → Continuous Conduction Mode

- every example so far
- which switches conduct is controlled entirely by PWM signals

DCM → Discontinuous Conduction Mode

- At least one uncontrolled switching action
- some element's ripple is large enough to invert a polarity of a switching device's v_{off} or I_{on} , \ddagger switch is unidirectional
- Most common → $\Delta i_L > I_L$ \ddagger some diode shuts off as a result

CRM/BCM/TCM → "Critical", "Boundary", "Triangular" conduction mode
CCM/DCM boundary
eg. $\Delta i_L = I_L$

K_{crit} and R_{crit}

For Buck Converter

DCM will occur if $\Delta i_L > I_L$

CCM when $\Delta i_L < I_L$
 $\frac{V_g - V}{2L} DT_s < \frac{V}{R}$

~~DT_s~~ ~~$\frac{V_g(1-D)}{2L}$~~ $<$ ~~$\frac{DV_g}{R}$~~

CCM when $D' < \frac{2L}{RT_s}$

$K_{crit}(D) < k = \frac{2L}{RT_s}$
 $= D'$ for Buck converter



$R < \frac{2L}{D'T_s}$
 \downarrow
 $R_{crit}(D)$

Small-Ripple Modifications in DCM


In DCM, by definition, some element has large ripple
- SRA must be dropped on that element, but can still be used elsewhere
e.g. in our DCM Buck $i_c(t) \neq I_L$ but $v(t) \approx V$

- Volt-second balance & cap charge balance still apply

$$\langle v_c \rangle = \frac{1}{T_s} \int_0^{T_s} v_c(t) dt = 0$$

$$\langle i_c \rangle = \frac{1}{T_s} \int_0^{T_s} i_c(t) dt = 0$$

Buck Converter in DCM

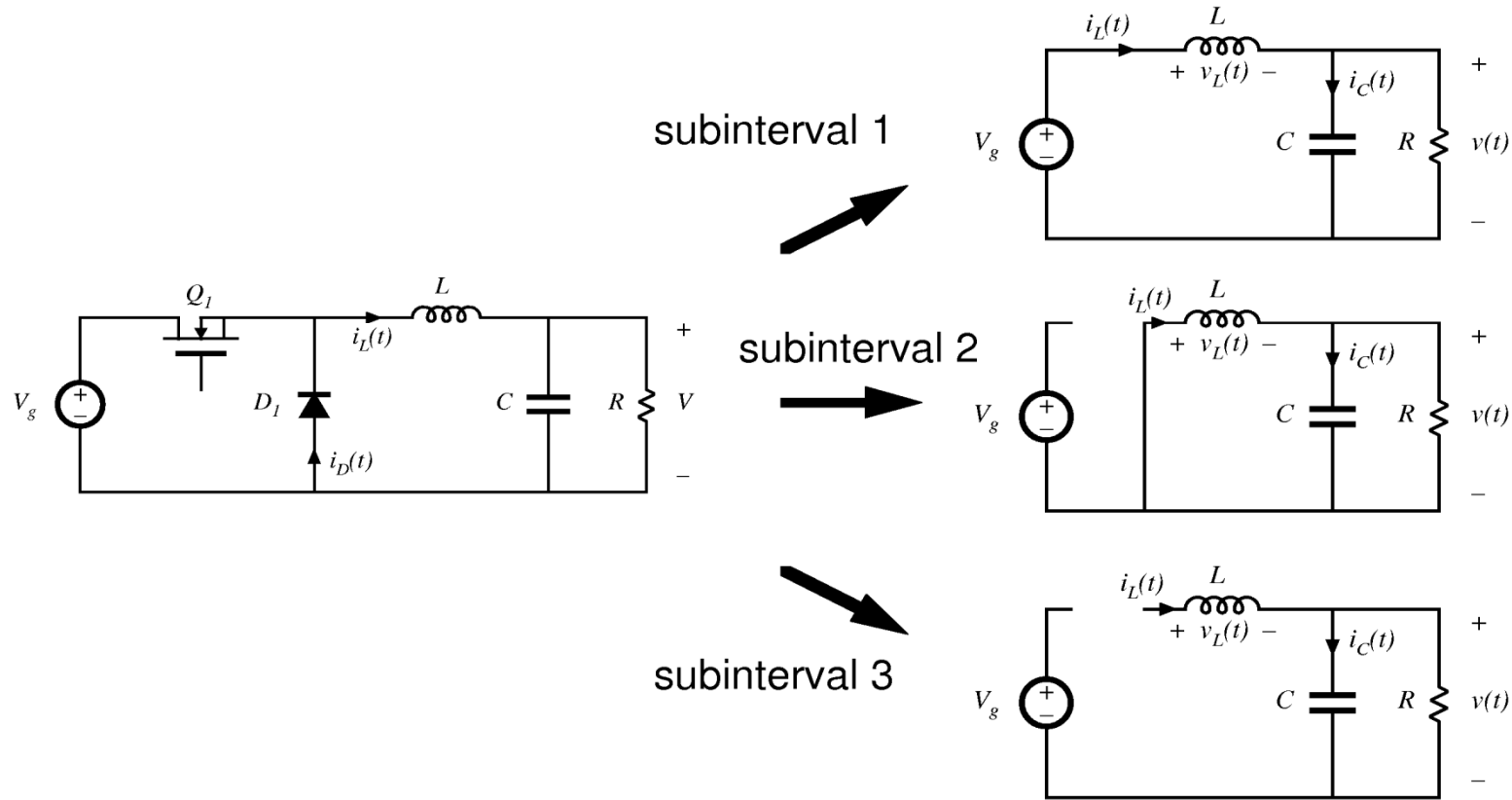

FET ON
 $D_1 T_s \rightarrow$ old
 $D_1 T_s$
 controlled by PWM
 signal

Diode ON

$D_2 T_s$
 time for $i_L(t) \rightarrow 0$

Nothing ON


$D_3 T_s = T_s - D_1 T_s - D_2 T_s$

Subinterval Analysis

$$v_L(t) = V_g - v(t) \xrightarrow{\text{SRA}} V_g - V$$

①

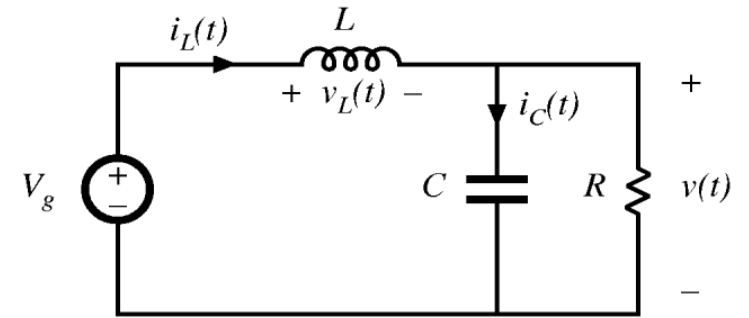
$$i_c(t) = i_L(t) - \frac{v(t)}{R} \xrightarrow[\text{on } v(t) \text{ only}]{\text{SRA}} i_L(t) - \frac{V}{R}$$



$$v_L(t) = 0 - v(t) \xrightarrow{\text{SRA}} -V$$

②
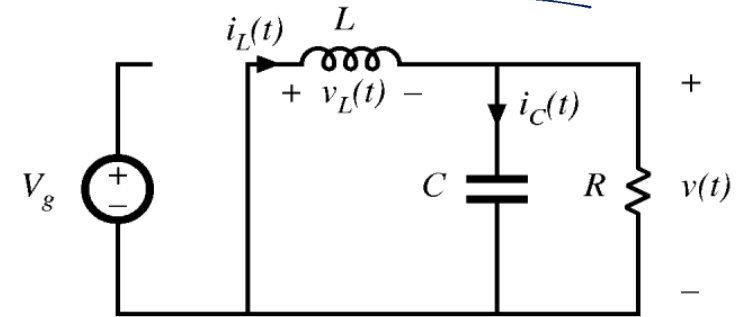
$$i_c(t) = i_L(t) - \frac{v(t)}{R} \xrightarrow{\text{SRA}^*} i_L(t) - \frac{V}{R}$$




$$v_L(t) = \phi$$

$i_c(t) = \phi$ in ③

③
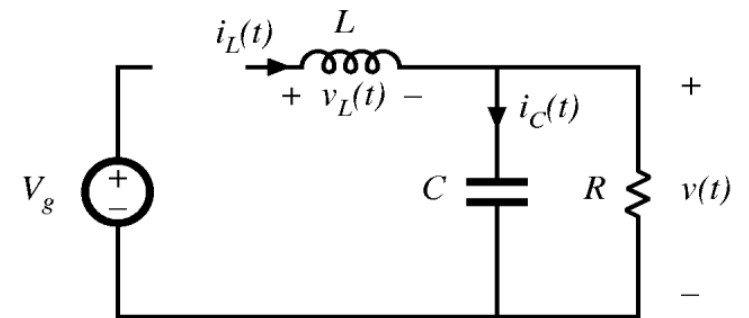
$$i_c(t) = i_L(t) - \frac{v(t)}{R} \xrightarrow{\text{SRA}^*} i_L(t) - \frac{V}{R} \rightarrow -\frac{V}{R}$$



Waveforms in DCM

Volt-sec Balance

$$\langle v_L \rangle = \phi = D_1(V_g - V) + D_2(-V) + D_3(\phi)$$

$$\phi = D_1 V_g - V(D_1 + D_2)$$

$$V = V_g \frac{D_1}{D_1 + D_2}$$

Cap-Charge Balance

$$\langle i_C \rangle = \phi = \frac{1}{T_s} \int_0^{T_s} i_C(t) dt = \frac{1}{T_s} \int_0^{T_s} \left(i_L(t) - \frac{V}{R} \right) dt$$


$$\phi = \frac{1}{T_s} \int_0^{T_s} i_L(t) dt - \frac{V}{R}$$

$$I_{L, \text{pk}} = \frac{V_g - V}{L} D_1 T_s$$

$$\phi = \frac{1}{T_s} \left[\frac{1}{2} (D_1 + D_2) T_s I_{L, \text{pk}} \right] - \frac{V}{R}$$

$$\phi = \frac{1}{T_s} \left[\frac{1}{2} (D_1 + D_2) \frac{V_g - V}{L} D_1 T_s \right] - \frac{V}{R}$$
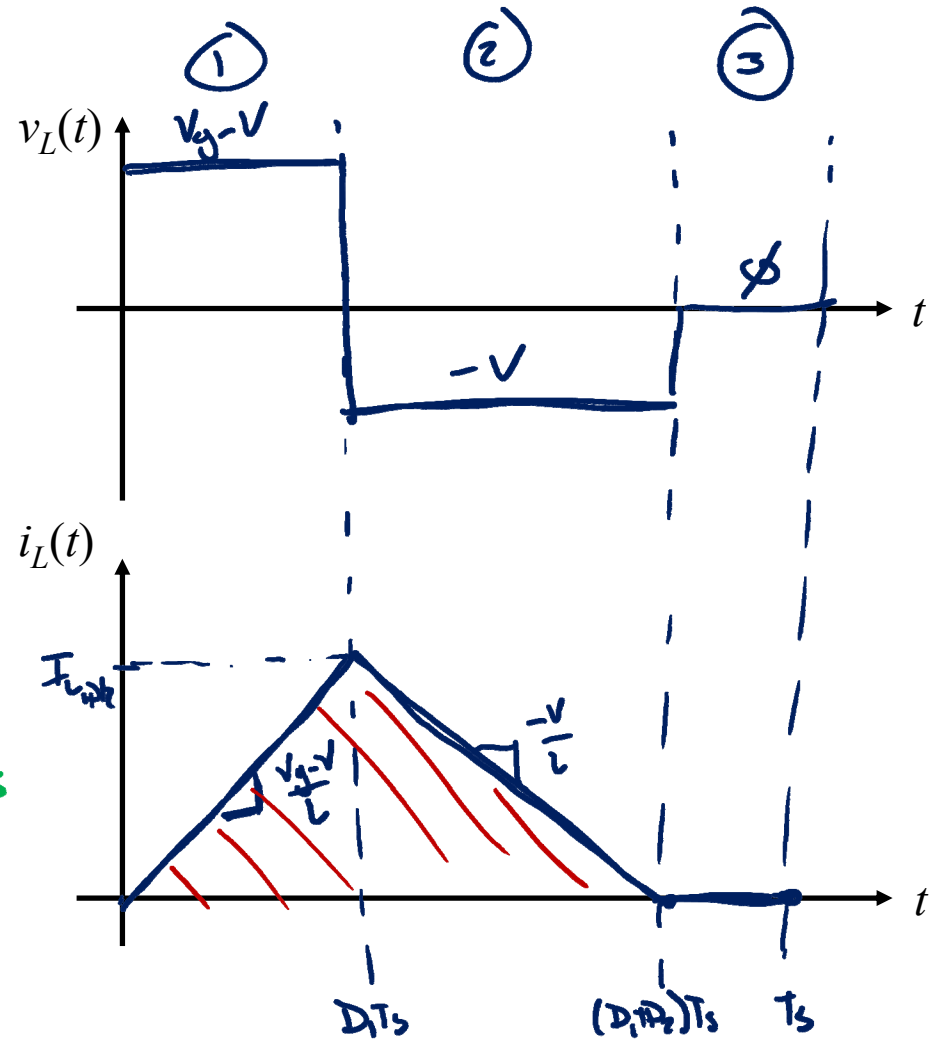
$$\frac{V}{R} = D_1 \frac{T_s}{2L} (D_1 + D_2) (V_g - V)$$



$$v = v_g \frac{D_1}{D_1 + D_2}$$

$$v(D_1 + D_2) = v_g D_1$$

$$D_2 = \frac{v_g}{v} D_1 - D_1$$

$$v = D_1 \frac{RT_s}{2L} (D_1 + D_2) (v_g - v)$$

$$v = \frac{D_1}{k} \left(\cancel{D_1} + \frac{v_g}{v} D_1 - \cancel{D_1} \right) (v_g - v)$$

$$v = \frac{D_1^2}{k} \left(\frac{v_g^2}{v} - v_g \right)$$

$$\frac{k}{D_1^2} = v_g^2 \frac{1}{v^2} - v_g \frac{1}{v}$$

$$0 = v_g^2 \left(\frac{1}{v} \right)^2 - v_g \left(\frac{1}{v} \right) - \frac{k}{D_1^2}$$

→

$$\frac{1}{v} = \frac{v_g \pm \sqrt{v_g^2 - 4 v_g^2 \left(-\frac{k}{D_1^2} \right)}}{2 v_g^2}$$

Recall: $k = \frac{2L}{RT_s}$

Solving $M(D,K)$

$$\frac{1}{v} = \frac{v}{g} \frac{1 \pm \sqrt{1 + 4 \frac{K}{D^2}}}{2}$$

$$M(D,K) = \frac{v}{g} = \frac{2}{1 \pm \sqrt{1 + 4 \frac{K}{D^2}}}$$

$$K = \frac{2L}{RT_S}$$