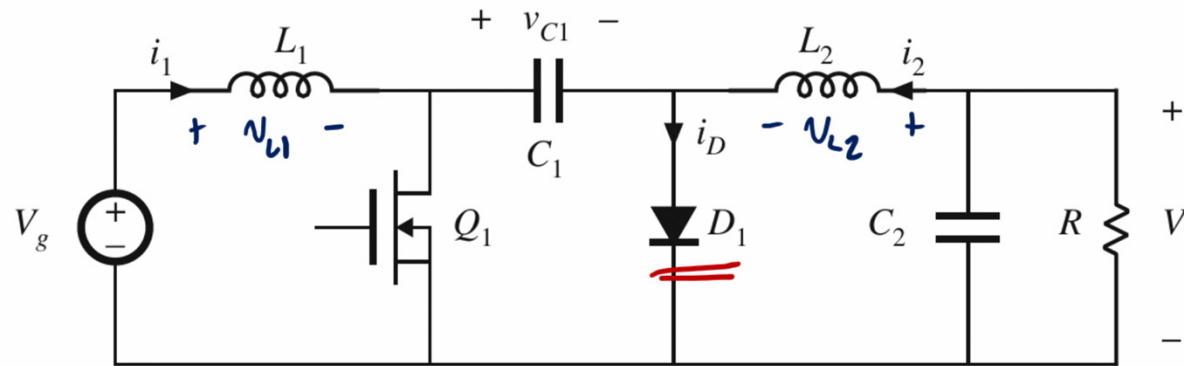


Cuk Converter in CCM



Recall CCM:

$$\langle v_{L1} \rangle = \phi = V_g - D'v_{C1} \rightarrow v_{C1} = \frac{V_g}{D'}$$

$$\langle v_{L2} \rangle = \phi = Dv_{C1} + V \rightarrow v_{C1} = -\frac{V}{D}$$

$$\langle i_{L1} \rangle = \phi = D(-I_2) + D'I_1 \rightarrow I_1 = \frac{D}{D'}I_2$$

$$\langle i_{L2} \rangle = \phi = -I_2 - \frac{V}{R} \rightarrow I_2 = -\frac{V}{R}$$

$$v = V_g \left(\frac{-D}{D'} \right), m = \frac{V}{V_g} = -\frac{D}{D'}$$

when diode is on, $i_D = I_1 + I_2$

CCM when $I_1 + I_2 > \Delta i_{L1} + \Delta i_{L2}$

$$\Delta i_{L1} = \frac{1}{2} \frac{V_g}{L_1} DT_s$$

$$\Delta i_{L2} = \frac{1}{2} \left(\frac{-V}{L_2} \right) D'T_s$$

Cuk Converter DCM Boundary

$$I_1 + I_2 = \left(\frac{-V}{R} \right) \left(1 + \frac{D}{D'} \right) \rightarrow \Delta i_{L1} + \Delta i_{L2} = \frac{I_s}{2} \left(\frac{V_g}{L_1} D + \frac{-V}{L_2} D' \right)$$

$$\cancel{\frac{V}{R} \frac{D}{D'}} \left(1 + \frac{D}{D'} \right) \rightarrow \frac{I_s}{2} \left(\cancel{\frac{DV_g}{L_1}} + \cancel{\frac{-VD}{L_2} D'} \right)$$

$$\frac{1}{R D'} \left(\frac{1}{D'} \right) \rightarrow \frac{I_s}{2} \left(\frac{1}{L_1} + \frac{1}{L_2} \right)$$

$$\frac{2 \frac{1}{L_1} + \frac{1}{L_2}}{R I_s} \rightarrow (D')^2$$

$$\frac{1}{L_1} + \frac{1}{L_2} = L_{eq} = L_1 \parallel L_2$$

$$K = \left[\frac{2 L_{eq}}{R I_s} \rightarrow (D')^2 \right] = k_{crit}(D)$$

Cuk Converter in DCM

①

$$v_{L1} = V_g$$

$$v_{L2} = v(t) + v_{C1}(t) \\ \downarrow \\ v + v_{C1}$$

$$i_{C1} = -i_2(t)$$

$$i_{C2} = -i_2(t) - \frac{v(t)}{R}$$

$$i_{C2} = -i_2(t) - \frac{v}{R}$$

②

$$v_{L1} = V_g - v_{C1}$$

$$v_{L2} = V$$

$$\dot{v}_{C1} = \dot{i}_1(t)$$

$$\dot{i}_{C2} = -\dot{i}_2(t) - \frac{\dot{v}}{R}$$

③




$$v_{L1} = \phi$$

$$v_{L2} = \phi$$


$$v_{C1} = V_g - V$$

$$i_{C1} = i_1 = -i_2 = I_x$$

$$i_{C2} = -i_2(t) - \frac{v}{R}$$

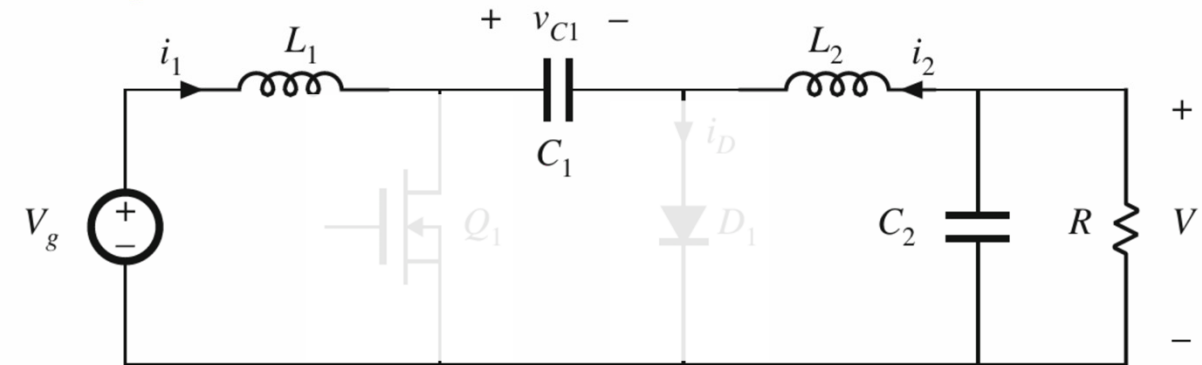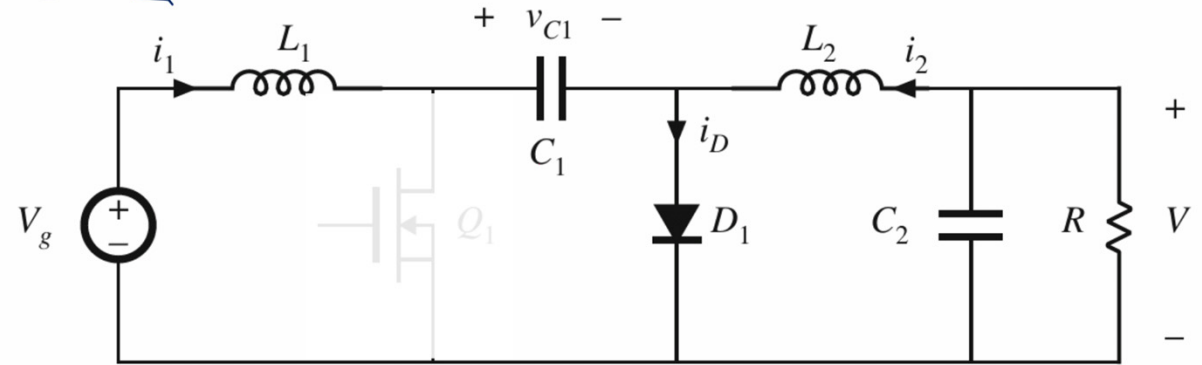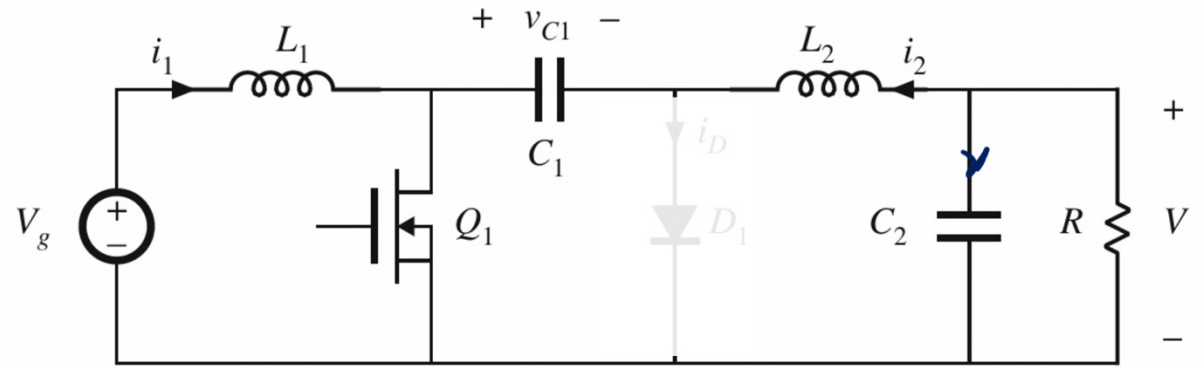

Cuk Waveforms in DCM

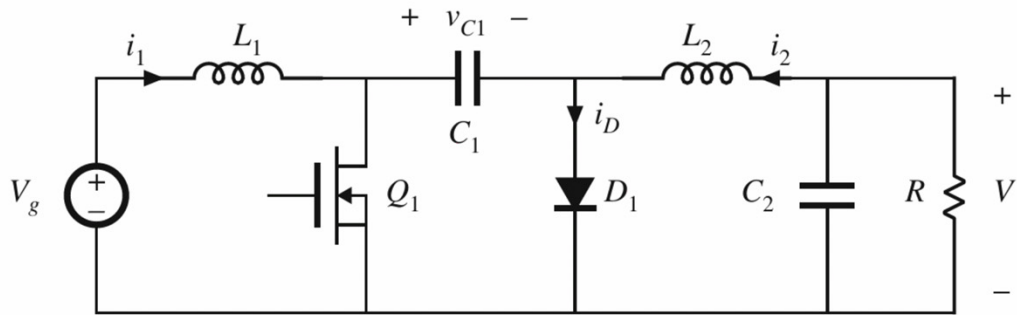

$$\langle v_{C1} \rangle = \phi = D_1 V_g + D_2 (V_g - v_{C1})$$


$$\phi = (D_1 + D_2) V_g - D_2 v_{C1}$$

$$v_{C1} = V_g \frac{D_1 + D_2}{D_2}$$

$$\langle v_{C2} \rangle = \phi = V (D_1 + D_2) + v_{C1} (D_1)$$

$$v_{C1} = -V \frac{D_1 + D_2}{D_1}$$
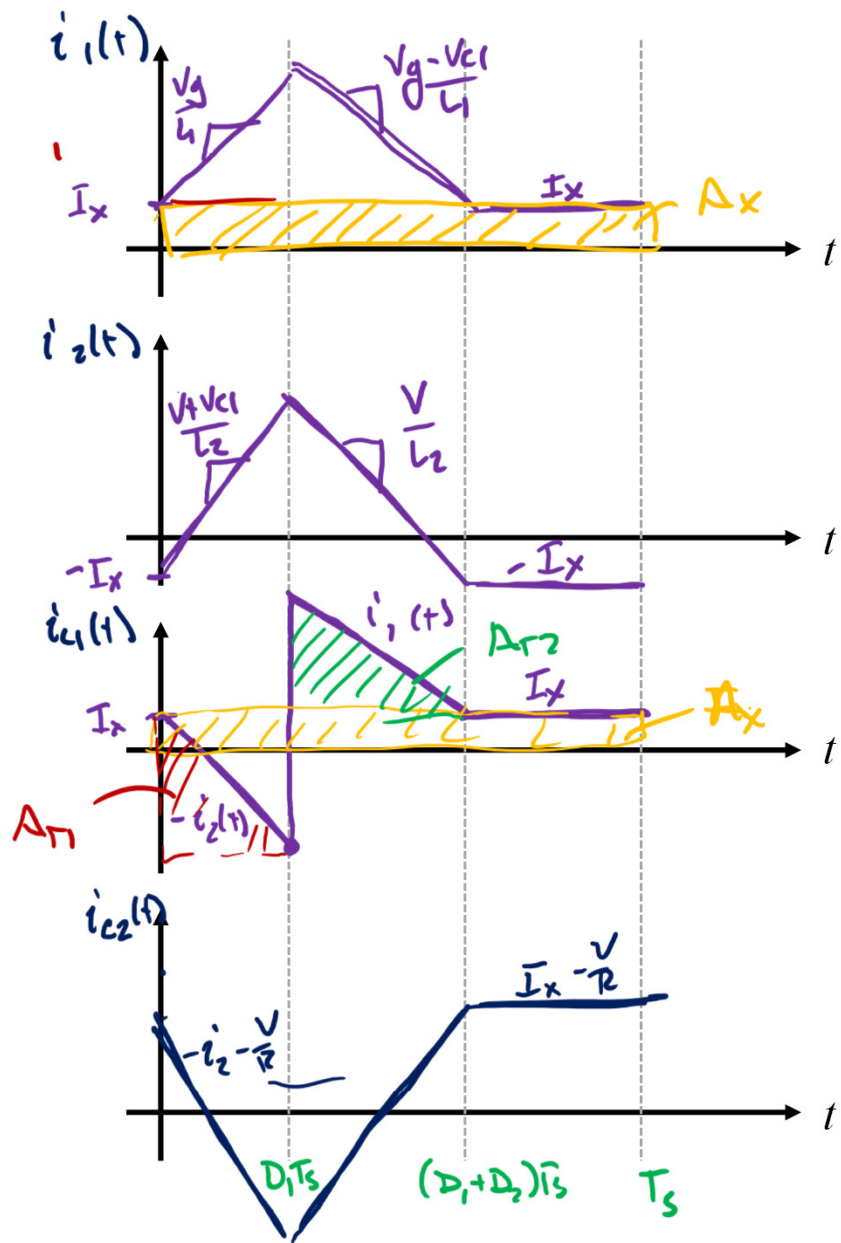
$$V = -V_g \frac{D_1}{D_2} \rightarrow D_2 = -\frac{V}{V_g} D_1$$



Cuk Conversion Ratio

$$\langle i_a \rangle = \phi = \frac{1}{T_s} \int_0^{T_s} i_a(t) dt = \frac{1}{T_s} [A_{T1} + A_{T2} + A_x]$$

$$\phi = \frac{1}{T_s} \left[\frac{1}{2} D_1 T_s \frac{V}{L_2} D_2 T_s + \frac{1}{2} D_2 T_s \frac{V_g}{L_1} D_1 T_s + I_x T_s \right]$$

$$-I_x = \frac{1}{2} D_1 D_2 T_s \left(\frac{V}{L_2} + \frac{V_g}{L_1} \right)$$

$$\langle i_{e2} \rangle = \phi = \frac{1}{T_s} \int_0^{T_s} i_{e2}(t) dt = \frac{1}{T_s} \int_0^{T_s} \left[-i_2 - \frac{V}{R} \right] dt = -\frac{1}{T_s} \int_0^{T_s} i_2 dt - \frac{V}{R}$$

$$\phi = -\frac{1}{T_s} \left[\frac{1}{2} (D_1 + D_2) T_s \frac{V}{L_2} D_2 T_s - I_x T_s \right] - \frac{V}{R}$$

$$\phi = -\frac{1}{T_s} \left[\frac{1}{2} (D_1 + D_2) T_s \frac{V}{L_2} D_2 T_s + T_s \frac{1}{2} D_1 D_2 T_s \left(\frac{V}{L_2} + \frac{V_g}{L_1} \right) \right] - \frac{V}{R}$$