

Cuk DCM M(D,K)

$$D_2 = \frac{-V_g}{V} D_1$$

$$D_2 = \frac{-V_g}{V} D_1 + \frac{1}{2} T_s^2 D_1 D_2 \left(\frac{V}{L_2} + \frac{V_g}{L_1} \right) - \frac{V}{R}$$

$$\phi = -\frac{1}{T_s} \left[\frac{1}{2} (D_1 + D_2) T_s^2 \left(\frac{-V}{L_2} \right) D_2 + \frac{1}{2} T_s^2 D_1 D_2 \left(\frac{V}{L_2} + \frac{V_g}{L_1} \right) \right] - \frac{V}{R}$$

$$\frac{2}{T_s} \frac{V}{R} = \left[(D_1 - D_1 \frac{V_g}{V}) \left(\frac{V}{L_2} \right) \left(\frac{-V_g}{V} D_1 \right) - D_1 D_1 \left(\frac{-V_g}{V} \right) \left(\frac{V}{L_2} + \frac{V_g}{L_1} \right) \right]$$

$$\frac{2}{RT_s} V = D_1^2 \frac{V_g}{V} \left[\left(1 - \frac{V_g}{V} \right) \frac{V}{L_2} + \frac{V}{L_2} + \frac{V_g}{L_1} \right]$$

$$\frac{2}{RT_s} V = D_1^2 \frac{V_g}{V} \left[-\frac{V}{L_2} + \frac{V_g}{L_1} + \cancel{\frac{V}{L_2}} + \frac{V_g}{L_1} \right]$$


$$\frac{V^2}{Vg^2} = D_1^2 \frac{RT_s}{2} \left[\frac{1}{L_2} + \frac{1}{L_1} \right]$$

$$M^2 = D_1^2 \frac{RT_s}{2 \text{Leg}} \rightarrow$$

$$\text{Leg} = L_1 || L_2 = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}}$$

$$M^2 = \frac{D_1^2}{K} \rightarrow$$
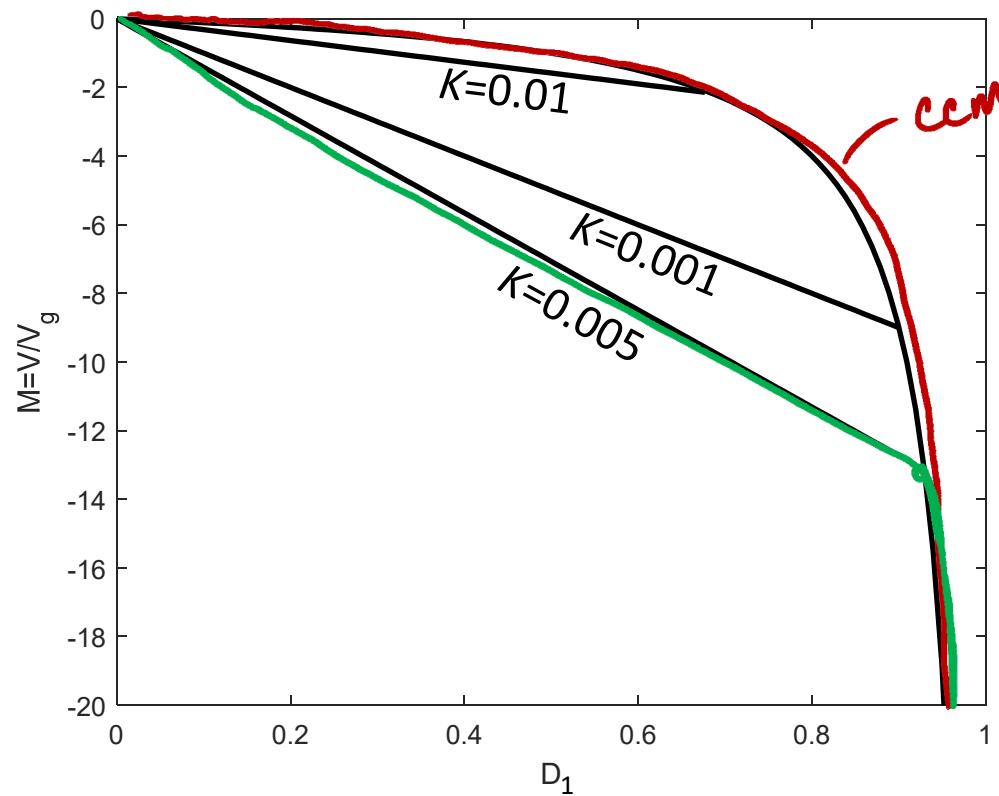
$$M_{\text{out}} = -\frac{D_1}{\sqrt{K}}$$



Summary of DCM Characteristics

Table 5.2. Summary of CCM-DCM characteristics for the buck, boost, and buck-boost converters

Converter	$K_{crit}(D)$	$DCM\ M(D,K)$	$DCM\ D_2(D,K)$	$CCM\ M(D)$
Buck	$(1 - D)$	$\frac{2}{1 + \sqrt{1 + 4K / D^2}}$	$\frac{K}{D} M(D,K)$	D
Boost	$D (1 - D)^2$	$\frac{1 + \sqrt{1 + 4D^2 / K}}{2}$	$\frac{K}{D} M(D,K)$	$\frac{1}{1 - D}$
Buck-boost	$(1 - D)^2$	$-\frac{D}{\sqrt{K}}$	\sqrt{K}	$-\frac{D}{1 - D}$

with $K = 2L / RT_s$. DCM occurs for $K < K_{crit}$.

Chapter 6

CONVERTER TOPOLOGIES

6.2 - A Short List of Converters

An infinite number of converters are possible, which contain switches embedded in a network of inductors and capacitors

Two simple classes of converters are listed here:

- Single-input single-output converters containing a single inductor. The switching period is divided into two subintervals. This class contains eight converters.
- Single-input single-output converters containing two inductors. The switching period is divided into two subintervals. Several of the more interesting members of this class are listed.

Single Input/Output/Inductor Converters

- Use switches to connect inductor between source and load, in one manner during first subinterval and in another during second subinterval
- There are a limited number of ways to do this, so all possible combinations can be found
- After elimination of degenerate and redundant cases, eight converters are found:

dc-dc converters

buck boost buck-boost noninverting buck-boost

dc-ac converters


bridge Watkins-Johnson

ac-dc converters


current-fed bridge inverse of Watkins-Johnson

Unipolar Output Converters


1. Buck

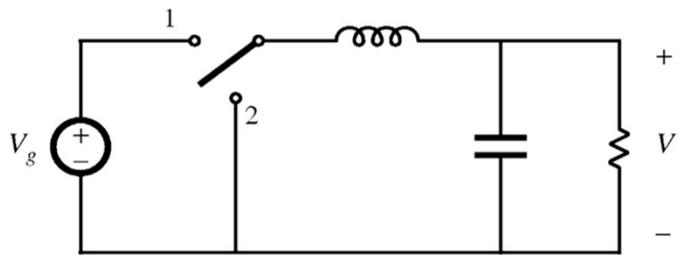


$$M(D) = D$$

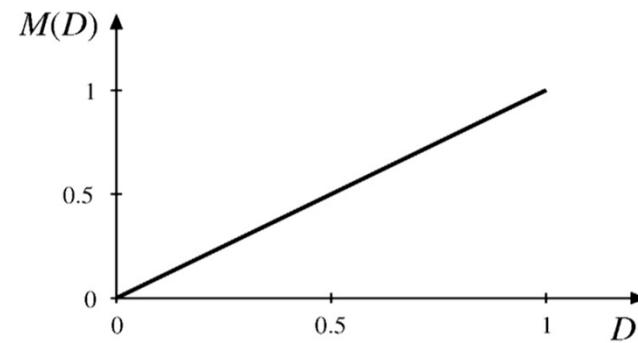

2. Boost

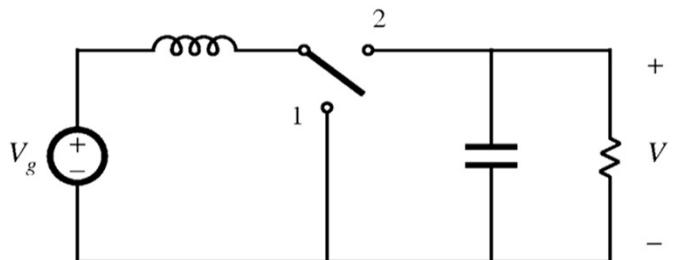


$$M(D) = \frac{1}{1 - D}$$

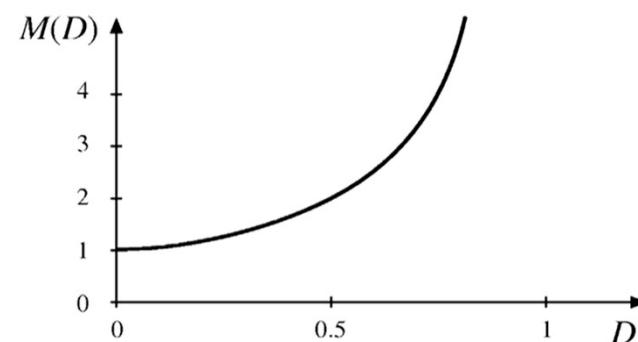


Unipolar Output Converters (cont.)


3. Buck-boost

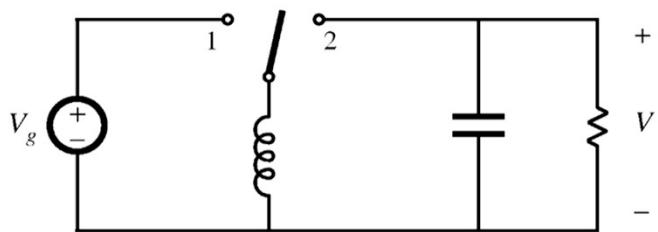


$$M(D) = -\frac{D}{1-D}$$

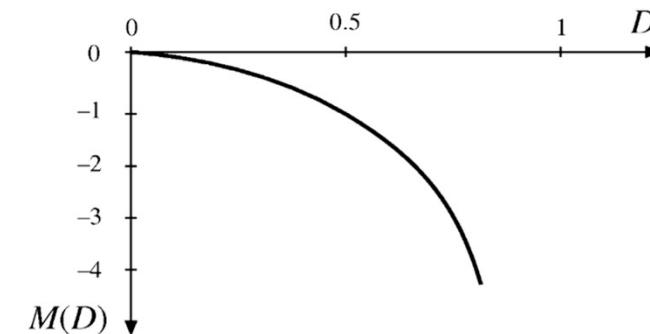

4. Noninverting buck-boost

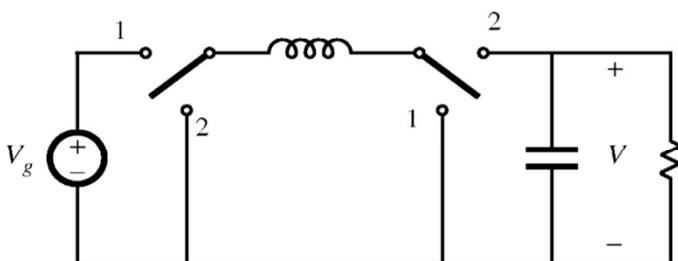


$$M(D) = \frac{D}{1-D}$$

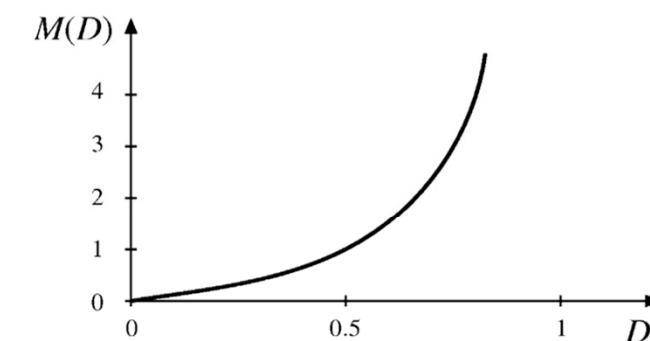


Bipolar Output Converters


5. Bridge

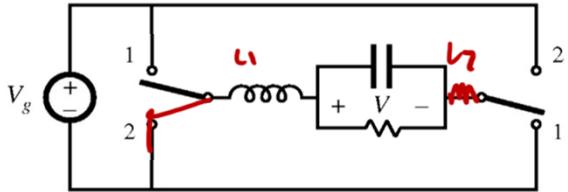


$$M(D) = 2D - 1$$

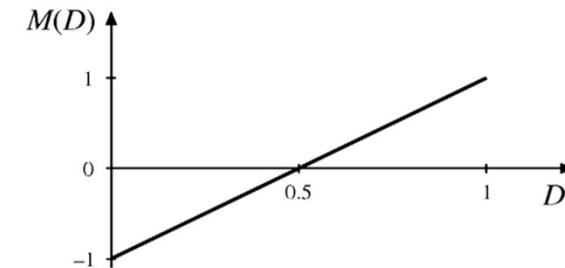

6. Watkins-Johnson

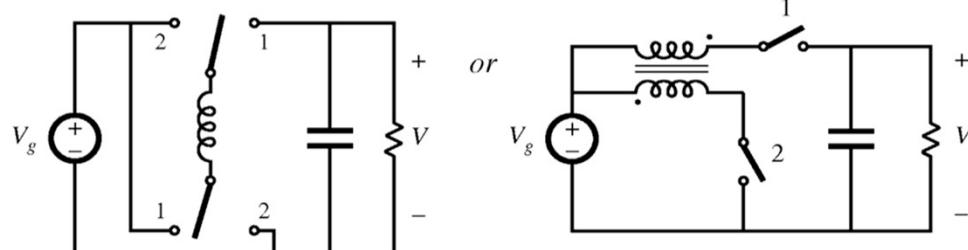



$$M(D) = \frac{2D-1}{D}$$

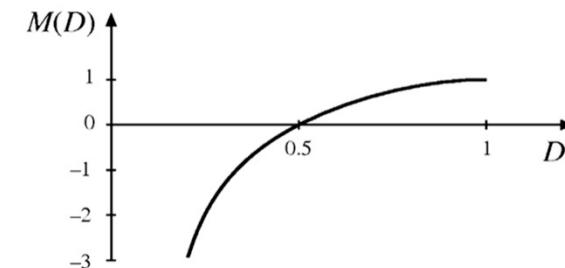

Bipolar Output Converters (cont.)



7. Current-fed bridge

$$M(D) = \frac{1}{2D - 1}$$

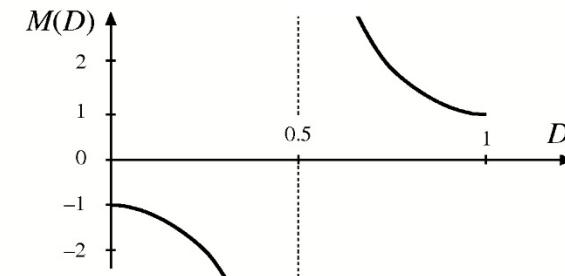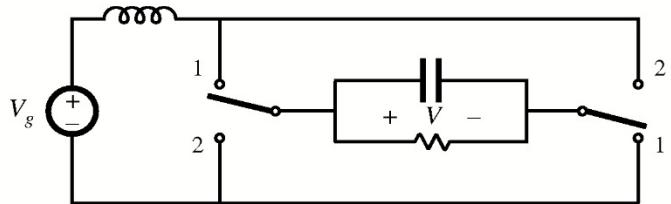

8. Inverse of Watkins-Johnson



$$M(D) = \frac{D}{2D - 1}$$

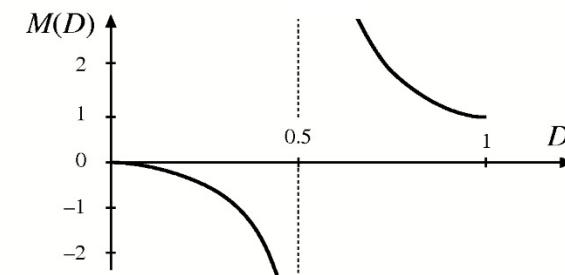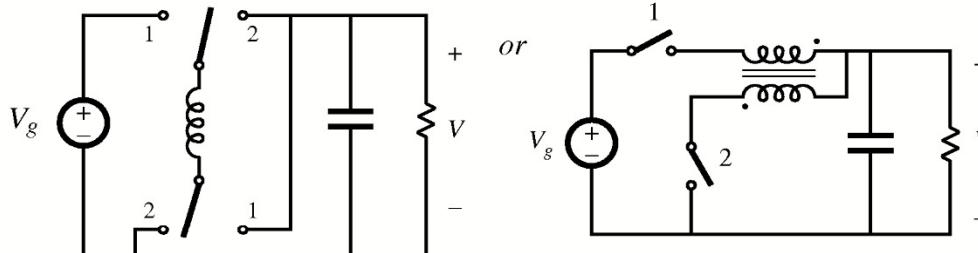

Example Two-Inductor Converters



1. *Cuk*

$$M(D) = -\frac{D}{1-D}$$

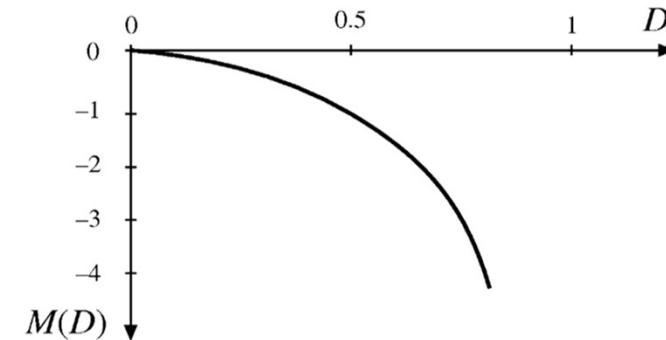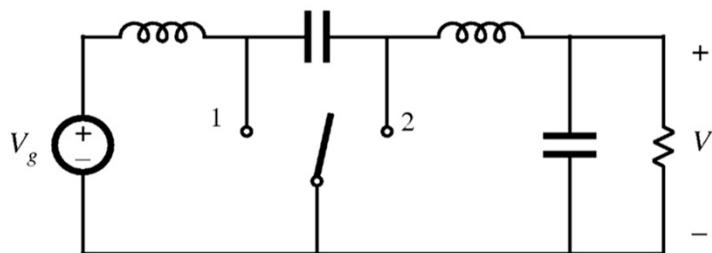


2. *SEPIC*

$$M(D) = \frac{D}{1-D}$$

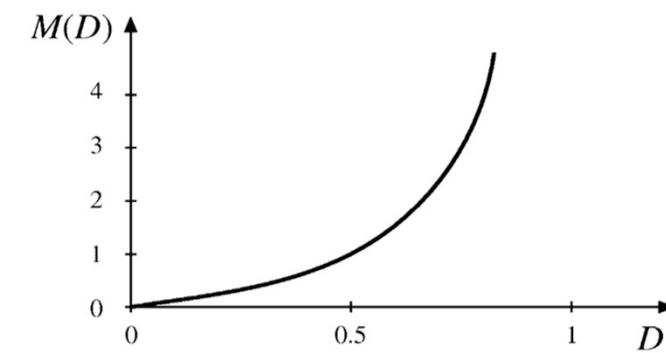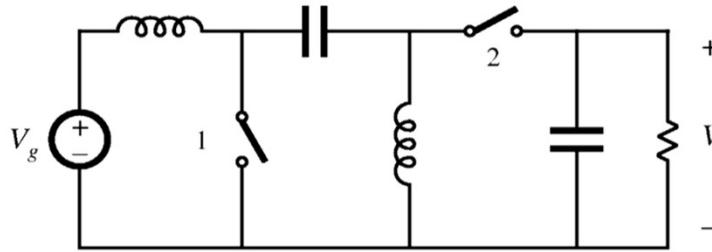


Example Two-Inductor Converters (cont.)

3. Inverse of SEPIC

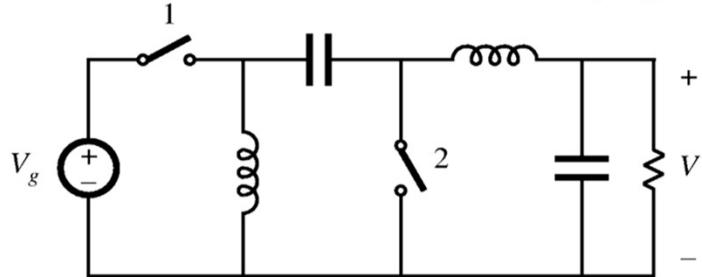


$$M(D) = \frac{D}{1-D}$$

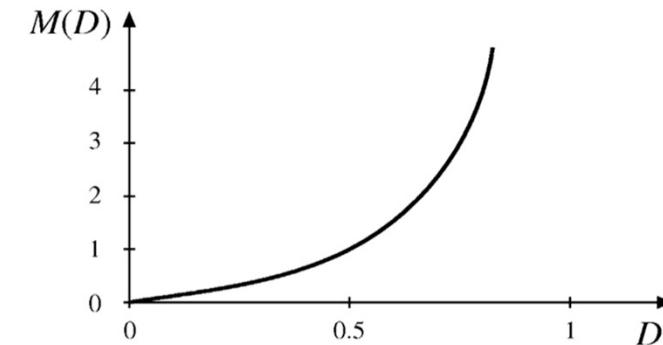


4. Buck²

"Maksimovic"

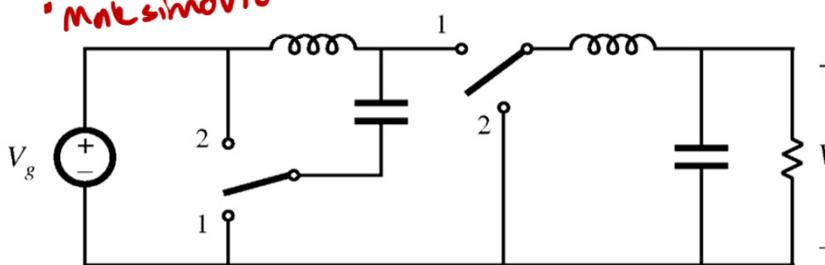


$$M(D) = D^2$$

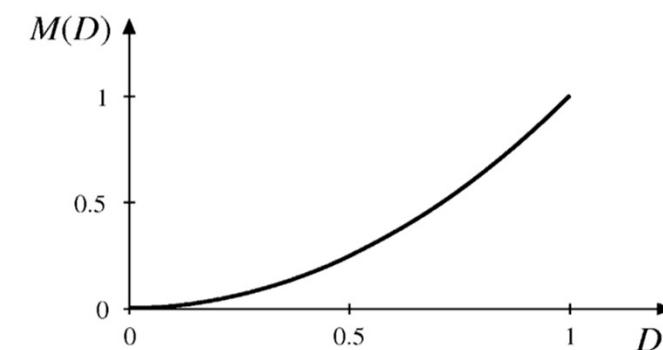

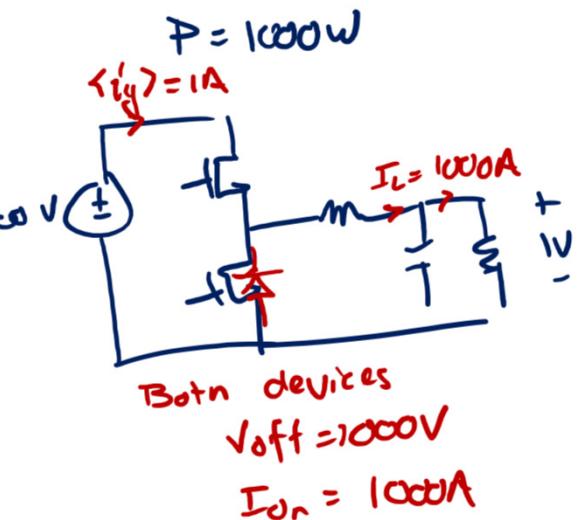
6.3 - Transformer Isolation

Objectives:

- Isolation of input and output ground connections, to meet safety requirements
- Reduction of transformer size by incorporating high frequency isolation transformer inside converter
- Minimization of current and voltage stresses when a large step-up or step-down conversion ratio is needed
—use transformer turns ratio
- Obtain multiple output voltages via multiple transformer secondary windings and multiple converter secondary circuits



Ideal Transformer Model

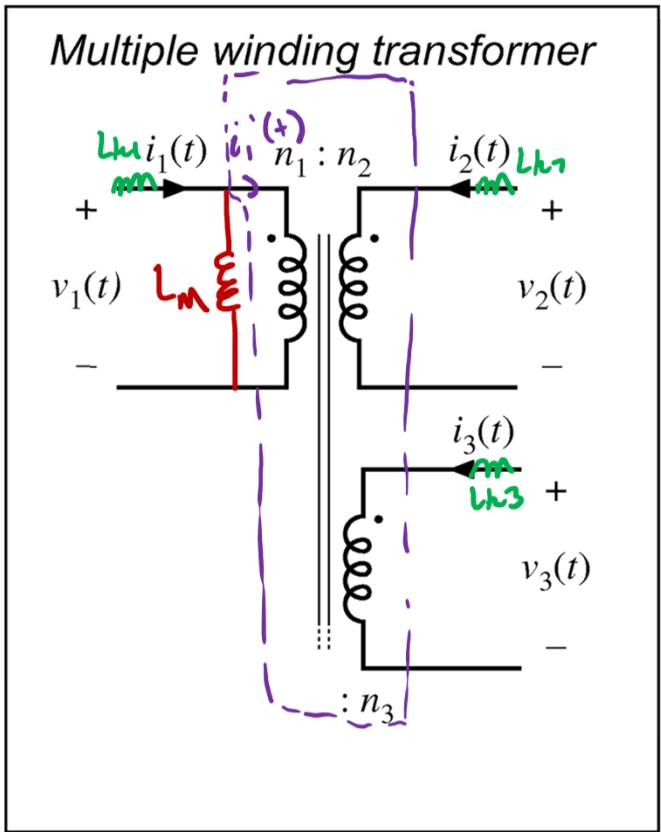

$$\frac{v_1(t)}{n_1} = \frac{v_2(t)}{n_2} = \frac{v_3(t)}{n_3} = \dots$$

$$0 = \underline{n_1 i_1'(t)} + n_2 i_2(t) + n_3 i_3(t) + \dots$$

$L_{hi} \rightarrow$ leakage inductance

$L_m \rightarrow$ magnetizing inductance

Ideal
 $L_{hi} \rightarrow 0$
 $L_m \rightarrow \infty$

$k_{ij} \rightarrow 1$
 $\Rightarrow L_m$ very large


Core is unsaturated

Cannot apply DC to any XF winding

Transformer Saturation

$$L_M = \frac{\mu N_i^2 A_c}{l_m}$$

$$B = \mu H$$

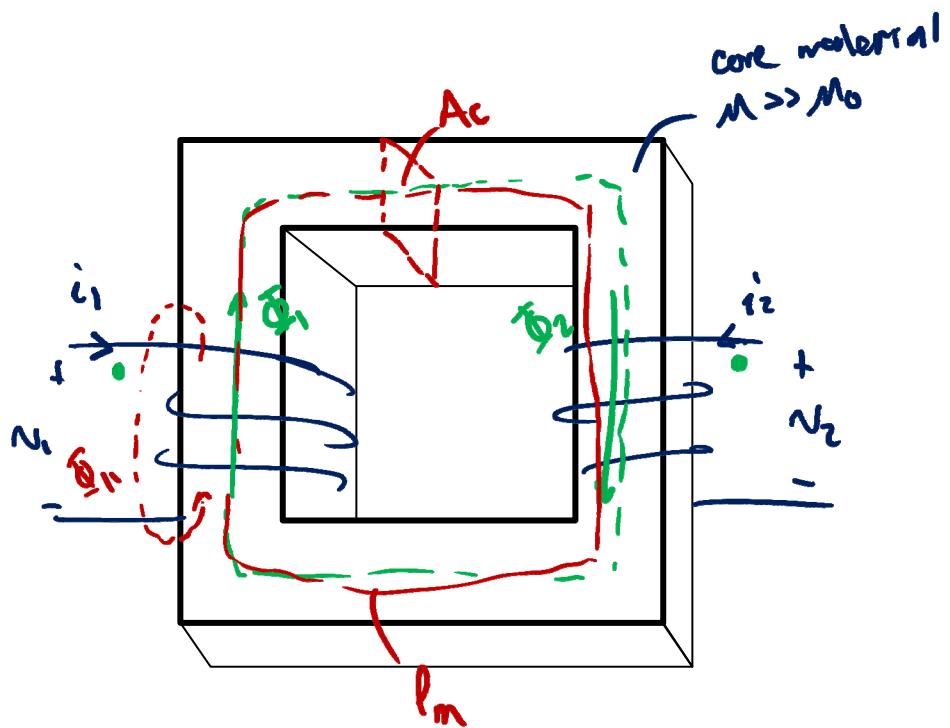

Transformer core B - H characteristic

