

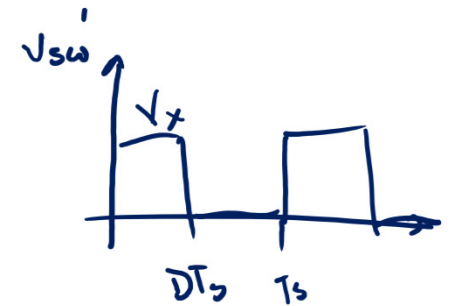
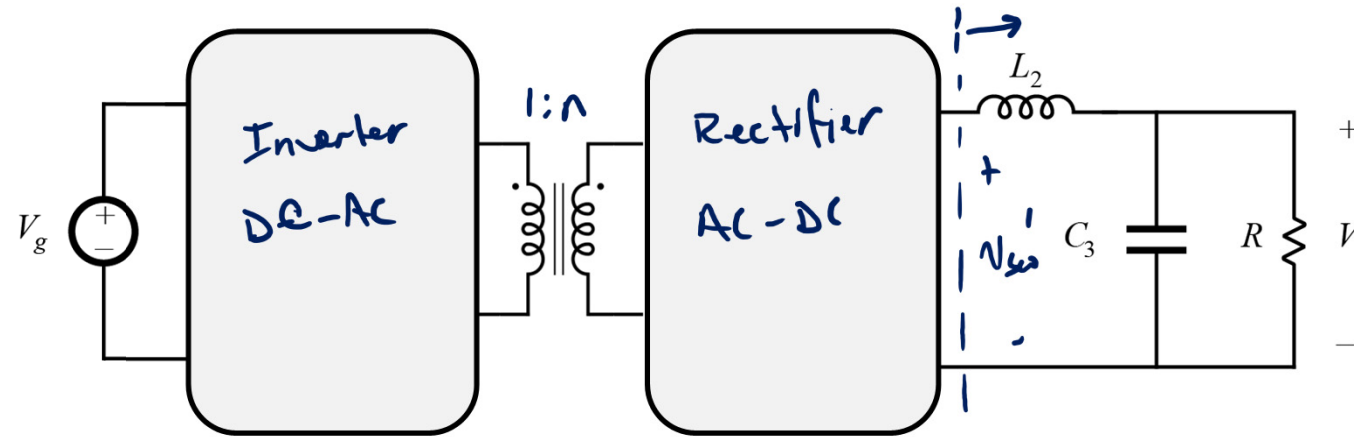


# Buck-derived Isolated Converters

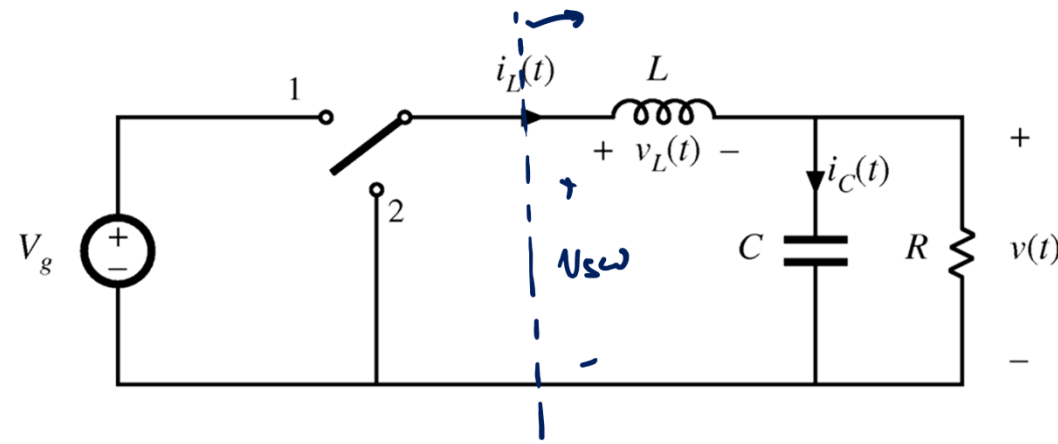


# Full Bridge Converter

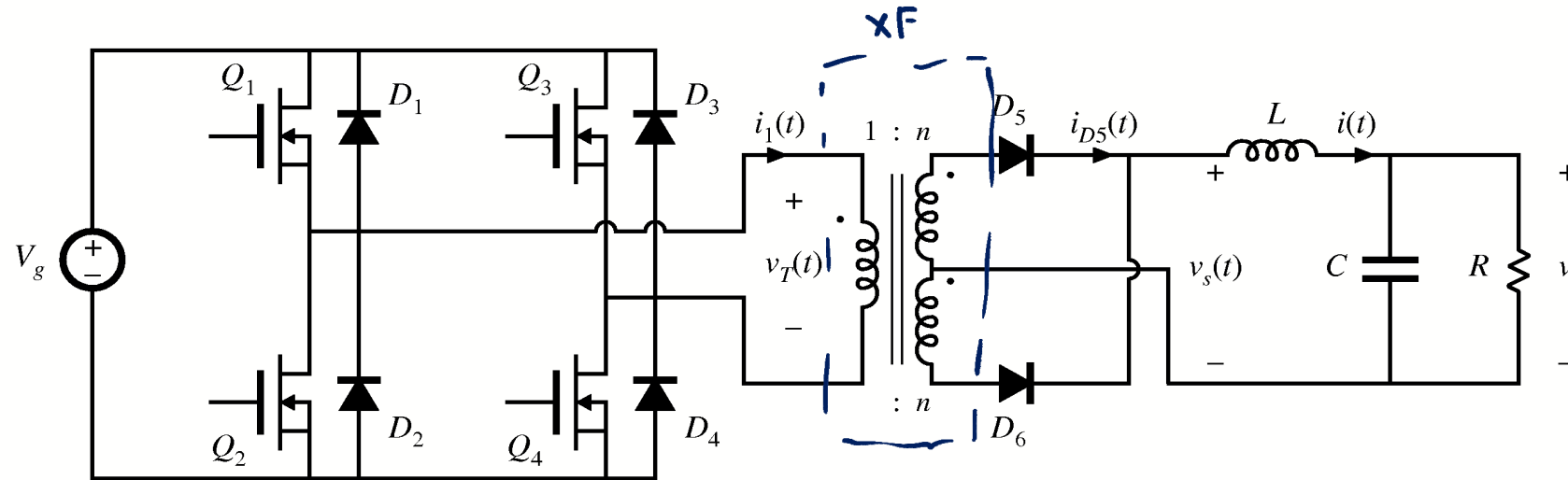

$\times F$  nearly ideal



$-L_m$  is "very large"  $\rightarrow$  Negligible as long as it doesn't saturate

# Full Bridge Converter

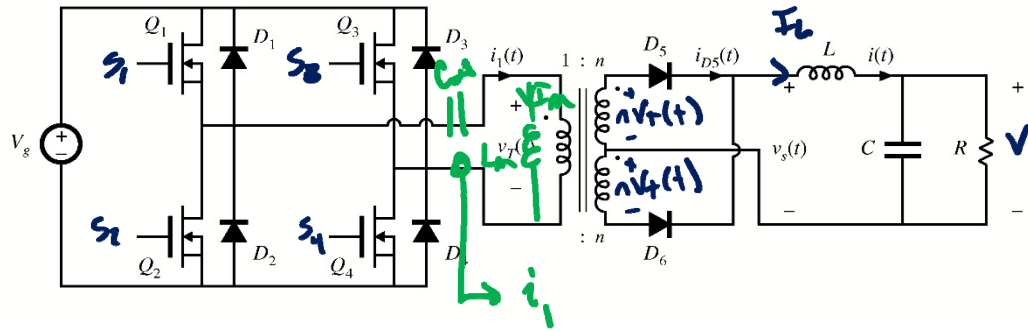

conducting

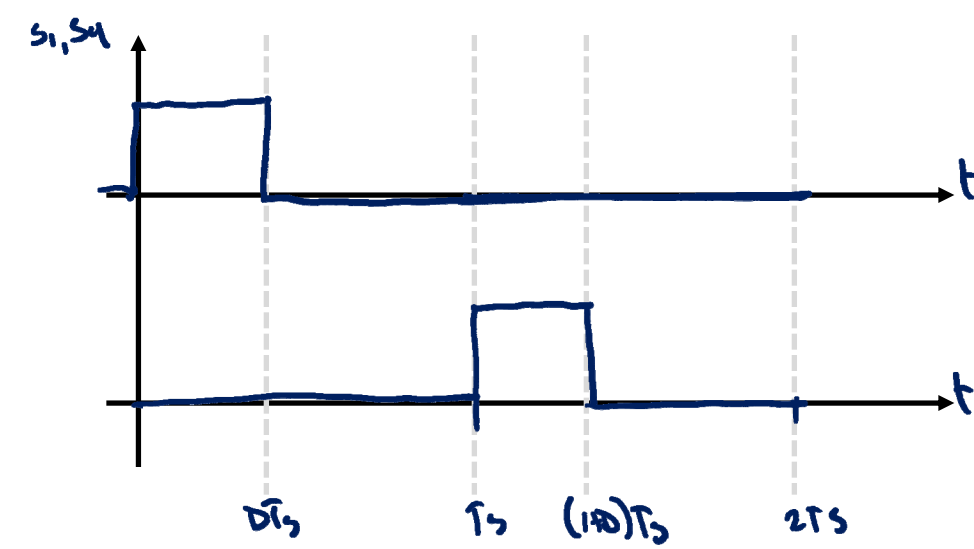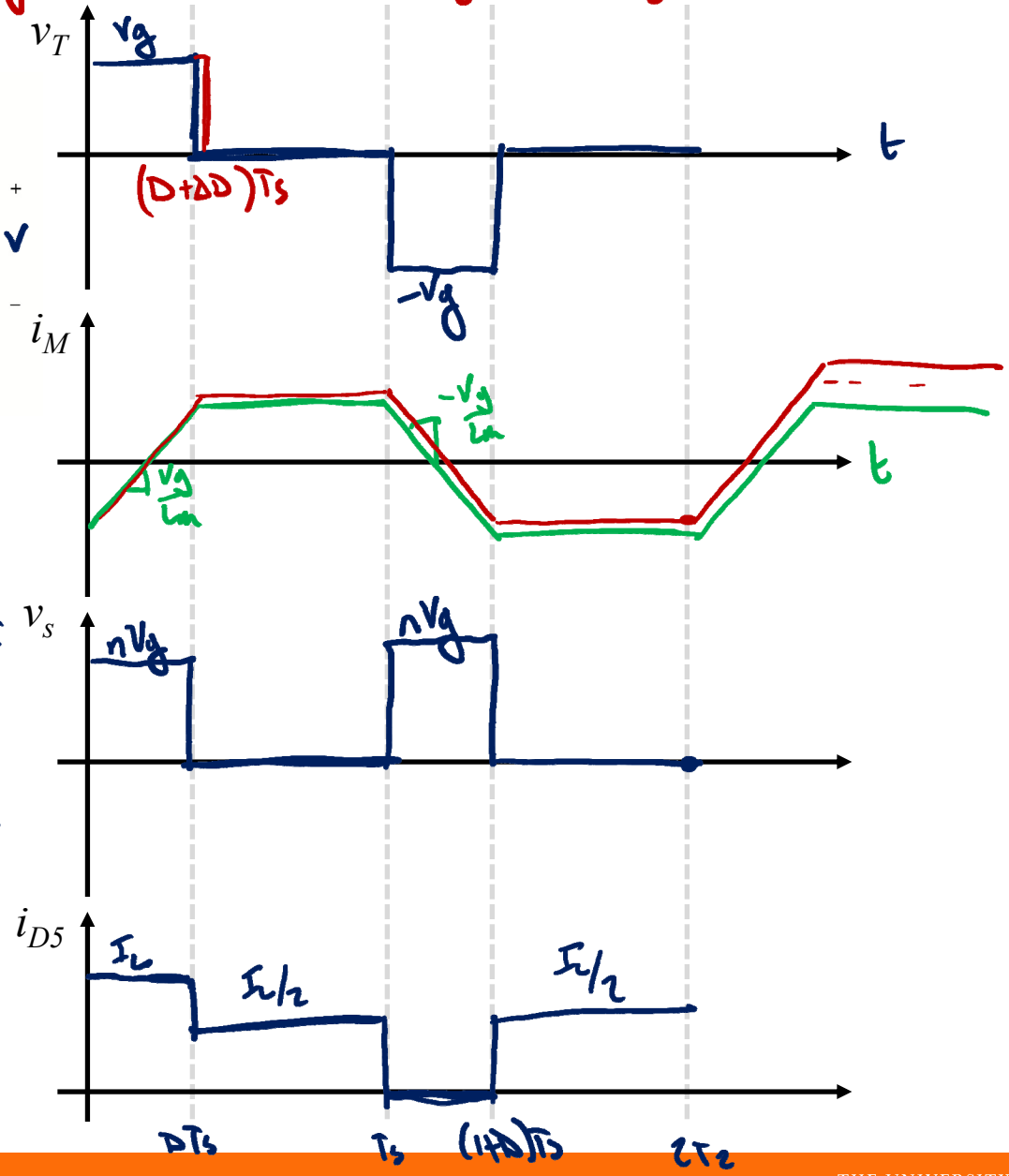$Q_1, Q_4$   
 $D_5$   $D_5 \& D_6$   $Q_1, Q_3$   
 $D_6$   $D_5 \& D_6$



# Conversion Ratio

$$\langle N_c \rangle = \phi = \left[ \frac{1}{2\tau_s} \int_0^{2\tau_s} n_s(t) dt \right] \cdot v = \frac{1}{2\tau_s} \left[ z \cdot n D V g \cdot \tau_s \right] - v = 0$$

$$v = n D V g$$
$$n = \frac{v}{V g} = n D$$

$$0 \leq n \leq \infty$$

$$0 \leq D \leq 1$$

# Transformer Saturation


$$\langle N_T \rangle = \phi = D V_g + D(-V_g) = \phi$$

- Ideally, volt-sec balance always maintained in every period
- If there is any unbalanced nonideality, we will accumulate volt-seconds & saturate
- Timing errors e.g. DTs mismatch between  $Q_1/Q_4$  &  $Q_2/Q_3$
  - Minor variations in bes

$$\langle V_T \rangle = \phi = D \left( V_g - \frac{I_L}{n} (R_{on1} + R_{on4}) \right) + D \left( -V_g + \frac{I_L}{n} (R_{on2} + R_{on3}) \right)$$



Practically  $\rightarrow$  use either current sensing or DC block in series w/ XF

# Push Pull Converter

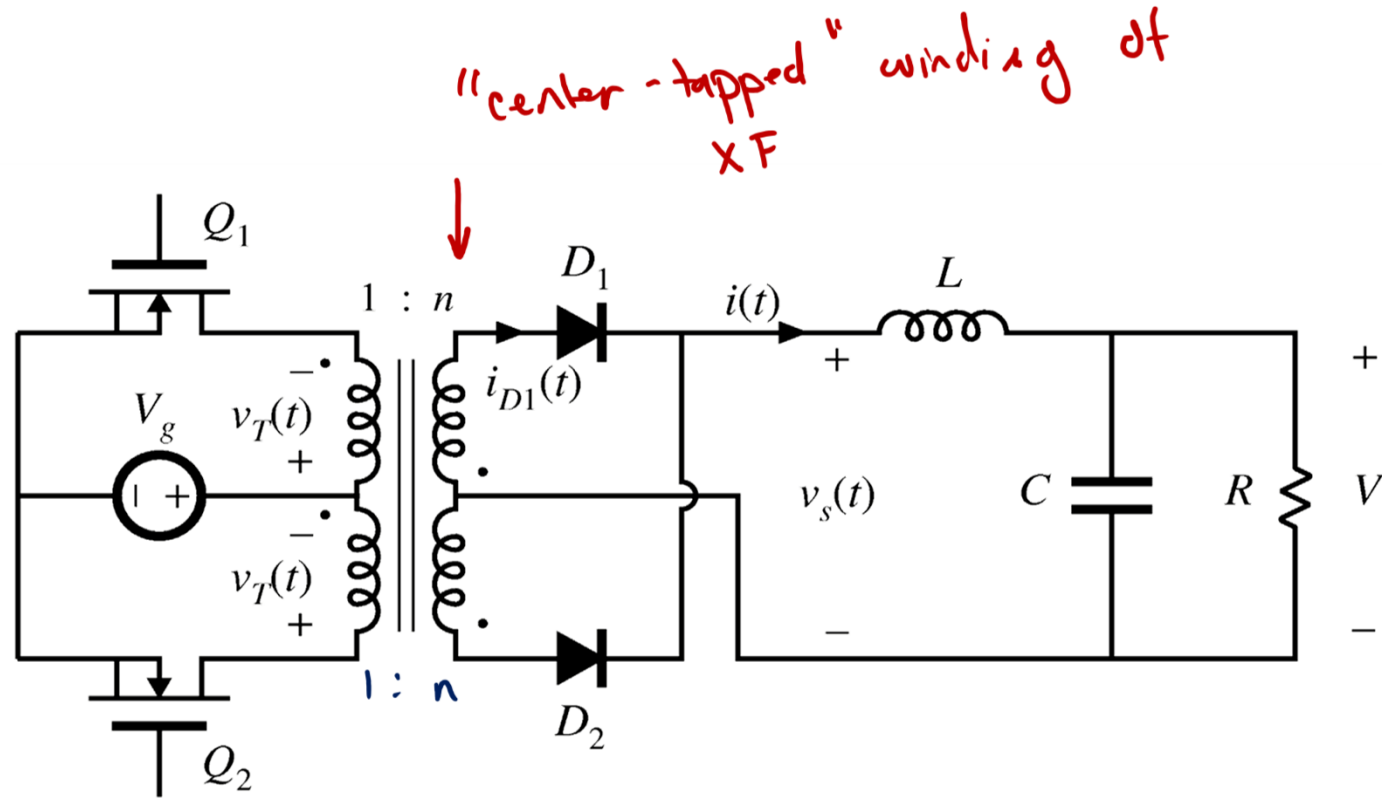

same waveforms :  $M = nD$

# Half Bridge Isolated Buck

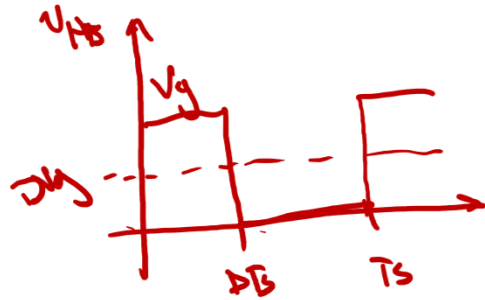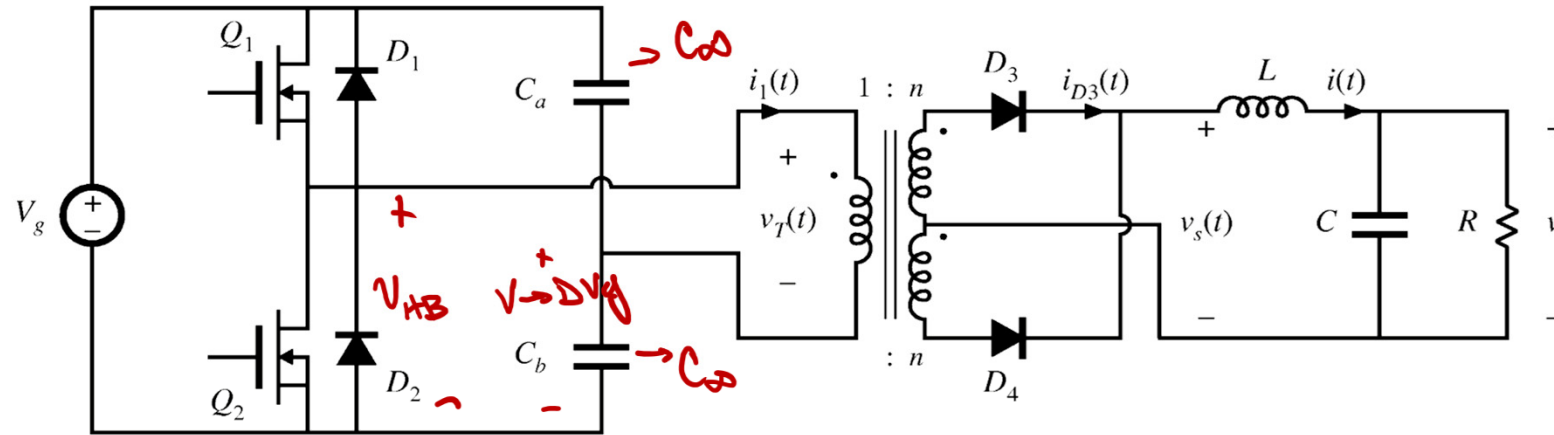

$$M = \frac{1}{2} n D$$