
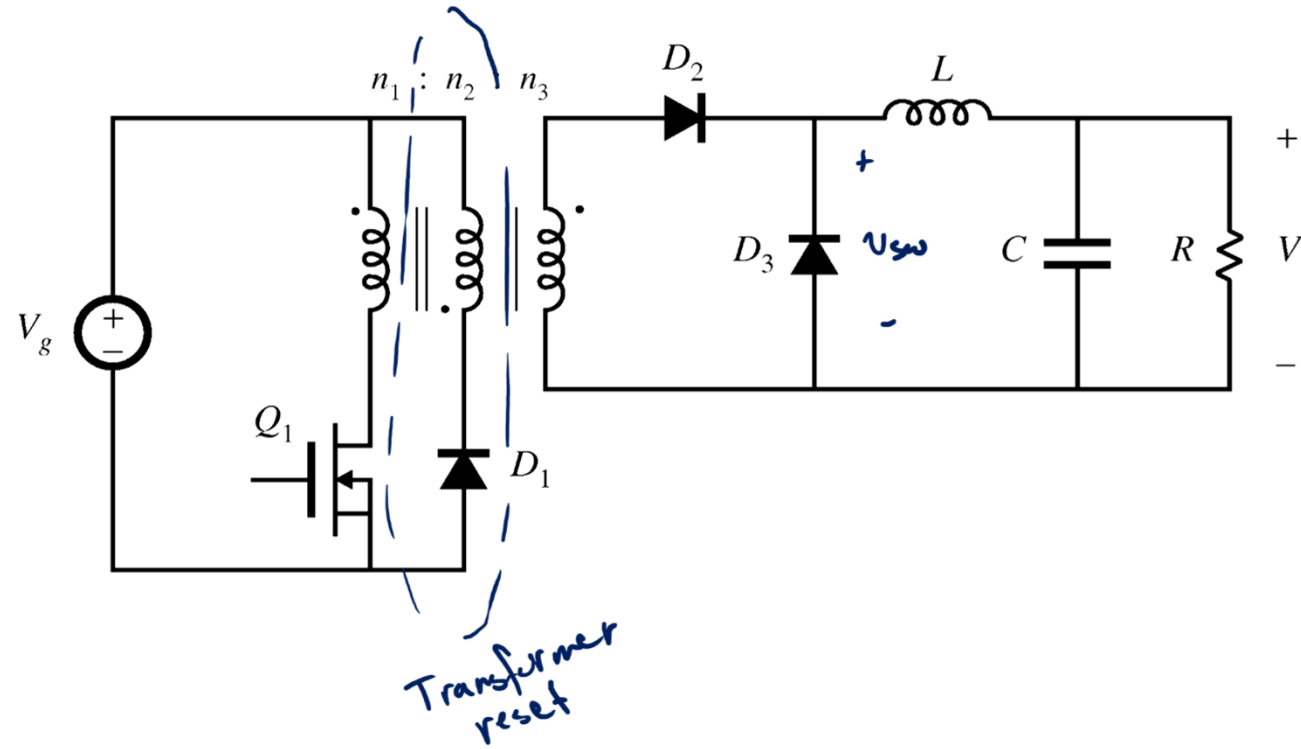



# 6.3.2 Forward Converter

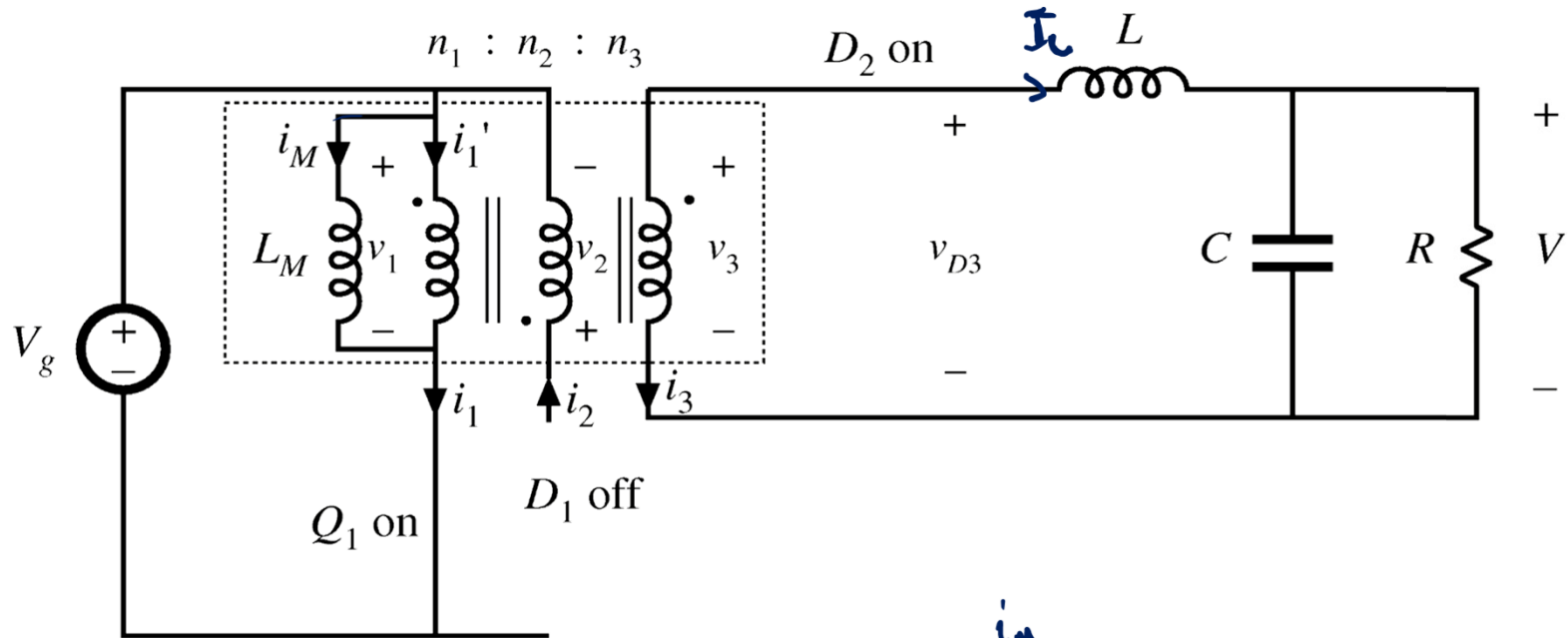

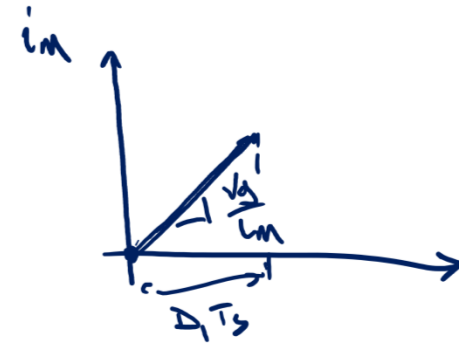
# Subinterval 1



$$\begin{aligned}
 v_1 &= V_g \\
 v_3 &= V_g \frac{n_3}{n_1} \\
 v_2 &= V_g \frac{n_2}{n_1}
 \end{aligned}$$



# Subinterval 2

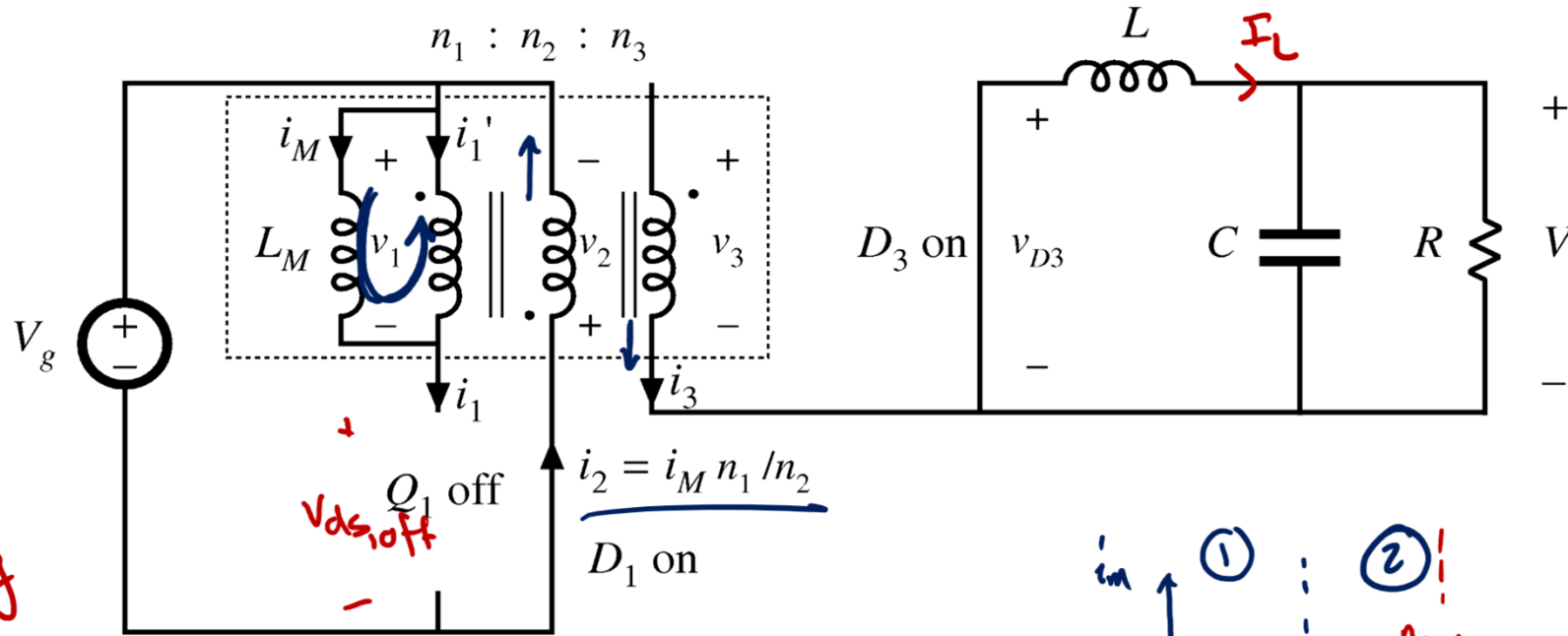


$Q_1$ : Blocking  
 $V_{ds,off} = V_g + \frac{n_1}{n_2} V_g$   
 $= V_g (1 + \frac{n_1}{n_2})$


$v_2 = -V_g$

$v_1 = -\frac{n_1}{n_2} V_g$


$v_3 = -\frac{n_3}{n_2} V_g$

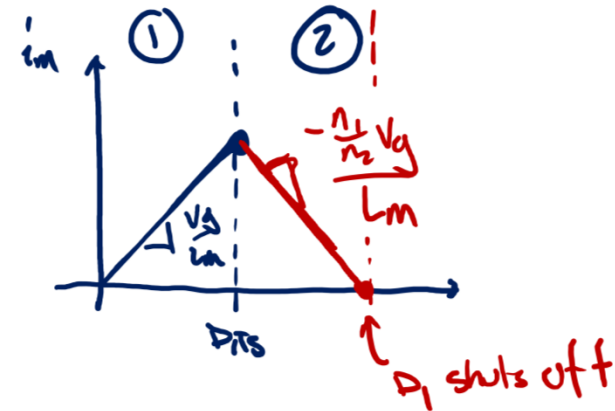

# Subinterval 3

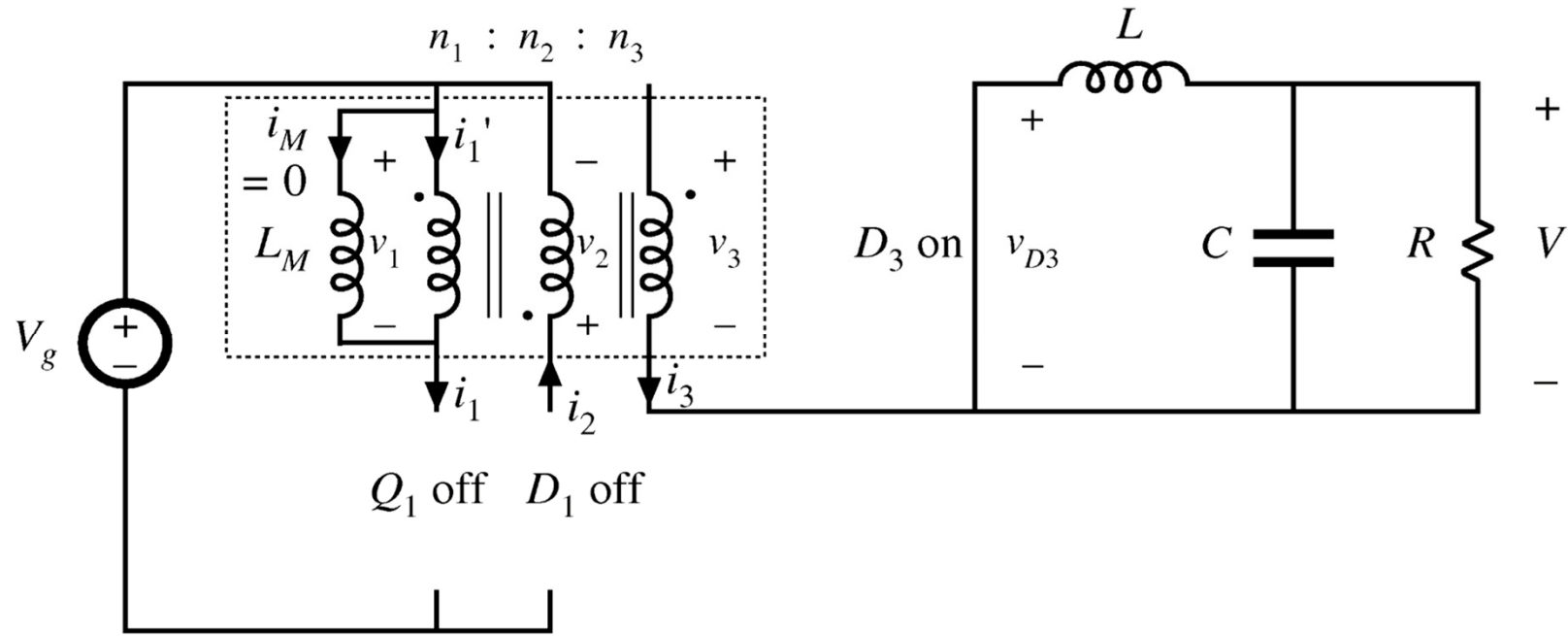

# Forward Waveforms

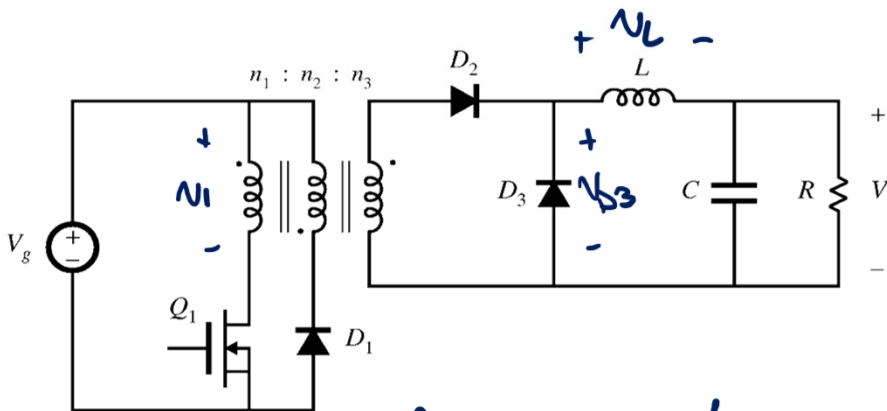

$$\langle V_L \rangle = \phi = \frac{n_3}{n_1} V_g D_1 - V$$

$$M = \frac{V}{V_g} = \frac{n_3}{n_1} D_1$$

check  $L_m$  saturation:

$$\langle V_L \rangle = \phi = D_1 V_g - \frac{n_1}{n_2} D_2 V_g$$


$$D_1 = \frac{n_1}{n_2} D_2$$

We know  $D_1 + D_2 + D_3 = 1, \quad D_3 \geq \phi$

$$D_1 + D_2 \leq 1$$

Limit
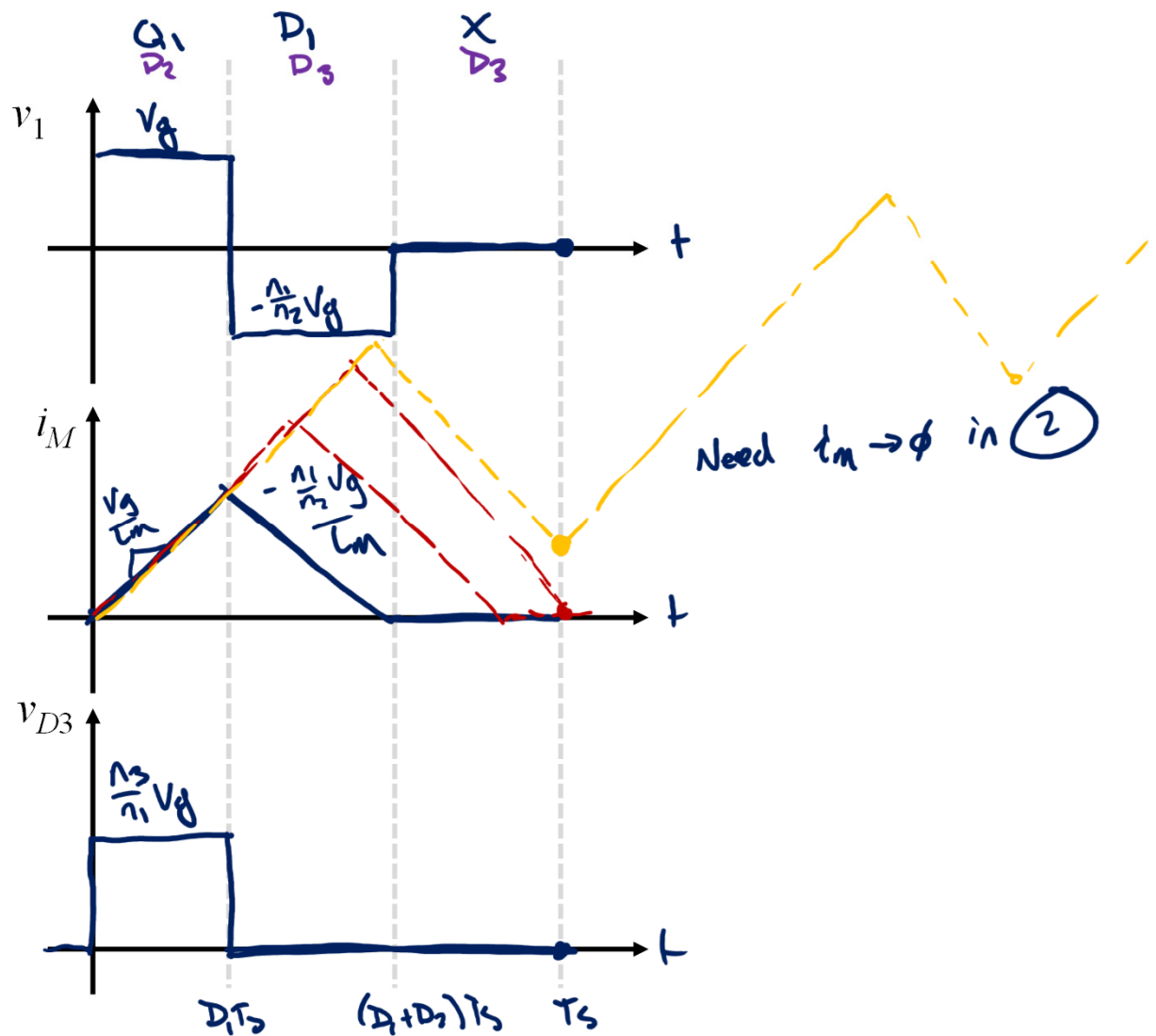
$$1 - D_1 - D_2 = \phi = 1 - D_1 - \frac{n_2}{n_1} D_1 = \phi$$



$$D_1 \left( 1 + \frac{n_2}{n_1} \right) = 1$$

$$D_{1,max} = \frac{1}{1 + \frac{n_2}{n_1}}$$



Non-saturation limit

$$V_{ds,off} = V_g \left( 1 + \frac{n_1}{n_2} \right)$$

$$D_1 \leq \frac{1}{1 + \frac{n_2}{n_1}}$$


$$\rightarrow \frac{n_1}{n_2} \text{ very small}$$

$\rightarrow \frac{n_1}{n_2}$  very large

$\rightarrow$  full range  $D_1$

small to reduce  $Q_1$  rating

# Two-Transistor Forward Converter




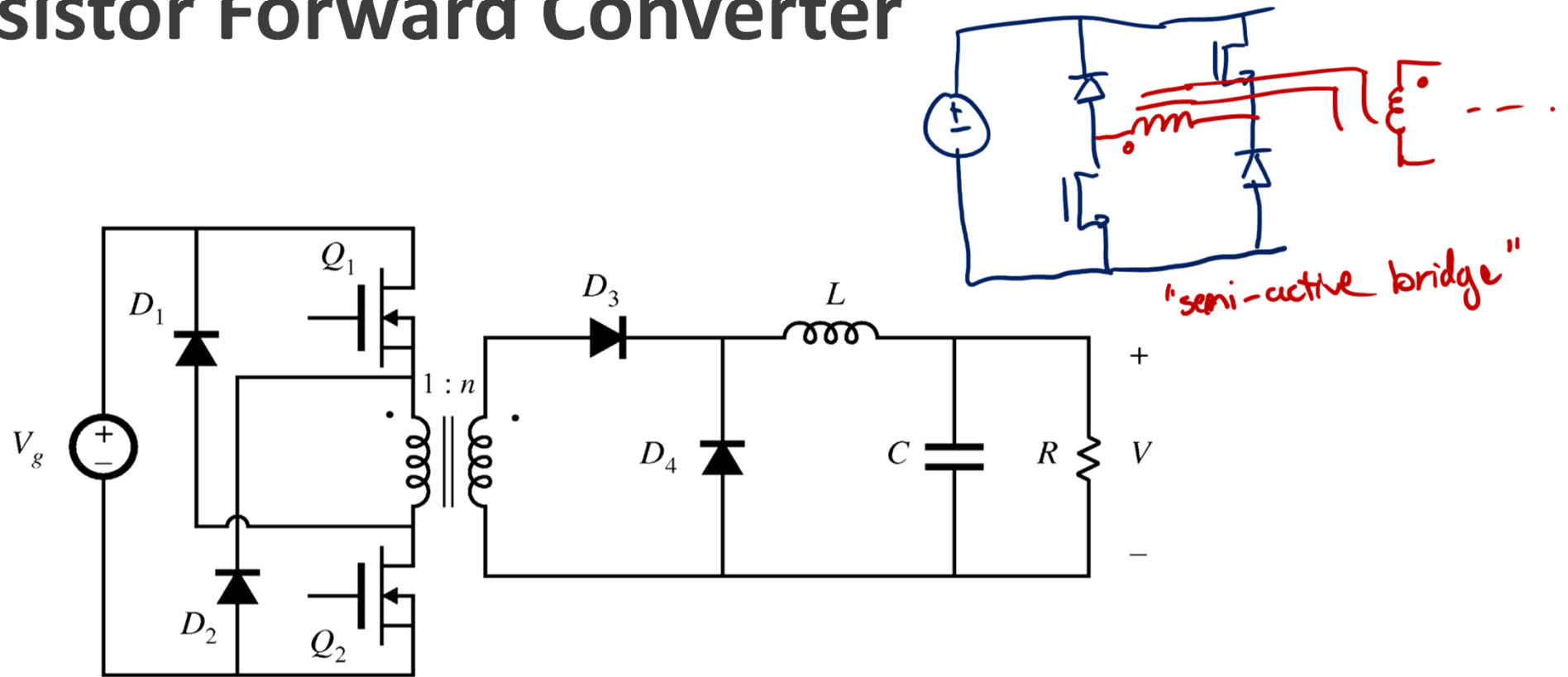


$$V = nDV_g$$

$$D \leq \frac{1}{2}$$


$$\max(v_{Q1}) = \max(v_{Q2}) = V_g$$

# Flyback Converter: Isolated Buck-Boost

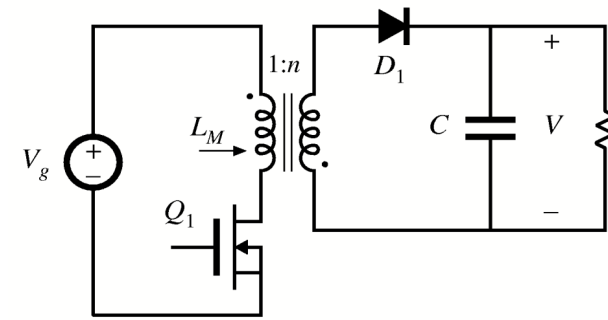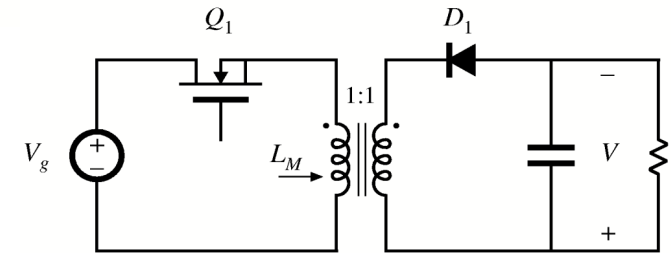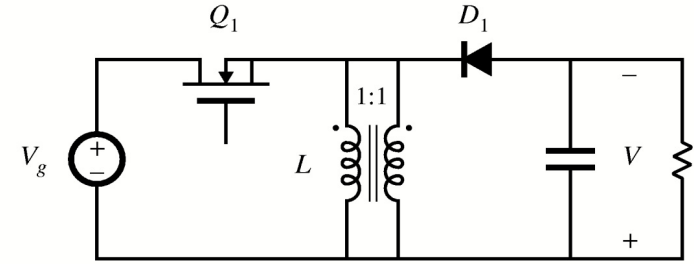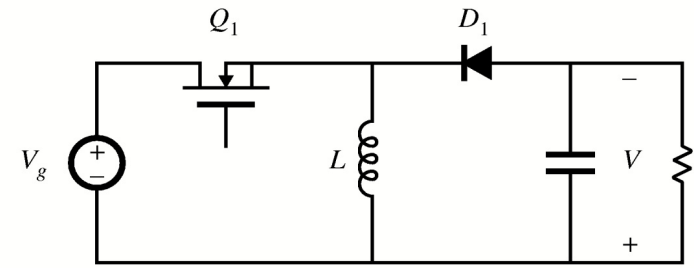





# Flyback Transformer

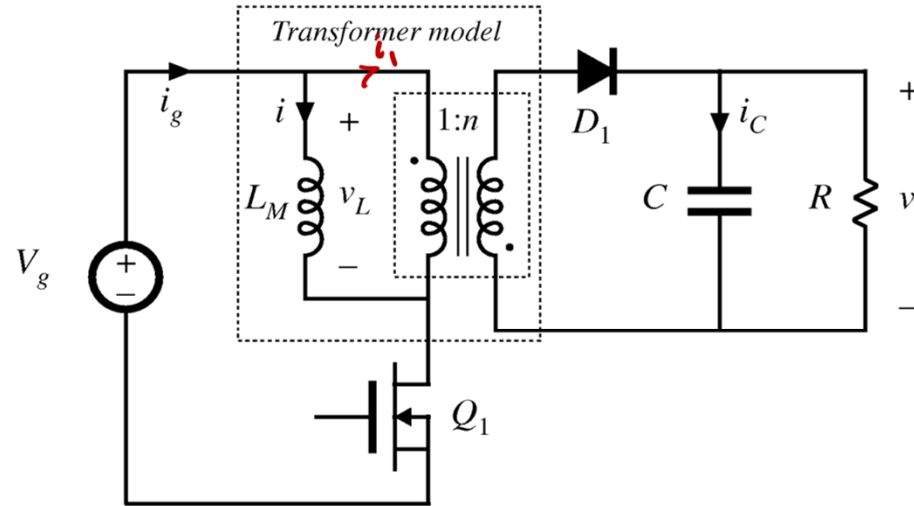

$L_M$  is the energy conversion inductor.  
it is not parasitic or "near infinite"  
we want substantially non-zero current  
Behaves more like a coupled inductor than  
a XF

# Flyback Application: iPad Charger

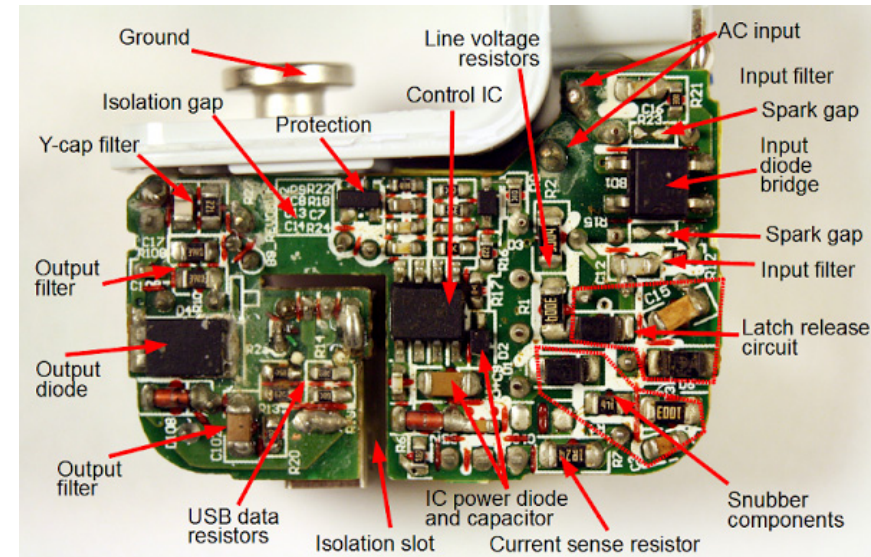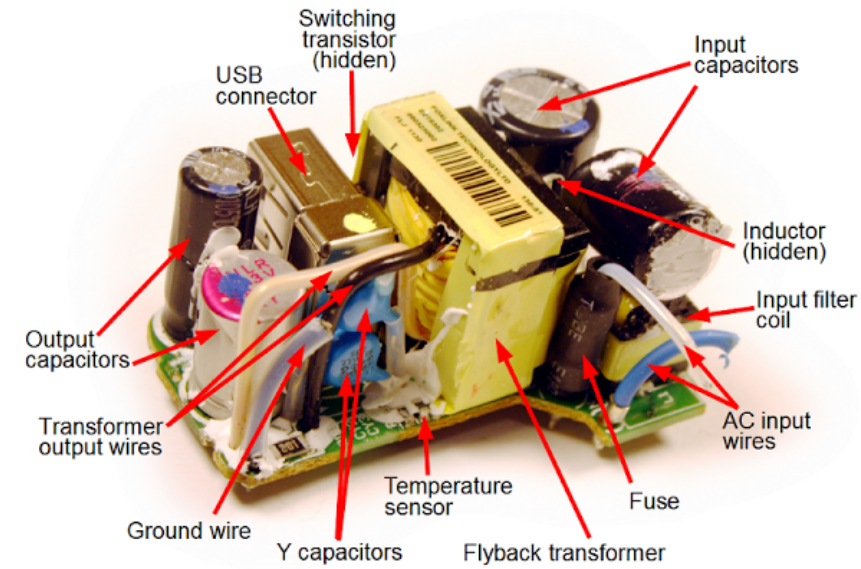

# Flyback Off-Line Charger Application Circuit

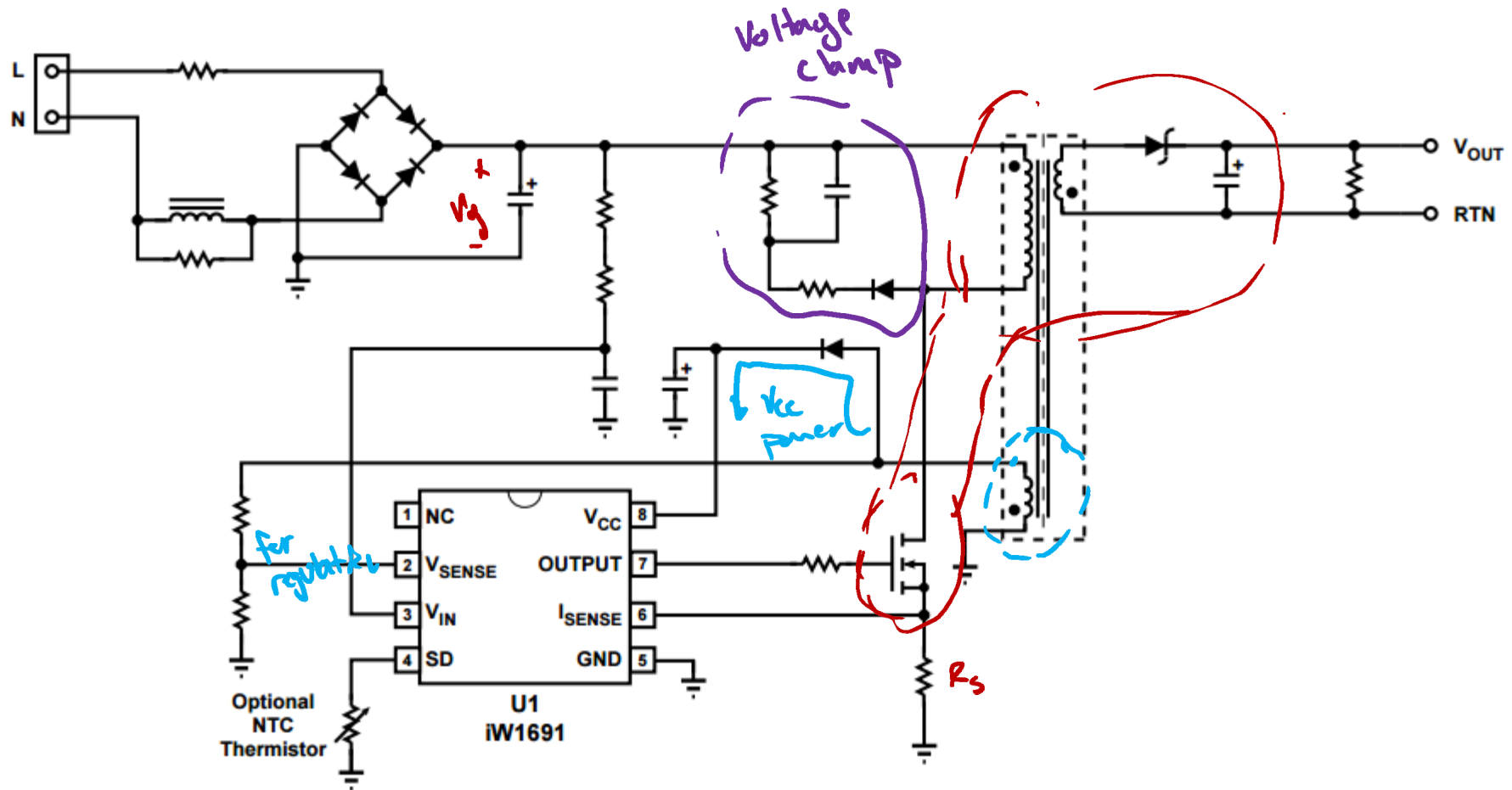


Figure 3.1 : Typical Application Circuit