

Low-frequency Averaging

$$\langle x(t) \rangle_{T_s} \equiv \frac{1}{T_s} \int_{t-\frac{T_s}{2}}^{t+\frac{T_s}{2}} x(\tau) d\tau \quad \rightarrow \text{Removes switching ripple on } x(t)$$

for an inductor

$$\langle i_L(t) \rangle_{T_s} = \frac{1}{T_s} \int_{t-\frac{T_s}{2}}^{t+\frac{T_s}{2}} i_L(\tau) d\tau$$

what is:

$$\frac{d \langle i_L(t) \rangle_{T_s}}{dt}$$

$$= \frac{d}{dt} \left[\frac{1}{T_s} \int_{t-\frac{T_s}{2}}^{t+\frac{T_s}{2}} i_L(\tau) d\tau \right]$$

$$= \frac{1}{T_s} \int_{t-\frac{T_s}{2}}^{t+\frac{T_s}{2}} \frac{d}{d\tau} i_L(\tau) d\tau$$

$$= \frac{1}{T_s} \int_{t-\frac{T_s}{2}}^{t+\frac{T_s}{2}} \frac{v_L(\tau)}{L} d\tau$$


$$\boxed{L \frac{d \langle i_L(t) \rangle_{T_s}}{dt} = \langle v_L(t) \rangle_{T_s}}$$

⊘ same for capacitor

as we go on. $\langle x(t) \rangle_{T_s} \equiv \langle x \rangle$ (short-hand notation)



Averaging Operator

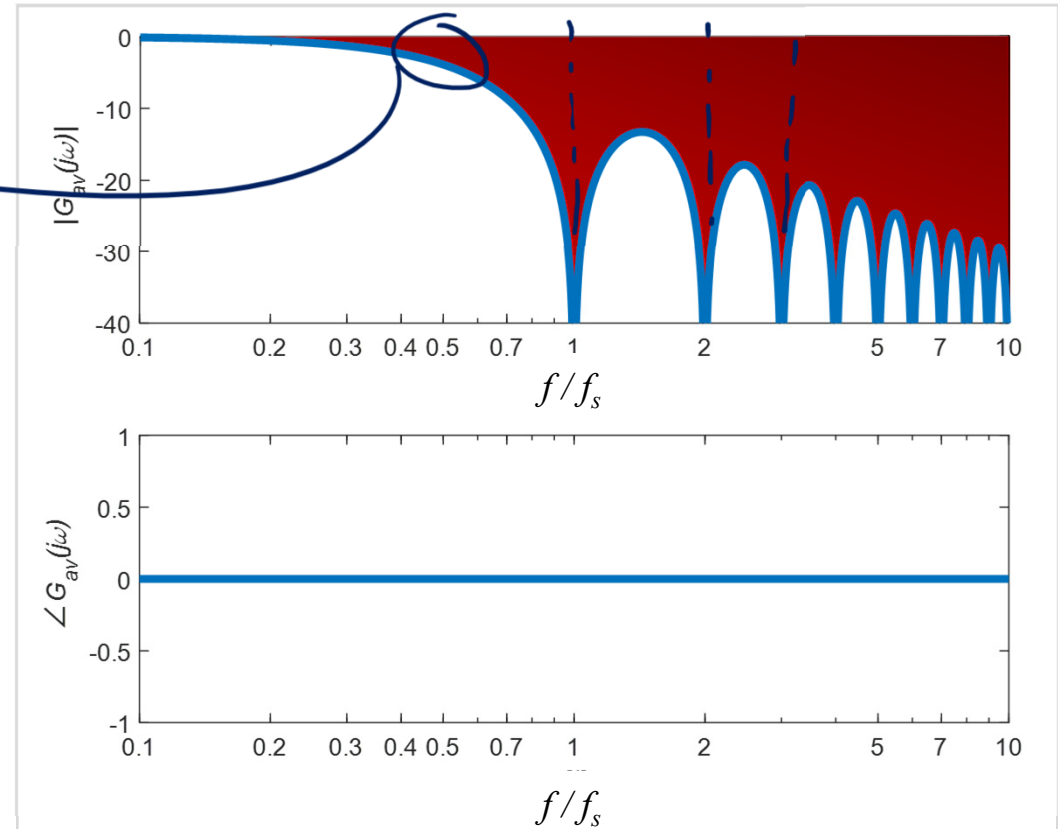Average Models inaccurate above $\sim f_s/10$



$$\begin{aligned}\mathcal{F}\left\{\frac{1}{T_s}\int_{t-\frac{T_s}{2}}^{t+\frac{T_s}{2}}x(\tau)d\tau\right\} &= \frac{e^{j\omega\frac{T_s}{2}}X(j\omega) - e^{-j\omega\frac{T_s}{2}}X(j\omega)}{j\omega T_s} \\ &= \text{sinc}\left(\omega\frac{T_s}{2}\right) \cdot X(j\omega) \\ &= G_{av}(j\omega) \cdot X(j\omega)\end{aligned}$$

Averaging in Steady-State

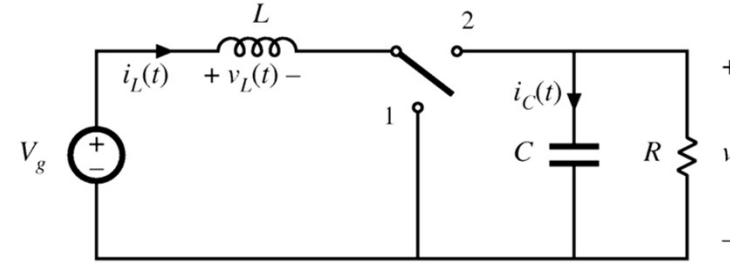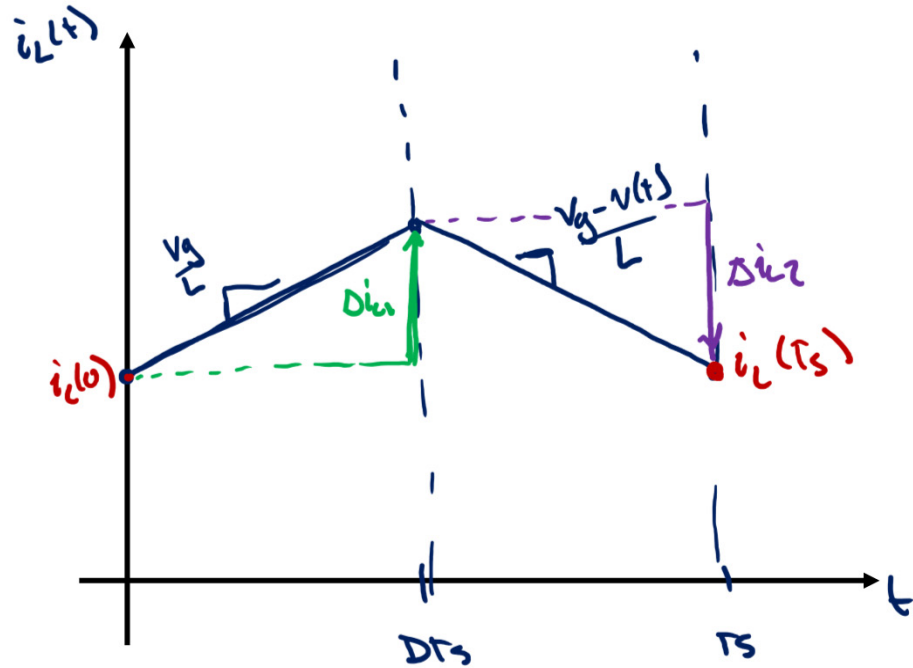

$$i_L(T_s) = i_L(0) + \frac{1}{L} \int_0^{DT_s} V_g dt + \frac{1}{L} \int_{DT_s}^{T_s} V_g - v(t) dt$$



small ripple approx $v(t) \rightarrow V$

$$i_L(T_s) = i_L(0) + \frac{V_g}{L} DT_s + \frac{V_g}{L} D' T_s - \frac{V}{L} D' T_s \quad (1)$$

(2) $L \frac{[i_L(T_s) - i_L(0)]}{T_s} = V_g - D'V$

$L \frac{\Delta i_L}{\Delta t} \Big|_{T_s} = V_g - D'V \rightarrow \phi = V_g - D'V, \quad m = \frac{1}{D'}$

Averaging in Transient Operation

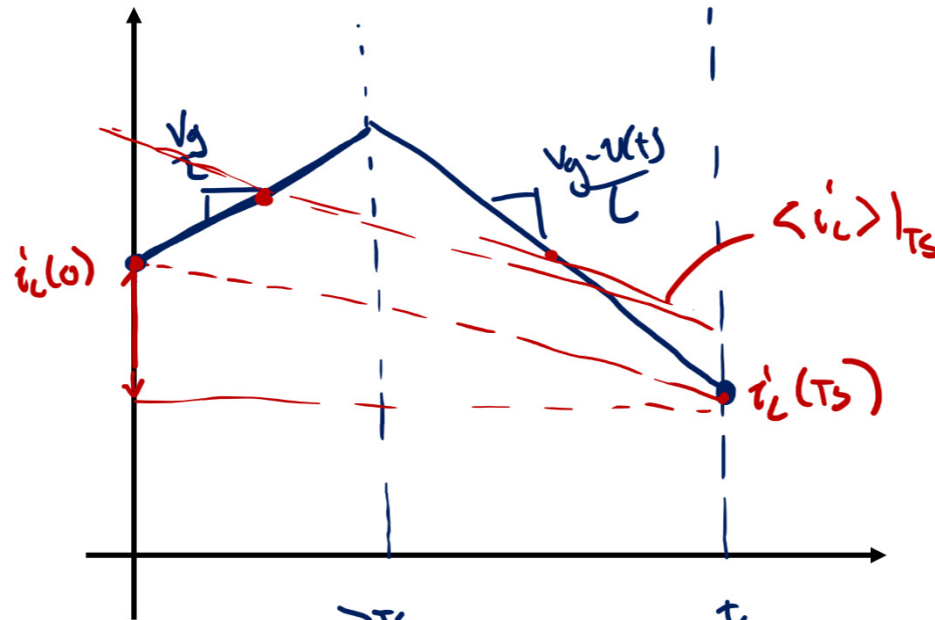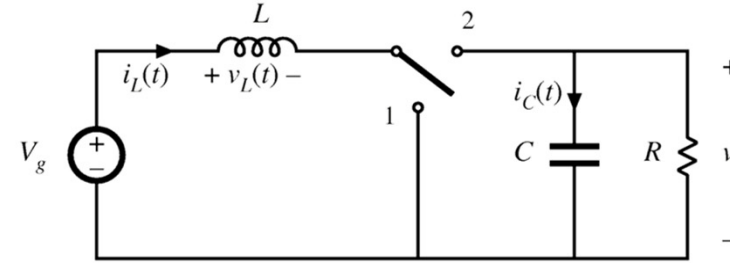

$$i_C(Ts) = i_C(0) + \Delta i_{C1} + \Delta i_{C2}$$

Rather than SRA replacing signals w/ DC, we'll replace them with their average value (slowly time-varying)

$$i_C(Ts) = i_C(0) + \frac{\langle V_g \rangle}{L} Ts - \frac{\langle v \rangle}{L} d'(t) Ts$$

$$L \frac{[i_C(Ts) - i_C(0)]}{Ts} = \langle V_g \rangle - \langle v \rangle d'(t)$$


$$L \frac{d \langle i_C(t) \rangle}{dt} = \langle v_L(t) \rangle = \langle V_g(t) \rangle - \langle v(t) \rangle d'(t)$$

Averaging: Discussion

Replace signals with slowly-varying averages
- All switching ripple removed from signal

Limitations:

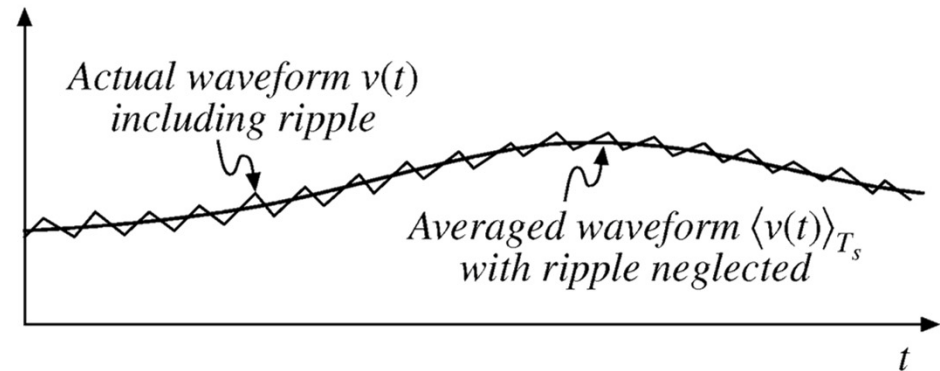- (1) must have small switching ripple
- (2) Valid only for $f \ll f_s$ (common $f < f_s/10$)
- (3) Generally, circuit is still nonlinear after averaging





Averaged (Nonlinear) Model

Boost Converter

$$\langle v_L \rangle = L \frac{d\langle i_L \rangle}{dt} = \langle v_g \rangle - \langle v \rangle d'(t)$$

$$\langle i_C \rangle = C \frac{d\langle v \rangle}{dt} = d'(t) \langle i_L \rangle - \frac{\langle v \rangle}{R}$$

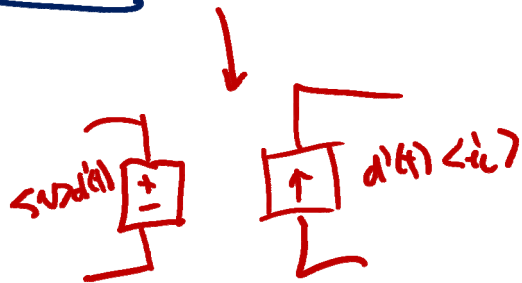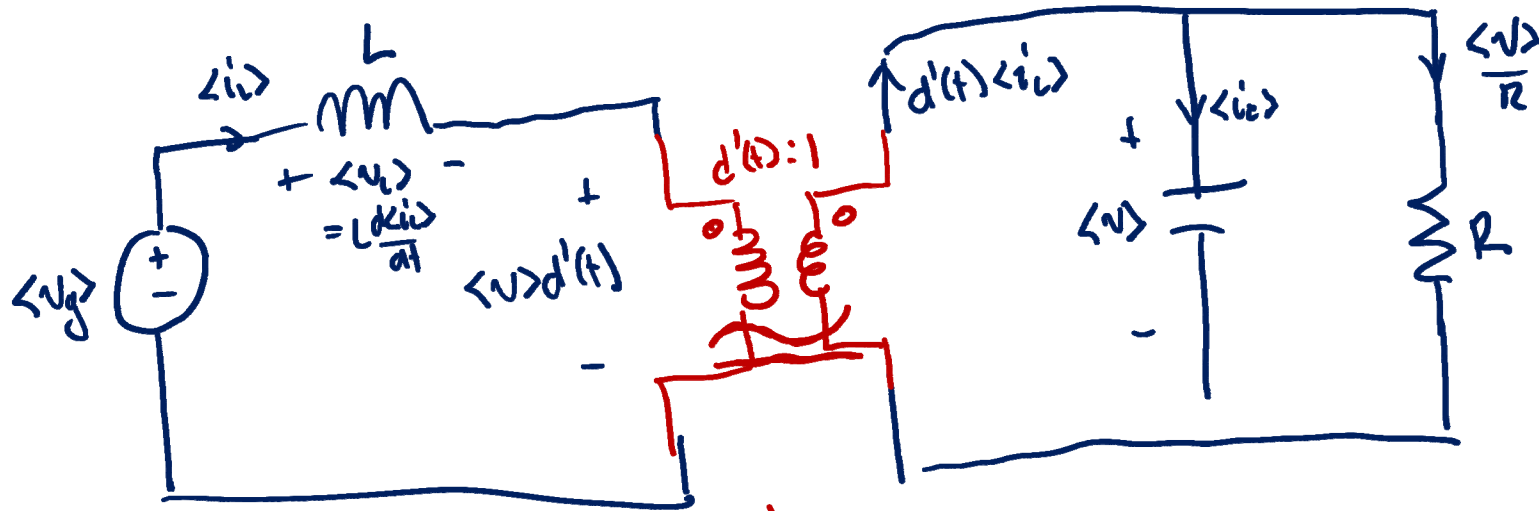Nonlinear, averaged model
(is time-invariant)



Nonlinear, time-invariant
averaged model useful
for simulation

SPICE can linearize this
(Time-invariant) circuit
(i.e. ac simulations work)

Small Signal Modeling: Linearization

