

Chapter 2: Converters in Equilibrium





THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Chapter 2: Goals



- Develop techniques for easily determining output voltage of an arbitrary converter circuit
- Derive the principles of *inductor volt-second balance* and *capacitor charge (amp-second) balance*
- Introduce the key *small ripple approximation*
- Develop simple methods for selecting filter element values
- Illustrate via examples

Buck Converter Review

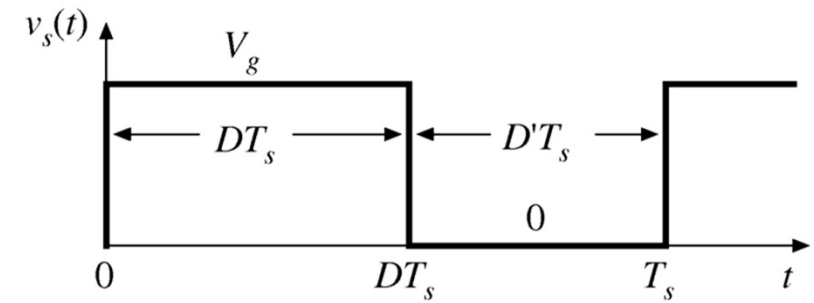
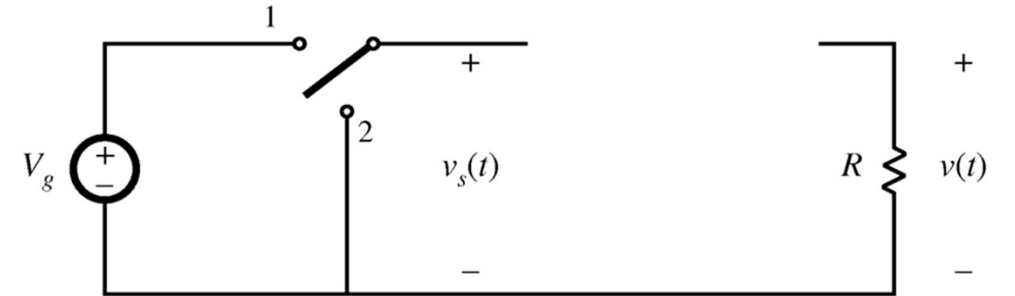


Three Basic DC-DC PWM Converters



Buck

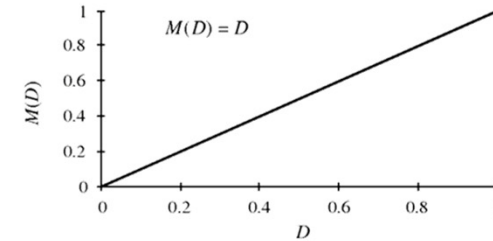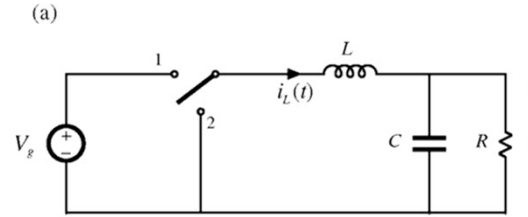


Boost

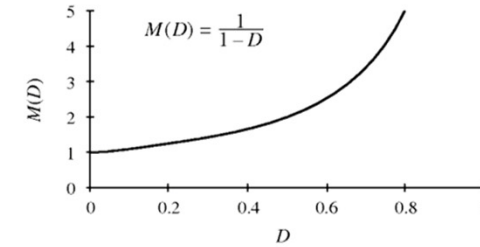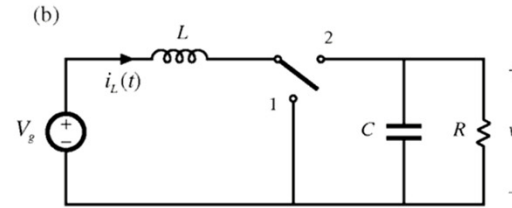


Buck-boost

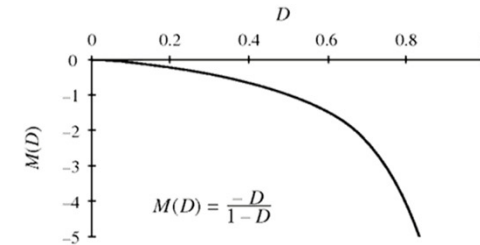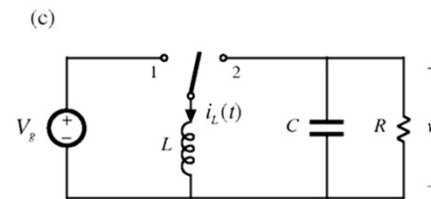


The Small Ripple Approximation

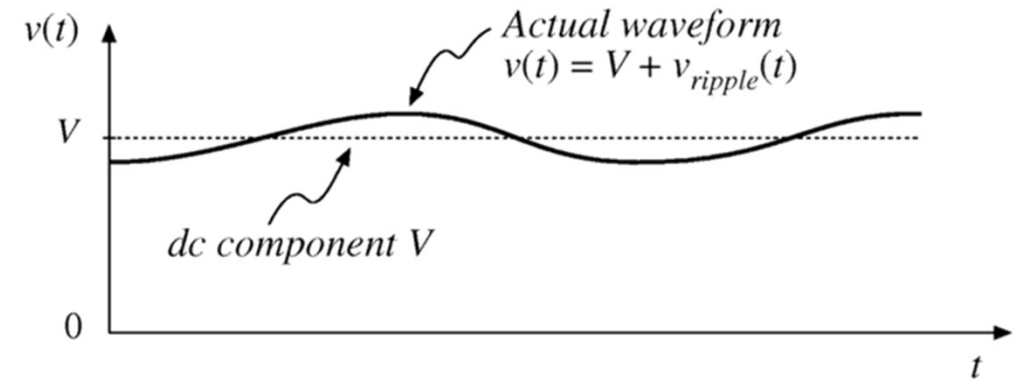


Buck Switching Intervals: Inductor Current

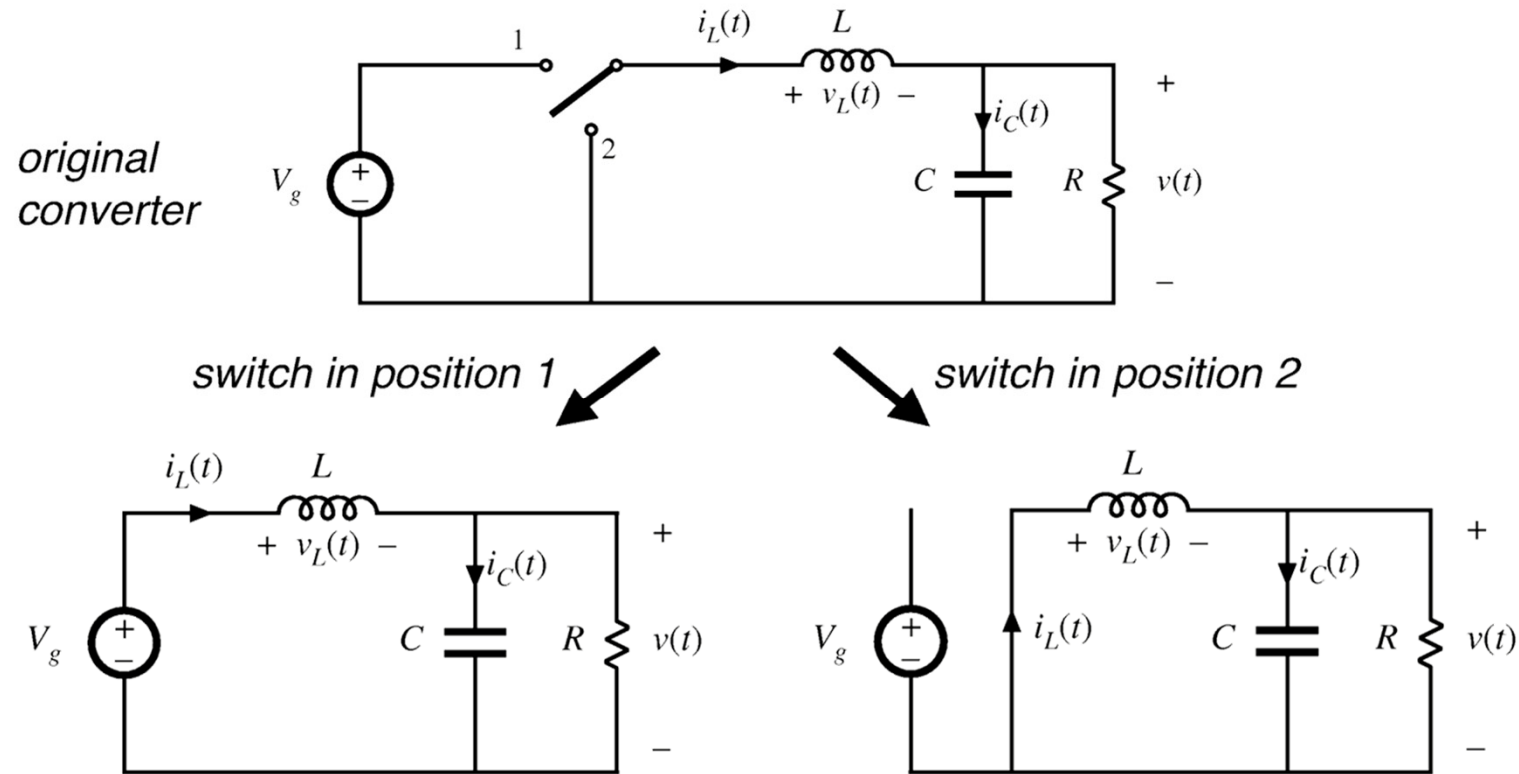



Subinterval 1

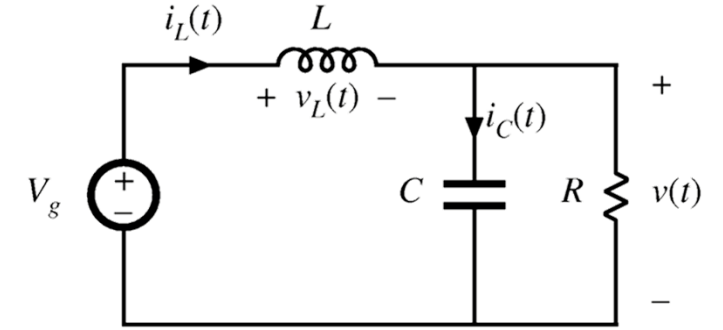


Subinterval 2

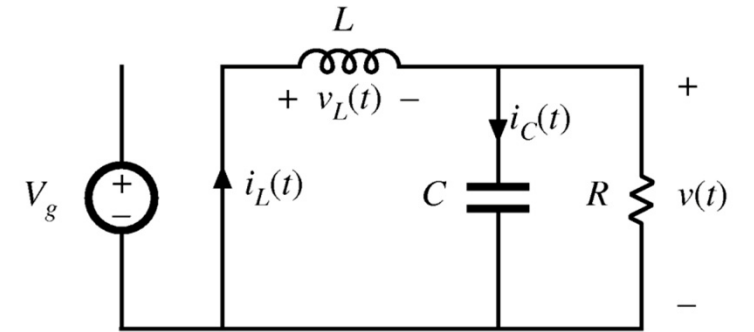


Current Waveform

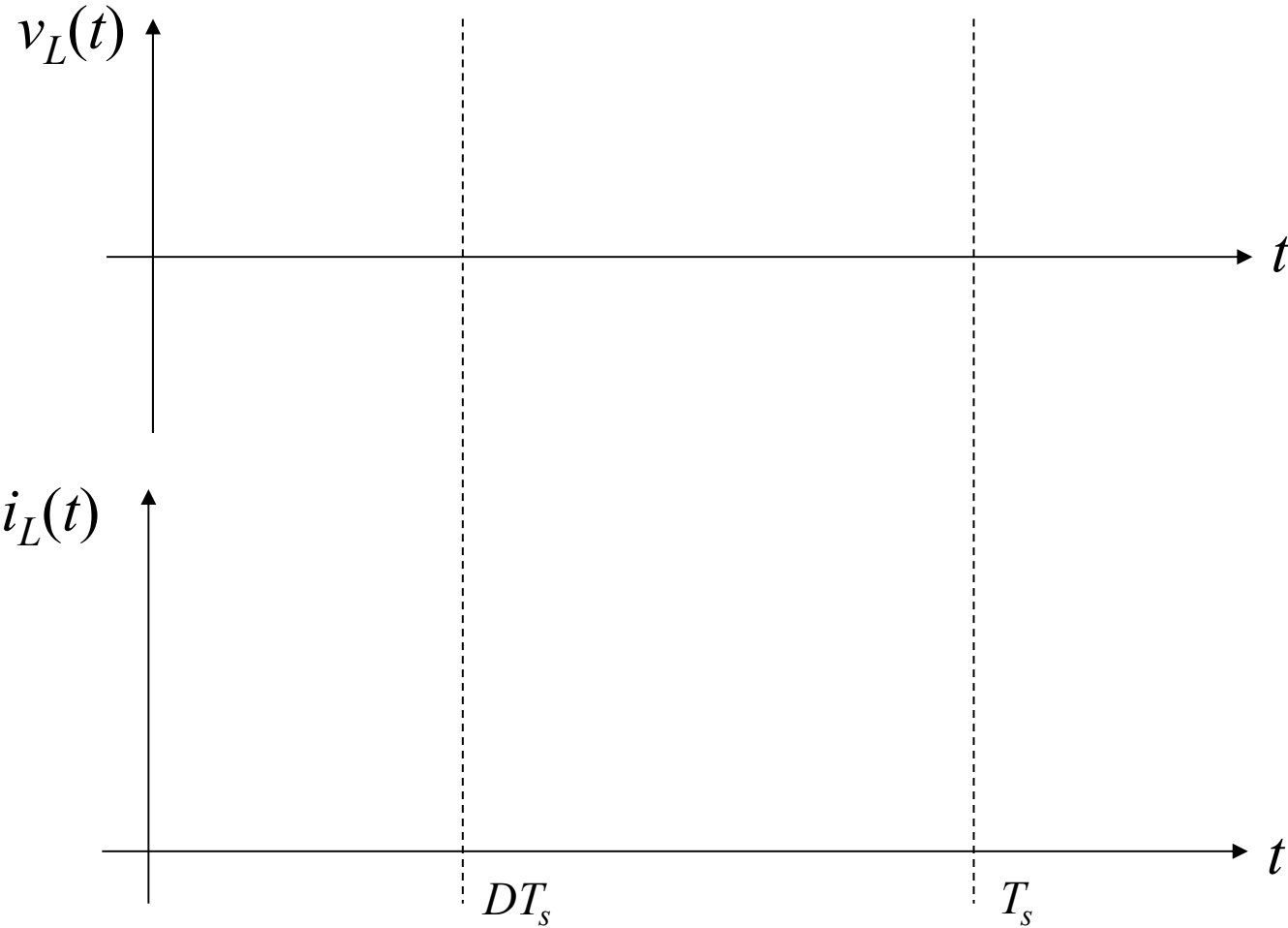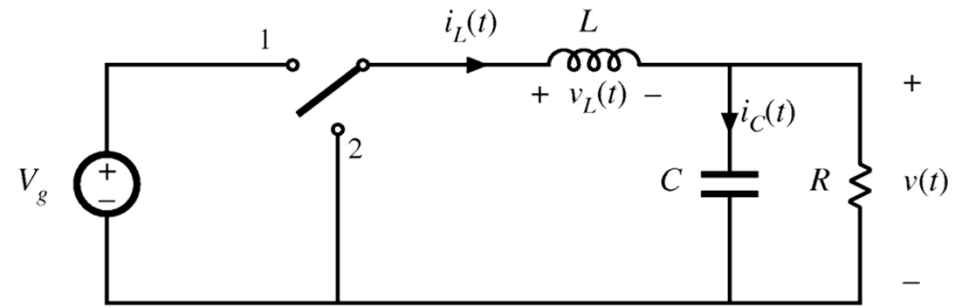

Transient vs. Steady-State Operation

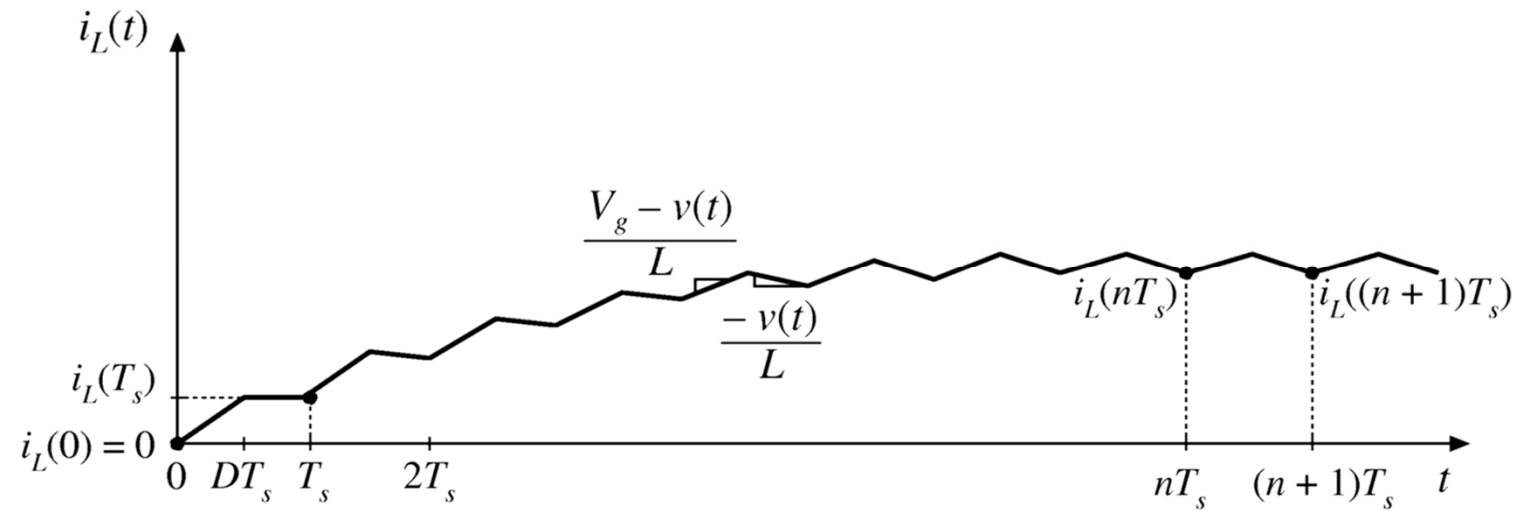

Volt-Second Balance

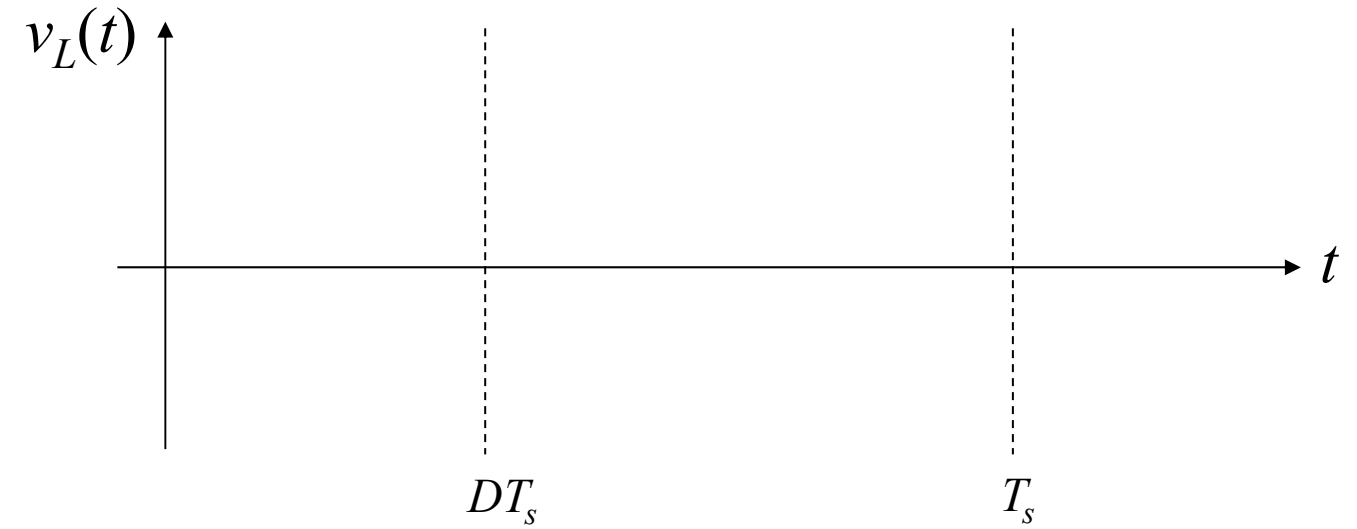



Derivation of Volt-second Balance

Volt-Second Balance: Direct Application

