


Design Approach

- Assume $G_c(s) = 1$, and plot the resulting uncompensated loop gain $T_u(s)$
- Examine uncompensated loop gain to determine the needs of the compensator
 - Is low-frequency loop gain amplitude $\|T(0)\|$ large enough to result in **low steady-state error**?
 $\hookrightarrow \|T(0)\| \xrightarrow[\text{zero steady-state error}]{} \infty$
 - Is φ_m sufficient for stability and requirements **on ringing/overshoot**?
 - Is f_c high enough for a sufficiently **fast response**?
- Construct compensator to address shortcomings of $T_u(s)$
 - Use “toolbox” of compensators


Additional Considerations:

$$\left\{ \begin{array}{l} f_c \leq f_s/10 \rightarrow \text{Due to effects neglected in average model} \\ \|T(f < f_c)\| = \text{"large"} \\ \|T(f > f_c)\| = \text{"small"} \end{array} \right\} \text{Based on phase margin test limitations}$$


Example: Uncompensated Loop Gain

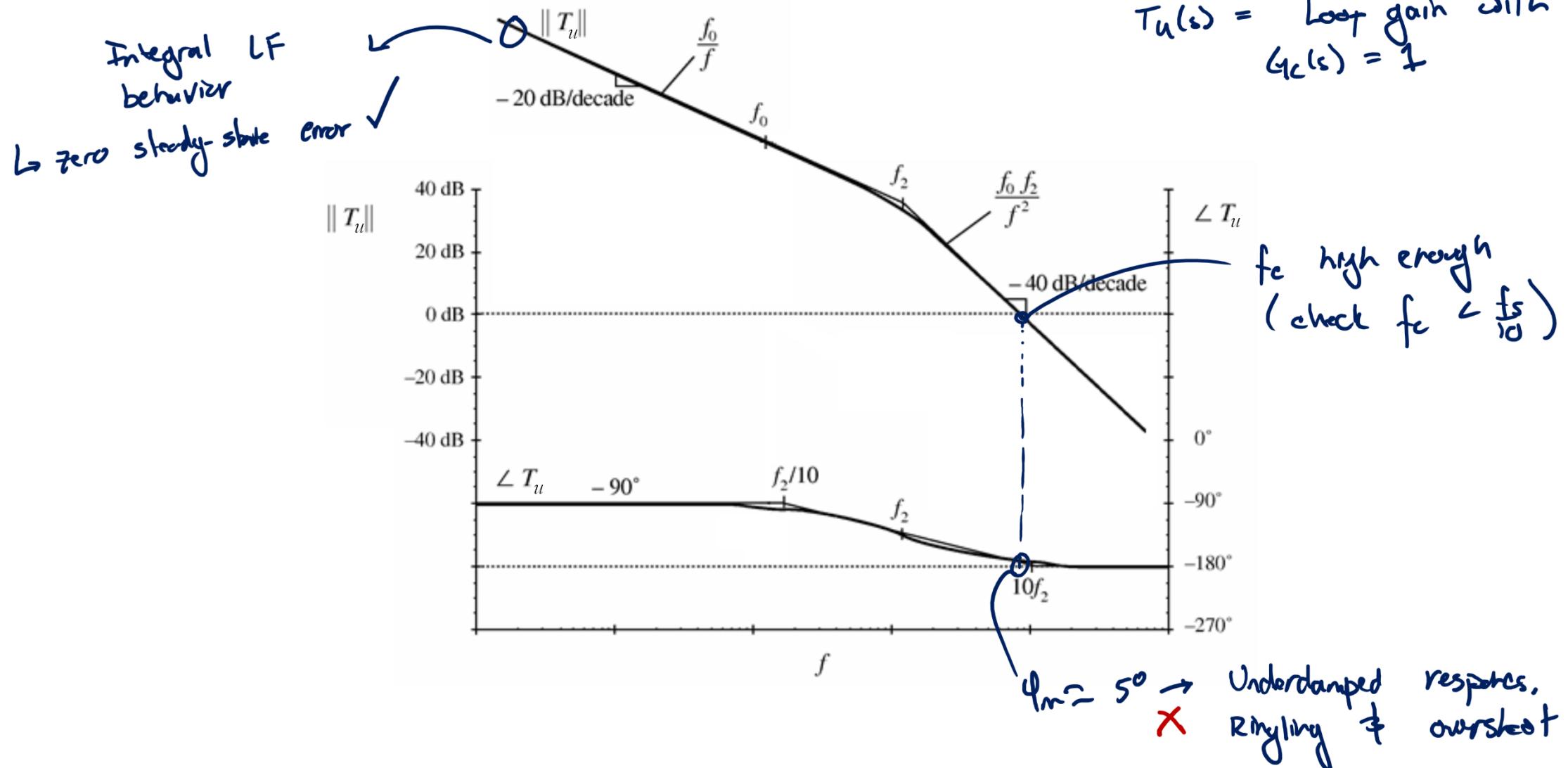

Proportional (P) Compensator

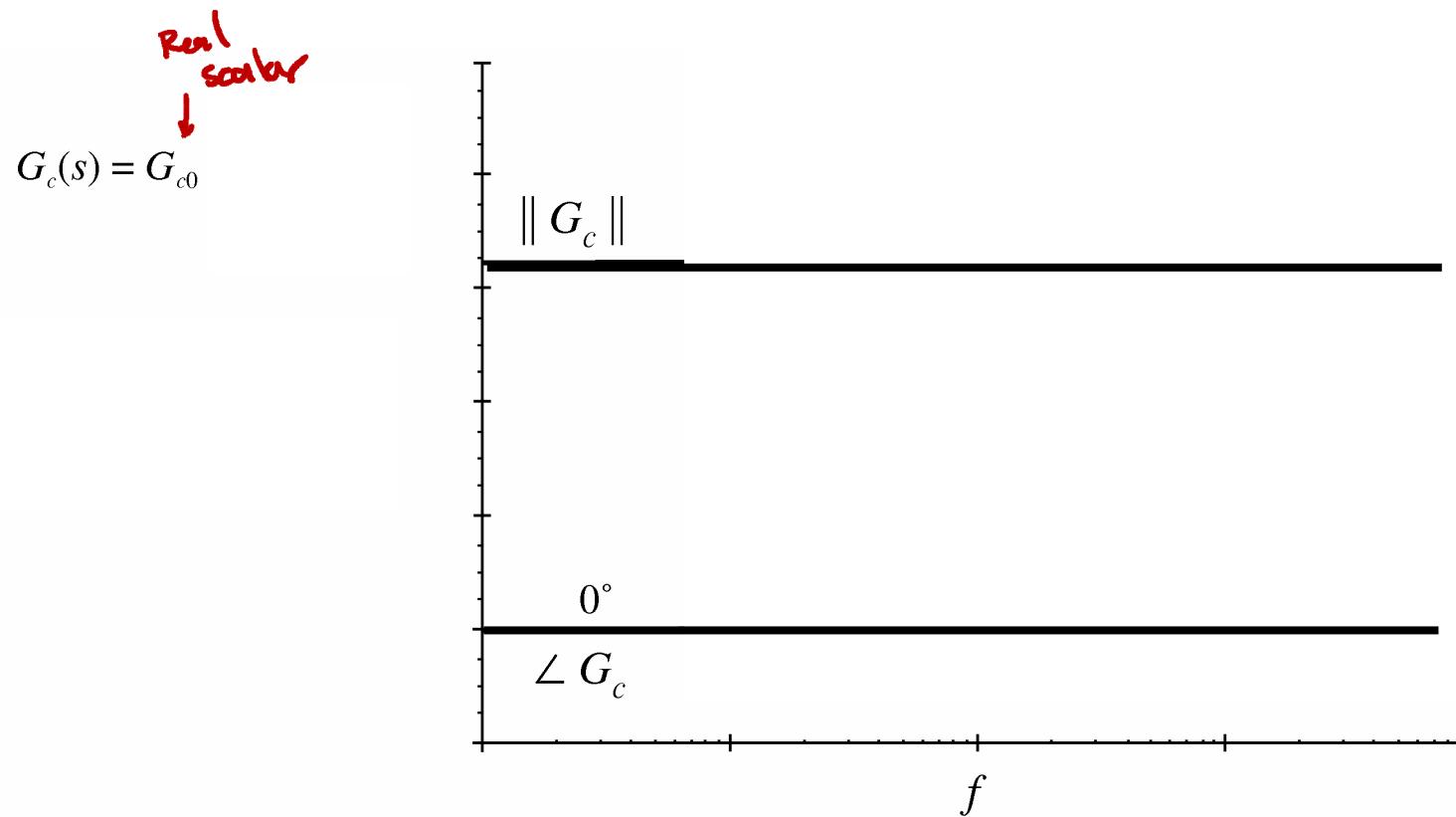


Stabilization by (P) Compensator

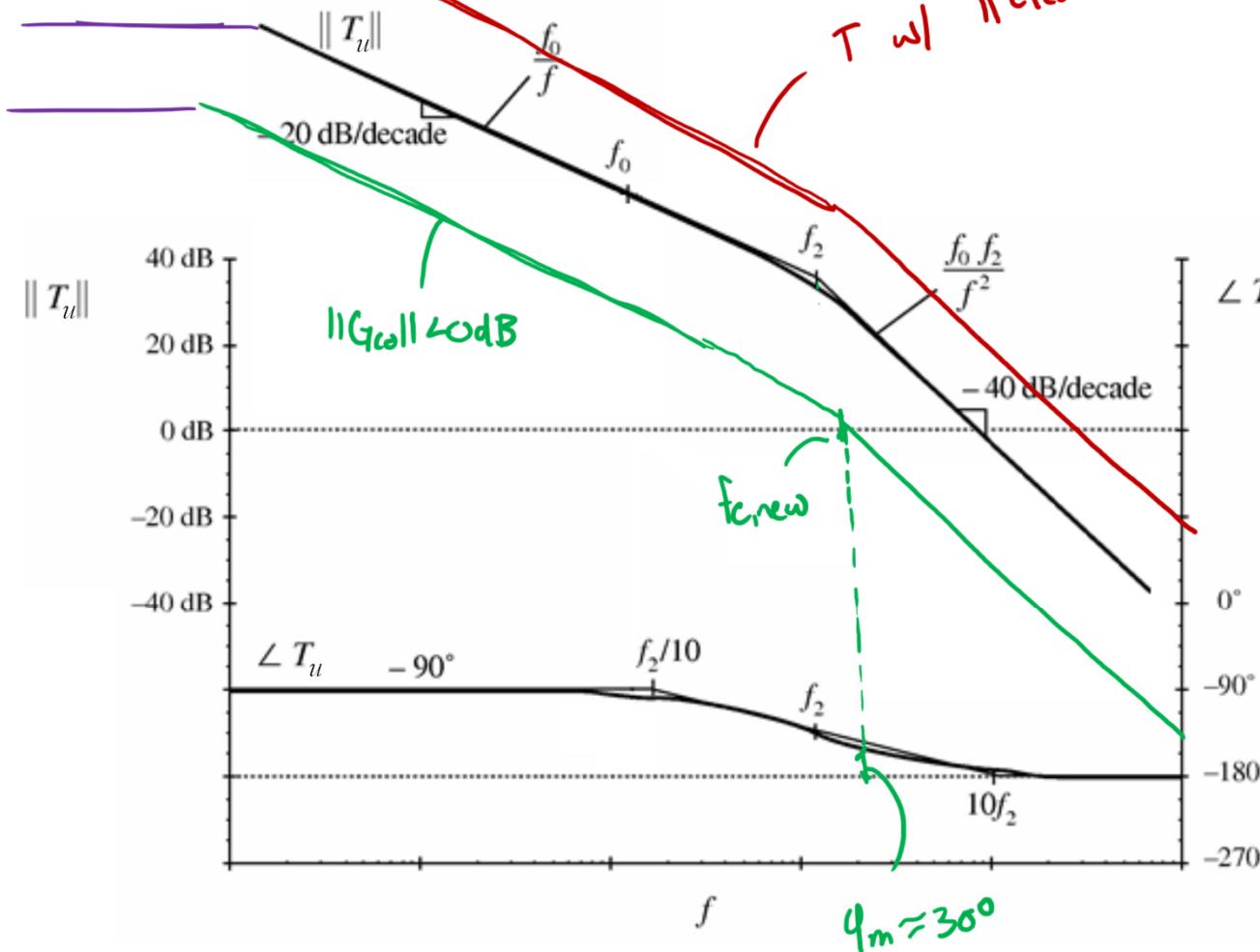

w/ (P) compensator
- shifting curve up &
down
for systems w/ integral
behavior
can ↑ fm at expense
of fc


Another Example

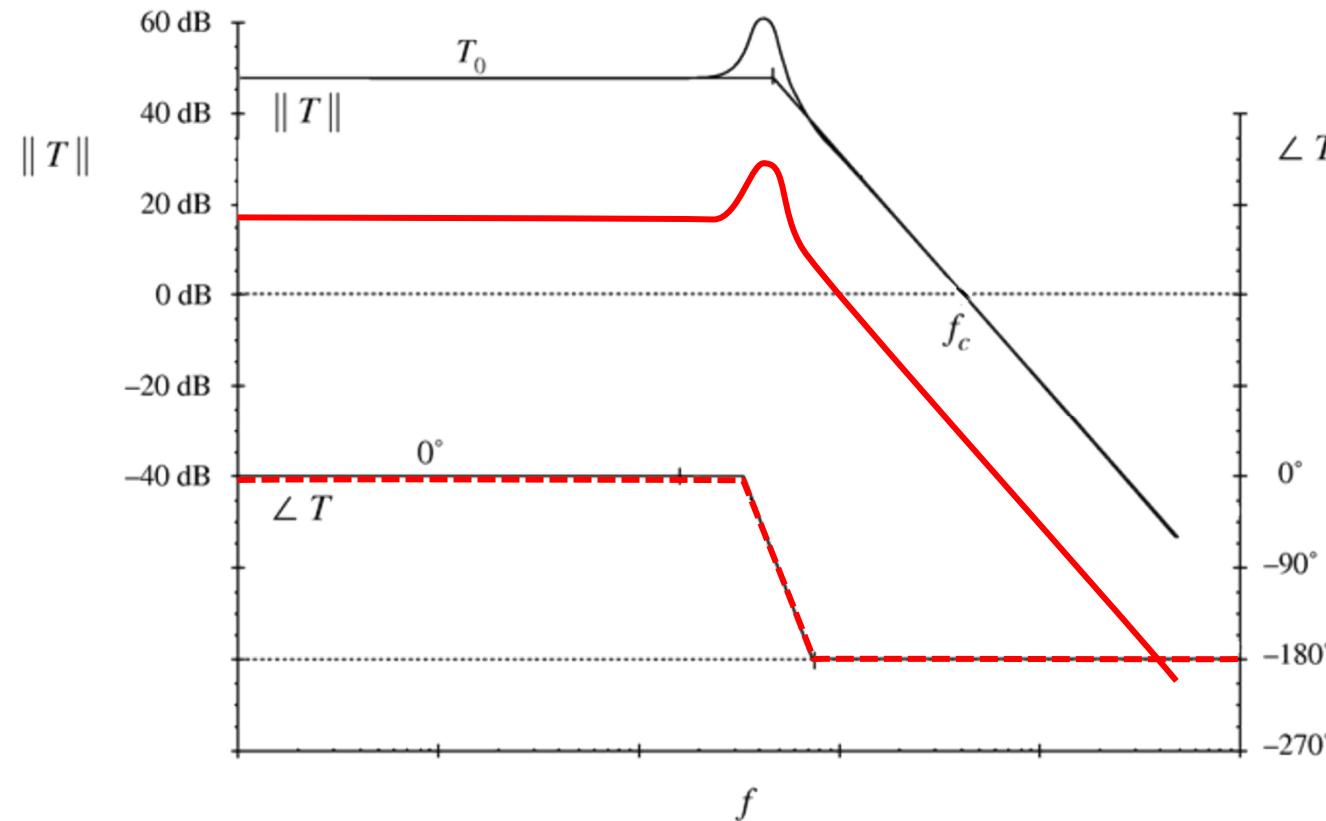


Proportional
compensator
can't fix φ_m
here

Integral (I) Compensator

$$G_c(s) = \frac{K}{s}$$

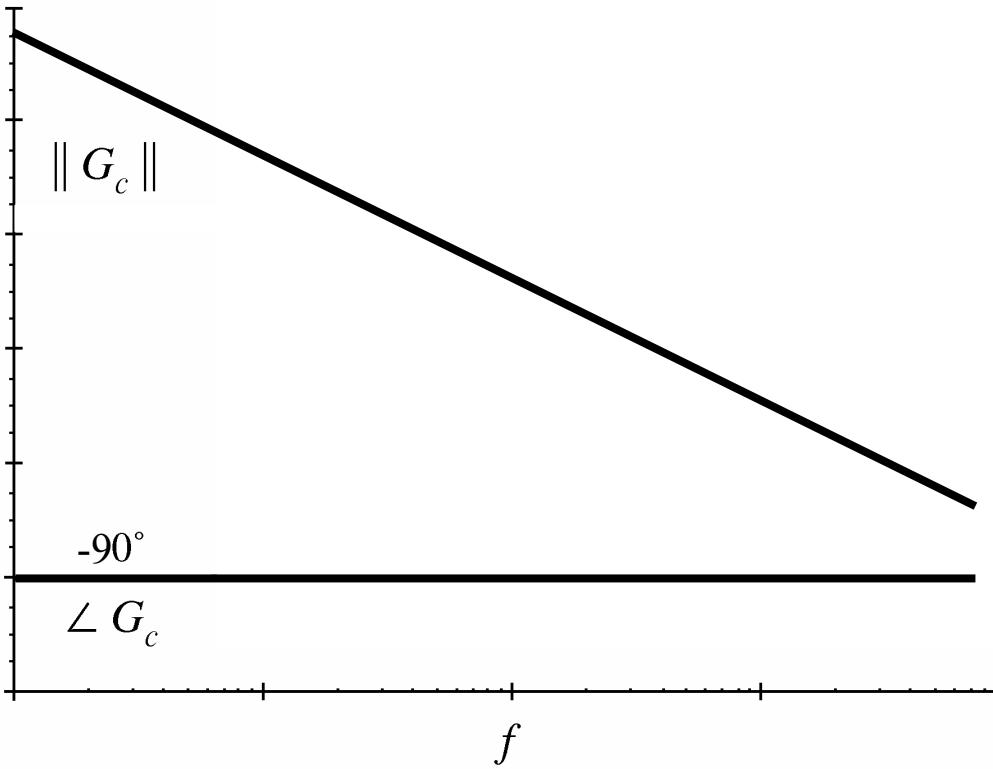


Stabilization by (I) Compensator

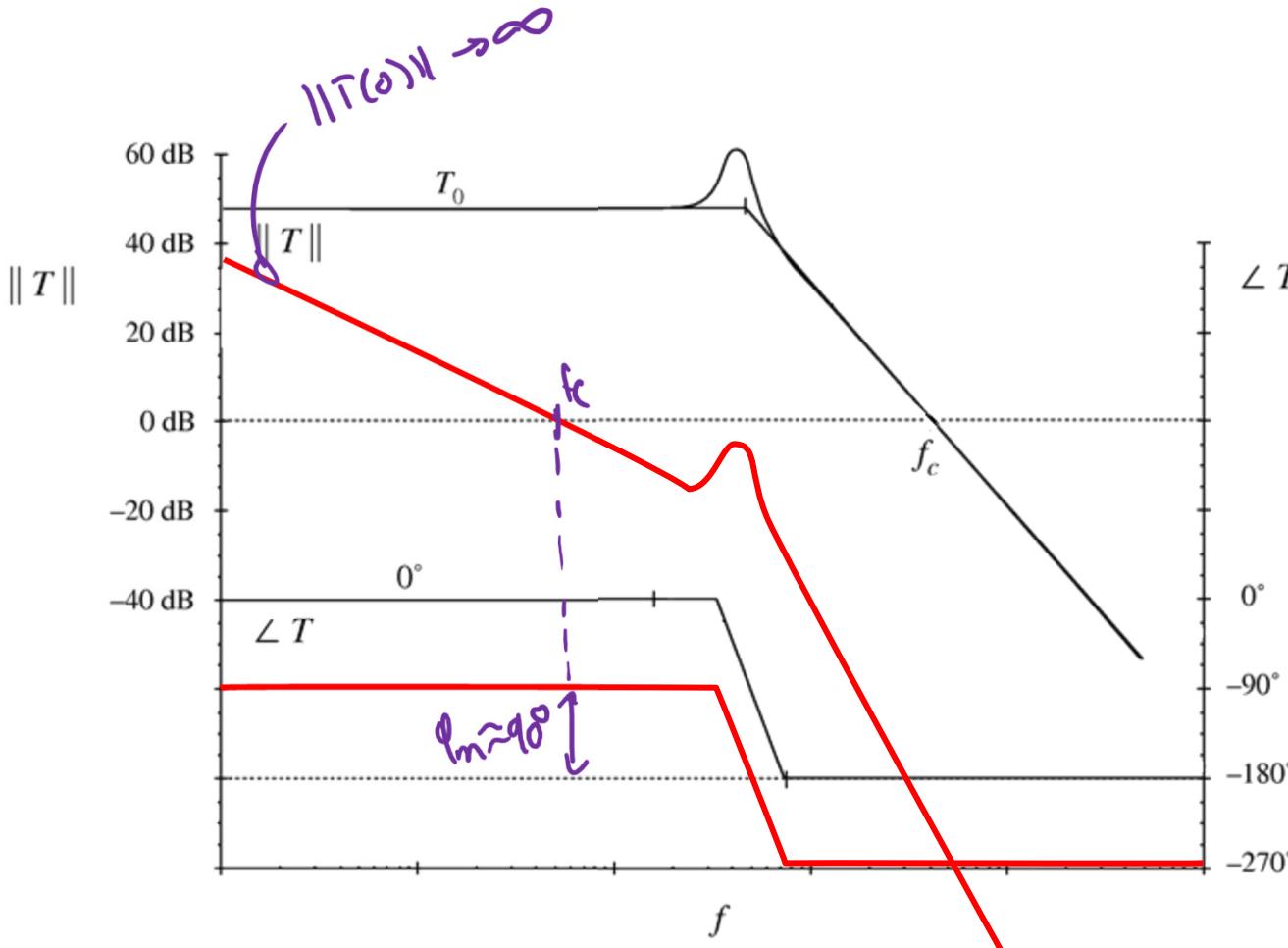


Lag (PI) Compensator

$$G_c(s) = G_{c^\infty} \left(1 + \frac{\omega_L}{s} \right)$$

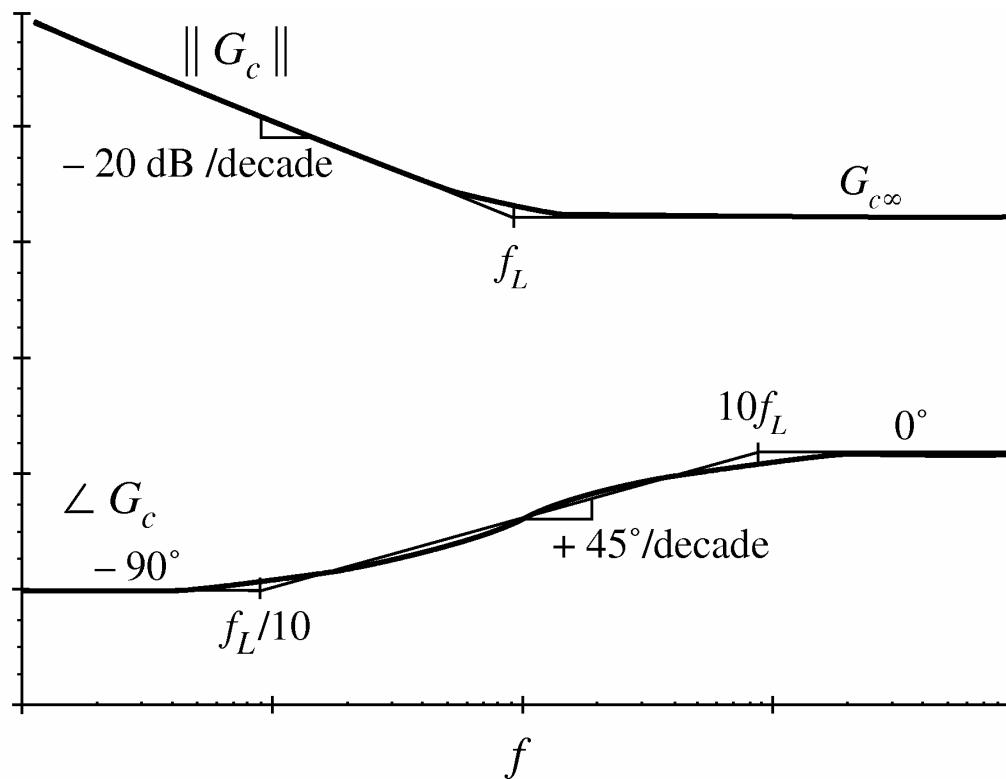Improves low-frequency loop gain and regulation




Stabilization by (PI) Compensator

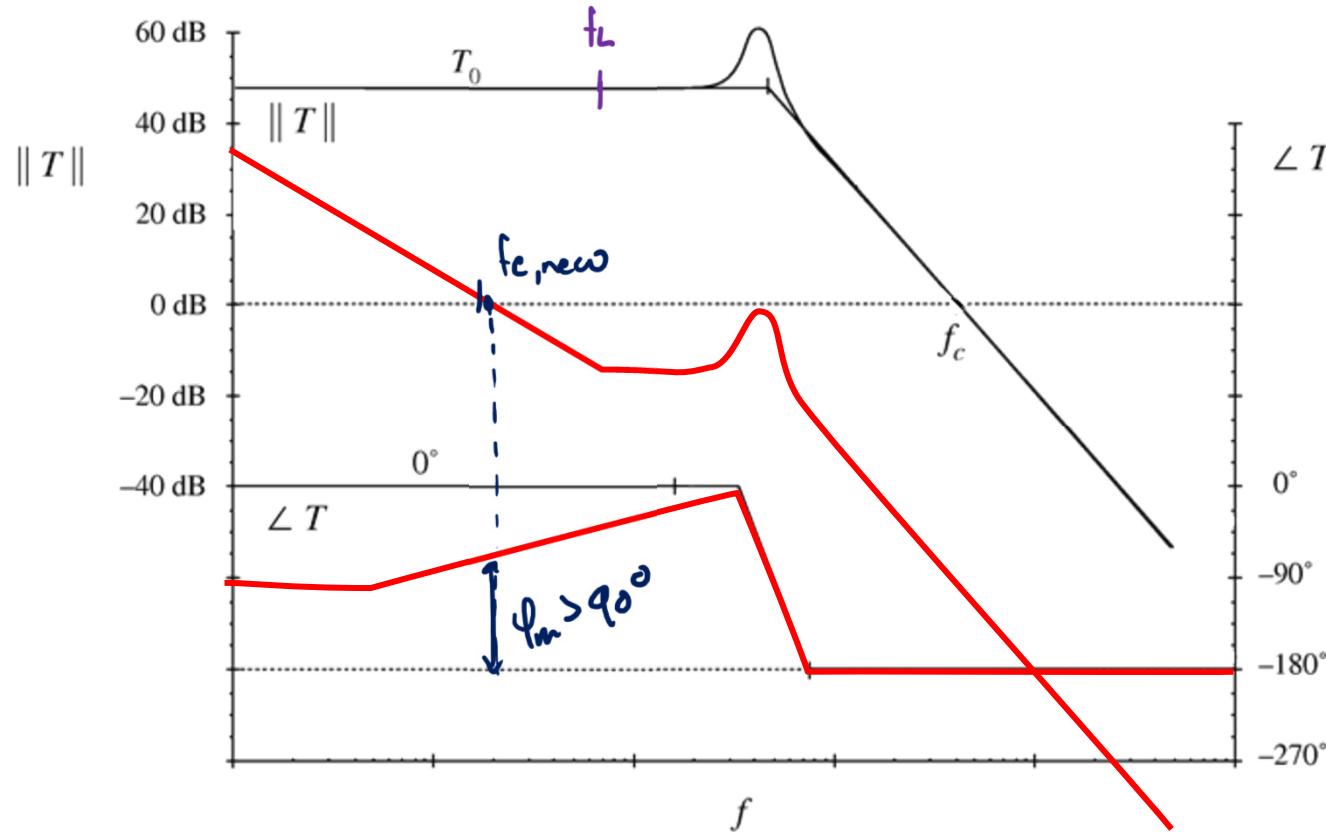


Lead (PD) Compensator

$$G_c(s) = G_{c0} \frac{\left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_p}\right)}$$


Improves phase margin

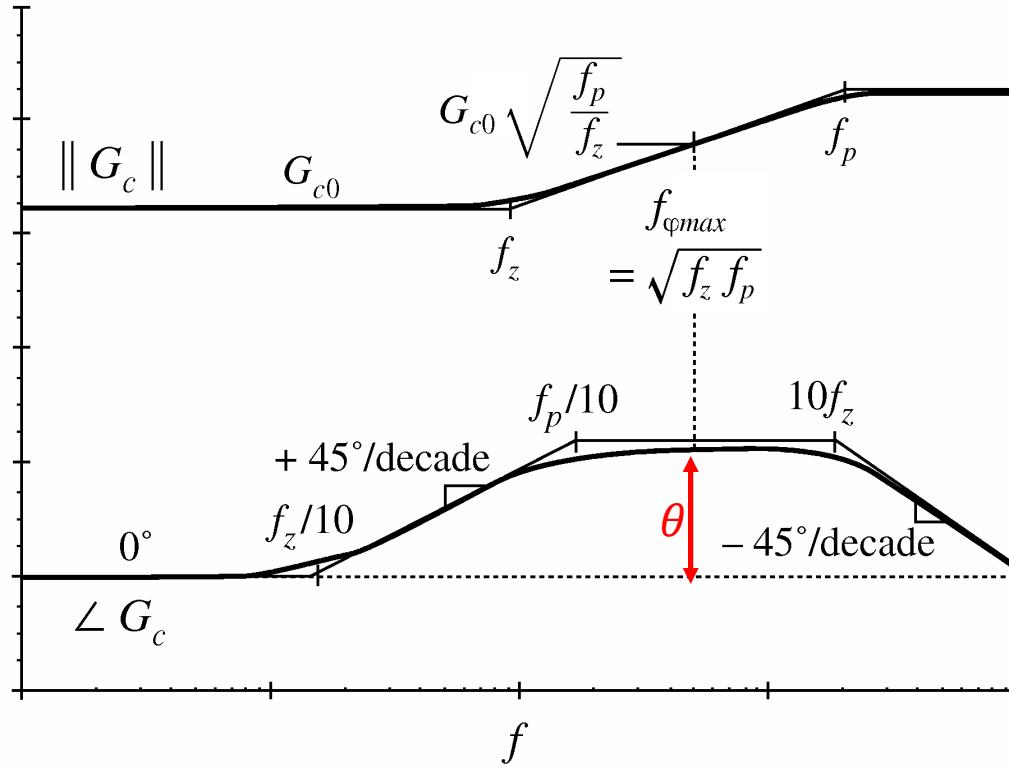

Maximum Phase Lead

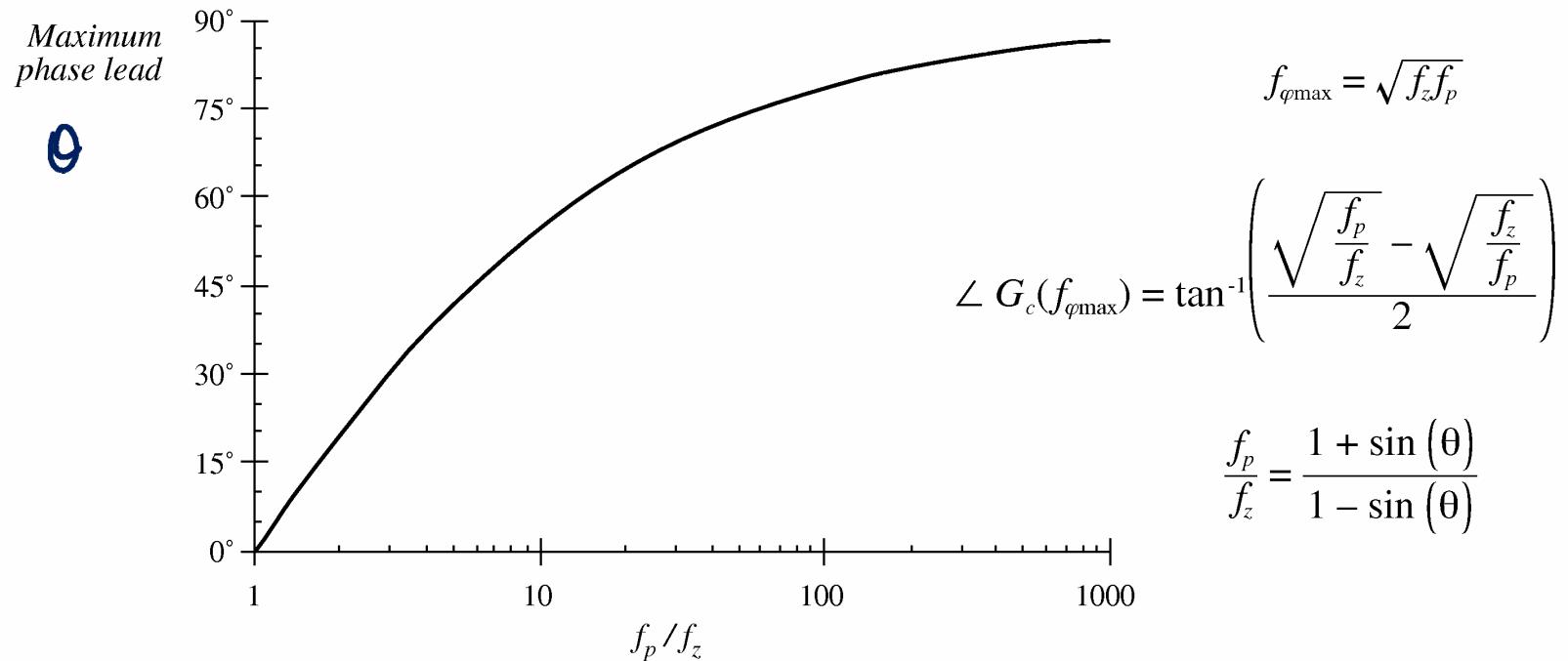

Example Lead Compensator Design

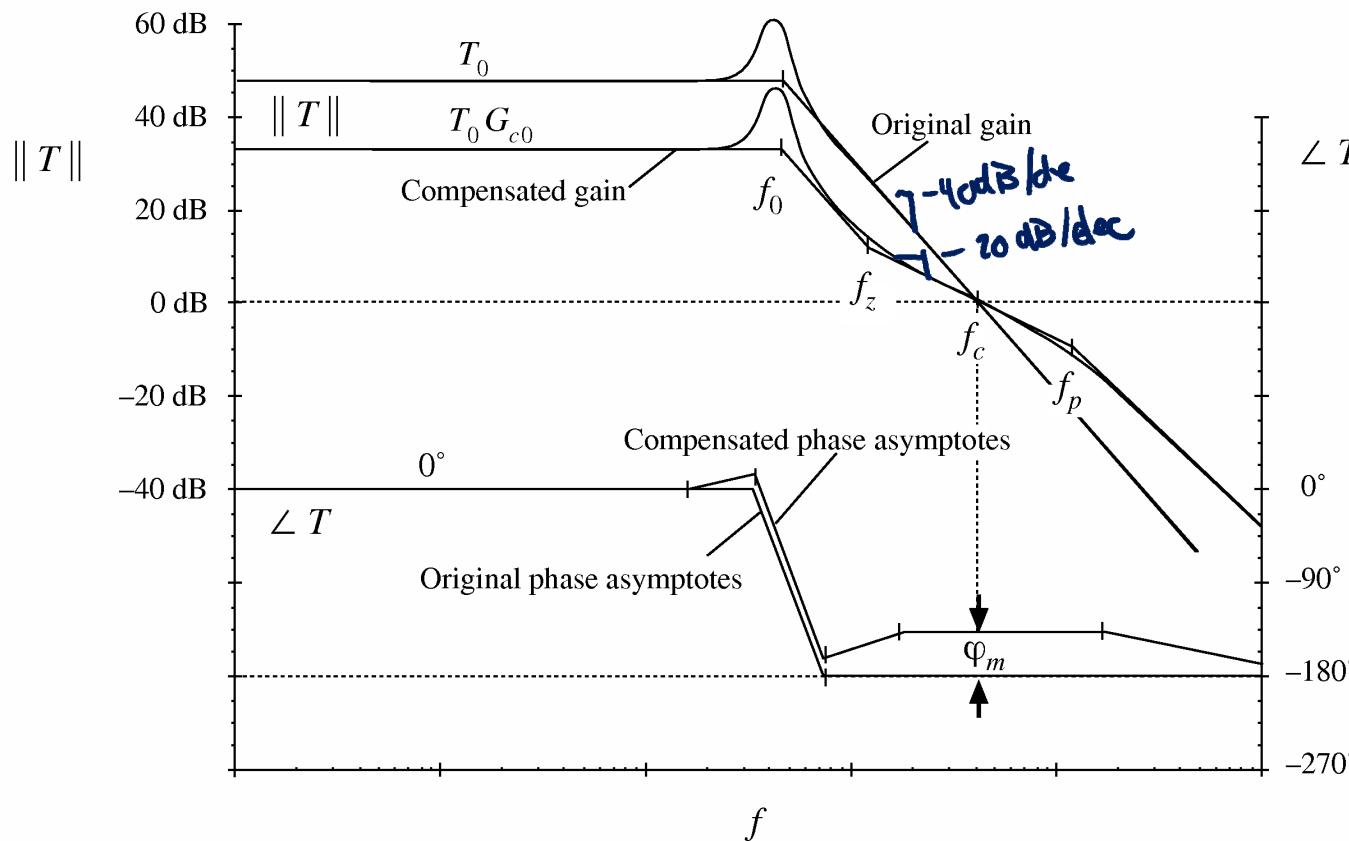

$$f_{\varphi\max} = f_c$$


$$f_z = f_{\varphi\max} \sqrt{\frac{1 - \sin(\theta)}{1 + \sin(\theta)}}$$

$$f_p = f_{\varphi\max} \sqrt{\frac{1 + \sin(\theta)}{1 - \sin(\theta)}}$$


$$G_{c0} = \sqrt{\frac{f_z}{f_p}}$$

to keep f_c

Combined (PID) Compensator

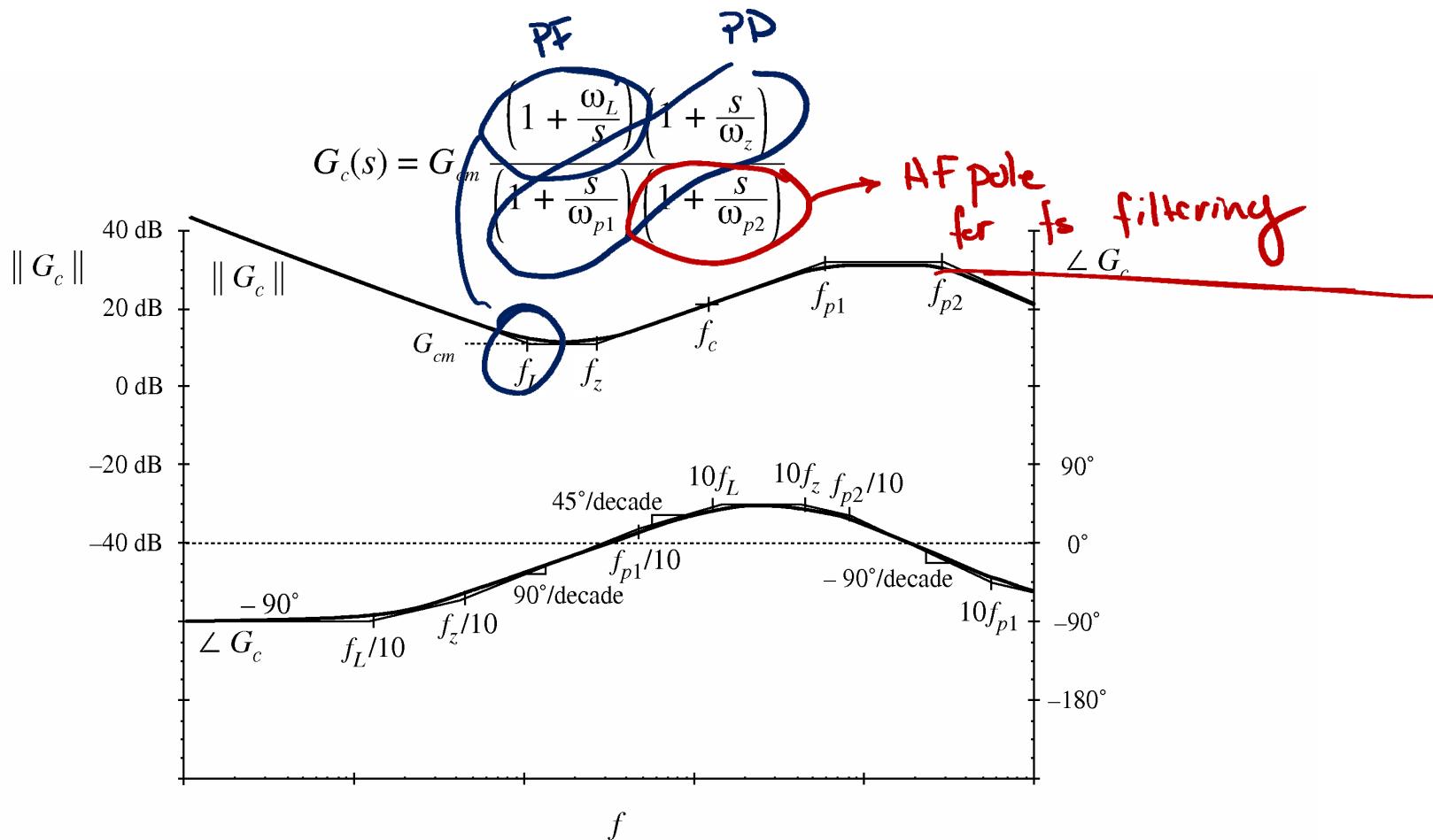

Example Design of Buck Compensator

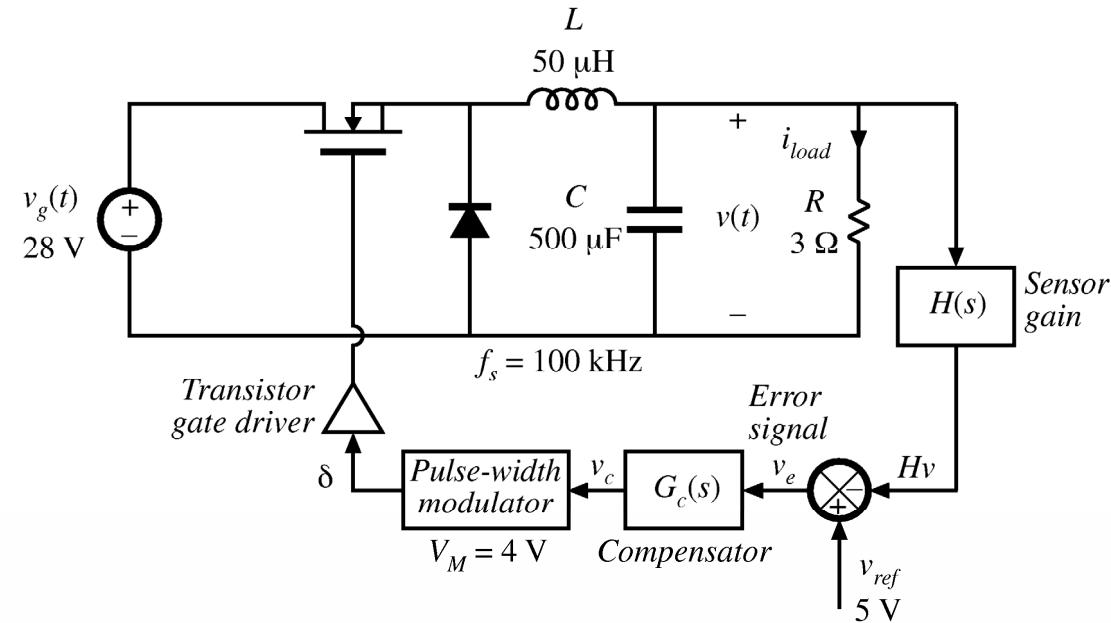

Input voltage

$$V_g = 28\text{V}$$

Output

$$V = 15\text{V}, I_{load} = 5\text{A}, R = 3\Omega$$

Quiescent duty cycle

$$D = 15/28 = 0.536$$

Reference voltage

$$V_{ref} = 5\text{V}$$


Quiescent value of control voltage

$$V_c = DV_M = 2.14\text{V}$$

Gain $H(s)$

$$H = V_{ref}/V = 5/15 = 1/3$$


AC Power Stage Model

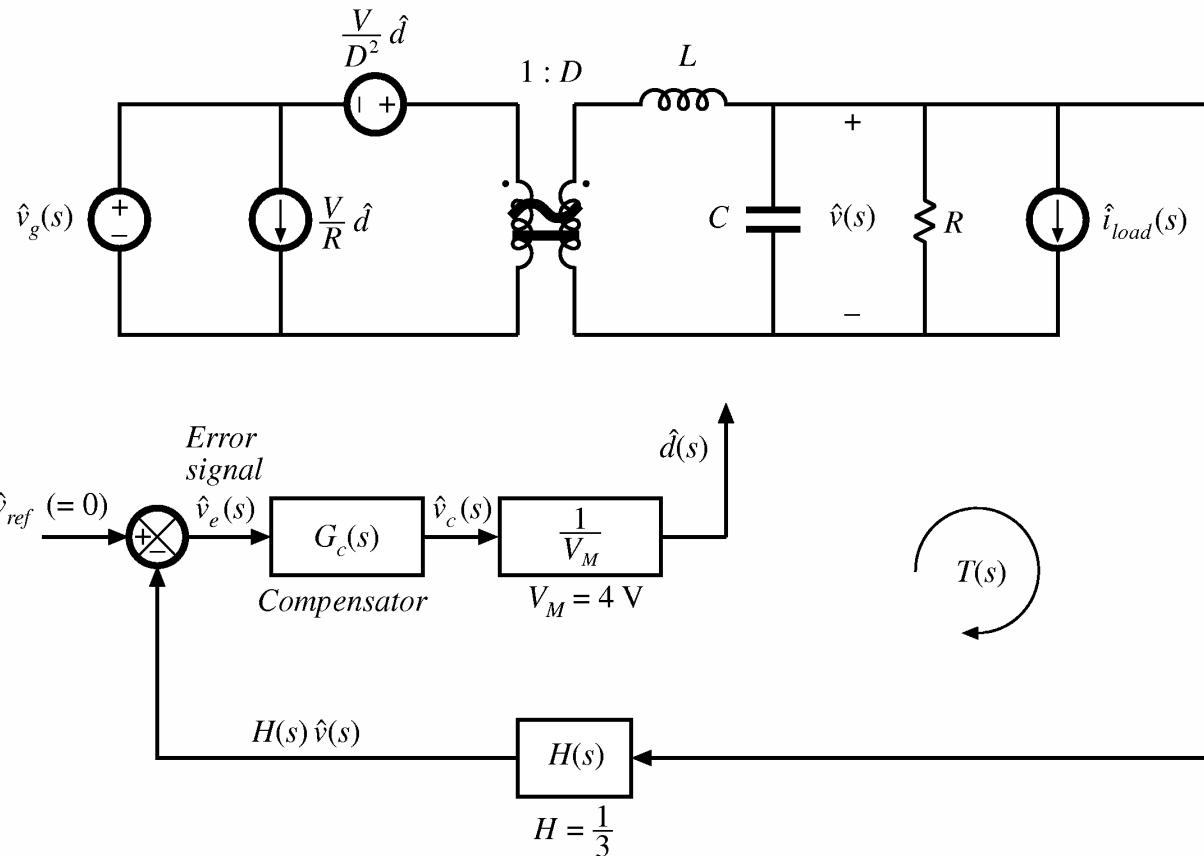

System Block Diagram

$$T(s) = G_c(s) \left(\frac{1}{V_M} \right) G_{vd}(s) H(s)$$
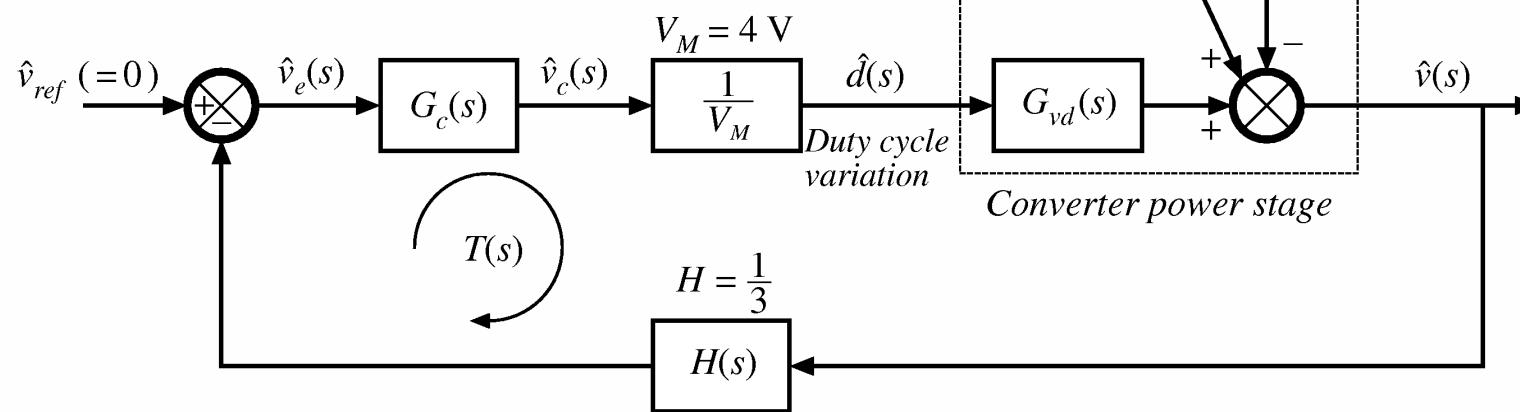
$$T(s) = \frac{G_c(s) H(s)}{V_M} \frac{V}{D} \frac{1}{1 + \frac{s}{Q_0 \omega_0} + \left(\frac{s}{\omega_0} \right)^2}$$




Plotting Uncompensated Loop Gain

With $G_c = 1$, the loop gain is


$$T_u(s) = T_{u0} \frac{1}{1 + \frac{s}{Q_0 \omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$
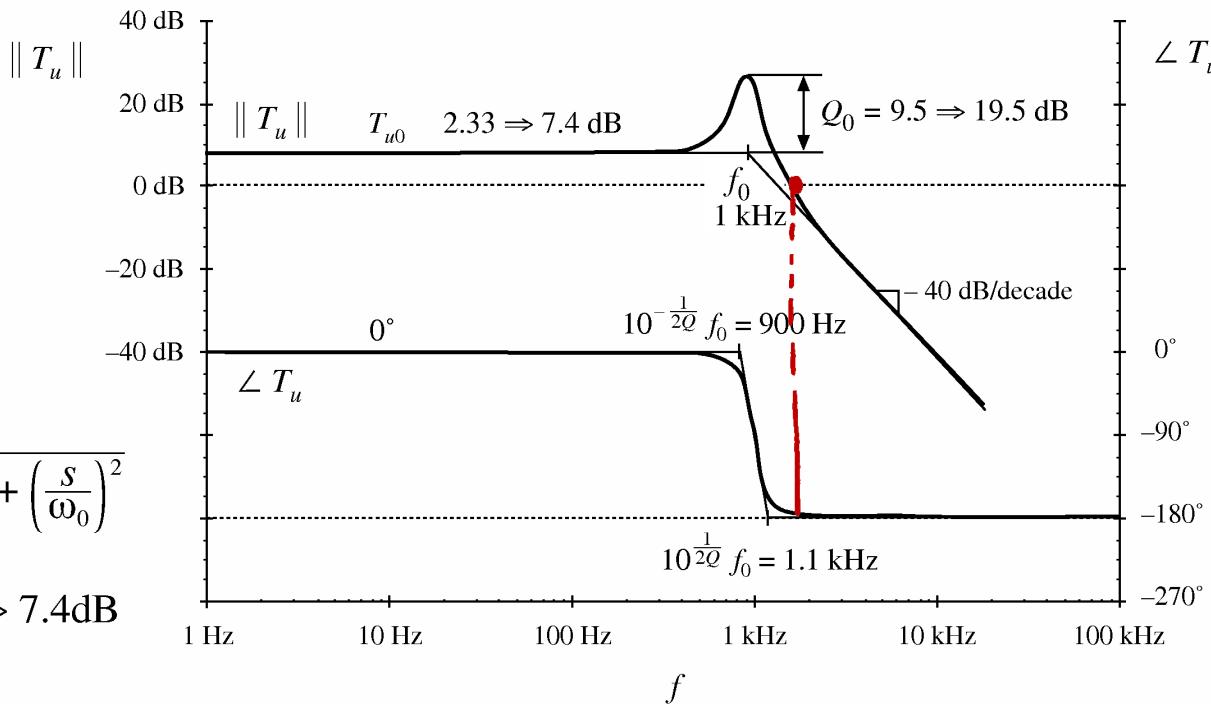
$$T_{u0} = \frac{H V}{D V_M} = 2.33 \Rightarrow 7.4 \text{ dB}$$




$$f_c = 1.8 \text{ kHz}, \varphi_m = 5^\circ$$


LTS spice Simulation – AC, Uncompensated

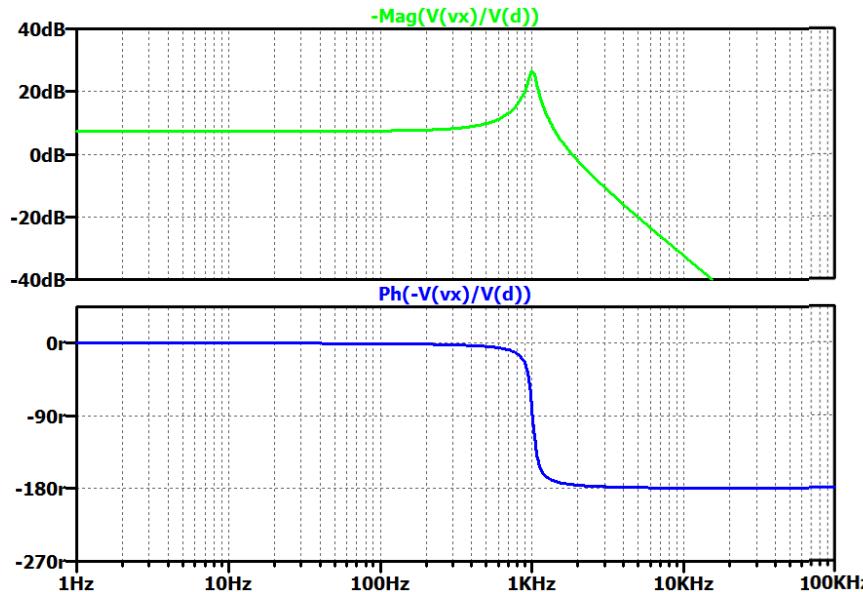
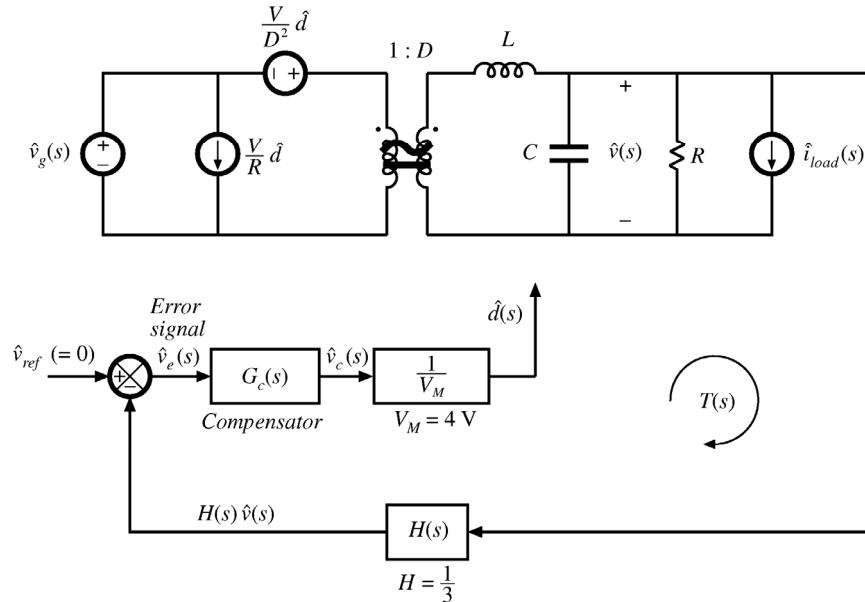
```
.param Vg = 28 V = 15 R = 3 D = .536  
.param Vref = 5 H = 1/3 Vm = 4  
.param L = 50u C = 500u  
.lib myParts.lib  
.ac dec 1000 1 1Meg
```



Transient Simulation, Uncompensated

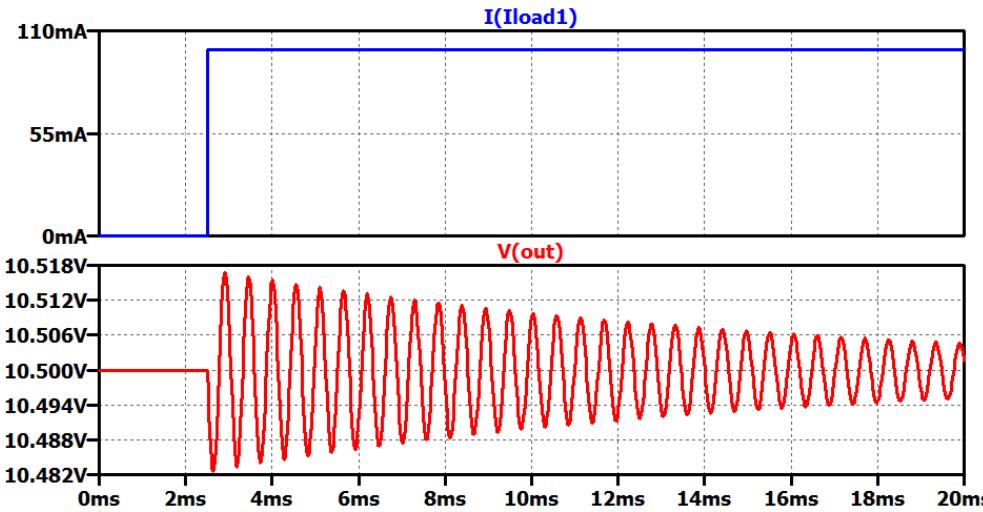

```
.lib switch.lib  
.lib myParts.lib  
.tran 0 20m 3m  
  
.param Vg = 28 V = 15 R = 3 D = .536  
.param Vref = 5 H = 1/3 Vm = 4  
.param L = 50u C = 500u  
  
.jc V(out) = 15 I(L1) = 5 V(vc) = {D*Vm}
```

