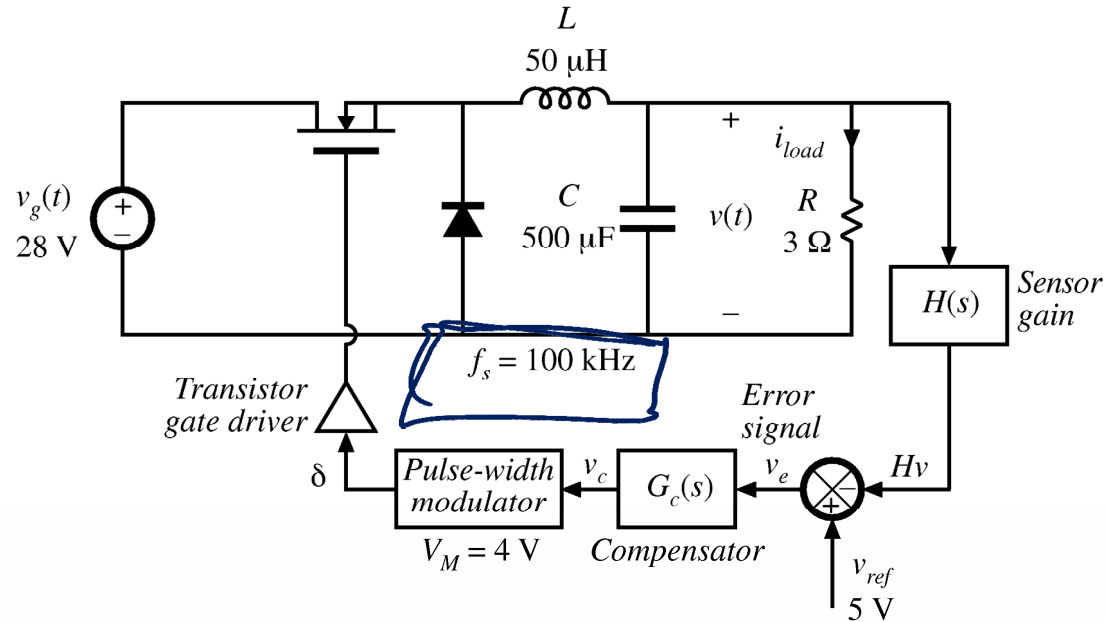


Example Design of Buck Compensator



Input voltage

$$V_g = 28\text{V}$$

Output

$$V = 15\text{V}, I_{load} = 5\text{A}, R = 3\ \Omega$$

Quiescent duty cycle

$$D = 15/28 = 0.536$$

Reference voltage

$$V_{ref} = 5\text{V}$$

Quiescent value of control voltage


$$V_c = DV_M = 2.14\text{V}$$

Gain $H(s)$

$$H = V_{ref}/V = 5/15 = 1/3$$

AC Power Stage Model

Table 7.1

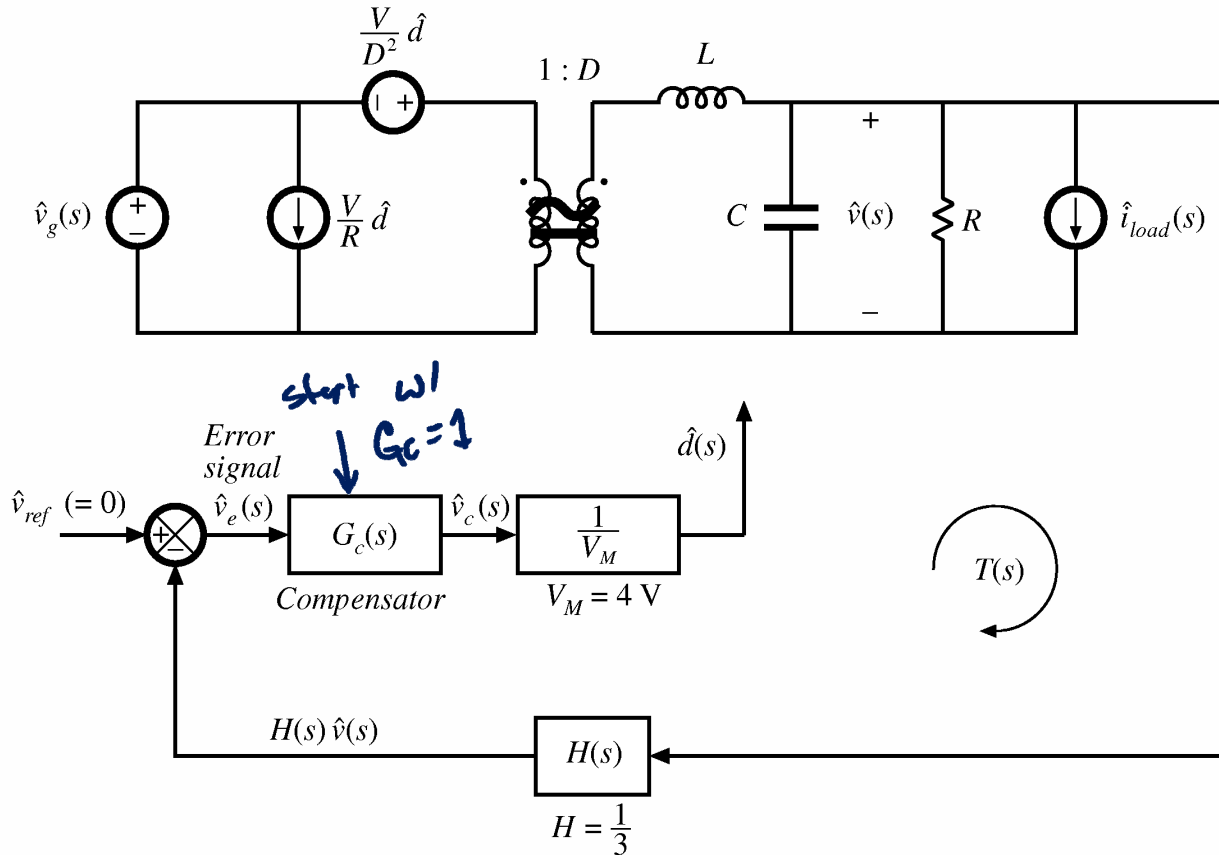

System Block Diagram


$$\hat{v} = \frac{1}{H} \frac{T}{1+T} \hat{v}_{ref} + \frac{1}{1+T} G_{vg} \hat{v}_g - \frac{1}{1+T} Z_{out} \hat{i}_{load}$$

"Uncompensated loop gain"

$$T_u(s) = 1 \cdot \frac{1}{V_M} G_{vd}(s) H(s)$$

$$T(s) = G_c(s) \left(\frac{1}{V_M} \right) G_{vd}(s) H(s)$$
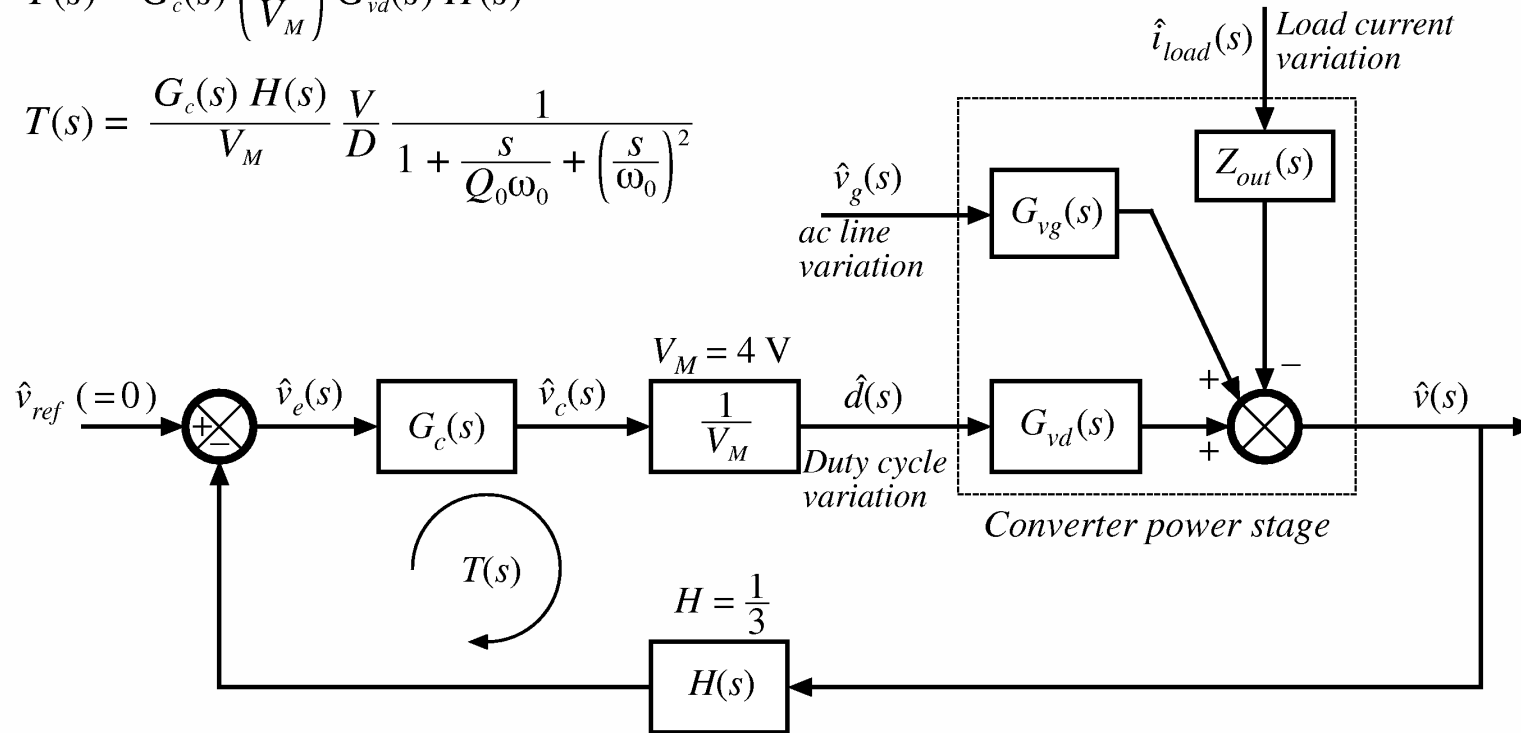
$$T(s) = \frac{G_c(s) H(s)}{V_M} \frac{V}{D} \frac{1}{1 + \frac{s}{Q_0 \omega_0} + \left(\frac{s}{\omega_0} \right)^2}$$




Plotting Uncompensated Loop Gain

- (1) $T(0)$ is too small \rightarrow will have significant steady-state error
- (2) $\phi_m = 5^\circ$ is too small \rightarrow lots of ringing/overshoot & risk of instability
- (3) $f_c = 1.8 \text{ kHz} \approx \text{ok}$
 can push further to $\frac{f_s}{10} = 10 \text{ kHz}$

With $G_c = 1$, the loop gain is


$$T_u(s) = T_{u0} \frac{1}{1 + \frac{s}{Q_0 \omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$
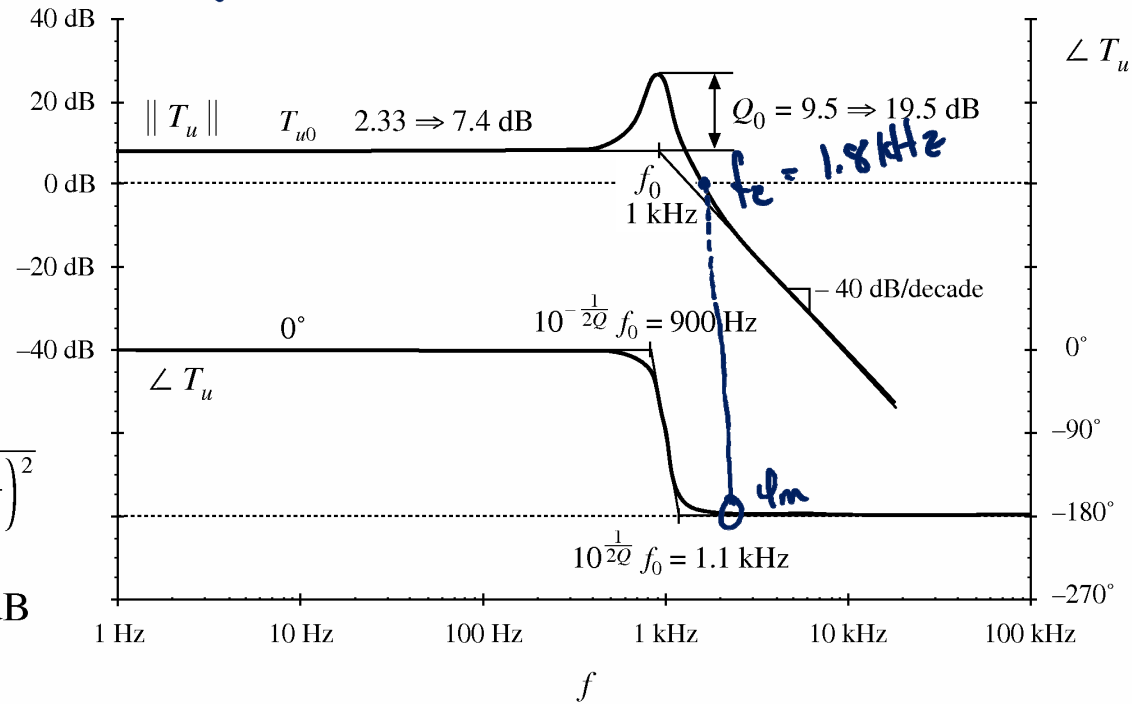
$$T_{u0} = \frac{H V}{D V_M} = 2.33 \Rightarrow 7.4 \text{ dB}$$




$f_c = 1.8 \text{ kHz}$, $\phi_m = 5^\circ$

LTSpice Simulation – AC, Uncompensated

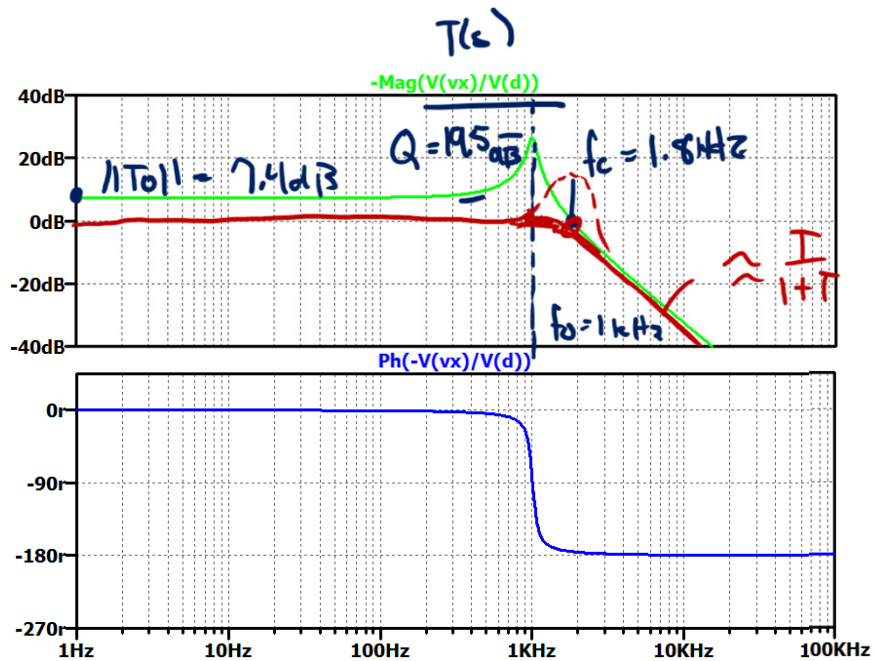

```

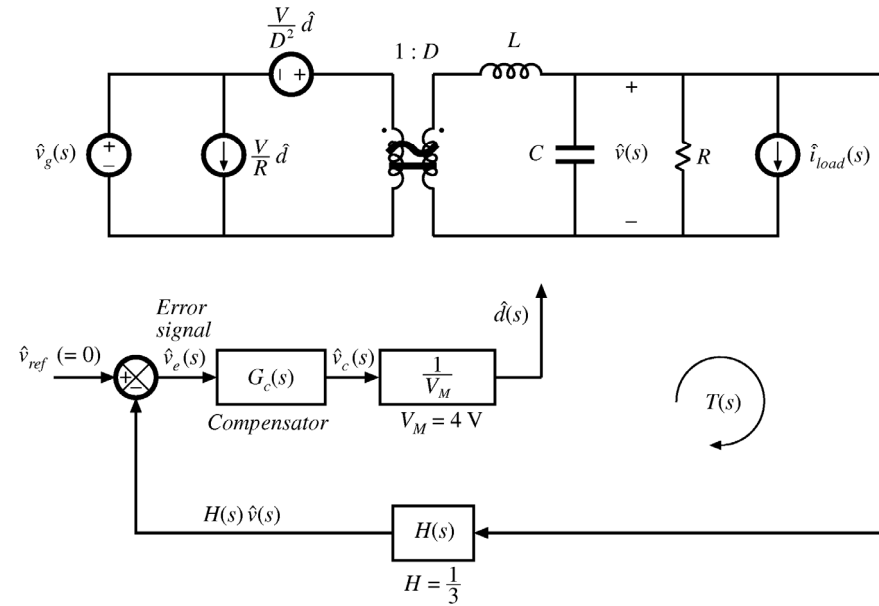.param Vg = 28 V = 15 R = 3 D = .536
.param Vref = 5 H = 1/3 Vm = 4
.param L = 50u C = 500u
.lib myParts.lib
.ac dec 1000 1 1Meg
    
```



LTSpice ac Simulations


usually, run a .op first to make sure LTSpice finds the correct operating point, then run .ac

$$T = -\frac{V(vx)}{V(d)}$$

Averaged, linearized

```
.lib myParts.lib
.ac dec 1000 1 1Meg
```
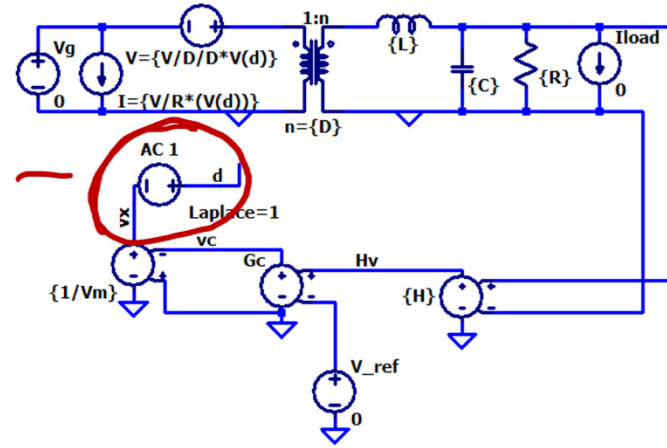
```
.param Vg = 28 V = 15 R = 3 D = .536
.param Vref = 5 H = 1/3 Vm = 4
.param L = 50u C = 500u
```




Averaged mode 1



```
.lib switch.lib
.lib myParts.lib
.tran 0 20m 3m
```

```
.param Vg = 28 V = 15 R = 3 D = .536
.param Vref = 5 H = 1/3 Vm = 4
.param L = 50u C = 500u
```
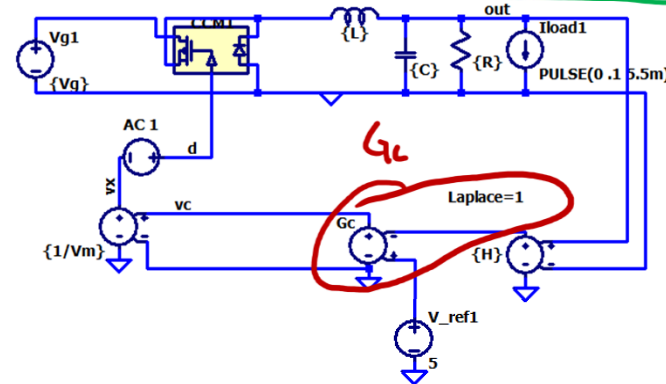
```
.ic V(out) = 15 I(L1) = 5 V(vc) = {D*Vm}
```




Model Simulation (L24)

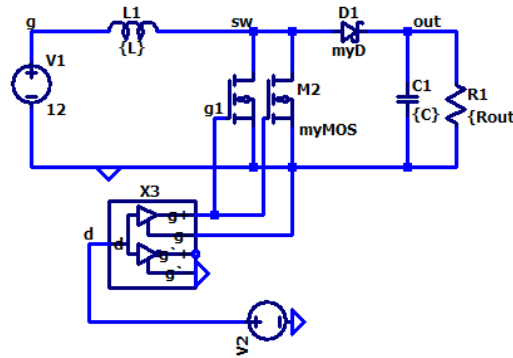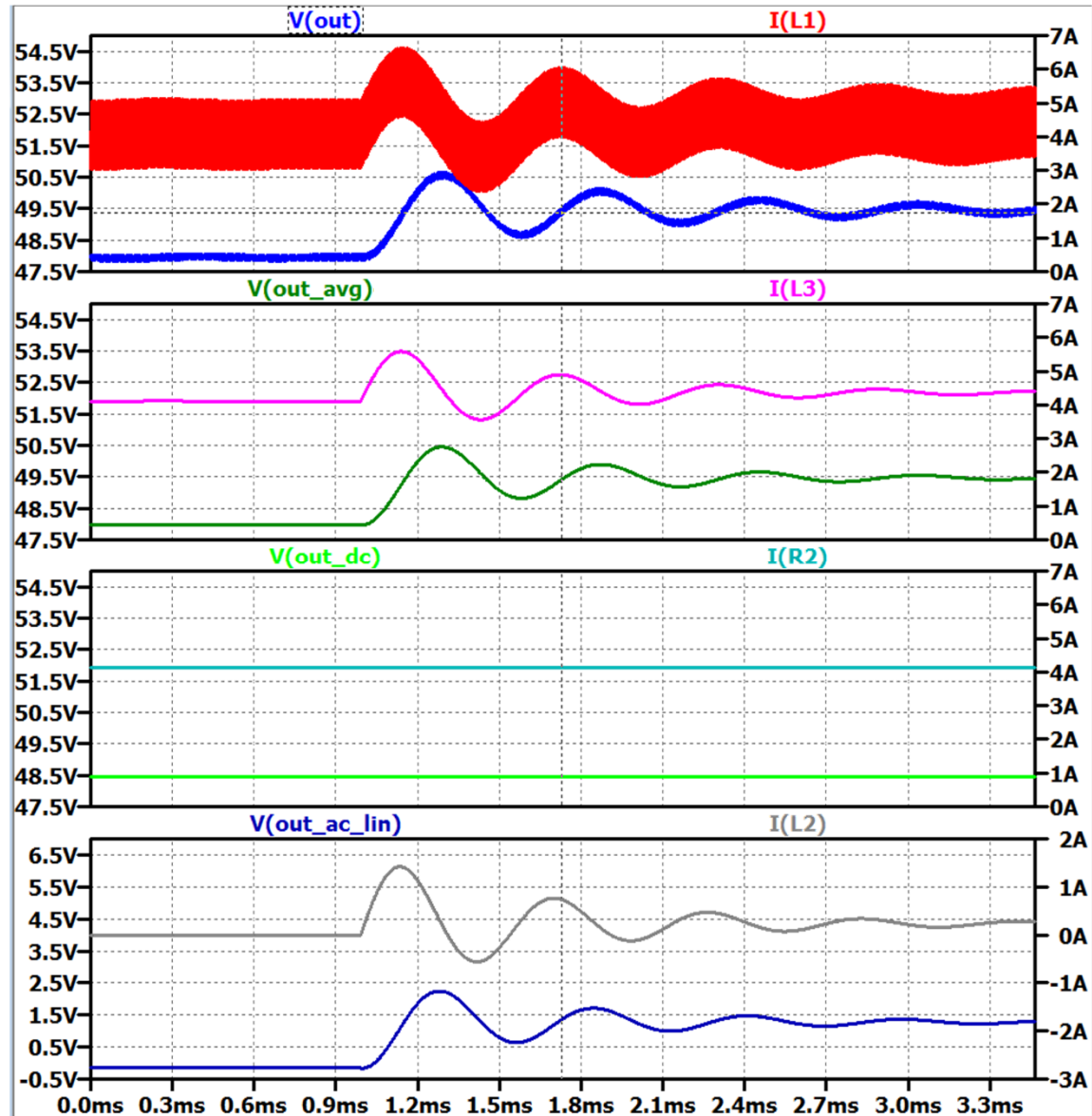

```
.param
+ L = 22u
+ C = 22u
+ Rout = 48
+ D = .755
```


```
.ic V(out)=48 I(L1)=3.1A
.tran 0 {1500/202k} {800/202k} startup
.lib myParts.lib
```

only transient sims
Full Switching Model

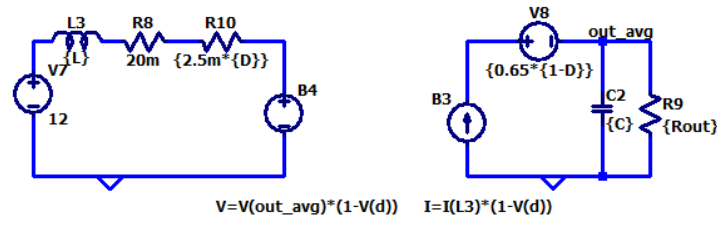


```
.ic V(out_avg)=48 I(L3)=4A
```

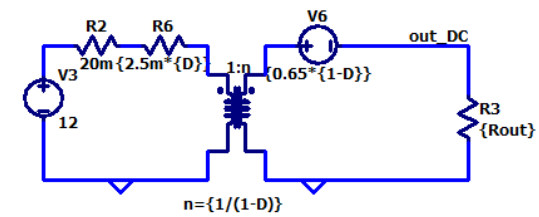ac, transient .op simulation
Averaged, Nonlinear




DC Averaged Model

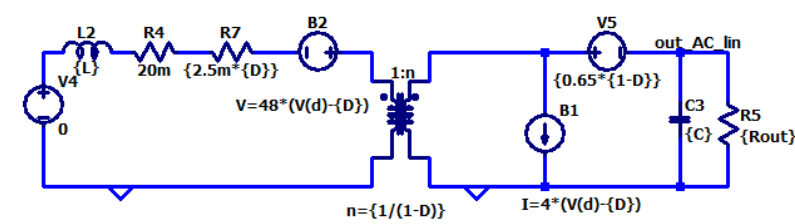

ac, transient .op all ac
AC Averaged, Linearized Model

Transient Simulation, Uncompensated

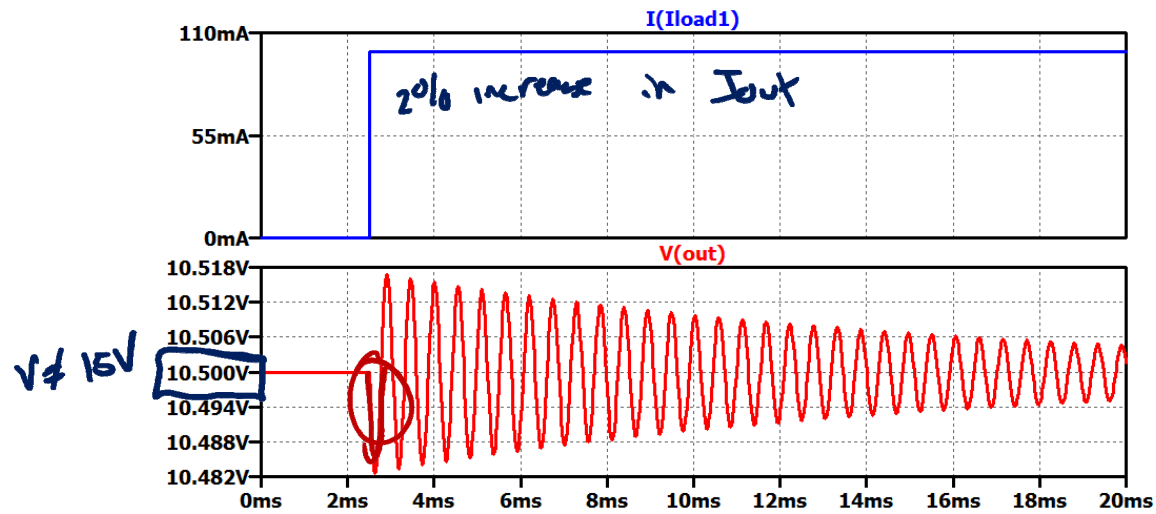


$$V_{ref} \frac{1}{H} \frac{11T_{OH}}{1 + 11T_{OH}} = (15V) \frac{2.33}{1 + 2.33} = 10.5V$$


```
.lib switch.lib
.lib myParts.lib
.tran 0 20m 3m
```

```
.param Vg = 28 V = 15 R = 3 D = .536
.param Vref = 5 H = 1/3 Vm = 4
.param L = 50u C = 500u
```
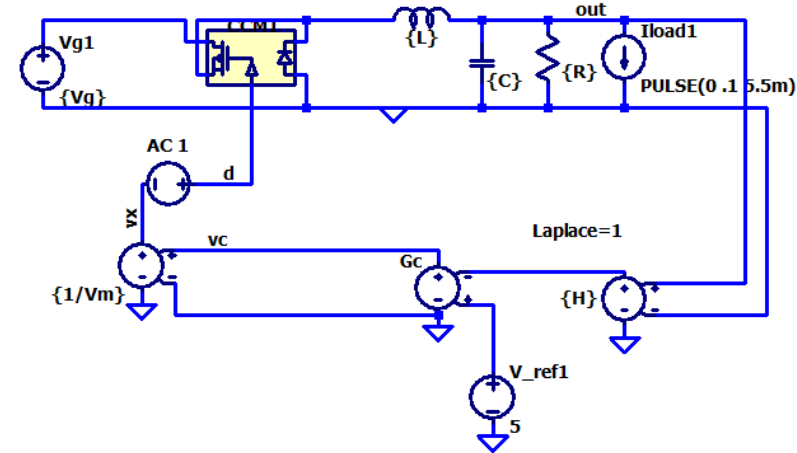
```
.ic V(out) = 15 I(L1) = 5 V(vc) = {D*Vm}
```



Ringing Frequency

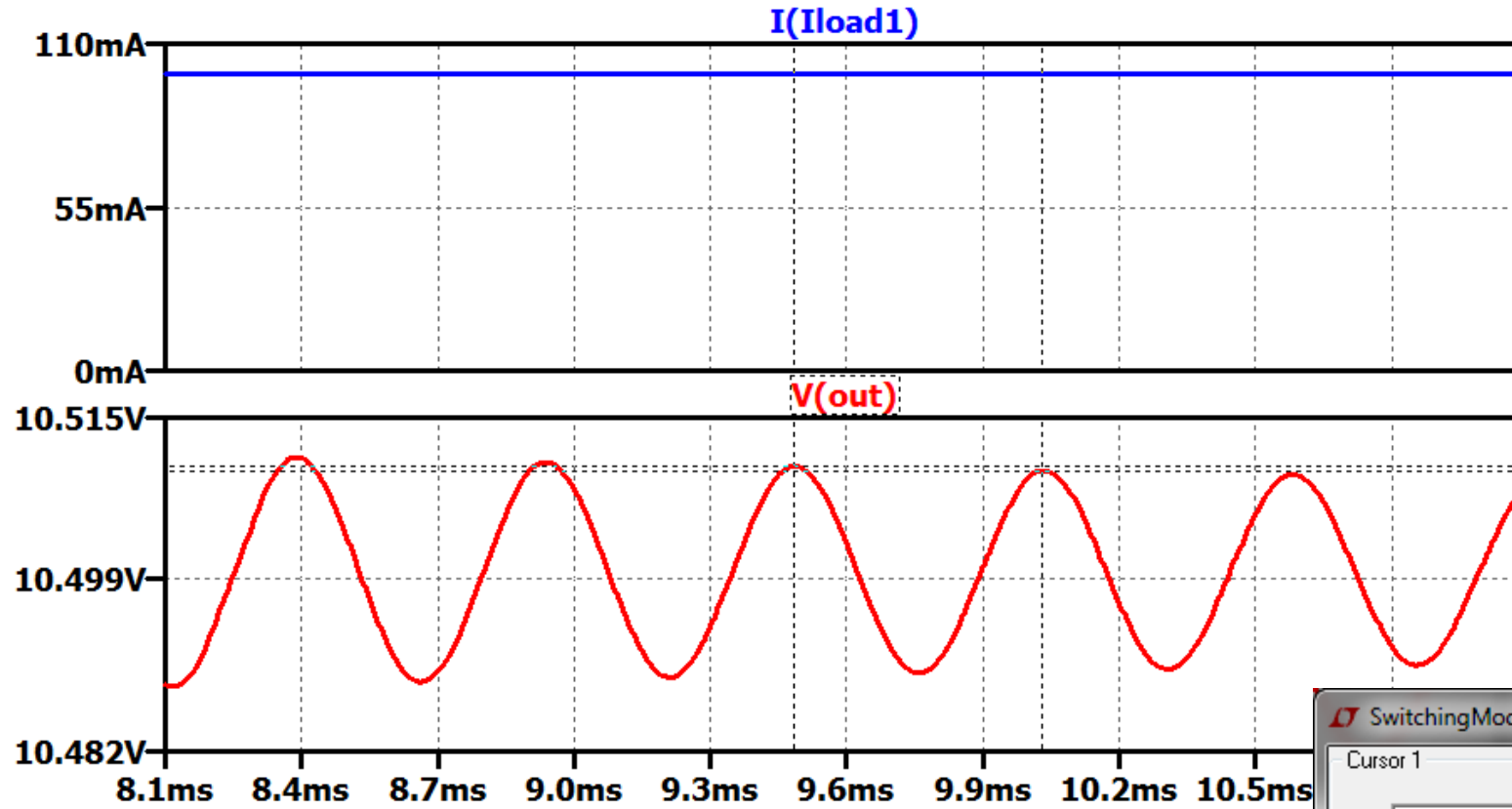


SwitchingModel.raw

Cursor 1	
V(out)	
Horz: 9.4837638ms	Vert: 10.510181V
Cursor 2	
V(out)	
Horz: 10.029889ms	Vert: 10.509752V
Diff (Cursor2 - Cursor1)	
Horz: 546.12546μs	Vert: -429.27875μV
Freq: 1.8310811KHz	Slope: -0.786044

$1.8\text{kHz} = f_c$

$$T/(1+T)$$

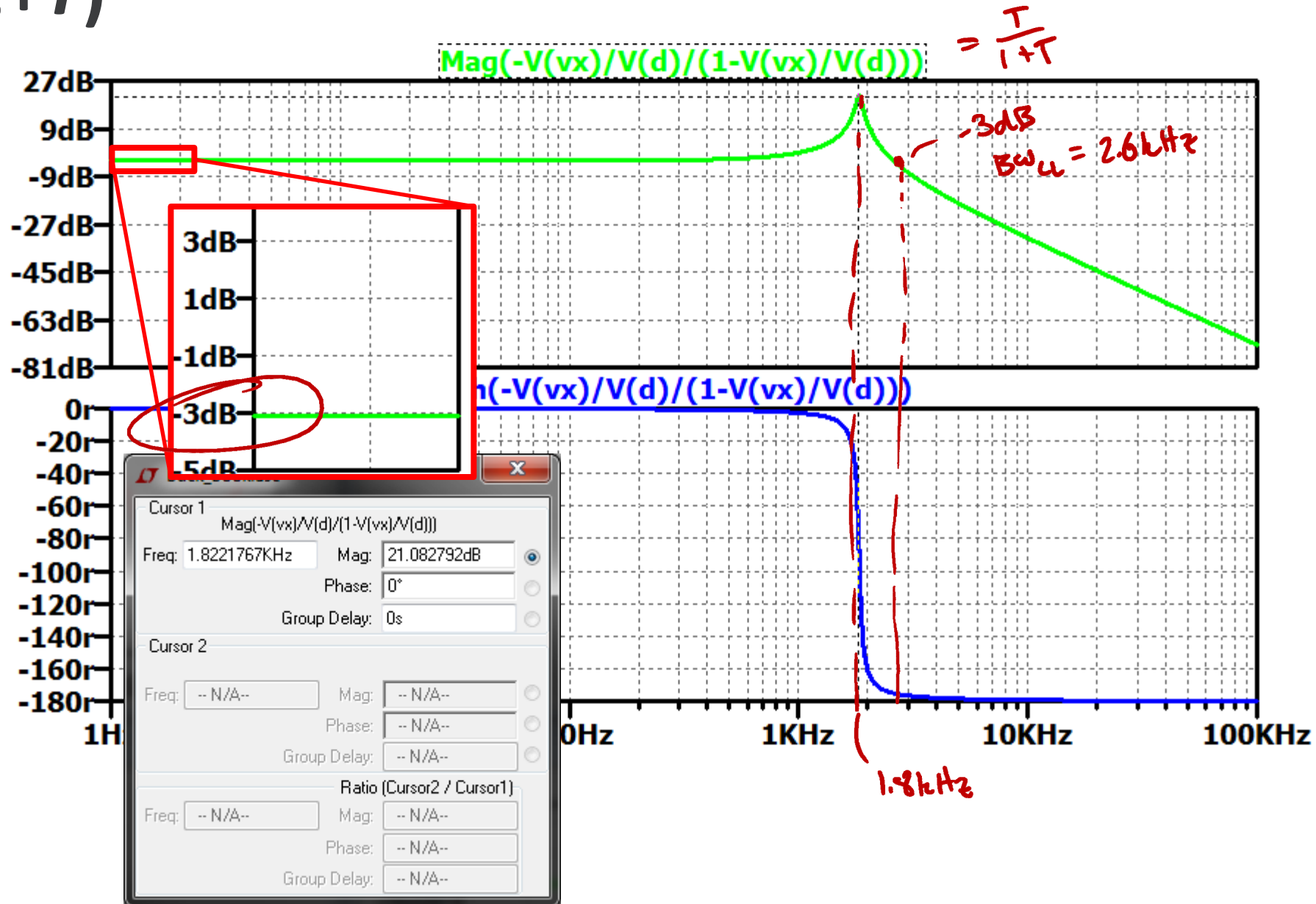


Summary: Uncompensated Behavior

- Significant steady-state error
 - Need to increase low-frequency gain
- Barely stable; significant ringing
 - Need to increase ϕ_m
- Speed: ~ok
 - $f_c = 1.8$ kHz
 - $(BW)_{CL} = 2.6$ kHz
 - OK for $f_s \approx 10$ kHz or above

Compensator Design

- As an example, try to
 - Increase f_c to 10 kHz = $\frac{fs}{10}$
 - Increase ϕ_m to 76° ($Q_{CL}=0.5$) \rightarrow No ringing
 - Increase $\|T_0\|$ to ∞ \rightarrow zero steady-state error
- Note: Book Chooses $f_c = 5$ kHz and $\phi_m = 52^\circ$ ($Q=1$)


PI Design

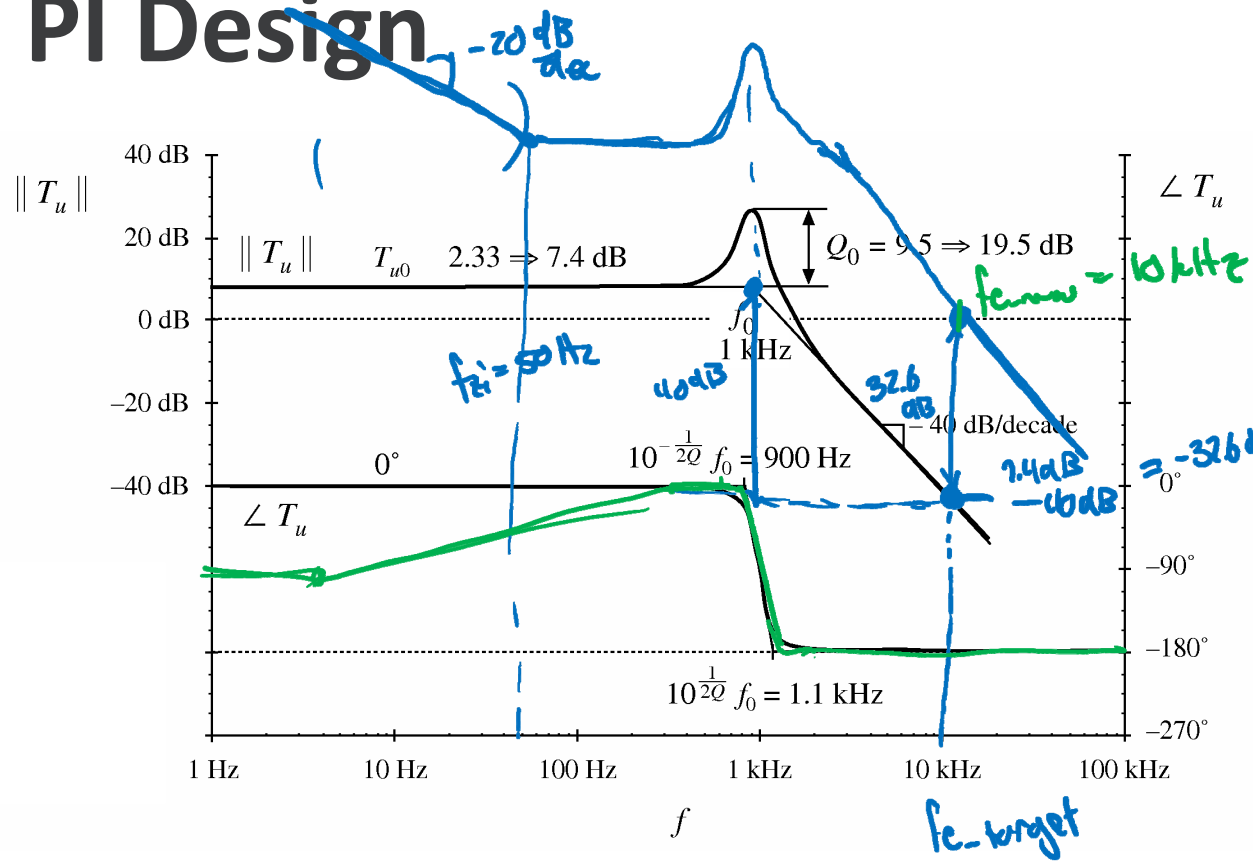

set G_{c0} to $37.6 \text{ dB} = 42.6$ to move f_c to 10 kHz
 & set $f_{zi} = 50 \text{ Hz}$



Design PI to give
 (1) $f_c = 10 \text{ kHz} \rightarrow$ use G_{c0} to move f_c
 (2) $\|T_o\| \rightarrow \infty \rightarrow$ Inherent
 (3) Not significantly hurt $\phi_m \rightarrow t_{zi} \ll \frac{f_c}{10}$
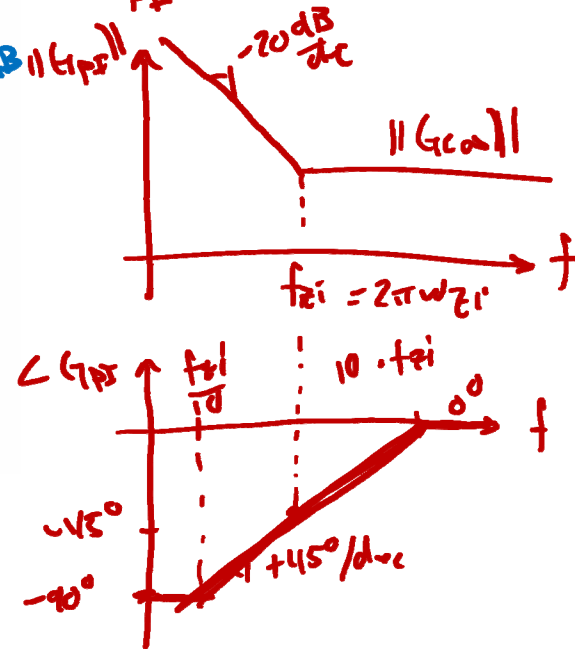
$$G_{PI}(s) = G_{c0} \left(1 + \frac{\omega_{zi}}{s} \right)$$




$$G_{PI} = 42.6 \left(1 + \frac{20s}{s} \right)$$

PI Simulation

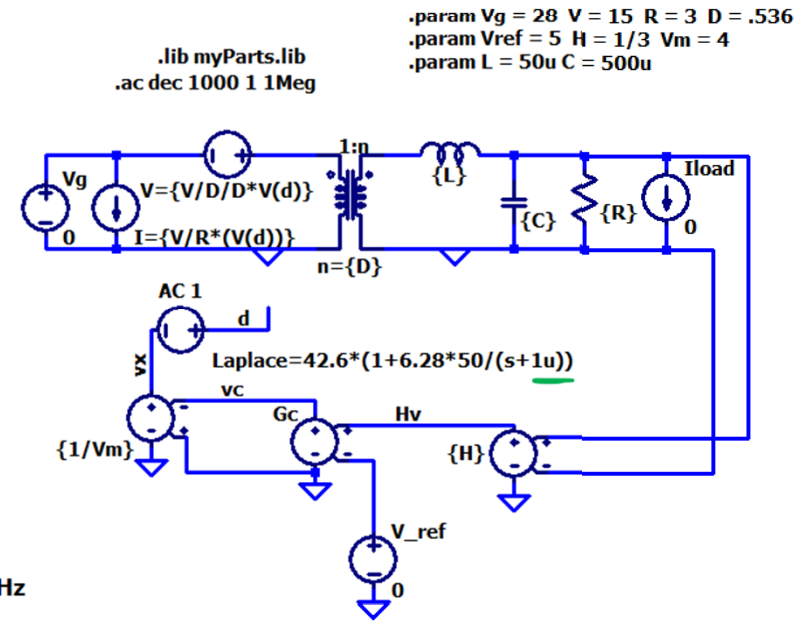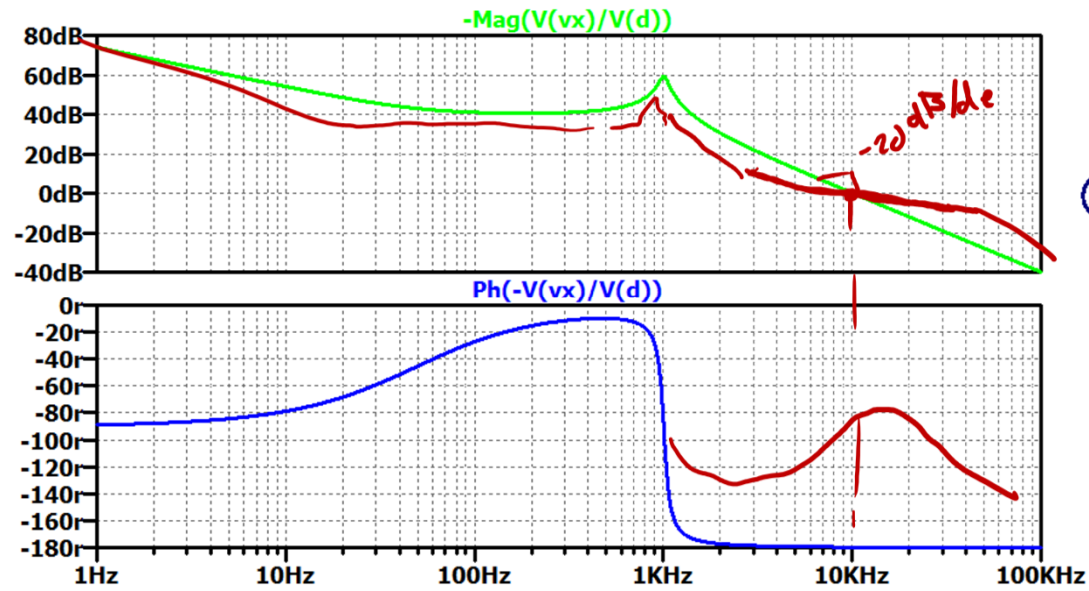

PI Transient Simulation

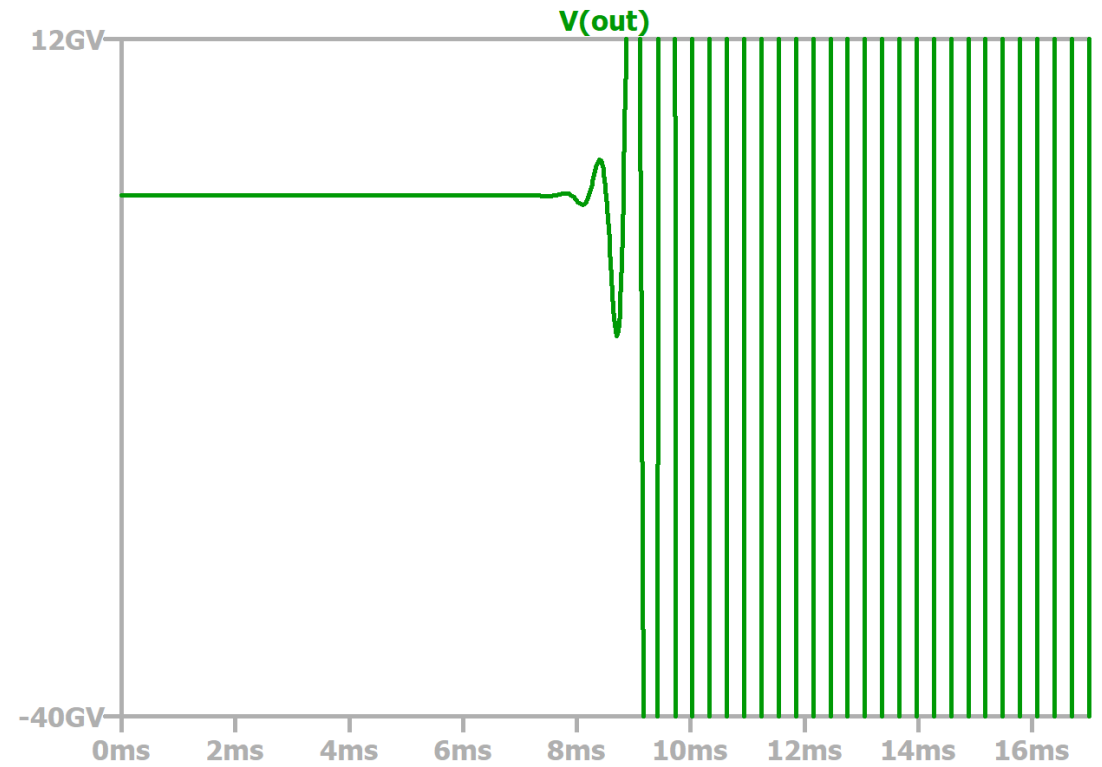

PD Design

$$f_z = f_c \sqrt{\frac{1 - \sin(\theta)}{1 + \sin(\theta)}}$$


$$f_p = f_c \sqrt{\frac{1 + \sin(\theta)}{1 - \sin(\theta)}}$$

$$G_{c0} = \sqrt{\frac{f_z}{f_p}}$$

Design: wanted $\phi_m = 76^\circ$
currently have $\phi_m = 0^\circ$
 \hookrightarrow set $\theta = 76^\circ$


$$G_{PD} = G_{c0} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}}$$

PID Simulation

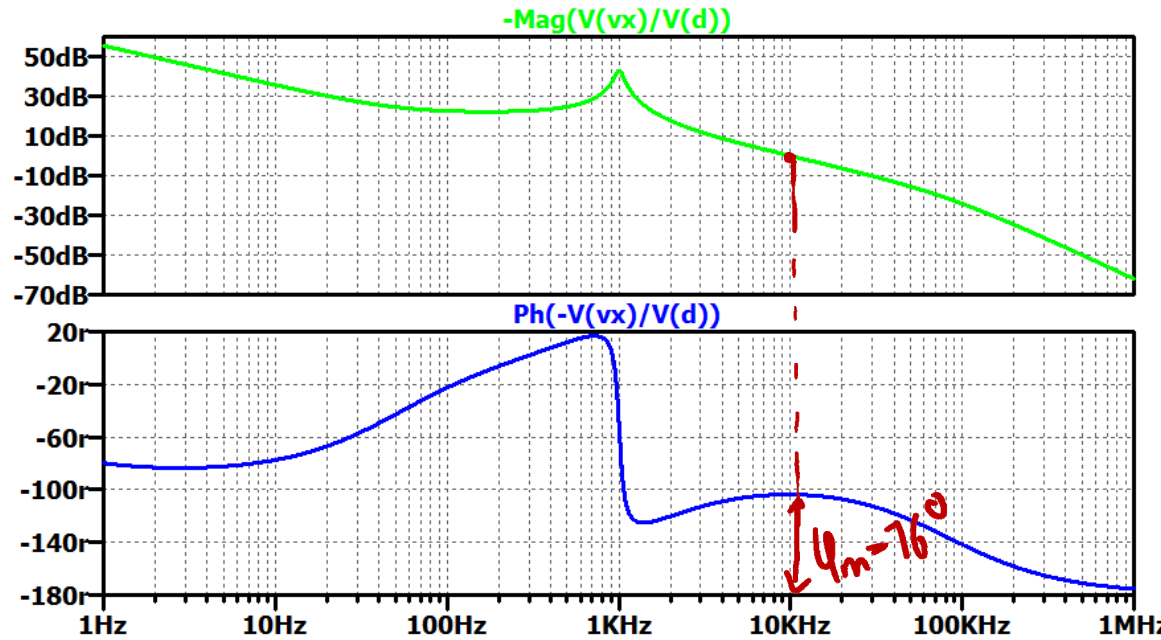


```
.lib myParts.lib
.ac dec 1000 1 1Meg
```

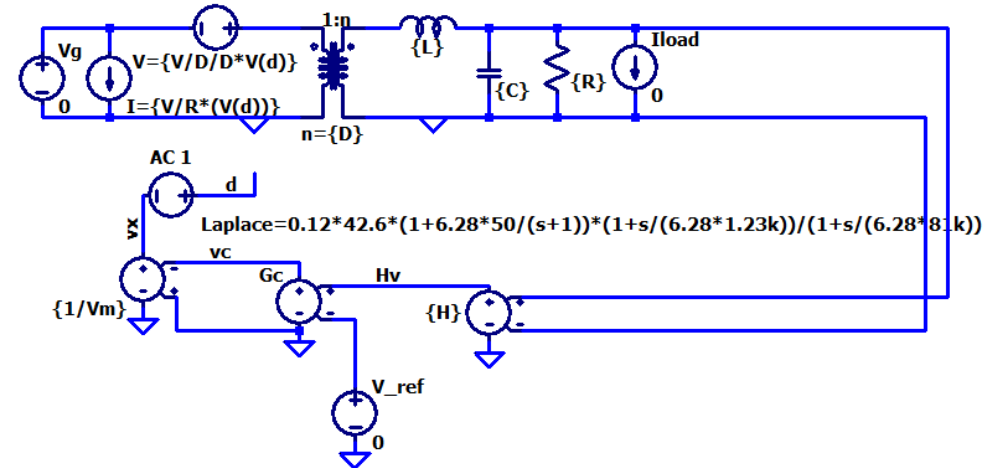
```
.param Vg = 28 V = 15 R = 3 D = .536
.param Vref = 5 H = 1/3 Vm = 4
.param L = 50u C = 500u
```



$$T/(1+T)$$

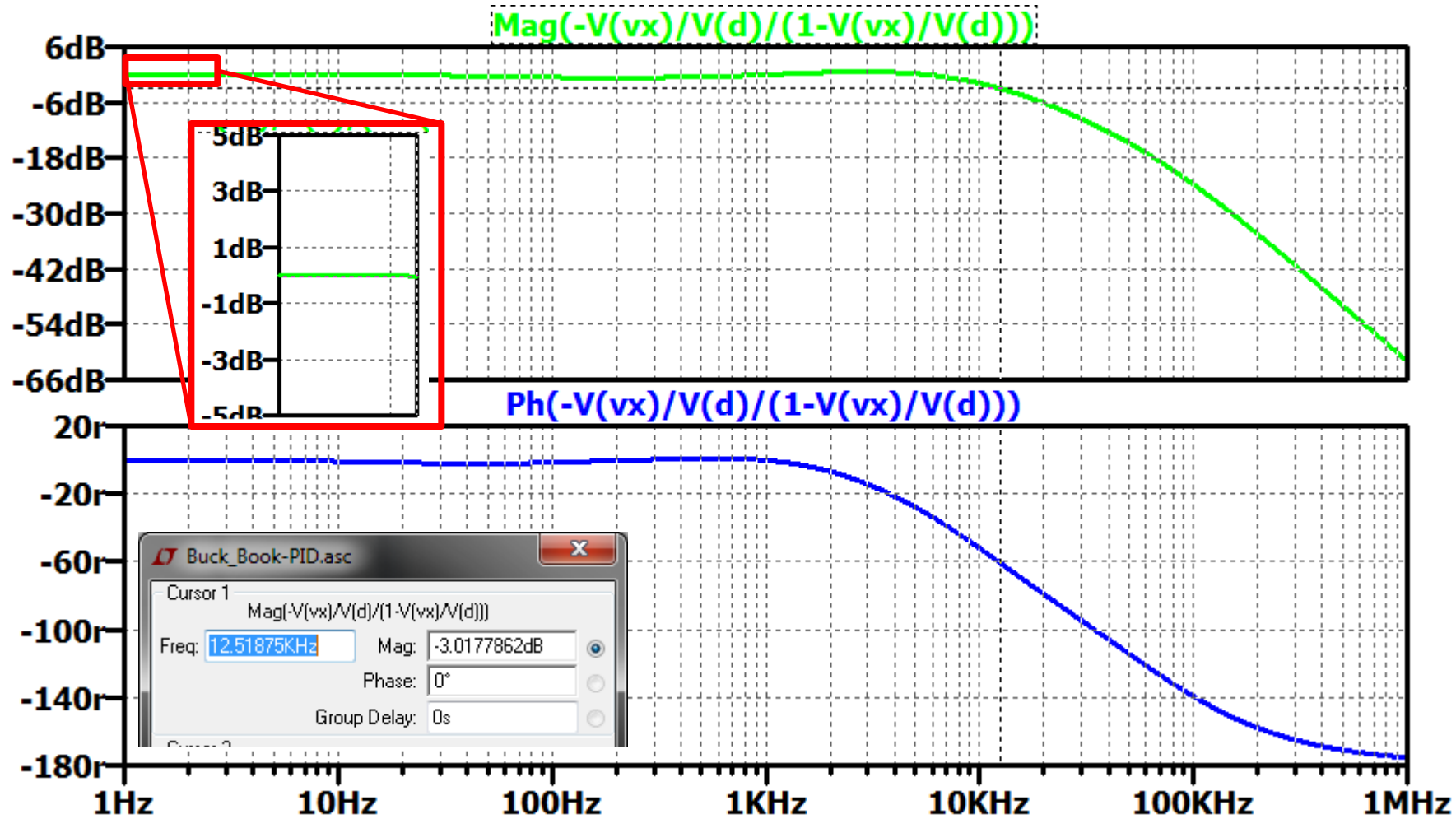


Transient Simulation

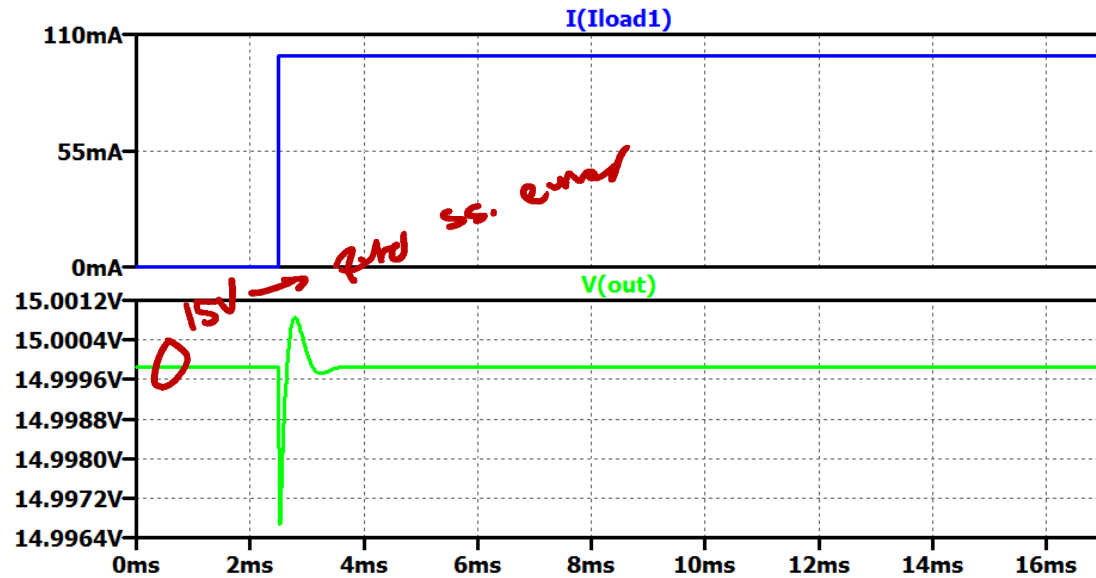

```
.lib switch.lib
.lib myParts.lib
.tran 0 20m 3m
```

```
.param Vg = 28 V = 15 R = 3 D = .536
.param Vref = 5 H = 1/3 Vm = 4
.param L = 50u C = 500u
```
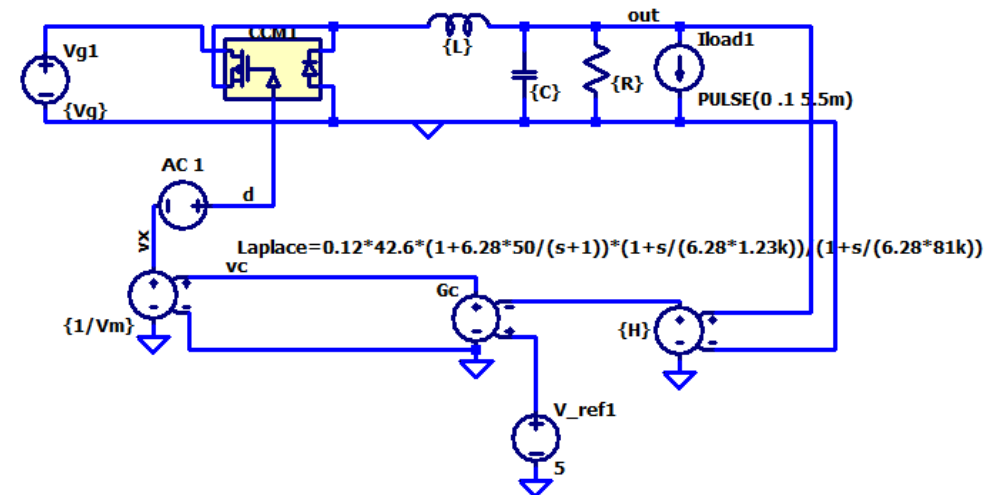
```
.ic V(out) = 15 I(L1) = 5 V(vc) = {D*Vm}
```



Switching Simulation

