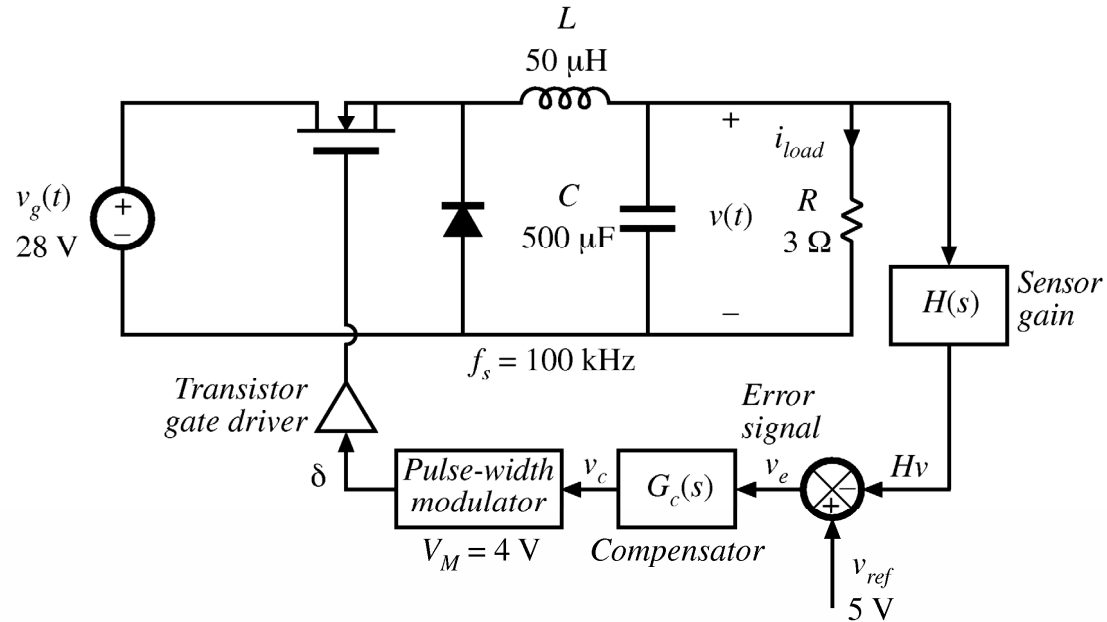


Example Design of Buck Compensator



Input voltage

$$V_g = 28\text{ V}$$

Output

$$V = 15\text{ V}, I_{load} = 5\text{ A}, R = 3\ \Omega$$

Quiescent duty cycle

$$D = 15/28 = 0.536$$

Reference voltage

$$V_{ref} = 5\text{ V}$$

Quiescent value of control voltage

$$V_c = DV_M = 2.14\text{ V}$$

Gain $H(s)$


$$H = V_{ref}/V = 5/15 = 1/3$$

Plotting Uncompensated Loop Gain

With $G_c = 1$, the loop gain is


$$T_u(s) = T_{u0} \frac{1}{1 + \frac{s}{Q_0 \omega_0} + \left(\frac{s}{\omega_0}\right)^2}$$
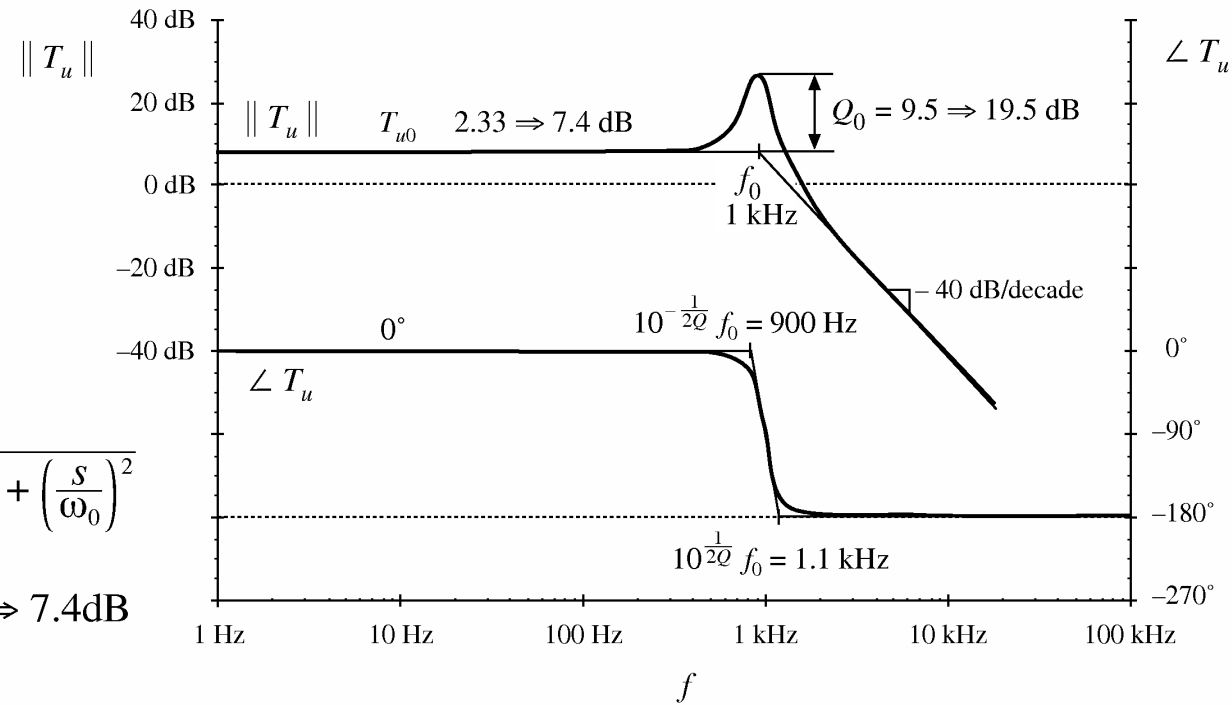
$$T_{u0} = \frac{H V}{D V_M} = 2.33 \Rightarrow 7.4 \text{ dB}$$




$$f_c = 1.8 \text{ kHz}, \varphi_m = 5^\circ$$



LTSpice Simulation – AC, Uncompensated

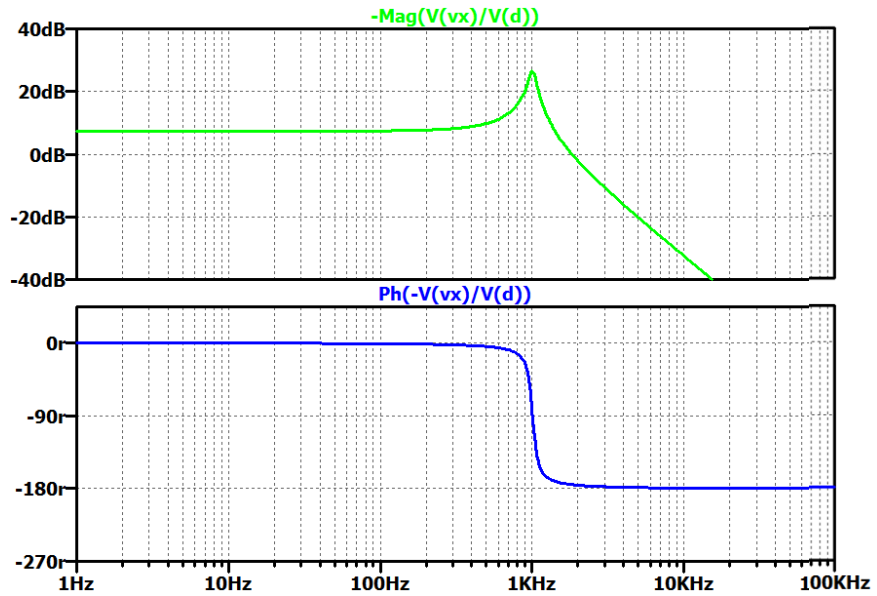

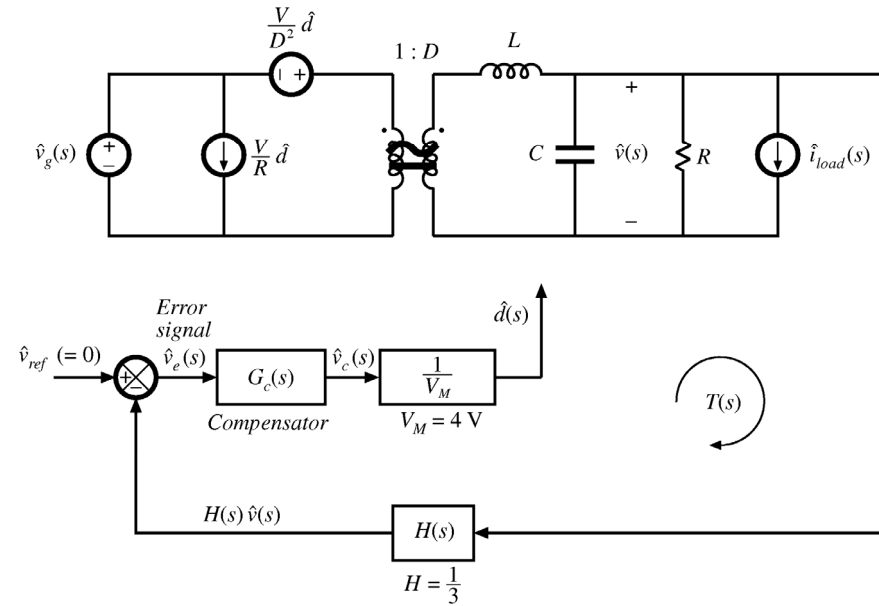
```
.lib myParts.lib
.ac dec 1000 1 1Meg
.param Vg = 28 V = 15 R = 3 D = .536
.param Vref = 5 H = 1/3 Vm = 4
.param L = 50u C = 500u
```




Transient Simulation, Uncompensated

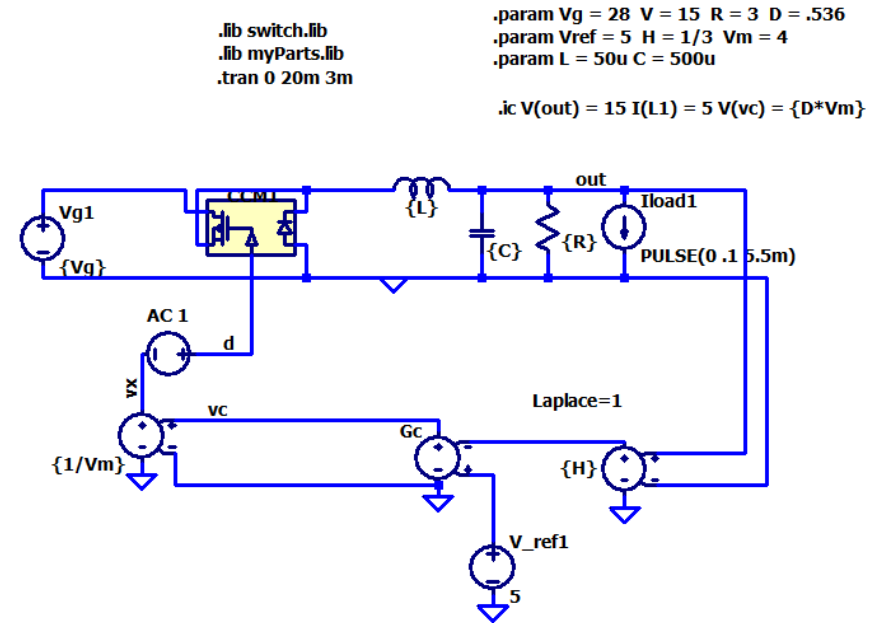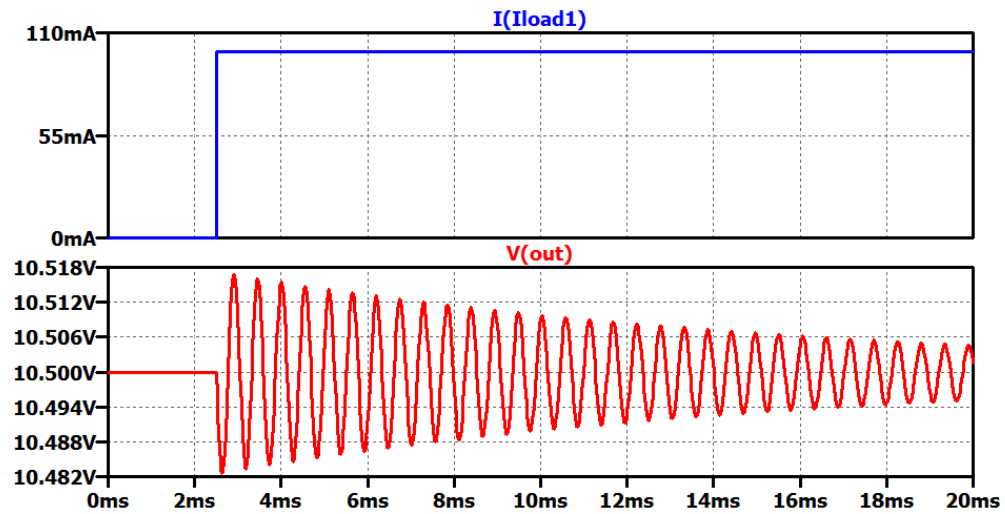

Ringing Frequency

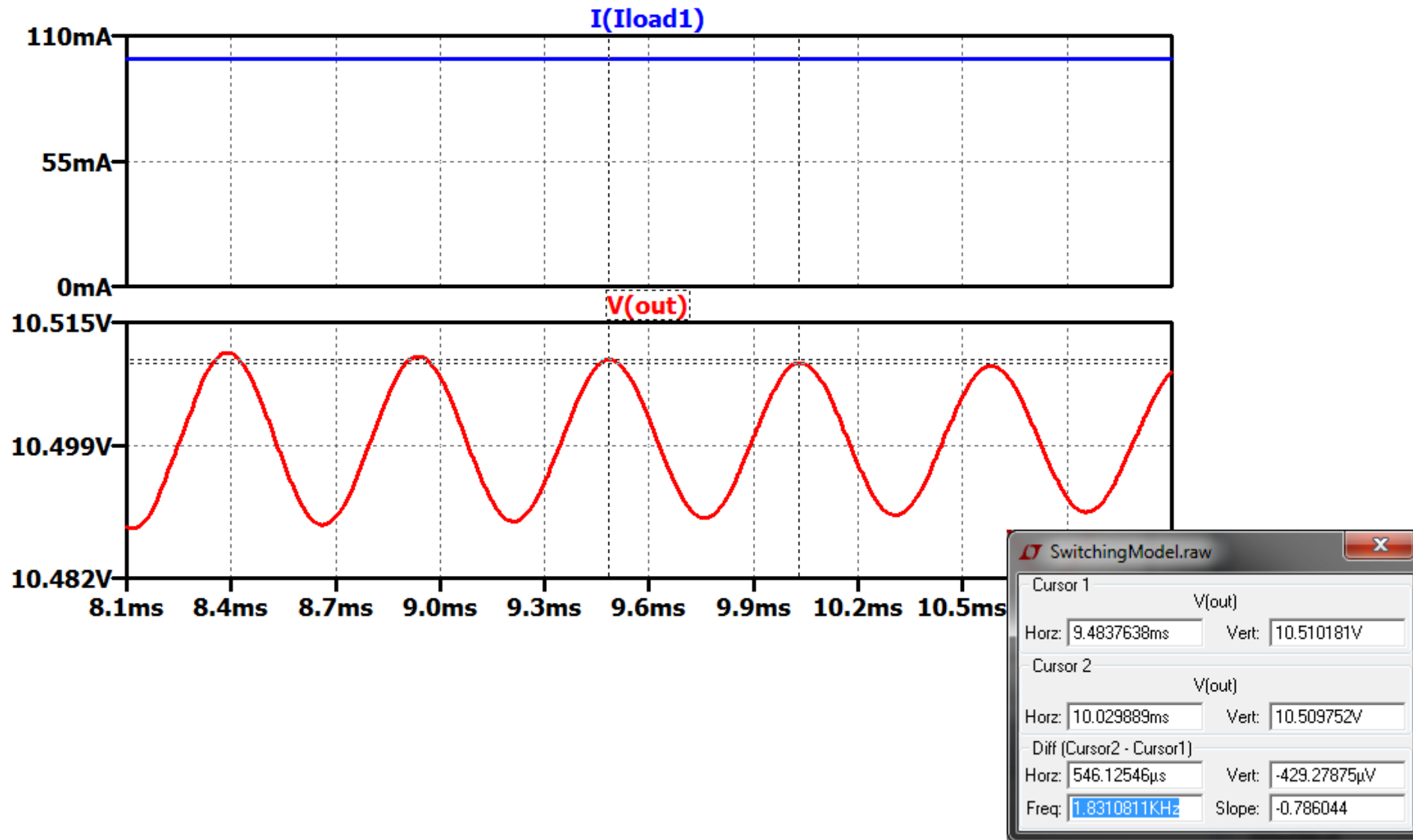

$$T/(1+T)$$

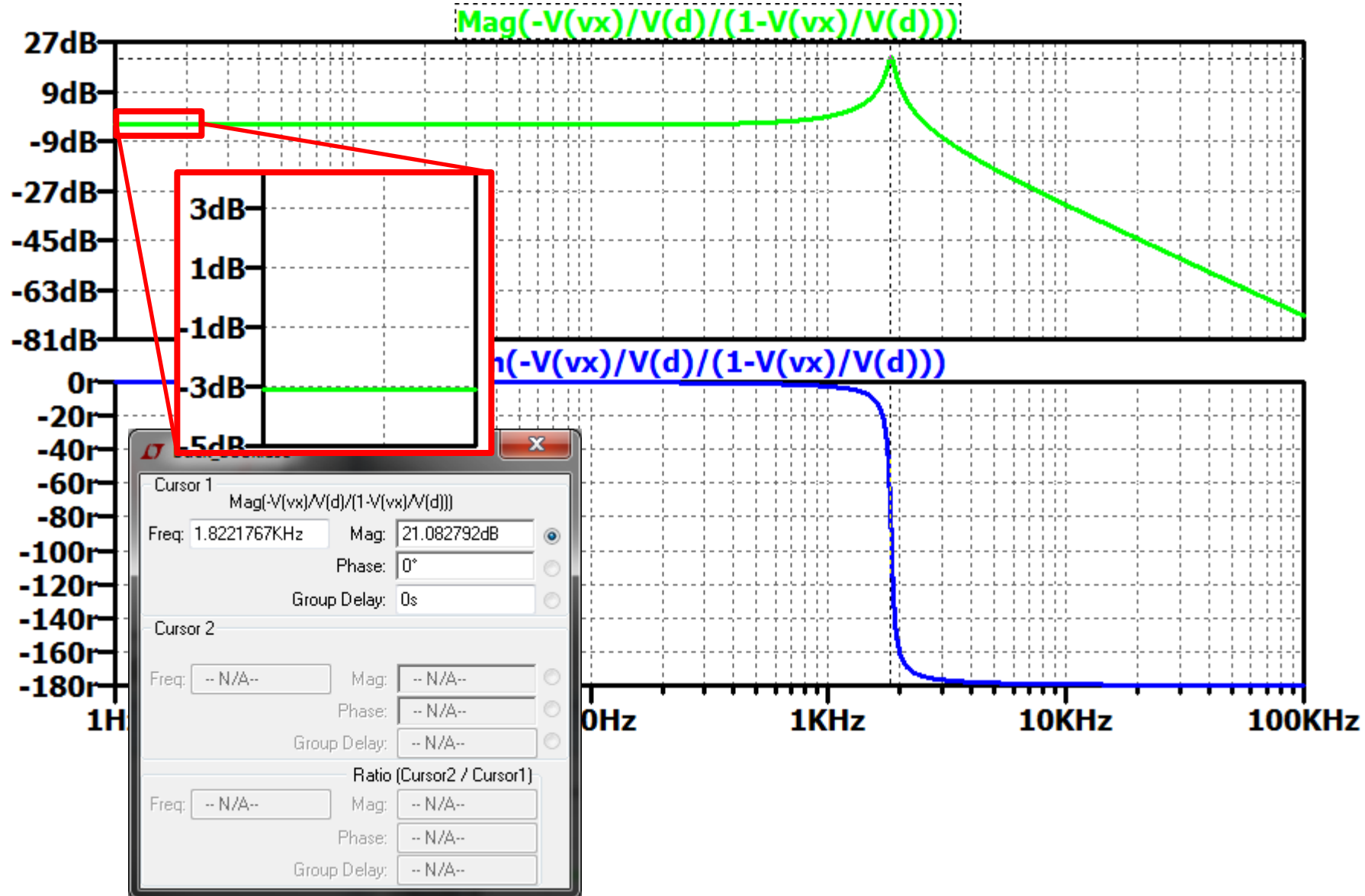


Summary: Uncompensated Behavior

- Significant steady-state error
 - Need to increase low-frequency gain
- Barely stable; significant ringing
 - Need to increase ϕ_m
- Speed: ~ok
 - $f_c = 1.8$ kHz
 - $(BW)_{CL} = 2.6$ kHz
 - OK for $f_s \approx 10$ kHz or above



Compensator Design

- As an example, try to
 - Increase f_c to 10 kHz
 - Increase ϕ_m to 76° ($Q_{CL}=0.5$)
 - Increase $\|T_0\|$ to ∞
- Note: Book Chooses $f_c = 5$ kHz and $\phi_m = 52^\circ$ ($Q=0.5$)

PI Design

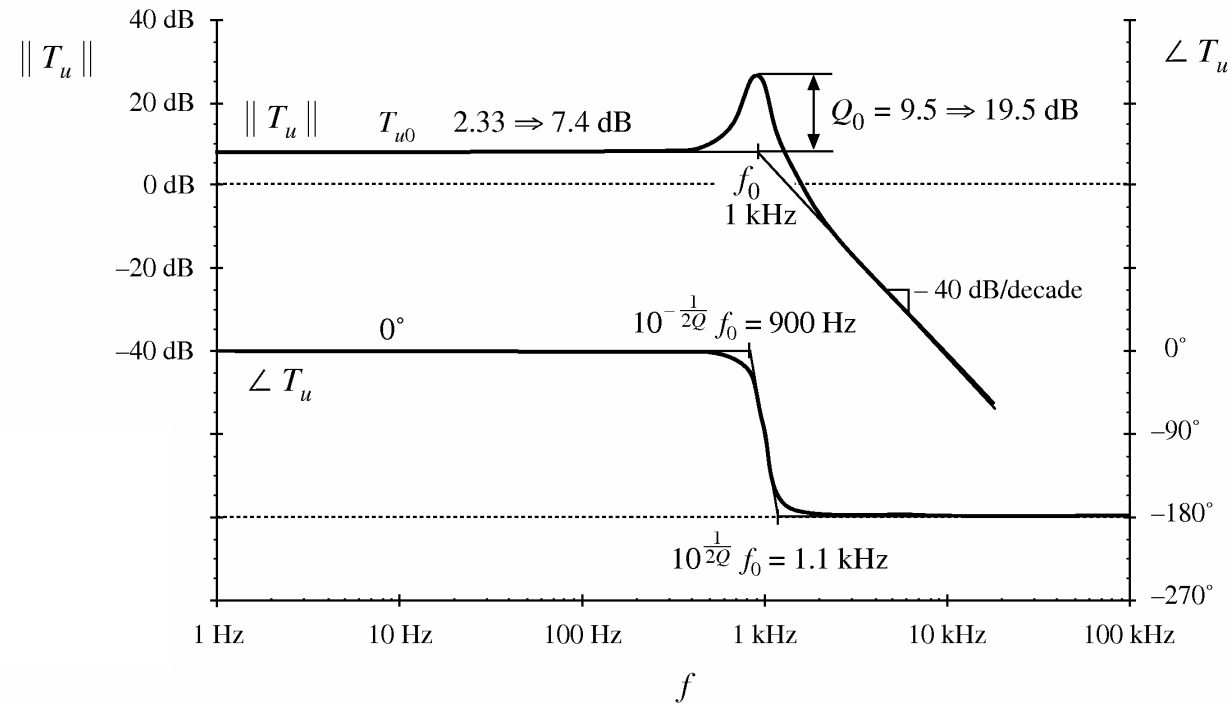

PI Simulation

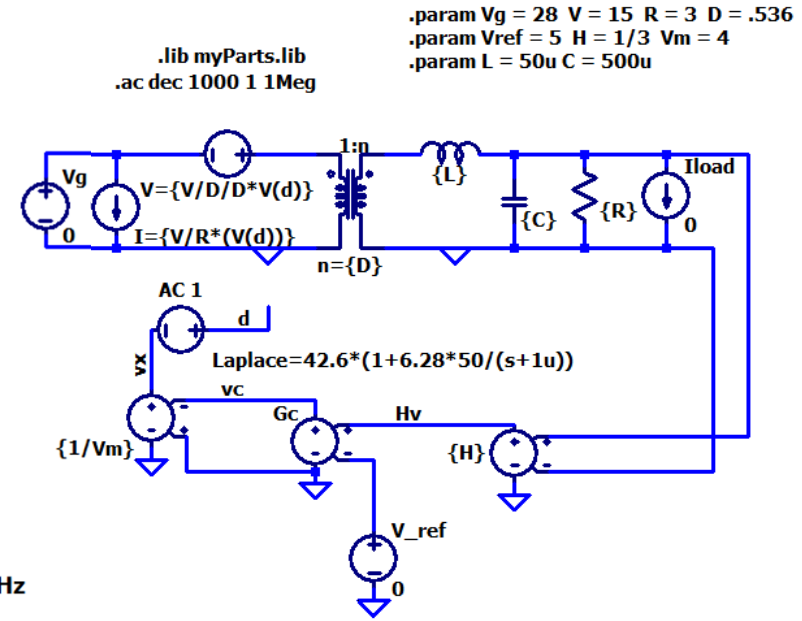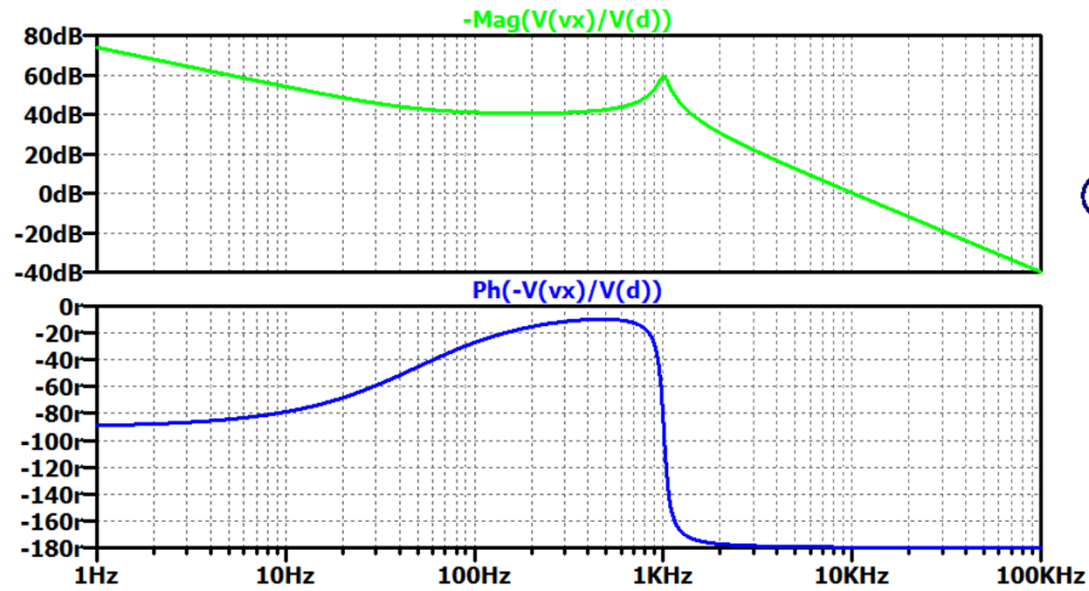


PD Design

$$f_z = f_c \sqrt{\frac{1 - \sin(\theta)}{1 + \sin(\theta)}}$$

$$f_p = f_c \sqrt{\frac{1 + \sin(\theta)}{1 - \sin(\theta)}}$$


$$G_{c0} = \sqrt{\frac{f_z}{f_p}}$$

PID Simulation

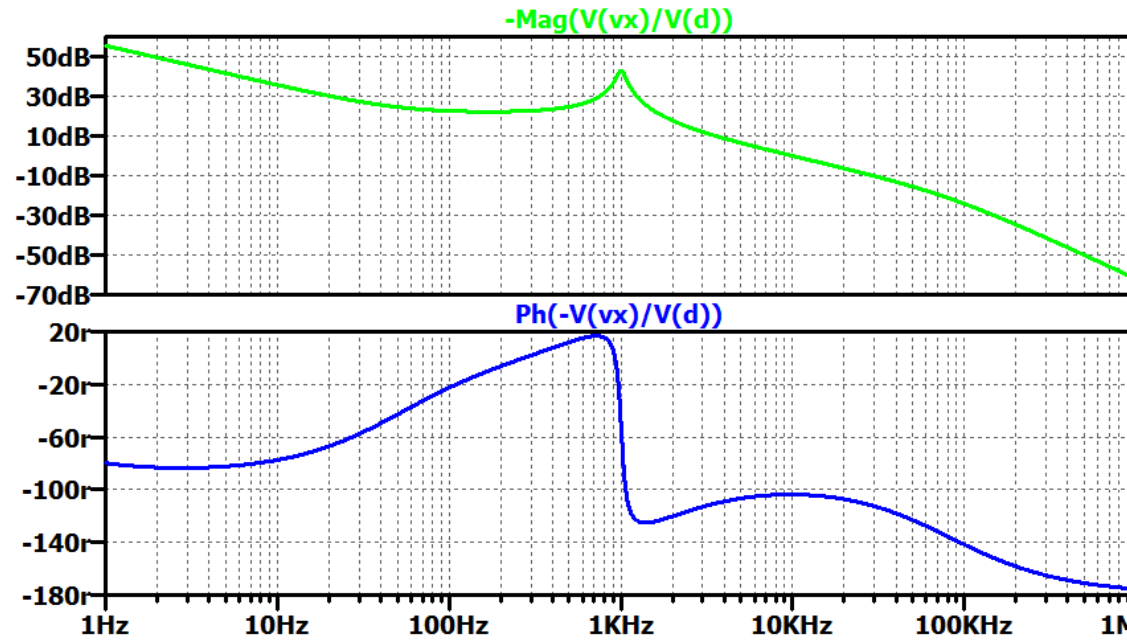


```
.lib myParts.lib
.ac dec 1000 1 1Meg
```

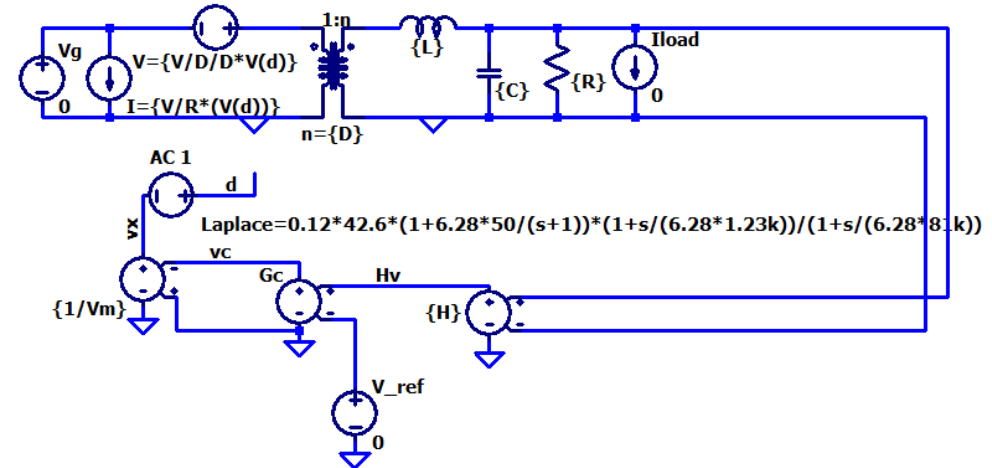
```
.param Vg = 28 V = 15 R = 3 D = .536
.param Vref = 5 H = 1/3 Vm = 4
.param L = 50u C = 500u
```



$$T/(1+T)$$

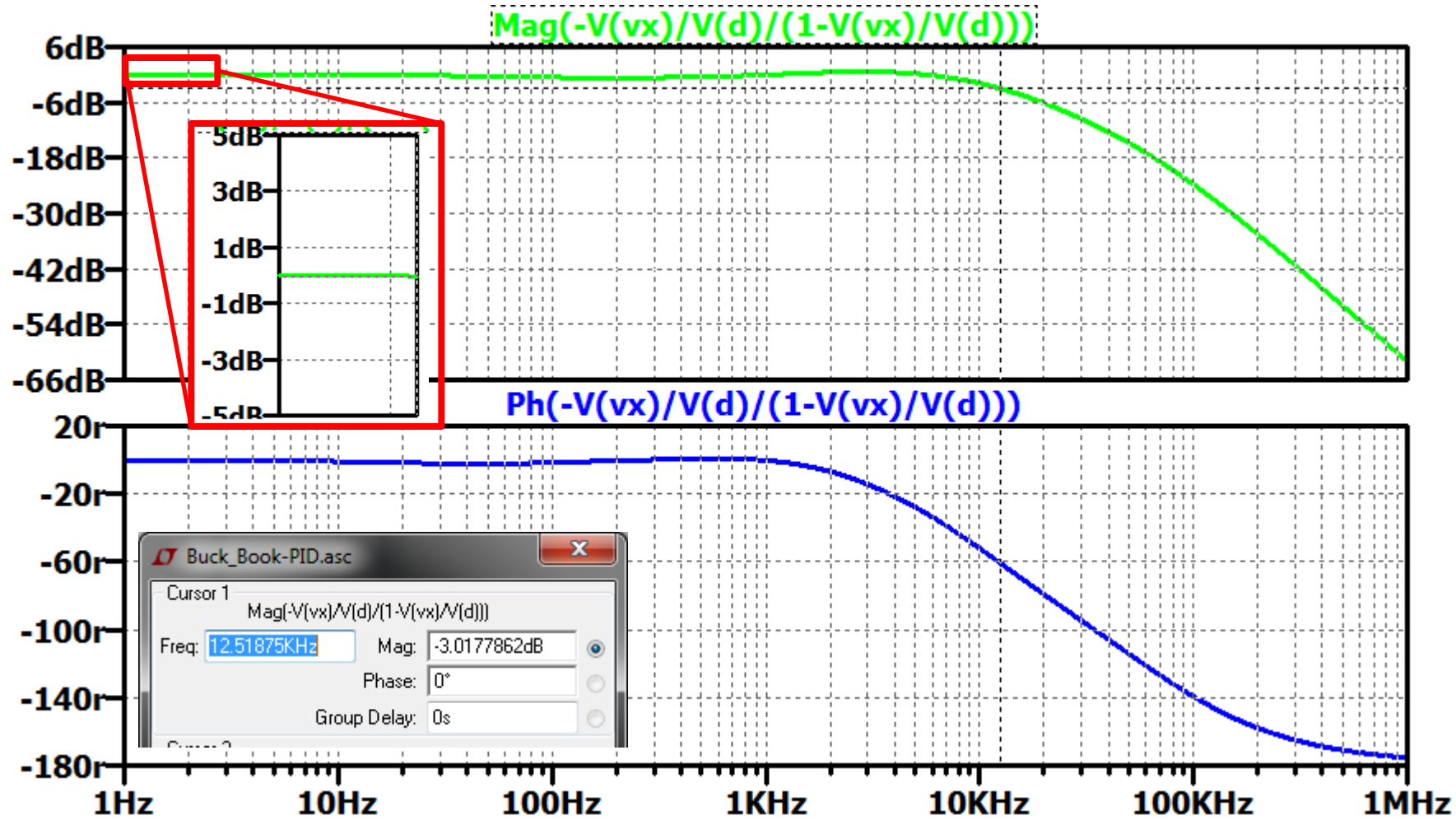


Transient Simulation

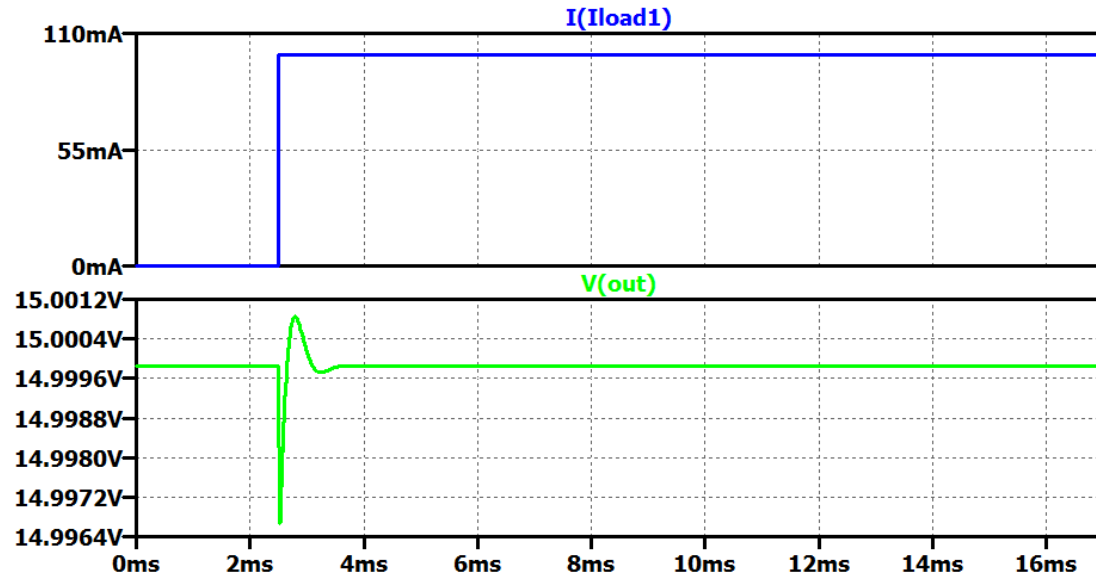



```
.lib switch.lib
.lib myParts.lib
.tran 0 20m 3m
```

```
.param Vg = 28 V = 15 R = 3 D = .536
.param Vref = 5 H = 1/3 Vm = 4
.param L = 50u C = 500u

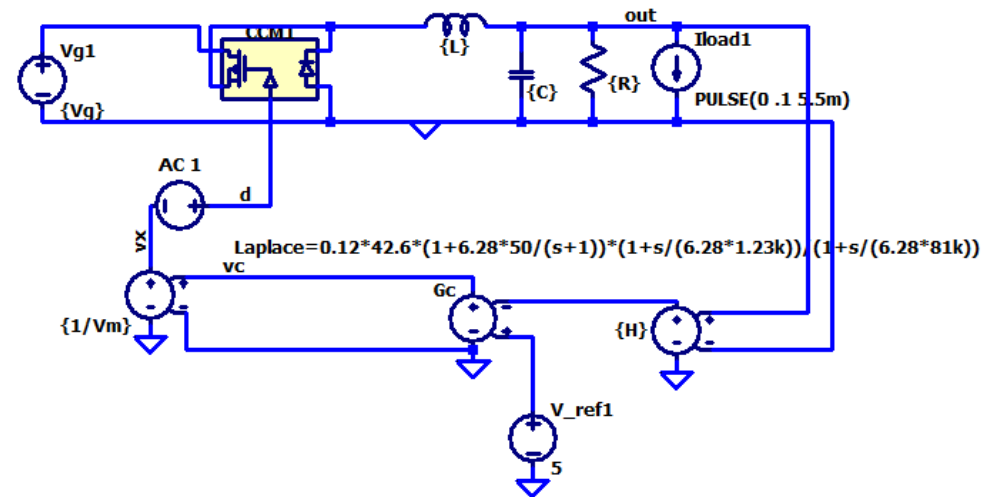
.ic V(out) = 15 I(L1) = 5 V(vc) = {D*Vm}
```



Switching Simulation

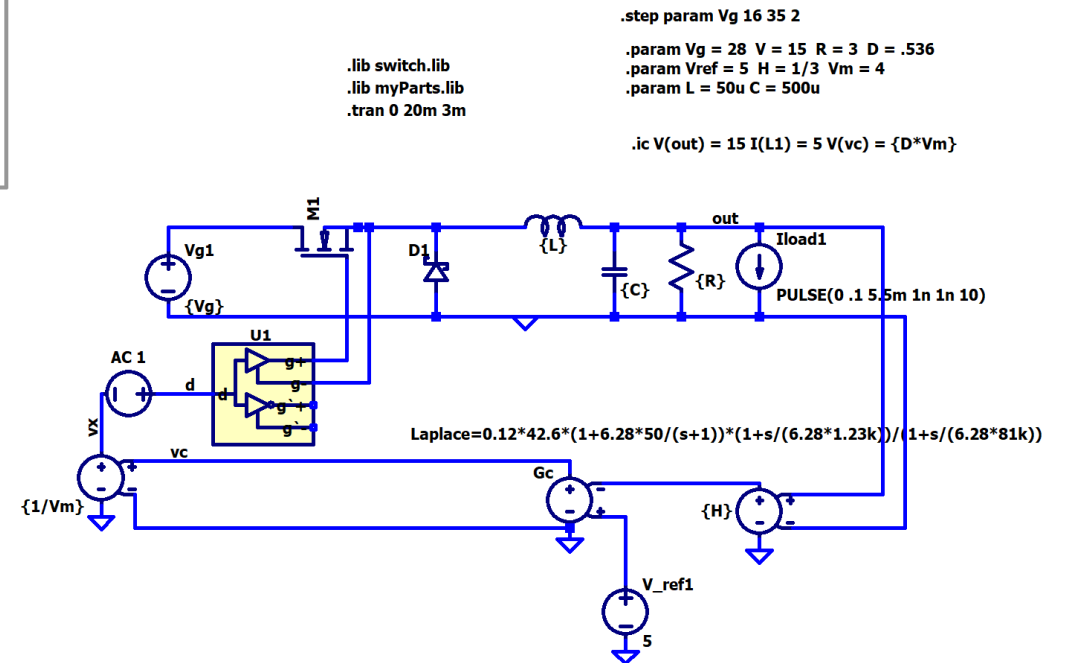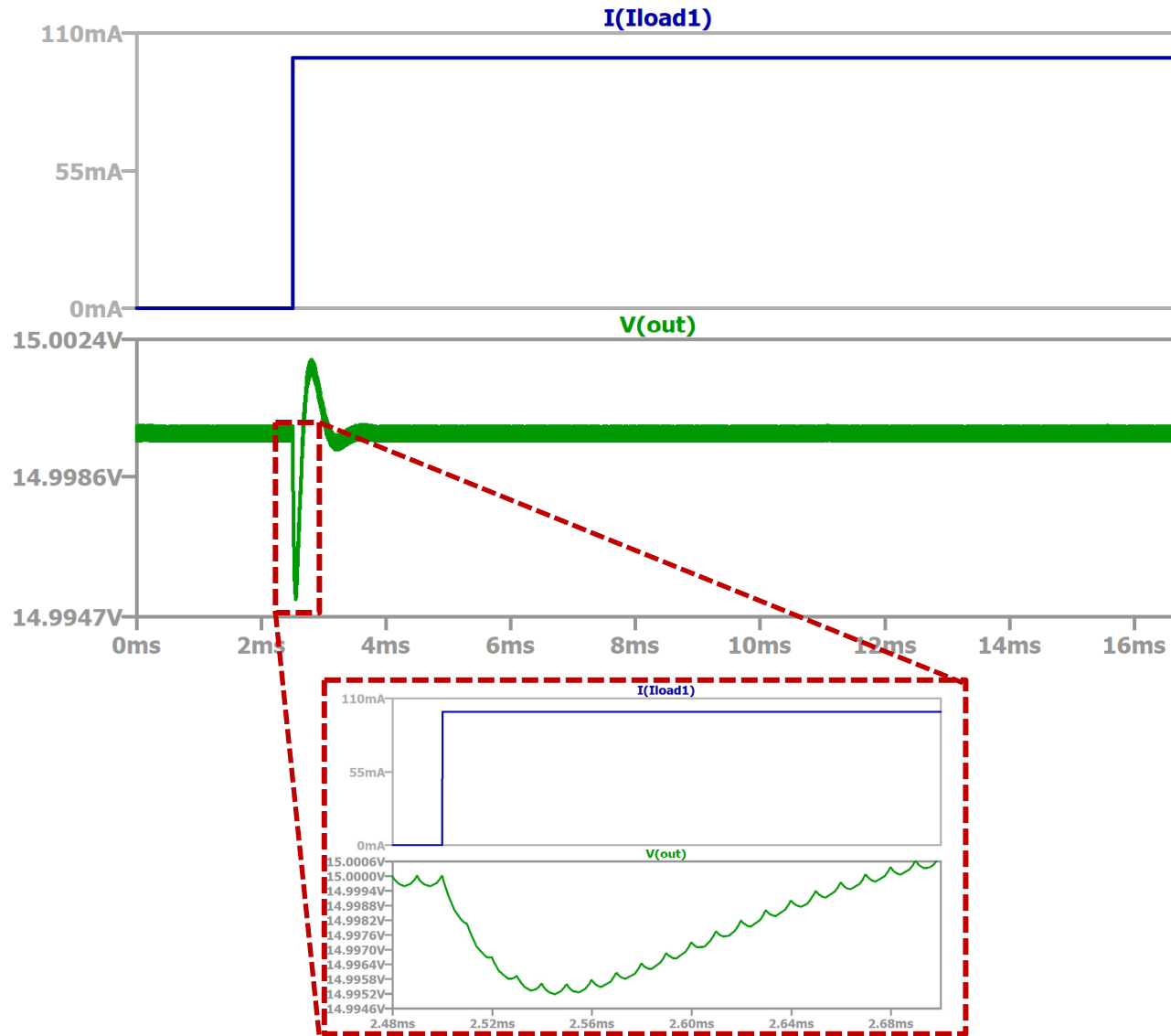

Complete Compensator

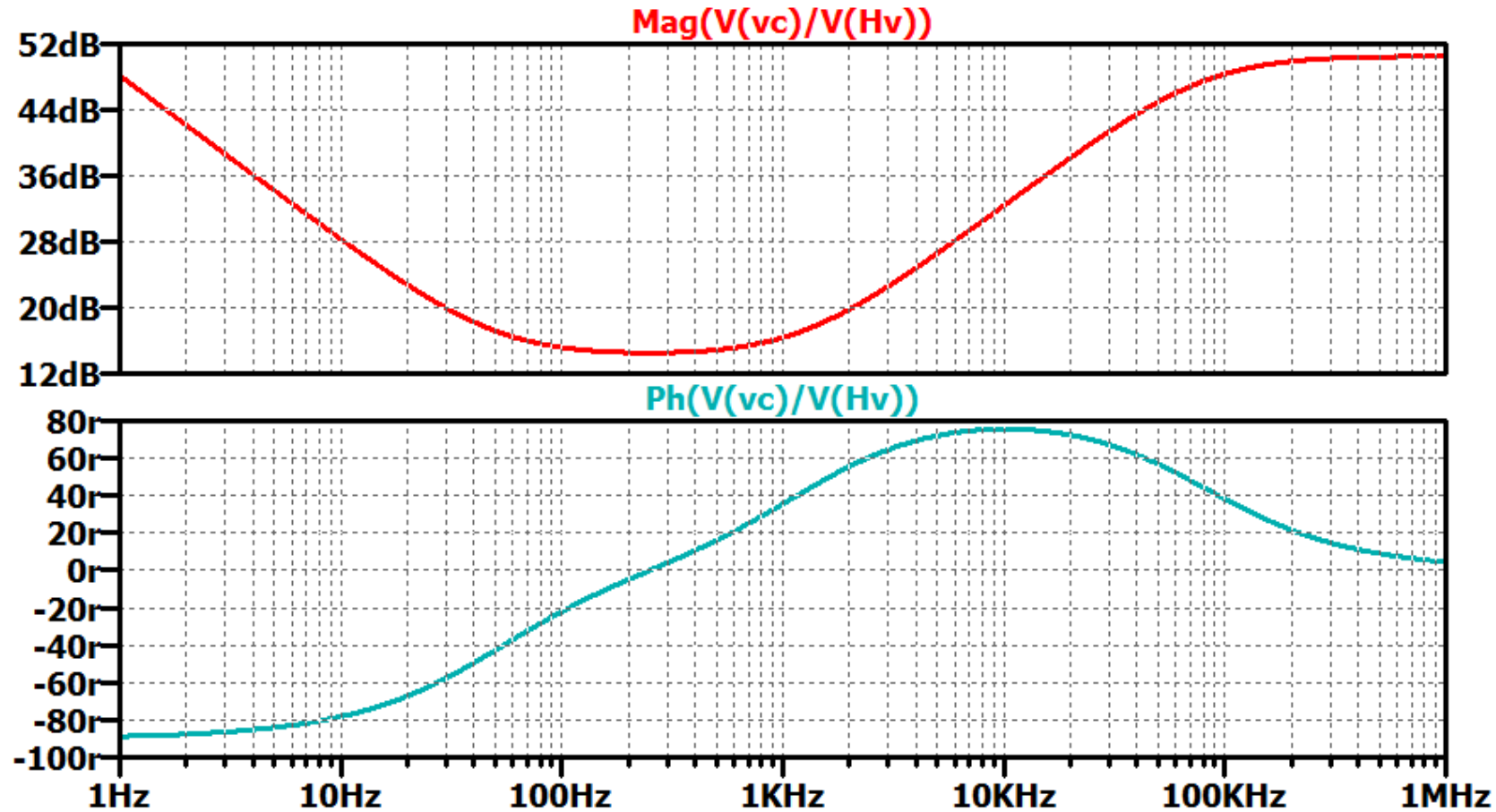

$$G_c = G_{cm} \left(1 + \frac{2\pi(50\text{Hz})}{s} \right) \frac{\left(1 + \frac{s}{2\pi(1.2\text{kHz})} \right)}{\left(1 + \frac{s}{2\pi(81\text{kHz})} \right)}$$

Compensator Realization

