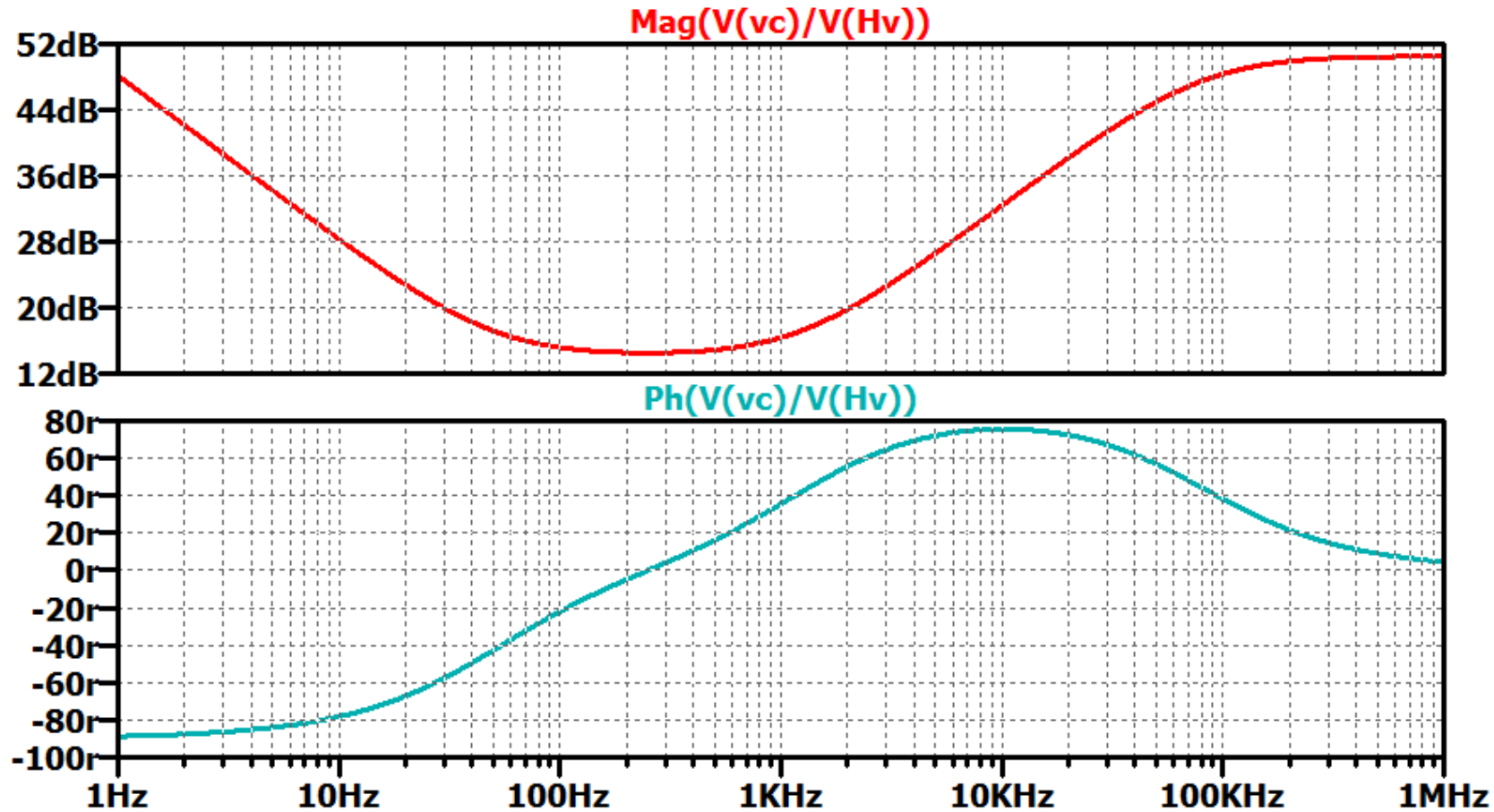


Complete Compensator




$$G_c = G_{cm} \left(1 + \frac{2\pi(50\text{Hz})}{s} \right) \frac{\left(1 + \frac{s}{2\pi(1.2\text{kHz})} \right)}{\left(1 + \frac{s}{2\pi(81\text{kHz})} \right)}$$

Compensator Realization


Designed Behavior
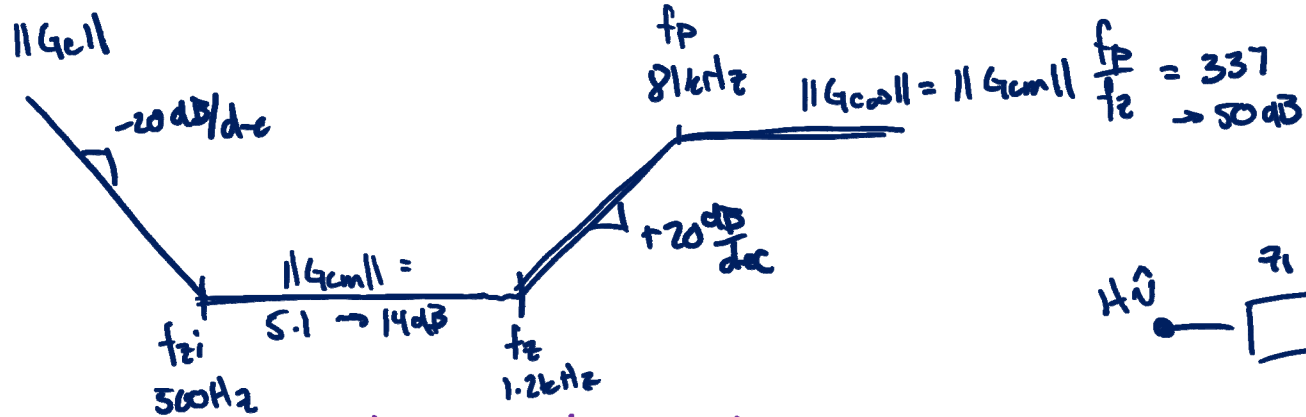
$$\hat{v}_e = G_c(s) (\hat{v}_{ref} - H\hat{u})$$




$$\hat{v}_e = H\hat{u} \left(\frac{-z_2}{z_1} \right) + \hat{v}_{ref} \left(1 + \frac{z_2}{z_1} \right)$$

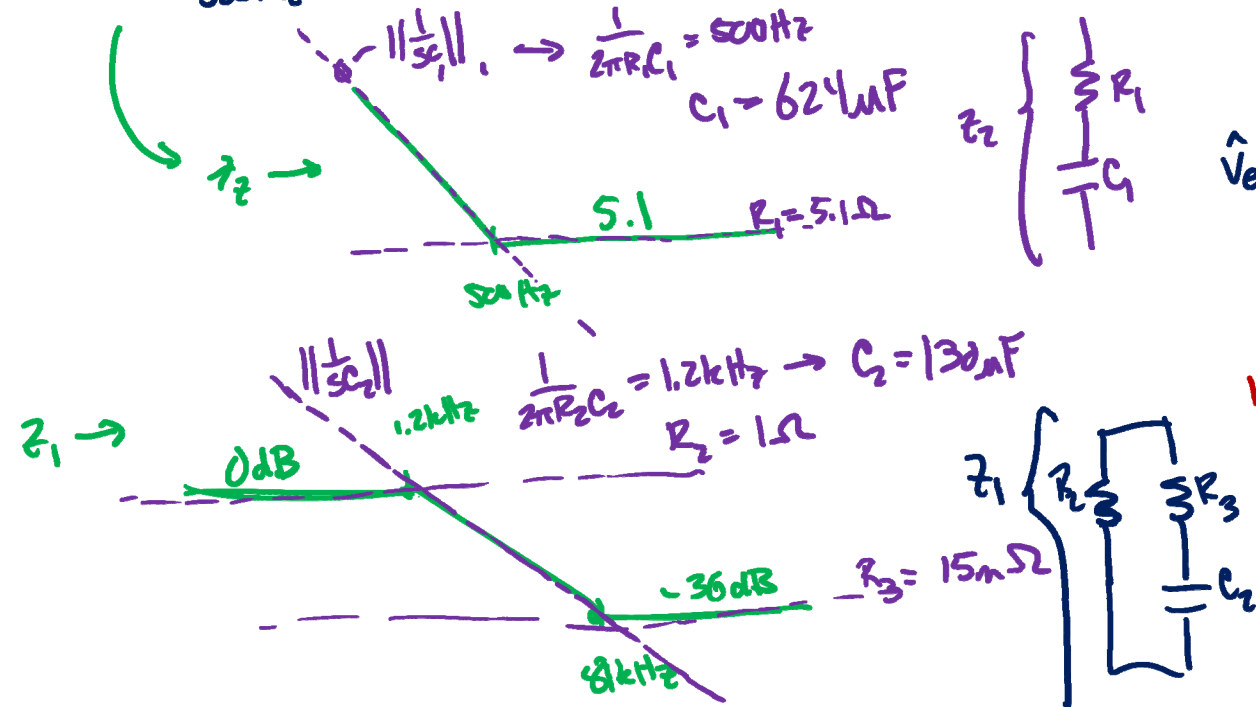\rightarrow ok if we won't dynamically vary v_{ref} ($v = \text{const}$)




Can make a balanced implementation

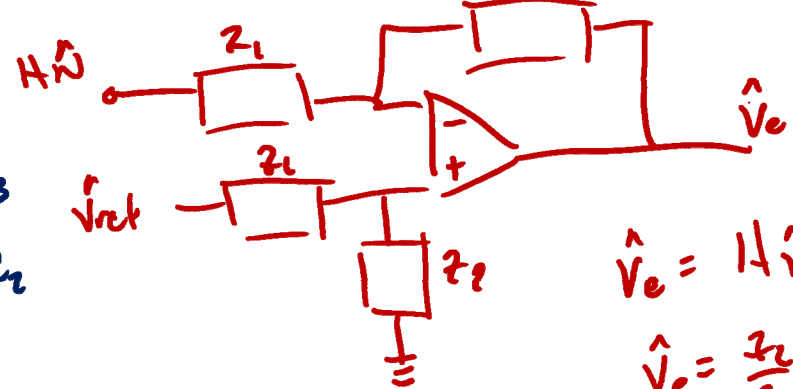


$$\hat{v}_e = H\hat{u} \left(\frac{-z_2}{z_1} \right) + \hat{v}_{ref} \left(\frac{z_2}{z_1 + z_2} \right) \left(\frac{z_1 + z_2}{z_1} \right)$$
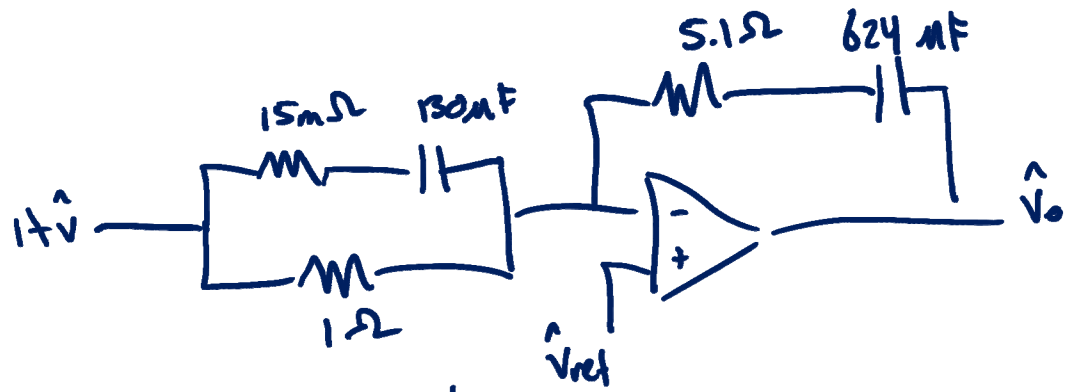
$$\hat{v}_e = \frac{z_2}{z_1} (\hat{v}_{ref} - H\hat{u})$$




→ R's too small } Op-amp will be
 C's too big } slew rate limited

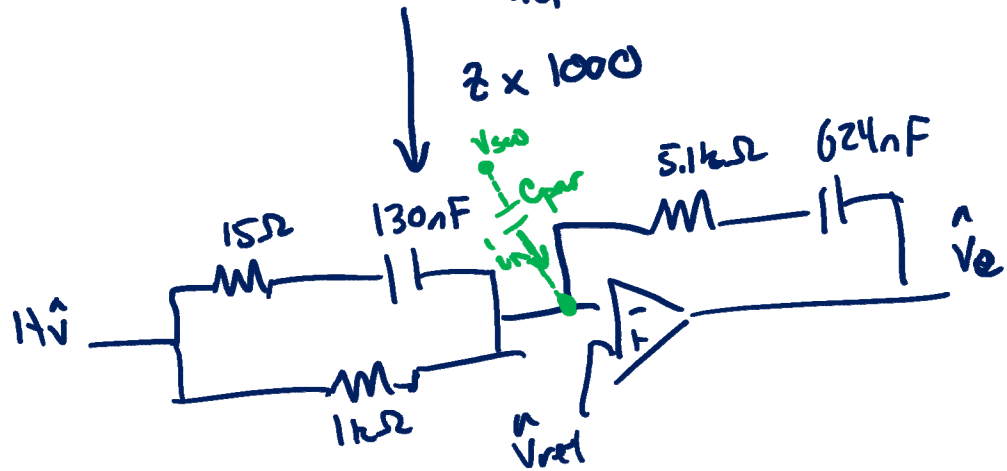If Z_i too large, increased noise susceptibility




Compensator TF


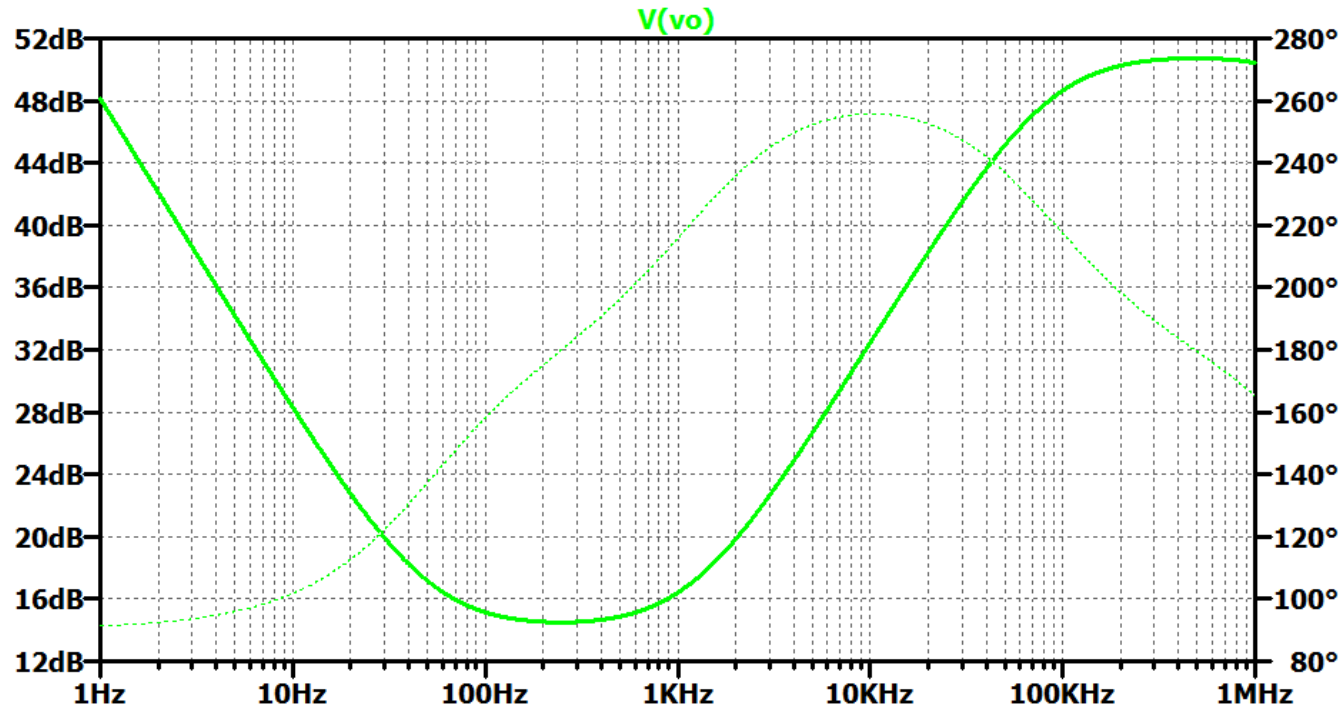


.ac dec 1000 1 1Meg


.lib opamp.sub

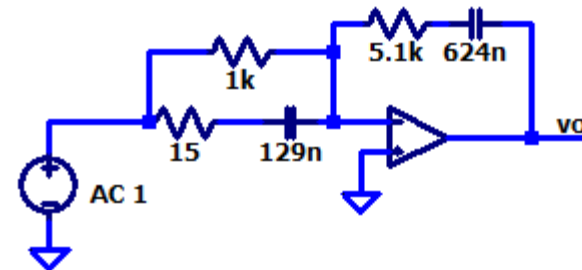

Op-amp GBW

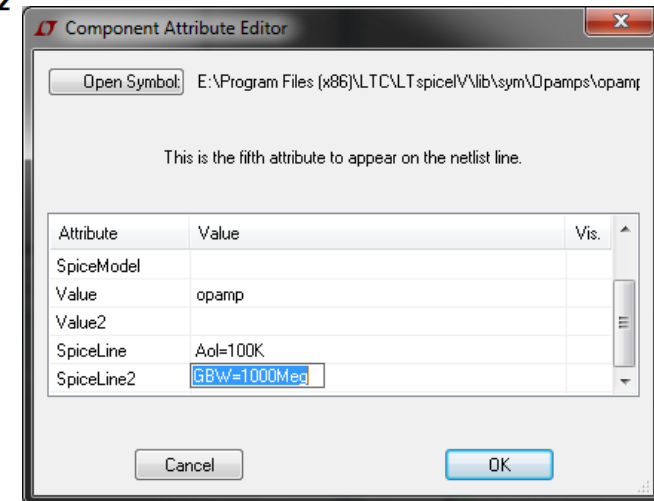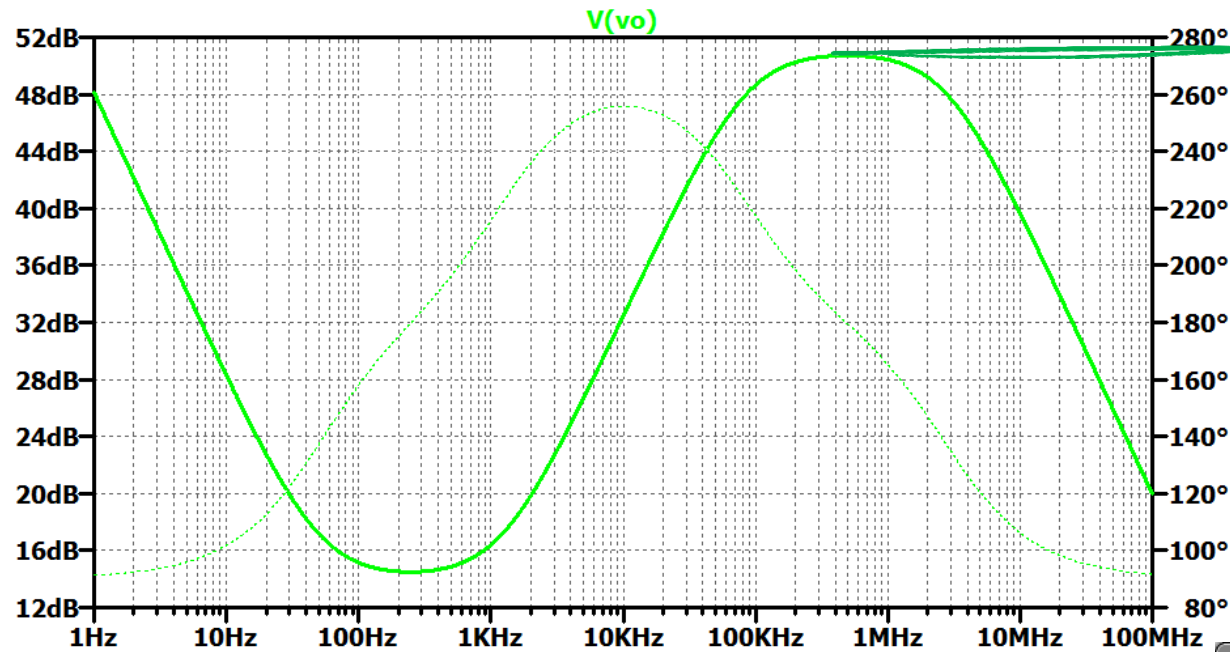

Boost Converter Example

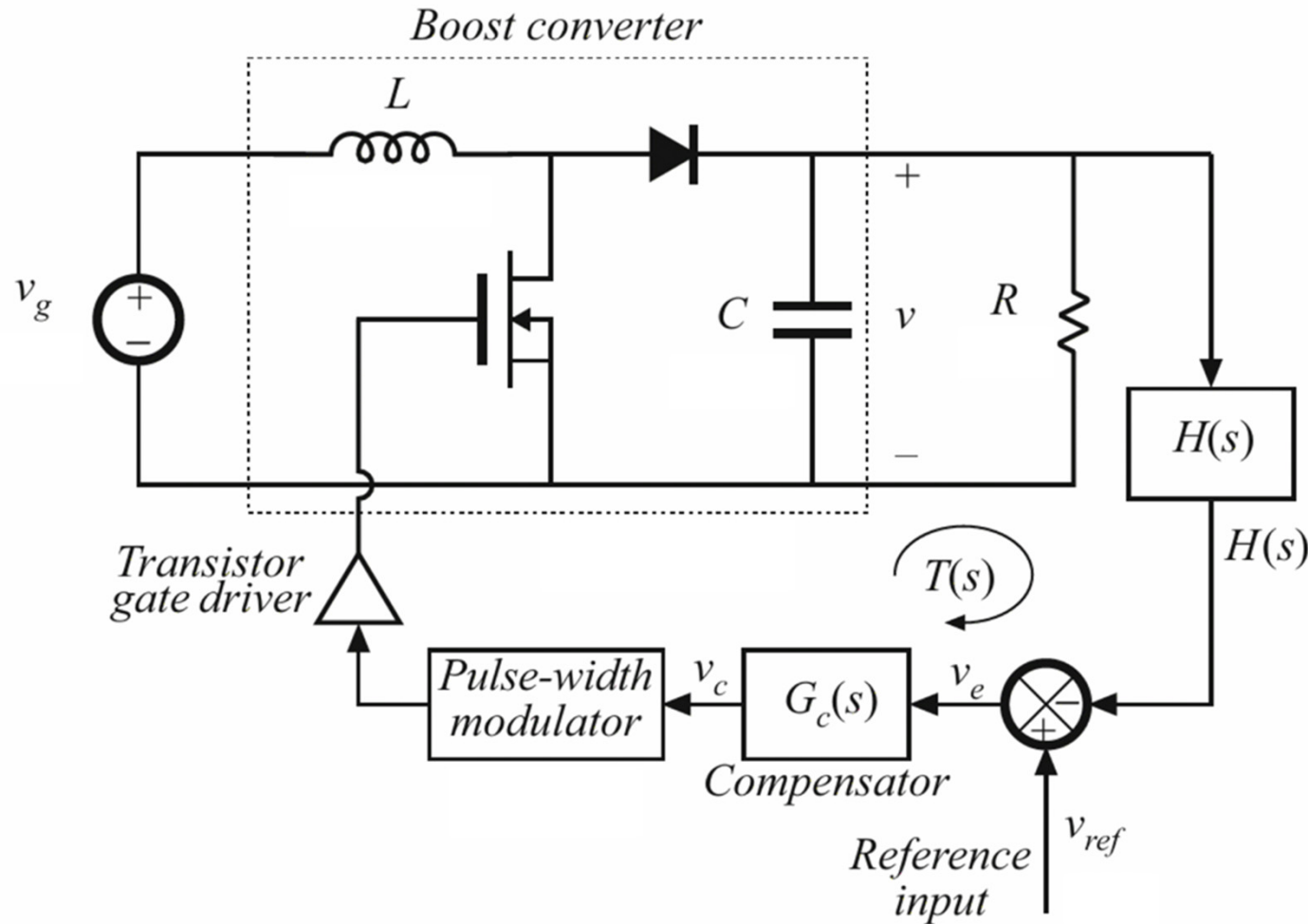

$$V_g = 12V$$

$$R = 10\Omega$$

$$H = \frac{1}{20}$$

$$L = 5\mu H$$

$$C = 100\mu F$$

$$f_s = 500\text{kHz}$$

$$V_m = 4V$$

$$V_{ref} = 3V$$

Boost TFs

$$G_{vd}(s) = G_{d0} \frac{\left(1 - \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2\right)}$$

$$G_{d0} = 300 \rightarrow 49.5\text{dB}$$


$$\omega_0 = 8.96\text{krad/s} \rightarrow 1.4\text{kHz}$$

$$Q = 8.94 \rightarrow 19\text{dB}$$


$$\omega_z = 80\text{krad/s} \rightarrow 12.7\text{kHz}$$

Table 8.2 Salient features of the small-signal CCM transfer functions of some basic dc–dc converters

Converter	G_{g0}	G_{d0}	ω_0	Q	ω_z
Buck	D	$\frac{V}{D}$	$\frac{1}{\sqrt{LC}}$	$R\sqrt{\frac{C}{L}}$	∞
Boost	$\frac{1}{D'}$	$\frac{V}{D'}$	$\frac{D'}{\sqrt{LC}}$	$D'R\sqrt{\frac{C}{L}}$	$\frac{D'^2R}{L}$
Buck–boost	$-\frac{D}{D'}$	$\frac{V}{DD'}$	$\frac{D'}{\sqrt{LC}}$	$D'R\sqrt{\frac{C}{L}}$	$\frac{D'^2R}{DL}$

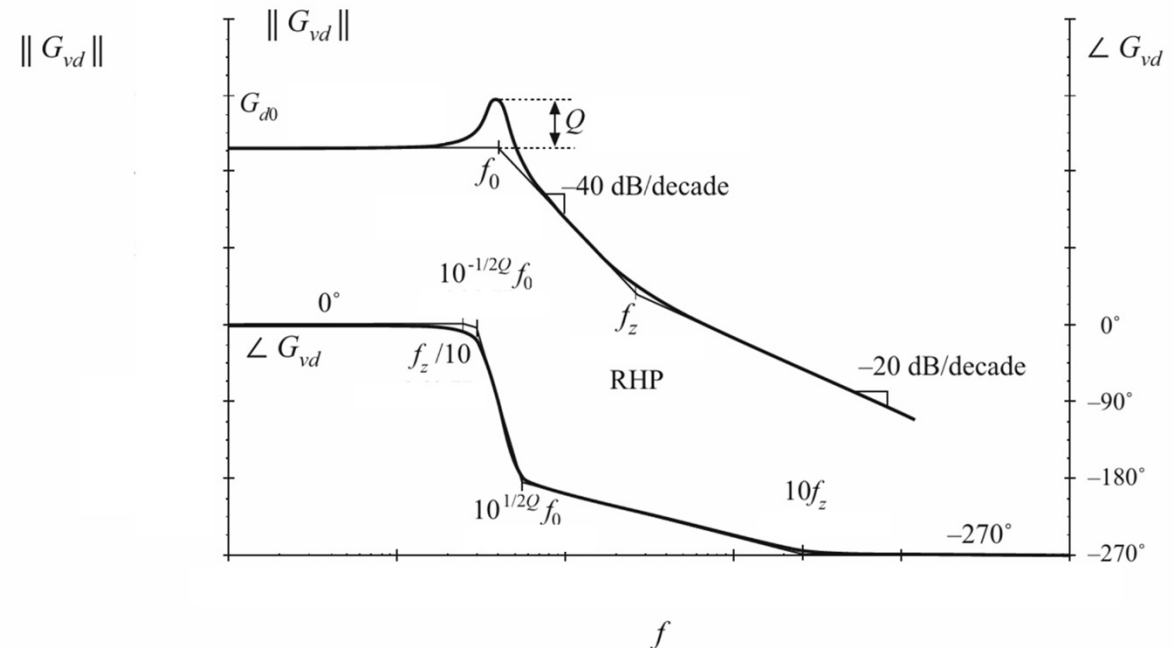

System Block Diagram

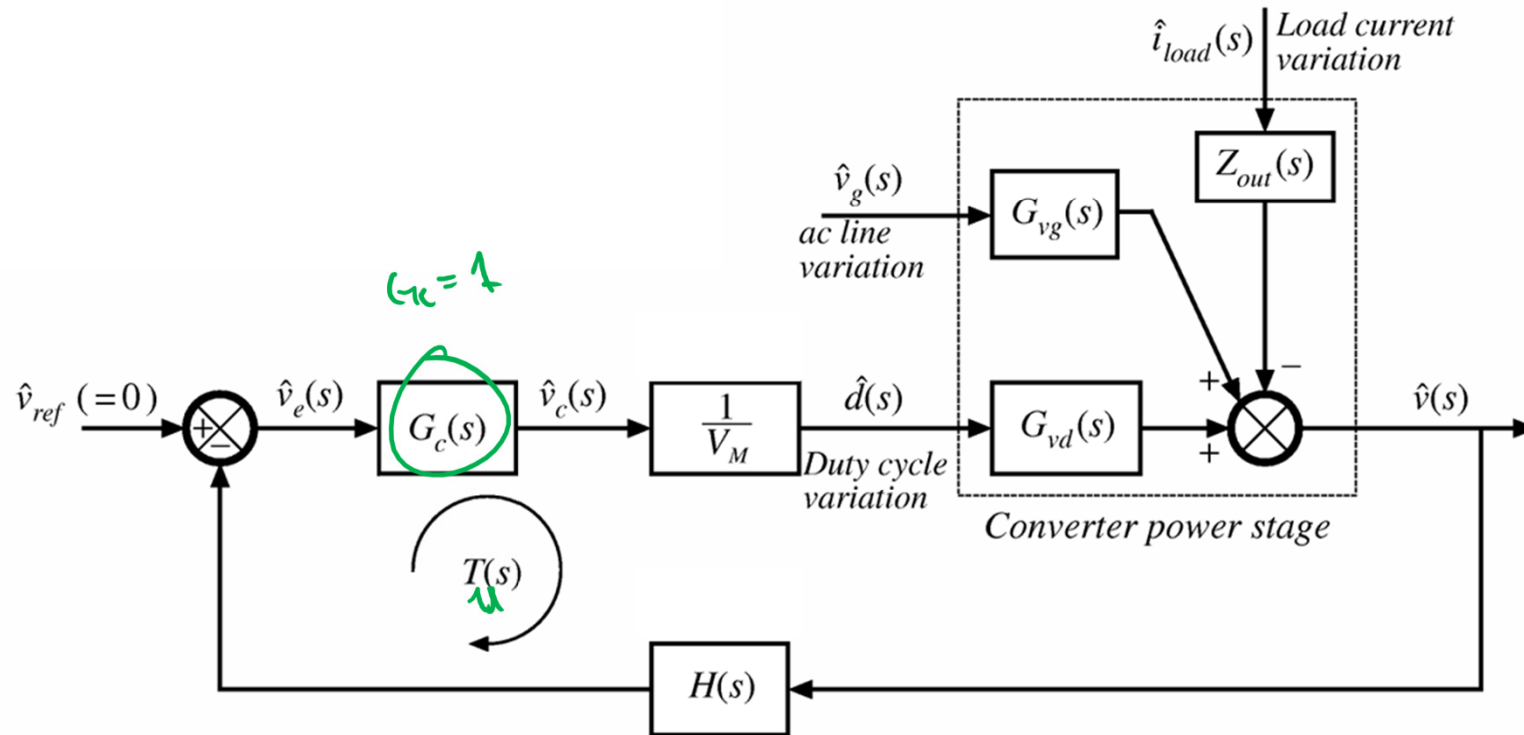

LTspice Simulation



$$T_u(s) = G_{vd} H \frac{1}{V_m}$$

```


.lib switch.lib
.lib myParts.lib
;.tran 0 500m 250m
.ac dec 100 10 1Meg
.op

.param Vg=12 V=60 R=10 D=.8
.param Vref=3 H=1/20 Vm=4
.param L=5u C=100u

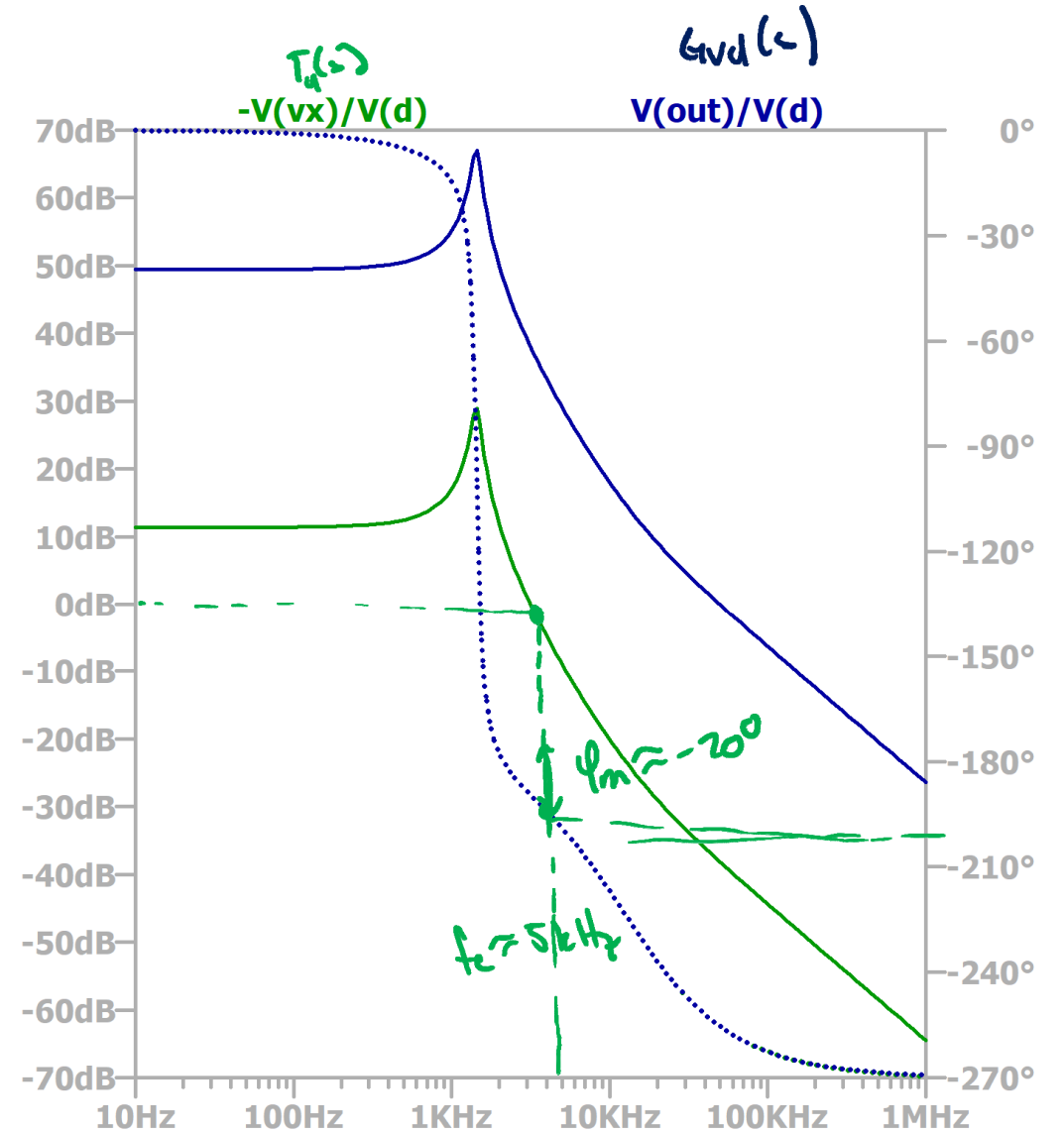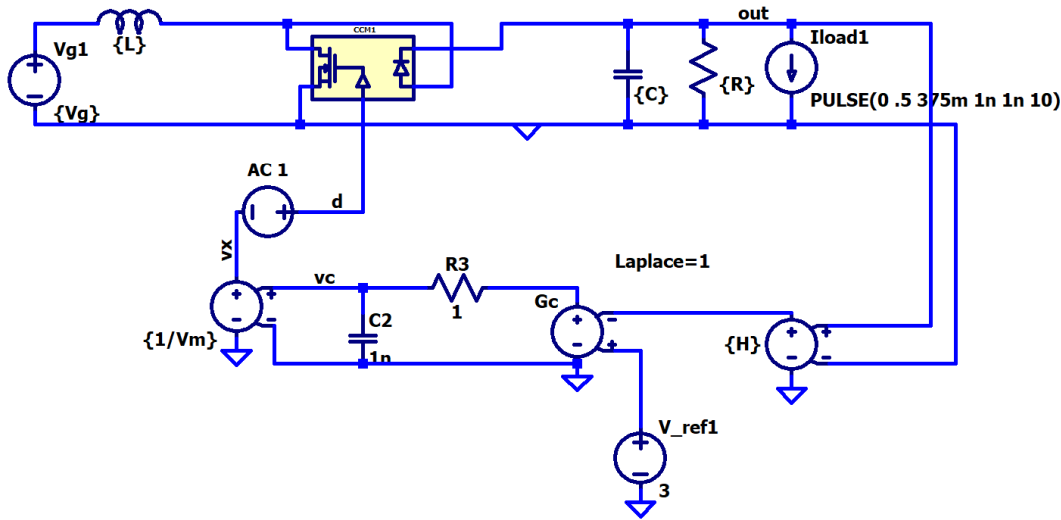
.ic V(out)=60 I(L1)={6*5} V(vc)={D*Vm}
    
```



Impact of RHP Zero

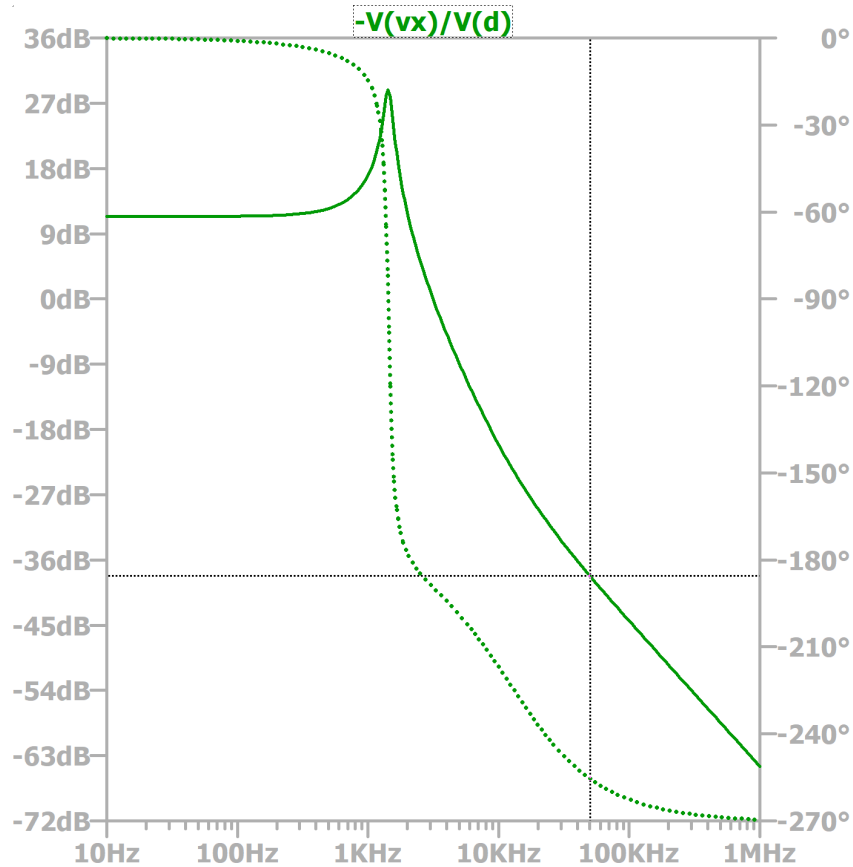

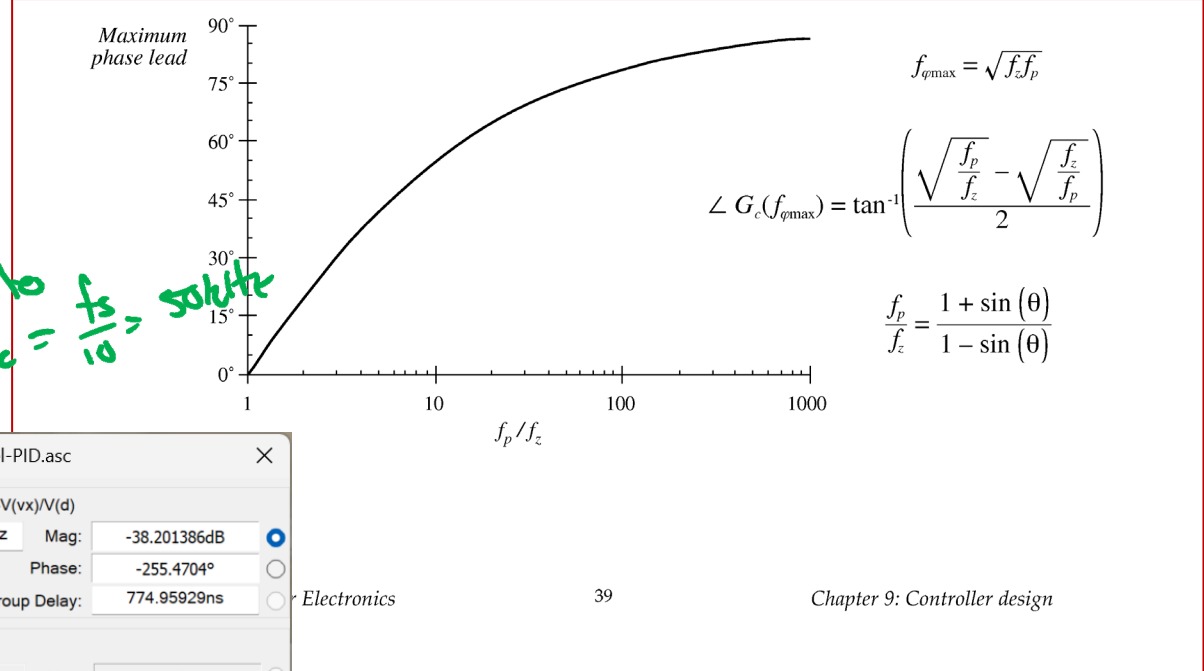if we try to set $f_c = \frac{f_s}{10}$, solve



SwitchingModel-PID.asc

Cursor 1

-V(vx)/V(d)

Freq: 50.118723KHz Mag: -38.201386dB

Phase: -255.4704°

Group Delay: 774.95929ns

Cursor 2

Freq: -- N/A-- Mag: -- N/A--

Phase: -- N/A--

Group Delay: -- N/A--

Ratio (Cursor2 / Cursor1)

Freq: -- N/A-- Mag: -- N/A--

Phase: -- N/A--

Group Delay: -- N/A--



PD Design: $f_c=50\text{kHz}$, $\theta=80^\circ$

```

.lib switch.lib
.lib myParts.lib
;.tran 0 500m 250m
.ac dec 100 10 1Meg
.op

.param Vg=12 V=60 R=10 D=.8
.param Vref=3 H=1/20 Vm=4
.param L=5u C=100u

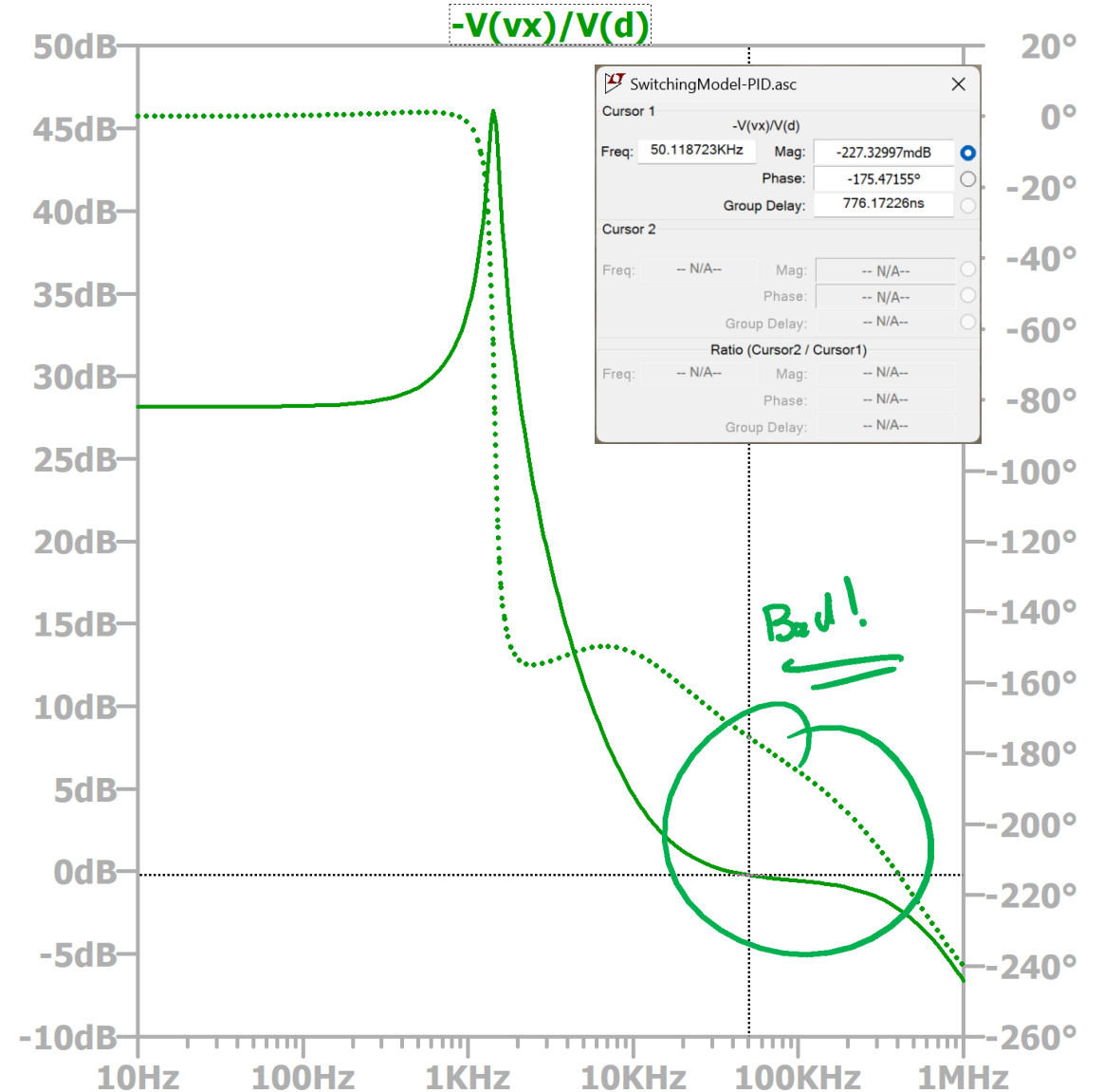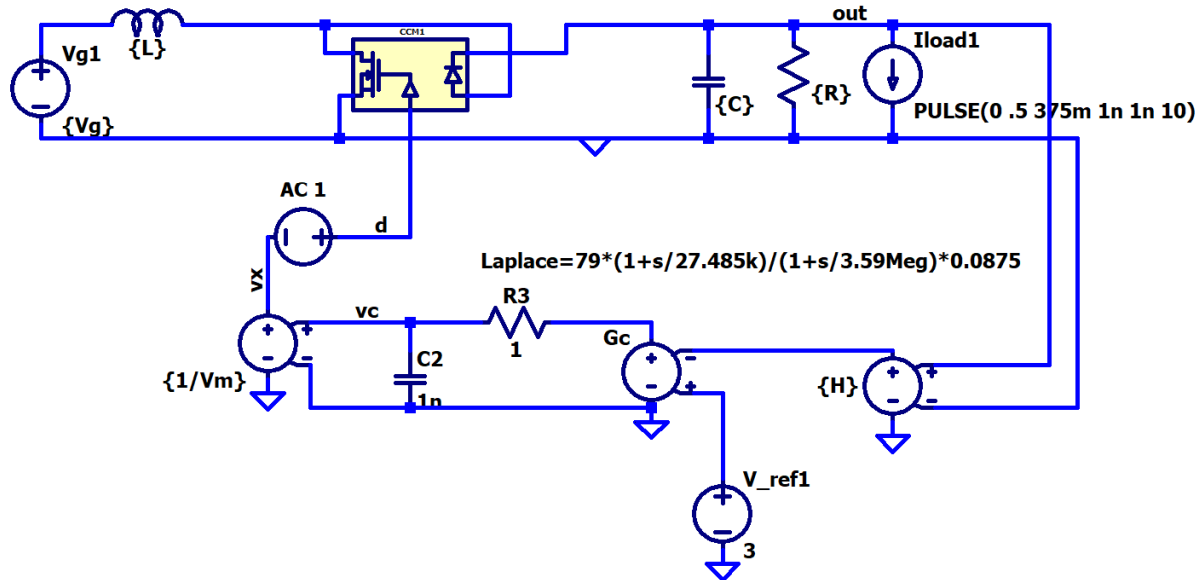.ic V(out)=60 I(L1)={6*5} V(vc)={D*Vm}
    
```




Design: $f_c = 5\text{kHz}$

```
.lib switch.lib
.lib myParts.lib
;tran 0 500m 250m
.ac dec 100 10 1Meg
.op


.param Vg=12 V=60 R=10 D=.8
.param Vref=3 H=1/20 Vm=4
.param L=5u C=100u

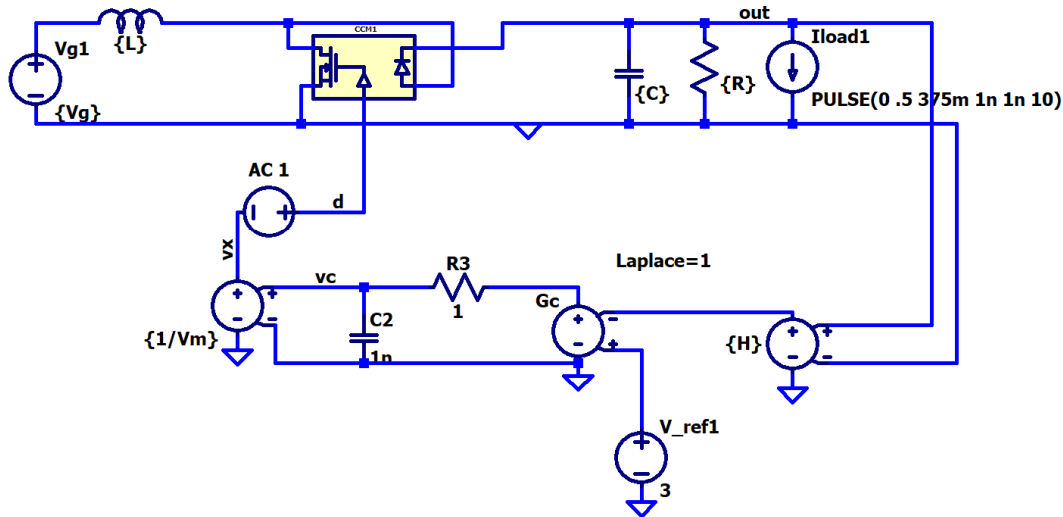.ic V(out)=60 I(L1)={6*5} V(vc)={D*Vm}
```




Targets:

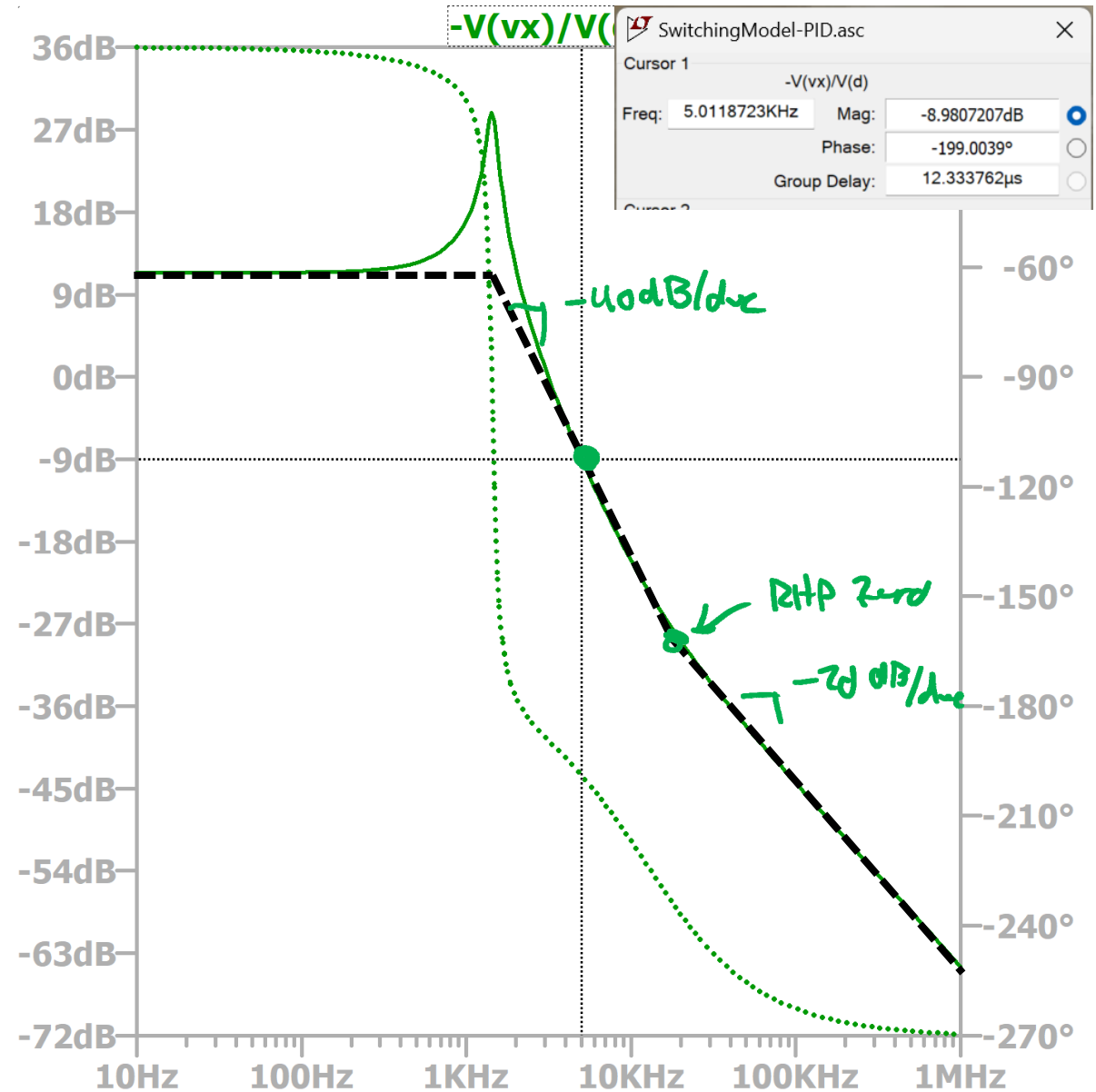- Set $f_c = 5\text{kHz}$
- Set $\varphi_m = 52^\circ$
- Add PI zero at $f_c/10$



Compensator Design

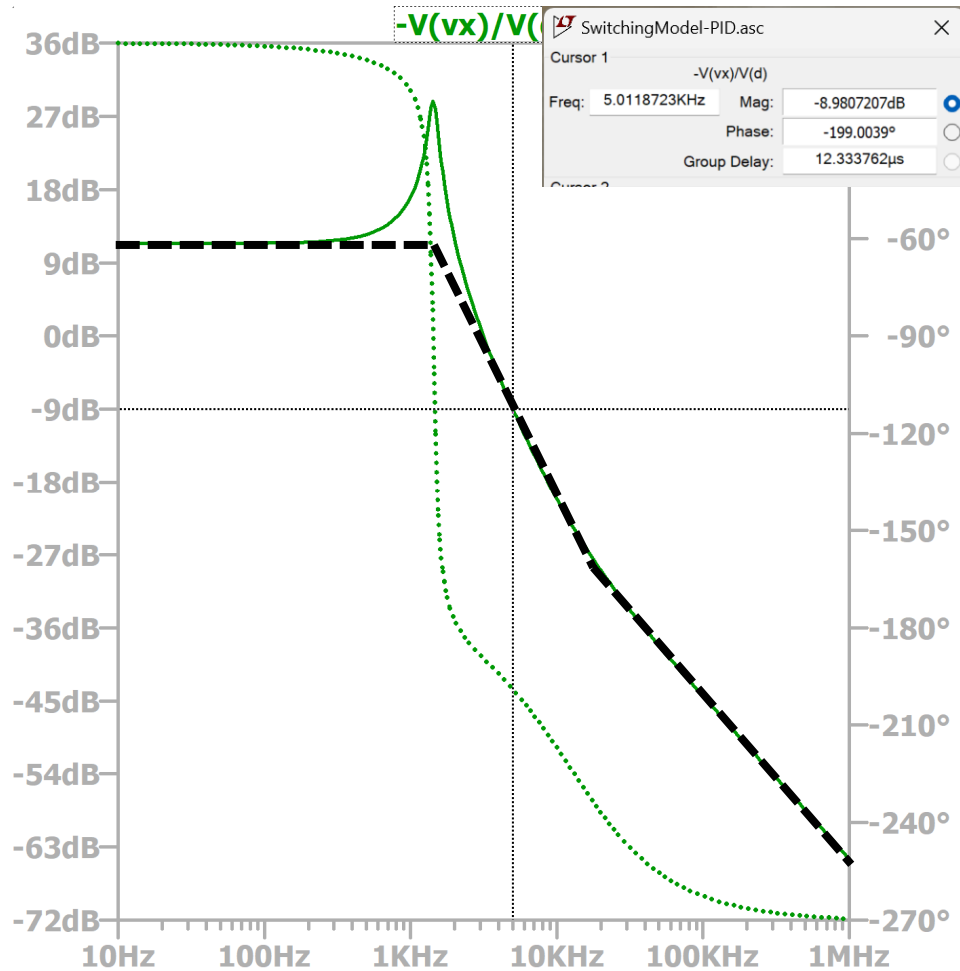

PD

$$\theta = \varphi_m + 19^\circ = 52^\circ + 19^\circ = 71^\circ$$

PI :

$$\text{set } f_{zi} = \frac{f_c}{10} = 500 \text{ Hz}$$



$$f_z = f_c \sqrt{\frac{1 - \sin(\theta)}{1 + \sin(\theta)}}$$

$$f_p = f_c \sqrt{\frac{1 + \sin(\theta)}{1 - \sin(\theta)}}$$

$$G_{c0} = \sqrt{\frac{f_z}{f_p}}$$

$$G_c = 0.46 \left(1 + \frac{2\pi(500\text{Hz})}{s} \right) \frac{\left(1 + \frac{s}{2\pi(816\text{Hz})} \right)}{\left(1 + \frac{s}{2\pi(30.6\text{kHz})} \right)}$$

AC simulation

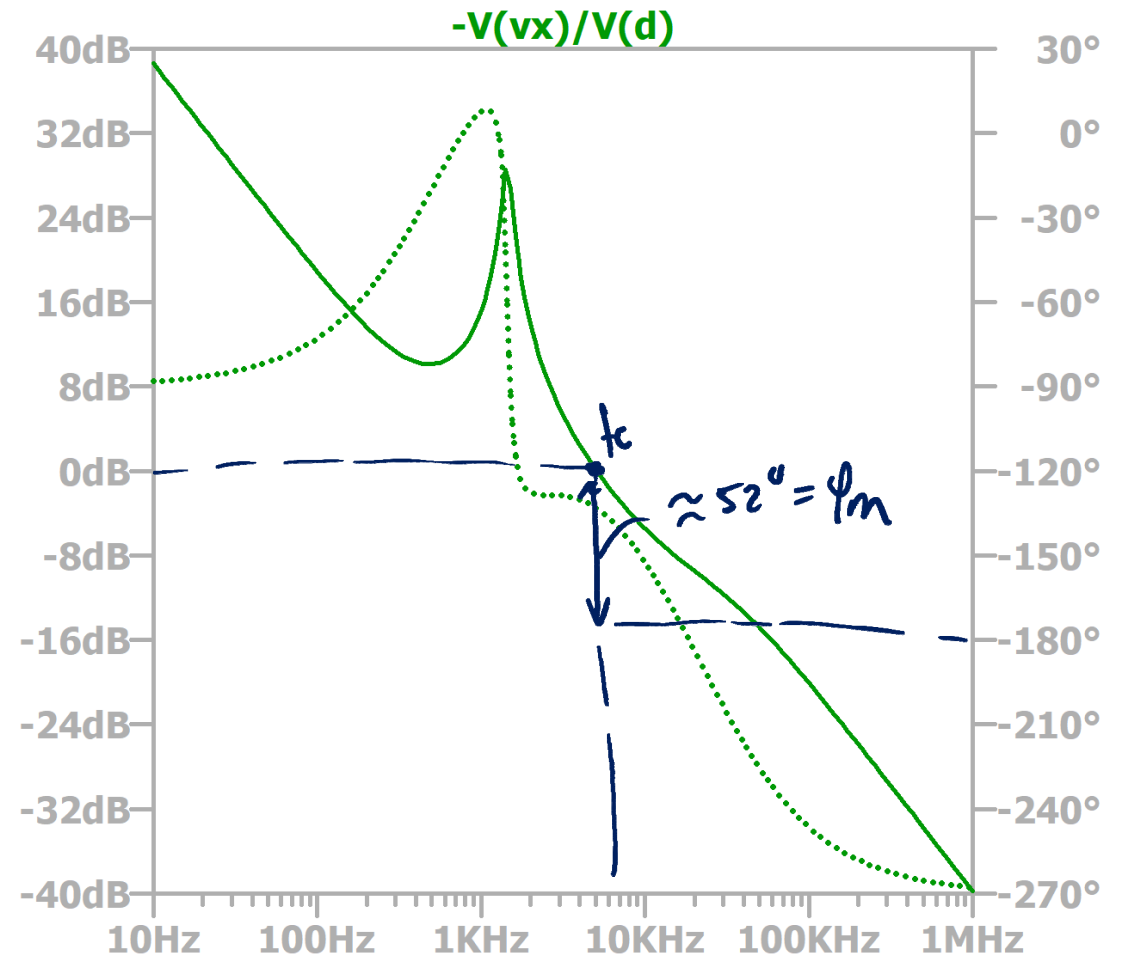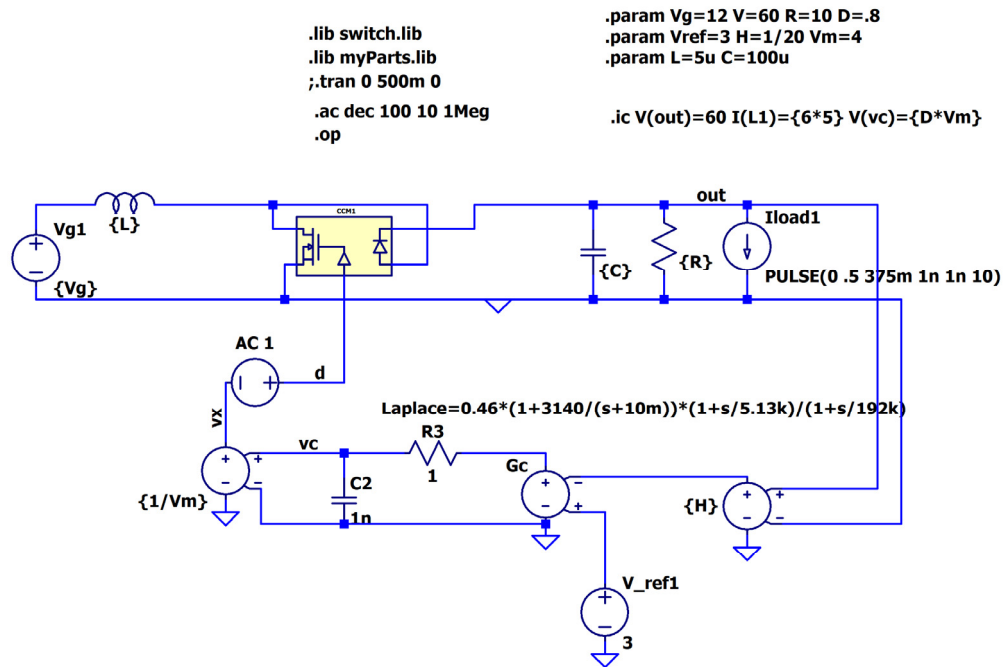

Transient Simulation

Characteristic of
RHP zero

