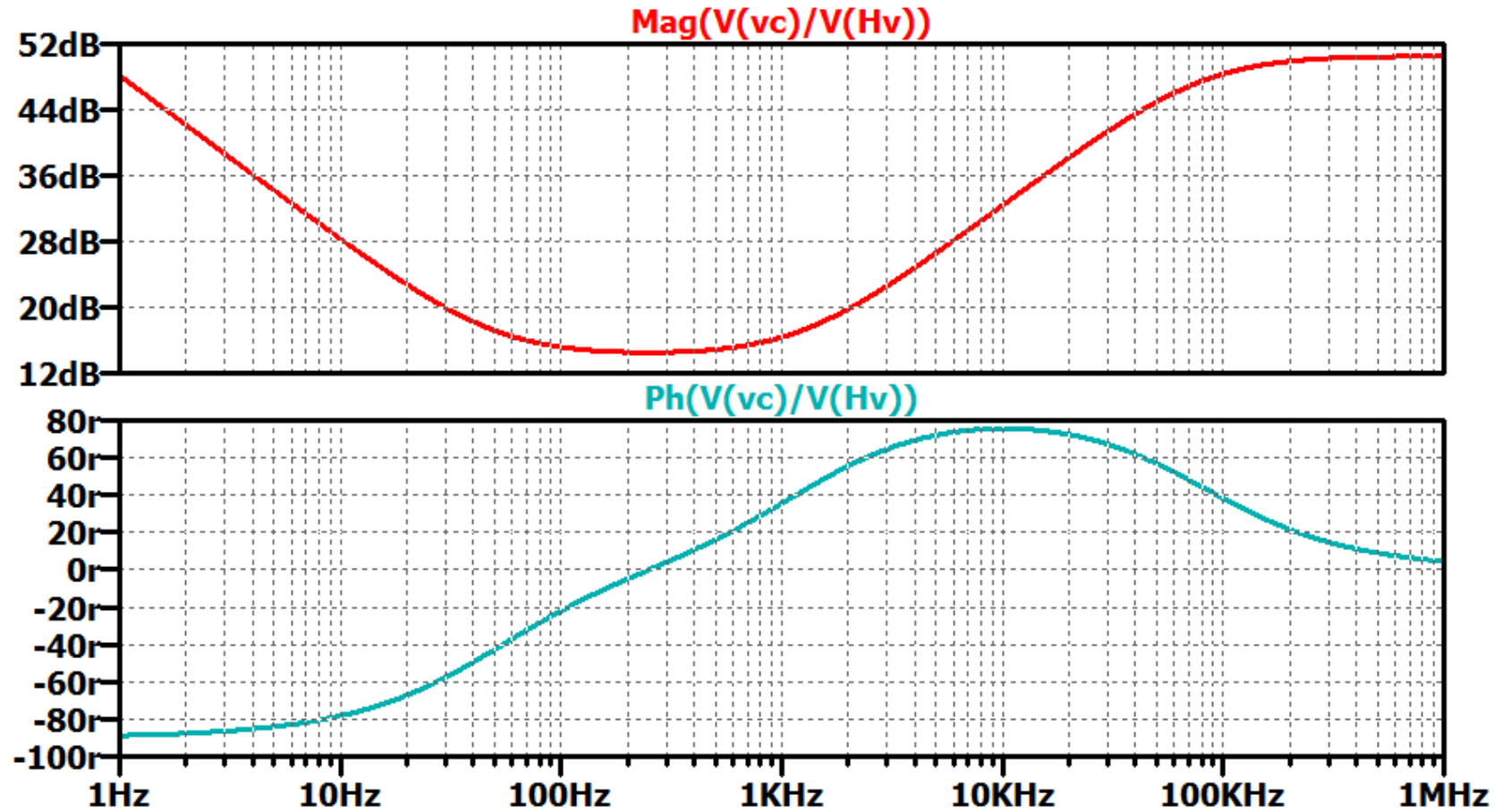


Complete Compensator




$$G_c = G_{cm} \left(1 + \frac{2\pi(50\text{Hz})}{s} \right) \frac{\left(1 + \frac{s}{2\pi(1.2\text{kHz})} \right)}{\left(1 + \frac{s}{2\pi(81\text{kHz})} \right)}$$

Compensator Realization




Compensator TF

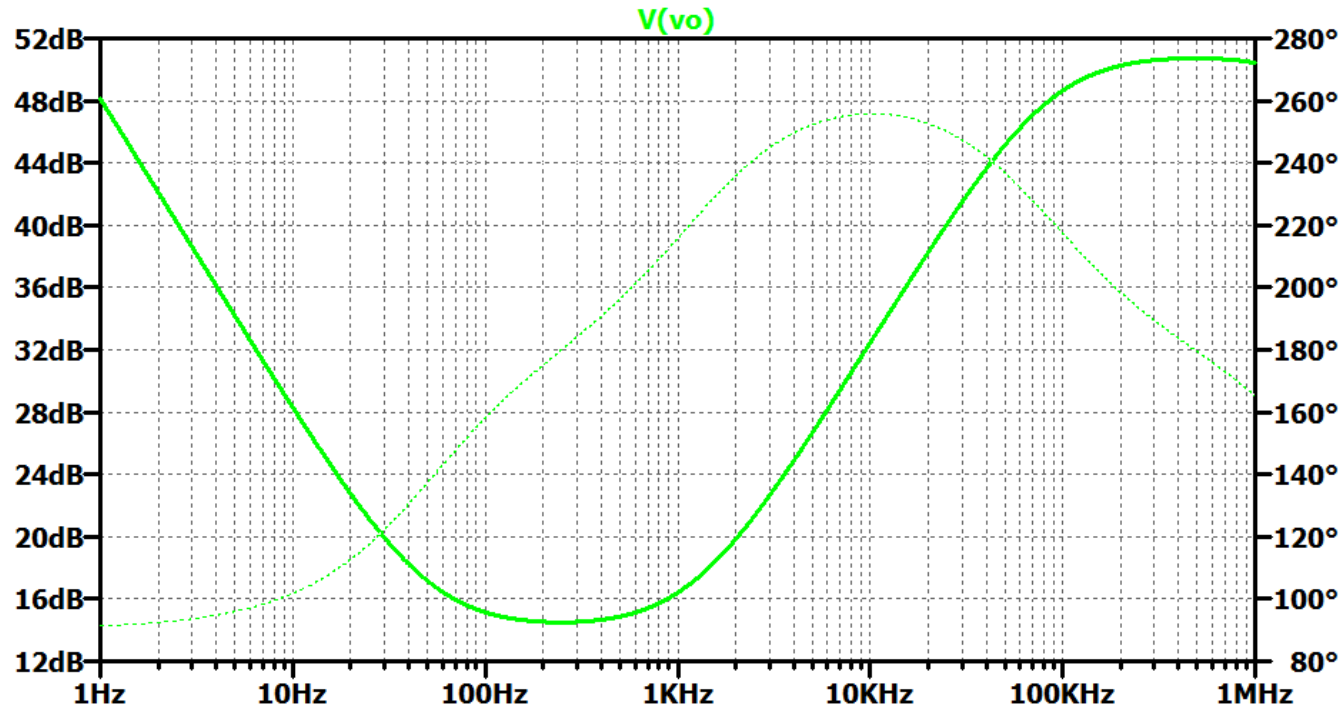

.ac dec 1000 1 1Meg

.lib opamp.sub

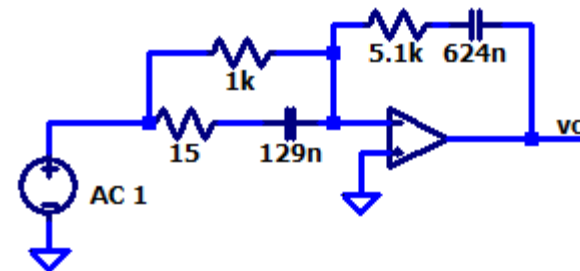

Op-amp GBW

