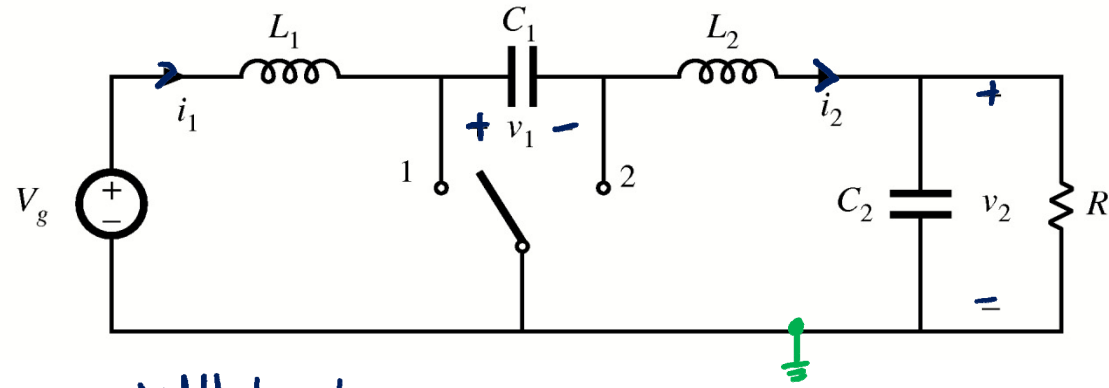


Ćuk Converter



Robert Middlebrook
PhD in 1955 on FET modeling
- "Design-oriented Analysis"


Stokodon Ćuk (PhD 1976) → Prof @ Caltech
- Average Modeling of SMPS

Dragan Maksimović (PhD 1989)
- Synthesis of Power Converters


Robert Erickson (PhD 1982)
- large-signal models of SMPS

→ Authors of our textbook
↳ Both Professors @ University of Colorado

Cuk Equivalent Circuits

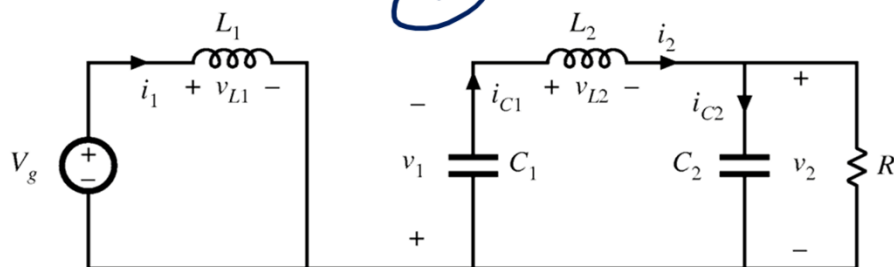

Apply SRA

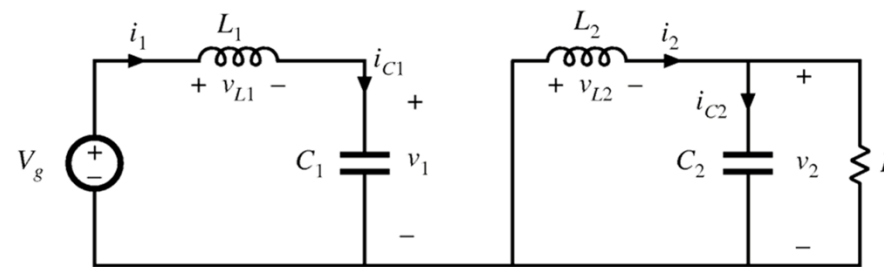

$$v_{L1} = v_g$$

$$v_{L2} = -v_1 - v_2$$

$$i_{C1} = I_2$$

$$i_{C2} = I_2 - \frac{v_2}{R}$$

$$v_{L1} = v_g - v_1$$

$$v_{L2} = -v_2$$

$$i_{C1} = I_1$$


$$i_{C2} = I_2 - \frac{v_2}{R}$$

We want to write

$$v_{Cx} = f(v_{src} \text{ \& } v_{Cx}, \text{ or } I_x R_y)$$

$$i_{Cx} = f(I_{src} \text{ \& } I_{Cx}, \text{ or } \frac{v_x}{R_y})$$

Cuk Converter Waveforms

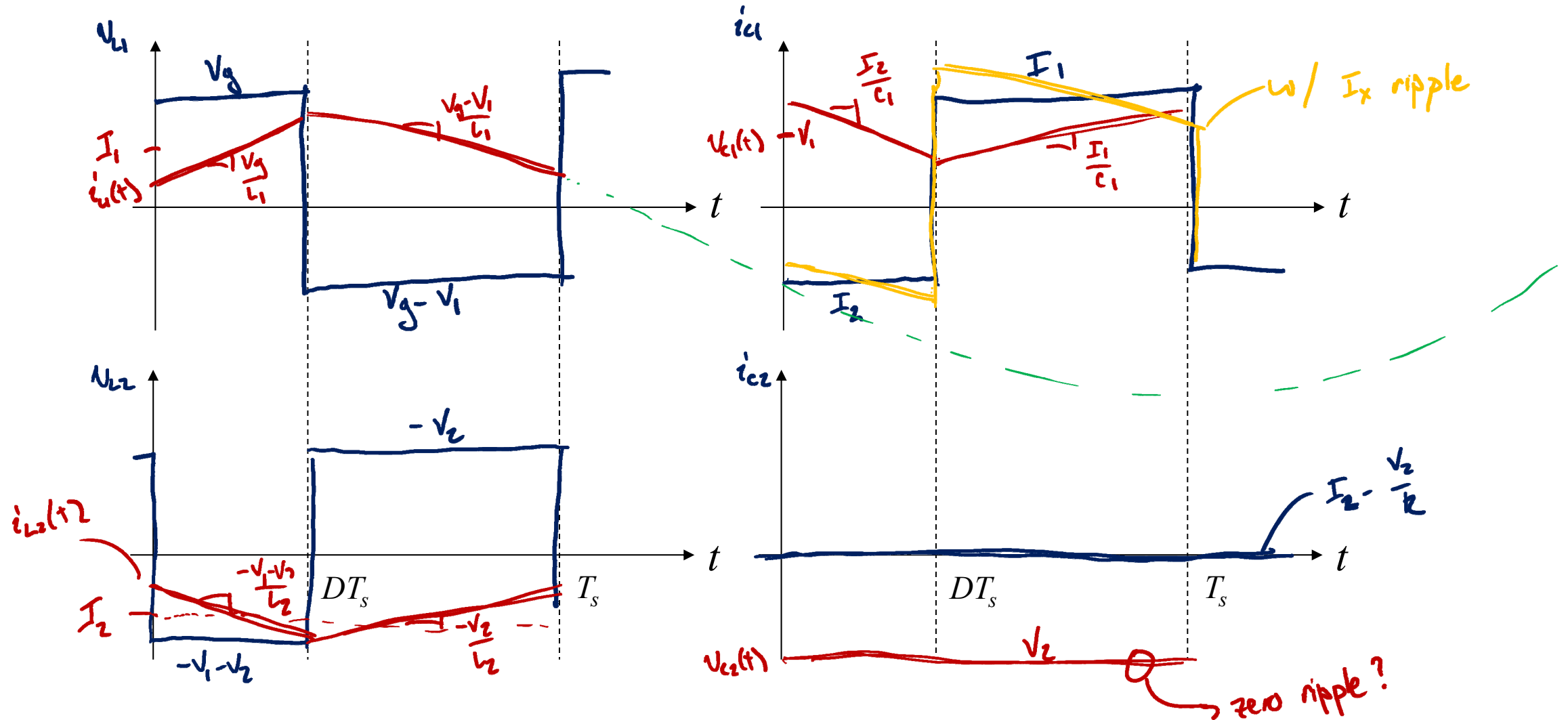

Waveform Averaging

Volt-second Balance:

$$\langle v_{L1} \rangle_{T_s} = \phi = V_g - D'V_1 \rightarrow$$

$$\langle v_{L2} \rangle_{T_s} = \phi = D(-V_1) - V_2 \rightarrow$$

$$V_1 = \frac{V_g}{D'}$$

$$V_2 = -DV_1$$

$$V_2 = -\frac{D}{D'} V_g$$

$$M(D) = -\frac{D}{D'} = \frac{V_2}{V_g}$$

Cap-Charge Balance

$$\langle i_{C1} \rangle_{T_s} = \phi = DI_2 + D'I_1 \rightarrow$$

$$\langle i_{C2} \rangle_{T_s} = \phi = I_2 - \frac{V_2}{R} \rightarrow$$

$$I_1 = -\frac{D}{D'} I_2$$

$$I_2 = \frac{V_2}{R}$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V_2^2/R}{V_g \cdot I_1} = \frac{V_2 I_2}{V_g \left(\frac{D}{D'} I_2\right)} = \frac{-\left(\frac{D}{D'}\right) V_g I_2}{V_g \left(\frac{D}{D'}\right) I_2} = 1 \checkmark$$

- 100% efficiency in a lossless converter in steady-state

Cuk Conversion Ratio

