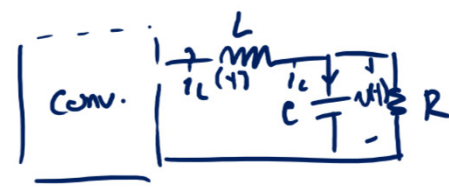


Ripple in Second Order Filters



$$\langle i_c \rangle_{T_s} = I_L - \frac{V}{R} = \phi$$


$$I_L = \frac{V}{R}$$

When SRA trivializes our calculation we need to relax it.

When we approx. $i_c(t) = I_L$
 $i_c(t) = \phi$ always in steady-state
 $\Delta v_c = \phi$

Relax SRA
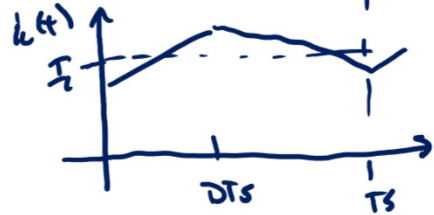
$$i_c(t) = I_L + \text{tri}(D, \Delta i_L)$$





$$i_c = C \frac{dv_c}{dt}$$

$$2\Delta v = \frac{1}{C} \int_{\text{positive portion}} i_c dt$$

$$2\Delta v = \frac{1}{C} \frac{1}{2} \frac{T_s}{2} \Delta i_L \rightarrow$$
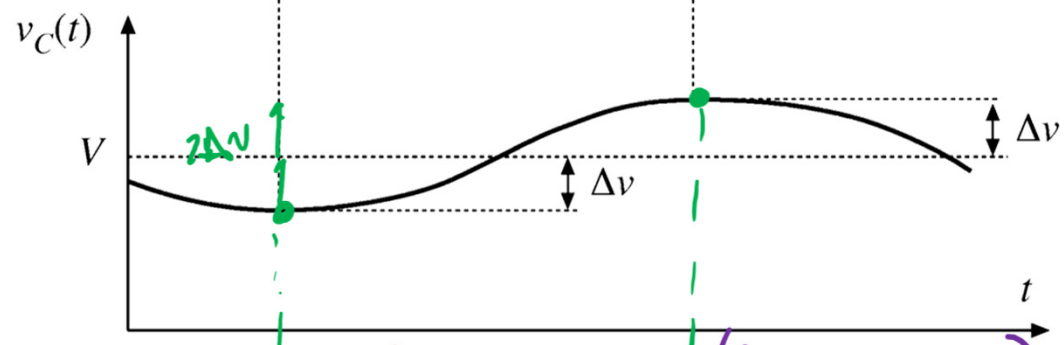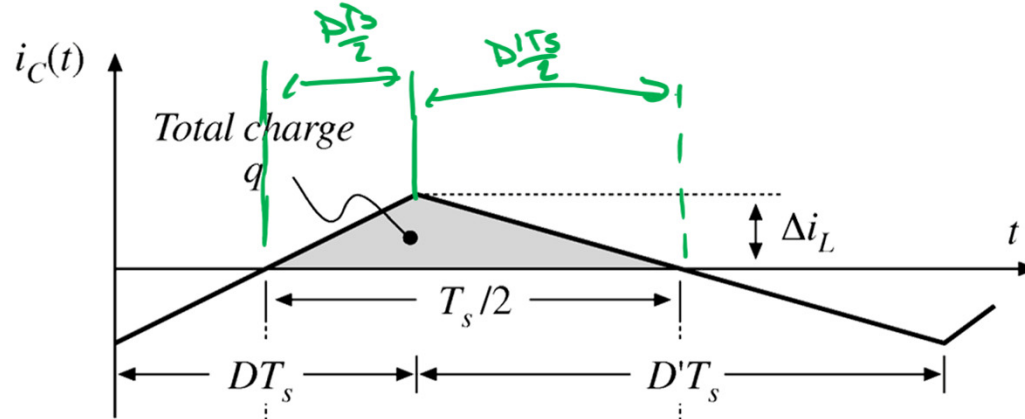
$$\Delta v_c = \frac{1}{8C} T_s \Delta i_L$$




from previous (for Buck)

$$\Delta i_L = \frac{V_g}{2L} D D' T_s$$

$$\Delta v_c = \frac{1}{8C} T_s^2 D D' V_g$$

Nonideal Boost Converter

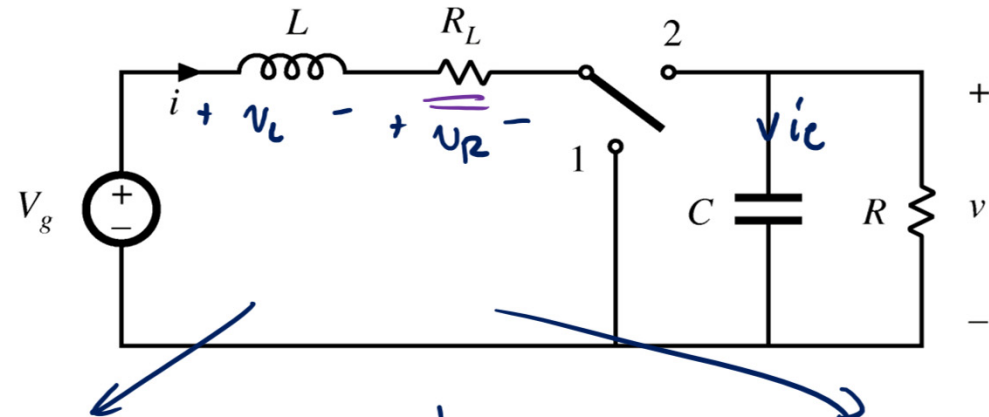

$$\begin{aligned}
 v_L(t) &= v_g - v_R(t) \\
 &= v_g - i(t) R_L \\
 &= v_g - I_L R_L \quad \text{SRA.} \\
 i_c(t) &= -\frac{v}{R}
 \end{aligned}$$

$$v_L(t) = v_g - I_L R_L - v$$

$$i_c(t) = -\frac{v}{R} + I_L$$

Volt-sec balance

$$\langle v_L \rangle_{T_s} = 0 = v_g - I_L R_L - D'v$$

Cap-Q balance

$$\langle i_c \rangle_{T_s} = 0 = D'I_L - \frac{v}{R}$$

Boost Conversion Ratio with Losses

$$\phi = V_g - I_L R_L - D'V$$

$$\phi = D'I_L - \frac{V}{R} \rightarrow I_L = \frac{V}{RD'}$$

$$\phi = V_g - R_L \frac{V}{RD'} - D'V$$

$$V \left(D' + \frac{R_L}{RD'} \right) = V_g$$


$$M = \frac{V}{V_g} = \frac{1}{D' + \frac{R_L}{RD'}}$$

Let's write this as $M = M_{ideal} \cdot f(R_L, R, D)$

$$M = \left(\frac{1}{D'} \right) \left(\frac{1}{1 + \frac{R_L}{RD'^2}} \right)$$

\uparrow M_{ideal} \uparrow $f(\cdot)$

Nonideal Boost Output Voltage

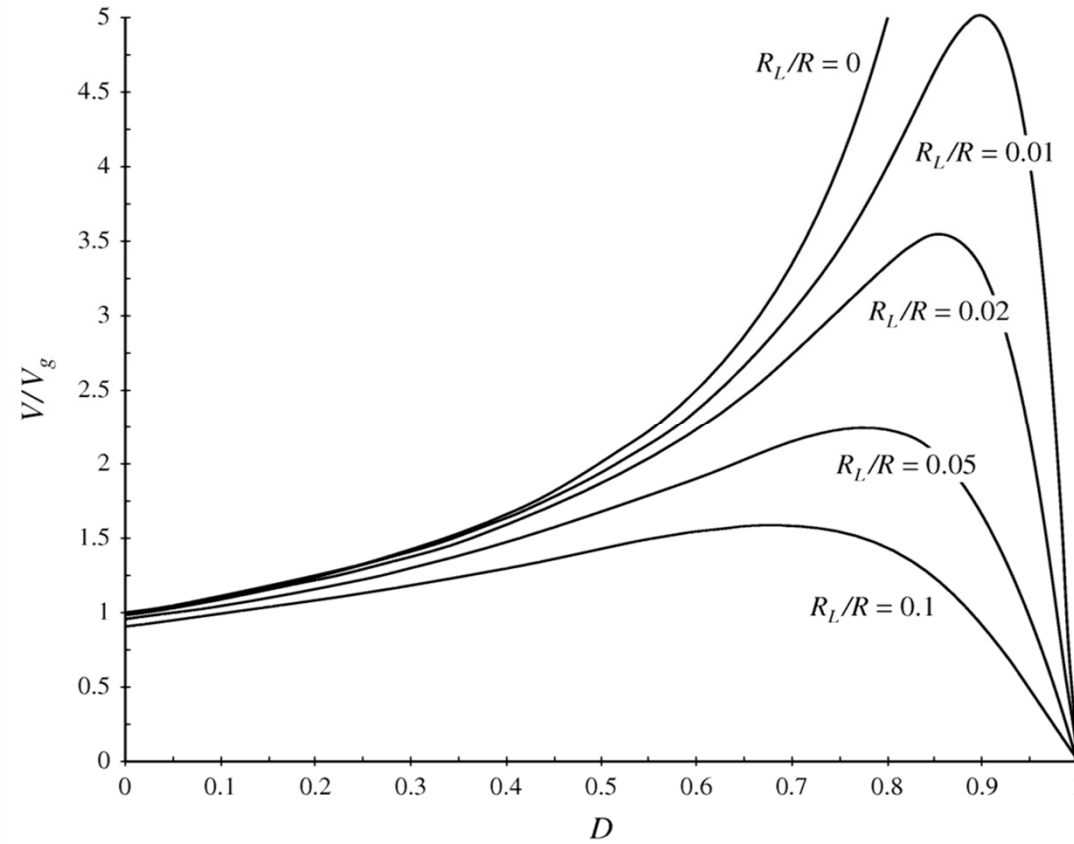

$$M = \frac{1}{D'} \left(1 + \frac{R_L}{RD'^2} \right)$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{v^2/R}{V_g I_L} = \frac{v^2/R}{V_g \frac{v}{RD'}} = \frac{v}{V_g \frac{1}{D'}} = \frac{v}{V_g} D'$$

$$\eta = M \cdot \frac{1}{M_{ideal}} = (\text{Mideal } f(\cdot)) \frac{1}{M_{ideal}}$$

$$\eta = f(\cdot) = \frac{1}{1 + \frac{R_L}{RD'^2}}$$


$$M = M_{ideal} \cdot \eta$$

with losses

General result for averaged converters including conduction losses

Boost Converter Efficiency
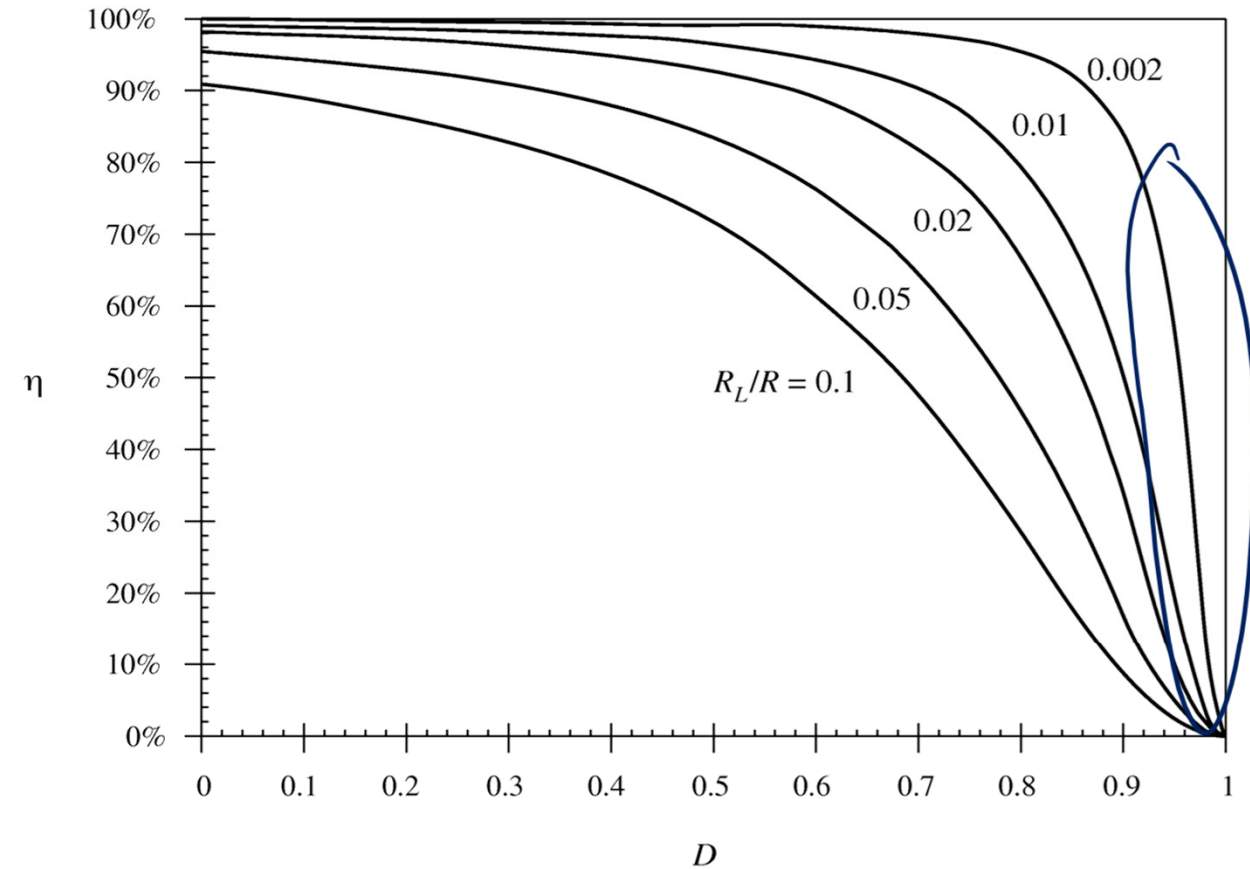
$$\eta = \frac{1}{1 + \frac{R_L}{D'^2 R}}$$





Equivalent Circuit Models

construct on SRA + "averaged equivalent circuit" that matches the equations derived by v-i / e-q balancing.

$$\langle v_L \rangle |_{T_s} = \phi = V_g - I_L R_L - D'V \rightarrow \text{KVL equation}$$

$$\langle i_C \rangle |_{T_s} = \phi = D'I_L - \frac{V}{R} \rightarrow \text{KCL equation}$$

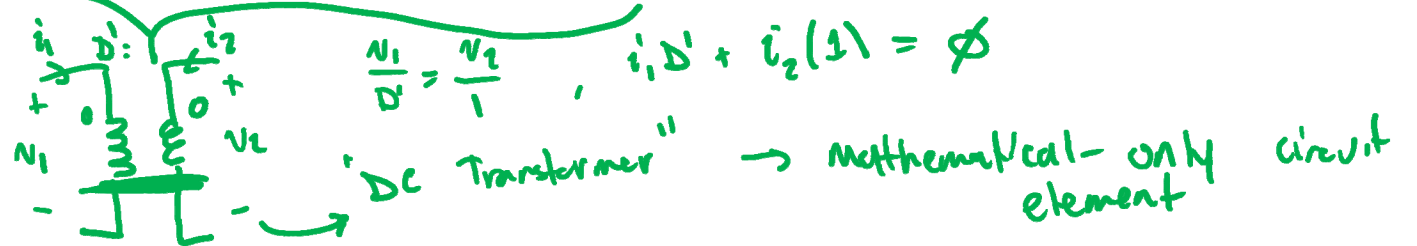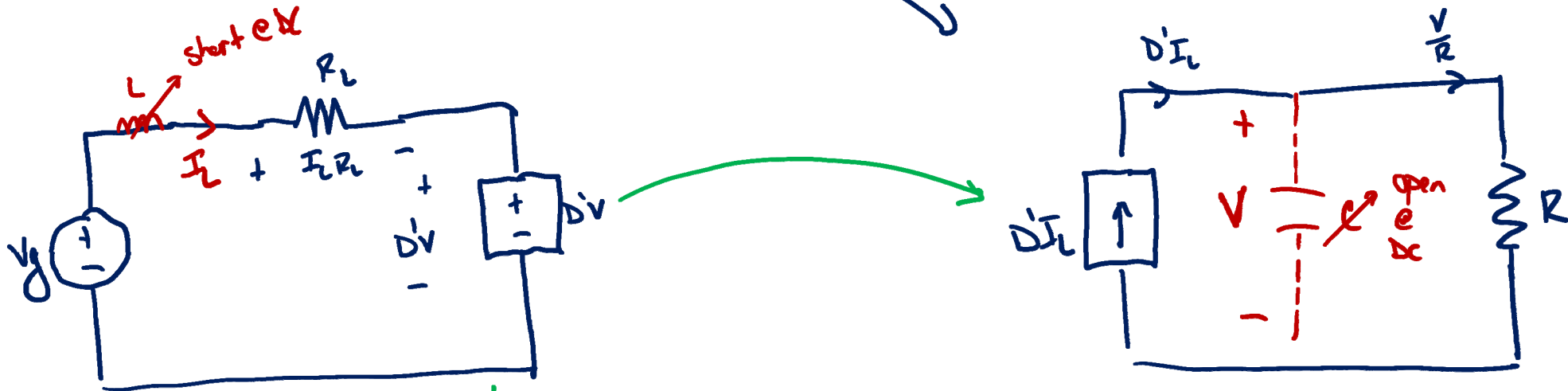

Boost Equivalent Circuit Model

