
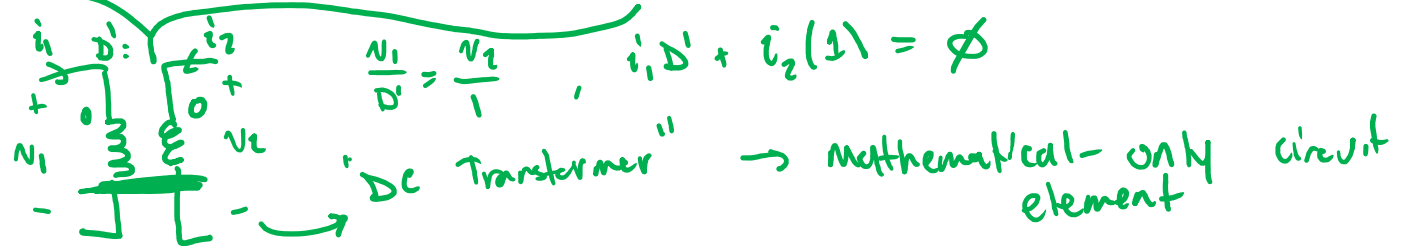


Equivalent Circuit Models

construct an "averaged equivalent circuit" that matches the equations derived by SRA + v-s / e-Q balancing.

$$\langle v_L \rangle |_{T_s} = \phi = V_g - I_L R_L - D'V \rightarrow \text{KVL equation}$$


$$\langle i_C \rangle |_{T_s} = \phi = D'I_L - \frac{V}{R} \rightarrow \text{KCL equation}$$

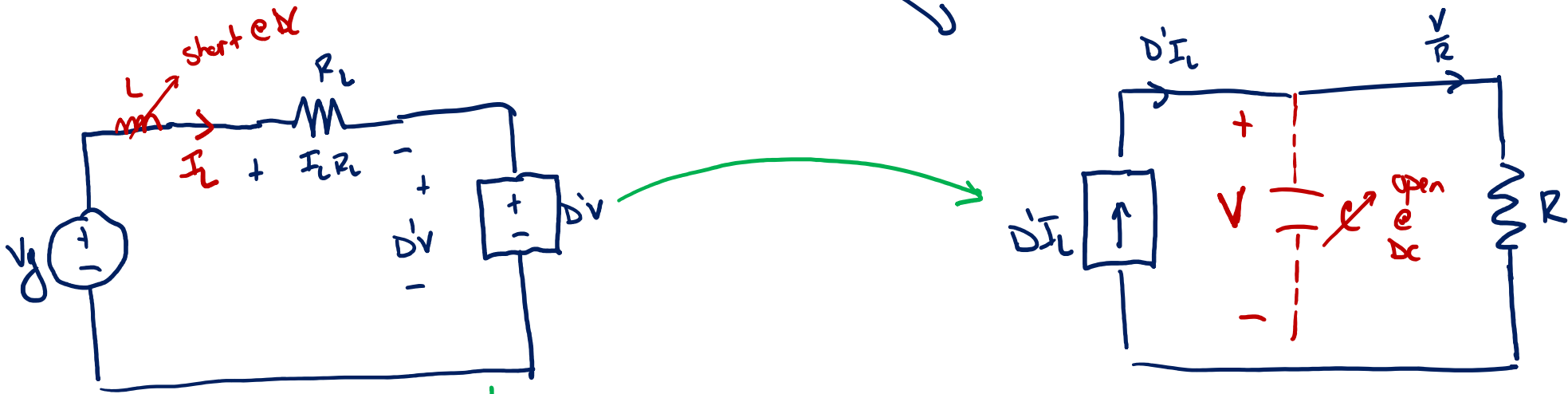

$$\frac{N_1}{N_2} = \frac{v_1}{v_2}, \quad i_1 D' + i_2 (1) = \phi$$

"DC Transformer" → mathematical-only circuit element

Boost Equivalent Circuit Model

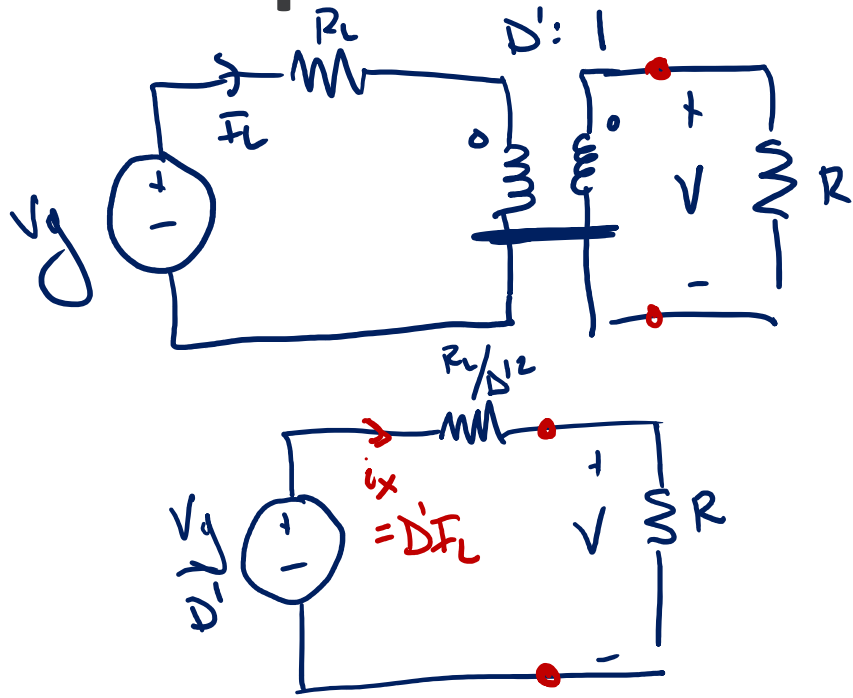


$$V = \frac{V_g}{D'} \frac{R}{R + \frac{R_L}{D'^2}} \rightarrow M = \frac{V}{V_g} = \frac{1}{D'} \frac{R}{R + \frac{R_L}{D'^2}} = \frac{1}{D'} \left(\frac{1}{1 + \frac{R_L}{RD'^2}} \right)$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V \cancel{i_x}}{D' V_g \cancel{i_x}} = D' \frac{V}{V_g} = \frac{1}{M_{ideal}} M = \eta$$


↑
Mideal

The DC Transformer Model

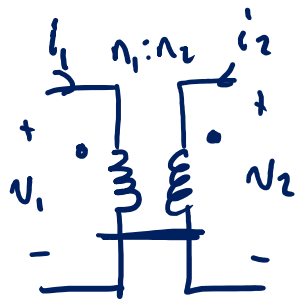


$$\left. \begin{aligned} \frac{v_1}{n_1} &= \frac{v_2}{n_2} \\ n_1 i_1 + n_2 i_2 &= \phi \end{aligned} \right\}$$
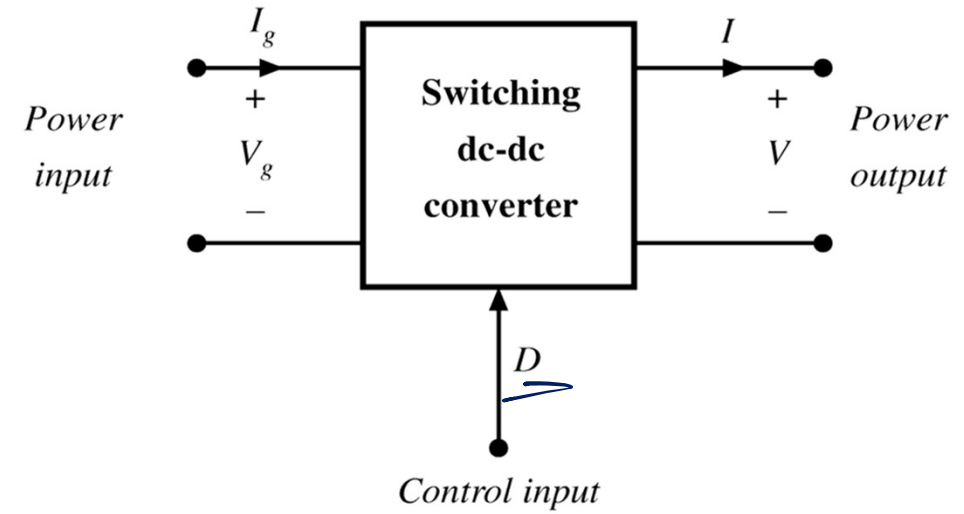
$$\frac{v_2}{v_1} = \frac{n_2}{n_1} \leftrightarrow M(D)$$




Buck Converter: Input Port Model

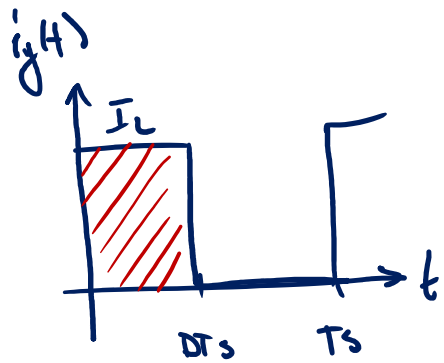

$$I_g = \frac{1}{T_s} \int_0^{T_s} i_g(t) dt$$




$$I_g = DI_L$$

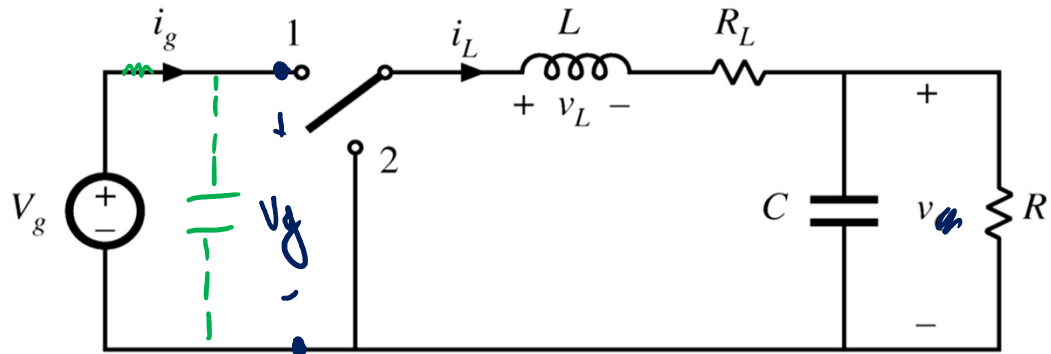

when pulsating waveform applied to a source, need to average the source for an additional equation

$$\langle v_L \rangle_{T_s} = \phi = DV_g - I_L R_L - V$$

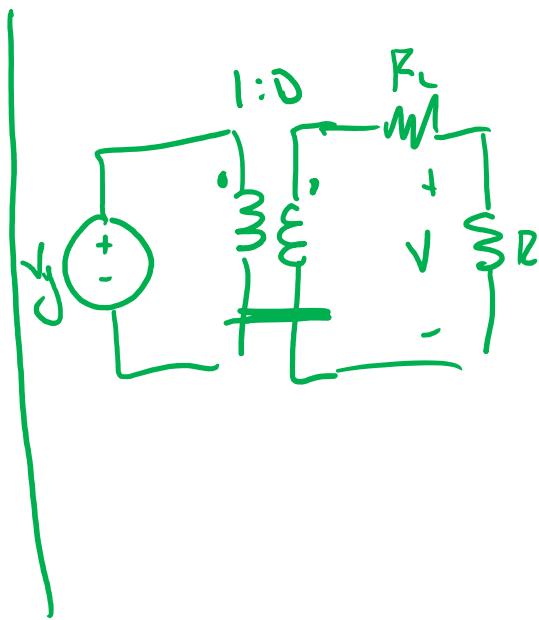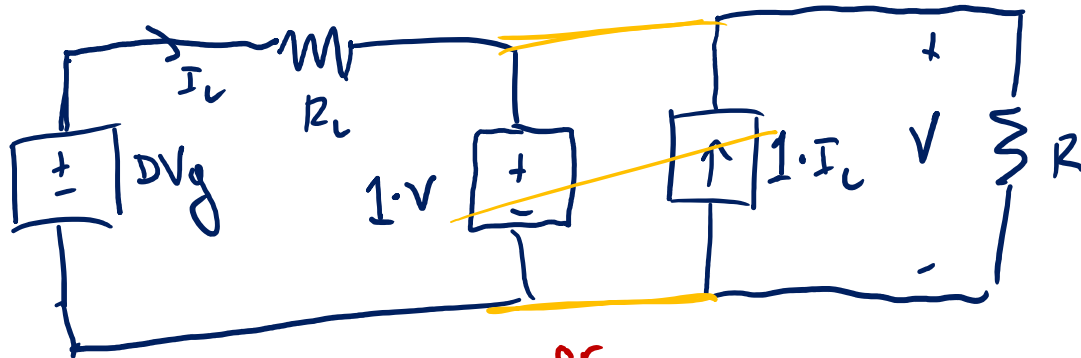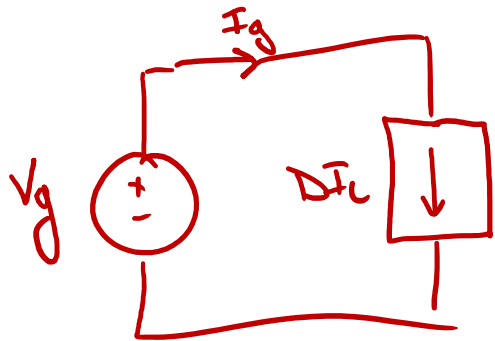
$$\langle i_C \rangle_{T_s} = \psi = I_L - \frac{V}{R}$$




$I = DI_L$

or $I = \frac{V}{R}$

Semiconductor Conduction Loss Models

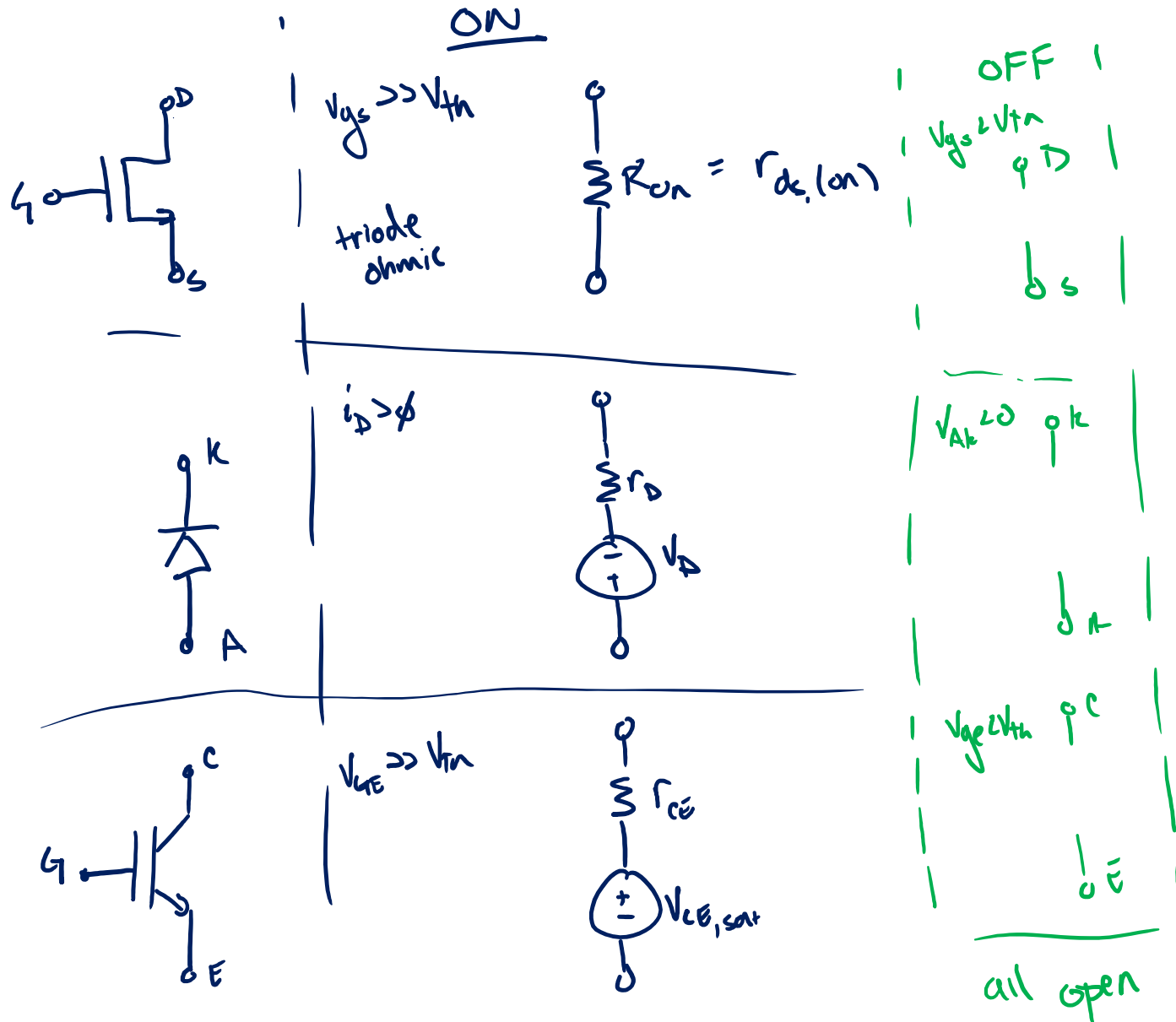

MOSFET vs IGBT

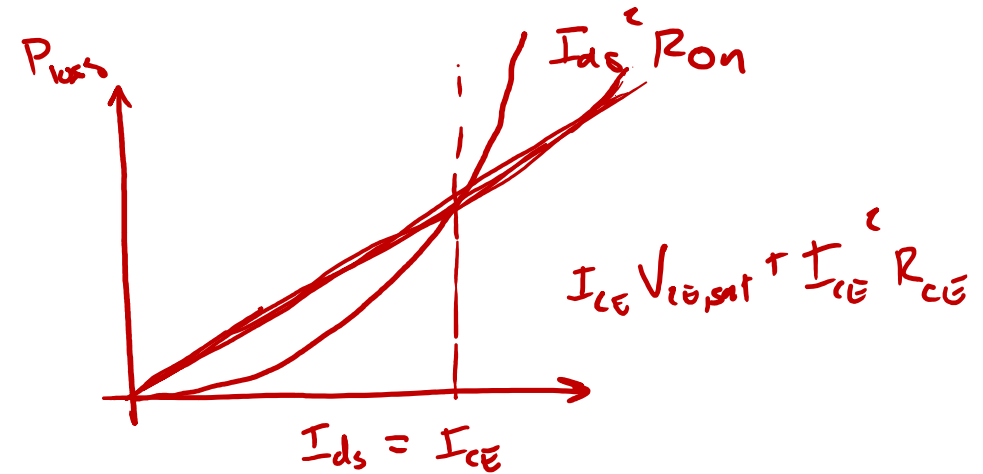

Schottky Diode

