
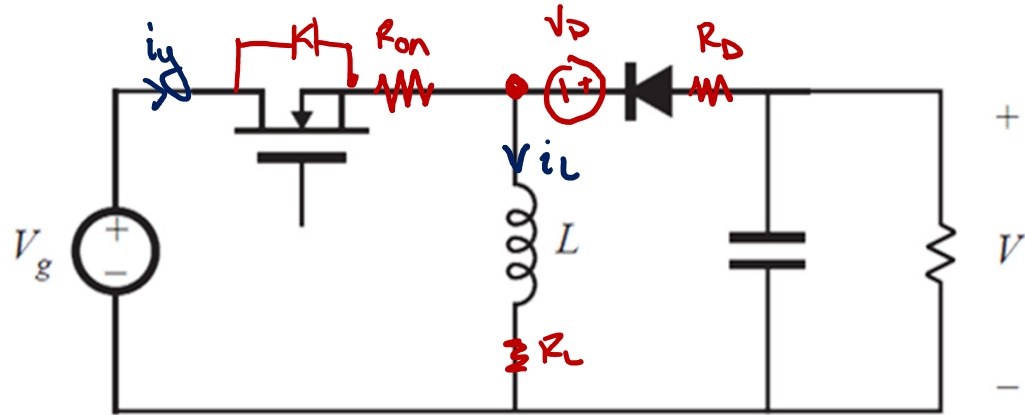


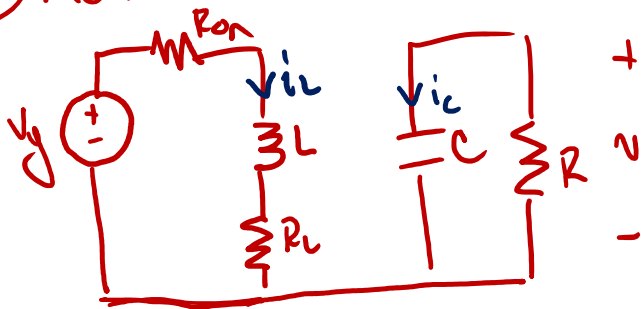
Buck-Boost Converter with Nonideal Semiconductors



① MOSFET ON



② Diode ON

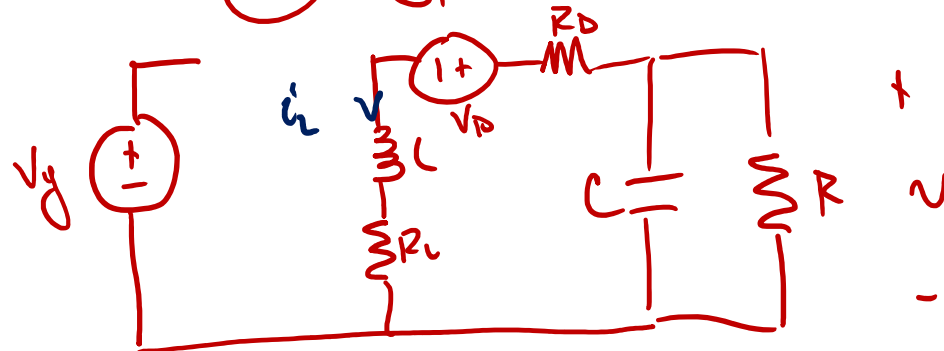

$$\langle v_L \rangle_{T_s} = \phi = D [V_g - I_L R_{on} - I_L R_L] + D' [V - I_L R_L - I_L R_D - V_D]$$

$$\phi = D V_g + D' V - D I_L R_{on} - D' I_L R_D - D' V_D - I_L R_L$$

$$\langle i_C \rangle_{T_s} = \phi = -\frac{V}{R} - D' I_L$$






$$\langle i_g \rangle_{T_s} = D I_L = I_g$$

Equivalent Circuit Model

$$I_g = D I_L$$

$$\phi = D V_g + D' V - D I_L R_{on} - D' I_L R_D - I_L R_L - D' V_D - I_L R_L$$

$$\phi = -\frac{V}{R} - D' I_L$$

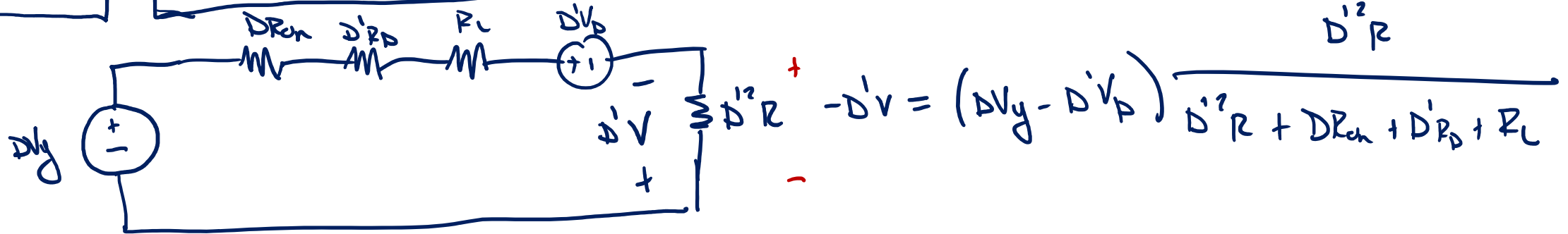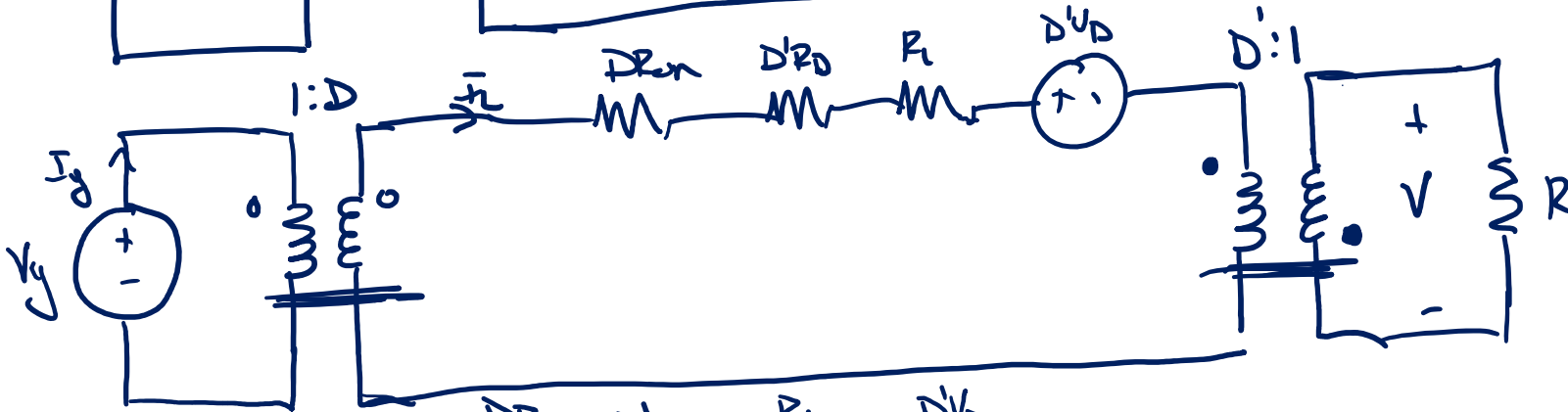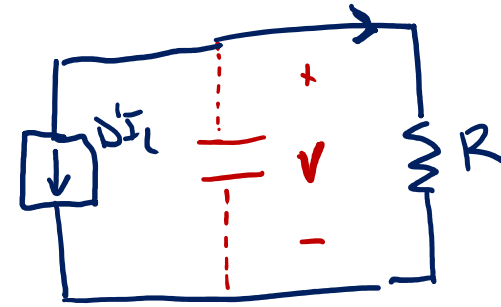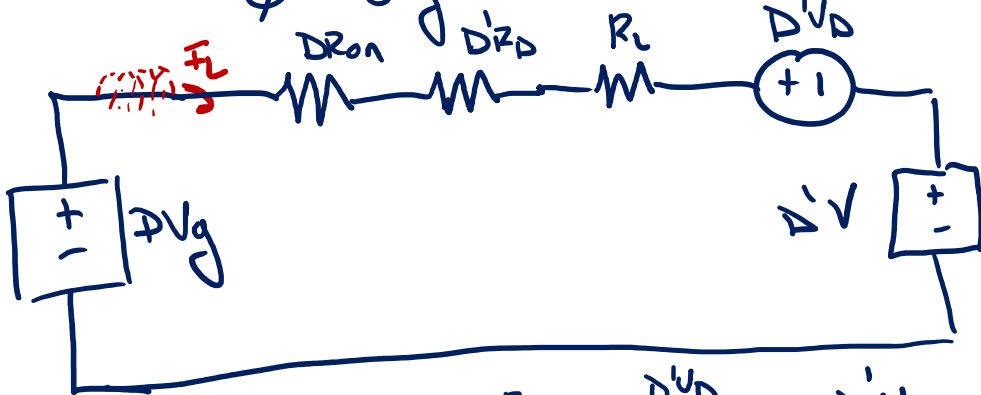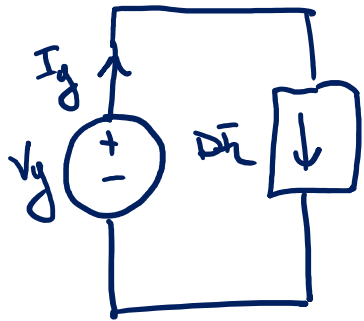

$$-D' V = (D V_g - D' V_D) \frac{D'^2 R}{D'^2 R + D R_{on} + D' R_D + R_L}$$

Circuit Solution

$$M = \frac{v}{v_g} = \frac{1}{D} \left(D - \frac{D' V_D}{v_g} \right) \frac{D'^2 R}{D'^2 R + D R_{on} + D' R_D + R_L}$$

$$M = \left(\frac{1-D}{D} \right) \underbrace{\left(1 - \frac{D' V_D}{v_g} \right)}_{\eta} \frac{D'^2 R}{D'^2 R + D R_{on} + D' R_D + R_L}$$

Mideal

η

$\frac{D' V_D}{D v_g} \rightarrow \frac{V_D}{v_g} \approx \frac{V_D}{V} \rightarrow$ % drop in η due to diode V_D

Average losses in diode V_D are $\frac{1}{T_s} \int_0^{T_s} V_D \cdot i_D dt = \frac{1}{T_s} V_D \int_0^{T_s} i_D dt = V_D \langle i_D \rangle_{T_s} = V_D I_D$


Average losses in a resistance R_x are $\frac{1}{T_s} \int_0^{T_s} v_R \cdot i_R dt = \frac{1}{T_s} \int_0^{T_s} (i_R \cdot R) i_R dt = R \frac{1}{T_s} \int_0^{T_s} i_R^2 dt = R i_{Rms}^2$

But, we are using $P_R = \frac{I_{R,DC}^2}{R} R$ X

Average vs RMS Currents

- Model uses average currents and voltages
- To correctly predict power loss in a resistor, use rms values
- Result is the same, provided ripple is small

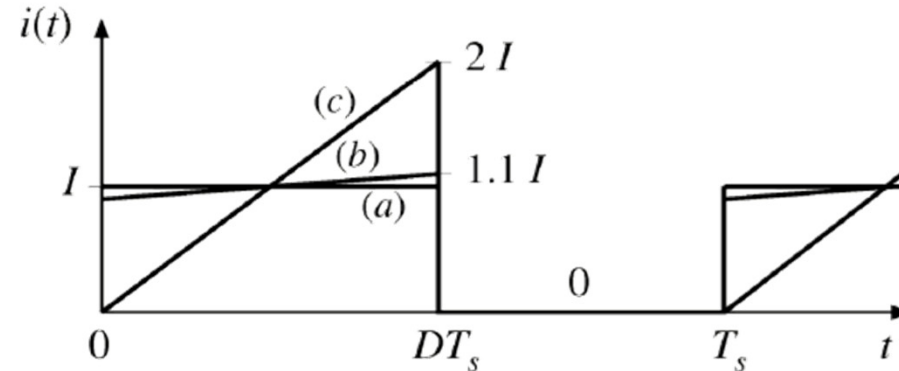MOSFET current waveforms, for various ripple magnitudes:



Inductor current ripple	MOSFET rms current	Average power loss in R_{on}
(a) $\Delta i = 0$	$I \sqrt{D}$	$D^2 R_{on}$
(b) $\Delta i = 0.1 I$	$(1.00167) I \sqrt{D}$	$(1.0033) D^2 R_{on}$
(c) $\Delta i = I$	$(1.155) I \sqrt{D}$	$(1.3333) D^2 R_{on}$

0.3% error in P_R
33% error in P_R

Chapter 4

SWITCH REALIZATION

Implementing with SPST Switches

Step 1: Implement circuit w/ only SPST switches

Use passive sign convention to look at each SPST switch

Now we have additional switching states possible

A on, B off \rightarrow ①


A off, B on \rightarrow ②

A off, B off \rightarrow dead time

A on, B on \rightarrow Very Bad
"shoot-through"

Buck converter

with SPDT switch:

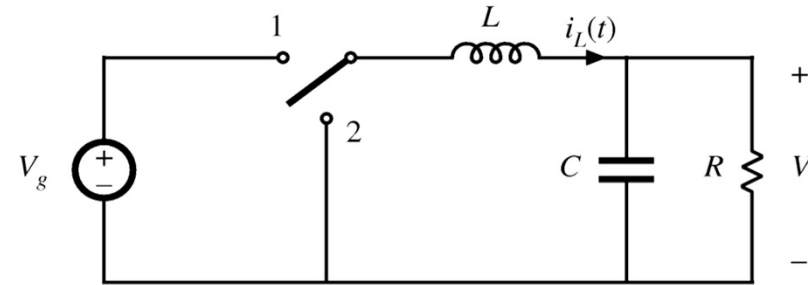

with two SPST switches:

