

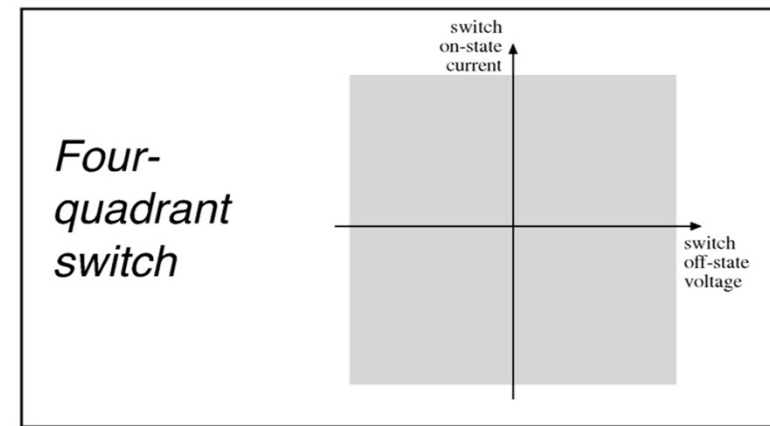
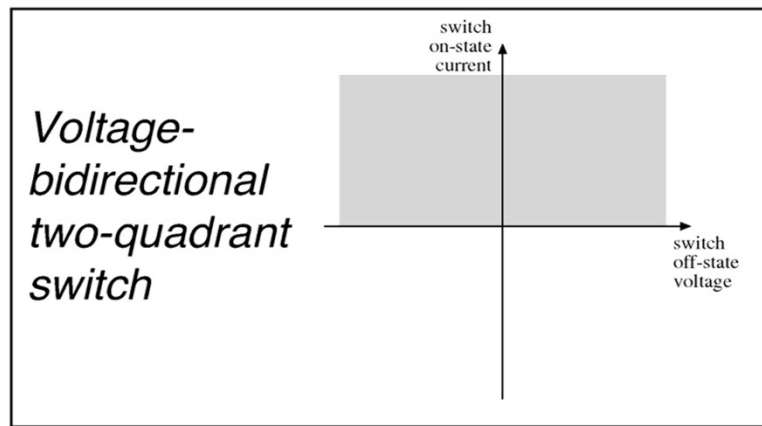
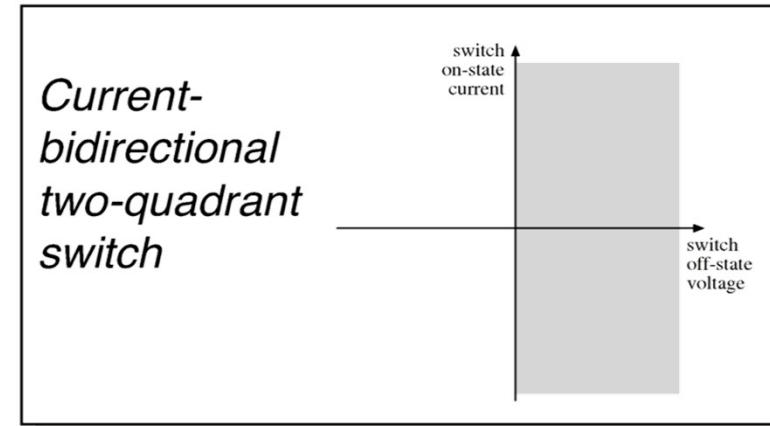
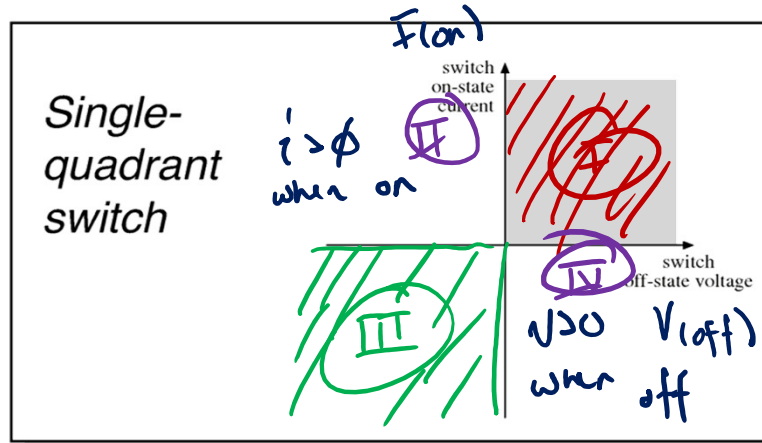


SPST Operating Quadrants



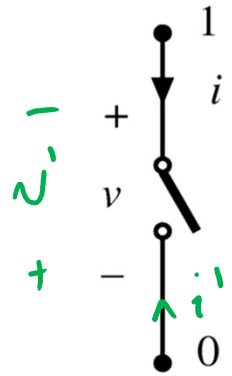


The Diode

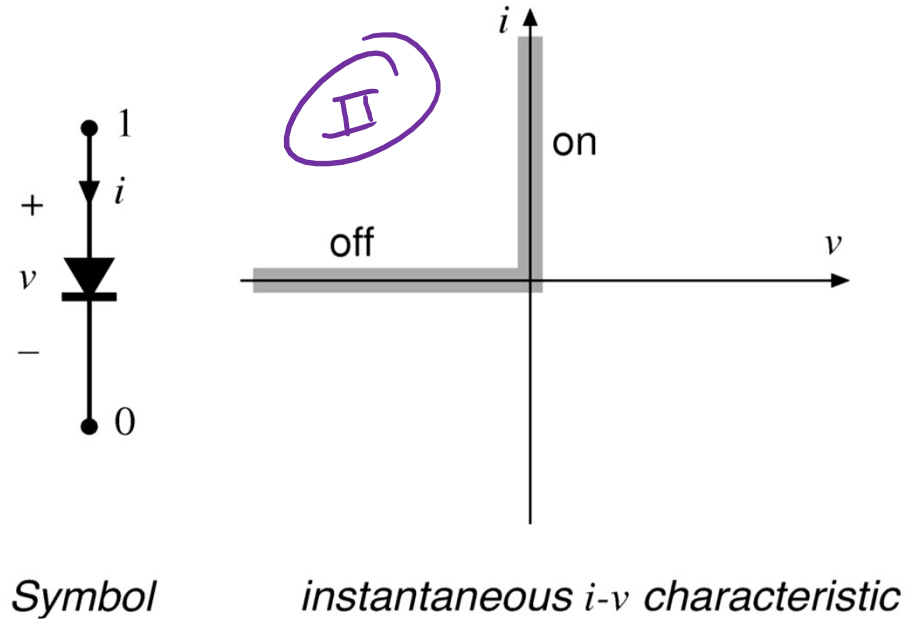

- A passive switch
- *Single-quadrant switch:*
- *can conduct positive on-state current*
- *can block negative off-state voltage*
- *provided that the intended on-state and off-state operating points lie on the diode i - v characteristic, then switch can be realized using a diode*

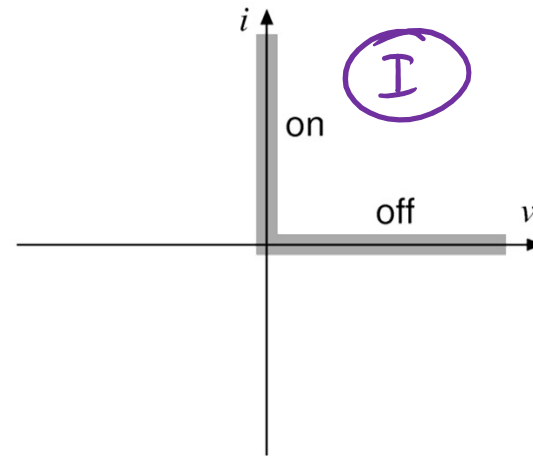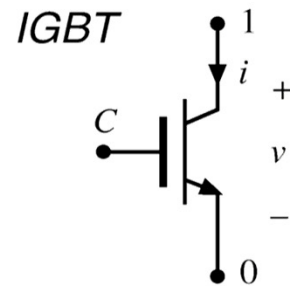
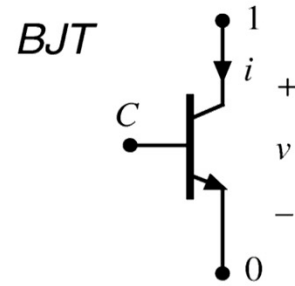
(Insulated Gate) Bipolar Junction Transistor



instantaneous i - v characteristic


- An active switch, controlled by terminal C
- Single-quadrant switch:
- can conduct positive on-state current
- can block positive off-state voltage
- provided that the intended on-state and off-state operating points lie on the transistor i - v characteristic, then switch can be realized using a BJT or IGBT

MOSFET

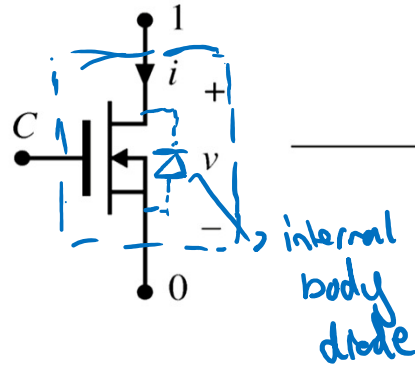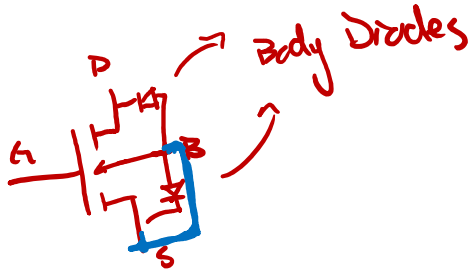


Symbol

instantaneous i - v characteristic

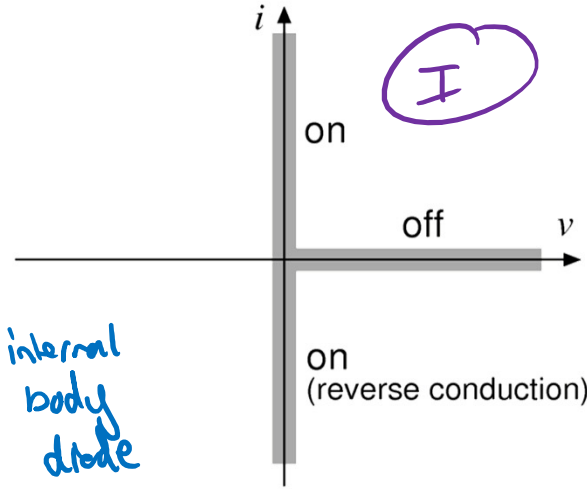

- An active switch, controlled by terminal C
- Normally operated as single-quadrant switch:
- can conduct positive on-state current (can also conduct negative current in some circumstances)
- can block positive off-state voltage
- provided that the intended on-state and off-state operating points lie on the MOSFET i - v characteristic, then switch can be realized using a MOSFET

Buck Converter: Switch Realization

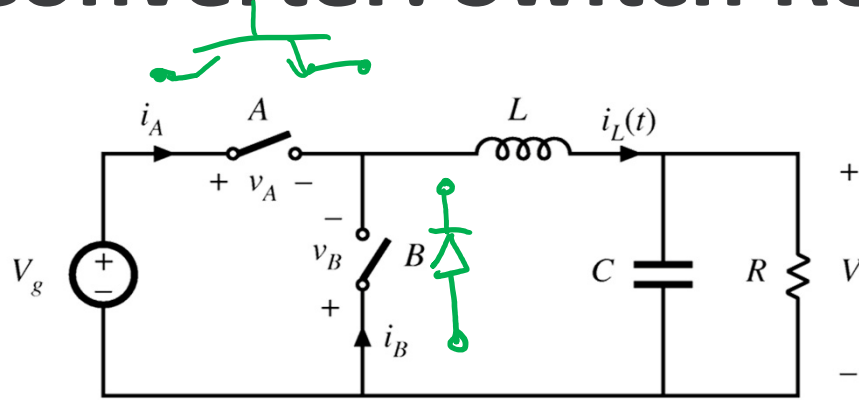

From previous:

$$V = DV_g$$

$$I_L = \frac{V}{R}$$


Can always use $V_g > \phi$, $0 \leq D \leq 1$

(A)

$$V_{off} = V_g > \phi$$

$$\rightarrow V_{off} > \phi$$
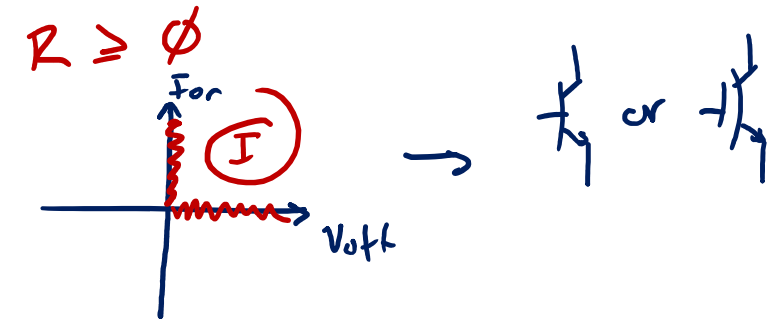
$$I_{on} = I_L = \frac{V}{R} = \frac{DV_g}{R} > \phi \rightarrow I_{on} > \phi$$



(B)


$$V_{off} = -V_g < \phi$$

$$\rightarrow V_{off} < \phi$$

$$I_{on} = I_L = \frac{V}{R} = \frac{DV_g}{R} > \phi \rightarrow I_{on} > \phi$$



Current Bidirectional Two-Quadrant


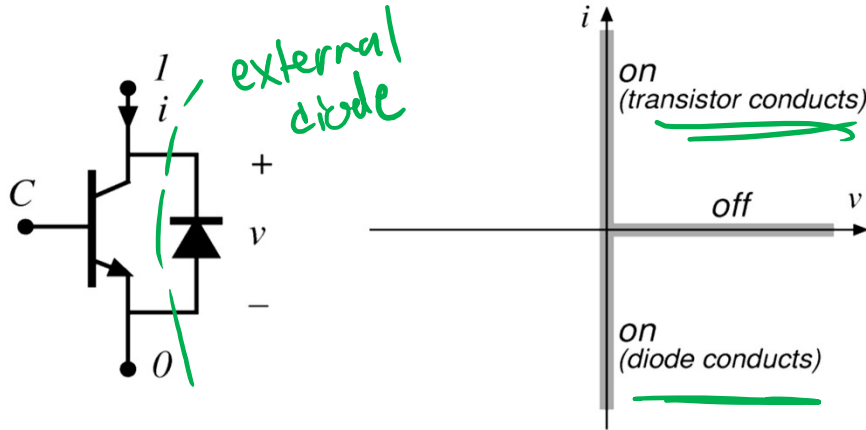


BJT / anti-parallel diode realization


instantaneous $i-v$ characteristic

- *Usually an active switch, controlled by terminal C*
- *Normally operated as two-quadrant switch:*
- *can conduct positive or negative on-state current*
- *can block positive off-state voltage*
- *provided that the intended on-state and off-state operating points lie on the composite $i-v$ characteristic, then switch can be realized as shown*


MOSFET Body Diode

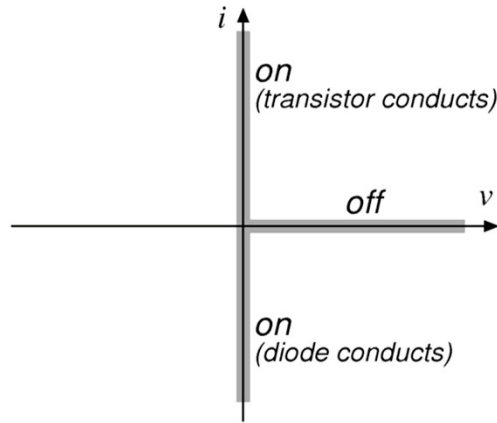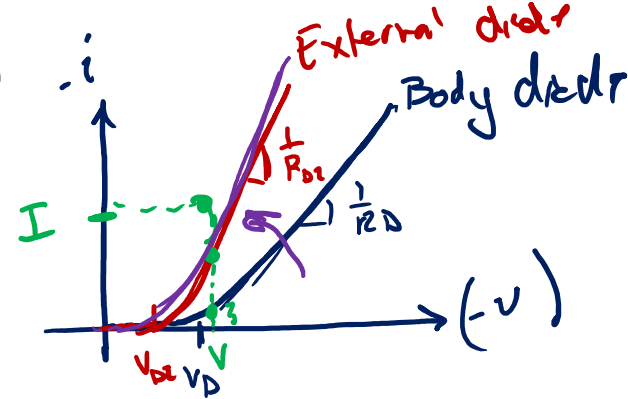

Power MOSFET characteristics

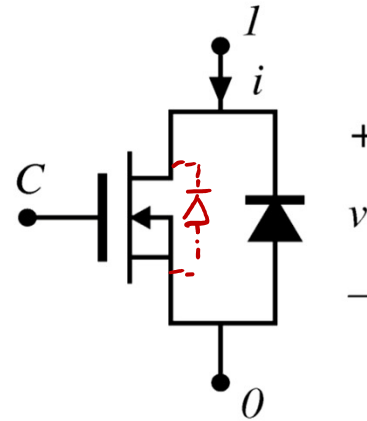


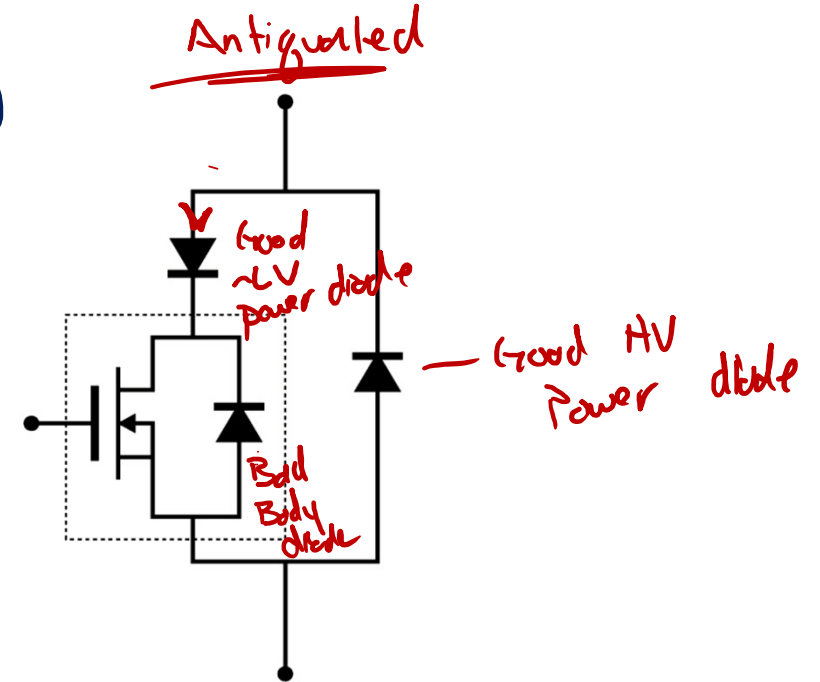Power MOSFET, and its integral body diode




Use of external diodes to prevent conduction of body diode

Voltage-bidirectional Two-Quadrant

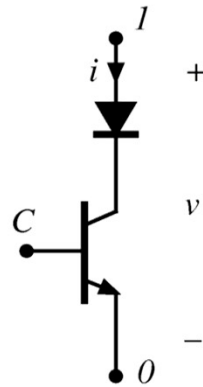


*BJT / series
diode realization*

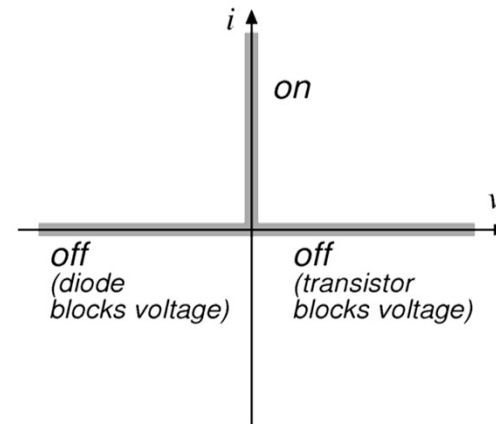

*instantaneous i - v
characteristic*



- *Usually an active switch, controlled by terminal C*
- *Normally operated as two-quadrant switch:*
- *can conduct positive on-state current*
- *can block positive or negative off-state voltage*
- *provided that the intended on-state and off-state operating points lie on the composite i - v characteristic, then switch can be realized as shown*
- *The SCR is such a device, without controlled turn-off*

Four-Quadrant Switches

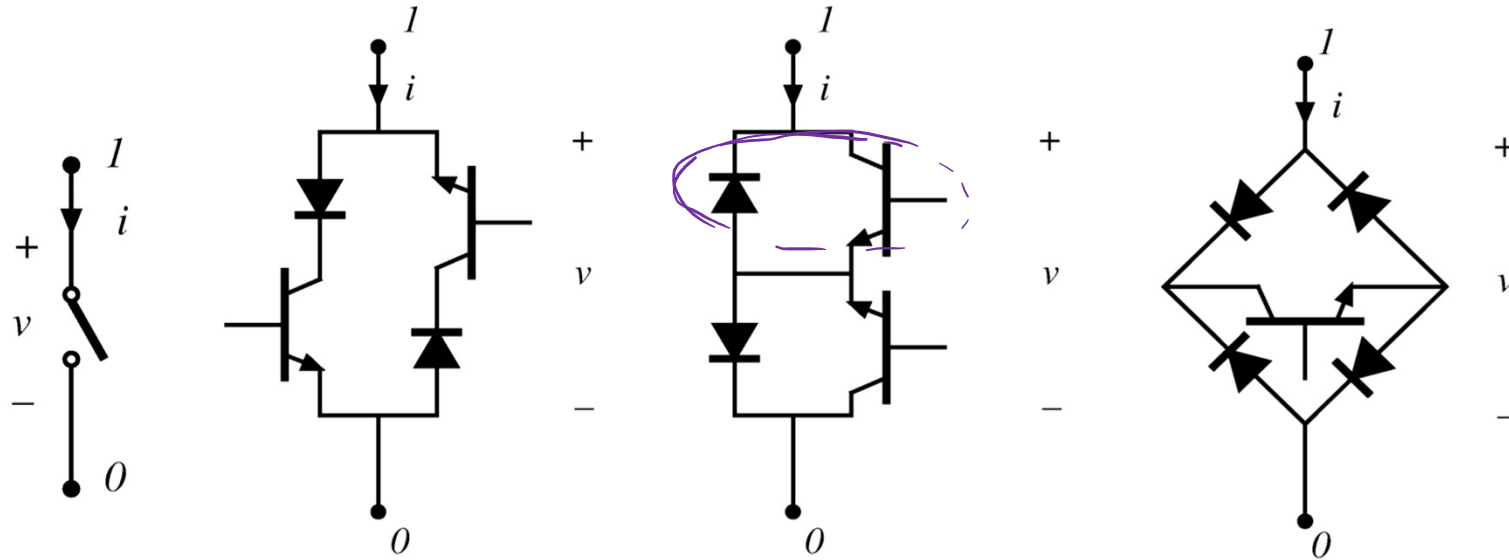


Synchronous Rectifiers

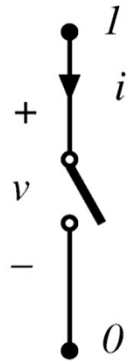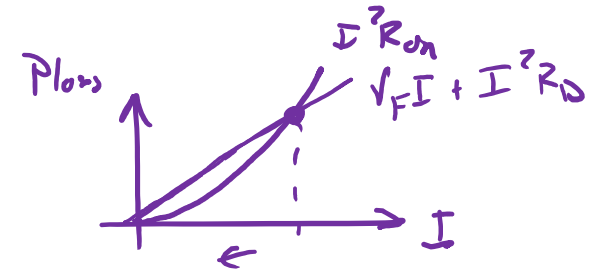
Replacement of diode with a backwards-connected MOSFET, to obtain reduced conduction loss




ideal switch

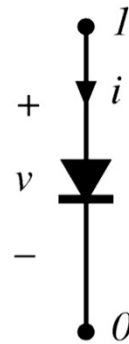

conventional diode rectifier

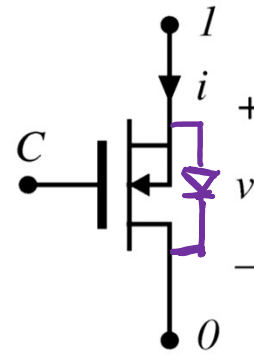

MOSFET as synchronous rectifier

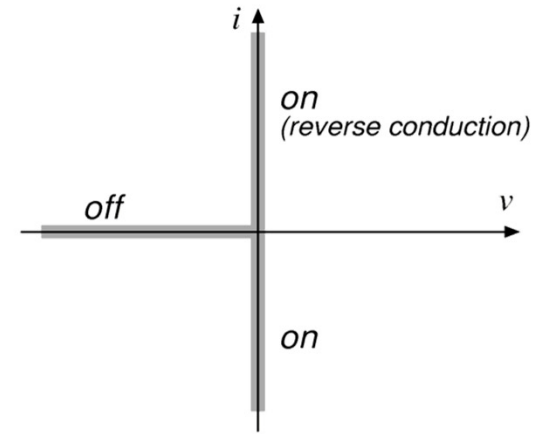

instantaneous i-v characteristic