

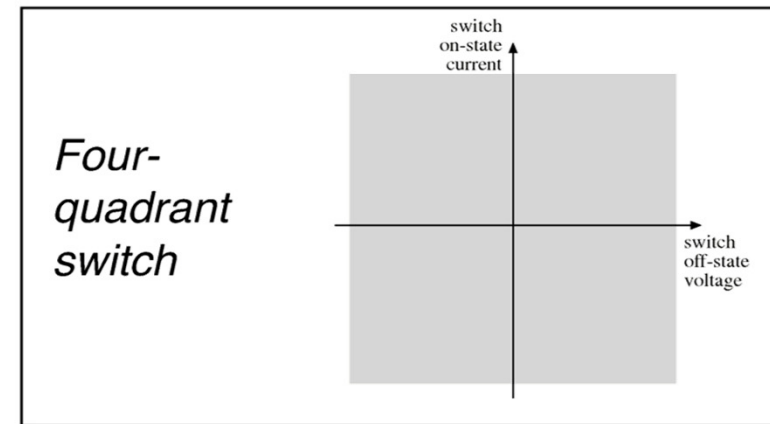
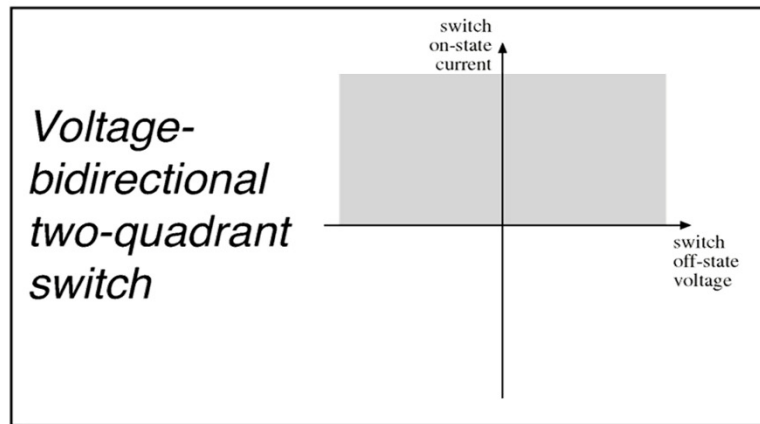
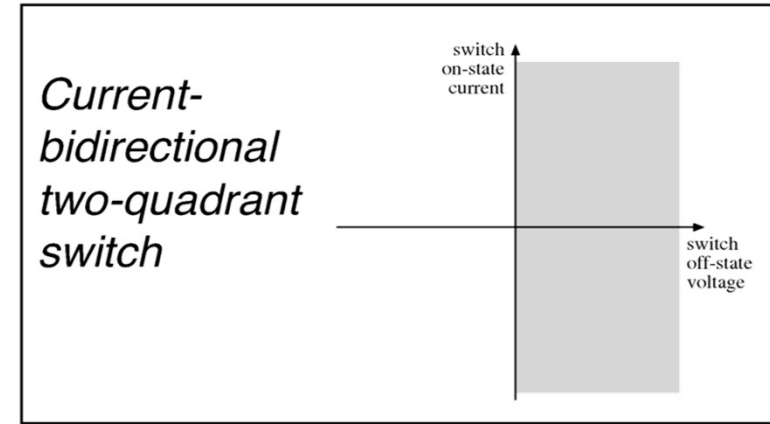
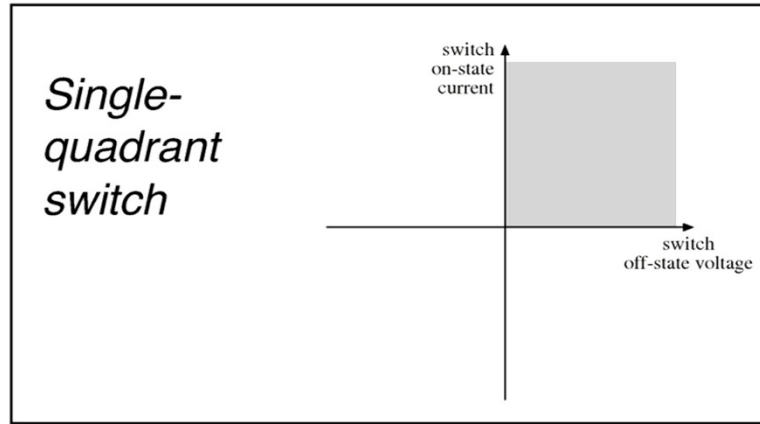


SPST Operating Quadrants



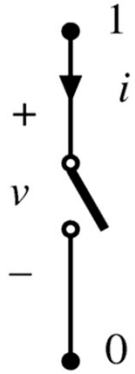


The Diode

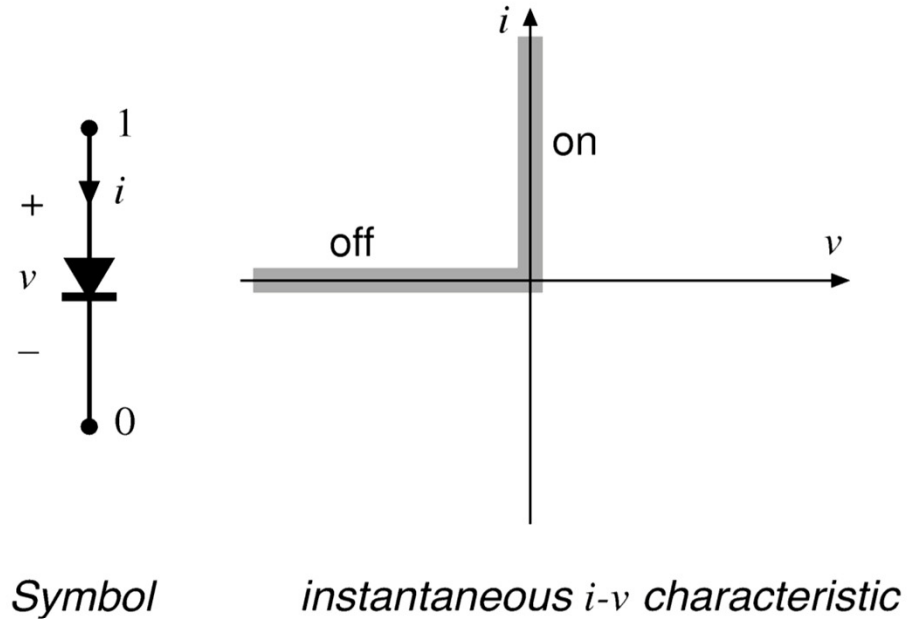

- *A passive switch*
- *Single-quadrant switch:*
- *can conduct positive on-state current*
- *can block negative off-state voltage*
- *provided that the intended on-state and off-state operating points lie on the diode i - v characteristic, then switch can be realized using a diode*

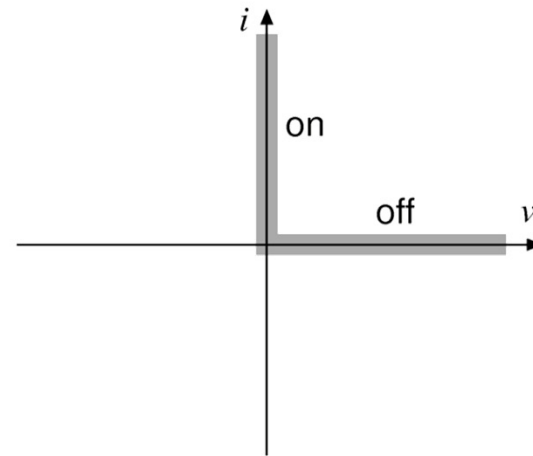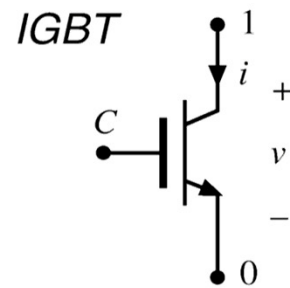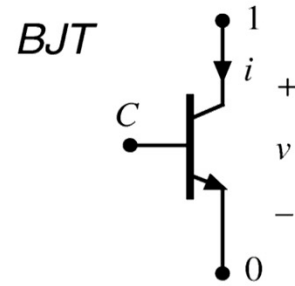
(Insulated Gate) Bipolar Junction Transistor




instantaneous i - v characteristic

- An active switch, controlled by terminal C
- Single-quadrant switch:
 - can conduct positive on-state current
 - can block positive off-state voltage
- provided that the intended on-state and off-state operating points lie on the transistor i - v characteristic, then switch can be realized using a BJT or IGBT

MOSFET

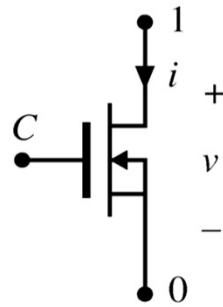


Symbol

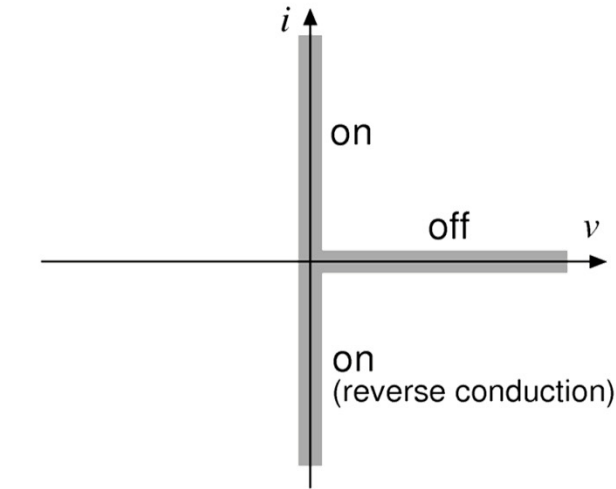


instantaneous i - v characteristic

- *An active switch, controlled by terminal C*
- *Normally operated as single-quadrant switch:*
- *can conduct positive on-state current (can also conduct negative current in some circumstances)*
- *can block positive off-state voltage*
- *provided that the intended on-state and off-state operating points lie on the MOSFET i - v characteristic, then switch can be realized using a MOSFET*


Buck Converter: Switch Realization

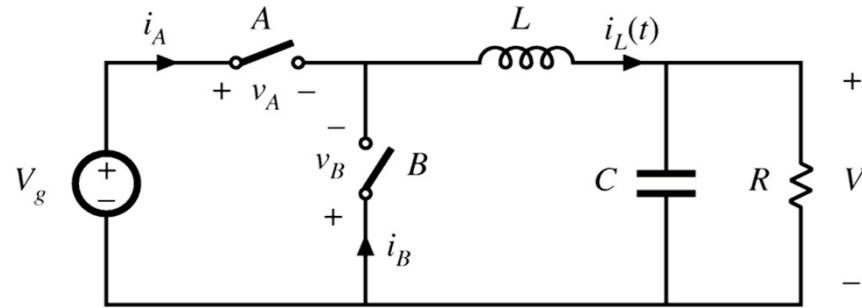

Current Bidirectional Two-Quadrant

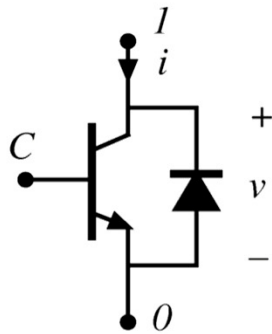


*BJT / anti-parallel
diode realization*

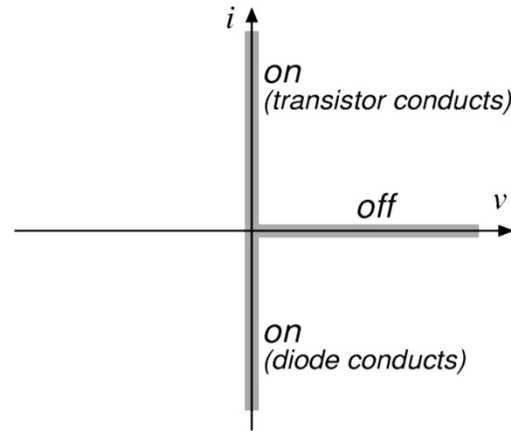


*instantaneous i - v
characteristic*

- *Usually an active switch, controlled by terminal C*
- *Normally operated as two-quadrant switch:*
- *can conduct positive or negative on-state current*
- *can block positive off-state voltage*
- *provided that the intended on-state and off-state operating points lie on the composite i - v characteristic, then switch can be realized as shown*


MOSFET Body Diode

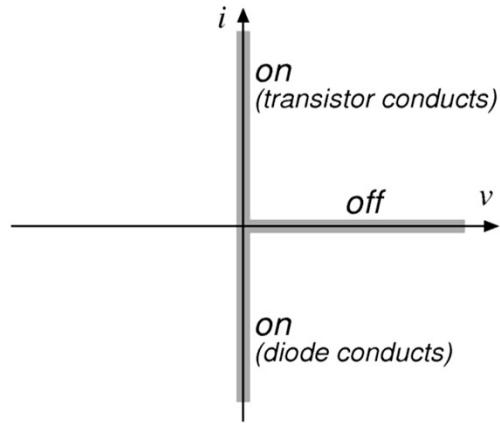

Power MOSFET characteristics

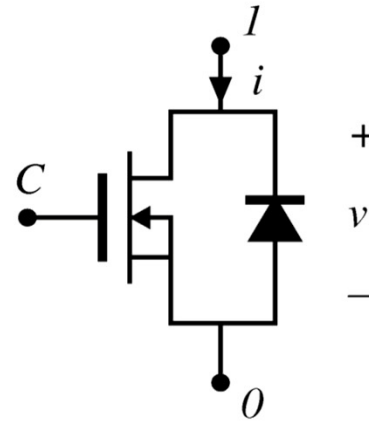


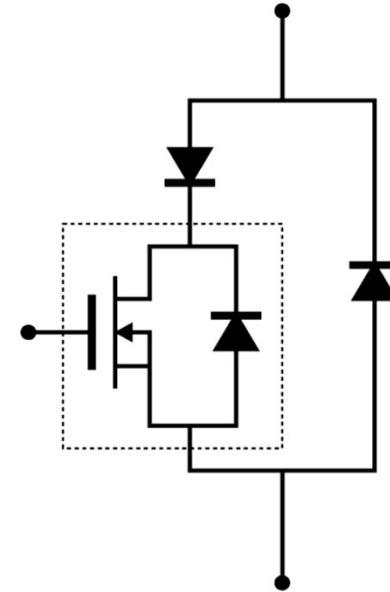Power MOSFET, and its integral body diode




Use of external diodes to prevent conduction of body diode

Voltage-bidirectional Two-Quadrant

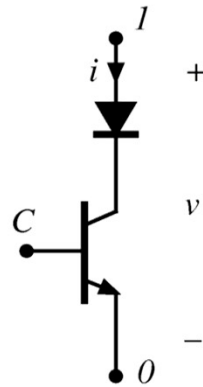


*BJT / series
diode realization*

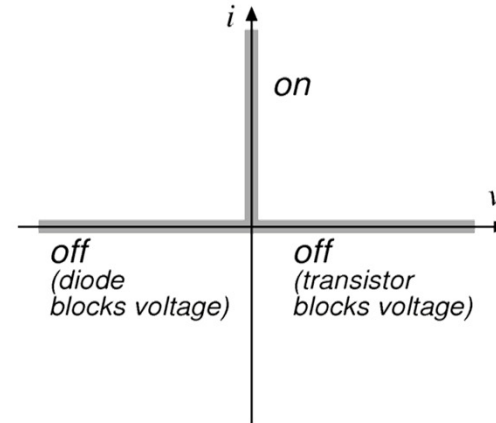

*instantaneous i - v
characteristic*


- *Usually an active switch, controlled by terminal C*
- *Normally operated as two-quadrant switch:*
- *can conduct positive on-state current*
- *can block positive or negative off-state voltage*
- *provided that the intended on-state and off-state operating points lie on the composite i - v characteristic, then switch can be realized as shown*
- *The SCR is such a device, without controlled turn-off*

Four-Quadrant Switches

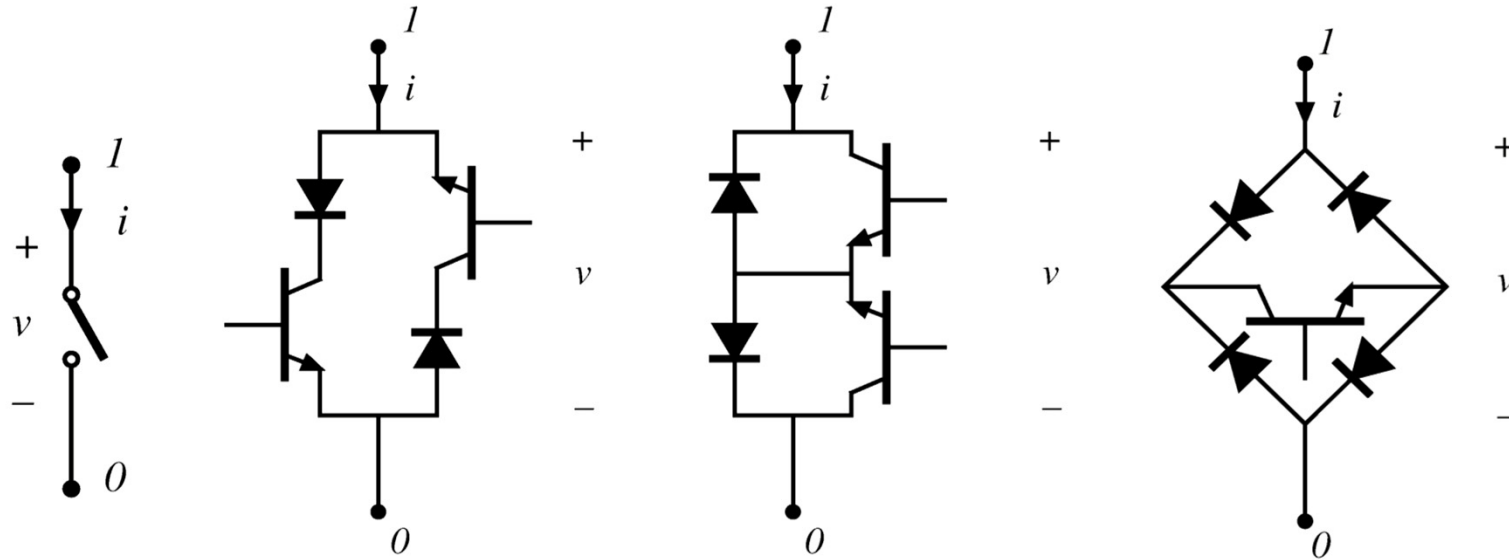


Synchronous Rectifiers

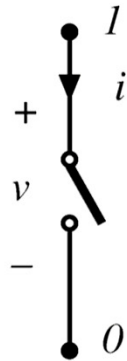
Replacement of diode with a backwards-connected MOSFET,
to obtain reduced conduction loss




ideal switch

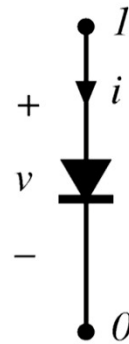

*conventional
diode rectifier*

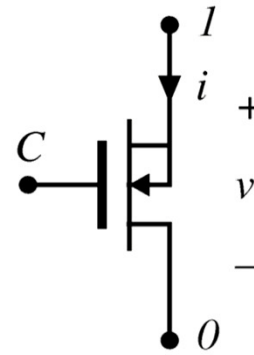

*MOSFET as
synchronous
rectifier*

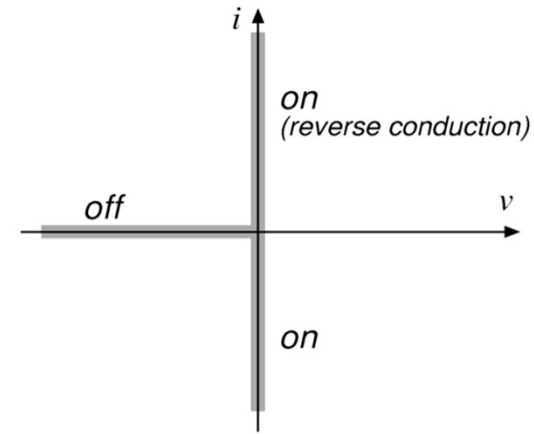

*instantaneous i - v
characteristic*