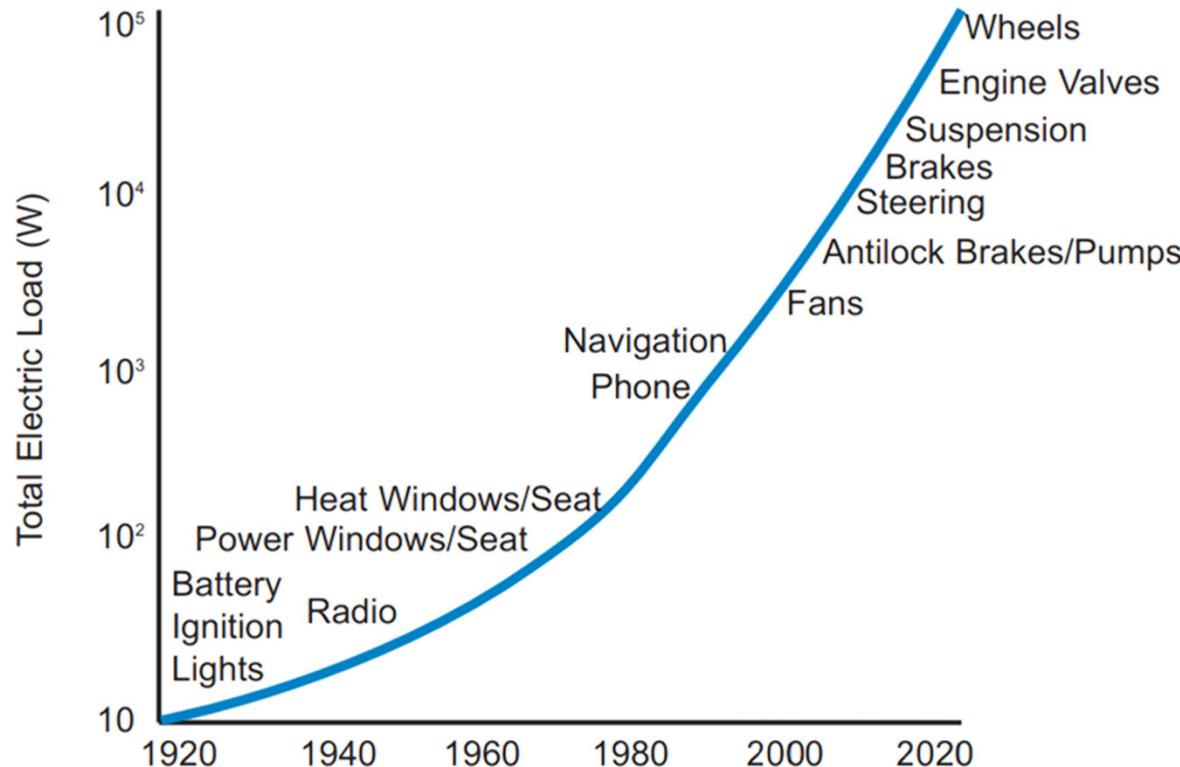


Example Application

48V VEHICLE ELECTRICAL SYSTEM

Automobile 12V Power

Figure 3. Electrification of the Auto




10kW @ 12V ~ 800A

Source: Kasakian, Miller, and Traub, "Automotive Electronics Power Up," IEEE Spectrum (May 2000).

48V Electrical System



12V/48V Electrical Architecture

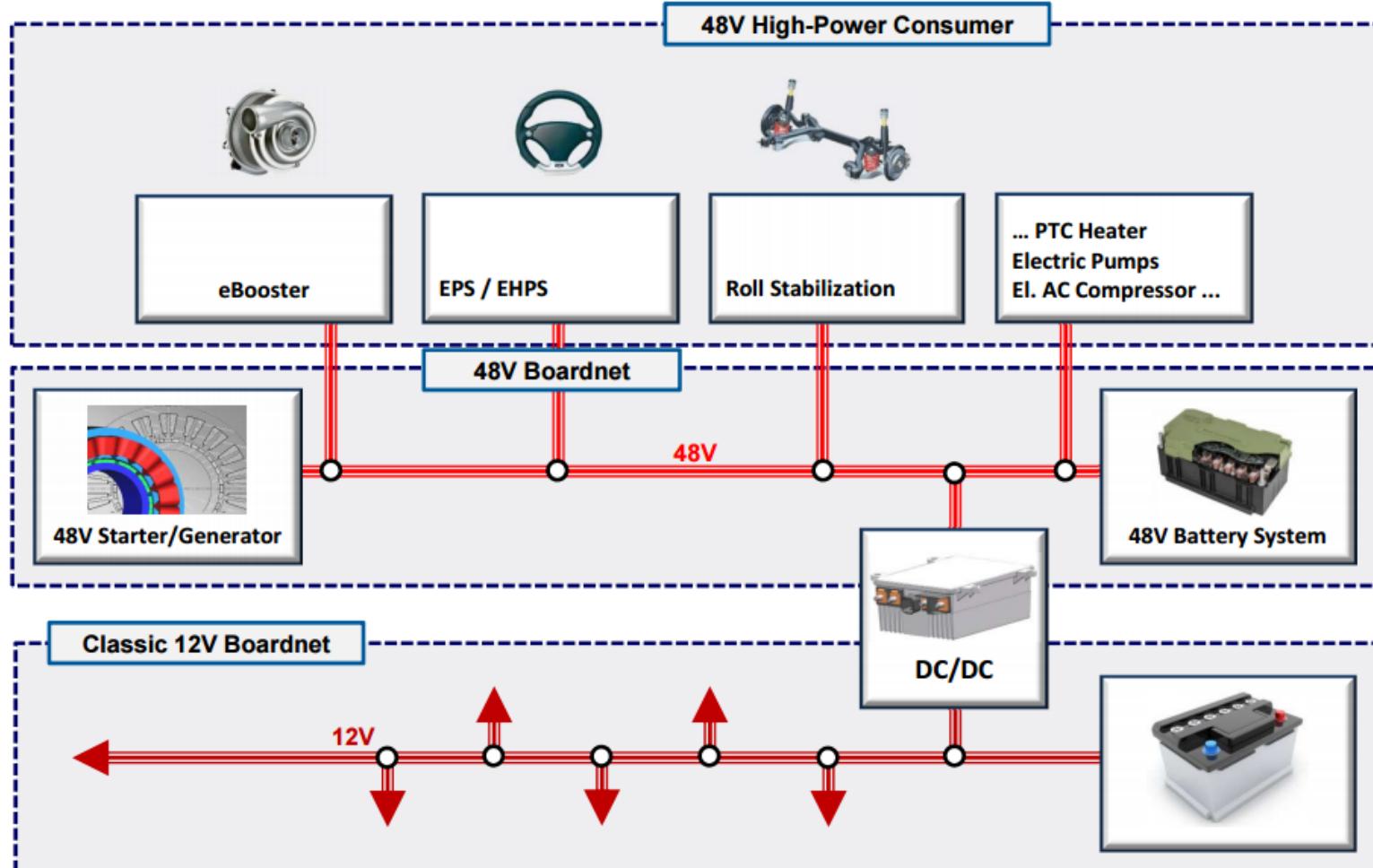

AVL UK Expo 2014 / Ulf Stenzel

12

NXP Semi, "Semiconductors – enablers of future mobility concepts", 2011


Audi, "Electric biturbo and hybridization", 2014

AVL, "48V Mild Hybrid Systems"

Example 12/48 V Vehicle

Audi RS 5 TDI concept

48-Volt-System
48 volt system
07/14

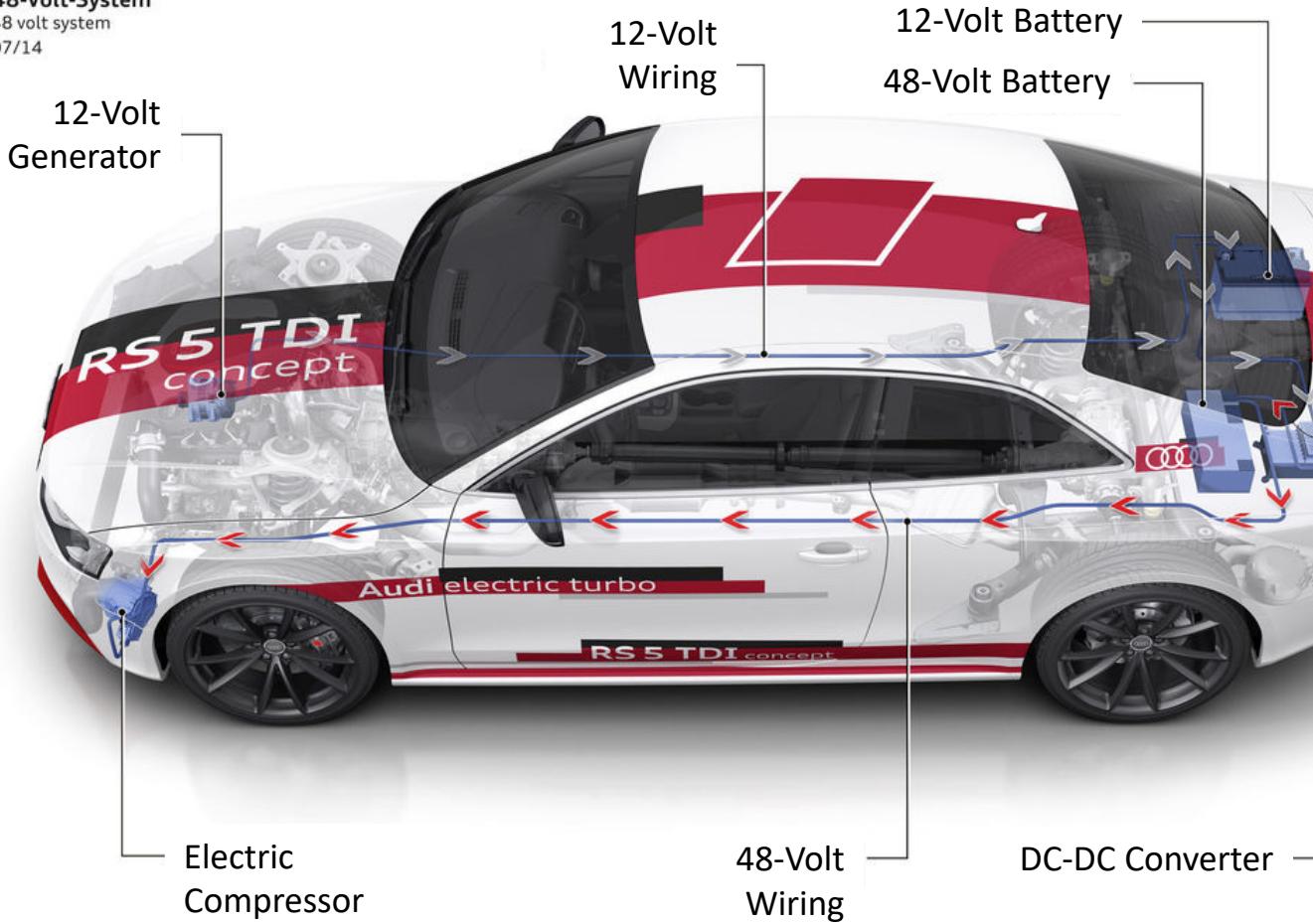

System to Design

Ideal Analysis


$$V = 48V$$

$$M = \frac{V}{V_g} = \frac{1}{D} = \frac{48V}{12V} = 4 \quad \rightarrow \quad D = 0.75$$

$$P_{out} = \frac{V^2}{R} = 48W$$


$$2DV = \frac{V_R}{C}DT_s \quad \rightarrow \quad C = \frac{\frac{V}{R}}{2DV_{out}}DT_s$$
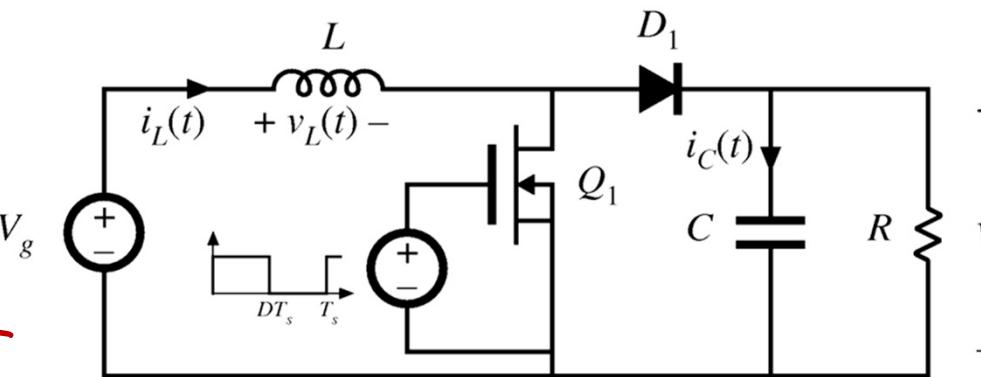
$$\textcircled{C} \quad f_s = 200\text{kHz} \quad C = 18.6\text{nF}$$




Param	Value
V_g	12 V
V_{out}	48 V
R_{out}	48 Ω
ΔV_{out}	0.1 V

Baseline Design

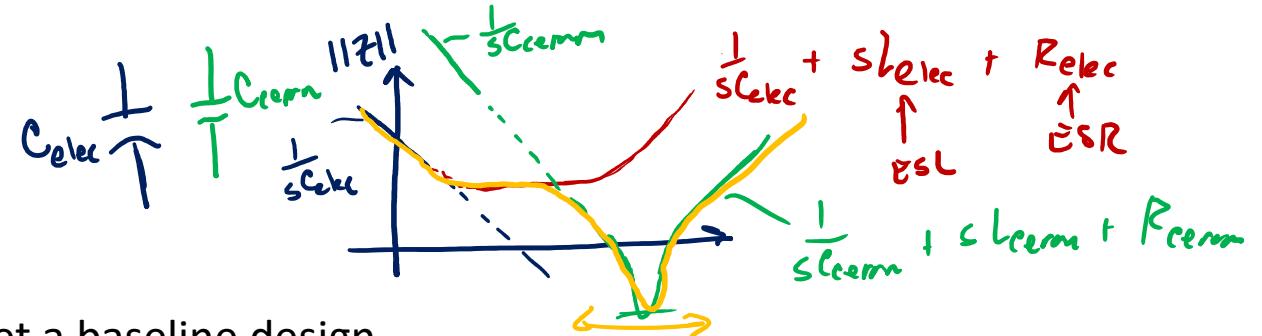


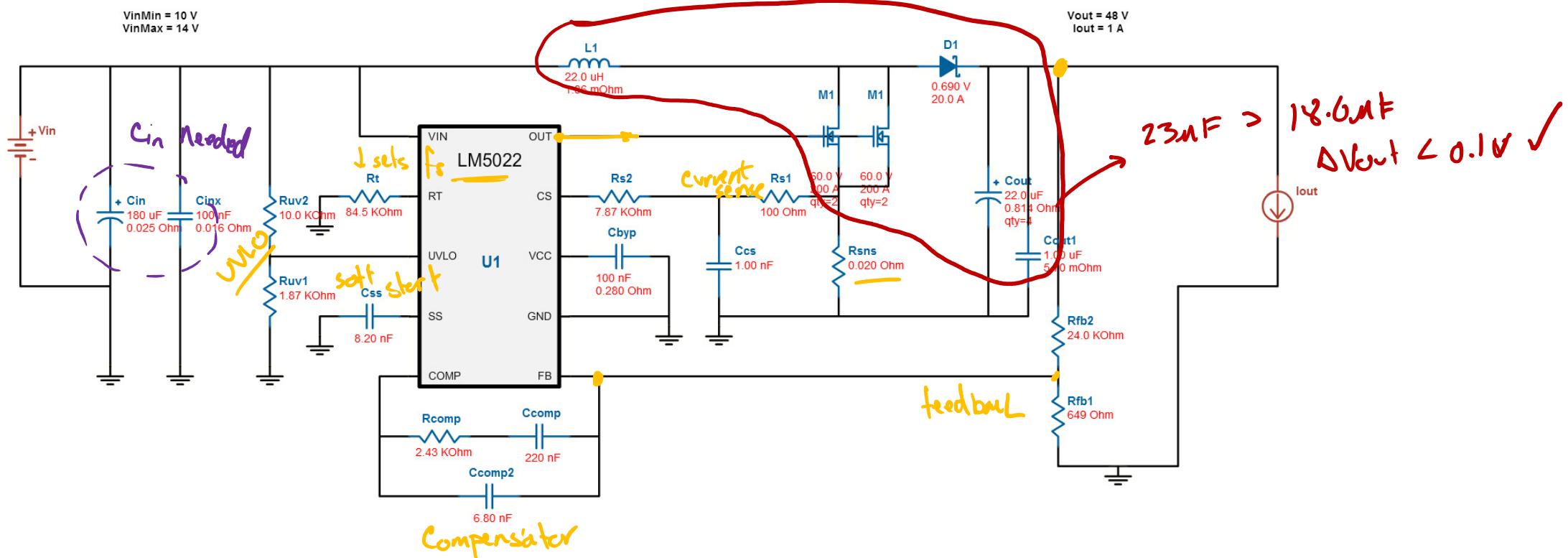- Use TI WebBench (webbench.ti.com) to get a baseline design



Device Parameters

Diode

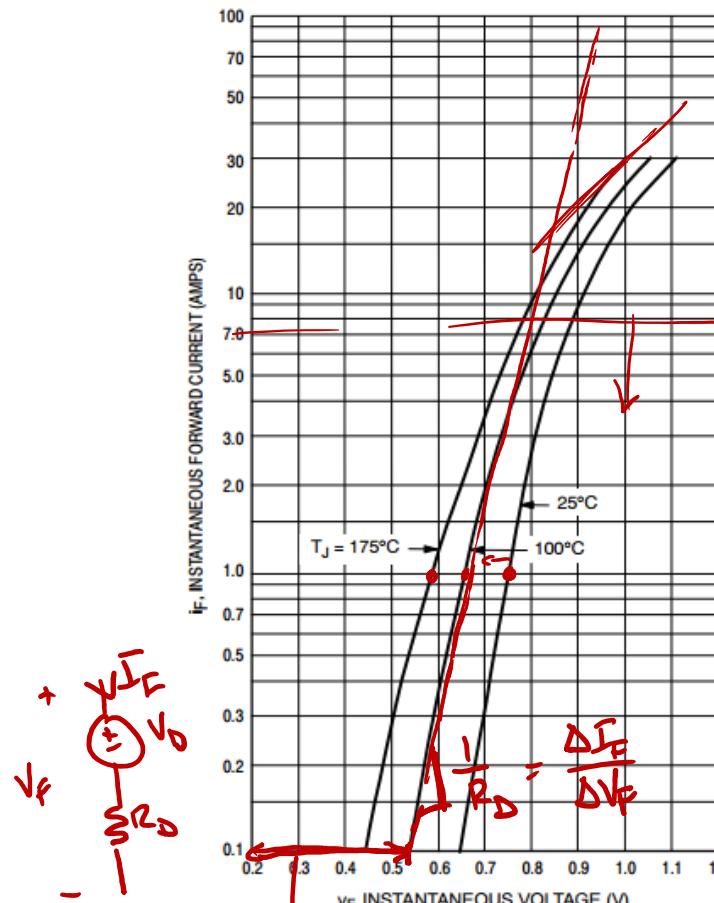


$$V_D \approx 0.5V \text{ @ } 100^\circ C$$

$$V_D \approx 0.65V \text{ @ } 25^\circ C$$

$$R_D \approx 0.1\Omega$$

MOSFET

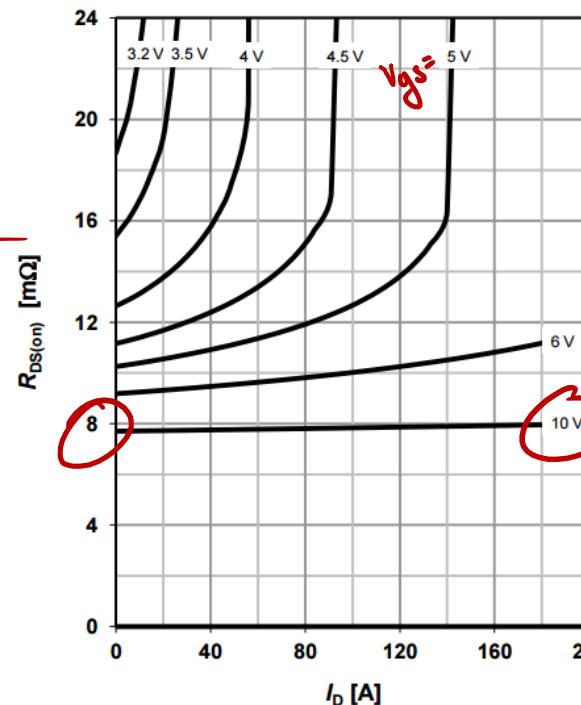


Inductor

DC Resistance

Part number ¹	Inductance ² ±10% (μH)	DCR ³ (mOhms) nom max	SRF typ ⁴ (MHz)
SER2915L-152KL	1.5	1.50 1.65	60
SER2915H-222KL	2.2	1.86 2.05	40
SER2915L-222KL	2.2	1.50 1.65	50
SER2918H-332KL	3.3	2.60 2.86	40
SER2915H-332KL	3.3	1.86 2.05	30
SER2915L-332KL	3.3	1.50 1.65	40
SER2918H-472KL	4.7	2.60 2.86	30
SER2915H-472KL	4.7	1.86 2.05	25
SER2915L-472KL	4.7	1.50 1.65	30
SER2918H-682KL	6.8	2.60 2.86	25
SER2915H-682KL	6.8	1.86 2.05	20
SER2915L-682KL	6.8	1.50 1.65	25
SER2918H-103KL	10	2.60 2.86	20
SER2915H-103KL	10	1.86 2.05	15
SER2915L-103KL	10	1.50 1.65	20
SER2918H-153KL	15	2.60 2.86	16
SER2915H-153KL	15	1.86 2.05	12
SER2915L-153KL	15	1.50 1.65	15
SER2918H-223KL	22	2.60 2.86	15
SER2915H-223KL	22	1.86 2.05	10
SER2915L-223KL	22	1.50 1.65	10
SER2918H-333KL	33	2.60 2.86	10
SER2915H-333KL	33	1.86 2.05	8
SER2915L-333KL	33	1.50 1.65	7


$$R_L = 1.86 \text{ mOhm}$$

Expected Behavior

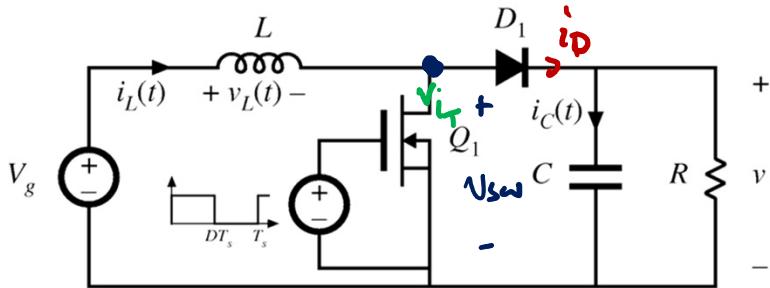


$$I_L = \frac{V}{RD} = 4A$$
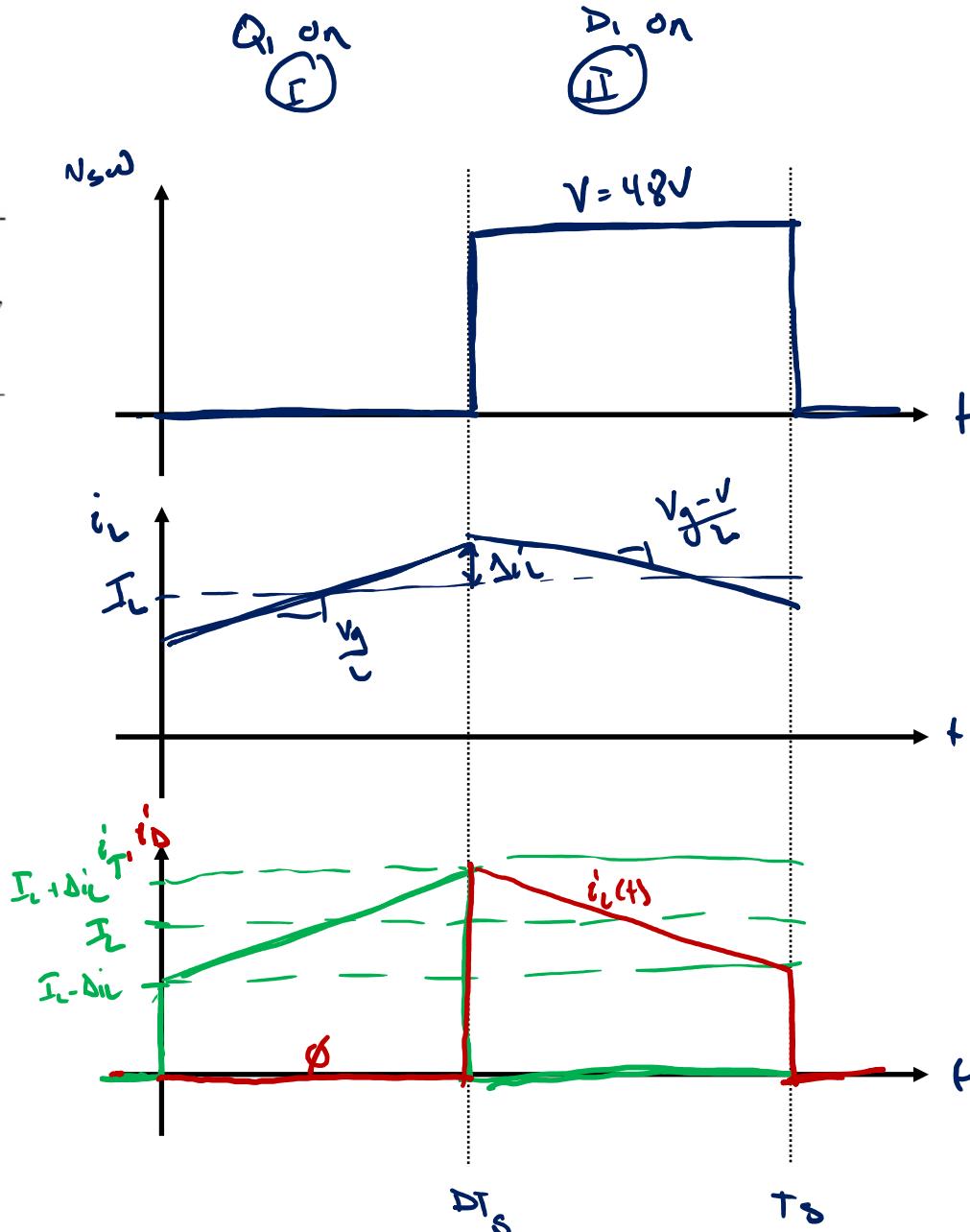
$$2\Delta i_L = \frac{V_g}{L}DT_s \rightarrow \Delta i_L = 1A$$



Equivalent Circuit Model

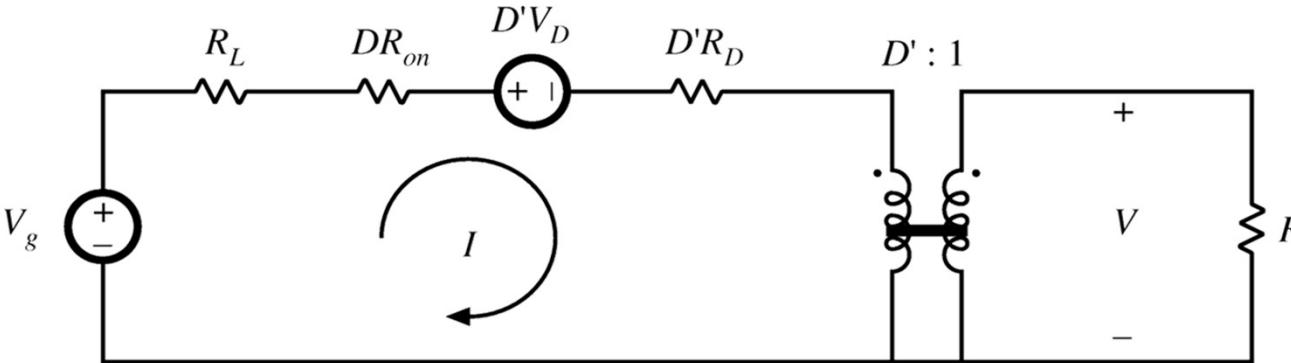

$$V = \left(\frac{1}{D'} \right) \left(V_g - D'V_D \right) \left(\frac{D'^2 R}{D'^2 R + R_L + DR_{on} + D'R_D} \right)$$

$D_{ideal} = 0.75$

$$\frac{V}{V_g} = \left(\frac{1}{D'} \right) \left(1 - \frac{D'V_D}{V_g} \right) \left(\frac{1}{1 + \frac{R_L + DR_{on} + D'R_D}{D'^2 R}} \right)$$

$D = 0.756$
Model-predicted
 $\eta = 97.6\%$

Model η

