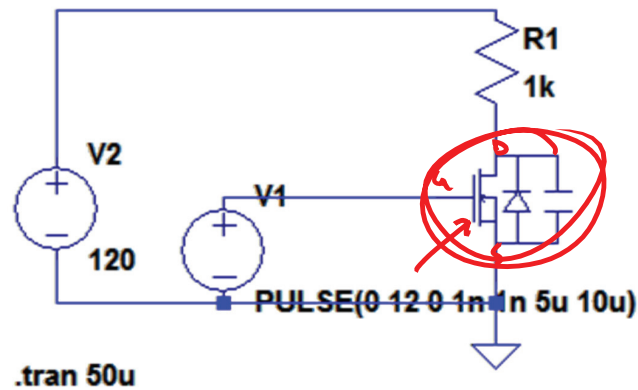


Simulation Modeling

Circuit Simulation

- LTSpice
 - Other tools accepted, but not supported
- Choose model type (switching, averaged, dynamic)
- Supplement analytical work rather than repeating it
- Show results which clearly demonstrate what matches and what does not with respect to experiments (i.e. ringing, slopes, etc.)

LTSpice Modeling Examples




- Example files added to course materials page
 - Custom model
 - VDMOS model
 - Manufacturer Model

Custom Transistor Model

```
.model myD D(n=.001)
```

 
```
.model mySw SW(Ron=10m Roff=1G Von=1 Voff = .5 )
```



VDMOS Model

Name	Description	Units	Default	Example
Vto	Threshold voltage	V	0	1.0
Kp	Transconductance parameter	A/V ²	1.	.5
Phi	Surface inversion potential	V	0.6	0.65
Lambda	Channel-length modulation	1/V	0.	0.02
mtriode	Conductance multiplier in triode region (allows independent fit of triode and saturation regions)	-	1.	2.
subthres	Current (per volt Vds) to switch from square law to exponential subthreshold conduction	A/V	0.	1n
BV	Vds breakdown voltage	V	Infin.	40
IBV	Current at Vds=BV	A	100pA	1u
NBV	Vds breakdown emission coefficient	-	1.	10
Rd	Drain ohmic resistance	Ω	0.	1.
Rs	Source ohmic resistance	Ω	0.	1.
Rg	Gate ohmic resistance	Ω	0.	2.
Rds	Drain-source shunt resistance	Ω	Infin.	10Meg
Rb	Body diode ohmic resistance	Ω	0.	.5
Cio	Zero-bias bodv diode	F	0.	1n
 
```
.model myMOS VDMOS(nchan Rg=3 Rd=14m Rs=10m Vto=-.8 Kp=32
+ Cgdmax=.5n Cgdmin=.07n Cgs=.9n Cjo=.26n Is=26p Rb=17m)
```



- Note: any other parameters **ignored**
 - E.g. ron = 3m Qg = 1n mfg = Infineon

http://ltwiki.org/LTspiceHelp/LTspiceHelp/M_MOSFET.htm


Manufacturer Device Model

- Text-only netlist model of device including additional parasitics and temperature effects
- May slow or stop simulation if timestep and accuracy are not adjusted appropriately

Full Switching Simulation

```
.tran 1 .model myMOS VDMOS(Rg=1 Vto=4.5 Rd=14m Rs=10m Rb=17m Kp=30 Cgdmax=.5p Cgdmin=.05n Cgs=.2n Cjo=.03n Is=88p)
```


```
.ic V(out)=0  
.ic I(L1)=0
```

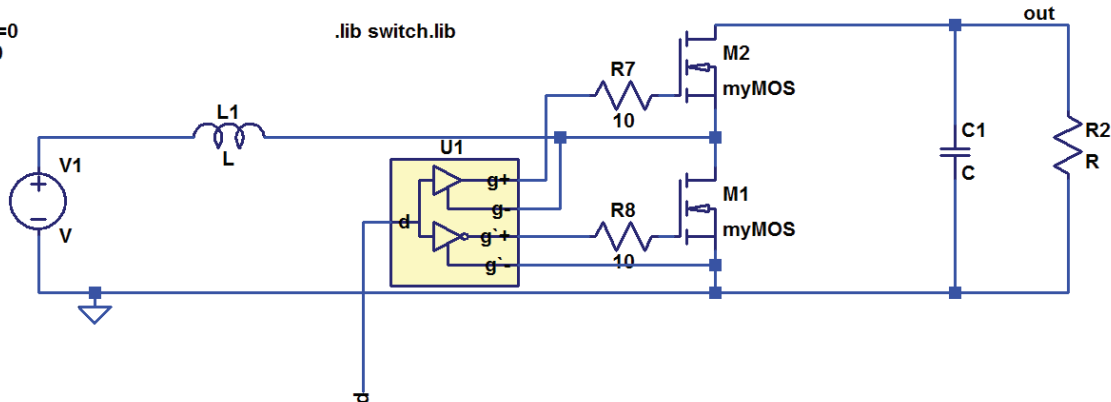

Full Switching Simulation

```
.tran 1 .model myMOS VDMOS(Rg=1 Vto=4.5 Rd=14m Rs=10m Rb=17m Kp=30 Cgdmax=.5p Cgdmin=.05n Cgs=.2n Cjo=.03n Is=88p)
```

```
.ic V(out)=0  
.ic I(L1)=0
```

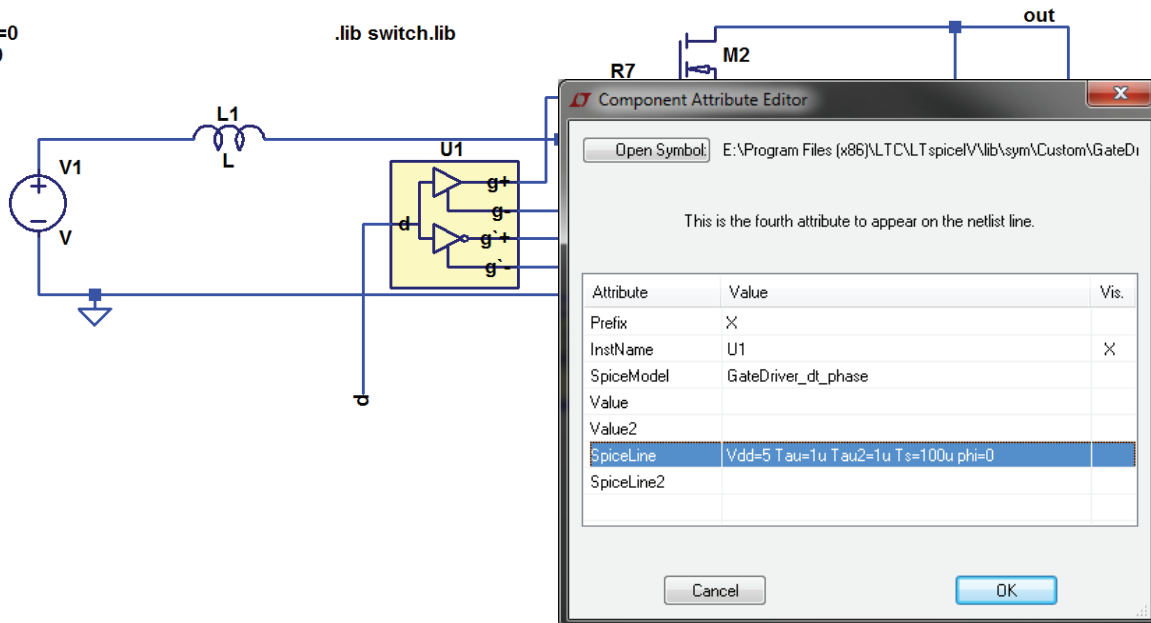

Experiment 2

Experiment 3

Experiment Procedure

Prelab Assignment
 Experiment 3 Procedure

Experiment 3 Components

Contents of the Experiment 3 Parts Kit
 Contents of the Magnetics Library
 Breakout Board Schematics and Layout (pdf)
 Breakout Board Schematics and PCB Layout (Altium)

Reference Materials

Designing Bootstrap Networks
 Power Converter Layout
 Reduction of Ringing in Power Converters (TI App. Note)
 RMS Values of Commonly Observed Waveforms

LTSpice Example Files


Examples of power semiconductor modeling using custom or manufacturer models
 Example Switching and Averaged Boost LTSpice Models

Magnetics Design

Filter Inductor Design Notes
 Kg Method Step-by-Step
 Kgfe Method Step-by-Step
 Overview of Empirical Core Loss Calculation Techniques
 Overview of Empirical State of Core Loss Prediction
 Magnetics Design Tables
 AWG Chart

Experiment 4

Available on Exp 3 Webpage

 


Full Switching Model

- Gives valuable insight into circuit operation
 - Understand expected waveforms
 - Identify discrepancies between predicted and experimental operation
- Slow to simulate; significant high frequency content
- Cannot perform AC analysis

Averaged Switch Modeling: Motivation

- A *large-signal, nonlinear* model of converter is difficult for hand analysis, but well suited to simulation across a wide range of operating points
- Want an *averaged* model to speed up simulation speed
- Also allows linearization (AC analysis) for control design

Nonlinear, Averaged Circuit

 

$$L \frac{d\langle i_L \rangle}{dt} = \langle v_{bat} \rangle - \underbrace{d(t) \cdot v_{bus}(t)}_{(1-d)\langle v_{bus} \rangle}$$



$$C \frac{d\langle v_{bus} \rangle}{dt} = (1-d)\langle i_L \rangle - \langle i_{bus} \rangle$$

DC analysis
 $\frac{dx}{dt} = \phi$
AC analysis
small-signal analysis
 $x(t) = X + \hat{x}$

↓
DC steady-state averaged behavior
↓
Averaged, linear small-signal equations


for simulation: no need to linearize.

Implementation in LTSpice

 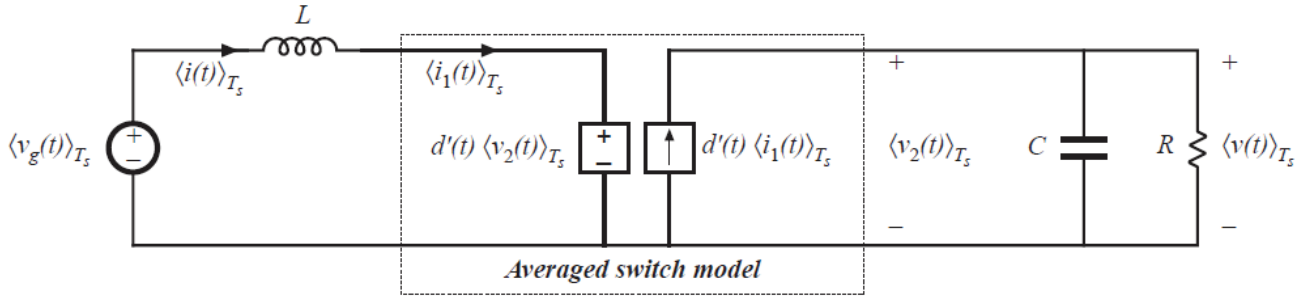


$$\langle v_1(t) \rangle_{T_s} = d'(t) \langle v_2(t) \rangle_{T_s}$$

 
$$\langle i_2(t) \rangle_{T_s} = d'(t) \langle i_1(t) \rangle_{T_s}$$



Averaged Switch Model

 

Averaged Model With Losses

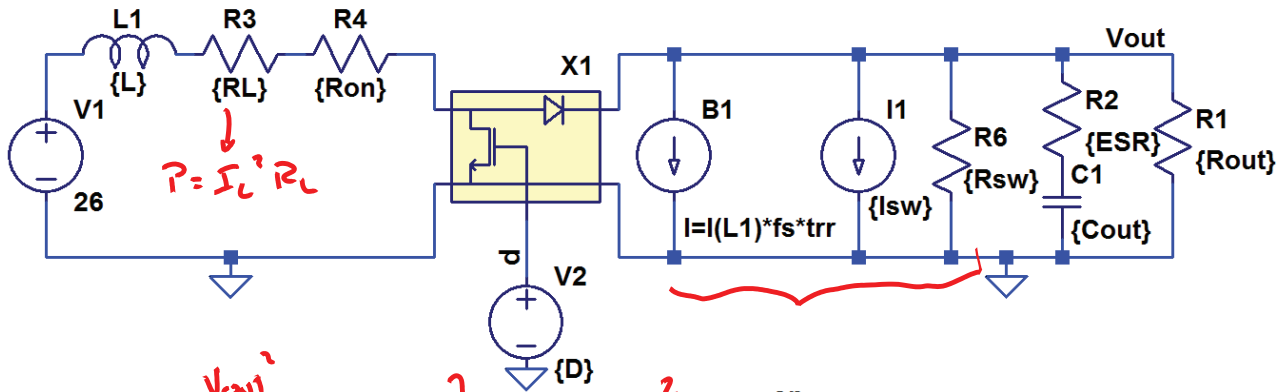


```
.op
.param Rout = 10
.step param Rout 10 100 10
```

What known error(s) will be present in loss predictions with this model?



Experiment 4

Experiment 4: Closed-Loop Boost


Experiment 3: Open Loop

 

Experiment 4: Closed Loop

 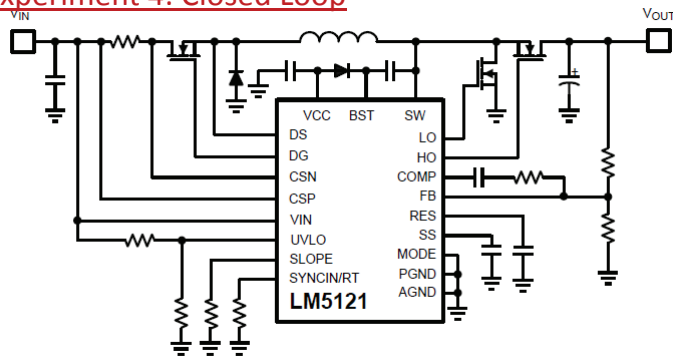

Current Control

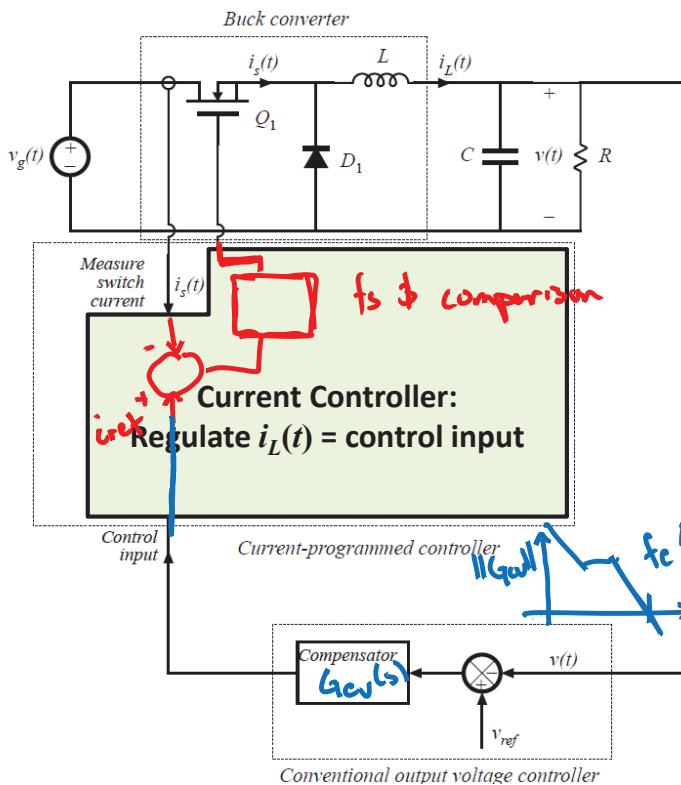


Two control loops:


- (1) Fast (inner) current loop control
- Not Averaged
- (2) Slow (outer) voltage loop control
- Averaged

Effective low-pass filter averaged models can be used when $f_c \ll f_s$

Averaged vs CPM

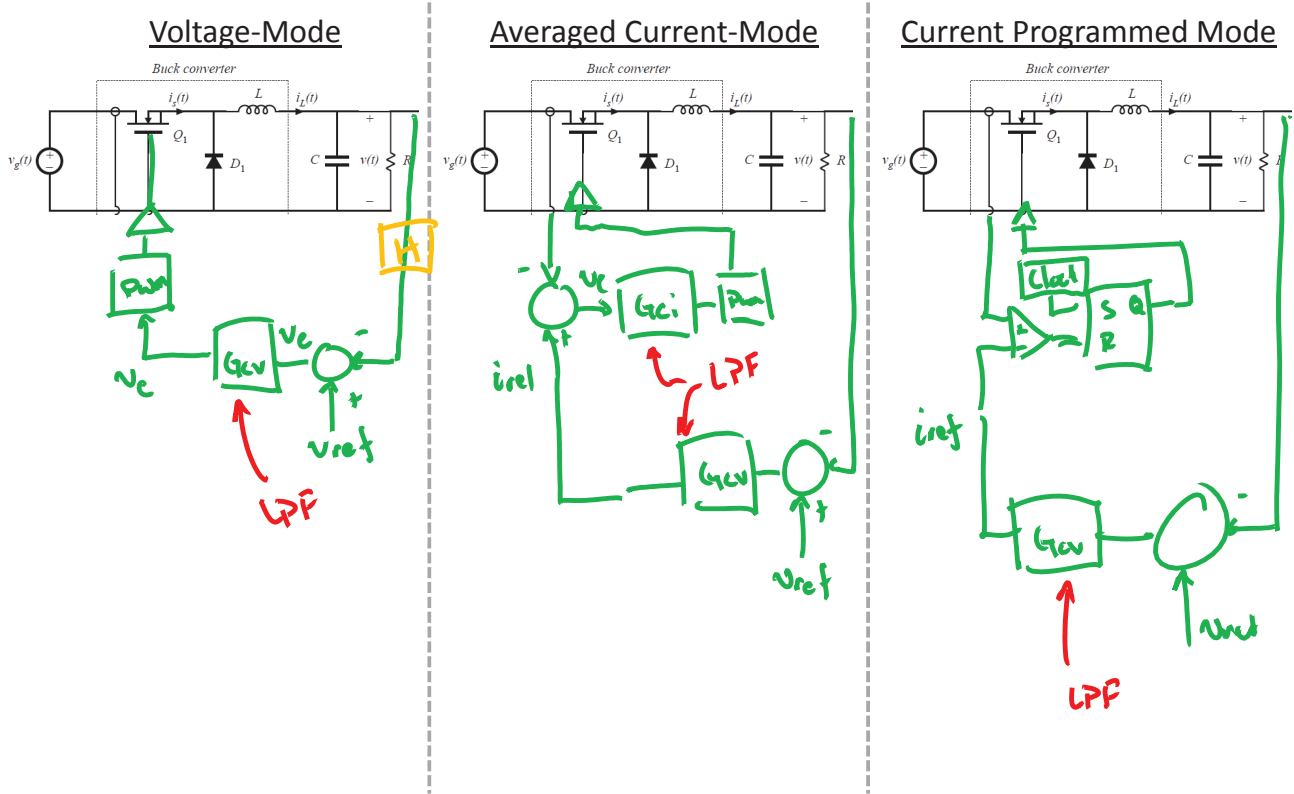


Current Programmed Control (CPM)

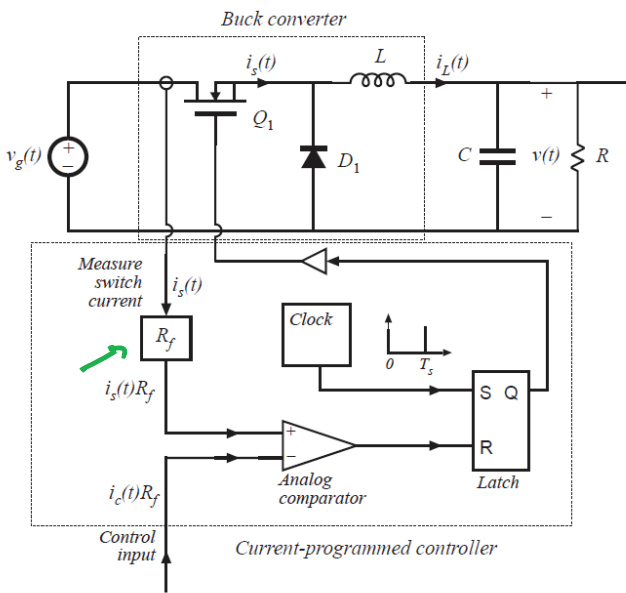


$R_f \rightarrow$ current-to-voltage gain of the sensing circuit

 
$i_{i,pt} = i_c(DT_s) = i_{ref}$ every period



CPM Voltage Loop

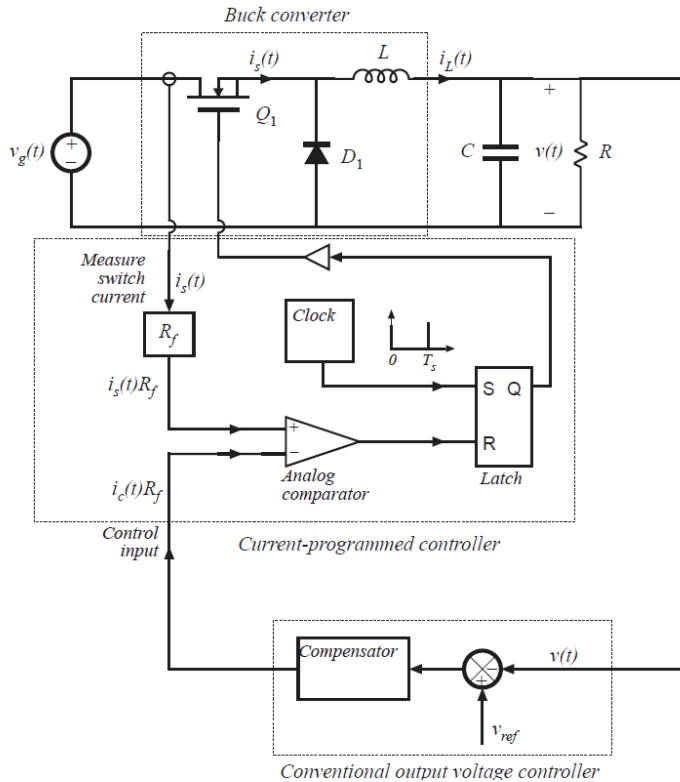

 
The peak transistor current replaces the duty cycle as the converter control input.



Current Programmed Control

- Covered in Ch. 12 of *Fundamentals of Power Electronics*
- Advantages of current programmed control:
 - Simpler dynamics — inductor pole is moved to high frequency
 - Simple robust output voltage control, with large phase margin, can be obtained without use of compensator lead networks
 - Transistor failures due to excessive current can be prevented simply by limiting $i_c(t)$
 - It is always necessary to sense the transistor current, to protect against overcurrent failures
 - Transformer saturation problems in bridge or push-pull converters can be mitigated
- A disadvantage: susceptibility to noise

A Simple First-Order Model

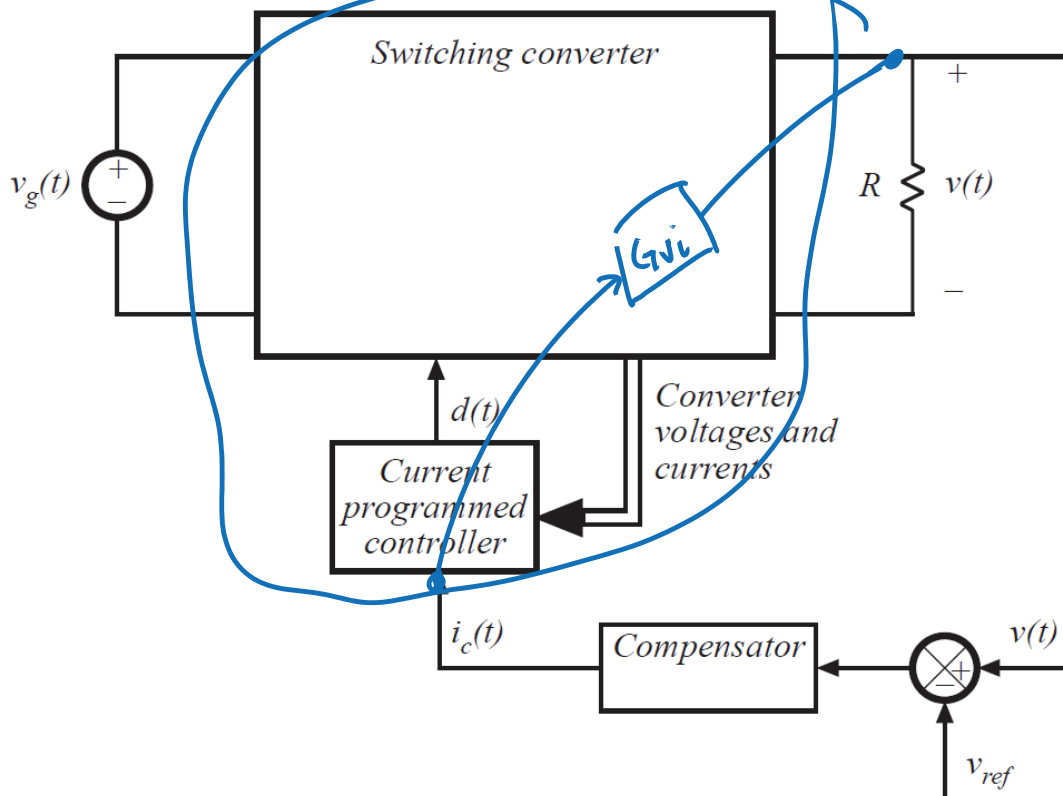



The First-Order Approximation

$$\langle i_L(t) \rangle_{T_s} = i_c(t)$$


- Neglects switching ripple
- Yields physical insight and simple first-order model
- Accurate when converter operates well into CCM (so that switching ripple is small)
- Accurate when artificial ramp (discussed later) is small
- Resulting small-signal relation:

$$i_L(s) \approx i_c(s)$$


Averaged Modeling

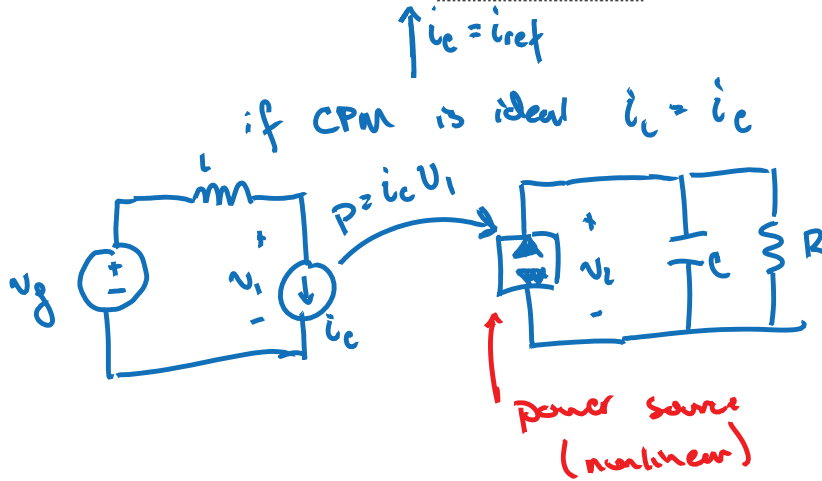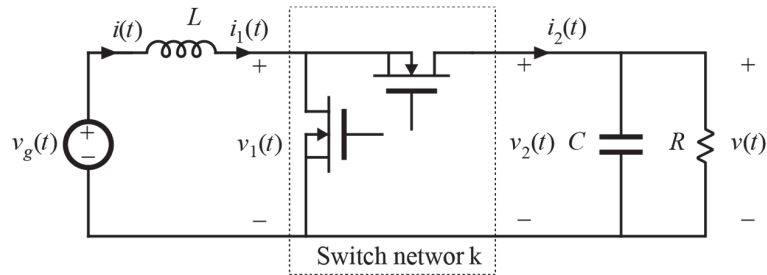


Large-Signal Nonlinear Model

 

Implementation in LTSpice

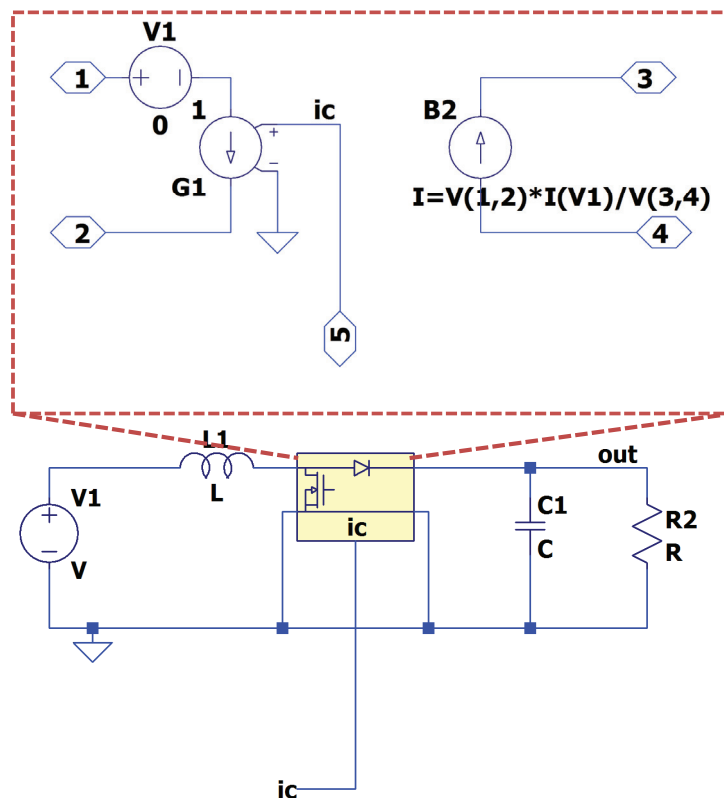

Averaged, Small-Signal Model

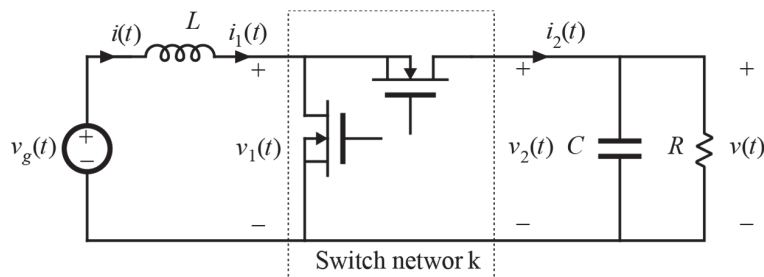

$$L \frac{d\langle i_c \rangle}{dt} = \langle v_g \rangle - d'(t) \langle v \rangle$$

$$C \frac{d\langle v \rangle}{dt} = d'(t) \langle i_c \rangle - \frac{\langle v \rangle}{R}$$

- Replace $i_c = i_e$ (assuming ideal CPM)

- Linearize in Laplace domain

$$sL \hat{i}_c = \hat{v}_g + v \hat{d} - D' \hat{v}$$

$$sC \hat{v} = D' \hat{i}_c - I_c \hat{d} - \frac{\hat{v}}{R}$$

- \hat{d} is no longer controlled \rightarrow eliminate


$$\hat{d} = \frac{1}{v} (sL \hat{i}_c - \hat{v}_g + D' \hat{v})$$

$$sC\hat{v} = D' \hat{i}_c - \frac{\hat{v}}{R} - \frac{I_L}{V} (sL \hat{i}_c - \hat{v}_y - D' \hat{v})$$


$$sC\hat{v} = \hat{i}_c \left(D' - \frac{I_L}{V} sL \right) + \hat{v}_y \frac{I_L}{V} - \frac{\hat{v}}{R} - \frac{I_L}{V} D' \hat{v}$$

$$I_{out} = D' I_L \rightarrow \frac{I_L}{V} = \frac{I_{out}}{D' V} = \frac{1}{R D'}$$
 
$$sC\hat{v} = \hat{i}_c \left(D' - \frac{sL}{R D'} \right) + \hat{v}_y \frac{1}{R D'} - \frac{\hat{v}}{R} - \frac{I_L}{V} D' \hat{v}$$



Boost CCM CPM Small-Signal Model

 

for PWM control

$$G_{vd} = \frac{V}{D'} \frac{\left(1 - \frac{sL}{D'R}\right)}{1 + \frac{sL}{R D'} + s^2 L C \frac{D'}{D'R^2}}$$

DC output $\hat{v}_y = \hat{v}$

$$= D' \left(1 - \frac{sL}{D'R}\right) \cdot \left(R \parallel R \parallel \frac{1}{sC}\right)$$

$$G_{vi} = \frac{D'R}{2} \frac{\left(1 - \frac{sL}{D'R}\right)}{1 + s \frac{RC}{2}}$$

$$\frac{1}{\frac{2}{R} + sC}$$

Same RHP zero as in G_{vd}

single pole!!

CPM Transfer Functions


 


Fig. 12.28 Comparison of CPM control with duty-cycle control, for the control-to-output frequency response of the buck converter example.


Voltage Control

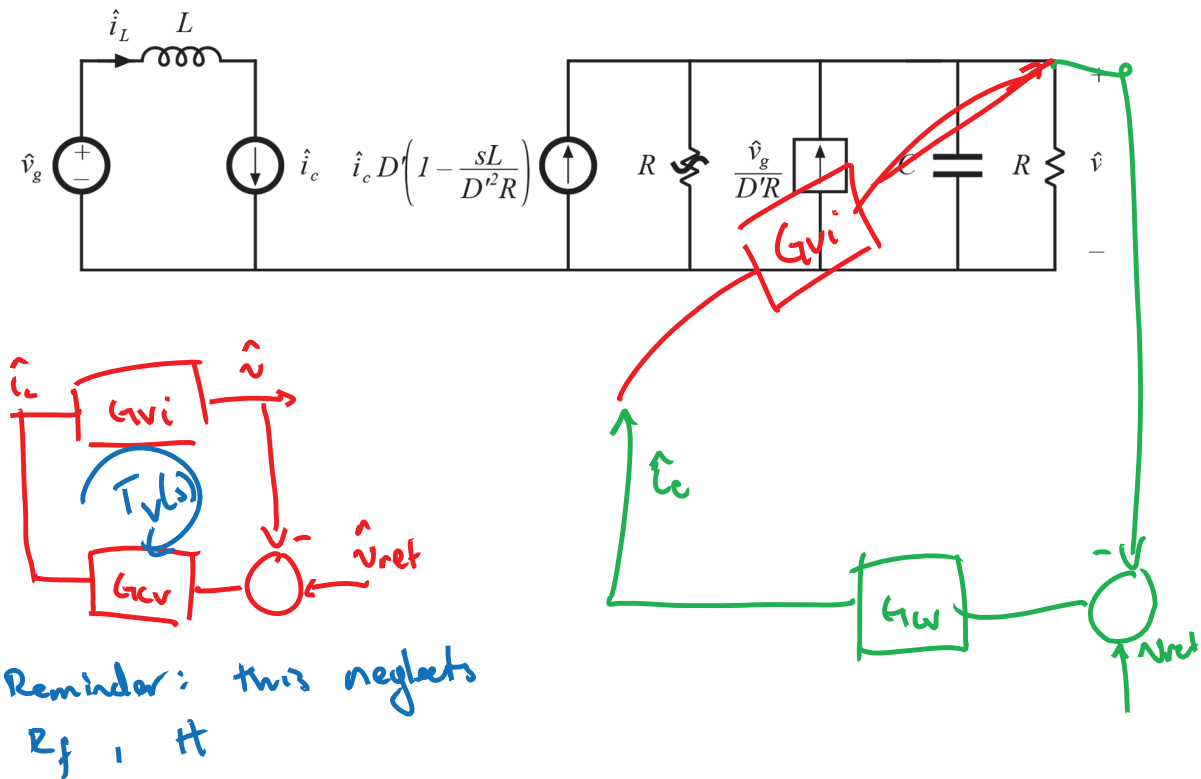

CPM Oscillations for $D > 0.5$

- The current programmed controller is inherently unstable for $D > 0.5$, regardless of the converter topology
- Controller can be stabilized by addition of an artificial ramp

Inductor Current Waveform in CCM

 

*$i_L(T_s) = i_L(0) + m_1 dT_s - m_2 d'T_s$
in steady-state*

$0 = m_1 dT_s - m_2 d'T_s$

$$\frac{m_2}{m_1} = \frac{D}{D'}$$

Inductor current slopes m_1 and $-m_2$

buck converter

$$m_1 = \frac{v_g - v}{L} \quad -m_2 = -\frac{v}{L}$$


boost converter

$$m_1 = \frac{v_g}{L} \quad -m_2 = \frac{v_g - v}{L}$$


buck-boost converter

$$m_1 = \frac{v_g}{L} \quad -m_2 = \frac{v}{L}$$

Introducing a Perturbation

 

Change in Inductor Current Over T_s

 

$$\left. \begin{aligned} \hat{i}_L(0) &= m_1 \hat{d} T_s \\ \hat{i}_L(T_s) &= -m_2 \hat{d} T_s \end{aligned} \right\} \hat{i}_L(T_s) = \hat{i}_L(0) \frac{-m_2}{m_1}$$

$$\hat{i}_L(2T_s) = \hat{i}_L(T_s) \left(\frac{-m_2}{m_1} \right) = \hat{i}_L(0) \left(\frac{-m_2}{m_1} \right)^2$$


$$\hat{i}_L(nT_s) = \hat{i}_L(0) \left(\frac{-m_2}{m_1} \right)^n$$

$$\alpha = \frac{-m_2}{m_1} = \frac{D}{D'} \alpha_0$$

need $|\alpha| < 1$ for stability

 
Example: Unstable operation for $D=0.6$

$$\alpha = -\frac{D}{D'} = \left(-\frac{0.6}{0.4}\right) = -1.5$$





 Example: Stable operation for $D=1/3$

$$\alpha = -\frac{D}{D'} = \left(-\frac{1/3}{2/3}\right) = -0.5$$



Stabilization Through Artificial Ramp

 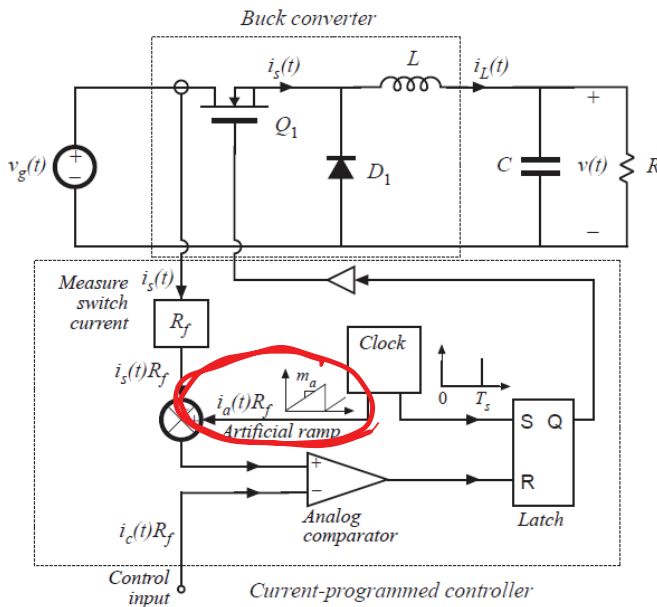

Now, transistor switches off when

$$i_a(dT_s) + i_L(dT_s) = i_c$$

or,

$$i_L(dT_s) = i_c - i_a(dT_s)$$

if $i_a \gg i_c \rightarrow$ PWM control
 if $i_a \ll i_c \rightarrow$ CPM

Final Value of Inductor Current

First subinterval:

$$\hat{i}_L(0) = -\hat{d}T_s (m_1 - m_a)$$

Second subinterval:

$$\hat{i}_L(T_s) = -\hat{d}T_s (m_a - m_2)$$

Net change over one switching period:

$$\hat{i}_L(T_s) = \hat{i}_L(0) \left(-\frac{m_2 - m_a}{m_1 + m_a} \right)$$

After n switching periods:

$$\hat{i}_L(nT_s) = \hat{i}_L((n-1)T_s) \left(-\frac{m_2 - m_a}{m_1 + m_a} \right) = \hat{i}_L(0) \left(-\frac{m_2 - m_a}{m_1 + m_a} \right)^n = \hat{i}_L(0) \alpha^n$$


Characteristic value:

$$\alpha = -\frac{m_2 - m_a}{m_1 + m_a} \quad \left| \hat{i}_L(nT_s) \right| \rightarrow \begin{cases} 0 & \text{when } |\alpha| < 1 \\ \infty & \text{when } |\alpha| > 1 \end{cases}$$

Artificial Ramp: Additional Notes

- For stability, require $|\alpha| < 1$
- Common choices:
 - $m_a = 0.5 m_2$ (stable for all duty cycles)
 - $m_a = m_2$ (deadbeat)
- Artificial ramp decreases sensitivity to noise
 
$$\alpha = -\frac{1 - \frac{m_a}{m_2}}{\frac{D'}{D} + \frac{m_a}{m_2}}$$



More Accurate Models

- The simple models of the previous section yield insight into the low-frequency behavior of CPM converters
- Unfortunately, they do not always predict everything that we need to know:
 - Line-to-output transfer function of the buck converter
 - Dynamics at frequencies approaching f_s
- More accurate model accounts for nonideal operation of current mode controller built-in feedback loop
- Converter duty-cycle-controlled model, plus block diagram that accurately models equations of current mode controller
- See Section 12.3 for additional info

More Accurate Model

- Simple model assumes $i_L = i_C$ always
- Accounting for ripple, and artificial ramp weakens this approximation
- Using sampled data modeling

$$\frac{\hat{i}_L}{\hat{i}_C} = \frac{1}{1 + \frac{1}{Q_s} \left(\frac{s}{2\pi f_s/2} \right) + \left(\frac{s}{2\pi f_s/2} \right)^2}$$

if my bandwidth of voltage loop is well below $f_s/2$ then $i_L \approx i_C$ applies

Where

$$Q_s = \frac{2}{\pi \left(\frac{2}{1-\alpha} - 1 \right)}$$

F. Dong Tan and R. D. Middlebrook, "A Unified Model for Current Programmed Converters," IEEE Transactions on Power Electronics, vol. 10, no. 4, July 1995.



Note: Comparison to Datasheet

Application Information (continued)

 


Figure 30. Effect of Initial Perturbation when $dl_1/dl_0 < -1$

dl_1/dl_0 can be calculated as:

$$\frac{dl_1}{dl_0} = 1 - \frac{1}{K}$$

$\alpha = 1 - \frac{1}{K}$

The relationship between dl_1/dl_0 and K factor is illustrated in the graphic below.


 


Figure 31. dl_1/dl_0 vs K Factor

The absolute minimum value of K is 0.5. When $K < 0.5$, the amplitude of dl_1 is greater than the amplitude of dl_0 and any initial perturbation results in sub-harmonic oscillation. If $K = 1$, any initial perturbation will be removed in one switching cycle. This is known as one-cycle damping. When $-1 < dl_1/dl_0 < 0$, any initial perturbation will be under-damped. Any perturbation will be over-damped when $0 < dl_1/dl_0 < 1$.


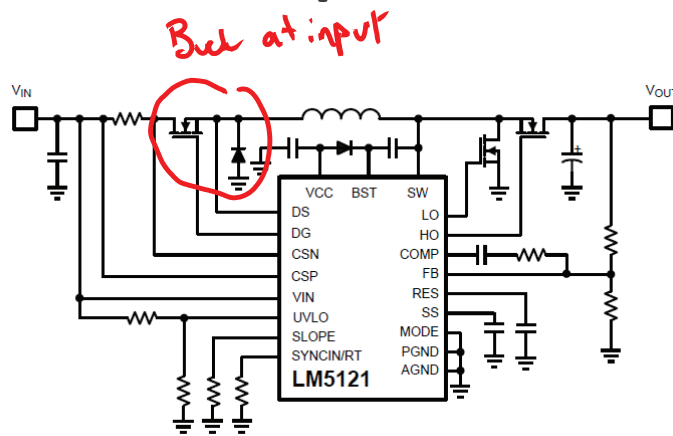


Application to Experiment 4





- Complex switching controller
- **Read the datasheet first**



Startup: Switching

  


Startup: No Switching

  


Short-Circuit: Switching

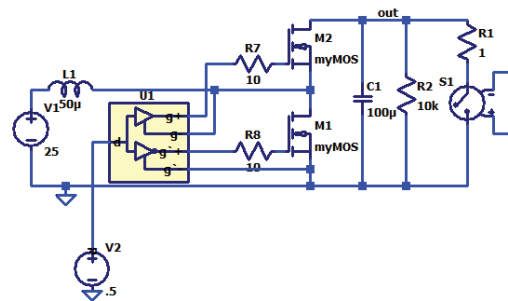
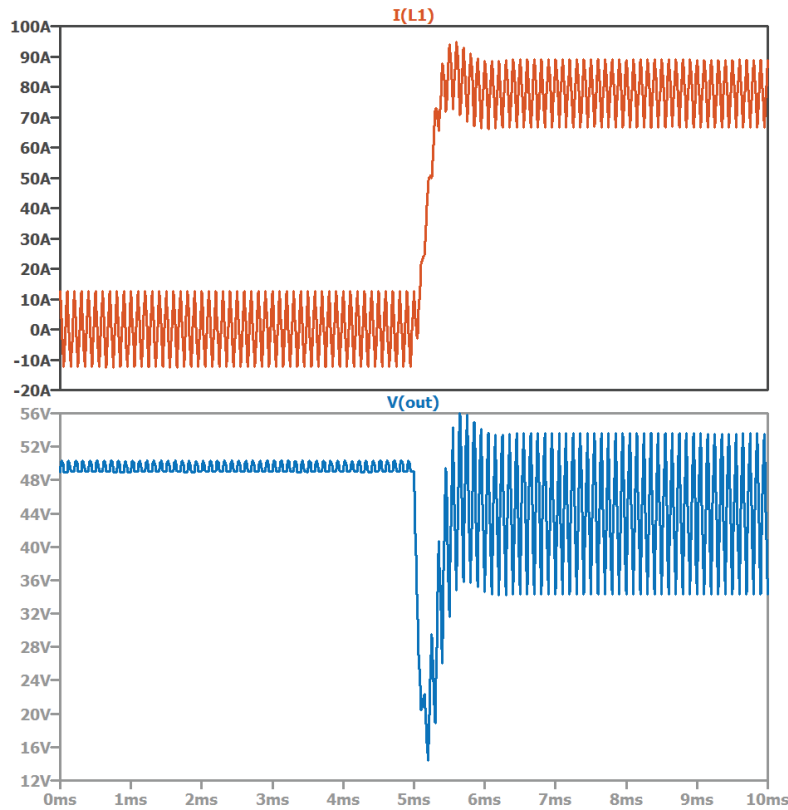


Short-Circuit: No Switching

 


LM5121: Functionality

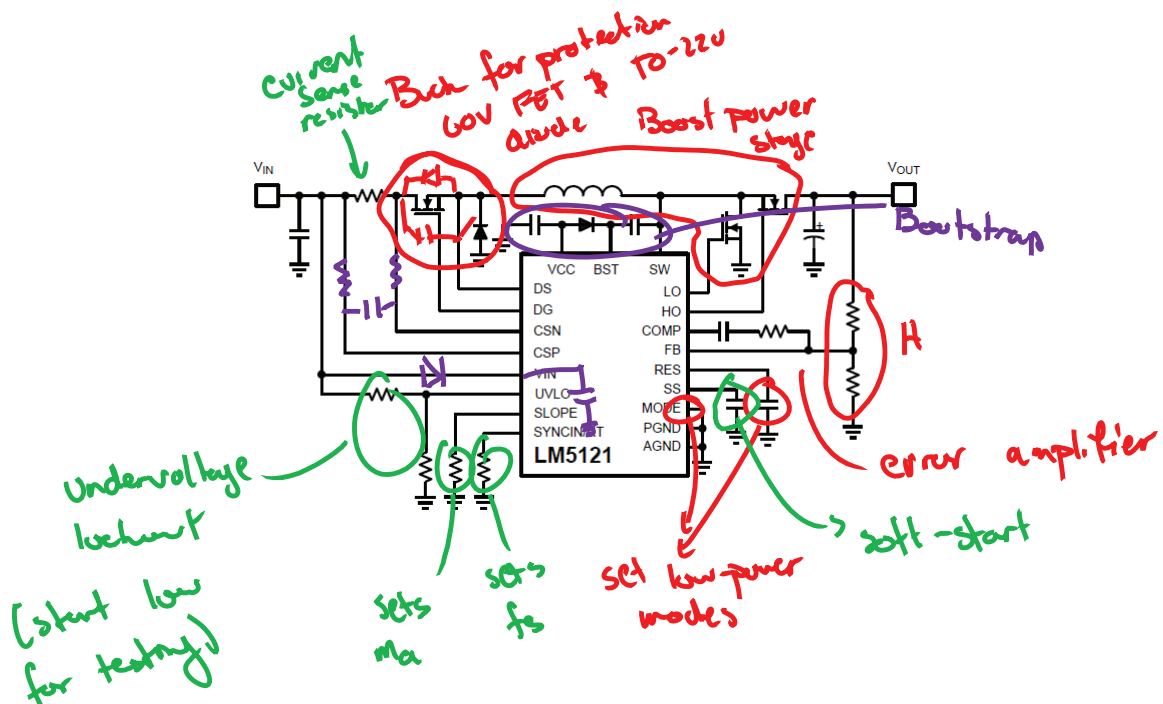

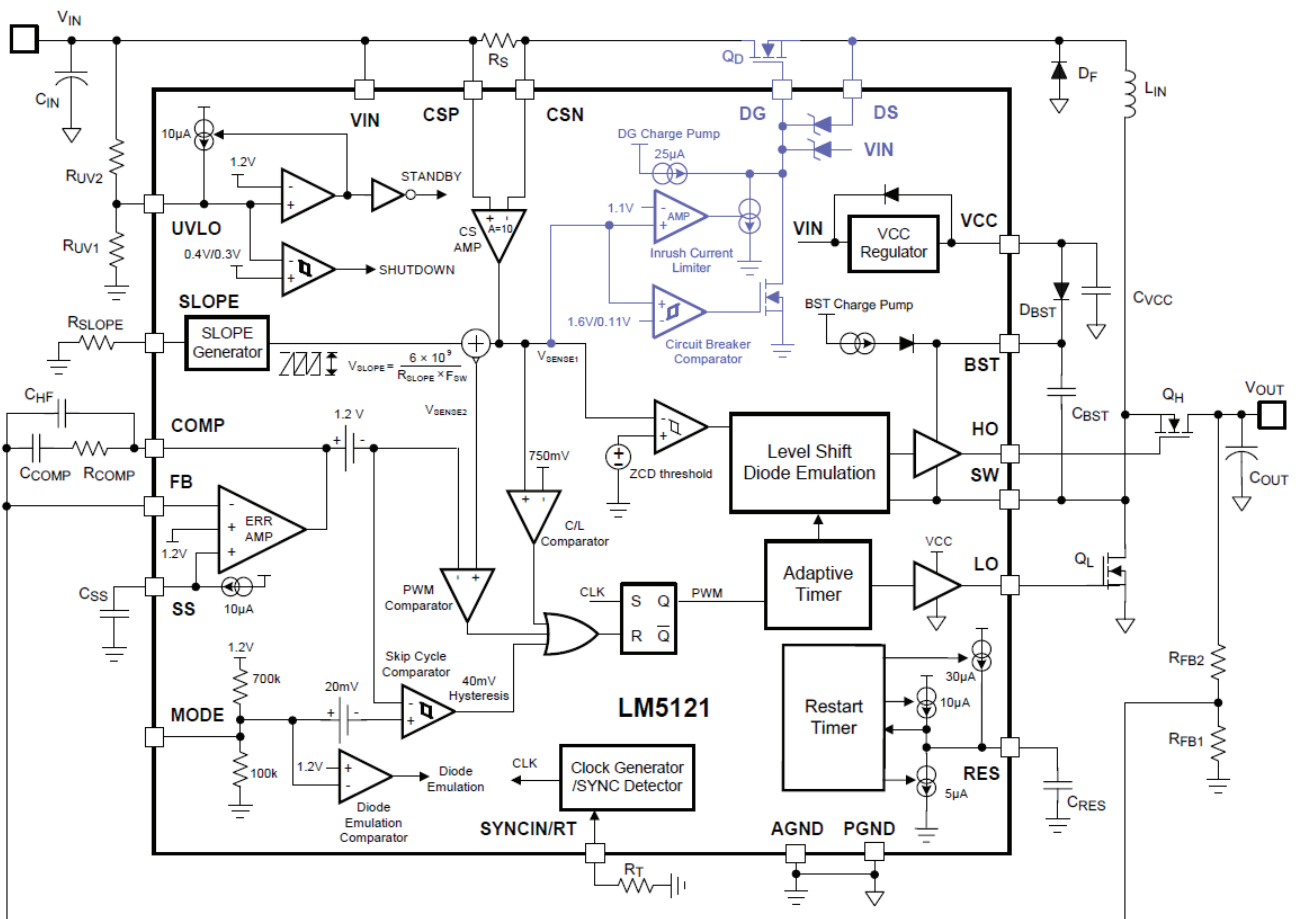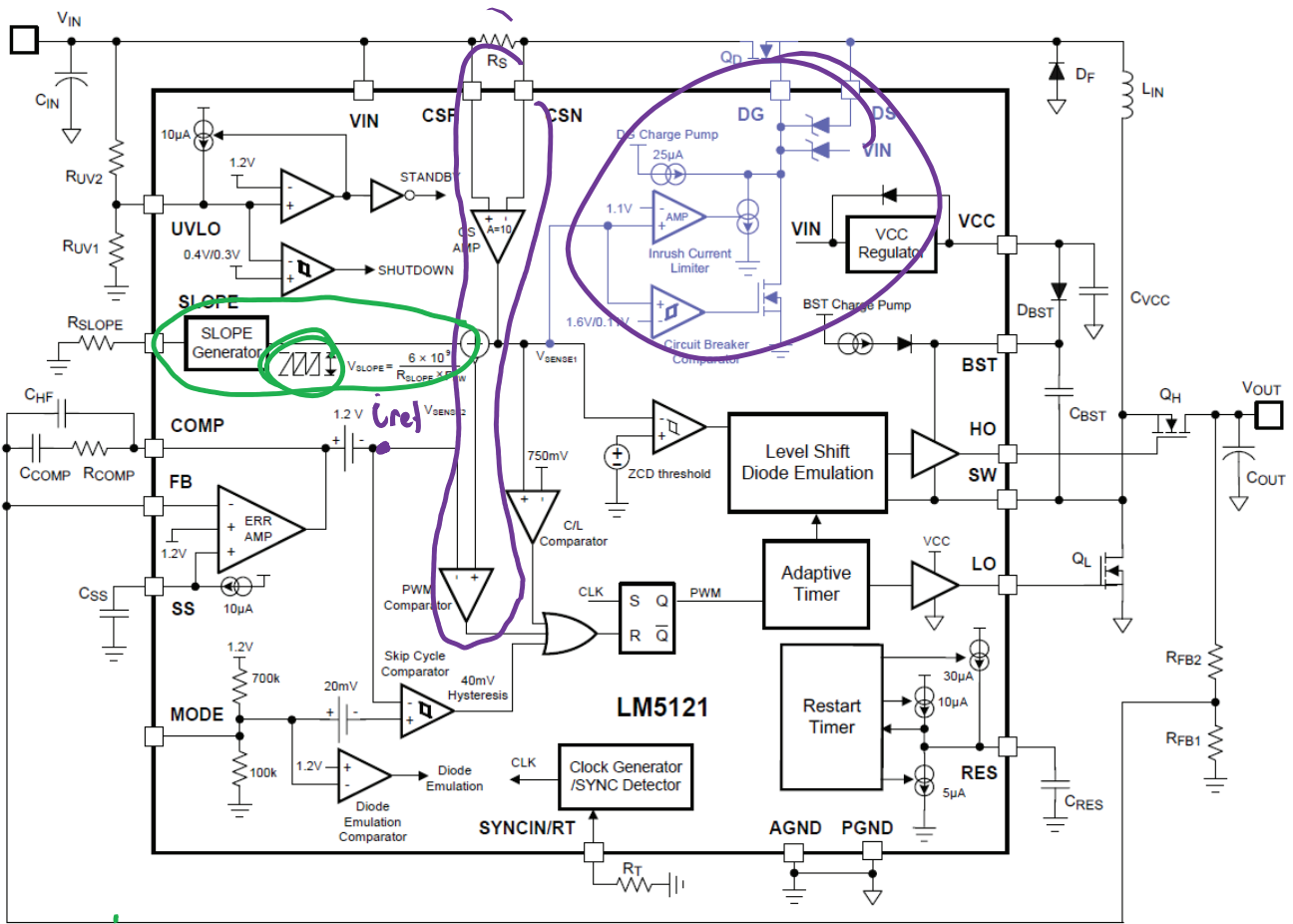

Internal Functional Model in LTSpice

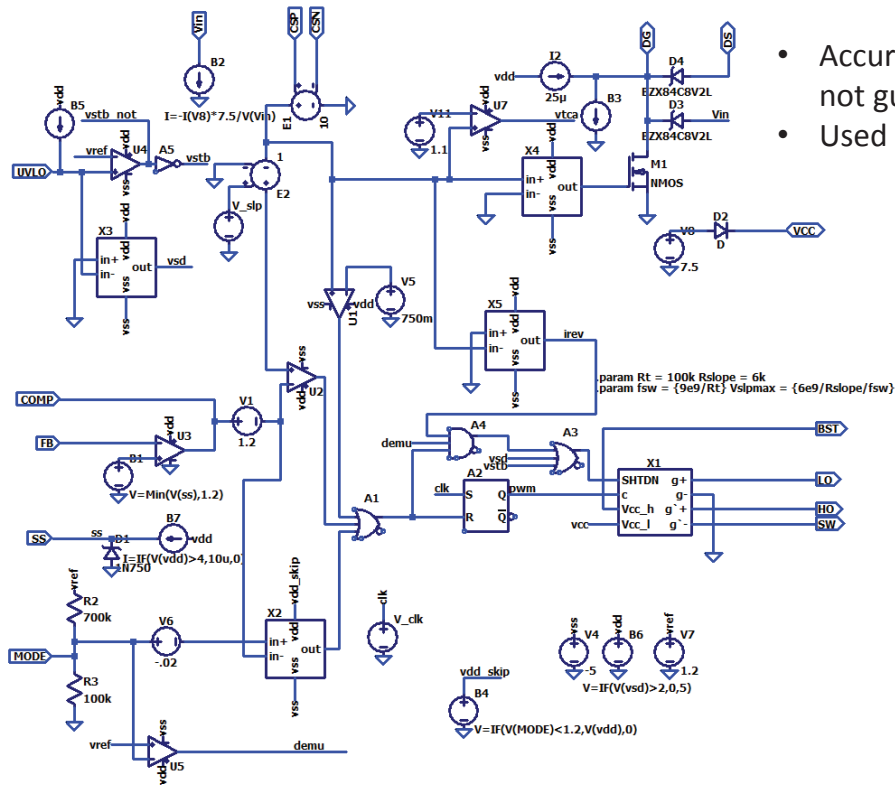

- Accuracy/functionality not guaranteed
- Used for insight only


In-Circuit Simulation

```
.model mysw sw(Von=3 Voff=2 Ron=.1 Roff = 1Meg)
```


```
.model myMOS VDMOS(Rg=1 Vto=4.5 Rd=14m Rs=10m Rb=17m Kp=30 Cgdmax=.5p Cgdmin=.05n Cgs=.2n Cjo=.03p Is=88p)
```

```
.tran 1 uic
```

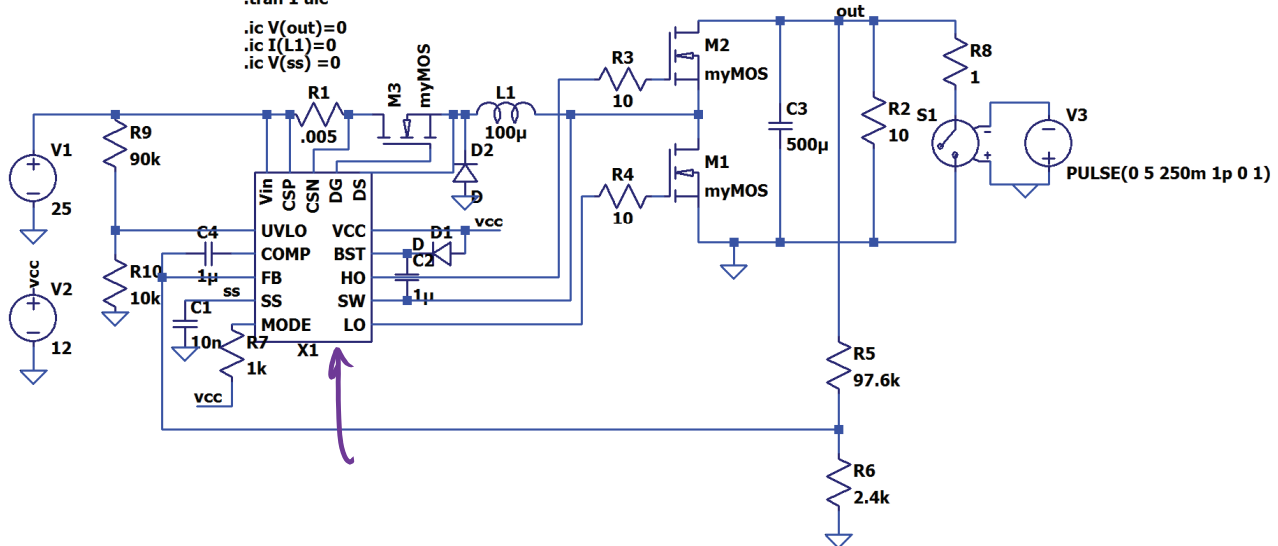
```
.ic V(out)=0  
.ic I(L1)=0  
.ic V(ss)=0
```




Sim Results

 

A Tip: Debug Internal of Subcircuit

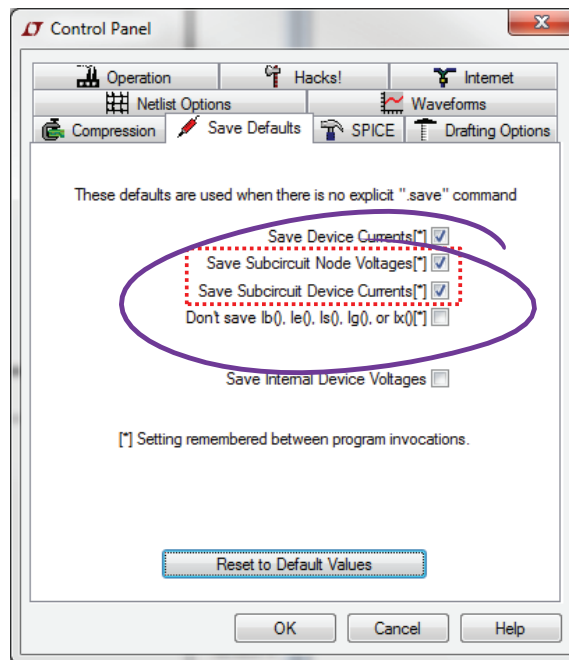


Experiment 4: Gate Driver Selection

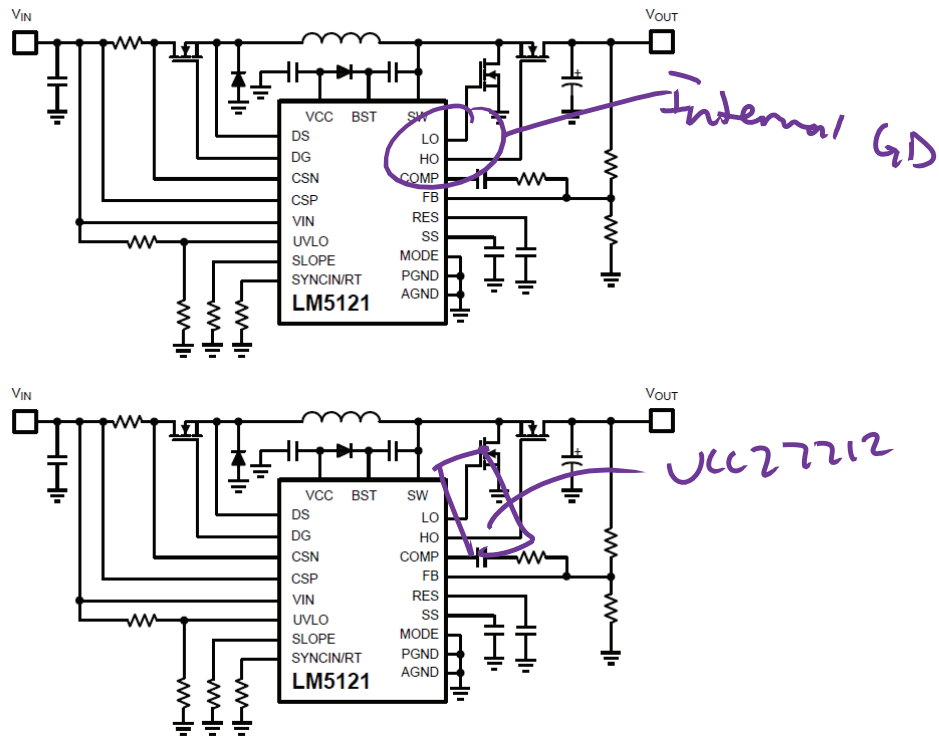


Experiment 4: Closing the Loop

- Closed-loop operation in steps
 1. Open-loop operation with LM5121 modulator
 - Requires “tricking” LM5121
 2. Closed-loop current regulation
 3. Closed-loop voltage and current regulation

Open-Loop Operation

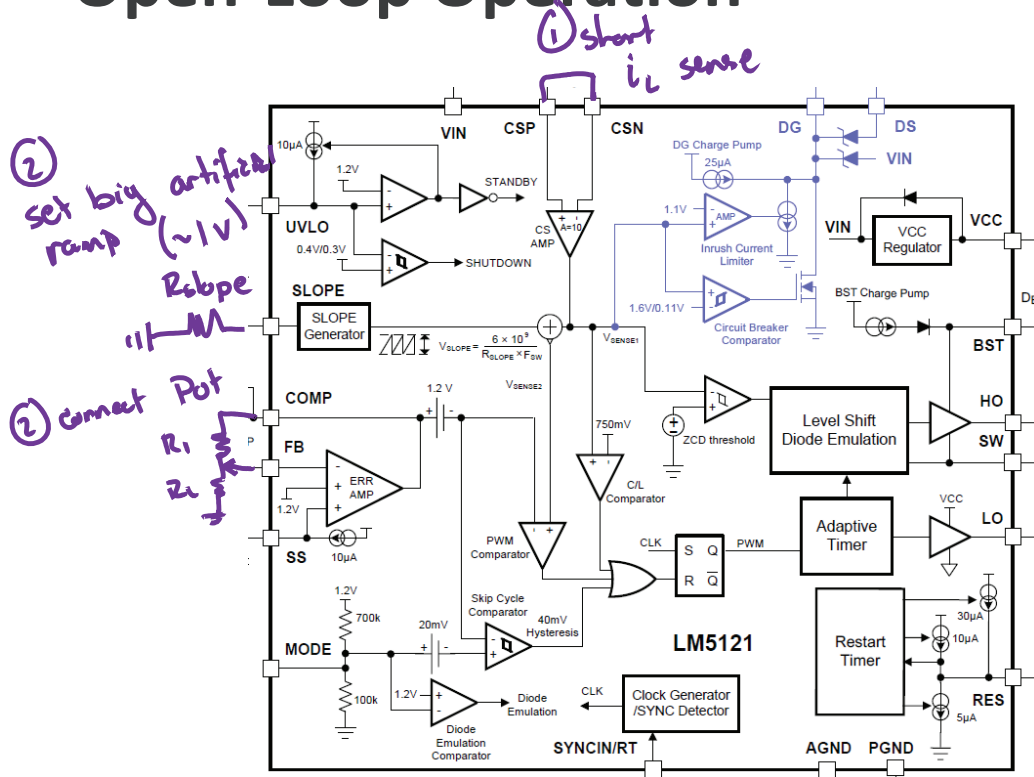


Setting the Electronic Load

 


Be careful with how you set electronic load
 Safest: ① & ③ current or resistance
 ② Voltage

Low-frequency model

① Open Loop:

 

 ② Current Loop Only Large R = large voltage!



③ Voltage & Current Loop

