

PCB Layout

ECE 482 Lecture 5
March 14, 2018




THE UNIVERSITY OF
TENNESSEE
KNOXVILLE

Announcements

- Prelab 5
 - Decide on System Improvements
 - Redesign using GaN Devices
- Midterm after Experiment 5
 - Open note, book, instructor
- Today: Experiment 5
 - No report; deliverables are layout files and BOM

Lab 5: PCB Layout

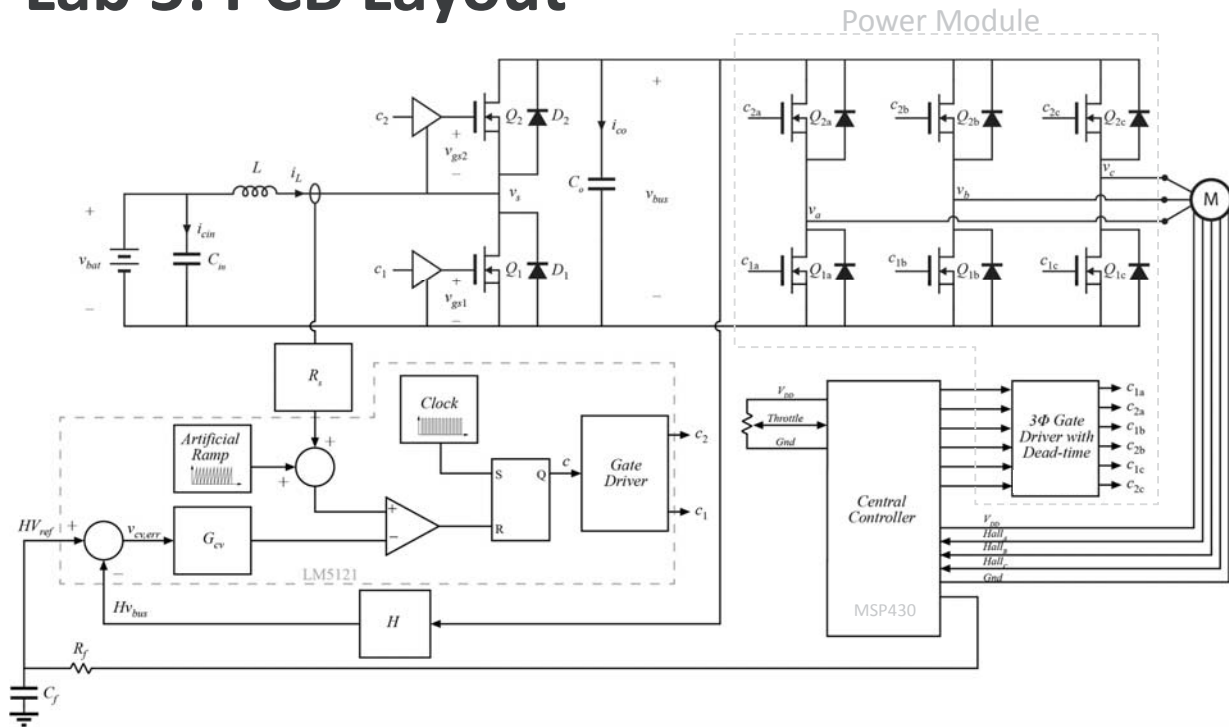


Design Modification

- You may order additional parts, at reasonable cost/benefit
 - Will need to provide a listing of parts from digikey with final Exp 5 files
 - May not exceed \$350 for parts and PCB
- Reuse components from lab kit where possible
- Use SMD ceramic, low ESR caps for power stage and gate drive decoupling

Circuit Enclosure




Circuit Enclosure - Mounting

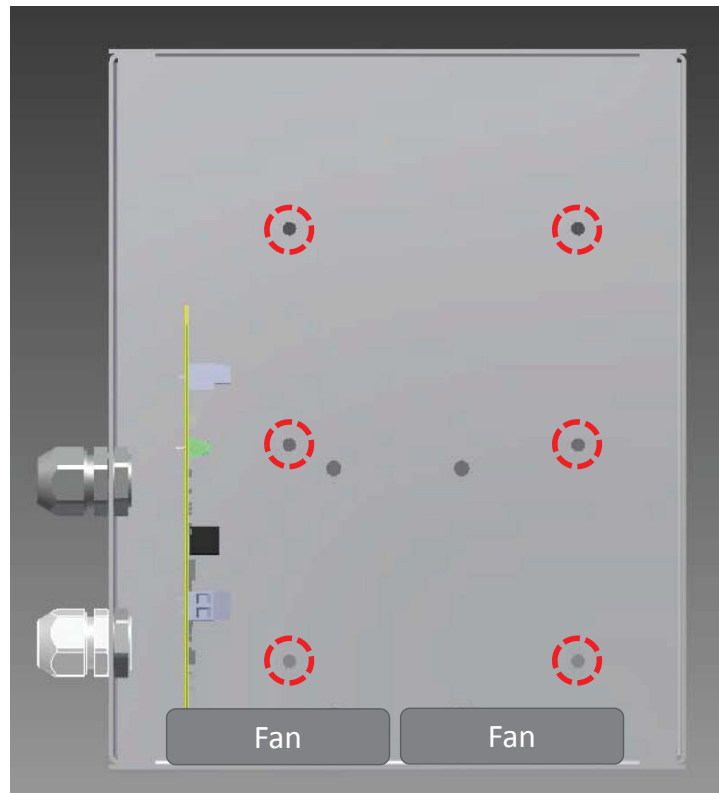

Fans – 1 W each, need to be powered from your board

Circuit Connections

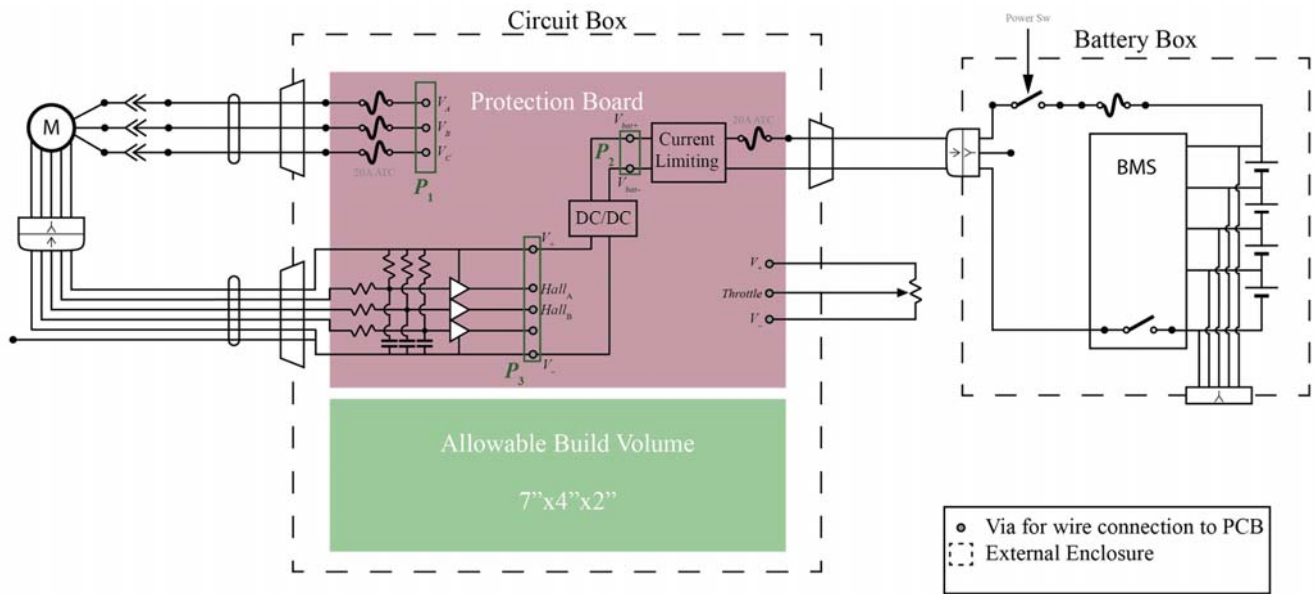

Prelab for Experiment 5: Redesign with GaN

GaN Systems GS61004T

- 15 mOhm
- 100V/40A
- $Q_g = 6.2$ nC
- $C_{oss} = 140$ pF (50V)




EPC EPC2001C


- 7 mOhm
- 100V/36A
- $Q_g = 9$ nC
- $C_{oss} = 375$ pF (80V)



GaN Devices

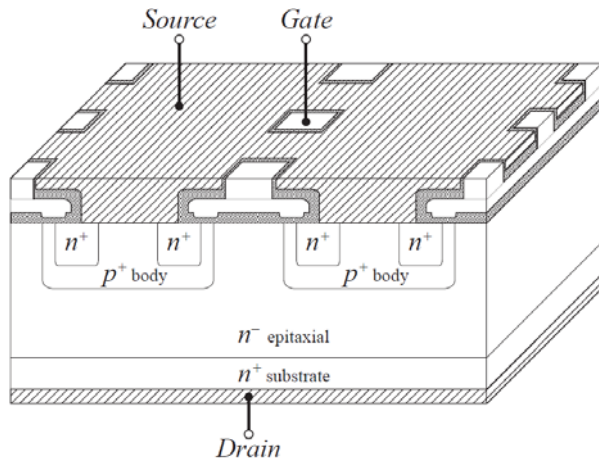

Vertical Silicon Power MOSFET

 

Lateral GaN HEMT

- No body diode (reverse conduction due to $V_{gd} > V_{gd,th} \approx 2V$)
 - Use antiparallel (schottky) diode or precise dead time
- Significantly faster switching

Designing with GaN


 





Fig. 1: Material properties of silicon, silicon carbide, and gallium nitride.

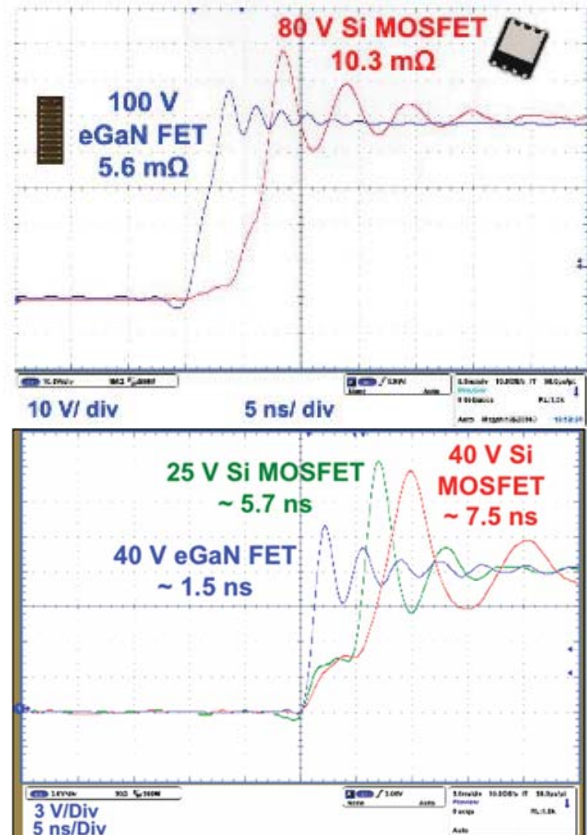- Because of high electric breakdown field and high electron velocity, GaN devices with comparable R_{on} can be significantly smaller and switch must faster.
- Need **very** good layout to prevent ringing from causing overvoltage and device failure.
- More information:
 - <http://potential.eecs.utk.edu/About.php?topic=PowerSemiconductors>




GaN Design Issues

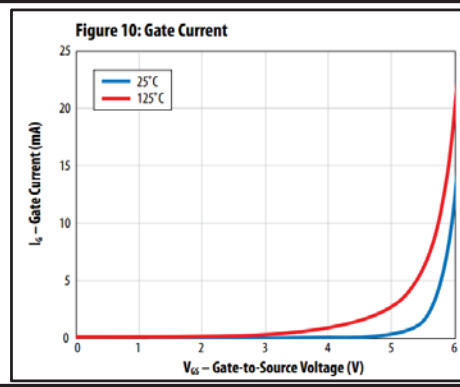  1. Reverse conduction mechanism
2. Sensitivity to parasitics
3. Gate robustness
4. Small size -> Thermal, soldering difficult



Daughter Boards

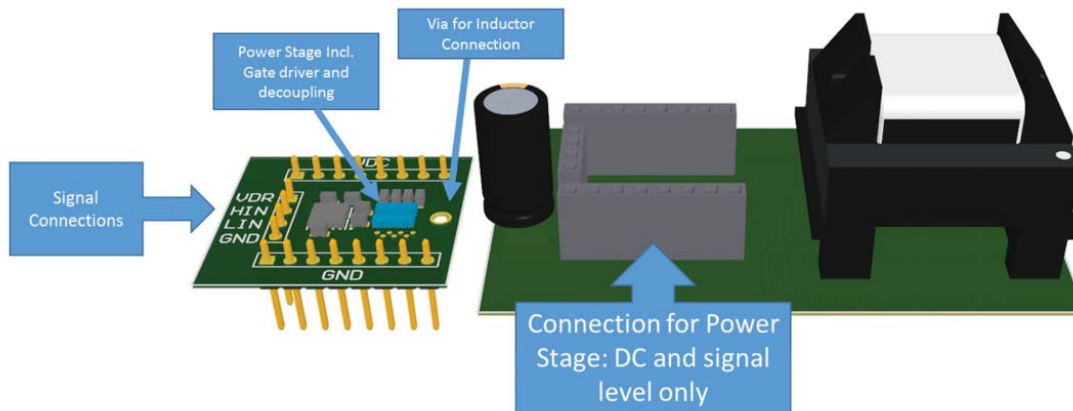

Motor Control

- Motor control is open-loop
- User throttle monotonically increases power
 - Controlled as BLDC motor
- Two options to change throttle
 - Alter boost output voltage
 - Alter duty cycle of motor drive

Motor Driver: Trapezoidal Control

 


FIGURE 3. BASIC BLDC MOTOR POWER TOPOLOGY

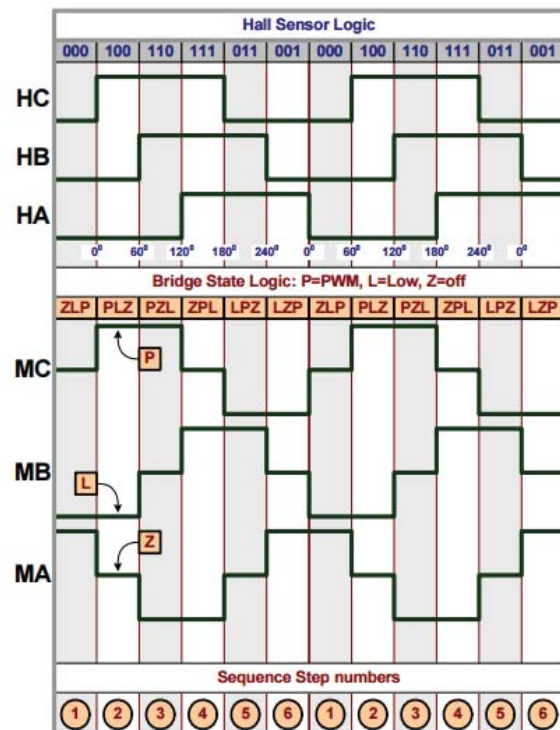


FIGURE 4. HALL SENSOR LOGIC vs BRIDGE STATE LOGIC

Trapezoidal Control: HF PWM

 


FIGURE 3. BASIC BLDC MOTOR POWER TOPOLOGY



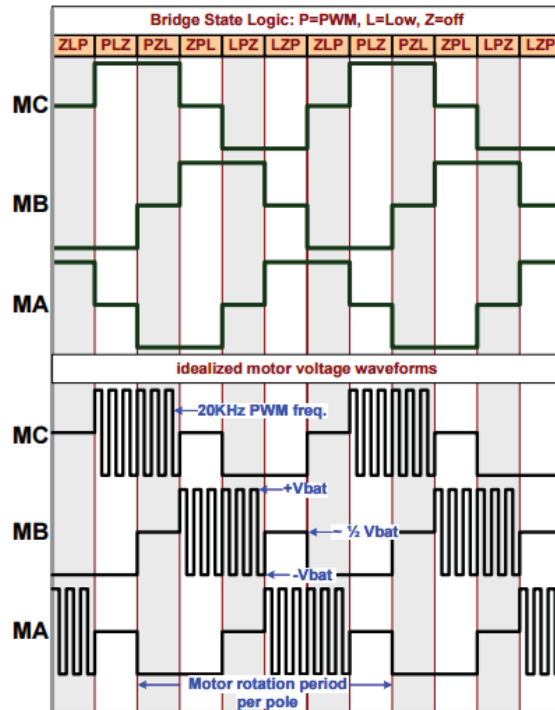
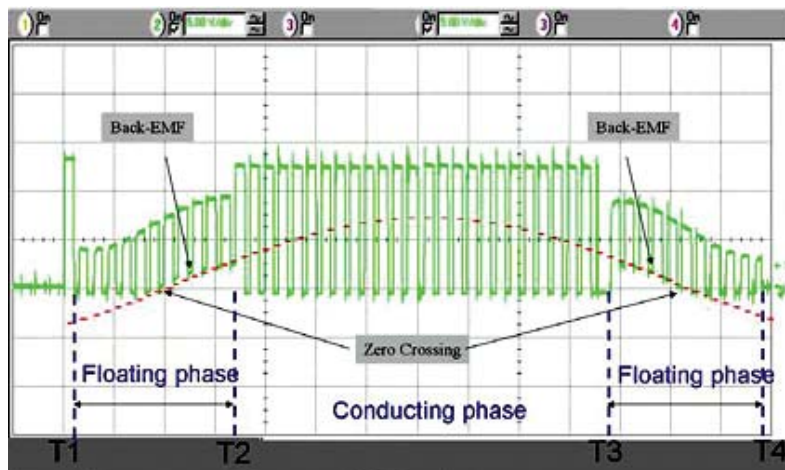


FIGURE 5. BRIDGE STATE LOGIC vs MOTOR VOLTAGE

A Note: Reflected Voltages

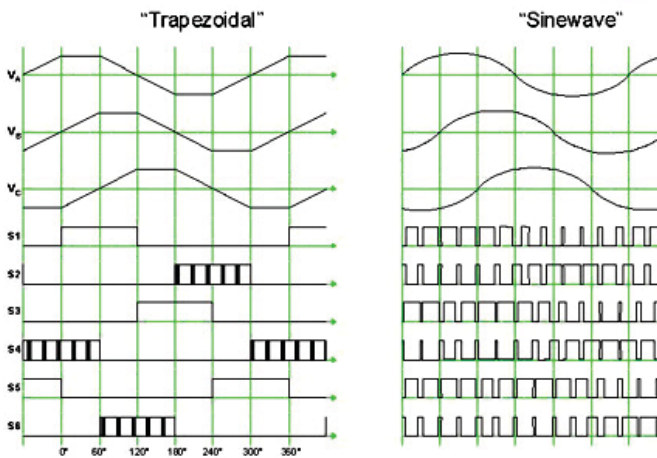


Sinusoidal (Vector) Control

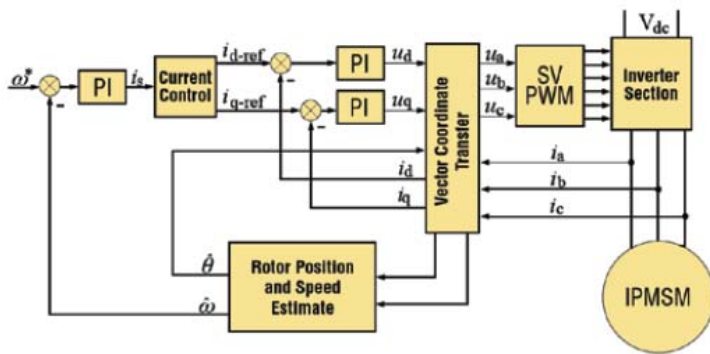


DC Bus Ripple – Trapezoidal Control

- $C_{DC} = 100\mu\text{F}$

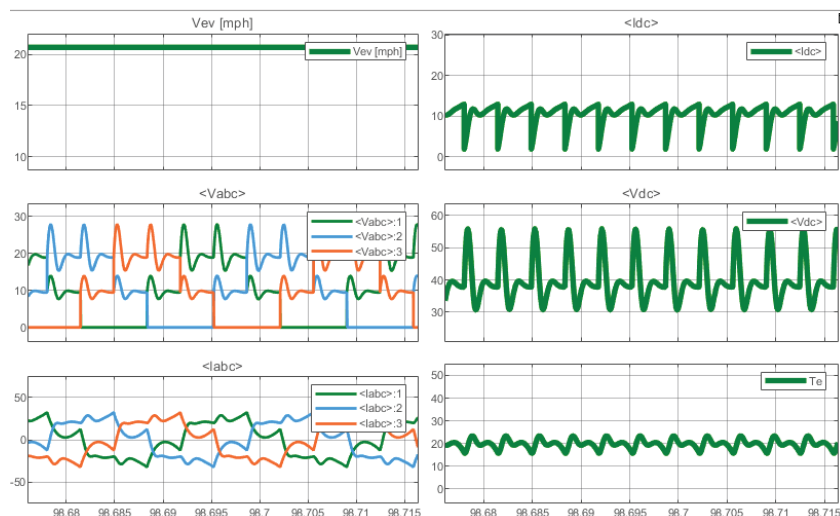


DC Bus Ripple – Sinusoidal Control

- $C_{DC} = 100\mu\text{F}$

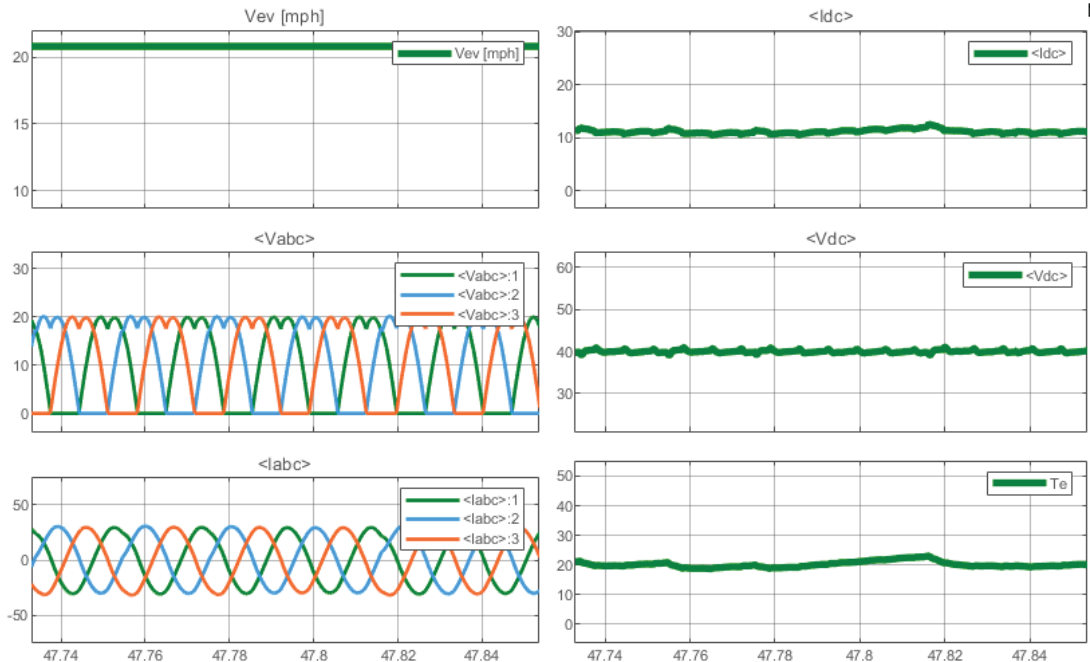


Reference Filtering

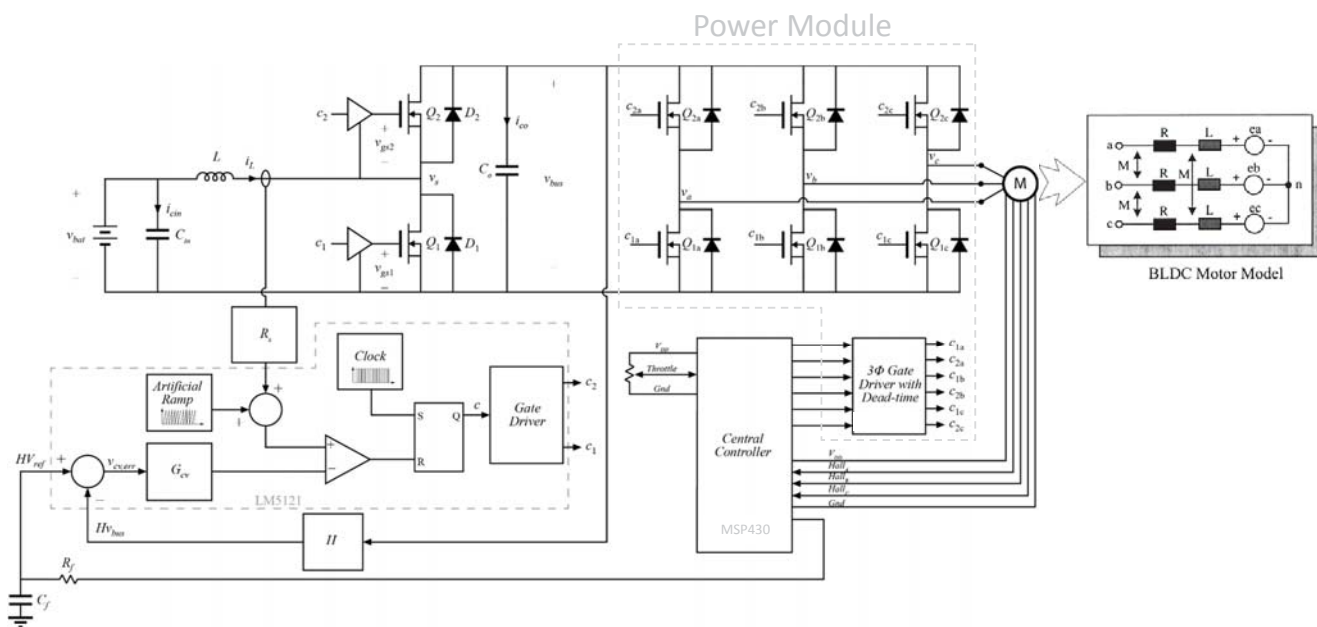

Motor Control Bandwidth


No Filter

May require braking circuit

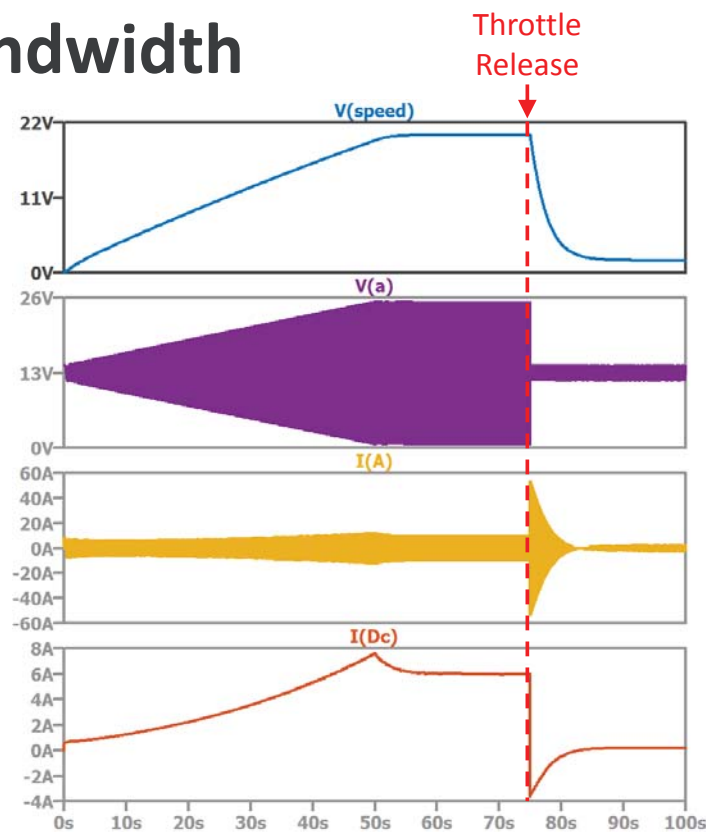

Motor Control Bandwidth

 $f_c = 8 \text{ mHz} + \text{ antiparallel diode}$



Motor Drive

- Power Stage
 - Power module
 - Integrated devices, and/or drivers
 - 3 Φ bridge (e.g. MTI85W100GC, IRAM136-3023B)
 - Half bridge (e.g. SQJ974EP, IPG20N10S4L)
 - Individual FETs
- Controller
 - Allegro A4915
 - Toshiba TB6551FAG
 - **TI DRV8308**
 - Other options
- Example Schematics in Starter Files for Experiment 5

PCB Layout for Experiment 5

- Include test points for voltages/currents to aid debugging
- Where possible, give yourself “backup options”
- Include option for heatsink
- Fans available, but consider power consumption
- Make sure parts you select are available and have sufficient stock
 - even if some get ordered in the interim



Basic PCB Layout Concepts

- Kelvin Connection
- Parasitic Capacitances and Decoupling
- Loop Inductances / Complete Routing
- Decoupling
- Ground Plane / Return Currents
- Partitioning



Trace Parasitics

 
 


Figure 12.18: Wire and Strip Inductance Calculations

 


Figure 12.24: Capacitance of two parallel plates

Figure 12.2: Calculation of Sheet Resistance and Linear Resistance for Standard Copper PCB Conductors



Kelvin Connection

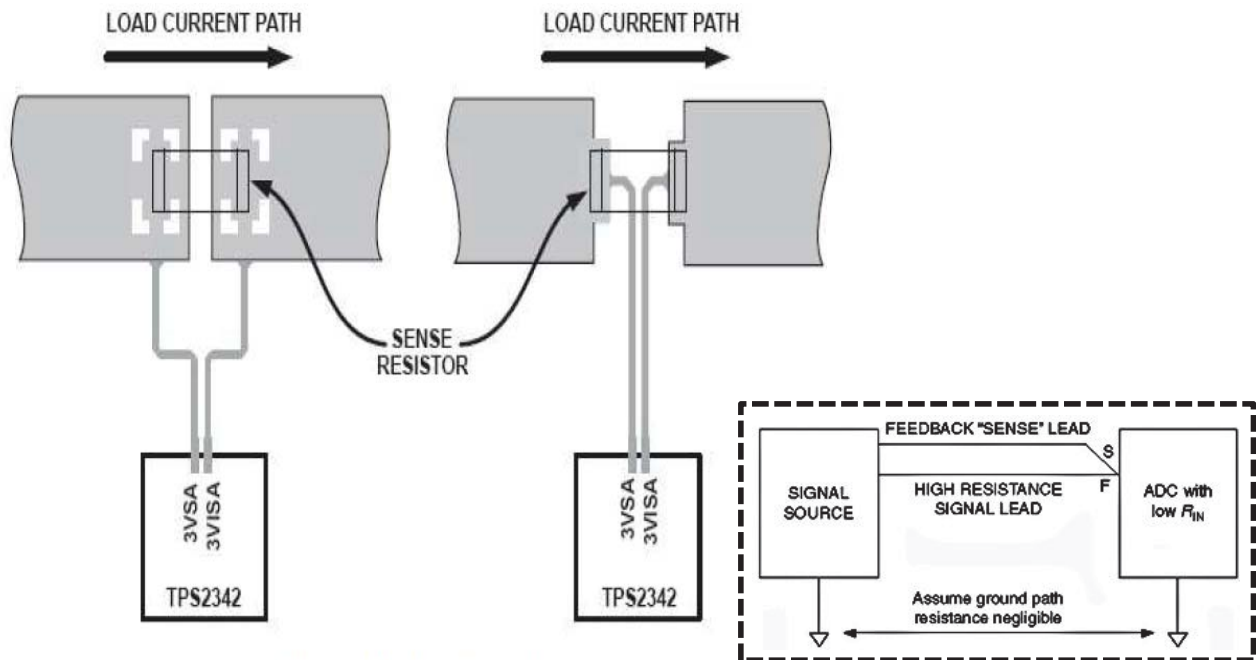


Figure 1. Kelvin Connection

Texas Instruments, "LMP8640/-Q1/HV Precision High Voltage Current Sense Amplifiers"

THE UNIVERSITY OF
TENNESSEE
KNOXVILLE




Decoupling

- Always add bypass capacitor at power supply for any IC/reference
- Use small-valued ($\sim 100\text{nf}$), low ESR and ESL capacitors (ceramic)
- Limit loop for any di/dt


THE UNIVERSITY OF
TENNESSEE
KNOXVILLE



Decoupling Capacitance

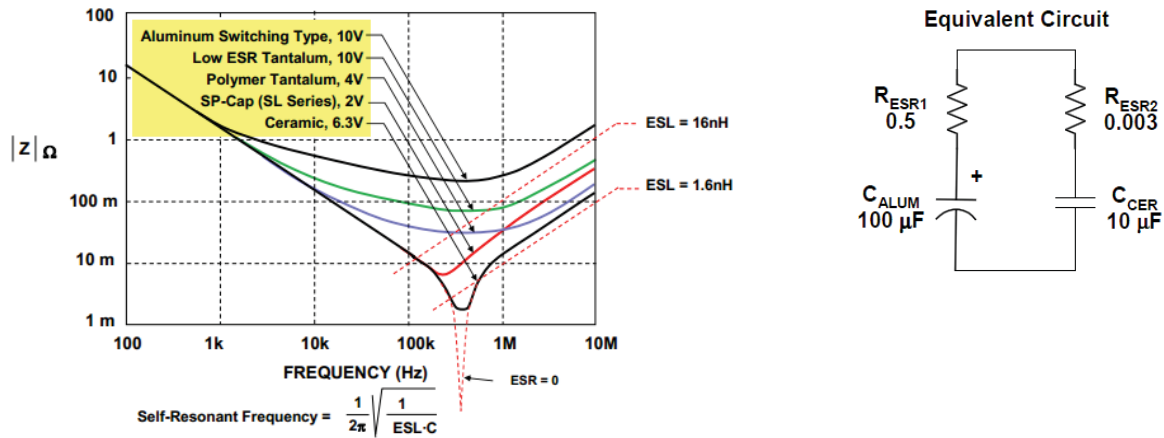

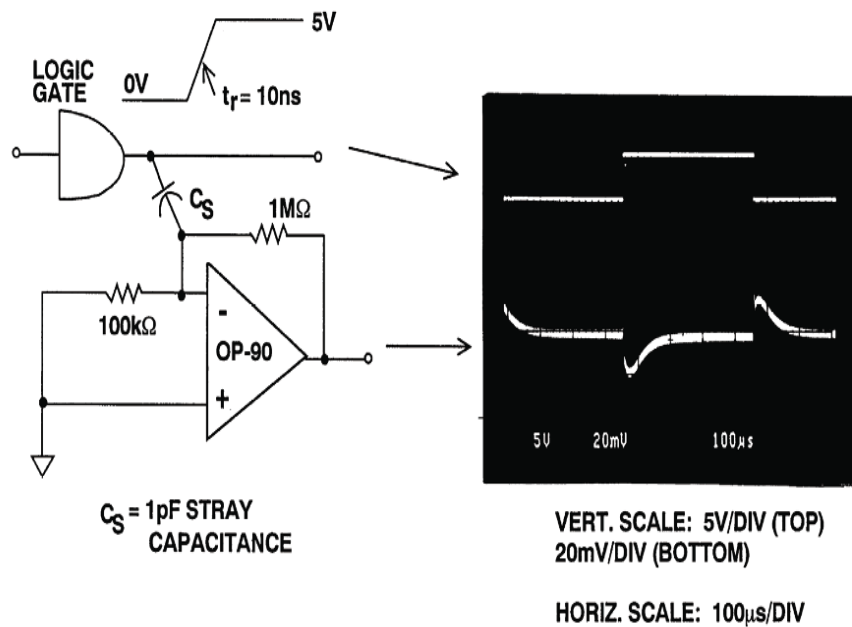High Impedance Nodes and Capacitive Coupling



Capacitive Shielding


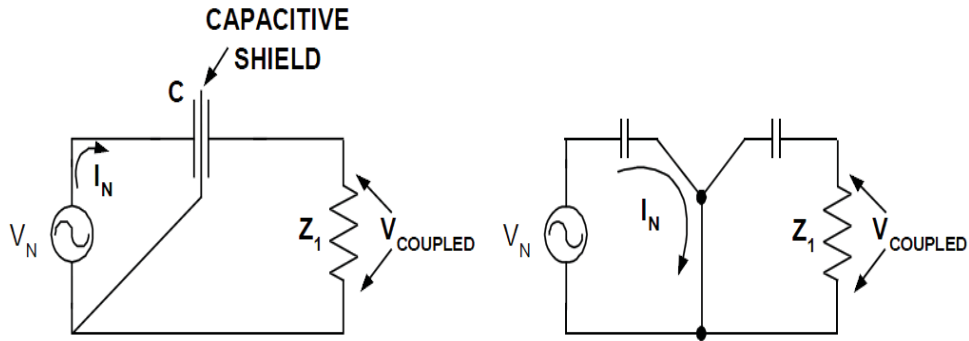


Figure 12.26: An Operational Model of a Faraday Shield

 


Analog Devices, "Decoupling Techniques," MT-101
 Analog Devices, "A Practical Guide to High-Speed Printed-Circuit-Board Layout"

Loop Inductances



 
Bad practice: wide separation of signal and return





Good practice: close coupling of signal and return

Ground Plane

 - Benefits:
 - Common reference
 - Shielding
 - Heat dissipation
 - Reduced inductance (increased capacitance)
- Resist urge to cut ground plane as much as possible; consider paths of return currents when cuts are unavoidable




Ground Plane Cuts

 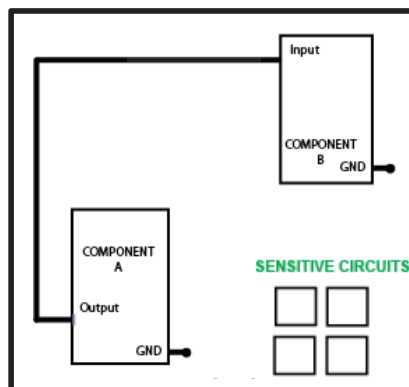

Ground return current path

Ground Plane Cuts

 

Cuts in Ground Plane


- Goals:
 - minimize inductance/loops
 - Minimize ground interference
- Routing cuts should be kept short and out of the path of any significant (high frequency) return paths
- Cuts can be used effectively for ground isolation, and to reduce noise coupled between digital/analog/power circuitry
- Reducing parasitic capacitance in sensitive signal locations (i.e. op-amp circuitry)

Ground Plane Example


<https://www.analog.com/en/analog-dialogue/articles/reducing-ground-bounce-in-dc-to-dc-converters.html>

Half Bridge Loop Inductance

 Parasitic inductances of input loop explicitly shown:




 Addition of bypass capacitor confines the pulsating current to a smaller loop:




high frequency currents are shunted through capacitor instead of input source

 
Even better: minimize area of the high frequency loop, thereby minimizing its inductance



Bridge Layout

 

Half Bridge Layout: Another Example

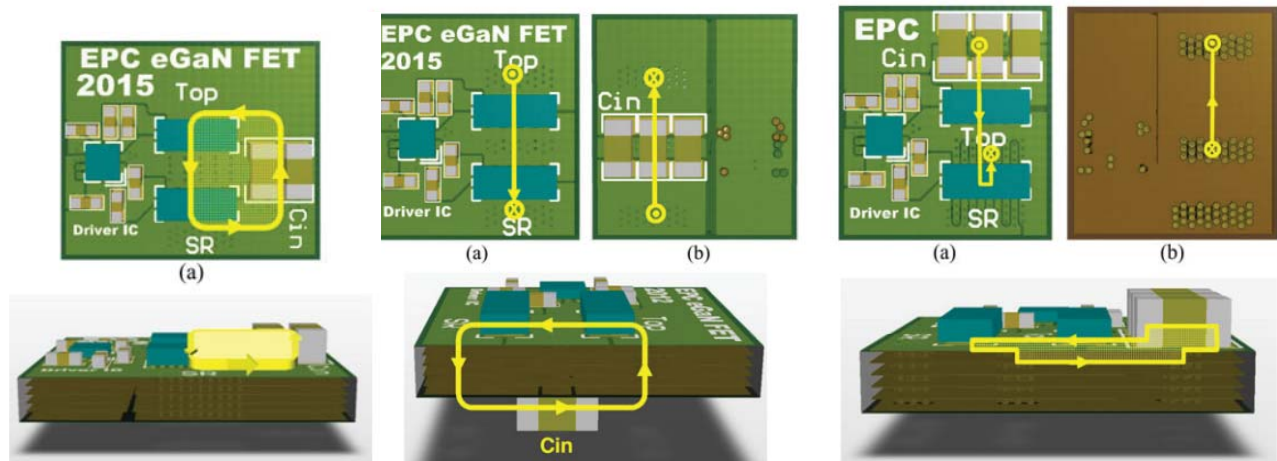


Lateral

Vertical

“Optimal”

Layout Impact Measurements

 

- Smallest Loop Area results in
 - Smaller overvoltage
 - Lower switching loss

D. Reusch & J Strydom, "Understanding the Effect of PCB Layout on Circuit Performance in a High-Frequency Gallium-Nitride-Based Point of Load Converter"

Experiment 5: Starting Files