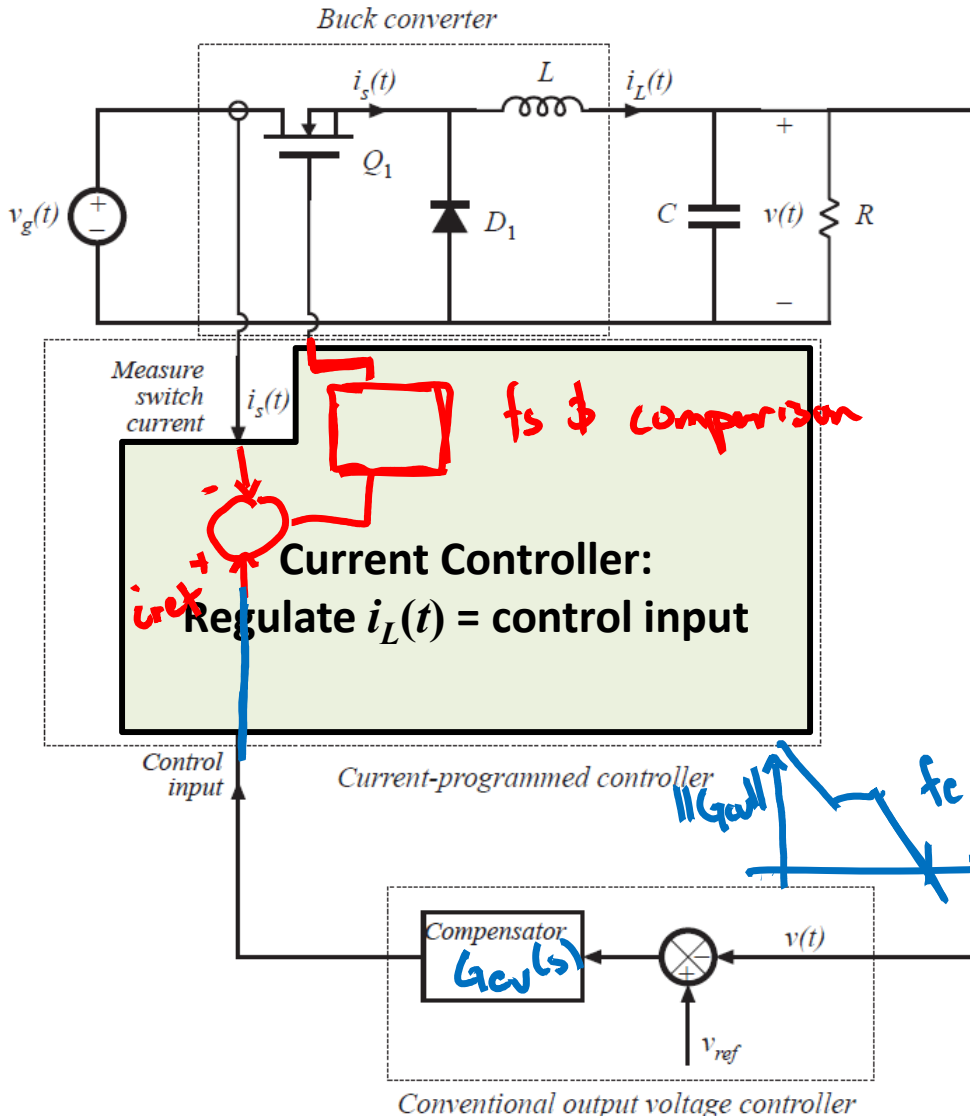


Current Control




Two control loops:

- (1) Fast (inner) current loop control
- Not Averaged
- (2) Slow (outer) voltage loop control
- Averaged


Effective averaged models can be used when $f_c \ll f_s$

Averaged vs CPM


Voltage-Mode

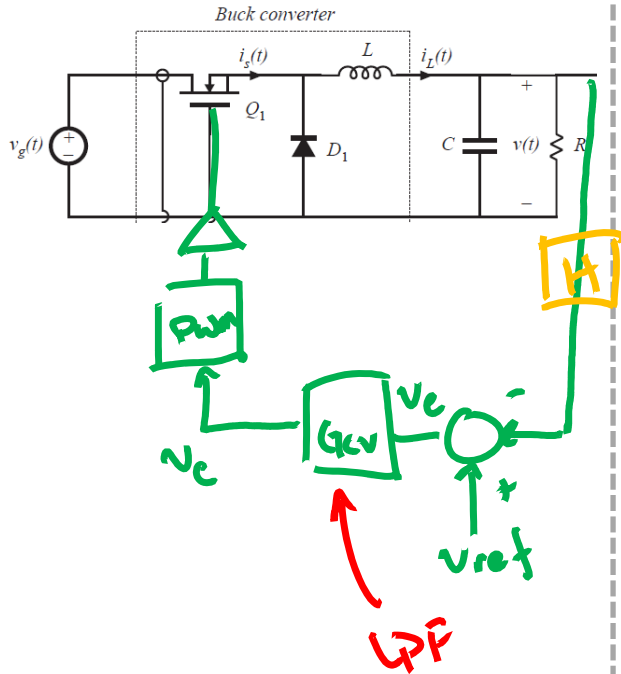


Averaged Current-Mode

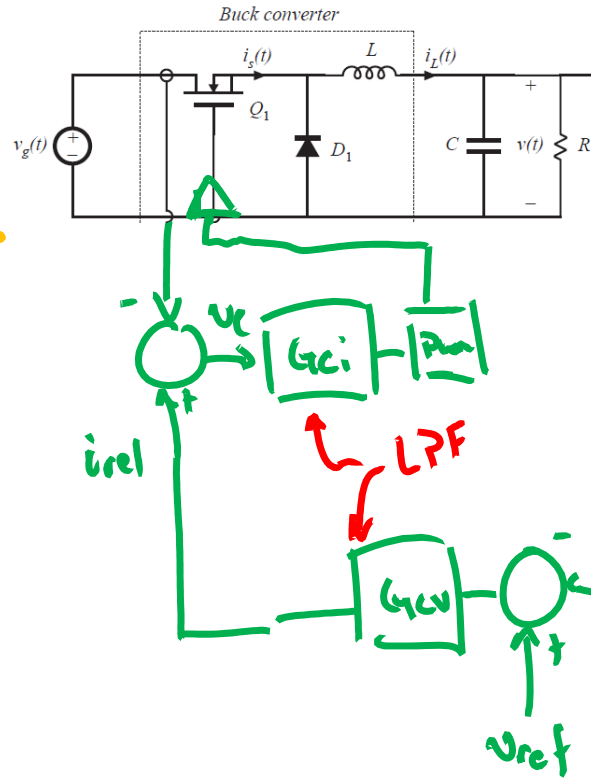

Current Programmed Mode

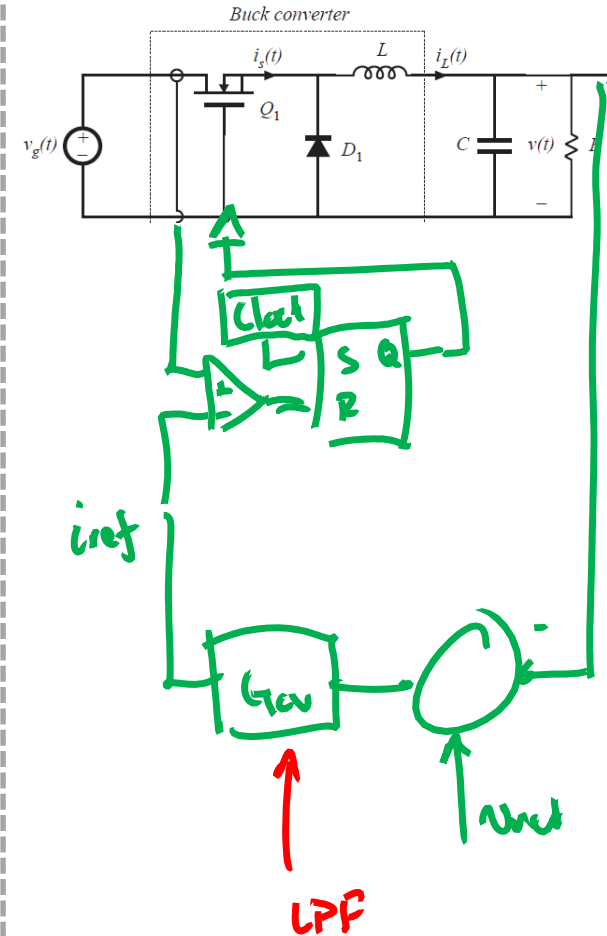


Current Programmed Control (CPM)

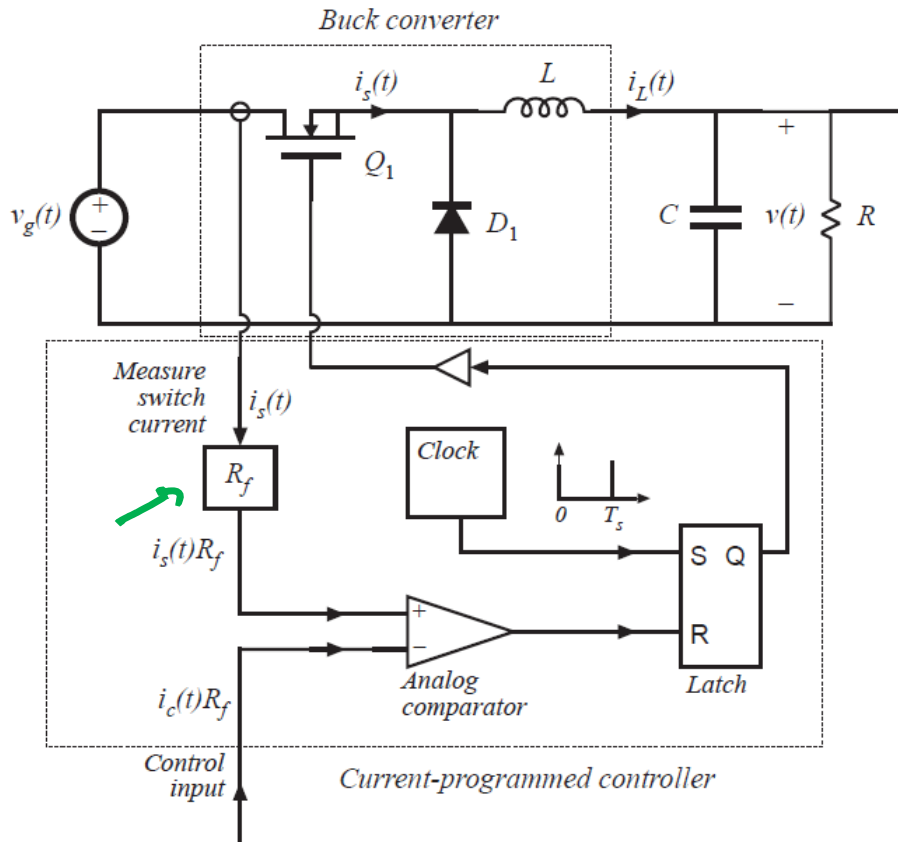


$R_f \rightarrow$ current-to-voltage gain of the sensing circuit

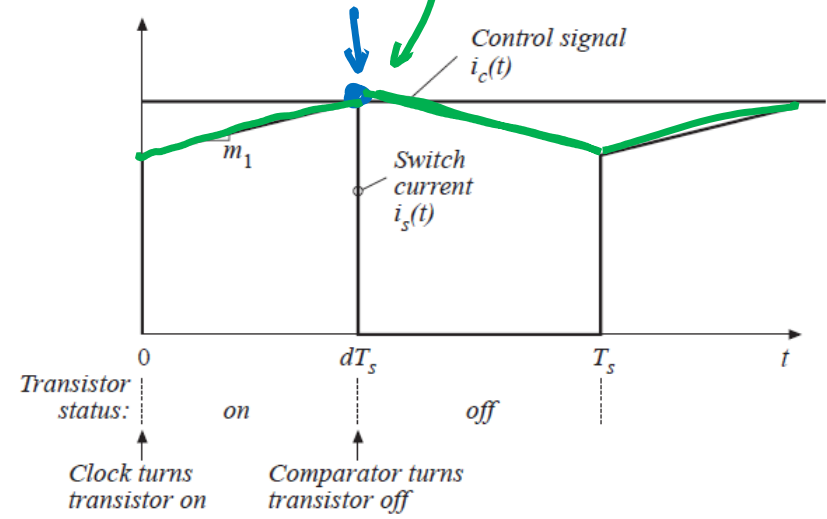
$i_{u,pt} = i_c(dT_s) = i_{ref}$ every period



CPM Voltage Loop

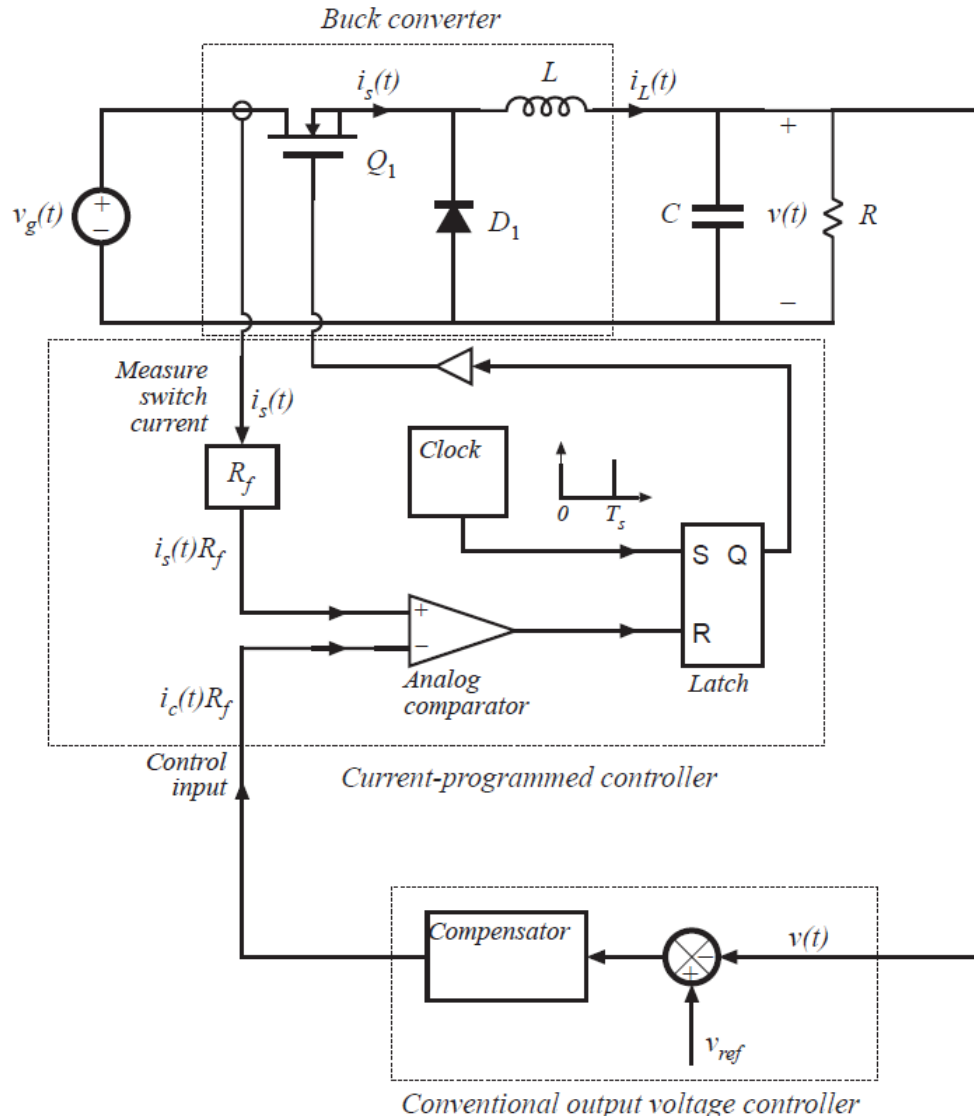

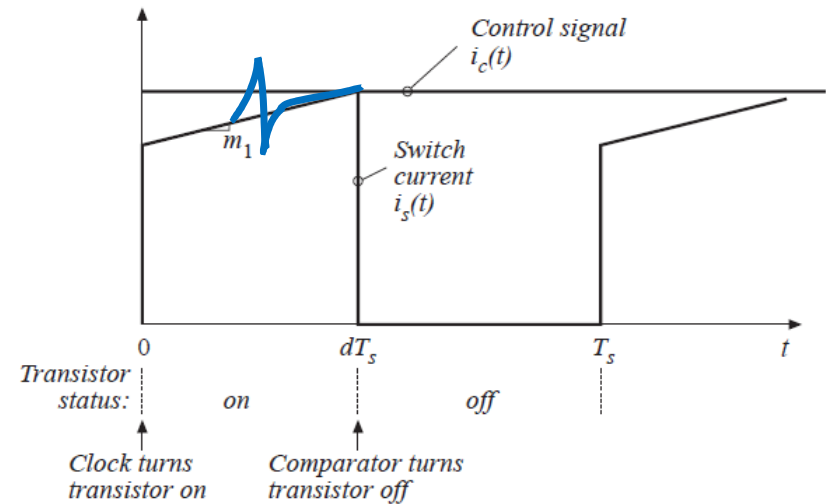
The peak transistor current replaces the duty cycle as the converter control input.



Current Programmed Control

- Covered in Ch. 12 of *Fundamentals of Power Electronics*
- Advantages of current programmed control:
 - Simpler dynamics — inductor pole is moved to high frequency
 - Simple robust output voltage control, with large phase margin, can be obtained without use of compensator lead networks
 - Transistor failures due to excessive current can be prevented simply by limiting $i_c(t)$
 - It is always necessary to sense the transistor current, to protect against overcurrent failures
 - Transformer saturation problems in bridge or push-pull converters can be mitigated
- A disadvantage: susceptibility to noise

A Simple First-Order Model

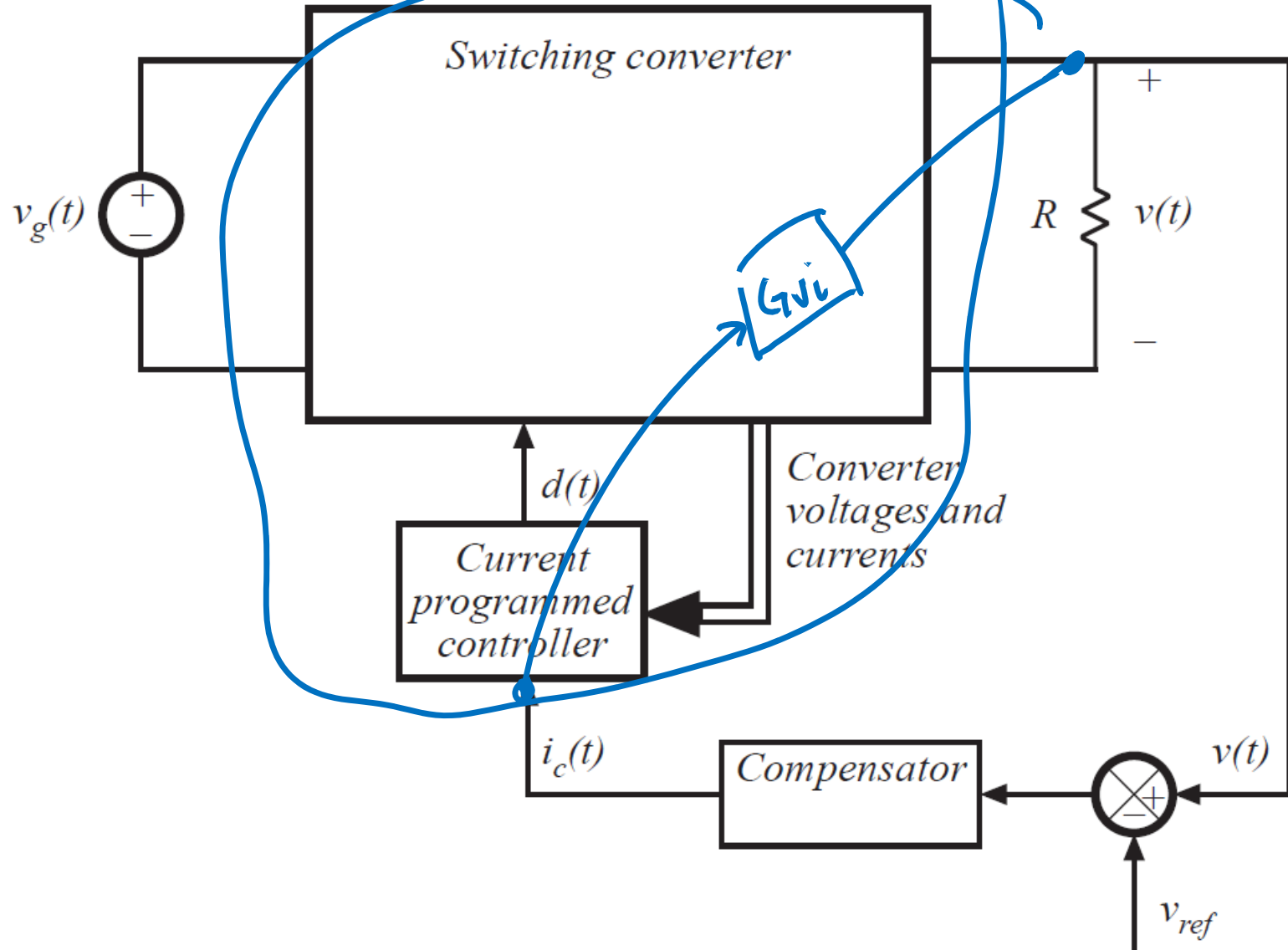


The First-Order Approximation

$$\langle i_L(t) \rangle_{T_s} = i_c(t)$$

- Neglects switching ripple
- Yields physical insight and simple first-order model
- Accurate when converter operates well into CCM (so that switching ripple is small)
- Accurate when artificial ramp (discussed later) is small
- Resulting small-signal relation:


$$i_L(s) \approx i_c(s)$$

Averaged Modeling

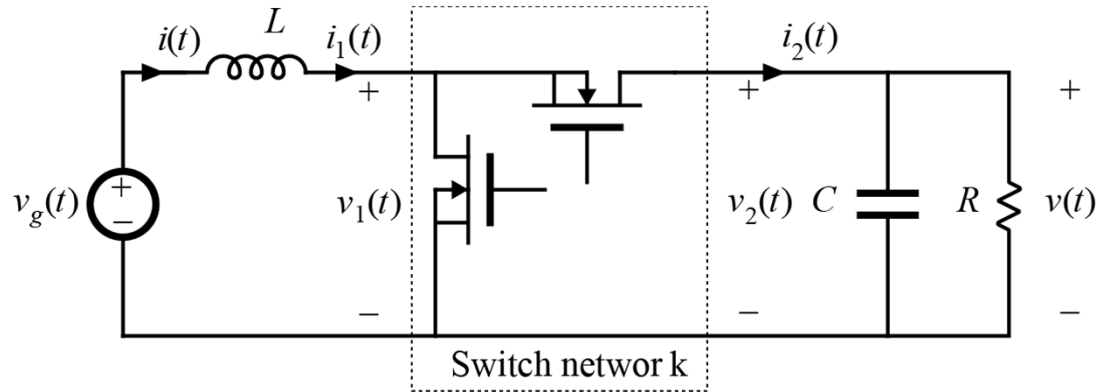


$\uparrow i_c = i_{ref}$



if CPM is ideal $i_c = i_c$

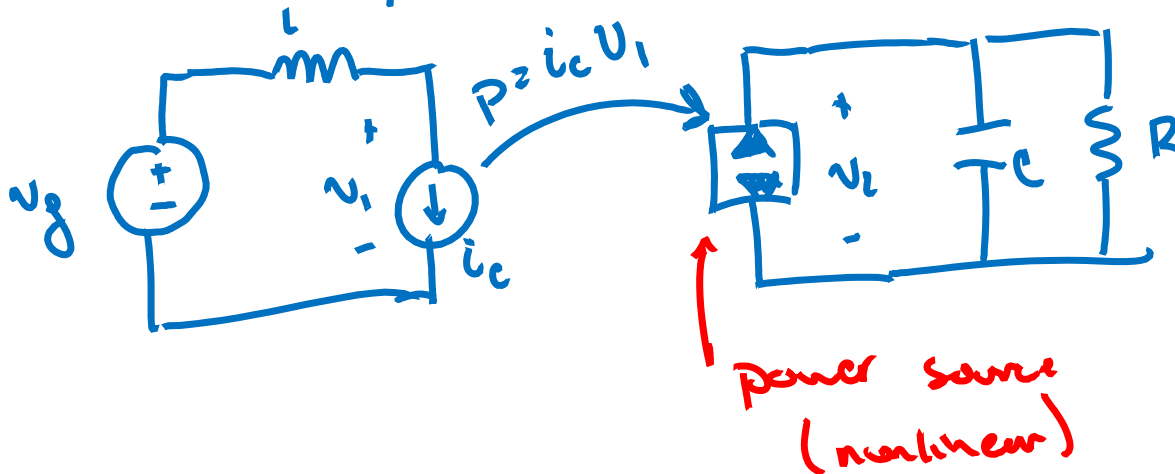


Large-Signal Nonlinear Model

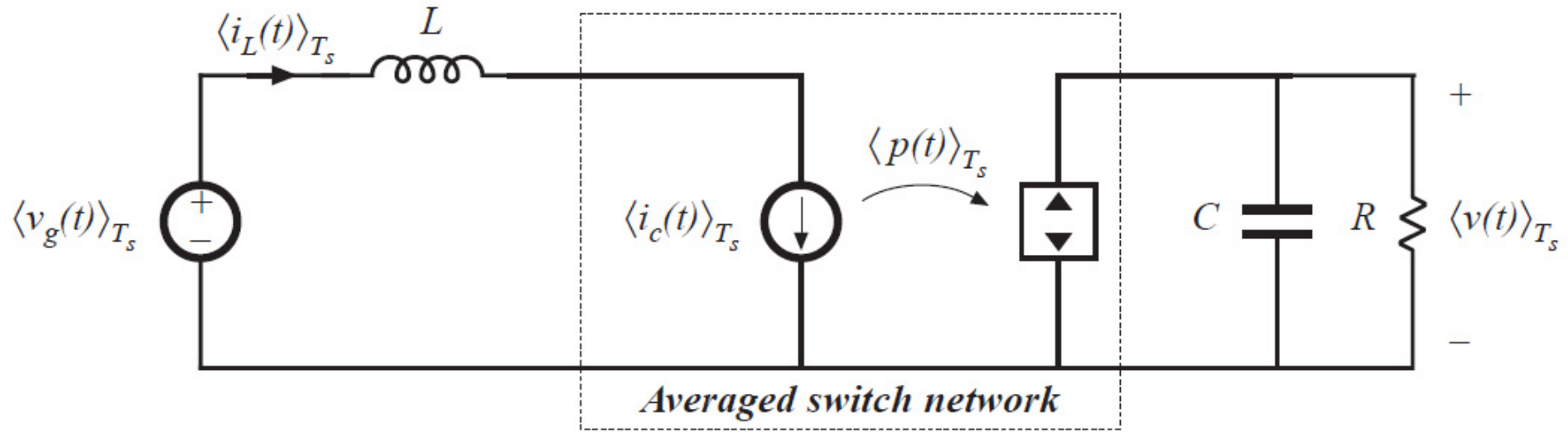

Implementation in LTSpice

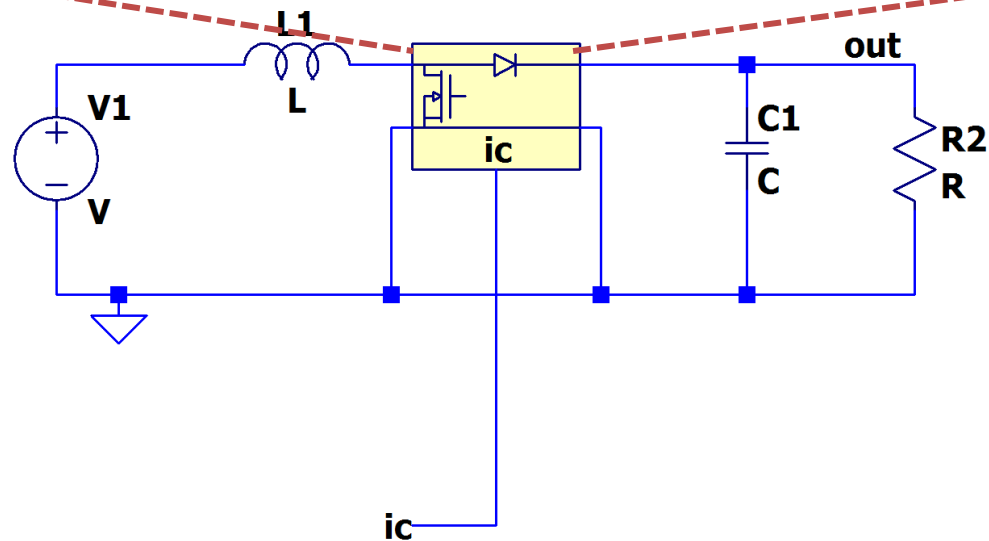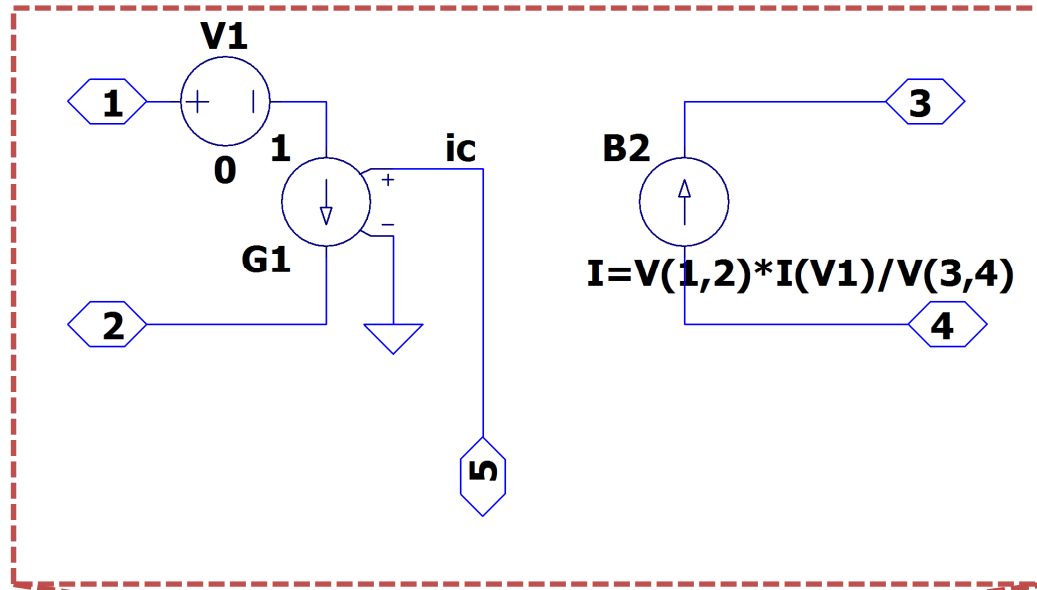

Averaged, Small-Signal Model

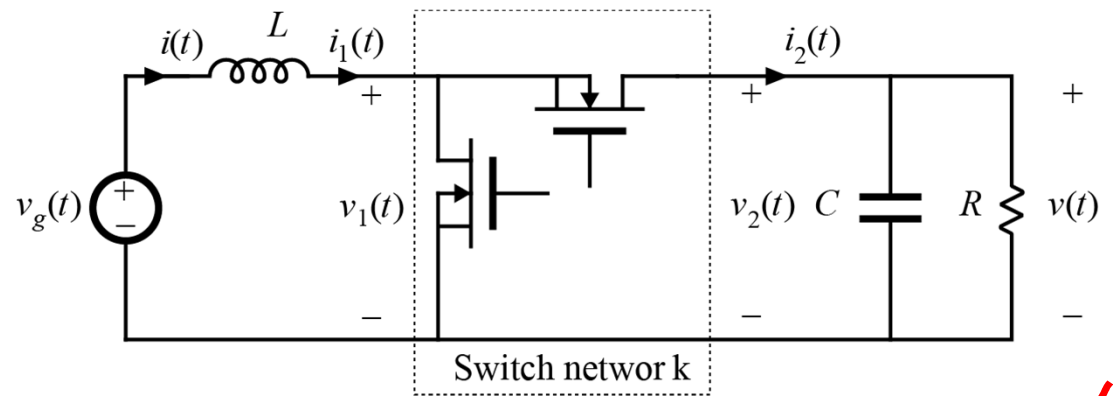

$$L \frac{d\langle i_L \rangle}{dt} = \langle v_g \rangle - d(t) \langle v \rangle$$

$$C \frac{d\langle v \rangle}{dt} = d(t) \langle i_L \rangle - \frac{\langle v \rangle}{R}$$

- Replace $i_L = i_c$ (assuming ideal CPM)

- Linearize in Laplace domain

$$sL \hat{i}_c = \hat{v}_g + v \hat{d} - D \hat{v}$$

$$sC \hat{v} = D \hat{i}_c - I_L \hat{d} - \frac{\hat{v}}{R}$$

- \hat{d} is no longer controlled \rightarrow eliminate


$$\hat{d} = \frac{1}{v} (sL \hat{i}_c - \hat{v}_g + D \hat{v})$$

$$sC\hat{v} = D' \hat{i}_c - \frac{\hat{v}}{R} - \frac{I_c}{V} (sL\hat{i}_c - \hat{v}_y - D\hat{v})$$


$$sC\hat{v} = \hat{i}_c \left(D' - \frac{I_c}{V} sL \right) + \hat{v}_y \frac{I_c}{V} - \frac{\hat{v}}{R} - \frac{I_c}{V} D\hat{v}$$

$$I_{out} = D'I_c \rightarrow \frac{I_c}{V} = \frac{D'I_{out}}{V} = \frac{R}{D'}$$
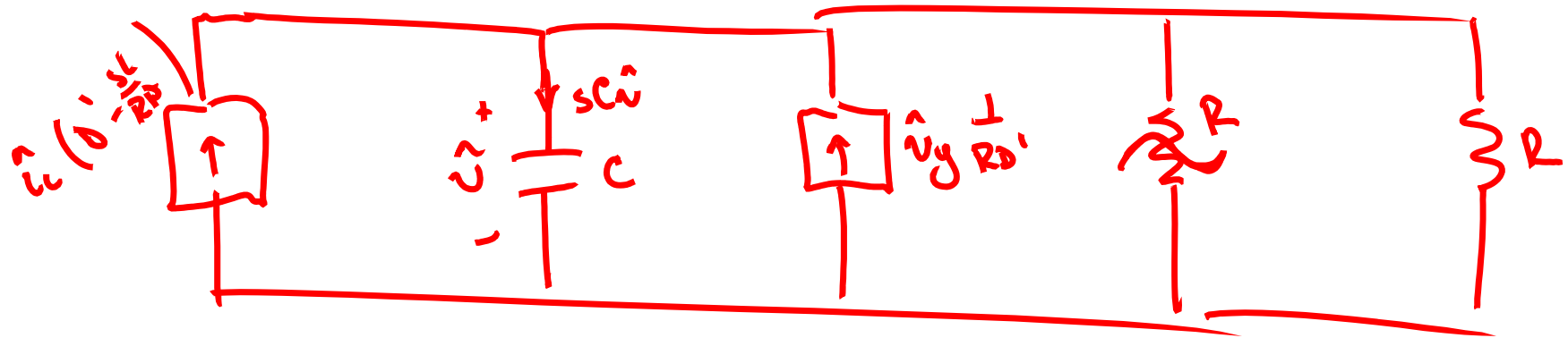
$$sC\hat{v} = \hat{i}_c \left(D' - \frac{sL}{RD'} \right) + \hat{v}_y \frac{1}{RD'} - \frac{\hat{v}}{R} - \frac{R}{D'} \hat{v}$$



Boost CCM CPM Small-Signal Model

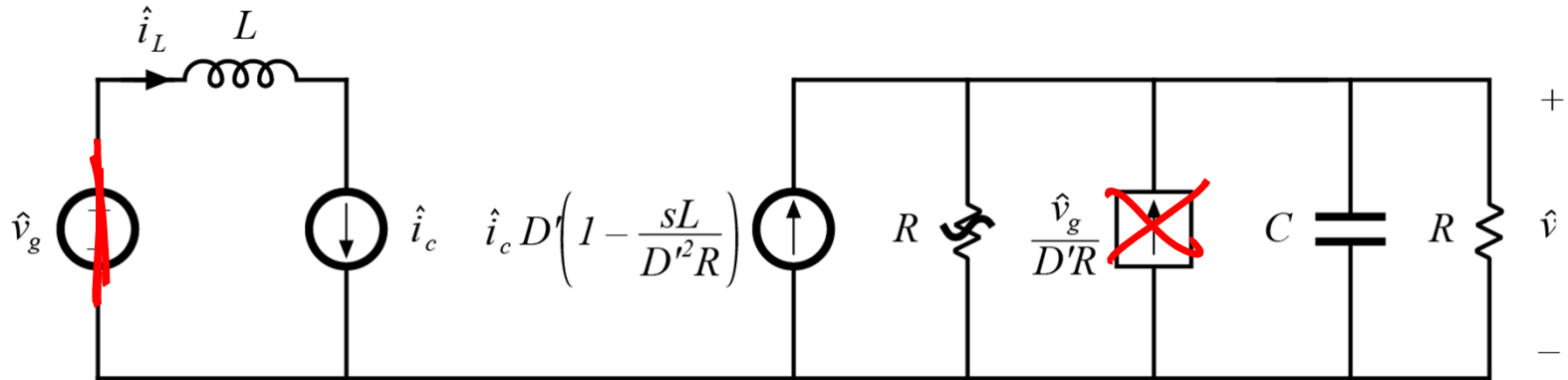

for PWM control

$G_{vd} = \frac{V}{D}$

$G_{vi} = \frac{\hat{v}_g}{\hat{i}_c} \Big|_{DC \text{ op point } \hat{v}_g = \hat{i}_c = 0}$

$\frac{(1 - \frac{sL}{D^2 R})}{1 + \frac{sL}{D^2 R} + s^2 \frac{LC}{D^2 R}}$

$$= D' \left(1 - \frac{sL}{D'^2 R} \right) \cdot \left(R \parallel R \parallel \frac{1}{sC} \right)$$

$$G_{vi} = \frac{D'R}{2} \frac{\left(1 - \frac{sL}{D'^2 R} \right)}{1 + s \frac{RC}{2}}$$

$\frac{1}{\frac{R}{2} + sC}$

Same RHP zero as in G_{vd}

single pole!!

CPM Transfer Functions



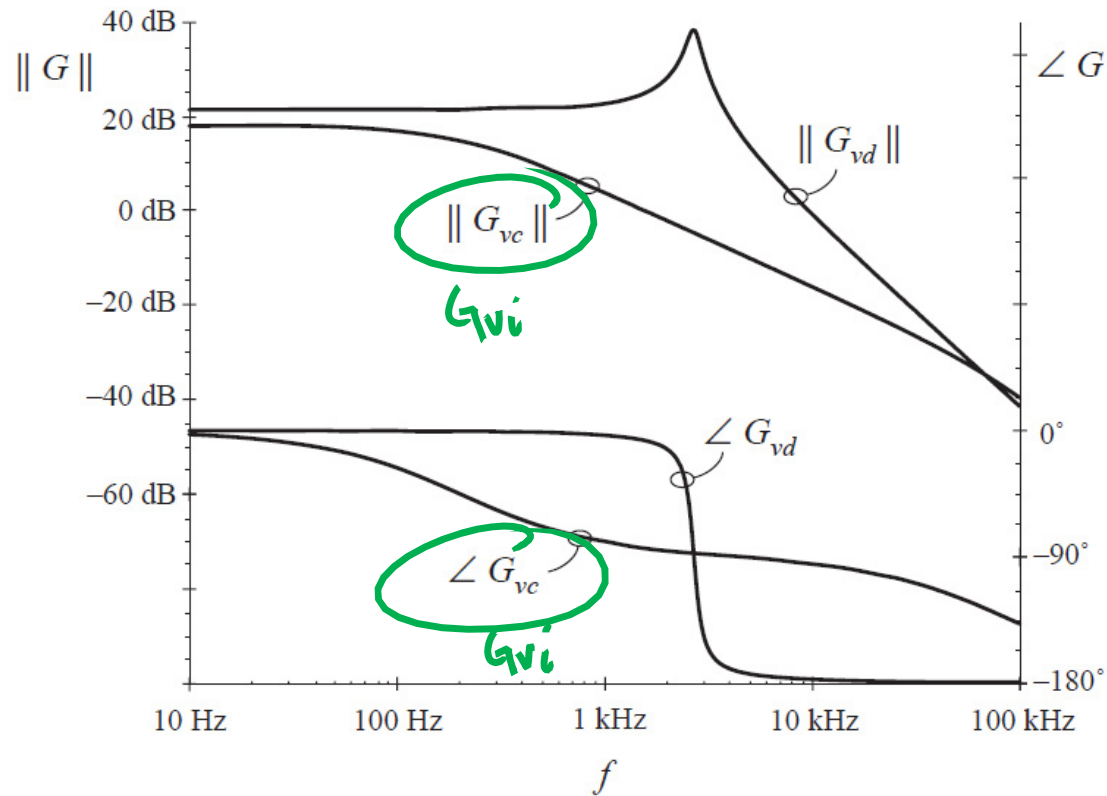


Fig. 12.28 Comparison of CPM control with duty-cycle control, for the control-to-output frequency response of the buck converter example.

Voltage Control

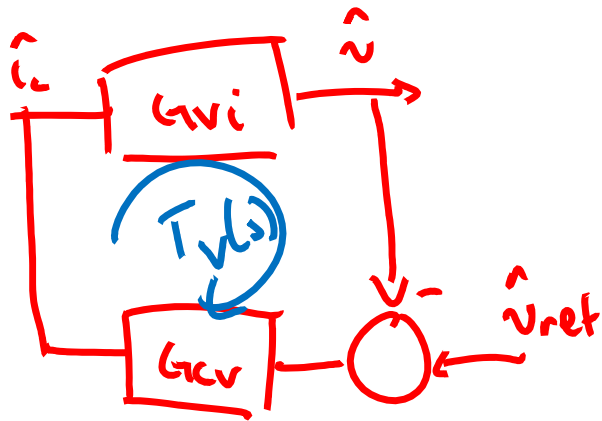

• Reminder: this neglects R_f & H

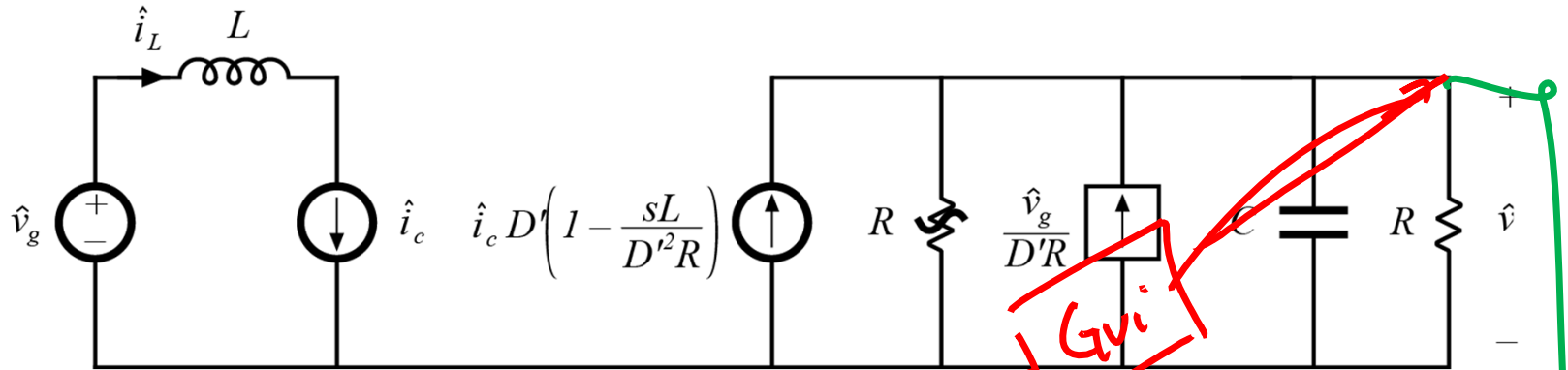