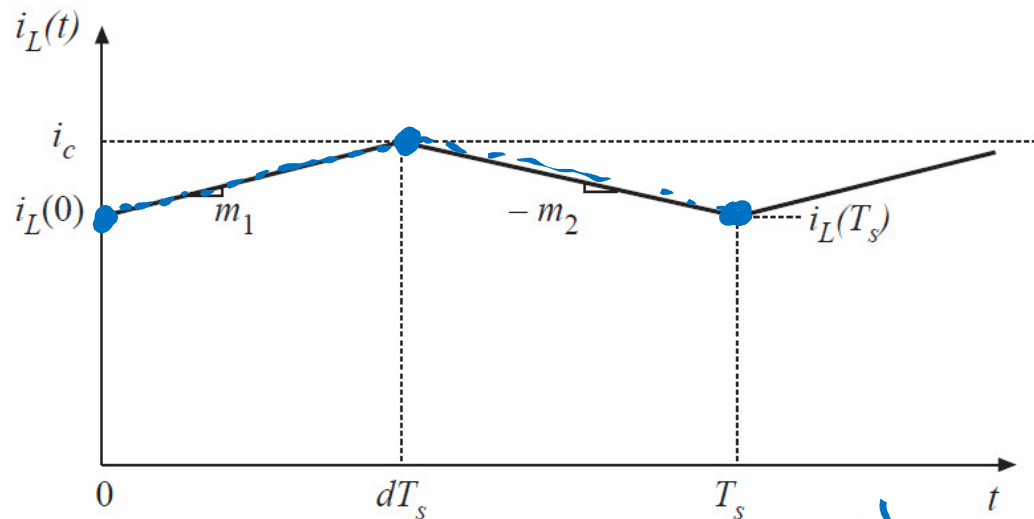


# CPM Oscillations for $D > 0.5$

- The current programmed controller is inherently unstable for  $D > 0.5$ , regardless of the converter topology
- Controller can be stabilized by addition of an artificial ramp

# Inductor Current Waveform in CCM

In steady-state  
 $i_L(0) = i_L(T_s)$



$i_L(T_s) = i_L(0) + m_1 dT_s - m_2 d'T_s$   
 in steady-state

$\Delta = m_1 dT_s - m_2 d'T_s$

$$\frac{\Delta}{m_1} = \frac{\Delta}{D}$$

Inductor current slopes  $m_1$   
 and  $-m_2$

buck converter

$$m_1 = \frac{v_g - v}{L} \quad -m_2 = -\frac{v}{L}$$


boost converter

$$m_1 = \frac{v_g}{L} \quad -m_2 = \frac{v_g - v}{L}$$


buck-boost converter

$$m_1 = \frac{v_g}{L} \quad -m_2 = \frac{v}{L}$$

# Introducing a Perturbation

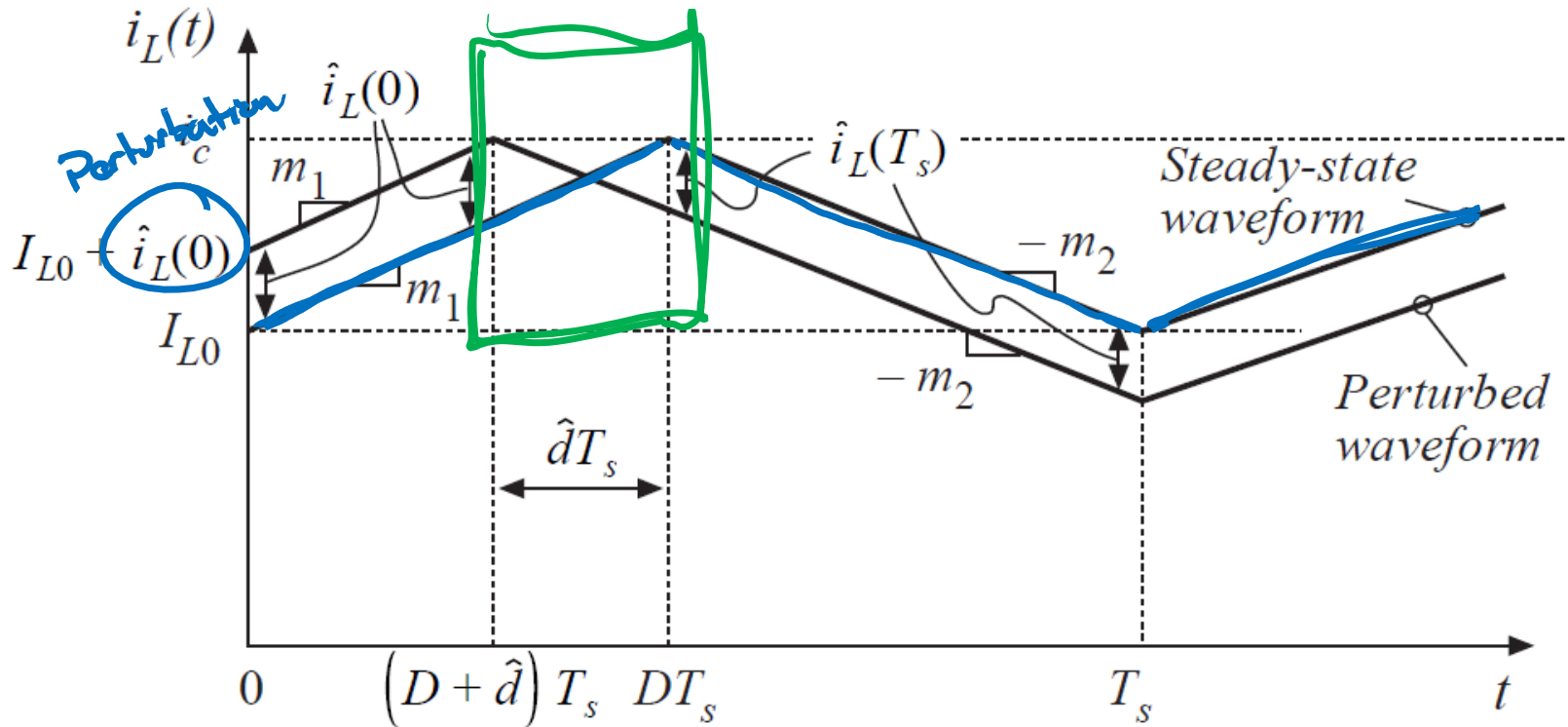

# Change in Inductor Current Over $T_s$

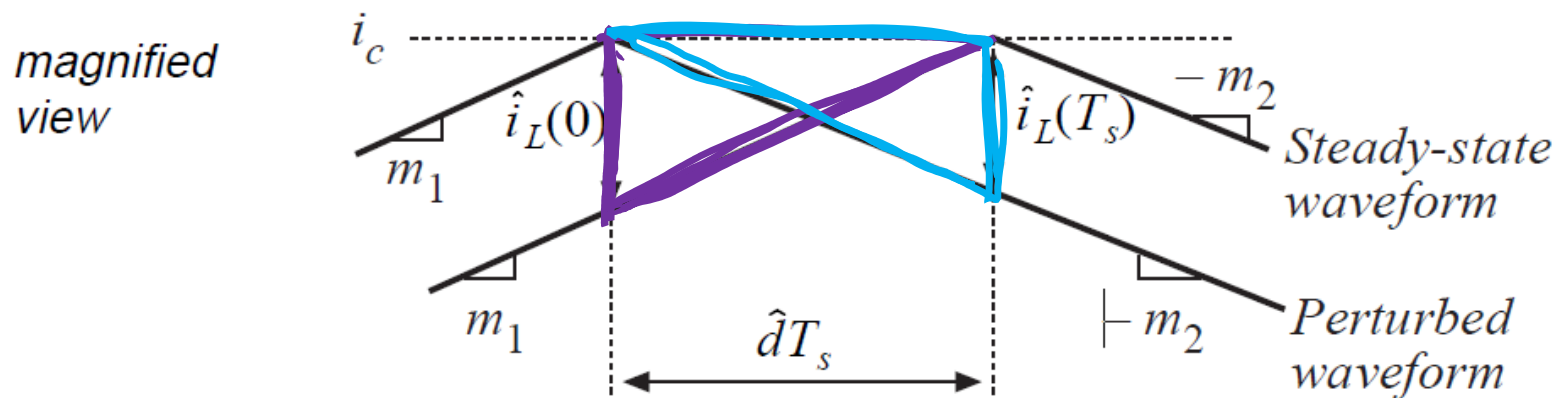

$$\hat{i}_L(0) = m_1 \hat{\Delta T}_s$$

$$\hat{i}_L(T_s) = -m_2 \hat{\Delta T}_s$$

$$\hat{i}_L(T_s) = \hat{i}_L(0) \left( \frac{-m_2}{m_1} \right)$$

$$\hat{i}_L(2T_s) = \hat{i}_L(T_s) \left( \frac{-m_2}{m_1} \right) = \hat{i}_L(0) \left( \frac{-m_2}{m_1} \right)^2$$


$$\hat{i}_L(nT_s) = \hat{i}_L(0) \left( \frac{-m_2}{m_1} \right)^n$$

$$\alpha = \frac{-m_2}{m_1} \ll 0$$

need  $|\alpha| < 1$  for stability

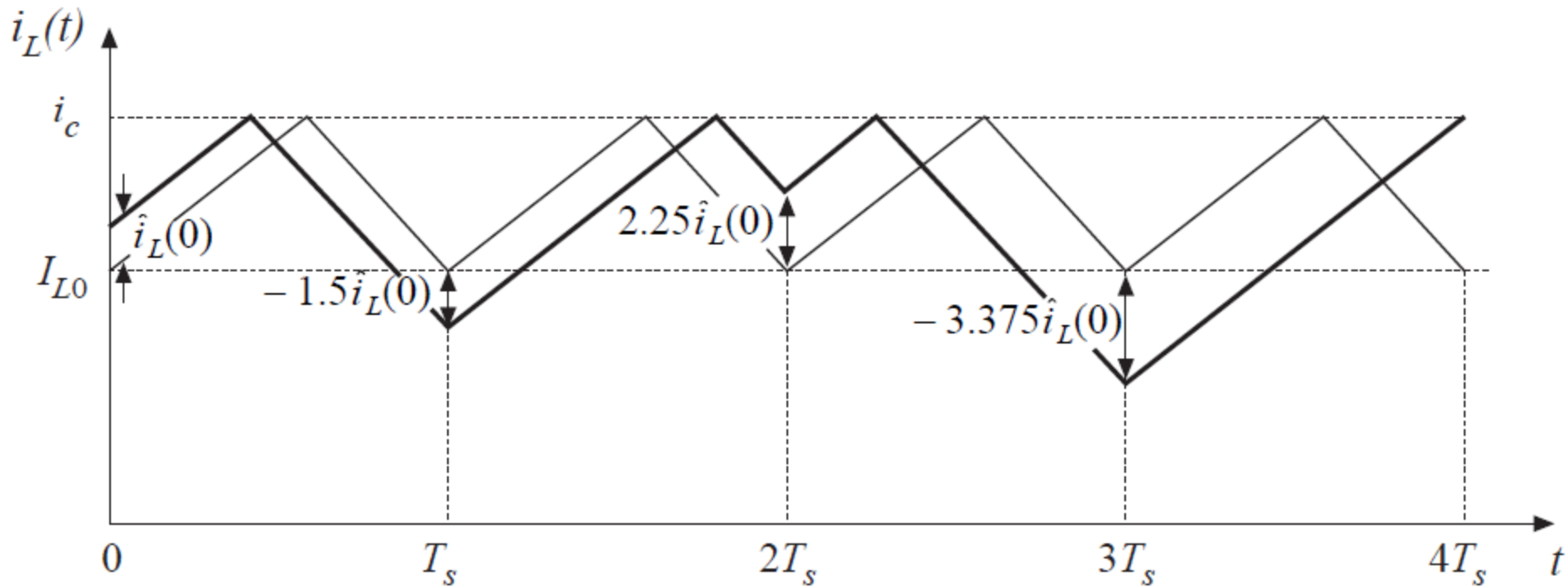
# Example: Unstable operation for $D=0.6$

$$\alpha = -\frac{D}{D'} = \left(-\frac{0.6}{0.4}\right) = -1.5$$




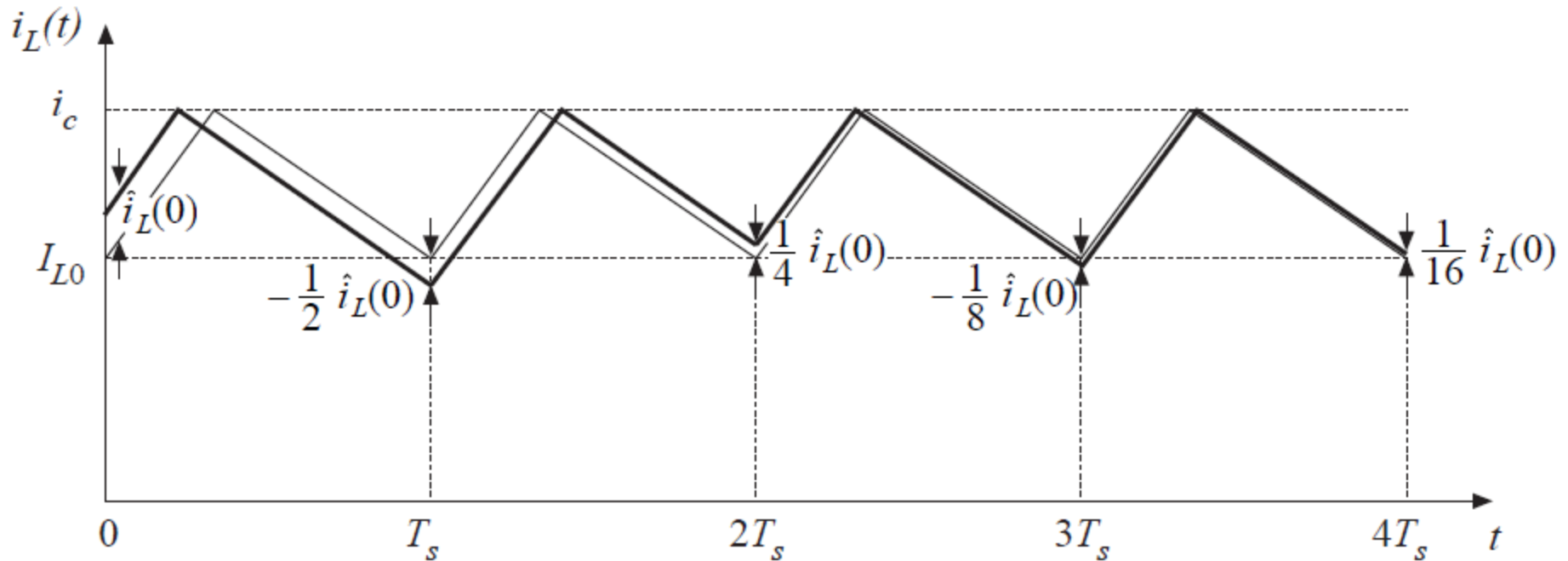
# Example: Stable operation for $D=1/3$

$$\alpha = -\frac{D}{D'} = \left(-\frac{1/3}{2/3}\right) = -0.5$$



# Stabilization Through Artificial Ramp

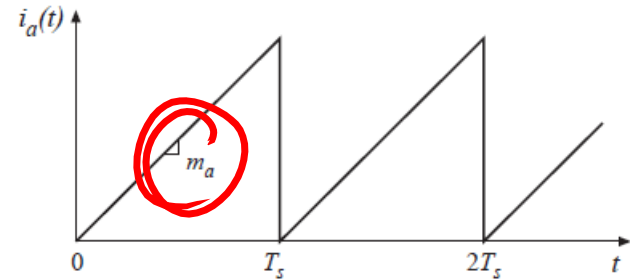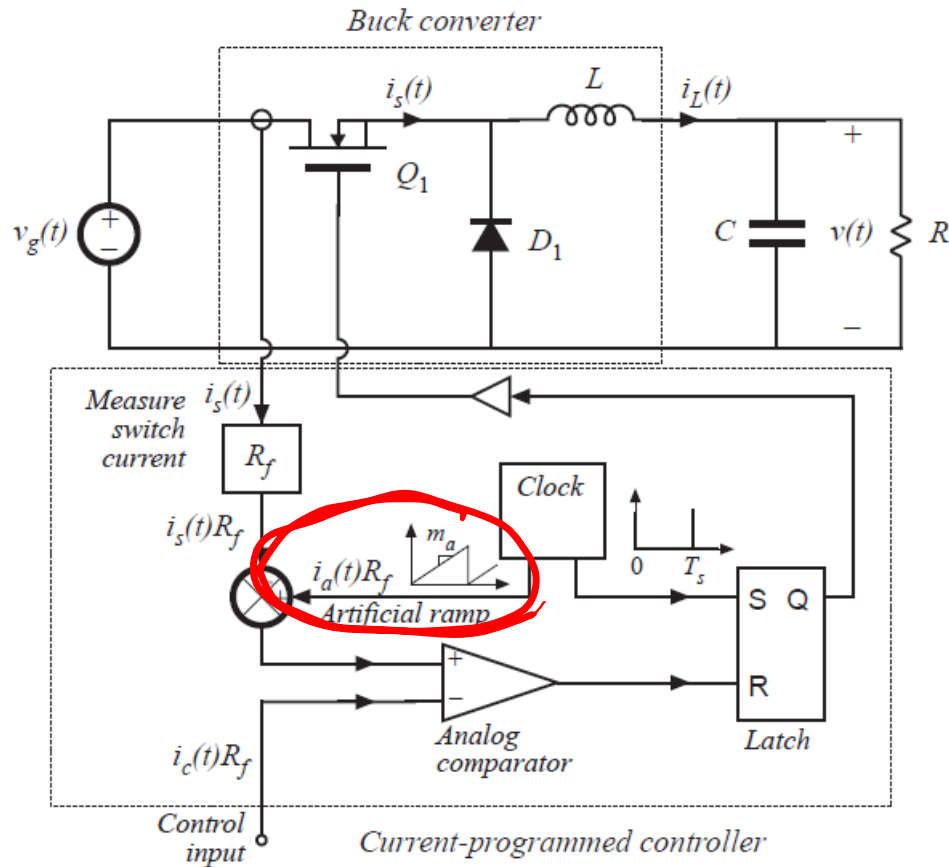

Now, transistor switches off when

$$i_a(dT_s) + i_L(dT_s) = i_c$$

or,

$$i_L(dT_s) = i_c - i_a(dT_s)$$

if  $i_a \gg i_c \rightarrow$  PWM control  
 if  $i_a \ll i_c \rightarrow$  CPM

# Final Value of Inductor Current

First subinterval:

$$\hat{i}_L(0) = -\hat{d}T_s (m_1 - m_a)$$

Second subinterval:

$$\hat{i}_L(T_s) = -\hat{d}T_s (m_a - m_2)$$

Net change over one switching period:

$$\hat{i}_L(T_s) = \hat{i}_L(0) \left( -\frac{m_2 - m_a}{m_1 + m_a} \right)$$

After  $n$  switching periods:

$$\hat{i}_L(nT_s) = \hat{i}_L((n-1)T_s) \left( -\frac{m_2 - m_a}{m_1 + m_a} \right) = \hat{i}_L(0) \left( -\frac{m_2 - m_a}{m_1 + m_a} \right)^n = \hat{i}_L(0) \alpha^n$$

Characteristic value:

$$\alpha = -\frac{m_2 - m_a}{m_1 + m_a}$$


$$|\hat{i}_L(nT_s)| \rightarrow \begin{cases} 0 & \text{when } |\alpha| < 1 \\ \infty & \text{when } |\alpha| > 1 \end{cases}$$



# Artificial Ramp: Additional Notes

- For stability, require  $|\alpha| < 1$
- Common choices:
  - $m_a = 0.5 m_2$  (stable for all duty cycles)
  - $m_a = m_2$  (deadbeat)
- Artificial ramp decreases sensitivity to noise
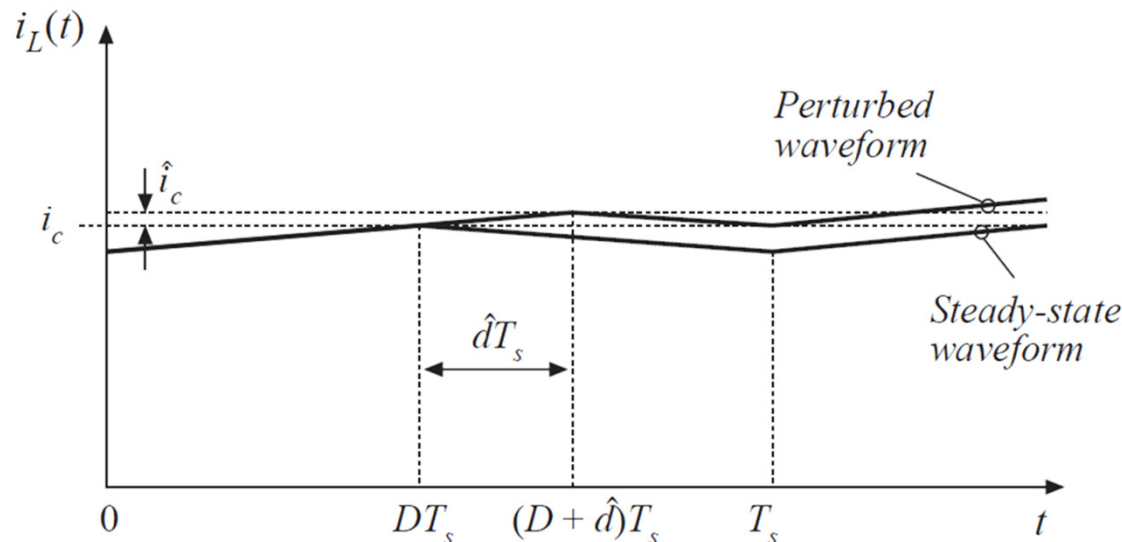
$$\alpha = - \frac{1 - \frac{m_a}{m_2}}{\frac{D'}{D} + \frac{m_a}{m_2}}$$



# More Accurate Models

- The simple models of the previous section yield insight into the low-frequency behavior of CPM converters
- Unfortunately, they do not always predict everything that we need to know:
  - Line-to-output transfer function of the buck converter
  - Dynamics at frequencies approaching  $f_s$
- More accurate model accounts for nonideal operation of current mode controller built-in feedback loop
- Converter duty-cycle-controlled model, plus block diagram that accurately models equations of current mode controller
- See Section 12.3 for additional info

# More Accurate Model

- Simple model assumes  $i_L = i_C$  always
- Accounting for ripple, and artificial ramp weakens this approximation
- Using sampled data modeling

$$\frac{\hat{i}_L}{\hat{i}_C} = \frac{1}{1 + \frac{1}{Q_s} \left( \frac{s}{2\pi f_s/2} \right) + \left( \frac{s}{2\pi f_s/2} \right)^2}$$

Where

$$Q_s = \frac{2}{\pi \left( \frac{2}{1-\alpha} - 1 \right)}$$

*if my bandwidth  
of voltage loop is  
well below  $f_s/2$   
then  $i_L \approx i_C$   
applies*

# Note: Comparison to Datasheet

## Application Information (continued)

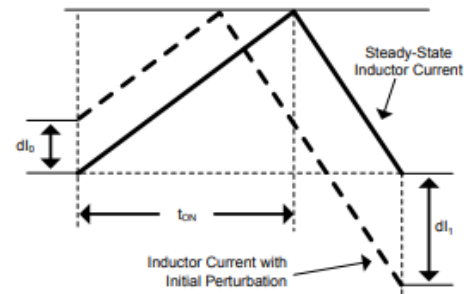


Figure 30. Effect of Initial Perturbation when  $dl_1/dl_0 < -1$

$dl_1/dl_0$  can be calculated as:

$$\frac{dl_1}{dl_0} = 1 - \frac{1}{K}$$

$$\alpha = 1 - \frac{1}{K}$$

The relationship between  $dl_1/dl_0$  and K factor is illustrated in the graphic below.

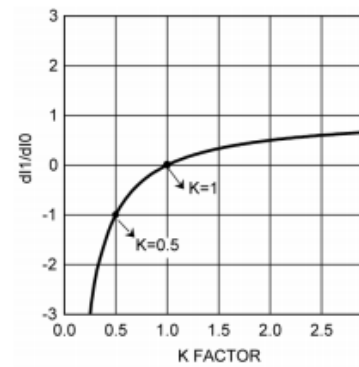


Figure 31.  $dl_1/dl_0$  vs K Factor

The absolute minimum value of K is 0.5. When  $K < 0.5$ , the amplitude of  $dl_1$  is greater than the amplitude of  $dl_0$  and any initial perturbation results in sub-harmonic oscillation. If  $K = 1$ , any initial perturbation will be removed in one switching cycle. This is known as one-cycle damping. When  $-1 < dl_1/dl_0 < 0$ , any initial perturbation will be under-damped. Any perturbation will be over-damped when  $0 < dl_1/dl_0 < 1$ .

(19)